



**BMS**

**INSTITUTE OF TECHNOLOGY AND MANAGEMENT**

Avalahalli, Doddaballapur Main Road, Bengaluru – 560064

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

**NETWORK THEORY**

**18EC32**

**STUDY MATERIAL**

**III SEMESTER**

<b>Content</b>	<b>Page No.</b>
Module 1: BASIC CONCEPTS	2-107
Module 2: NETWORK THEOREMS	108-176
Module 3: TRANSIENT BEHAVIOUR AND INITIAL CONDITIONS	177-200
Module 4: LAPLACE TRANSFORM AND ITS APPLICATIONS	201-250
Module 5: TWOPORT NETWORK, RESONANCE CIRCUITS	251-370

Dept. ECE., BMSIT&M

# **NETWORK ANALYSIS (18EC32)**

## **Syllabus:-**

### **Module -1**

**Basic Concepts:** Practical sources, Source transformations, Network reduction using Star – Delta transformation, Loop and node analysis With linearly dependent and independent sources for DC and AC networks, Concepts of super node and super mesh.

### **Text Books:**

1. M.E. Van Valkenberg (2000), “Network analysis”, Prentice Hall of India, 3<sup>rd</sup> edition, 2000, ISBN: 9780136110958.
2. Roy Choudhury, “Networks and systems”, 2nd edition, New Age International Publications, 2006, ISBN: 9788122427677.

### **Reference Books:**

1. Hayt, Kemmerly and Durbin “Engineering Circuit Analysis”, TMH 7th Edition, 2010.
2. J. David Irwin /R. Mark Nelms, “Basic Engineering Circuit Analysis”, John Wiley, 8th edition, 2006.
3. Charles K Alexander and Mathew N O Sadiku, “Fundamentals of Electric Circuits”, Tata McGraw-Hill, 3rd Ed, 2009.

Theory Questions.

Q1) Explain.

1. Unilateral and Bilateral elements
2. Independent and dependent Sources.
3. Linear and Non-linear.
4. Active and passive elements
5. Lumped and distributed.
6. Ideal and practical Sources.


JTS 2014 (6m)

Dec 2012 (8m)

Soln: 1. Unilateral and Bilateral elements


Unilateral -  $V-I$  characteristic is to be altered when the direction of current is to be changed.

Ex: diode, Transistor.

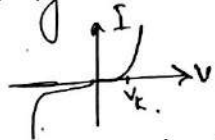

Bilateral -  $V-I$  characteristics remain same irrespective of current direction. When element properties and characteristics are dependent on the direction of current then the element is called Unidirectional or Unilateral element.

Ex: Resistor, Capacitor, Inductor.

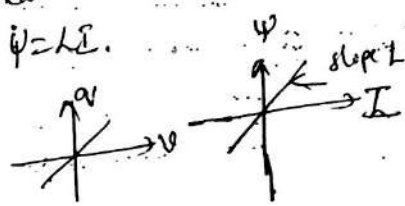

An element is to be bilateral if it has same impedance for both directions of current flow otherwise it is said to be Unilateral.

When element properties and characteristics are independent on the direction of the current then the element is called as directional or bilateral element.

Independent and Dependent Sources

Dependent Sources

\* The strength of dependent sources depends on one of the circuit parameters of the circuit in which it is connected.

Ex: (CCCS)

1. Current Controlled Current Source (BJT)

$I_c = \beta I_B$



2. Voltage Controlled Current Source (VCCS)

→ FET  
 $I_D = f_u(V_D)$



3. Voltage controlled voltage source (VCVS) (opamp)

(opamp)




4. Current Controlled voltage source (CCVS) (CFO)



Independent Sources

\* The strength of independent sources does not depend on the any of the circuit parameters.

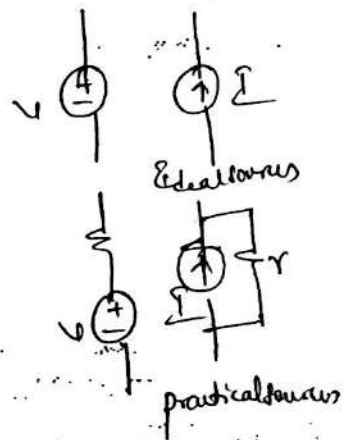Ex: ideal practical voltage & current sources.



### 3. Linear and Non-linear elements

Linear: A two terminal element is said to be linear if for all time  $t$  its characteristics is straight line through the origin otherwise it is said to be non-linear.

⊗ elements which obey Ohm's law.

⊗ Elements which obey the principle of Superposition (additivity and homogeneity rule).

Ex: R, L, C.

Non-linear: A two terminal element is said to be non-linear if for all time  $t$  its characteristics is not a straight line that passes through origin.

⊗ Don't obey Ohm's Law.

⊗ fails to obey the principle of Superposition.

Ex: Diode, transistor, transformer etc, Independent Voltage & Current Sources.


### 4. Active (or) Power element's

Active element: An element incapable of delivering energy independently for infinite time.

⊗ An element having property of internal amplification.

⊗ Signal rectification then the element is called as active element.

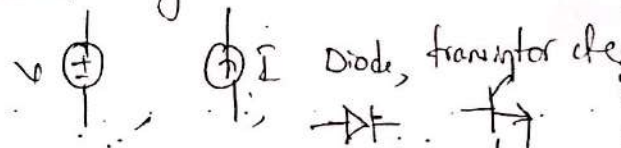Ex: Independent voltage and current sources.



Power element: An element which is not capable of delivering energy.

⊗ not capable to do signal amplification.

⊗ rectification then it is called as power element.

Ex: R, L, C, bulb, transformer etc.

### 5. Lumped & Distributed element's

Lumped element's

⊗ Ohm's law can be applied for lumped (linear) element's.

⊗ R, L, and C can be separable.

⊗ In lumped element's  $\lambda \gg l$ .

Ex: R, L, C.

Distributed element's

⊗ KVL and KCL fail's for distributed parameter since in distributed parameter electrically, it is not possible to separate resistance, Inductance, and capacitance effect.

⊗ but Ohm's law can be applied for lumped and distributed parameter's. Ex: Co-axial cable, Transmission etc.


## Time-Varying and Time-Invariant Elements

→ An element is said to be time-invariant if all time its characteristics do not change with time, otherwise it is said to be time-varying.

Ex: R, L, C ← Time Invariant elements.

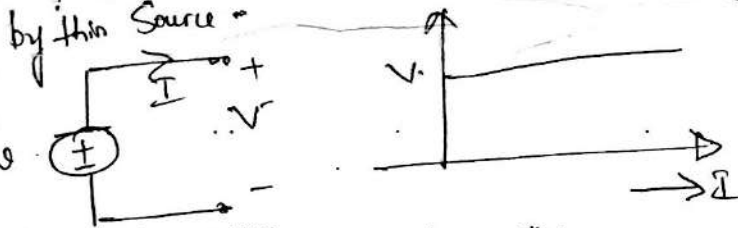
## Ideal and Practical Sources

→ Ideal voltage source: Ideal voltage source delivers energy at the specified voltage ( $V$ ), which is independent on current delivered by this source.



$R_s = 0$   
→ Practical voltage source:

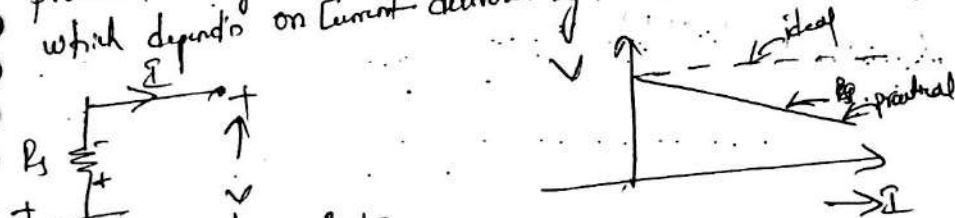Practical voltage source delivers energy at specified voltage ( $V$ ) which depends on current delivered by the source.




$$V_s - I R_s - V = 0 \Rightarrow V = V_s - I R_s$$
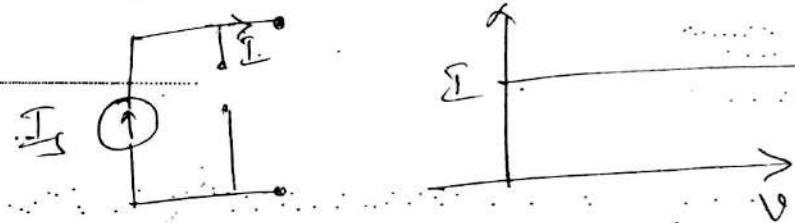
## → Ideal Current Source

Ideal current source delivers energy at specified current ( $I$ ) which is independent on voltage across the source.


Internal resistance of ideal current source =  $\infty$ .



$R_{int} = \infty \Omega$
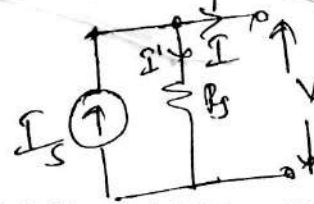
## → Practical Current Source

Practical current source delivers energy at specified current ( $I$ ) which depends on voltage across the source.



$$I_s = I' + I$$

$$I = I_s - I'$$

$$= I_s - \frac{V}{R_s}$$



### 3. Linear and Non-linear elements

Linear: A two terminal element is said to be linear if for all time  $t$  its characteristics is straight line through the origin otherwise it is said to be non-linear.

⊗ elements which obey Ohm's law.

⊗ Elements which obey the principle of Superposition (additivity and homogeneity rule).

Ex: R, L, C.

Non-linear: A two terminal element is said to be non-linear if for all time  $t$  its characteristics is not a straight line that passes through origin.

⊗ Doesn't obey Ohm's Law.


⊗ fails to obey the principle of Superposition.

Ex: Diode, transistor, transformer etc, <sup>Independent Voltage & Current Sources.</sup>
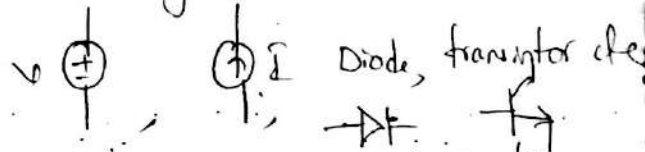
### 4. Active ⊗ or passive elements

Active element: An element incapable of delivering energy independently for infinite time ⊗ when the element is having property of internal amplification ⊗ signal rectification then the element is called as active element.

EX: Independent voltage and current sources



⊗ element which are not capable of delivering energy ⊗ not capable to do signal amplification ⊗ rectification then it is called as passive elements.

Ex: R, L, C, bulb, transformer etc.

### 5. Lumped & Distributed elements

Lumped elements:

⊗ Ohm's law can be applied for lumped (linear) elements.

⊗ R, L, and C can be separable.

⊗ In lumped elements  $\lambda \gg l$ .

Ex: R, L, C.


Distributed elements:

⊗ KVL and KCL fail for distributed parameters. Since in distributed parameters electrically, it is not possible to separate resistance, Inductance, and capacitance effect.

⊗ but Ohm's law can be applied for lumped and distributed parameters. Ex: Coaxial cable, Transmission etc.



# Star to Delta transformation

\* New reduction tool.

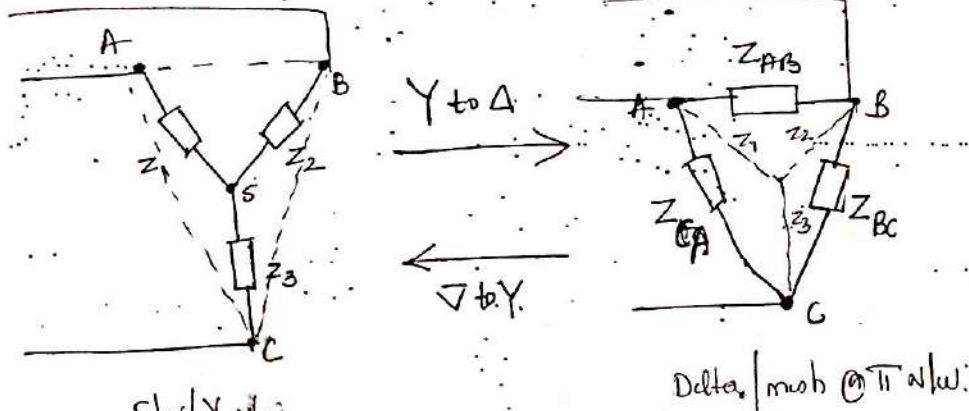

Star/Y New

Delta/mesh @ TI New

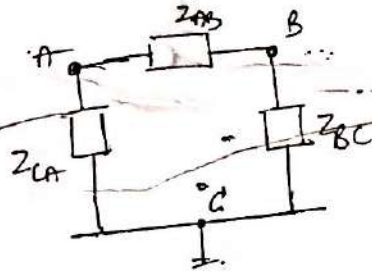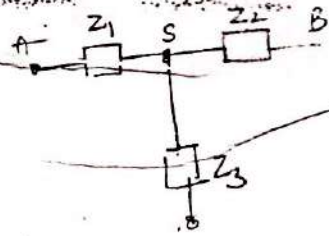

## a) Star to Delta Conversion

given  $Z_1, Z_2,$  and  $Z_3 \Rightarrow$  find  $Z_{AB}, Z_{CA}, Z_{BC}$ .

$$Z_{AB} = Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3}$$

$$= \frac{Z_1 Z_3 + Z_2 Z_3 + Z_1 Z_2}{Z_3} = \frac{\sum Z_1 Z_2}{Z_3}$$

$$\text{By } Z_{BC} = Z_2 + Z_3 + \frac{Z_2 Z_3}{Z_1}$$

$$= \frac{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}{Z_1} = \frac{\sum Z_1 Z_2}{Z_1}$$

and

$$Z_{CA} = Z_1 + Z_3 + \frac{Z_1 Z_3}{Z_2}$$

$$= \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_2} = \frac{\sum Z_1 Z_2}{Z_2}$$

Note: if  $Z_1 = Z_2 = Z_3 = R$  then


$$Z_{AB} = R + R + \frac{R \cdot R}{R} = 3R$$

$$\text{By } Z_{BC} = 3R \text{ and } Z_{CA} = 3R$$

In general  $Z_{\Delta} = 3 Z_Y$   $Z_Y = \frac{Z_{\Delta}}{3}$



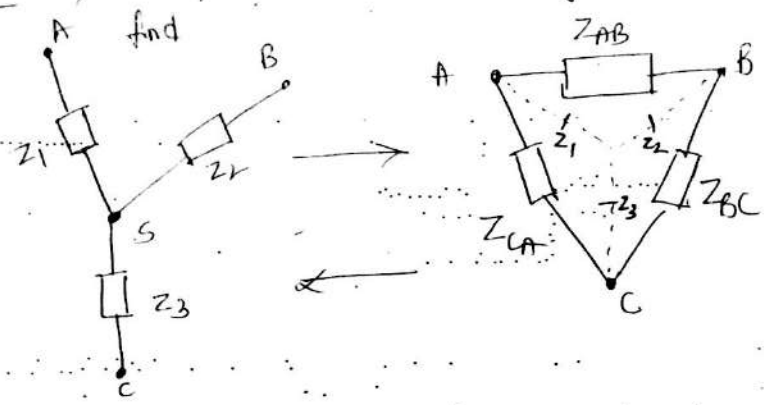Q.18  $\Delta \rightarrow$  Delta to star N/W



$$Z_1 = \frac{Z_{AB} \cdot Z_{CA}}{Z_{AB} + Z_{BC} + Z_{CA}} = \frac{Z_{AB} \cdot Z_{CA}}{\sum Z_{AB}}$$

$$Z_2 = \frac{Z_{AB} \cdot Z_{BC}}{Z_{AB} + Z_{BC} + Z_{CA}} = \frac{Z_{AB} \cdot Z_{BC}}{\sum Z_{AB}}$$

$$Z_3 = \frac{Z_{CA} \cdot Z_{BC}}{Z_{AB} + Z_{BC} + Z_{CA}} = \frac{Z_{BC} \cdot Z_{CA}}{\sum Z_{AB}}$$

Notes - If  $Z_{AB} = Z_{BC} = Z_{CA} = R \Omega$


then  $Z_1 = \frac{[R \cdot R]}{3R} = R/3 \Omega$

or  $Z_2 = R/3 \Omega$  and  $Z_3 = R/3 \Omega$

$\therefore$  In general  $Z_Y = \frac{Z_{\Delta}}{3} \Rightarrow \boxed{Z_Y = \frac{Z_{\Delta}}{3}} \Omega$   
 (1)  $\boxed{Z_{\Delta} = 3Z_Y}$

Example


(1) Given

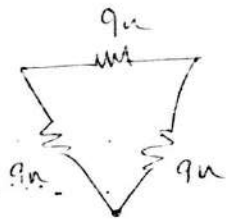

Convert it equivalent star N/W.

6


Sol.

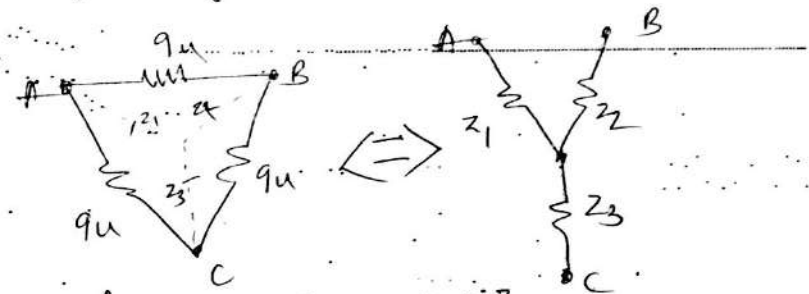

Ans.  $Z_{AB} = Z_{BC} = Z_{CA} = 9 \Omega = Z_{\Delta}$


$\therefore Z_Y = ? \quad \boxed{Z_Y = \frac{Z_{\Delta}}{3}}$

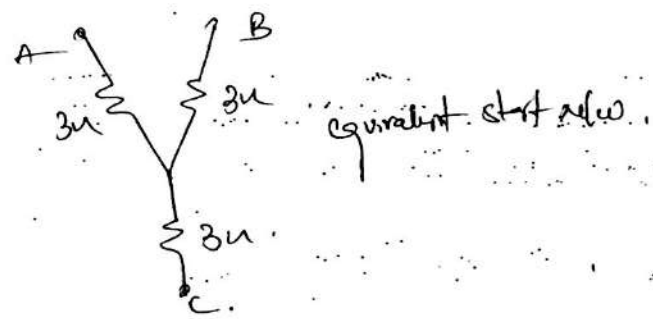or  $Z_Y = 9/3 = 3 \Omega = Z_1 = Z_2 = Z_3$




equivalent star N/W.

(2) given

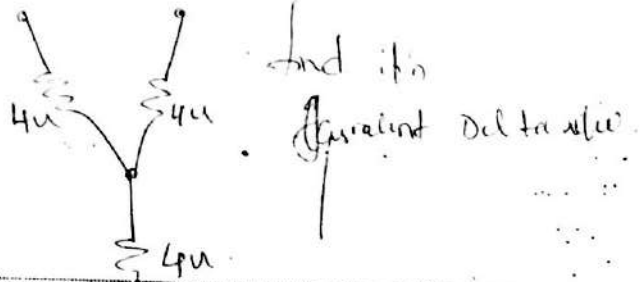


find its equivalent Delta network

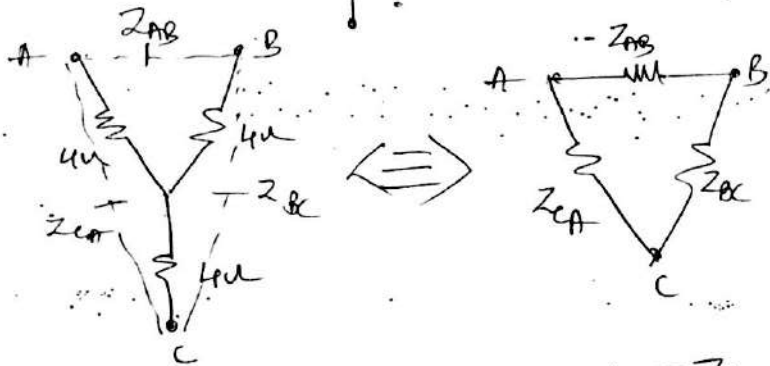

Since given  $Z_1 = Z_2 = Z_3 = 4 \Omega = Z_Y$   
 So that  $Z_Y = \frac{Z_\Delta}{3} \Rightarrow Z_\Delta = 3 Z_Y$


$Z_\Delta = 3(4) = 12 \Omega$

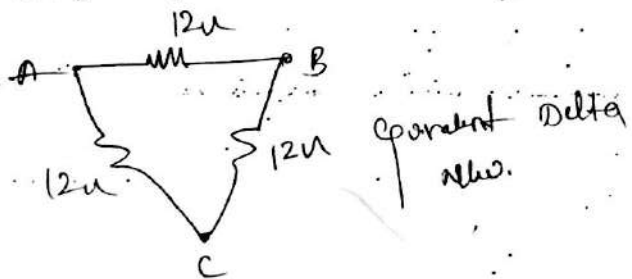

Equivalent Delta network

Note

(2)

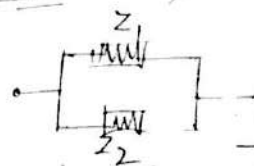


impedance  $(Z_1) \Omega$

Admittance  $Y_1 = \frac{1}{Z_1} \text{ v}$

$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2}$  ← impedance

$\Rightarrow Y_{eq} = Y_1 + Y_2$  ← admittance

(3)

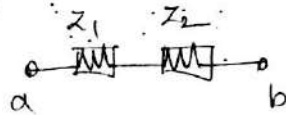

$Z_{ab} = Z_{eq} = Z_1 + Z_2 \Omega$


$Y_{ab} = \frac{1}{Z_{ab}} = \frac{1}{Z_1 + Z_2}$

$\Rightarrow Y_{ab} = \frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2}$

$\frac{1}{Y_{ab}} = \frac{Y_1 + Y_2}{Y_1 Y_2}$


$\Rightarrow Y_{ab} = Y_{eq} = \frac{Y_1 Y_2}{Y_1 + Y_2} \text{ v}$

Proof!  $\Delta$  to Y n/w

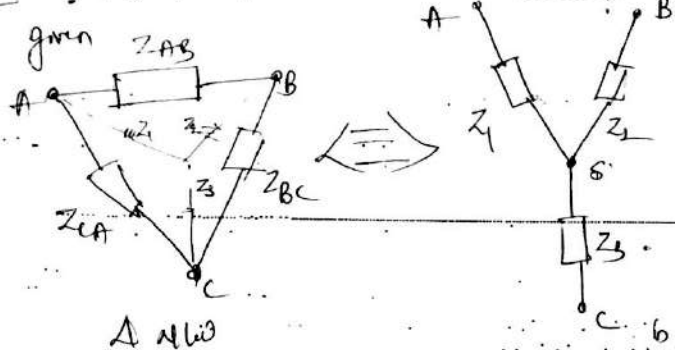


Equivalent impedance across terminals C-A with terminal B in open.
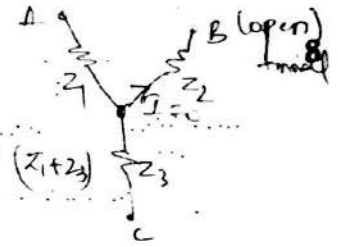
$$Z_1 + Z_3 = Z_{CA} \parallel (Z_{AB} + Z_{BC})$$



Equivalent impedance across terminals A-B with 'C' open

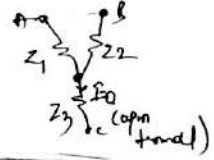
$$Z_1 + Z_2 = Z_{AB} \parallel (Z_{BC} + Z_{CA})$$



$$Z_1 + Z_2 = \frac{Z_{AB}(Z_{BC} + Z_{CA})}{Z_{AB} + Z_{BC} + Z_{CA}} \rightarrow (1)$$

Equivalent impedance across terminals B-C with terminal 'A' in open.
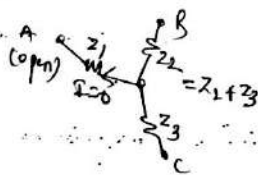
$$Z_2 + Z_3 = Z_{BC} \parallel (Z_{AB} + Z_{CA})$$



$$Z_2 + Z_3 = \frac{Z_{BC}(Z_{AB} + Z_{CA})}{Z_{AB} + Z_{BC} + Z_{CA}} \rightarrow (2)$$

$$Z_1 + Z_3 = \frac{Z_{CA}(Z_{AB} + Z_{BC})}{Z_{AB} + Z_{BC} + Z_{CA}} \rightarrow (3)$$

eq(1) - eq(2)

$$Z_1 + Z_2 - Z_2 - Z_3 = \frac{Z_{AB}(Z_{BC} + Z_{CA})}{Z_{AB} + Z_{BC} + Z_{CA}} - \frac{Z_{CA}(Z_{AB} + Z_{BC})}{Z_{AB} + Z_{BC} + Z_{CA}}$$

$$= \frac{Z_{AB}(Z_{BC} + Z_{CA}) - Z_{CA}(Z_{AB} + Z_{BC})}{Z_{AB} + Z_{BC} + Z_{CA}}$$

$$= \frac{Z_{AB}Z_{BC} + Z_{AB}Z_{CA} - Z_{CA}Z_{AB} - Z_{BC}Z_{CA}}{Z_{AB} + Z_{BC} + Z_{CA}}$$

$$= \frac{Z_{AB}Z_{BC} - Z_{BC}Z_{CA}}{Z_{AB} + Z_{BC} + Z_{CA}}$$

$$Z_1 - Z_3 = \frac{Z_{AB}Z_{CA} - Z_{BC}Z_{CA}}{Z_{AB} + Z_{BC} + Z_{CA}} \rightarrow (4)$$

eq(3) + eq(4)

$$Z_1 + Z_3 + Z_1 - Z_3 = \frac{Z_{CA}Z_{AB} + Z_{BC}Z_{CA} + Z_{AB}Z_{CA} - Z_{BC}Z_{CA}}{Z_{AB} + Z_{BC} + Z_{CA}}$$

$$Z_1 = \frac{Z_{AB} Z_{CA}}{Z_{AB} Z_{BC} + Z_{AB} Z_{CA} + Z_{BC} Z_{CA}}$$

$$Z_1 = \frac{Z_{AB} Z_{CA}}{\sum Z_{AB}}$$


we can simplify

$$Z_2 = \frac{Z_{AB} Z_{BC}}{\sum Z_{AB}}$$


and

$$Z_3 = \frac{Z_{BC} Z_{CA}}{\sum Z_{AB}}$$

Proof:  $Y$  to  $\Delta$  also

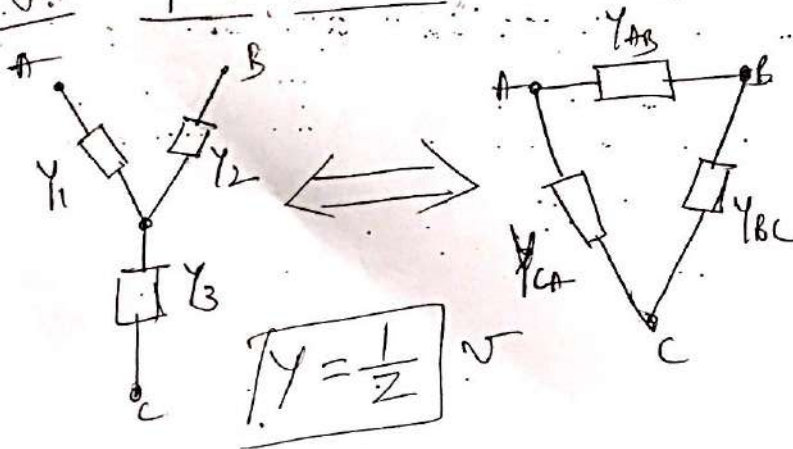

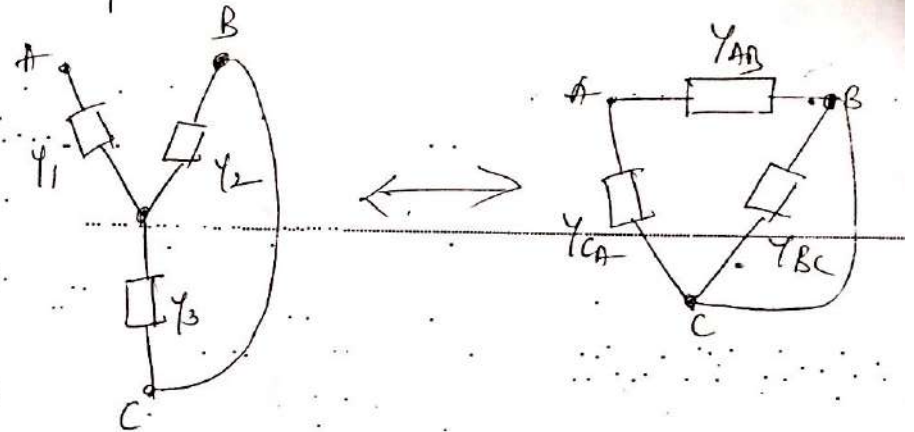
⇒ Equivalent admittance b/w AB with B shorted



$$Y_1 \parallel (Y_2 + Y_3) = Y_{AB} + Y_{CA}$$


$$\frac{Y_1(Y_2 + Y_3)}{Y_1 + Y_2 + Y_3} = Y_{AB} + Y_{CA} \rightarrow (1)$$

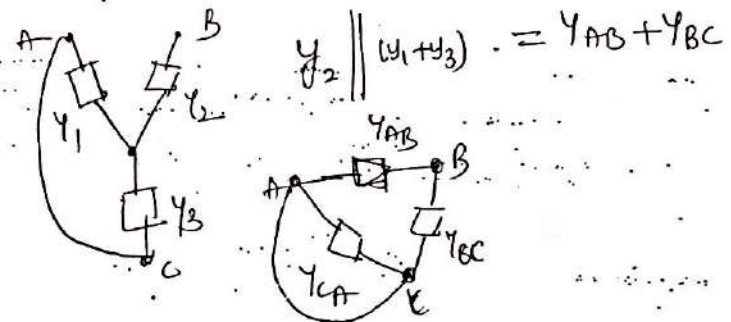⇒ Equivalent admittance b/w BC with C shorted to A.



$$\frac{Y_2(Y_1 + Y_3)}{Y_2 + Y_1 + Y_3} = Y_{AB} + Y_{BC} \rightarrow (2)$$

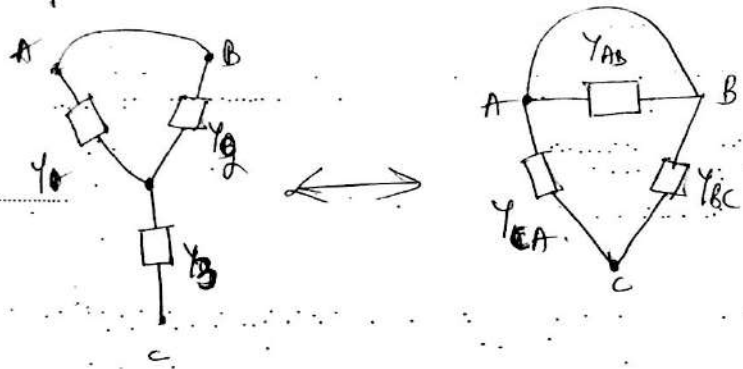equivalent admittance b/w CA with A shorted to B.



$$(Y_1 + Y_2) \parallel Y_3 = Y_{BC} + Y_{CA}$$

$$\frac{Y_3(Y_1 + Y_2)}{Y_1 + Y_2 + Y_3} = Y_{BC} + Y_{CA} \quad \text{--- (3)}$$

eq (1) - eq (2)

$$\frac{Y_1 Y_2 + Y_1 Y_3 - Y_2 Y_1 - Y_2 Y_3}{Y_1 + Y_2 + Y_3} = Y_{AB} + Y_{CA} - Y_{AB} - Y_{BC}$$

$$\frac{Y_1 Y_3 - Y_2 Y_3}{Y_1 + Y_2 + Y_3} = Y_{CA} - Y_{BC} \quad \text{--- (4)}$$

eq (3) + (4)

$$\frac{Y_1 Y_3 + Y_2 Y_3 + Y_1 Y_3 - Y_2 Y_3}{Y_1 + Y_2 + Y_3} = 2 Y_{CA}$$

$$\frac{Y_1 Y_3}{(Y_1 + Y_2 + Y_3)} = 2 Y_{CA}$$

$$\Rightarrow Y_{CA} = \frac{-Y_1 Y_3}{Y_1 + Y_2 + Y_3}$$

$$\frac{1}{Z_{CA}} = \frac{\frac{1}{Z_1 Z_3}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}} = \frac{1}{(Z_1 Z_3)} \times \frac{Z_1 Z_2 Z_3}{Z_2 Z_3 + Z_1 Z_3 + Z_1 Z_2}$$

$$\frac{1}{Z_{CA}} = \frac{Z_2}{Z_2 Z_3 + Z_1 Z_3 + Z_1 Z_2}$$

$$Z_{CA} = \frac{Z_2 Z_3 + Z_1 Z_3 + Z_1 Z_2}{Z_2} = \frac{\sum Z_1 Z_2}{Z_2}$$


we can solve

$$Z_{AB} = \frac{\sum Z_1 Z_2}{Z_3}$$


and

$$Z_{BC} = \frac{\sum Z_1 Z_2}{Z_1}$$

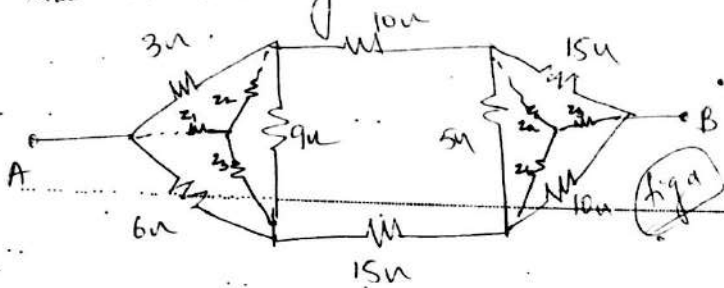8) Find the equivalent resistance across the terminals AB of the circuit shown in fig.



Soln:-

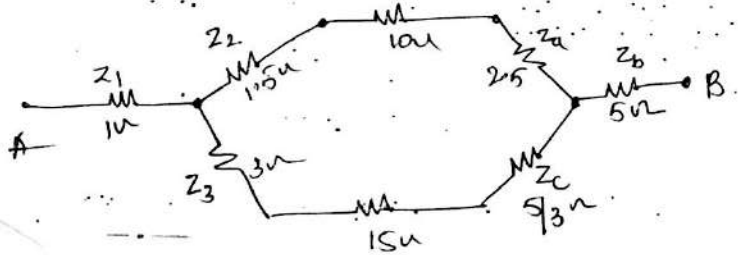

$$Z_1 = \frac{3 \times 6}{6+3+9} = 1 \Omega$$

$$Z_2 = \frac{3 \times 4}{18} = 1.5 \Omega$$



$$Z_3 = \frac{6 \times 9}{18} = 3 \Omega$$

$$Z_4 = \frac{5 \times 15}{30} = 2.5 \Omega$$

$$(5+15+10)$$

$$Z_5 = \frac{15 \times 10}{30} = 5 \Omega$$

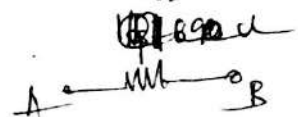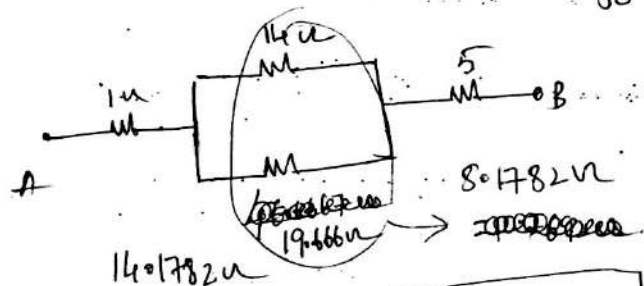
$$Z_6 = \frac{5 \times 10}{80} = 5/8 \Omega$$




$$R_{AB} = 14.0782 \Omega$$

9) In the circuit shown below (fig.) find the voltage across AB. Set the current drawn by the circuit is 1A.  $V_{AB} = 14.0782$  Volts

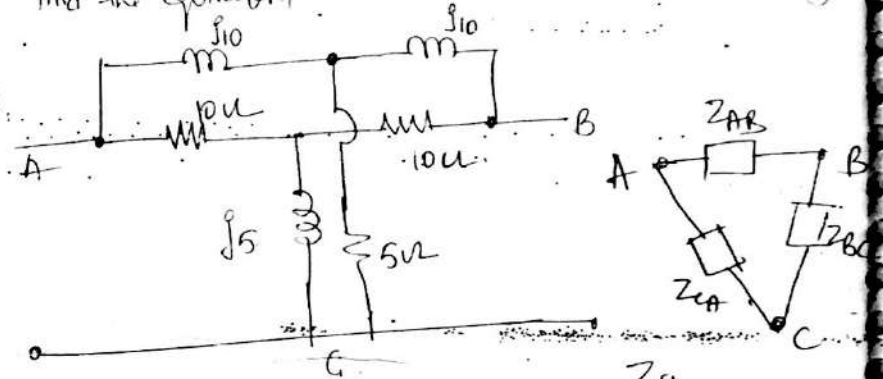83) Find the equivalent circuit of the circuit shown in fig.





Soln:-

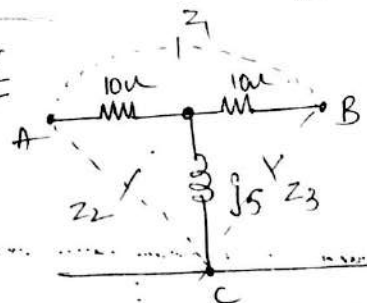

$$Z_1 = 10 + 10 + \frac{10 \times 10}{35} = (20 - 20/7) \Omega$$

$$Z_2 = 10 + 5 + \frac{5 \times 5}{10} = 10 + 5 + \frac{25}{10} = (10 + 5.5) \Omega$$
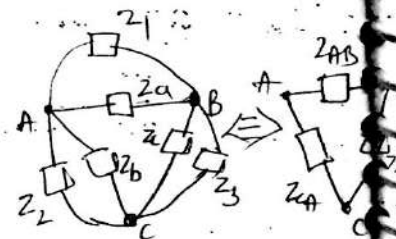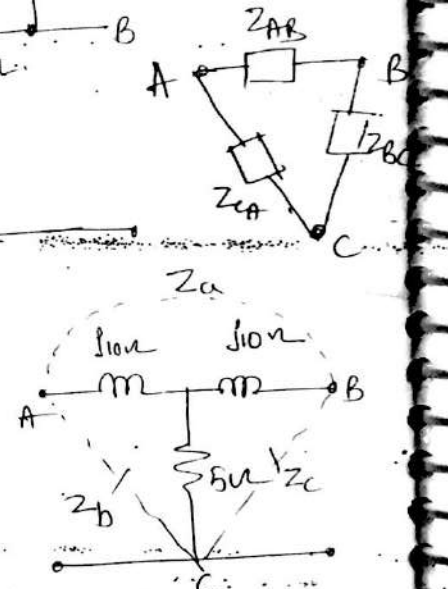
$$Z_3 = 10 + 5 + \frac{10 \times 5}{10} = (10 + 10) \Omega$$



$$Z_{AB} = Z_1 \parallel Z_2$$

$$Z_{CA} = Z_2 \parallel Z_3$$

$$Z_{BC} = Z_3 \parallel Z_4$$

$$Z_a = j10 + j10 + \frac{j10 \times j10}{5}$$

$$= j20 - \frac{100}{5} = (-20 + j20) \Omega$$

$$Z_b = j10 + 5 + \frac{j50}{j10} = (10 + j10) \Omega$$

$$Z_c = j10 + 5 + \frac{j50}{j10} = (10 + j10) \Omega$$

$$Z_1 = (20 - j20) \Omega$$

$$Z_2 = (10 + j10) \Omega$$


$$Z_3 = (10 + j10) \Omega$$

$$Z_{AB} = Z_1 \parallel Z_a = \frac{Z_1 Z_a}{Z_1 + Z_a} = \frac{(20 - j20)(-20 + j20)}{-20 + j20 + 20 - j20} = \infty$$

$$\frac{1}{Z_{AB}} = \frac{1}{Z_1} + \frac{1}{Z_2} \Rightarrow Z_{AB} = \infty \Omega$$



$$Z_{CA} = Z_2 \parallel Z_b = \frac{Z_2 Z_b}{Z_2 + Z_b} = \frac{(10 + j10)(10 + j10)}{(10 + j10) + (10 + j10)} = (5 + j5) \Omega$$

Since  $Z_b = Z_2$

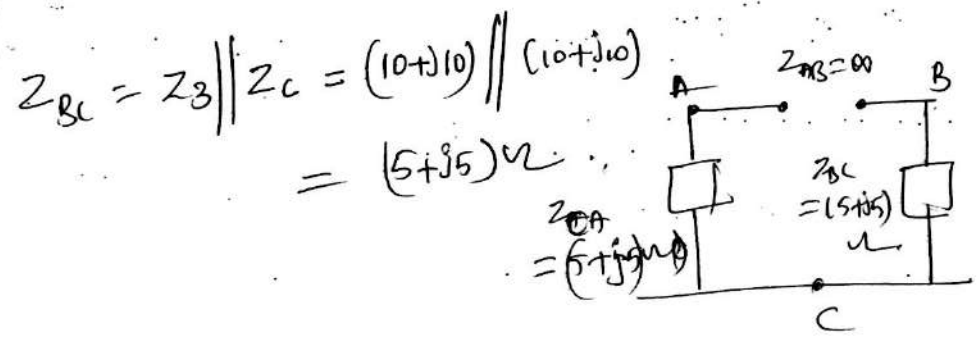


Q) A square based pyramid inscribed in a cube each of 60 cm. Find the equivalent resistance across the diagonally opposite corners.

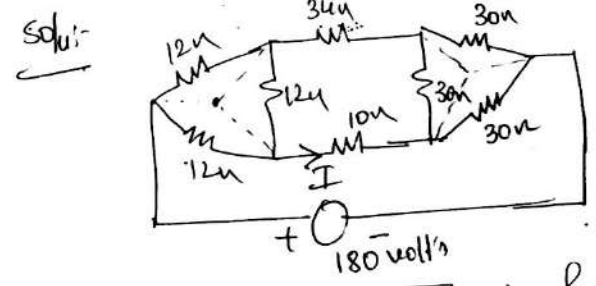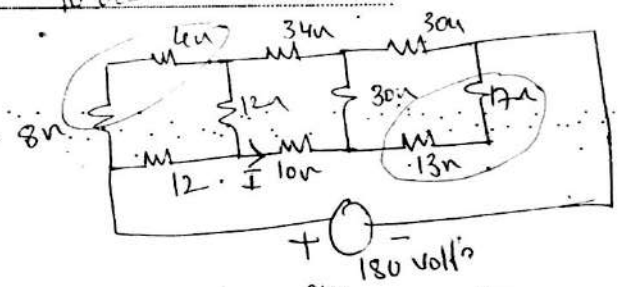Using Y-Δ transformation find the current through the 10 Ω resistor in the circuit shown.


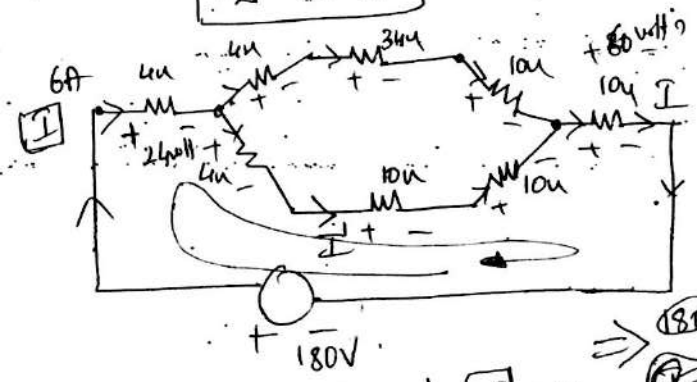
$$R_{\Delta} = 3 \cdot R_Y \Rightarrow R_Y = \frac{R_{\Delta}}{3}$$



$$180 = 4I - 4I' - 10I' - 10I' - 10I' = 0$$

The same current  $I = ?$

$$I = \frac{180}{4 + 48 \parallel 24 + 10} = 6A$$

$$\Rightarrow 180 = 4I + 34I$$

$$180 = 4(6) = 34I$$

$$\Rightarrow I = \frac{180 - 24}{34}$$

$$180 - 24 - 24I - 60 = 0$$



$$\boxed{I = \frac{180 - 60}{84}}$$

$$I = \frac{120}{84} = \frac{96}{84} = 4A$$

The current flows through  $10 \mu$  resistor

$$\boxed{I_{10\mu} = 4A}$$

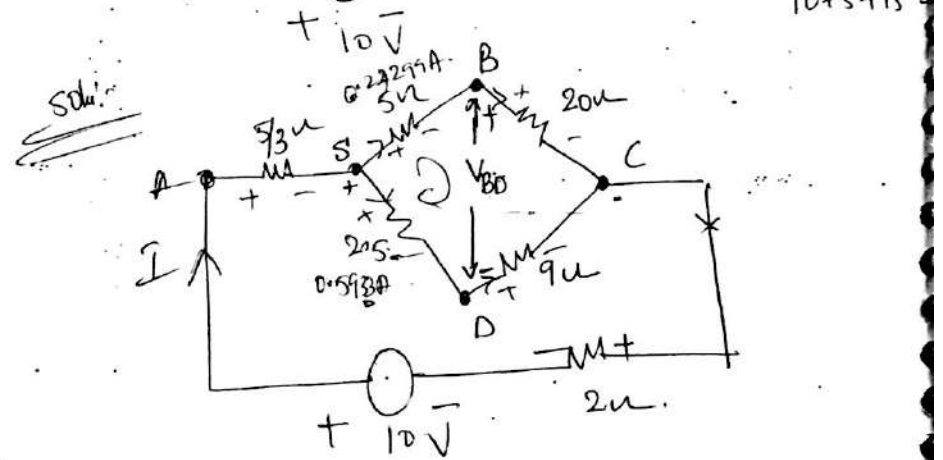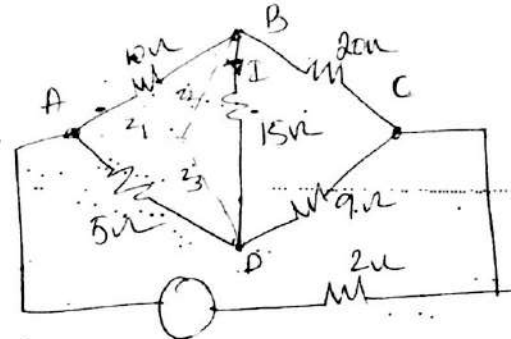8) using star-delta transformation find the current through the branch connected between B, D.



The same current  $I = \frac{10}{\frac{5}{3} + (2 \parallel 11.05) + 2} = 0.86629$

$$10 - \frac{5}{3}(I) - V_{sc} - 2(I) = 0$$

$$V_{sc} = 10 - \frac{5}{3}(0.86629) - 2(0.86629)$$

$$\boxed{V_{sc} = 6.823 \text{ Volts}}$$




$$0.5933(2.5) - 5(0.27889) - V_{BD} = 0$$

$$V_{BD} = 0.1183 \text{ V}$$


$$I = \frac{V_{BD}}{15\Omega} = \frac{0.1183}{15}$$

$$I = 7.886 \text{ mA} = 0.007886 \text{ Ampere}$$


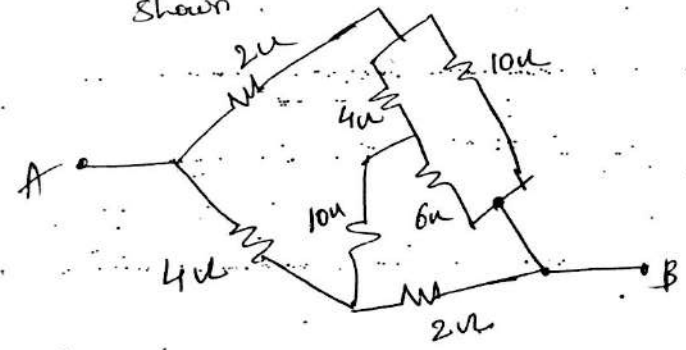
Q Find the equivalent Resistance across AB for the circuit shown




Soln:-

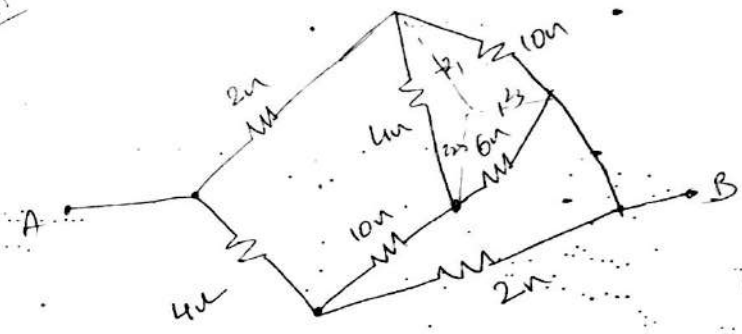

$$4 + 10 + 6 = 20$$

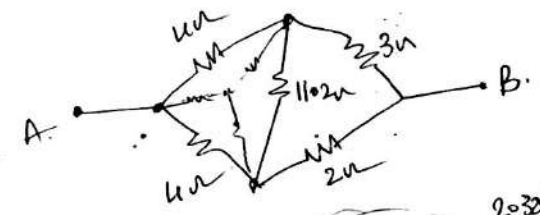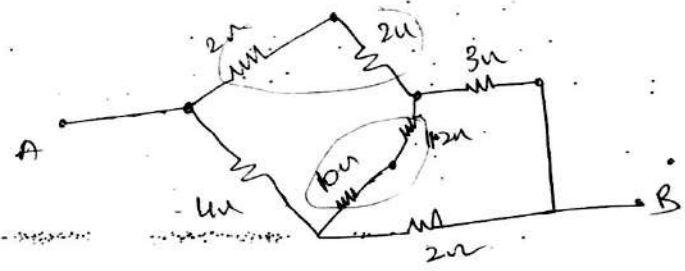


$$4 + 4 + 11.02 = 19.2$$





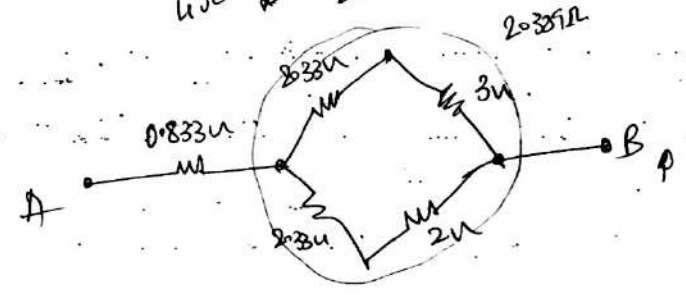


$$R_{AB} = 3.0229 \Omega$$

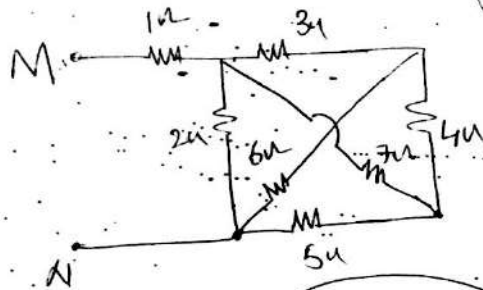Q) Using star/delta transformation, determine the resistance between M and N of net shown in fig.



Soln:-

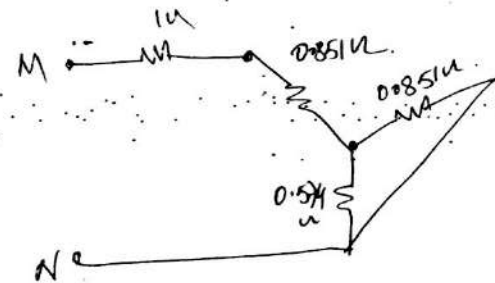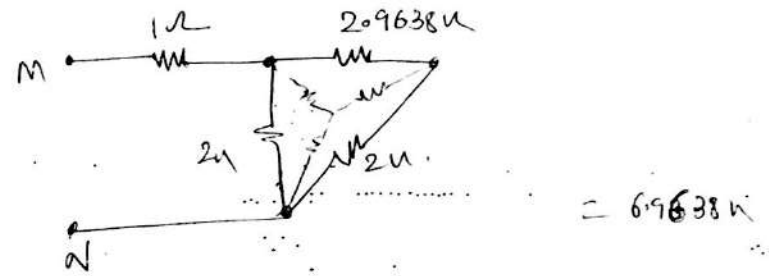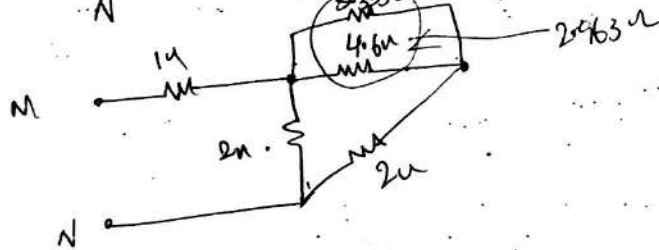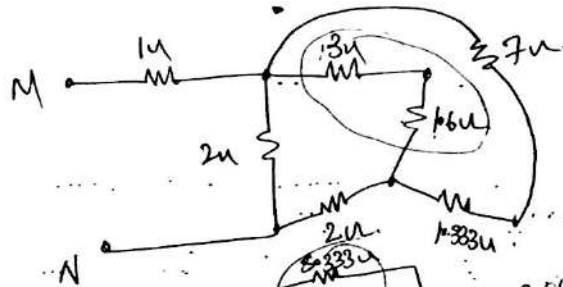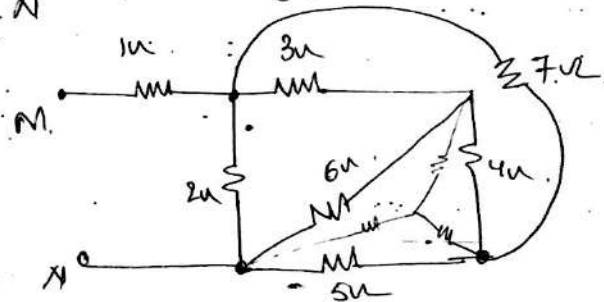


$$R_{MN} = 1 + 0.851 + (0.851) \parallel (0.574)$$

$$R_{MN} = 2.1937 \Omega$$

Q) Obtain expressions for an equivalent set of star connected impedances to replace a set of delta connected impedances. (5M) 3/5 2014.





8) Find the equivalent resistance at AB using Y-Δ transformation technique for the circuit shown in fig

(SN) Jan 2014

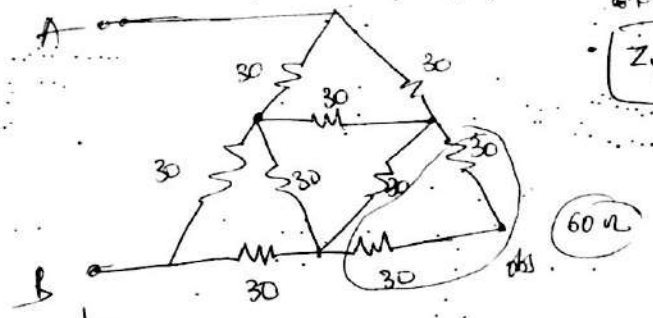


$$Z_Y = \frac{24}{3}$$

Solu:-

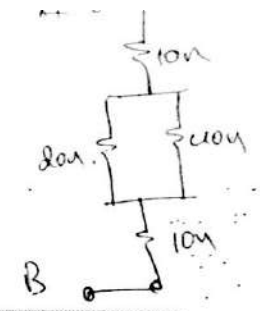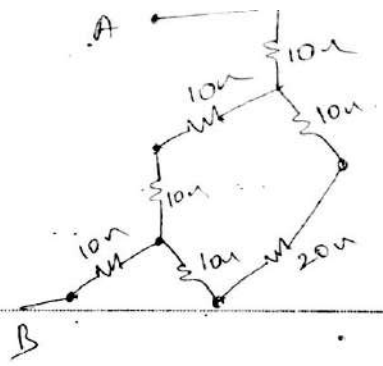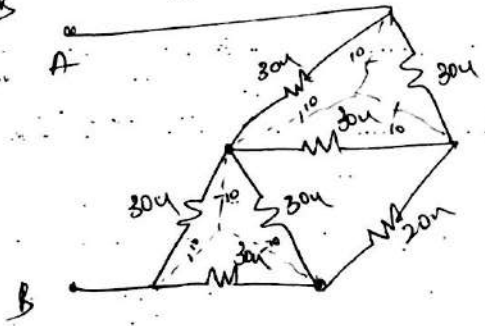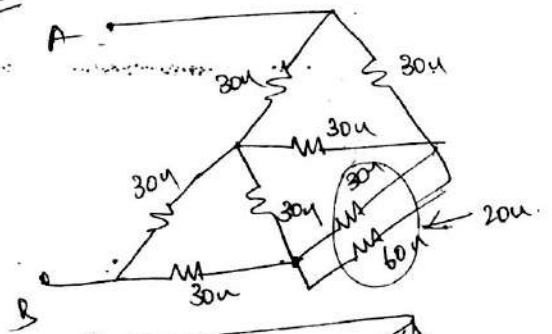




$$R_{AB} = 10 + (20 \parallel 10) + 10 = 33.33 \Omega$$

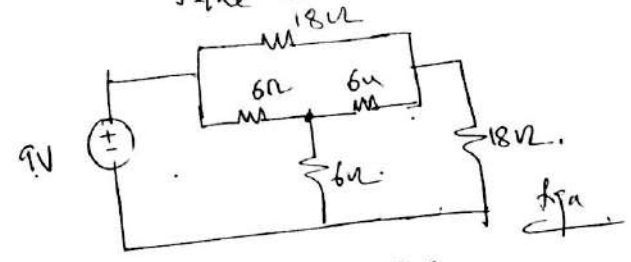8) Using star-delta transformation reduce the given network shown in fig (a) and determine the total current supplied by the source.



Solu:-

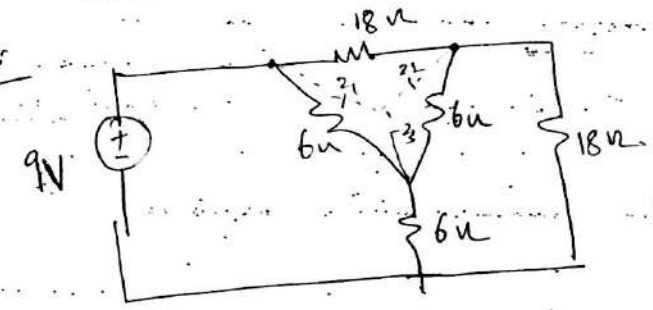

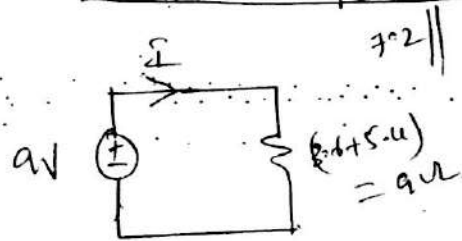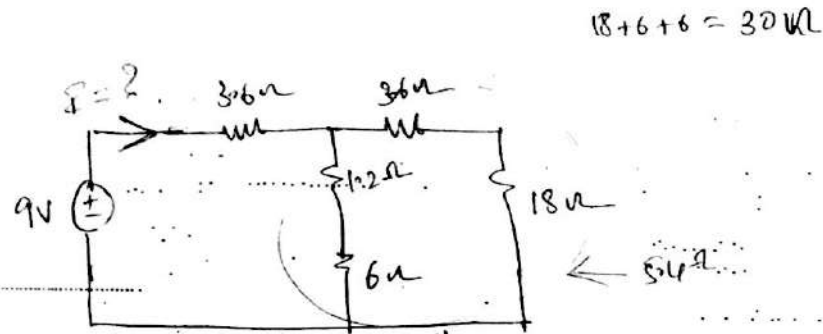


$$I = \frac{V}{R} = \frac{9}{9} = 1A$$



$I = 1 \text{ Ampere}$

the total current supplied by the source is 1 Ampere

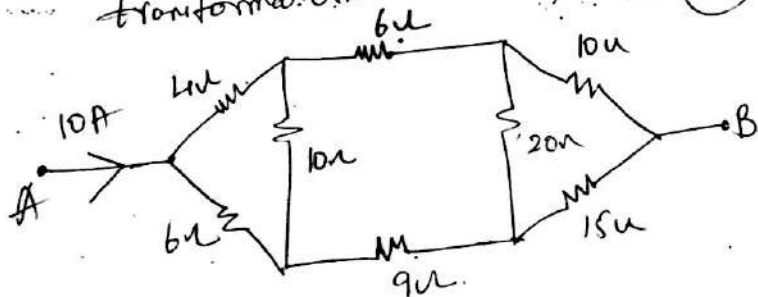Q) Find the voltage to be applied across AB in order to draw the current of 10A into the circuit using star-delta transformation.



Solu:-

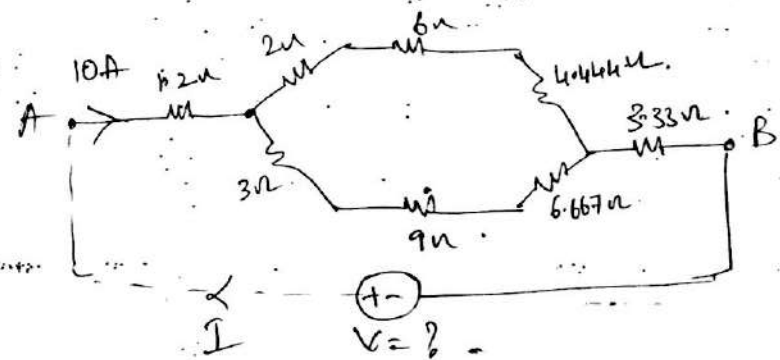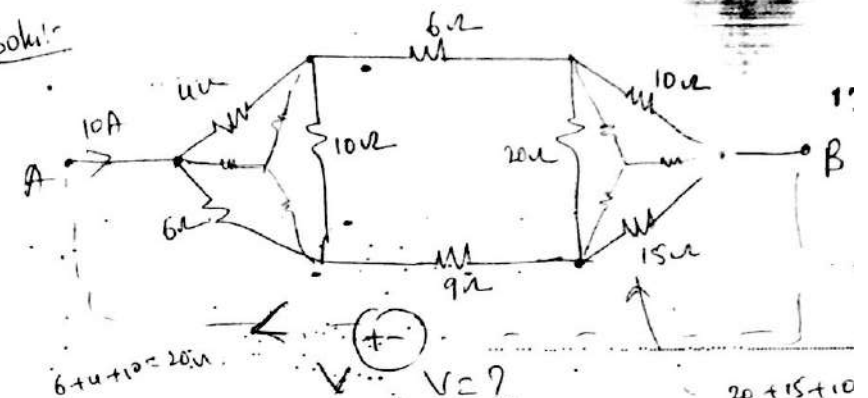

$$I = \frac{V}{R} \Rightarrow V = I \cdot R$$

$$V = 10 \left[ 1.2 + (2 \parallel 4.44) \parallel 18.667 + 3.33 \right]$$


$$= 10 \times 11.9967$$

$$V = 119.967 \approx 120 \text{ Volt}$$

(8) Determine current  $I_1$  in the circuit shown in fig. using star-delta conversion. (6m)



$$I_1 = \frac{V_{xy}}{(1+2+3)} = \frac{33.6}{4.2} = \underline{\underline{8A}}$$

18

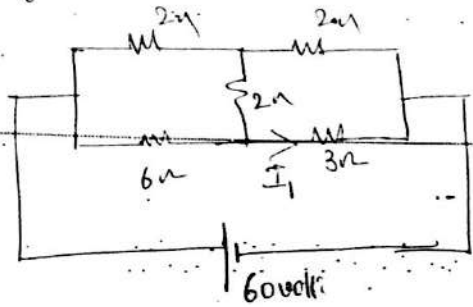

June 30/12

Soln

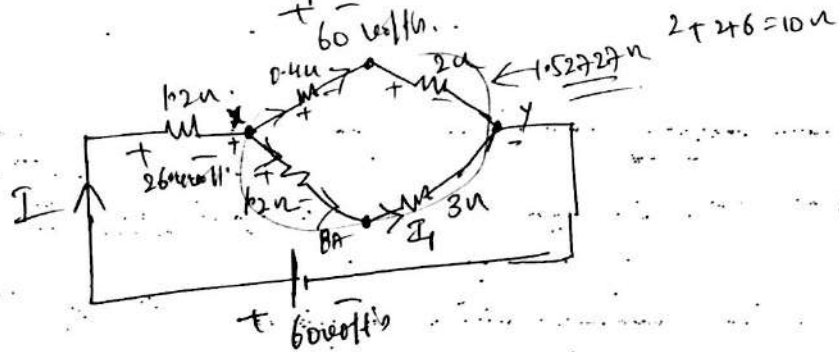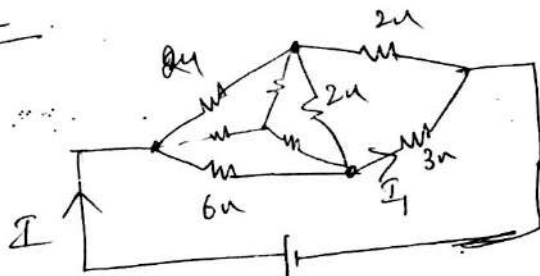

$$I = \frac{V}{R} = \frac{60}{10 + (2 \parallel 4.2)} = \frac{60}{20.272} = \underline{\underline{2.96A}}$$

$$60 - 26.4 - V_{xy} = 0 \Rightarrow \boxed{V_{xy} = 33.6 \text{ Volts}}$$

### MISSION

Provide quality and contemporary education, in the domain of Electronics and communication and related fields, which enable collaborative ventures with industries and research organizations. Emphasis laid on creating innovative teaching-learning processes that motivate self-learning.  
by imparting quality education embedded with discipline & national honor.

### VISION

To create a rich intellectual potential implanted with multidisciplinary knowledge, human values and professional ethics among the aspirant of becoming Engineers and technologies, so as to unlock their imagination and discover their potential.

### OBJECTIVES

1. To impart good technical knowledge to the students.
2. To produce Excellent Engineers in Electronics & Communication fields.
3. To fulfil the needs of the society in the various fields related to Electronics and Communication engineering.
4. To bring post-graduate program in the diverse field of electronics and communication Engineering.
5. To upgrade the facilities of Research & Development Centre of the department with the use of modern aid.
6. To organize training programs / workshops for upgrading staff performance.
7. To establish Industry - Institute Interaction.
8. To publish technical papers in National / International journals and conferences.

### GOALS (Short Term):



1. Modernizing the Laboratories with new software & state-of-the art hardware in tune with the latest technological developments.
2. To obtain Quality certification from an agency of reputed.
3. Teaching Aids: LCD Projector, Smart Boards.
4. Promoting Faculty Development Programmes.
5. Conducting the need based training programs for Faculty & Students.
6. To improve the pass percentage 2-5% compared to previous year.

### GOALS (Long Term):




1. To start additional P.G. Programmes in Electronic and Communication engineering discipline.
2. To enter into understanding with globally renowned universities for special programmes in emerging technologies.
3. Promoting Industry - Institute interaction through projects and R & D work.

Topic: Source transformation and Source Shifting:


→ Equivalent voltage source

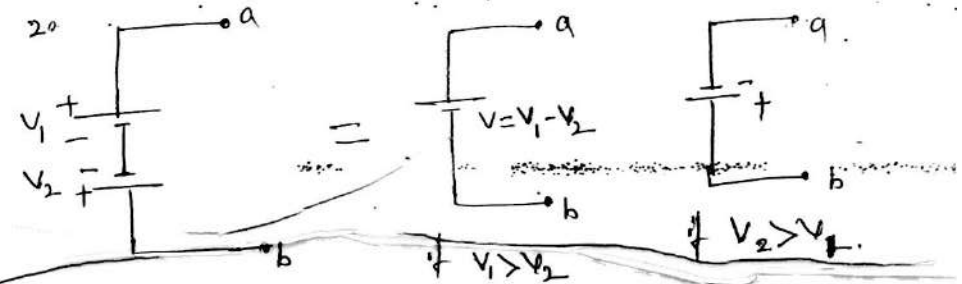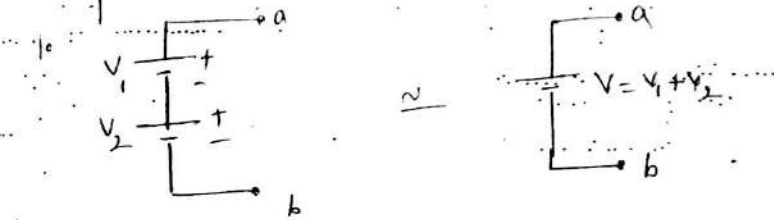

3. for ideal source's

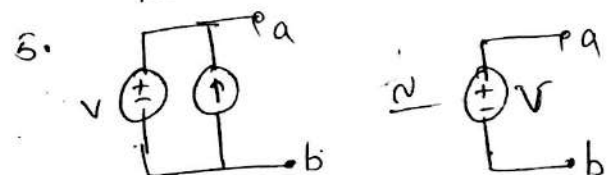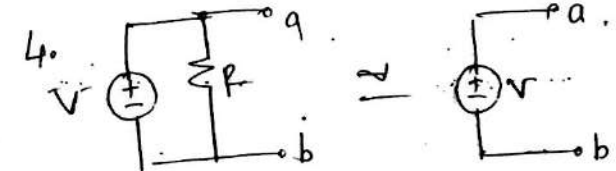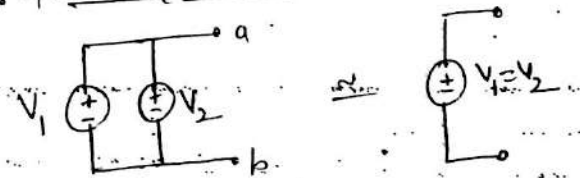

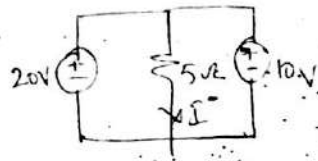
Find the value of  $I$  for the circuit shown below.




① 2A → 4A → 6A @ source.

Violation of KVL.

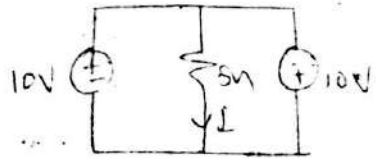Soln: In a voltage sensitive circuit the parallel branches should be equal.




Violation of KVL.

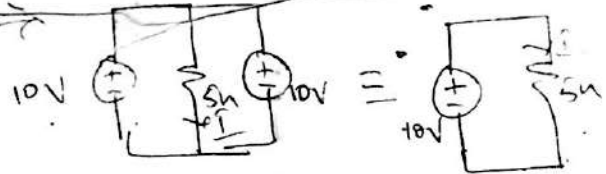


$$I = 10/5 = 2A$$

Example:

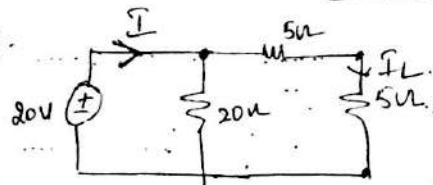

Find  $I_L$  and  $I$  and  $P_{del}$  by source.

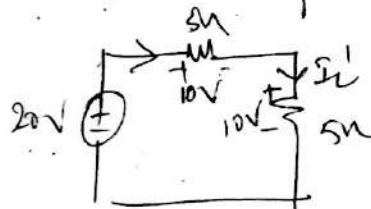As per the circuit equivalent circuit  $R = 20\Omega$




$$I = \frac{20}{10} = 2A$$

$$I_L = 2A$$

$$P_{del} = I \times V = 2 \times 20 = 40 \text{ Watt/h}$$

$$V_L = 2 \times 5 = 10 \text{ Volt}$$

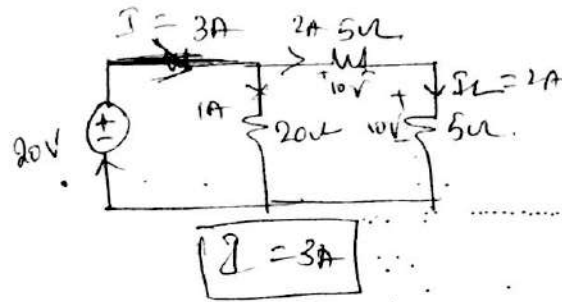

$$V_L = 10 \text{ Volt/h}$$

$$I_L = \frac{20}{10} = 2A$$


and  $P_{del} = VI = 20 \times 3 = 60 \text{ watt/h}$

Note:

(i) In the above circuit 20Ω resistance can be neglected while calculating either load current @ load voltage.

(ii) In the above circuit 20Ω resistance cannot be neglected while calculating source current @ power.

Sample 3:

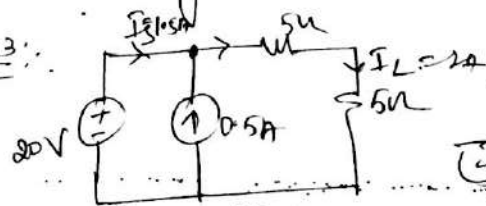


$$I_L = 2A$$

$$V_L = 10 \text{ Volt/h}$$

$$I_S = 1.5A$$

$$P_{del} = 1.5 \times 20 =$$

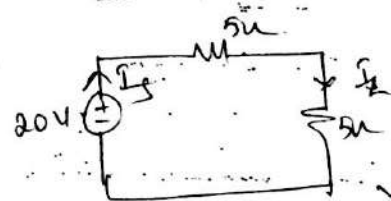






$$I_L = 2A$$

$$V_L = 10 \text{ Volt/h}$$



$$I_S = 2A$$

$$P_{del} = 20 \times 2 = 40 \text{ W}$$


Note 1: In the above circuit current source can be neglected while calculating either load current @ load voltage.  
2. In the above circuit current source cannot be neglected while calculating either voltage source current @ power.

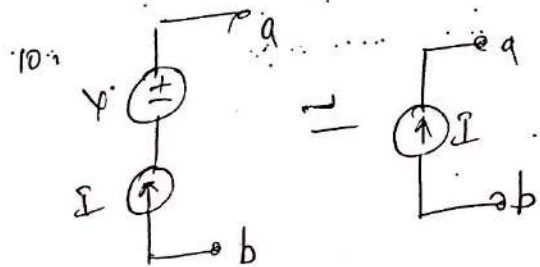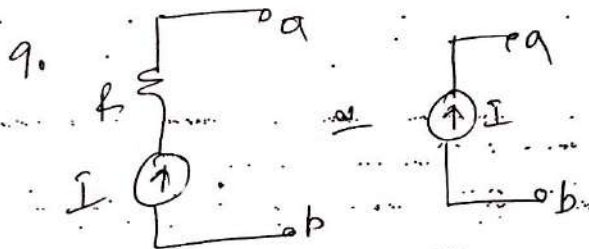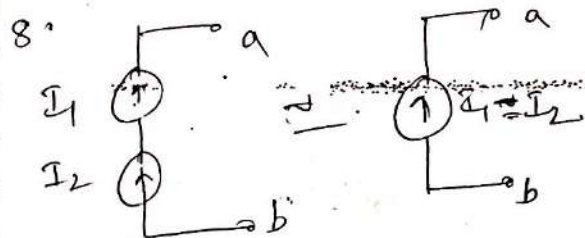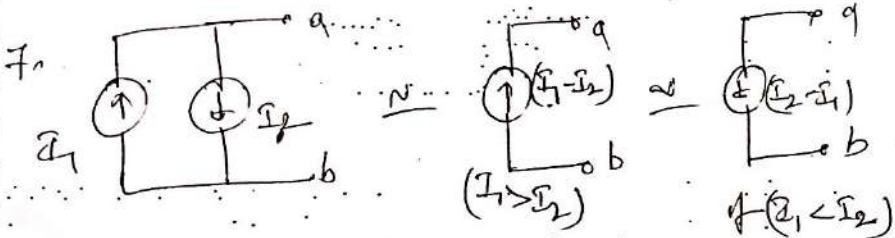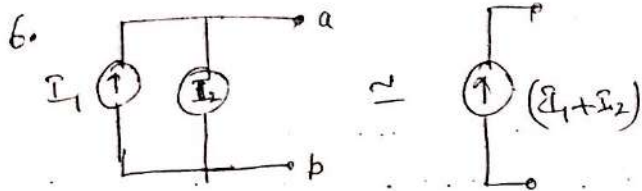

Example 1

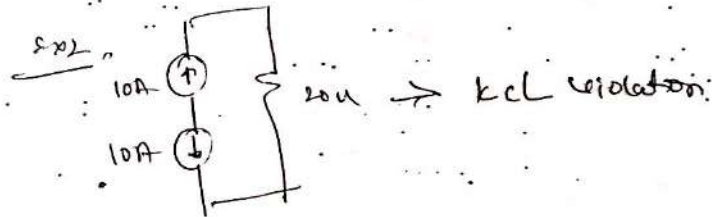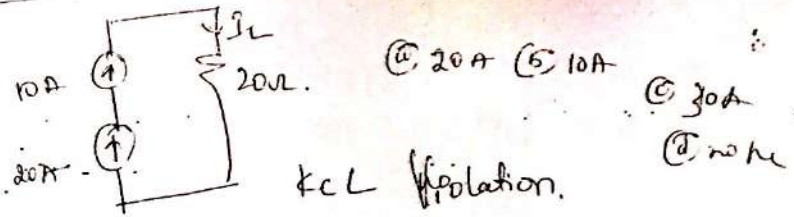

Ex 3

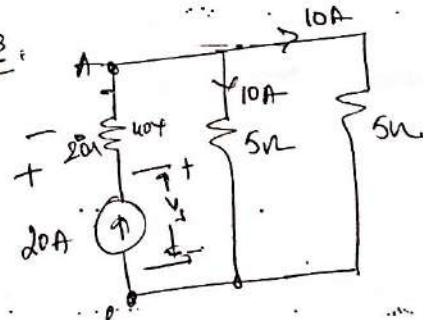


$V_{ab} = V_s - 40$  (where  $I_L = 10A$ ,  $V_L = 50V$ )  
 $V_{ab} = 10 \times 5 = 50V$

$V_s = V_{ab} + 40 = 50 + 40 = 90V$

$P_s = I \times V_s = 20 \times 90 = 1800 \text{ watt's}$

if neglect  $20\Omega$

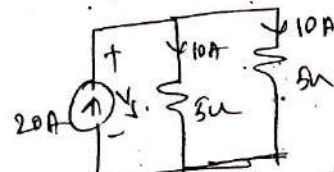


$V'_{ab} = 50V$   
 $P_s = 50 \times 20 = 1000 \text{ watt's}$  (where  $I_L = 10A$ ,  $V_L = 50V$ )

- Notes: ① In the above circuit  $20\Omega$  resistance can be neglected while calculating either load current or Load voltage.  
 ② In the above circuit  $20\Omega$  resistance cannot be neglected while calculating either source voltage or source power.



Ex:

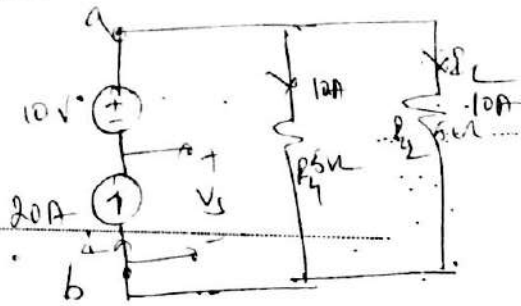

$$V_{ab} = V_s + 10$$


$$V_{ab} = 5 \times 10 = 50 \text{ volts}$$

$$V_s = V_{ab} - 10 = 50 - 10 = 40 \text{ volts}$$

$$V_s = 40 \text{ volts}$$

neglect 10V source
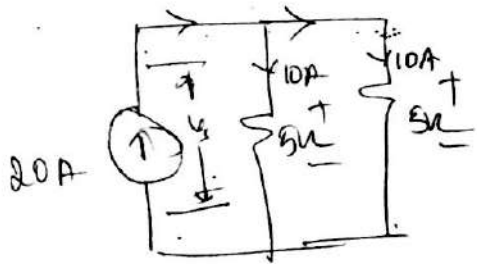
$$P_s = V_s I = 40 \times 20 = 800 \text{ watt}$$




$$V_s' = 5 \times 10 = 50 \text{ volts}$$

$$P_s' = 50 \times 20 = 1000 \text{ watt}$$


Note 1. In the above circuit voltage source can be neglected while calculating with load current @ load voltage.

Note 2. In the above circuit voltage source cannot be neglected while calculating the source voltage of same power.


### Source Transformation

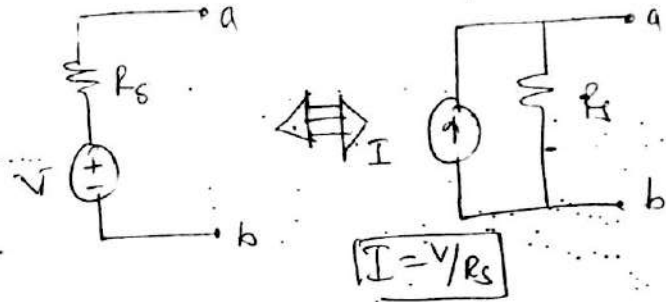


General

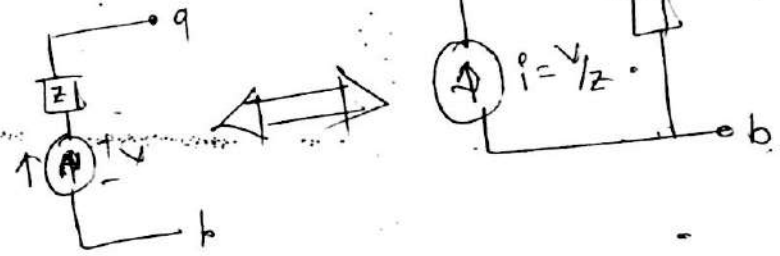




### Source shifting

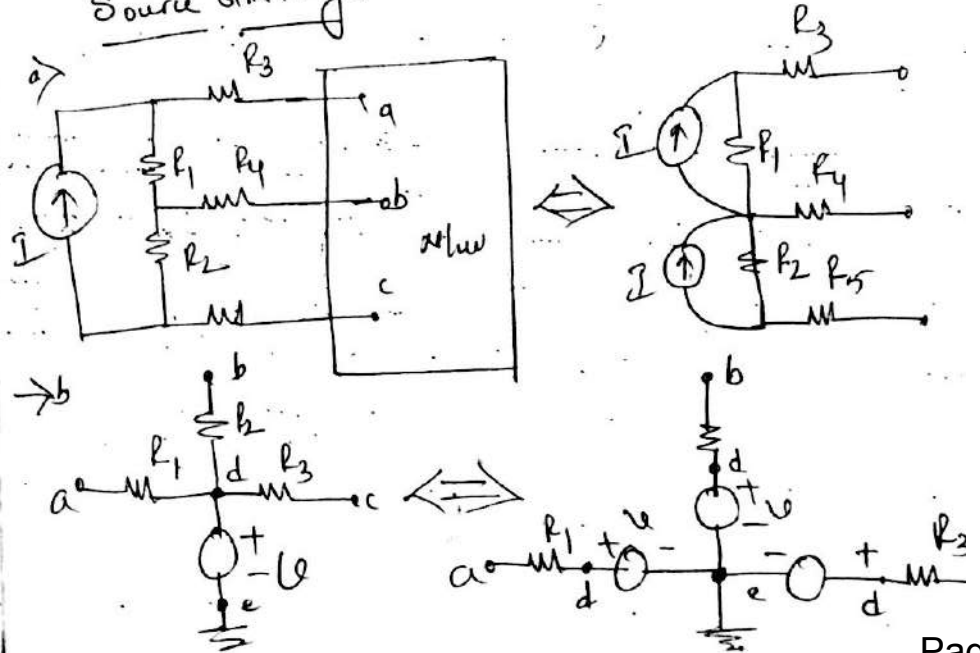

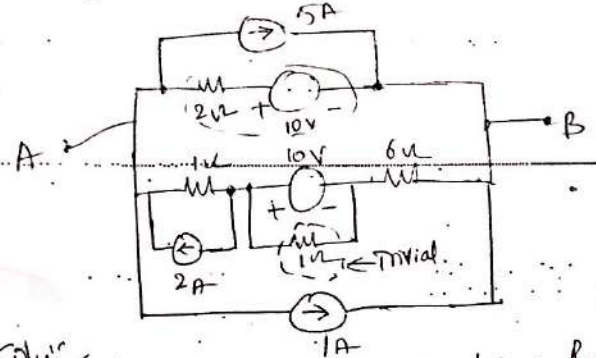
Q) Reduce the fig shown into a practical voltage source across the terminal AB.



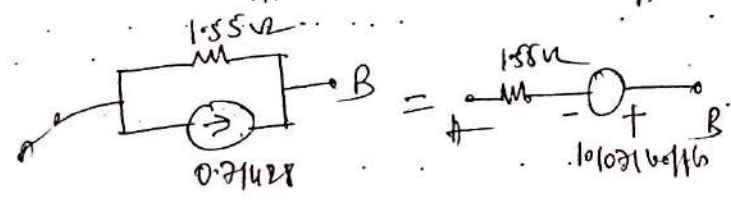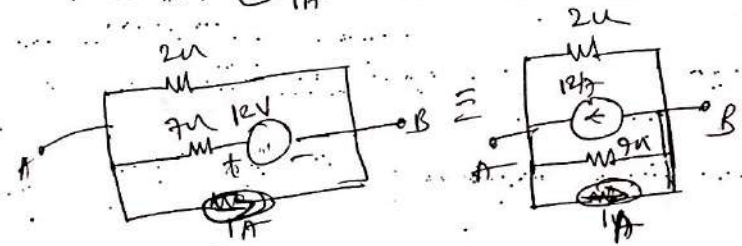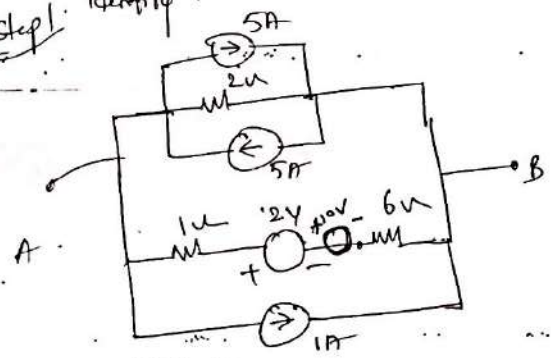Soln  
Step 1: identify the Trivial element & remove it if any.




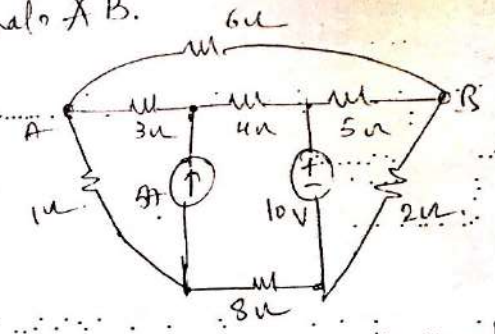
Q) Reduce a network into an equivalent voltage source across terminals A B.










Soln  
Step 1: no trivial element present.



Step 2: all are ideal sources. Source Transformation cannot be applied.

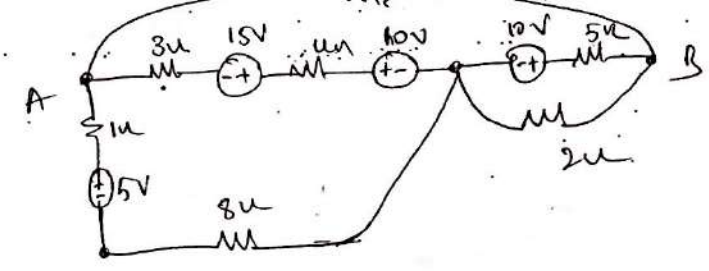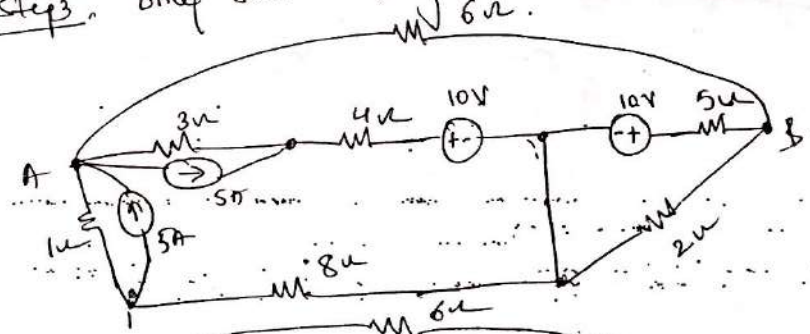Step 3: only source shifting is to be done.




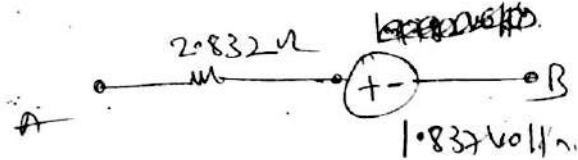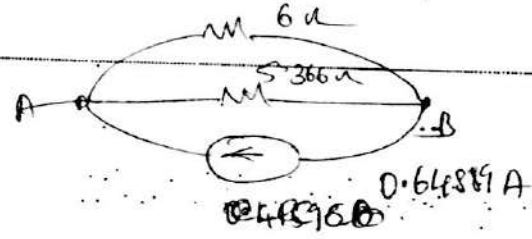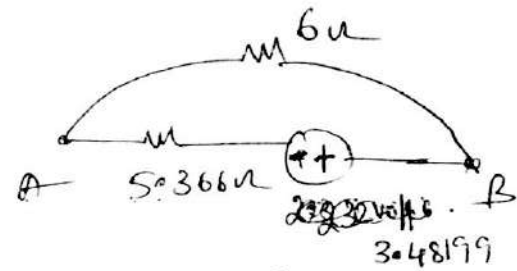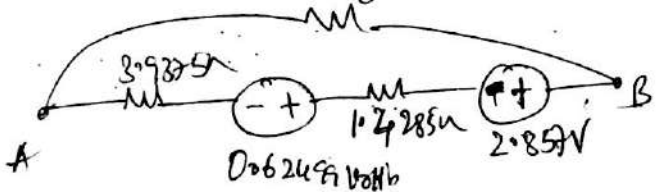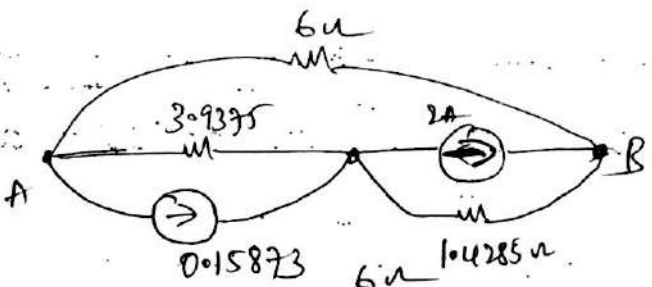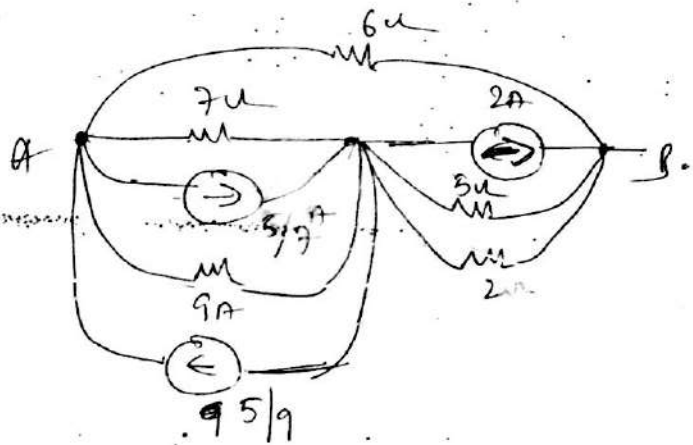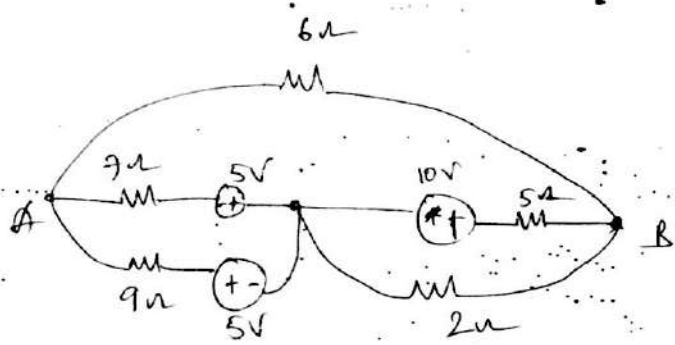

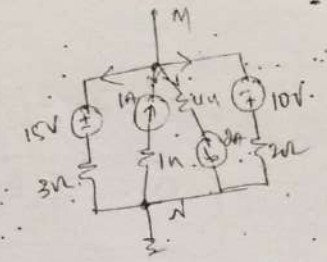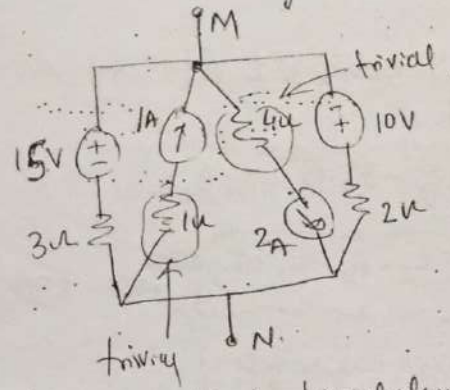Q. For the circuit shown in fig. Find the potential difference between M and N using source transformation. (4M)  
 Dec/Jan 2015.





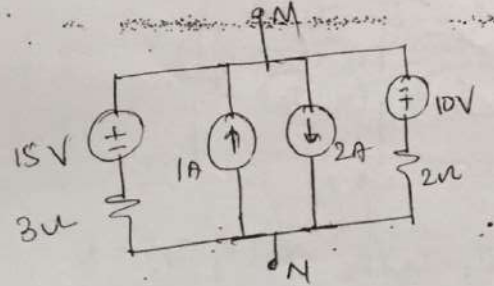
Soln: step 1. identify the trivial elements & remove them. KCL @ m.



$$\frac{V_m - 15 - 0}{3} - 1 + 2 + \frac{V_m + 10 - 0}{2} = 0$$

$$\Rightarrow 3 - (V_m - 15) + 2(V_m + 10) = 0$$




$$\Rightarrow V_m = -1.2 \text{ volt}$$

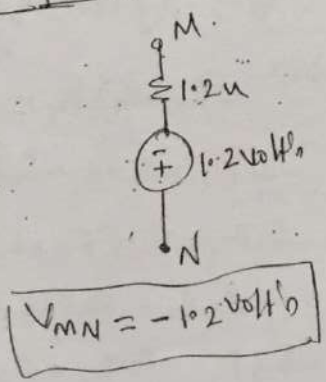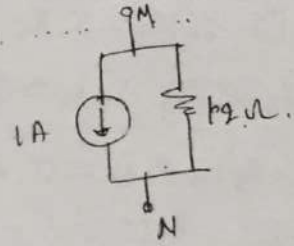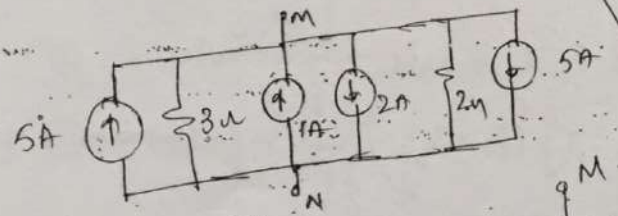

$$V_{MN} = -1.2 \text{ volt}$$

Tools  
 → 1. Loop Analysis @ Mesh Analysis ⇒ [KVL + Ohm's]  
 → 2. Node voltage method [KCL + Ohm's Law]

Fundamentals:

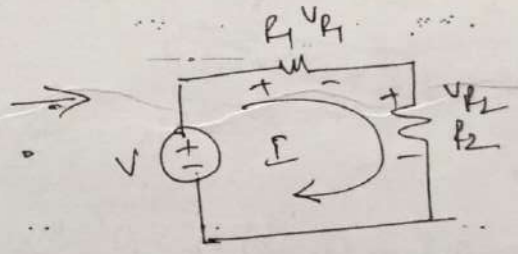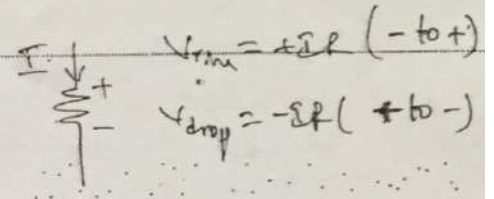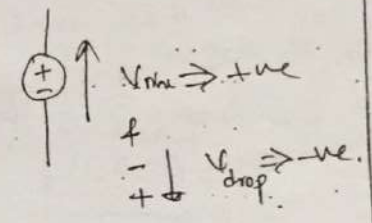


∴ circuit has only one loop  
 ∴ Loop current I is same as branch current.  
 i.e.  $I = I_{R1} = I_{R2}$

KVL

$$V - V_{R1} - V_{R2} = 0$$
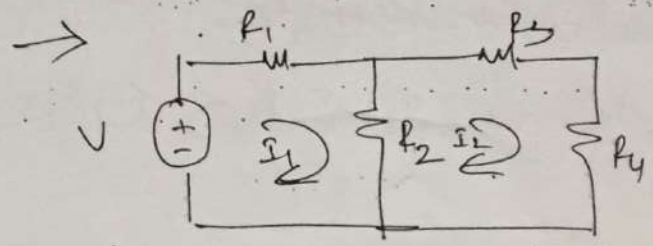
$$V - IR_1 - IR_2 = 0 \Rightarrow \boxed{V = IR_1 + IR_2} \text{ volt}$$





$$I_1 R_2 + I_2 R_3 - (R_1 + R_2 + R_3) I_3 = 0.$$





← (3)

through three unknowns solve?


for  $I_1, I_2, I_3$ .

Q

Note!

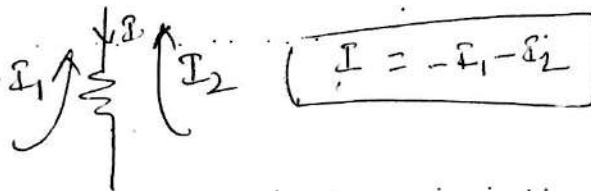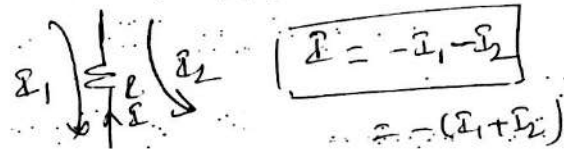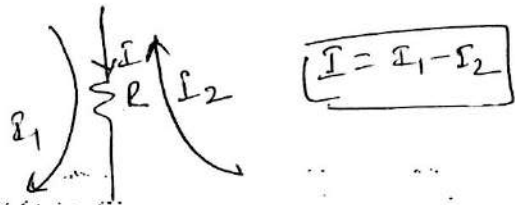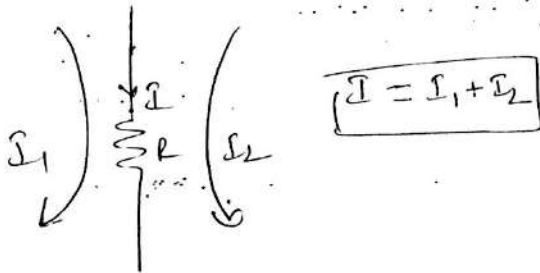

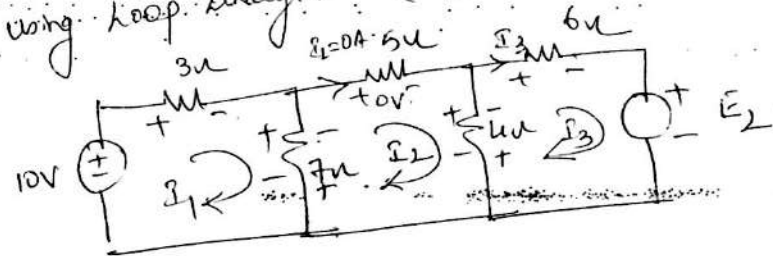Q In the network shown estimate the value of  $E_2$  such that the current through  $5\Omega$  resistor is zero. using loop analysis (6m)



Solve given  $I_{5\Omega} = 0$ .

KVL 1st loop

$$10 - 3I_1 - 7(I_1 - I_2) = 0$$

$$10 = 3I_1 + 7I_1 - 7I_2 = 10I_1 - 7I_2$$

$$10I_1 - 7I_2 = 10$$

$$\text{given } I_2 = I_{5\Omega} = 0A$$

$$10I_1 = 10 \Rightarrow I_1 = 1A$$

Loop 2

$$-7(0 - I_1) - 0 - 4(I_1 - I_3) = 0$$

$$I_1 = 1A$$

$$-7(-1) - 4(-I_3) = 0$$

$$+7 = -4I_3$$

$$I_3 = -7/4 = -1.75A$$

$$= -1.75A$$


Loop 3

$$-4(I_3 - I_2) - I_3 \cdot 6 - E_2 = 0$$


$$-10I_3 = E_2 \Rightarrow E_2 = -10I_3$$

$$\therefore E_2 = -10(-1.75) = +17.5 \text{ Volts}$$

2nd method using VDR

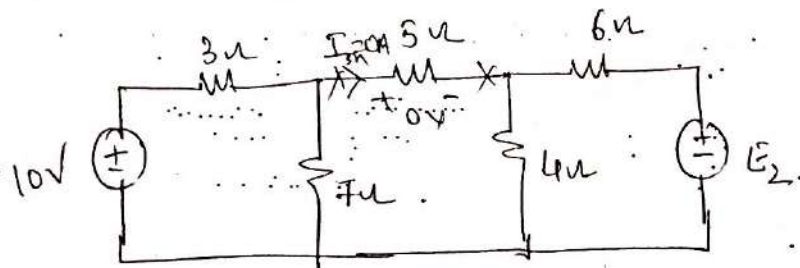

given  $I_{5\Omega} = 0 \text{ A}$

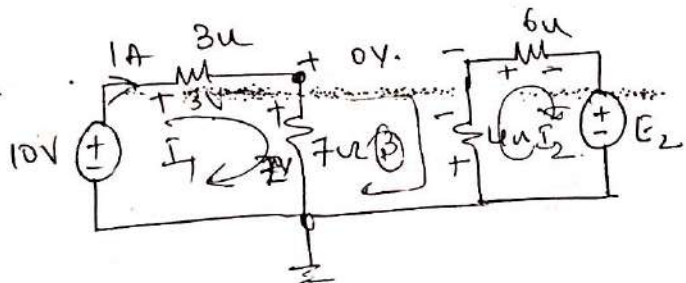

$$I_1 = \frac{10}{3+7} = 1 \text{ A}$$

KVL loops

$$-0 + 4(I_2) = 0$$


$$I_2 = -7/4 = -1.75 \text{ A}$$

KVL loop 2

$$E_2 + 6(-1.75) + 4(1.75) = 0$$

$$E_2 = 6 \times 1.75 + 4 \times 1.75 = 17.5 \text{ V}$$

Note:

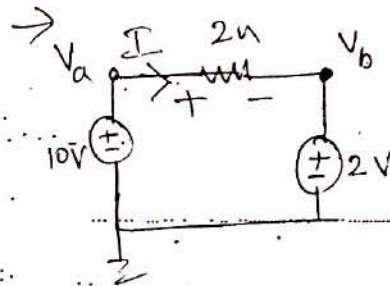


KVL

$$V_a - I(R) - V_b = 0$$

$$I(R) = V_a - V_b$$

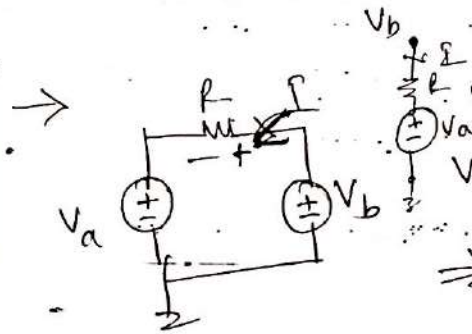
$$\Rightarrow I = \frac{V_a - V_b}{R} \text{ Amperes}$$



$$I = \frac{V_b - V_a}{R} \text{ A}$$


$$V_b - IR - V_a = 0$$
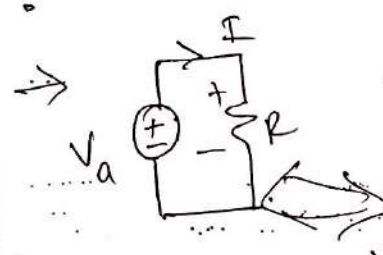
$$\Rightarrow I = \frac{V_b - V_a}{R} \text{ Amperes}$$




$$V_a = IR \Rightarrow I = \frac{V_a}{R}$$
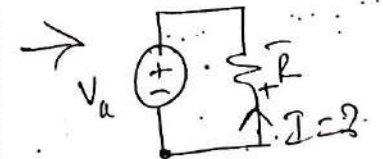
$$I = \frac{V_a - 0}{R} = \frac{V_a}{R}$$



$$V_a + IR = 0 \Rightarrow I = \frac{-V_a}{R}$$

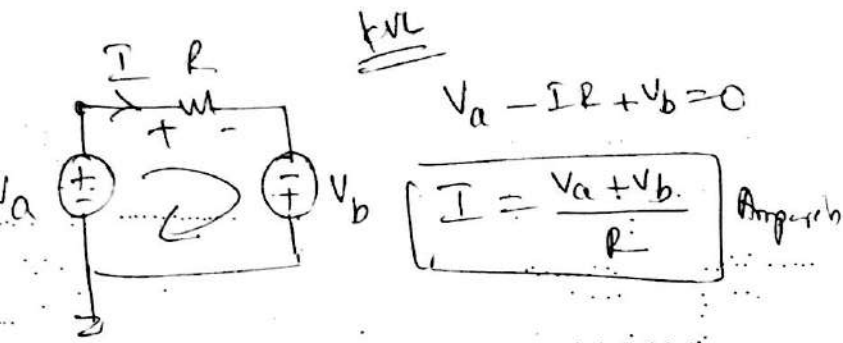
$$I = \frac{0 - V_a}{R} = \frac{-V_a}{R} \text{ Amperes}$$




KVL

$$V_a - IR + V_b = 0$$

$$I = \frac{V_a + V_b}{R} \text{ Amps}$$

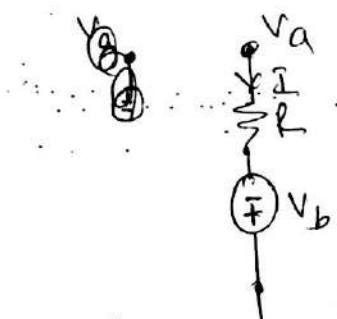


$$I = \frac{V_a + V_b}{R}$$

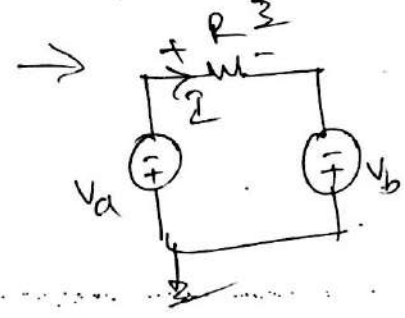

$$-V_a + IR + V_b = 0$$

$$I = \frac{V_b - V_a}{R} \text{ Amps}$$
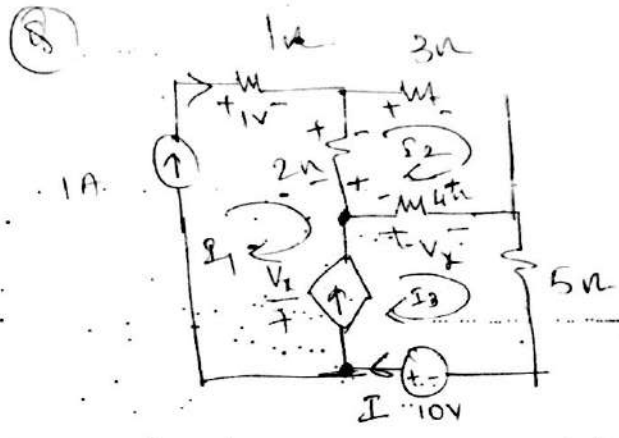
$$I = \frac{(-V_a) - (-V_b)}{R} = \frac{-V_a + V_b}{R} = \left( \frac{V_b - V_a}{R} \right) \text{ Amps}$$



find power supplied by 10V source using mesh current analysis.

$$I = 2$$

$$P_{del} = I \times V = 10 \times 2$$

$$P_{del} = 10 I$$

$$(I_3 - I_1) = \frac{V_x}{7} \leftarrow (1)$$

$$I = \frac{V_x}{7} + 1 \leftarrow (2)$$

$$I_1 = 1A \leftarrow (3)$$

KVL loop 2

$$-2(I_2 - I_1) - 3I_2 - 4(I_2 - I_3) = 0$$

$$-2I_2 + 2I_1 - 3I_2 - 4I_2 + 4I_3 = 0$$


$$2I_1 - 9I_2 + 4I_3 = 0 \leftarrow (3)$$

$$I_1 = 1A$$

$$V_x = (I_3 - I_2) 4 \leftarrow (4)$$
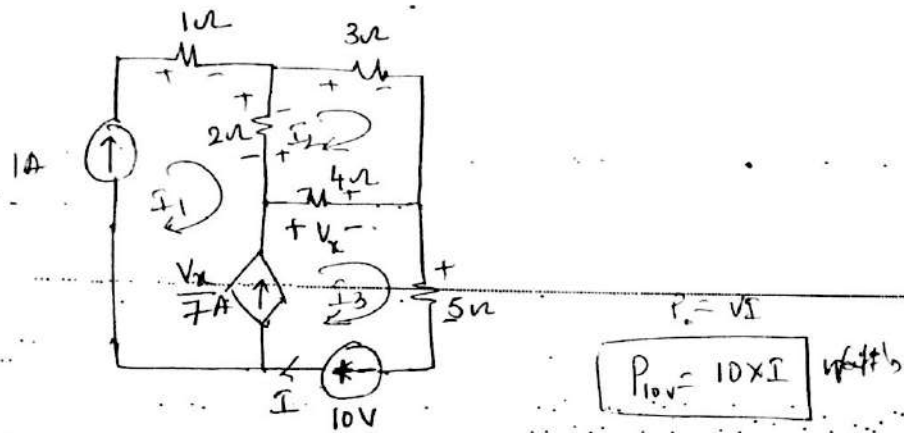
$$I_3 - 1 = \frac{V_x}{7} (I_3 - I_2) \leftarrow$$





Solve  
Loop 1:  $I_1 = 1A \leftarrow (1)$

Loop 2:  $-2(I_2 - I_1) - 3I_2 - 4(I_3 - I_2) = 0$   
 $-2I_2 + 2I_1 - 3I_2 - 4I_3 + 4I_2 = 0$   
 $2I_1 - 9I_2 + 4I_3 = 0 \leftarrow (2)$

Loop 3  
Summation  
 $I_3 - I_1 = \frac{V_x}{7}$   
 but  $V_x = (I_3 - I_2)4$   
 $I_3 - I_1 = \frac{4}{7}(I_3 - I_2)$   
 $I_3 - I_1 - \frac{4}{7}I_3 + \frac{4}{7}I_2 = 0$   
 $\frac{4}{7}I_2 + (1 - \frac{4}{7})I_3 = I_1$

$-9I_2 + 4I_3 = -2I_1$   
 $I_1 = 1$   
 $-9I_2 + 4I_3 = -2 \leftarrow (a)$

$$\frac{4}{7}I_2 + \frac{3}{7}I_3 = 1 \leftarrow (b)$$

Solving eq (a) and eq (b)


$$I_2 = 0.7906 A \quad I_3 = 1.279 \text{ Amperes}$$

from fig.  $I_3 = I$  A


$$\Rightarrow I = 1.279 \text{ Amperes}$$

$P_{\text{dissipated (10V)}} = 10 \times I = V \times I$   
 $= 10 \times 1.279 = 12.79 \text{ Watts}$

Node voltage method

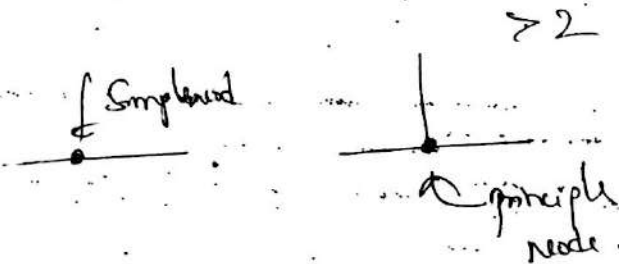


Node voltage method

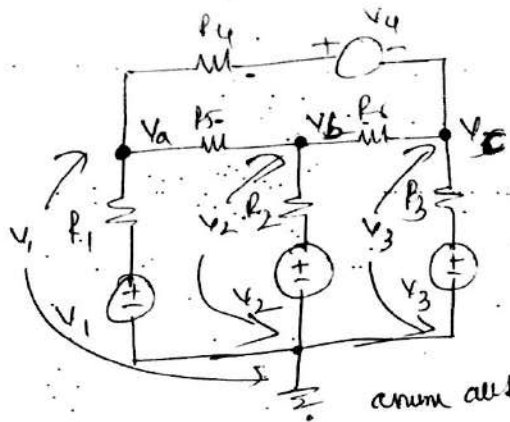

obs: 3 principal nodes + 1 GND


enum all the currents no leaving

KVL @ node a

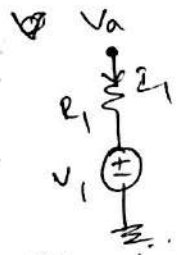

$$I_1 = \frac{V_a - V_1 - 0}{R_1}$$

$$I_2 = \frac{V_a - V_b}{R_2}$$

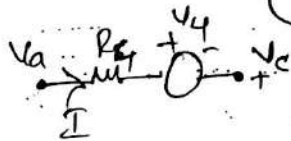

$$I = \frac{V_a - V_c - V_4}{R_4}$$

@ node a ( $V_a > V_b$ ,  $V_a > V_c$ )

$$\frac{V_a - V_1}{R_1} + \frac{V_a - V_b}{R_2} + \frac{V_a - V_4 - V_c}{R_4} = 0 \quad \text{--- (1)}$$


@ node b ( $V_b > V_a$ ,  $V_b > V_c$ )

$$\frac{V_b - V_2}{R_2} + \frac{V_b - V_a}{R_2} + \frac{V_b - V_c}{R_3} = 0 \quad \text{--- (2)}$$

@ node c ( $V_c > V_a$ ,  $V_c > V_b$ )

$$\frac{V_c + V_4 - V_a}{R_4} + \frac{V_c - V_b}{R_3} + \frac{V_c - V_3}{R_3} = 0 \quad \text{--- (3)}$$

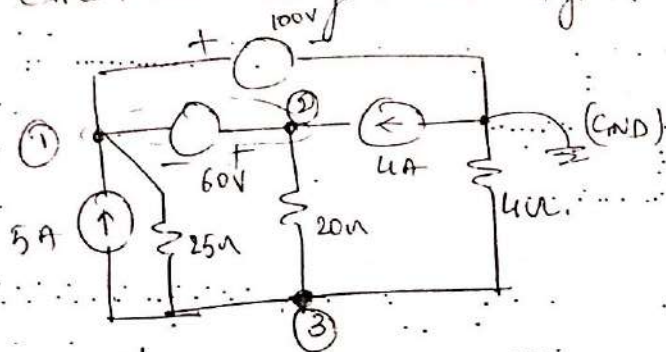Q8) Find the power <sup>absorbed</sup> delivered by the 4Ω resistor in the circuit shown using nodal analysis.



Soln:- w.r.t. node 1  
 $V_1 = 100V \leftarrow (1)$

$V_2 - V_1 = 60V \leftarrow (2)$


$V_2 = 100 + 60 = 160 \text{ volt}$

node 3  
 $5 + \frac{V_3 - V_2}{25} + \frac{V_3 - V_1}{4} = 0$

$\Rightarrow V_3 = 20.58 \text{ volt}$

$P_{4\Omega} = \frac{V_3^2}{R} = \frac{(20.58)^2}{4} = 105.96 \text{ watt}$

Q9) Determine all the node voltages.

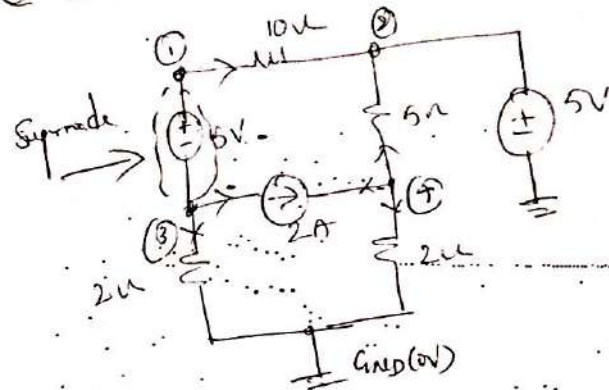

Soln  
 $V_2 = 5V \leftarrow (1)$   
 $V_1 - V_3 = 5V \leftarrow (2)$

@ node 4  
 $\frac{V_4}{2} + \frac{V_4 - V_2}{5} - 2 = 0$

$\Rightarrow \frac{V_4 - 5}{5} + \frac{V_4}{2} = 2$

$20 = 2V_4 - 2V_2 + 5V_4$

$\Rightarrow V_4 = 4.285 \text{ volt}$

@ Super node  
 $\frac{V_1 - V_2}{10} + \frac{V_3}{2} + 2 = 0$


$0.1V_1 - 0.1V_2 + 0.5V_3 + 2 = 0$

$V_2 = 5 \text{ volt}$  and  $V_2 = 5 \text{ volt}$

$V_1 = 1.66 \text{ volt}$

$V_3 = -3.33 \text{ volt}$

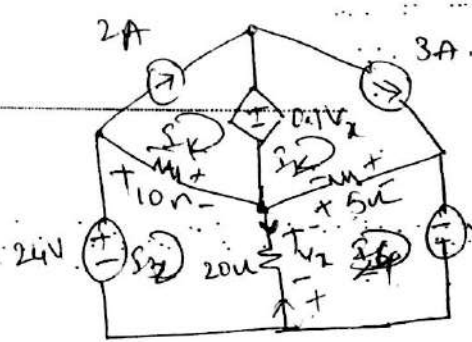8) Using mesh analysis determine the value of  $V_2$  which cause the voltage across the  $20\Omega$  resistor to be zero.



Soln  
 given  $V_{20\Omega} = 0$   
 $\Rightarrow V_{20\Omega} = V_x = 0 \text{ volts}$

$I_x = I_3 - I_4$   
 and  $V_x = I_x \times 20$   
 given  $V_x = 0$   
 $0 = [I_3 - I_4] \cdot 20$

$\Rightarrow \boxed{I_3 = I_4}$  Amperes.

Loop 1

$I_1 = 2A \leftarrow \textcircled{1}$   
 $I_2 = 3A \leftarrow \textcircled{2}$

Loop 3  $24 - 10(I_3 - I_1) - 20 = 0$

$24 = 10(I_3 - I_1)$   
 $I_1 = 2A$

$24 = 10I_3 - 10(2)$

$24 + 20 = 10I_3$   
 $\Rightarrow 10I_3 = 44 \Rightarrow \boxed{I_3 = 4.4} = I_4 \text{ Amperes}$

Envelope


$I_3 = I_4$

$20(I_4 - I_3) - 5(I_4 - I_2) + V_2 = 0$

$V_2 = 5(I_4 - I_2)$   
 $I_4 = I_3$   
 $= 5(4.4 - 3)$

$V_2 = 5 \times 1.4 = \underline{7 \text{ Volts}}$

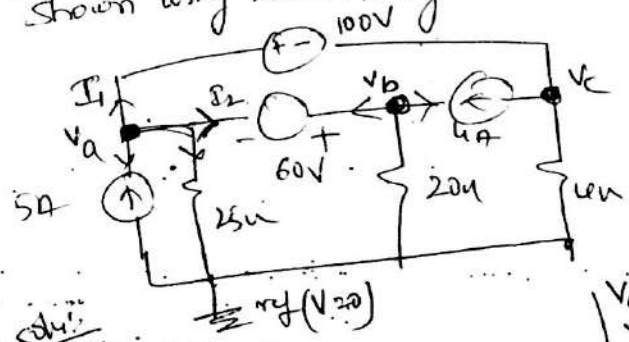9) Find the power delivered by the  $4\mu$  resistor in the circuit shown using nodal analysis.



$P_{4\Omega} = \frac{V_c^2}{4} \text{ Watts}$

Soln

@ a  $-5 + \frac{V_a}{25} + I_1 + I_2 = 0$

$\frac{V_a}{25} + I_1 + I_2 = 5 \leftarrow \textcircled{1}$

@ b

$\frac{V_b}{20} - I_2 - 4 = 0 \Rightarrow \frac{V_b}{20} - I_2 = 4 \leftarrow \textcircled{2}$

@ c

$\frac{V_c}{4} - I_1 + 4 = 0 \Rightarrow \frac{V_c}{4} - I_1 = -4 \leftarrow \textcircled{3}$

$V_a - V_c = 100 \leftarrow \textcircled{a}$   
 $V_b - V_a = 60 \leftarrow \textcircled{b}$   
 $V_b - V_c = 160 \text{ Volt} \leftarrow \textcircled{c}$

$$\begin{cases} 0.04 V_a + I_1 + I_2 = 5 \\ 0.05 V_b - I_2 = 4 \\ 0.25 V_c - I_1 = -4 \end{cases} \begin{cases} V_a - V_c = 100 \\ V_b - V_a = 60 \\ V_b - V_c = 160 \end{cases}$$

⇒  $0.04 V_a + I_1 + I_2 = 5$  ← (1)

$V_b = 60 + V_a$   
 $0.05(60 + V_a) - I_2 = 4$

⇒  $0.05 V_a - I_2 = 1$  ← (2)  
 $V_c = V_a - 100$

$0.25 [V_a - 100] - I_1 = -4$

$0.25 V_a - 25 - I_1 = -4$


⇒  $0.25 V_a - I_1 = (4 + 25) = 29$  ← (3)

$V_a = 79.41176 \text{ volts}$ ,  $I_1 = -110 \text{ Amps}$   
 $I_2 = 20.9705 \text{ Amps}$


⇒  $V_c = V_a + 100$   
 $V_c = 79.41176 - 100 = -20.588 \text{ volts}$

$P_{\text{uncorr}} = \frac{V_c^2}{4} = \frac{(-20.588)^2}{4} = 105.99 \text{ Watts}$

Find  $V_a$  by node analysis:

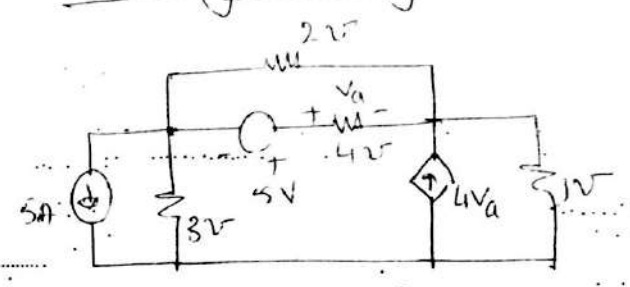

solu

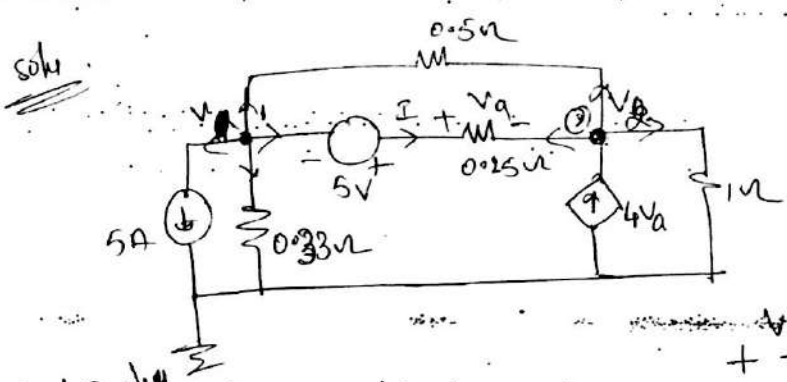

node 1  
 $\frac{V_1 - V_2}{0.5} + \frac{V_1}{0.333} + 5 = 0$

node 2  
 $\frac{V_2 - V_1}{0.5} + \frac{V_2 - 5}{0.25} + \frac{V_2}{1} - 4V_a = 0$

$V_a = \frac{V_1 - V_2}{0.25}$

$V_a = \left( \frac{V_1 - V_2}{0.25} \right) \times 0.25$

$V_a = V_1 - V_2 + 5 \text{ volts}$

$2V_1 - 2V_2 + 3V_1 + 5 + 4V_1 + 20 - 4V_2 = 0$   
 $9V_1 - 6V_2 = -25$  ← (4)

$$2v_2 - 2v_1 + 4v_2 - 20 + v_2 - 4(v_1 - v_2 + 5) = 0$$

$$(2v_2 - 2v_1 + 4v_2) - 20 + v_2 - 4v_1 + 4v_2 - 20 = 0$$

$$-6v_1 + 11v_2 - 40 = 0 \quad \text{--- (1)}$$

$$\begin{cases} 9v_1 - 6v_2 = -25 \\ -6v_1 + 11v_2 = 40 \end{cases}$$

$$v_a = 5.8 \text{ volts}$$

$$v_a = v_1 - v_2 + 5$$

$$= 5.8 - 6.8 + 5$$

$$v_a = 4 \text{ volts}$$

$$3v_1 + 2(v_1 - v_2) + (v_1 + 5 - v_2)4 + 5 = 0$$

$$3v_1 + 2v_1 - 2v_2 + 4v_1 + 20 - 4v_2 + 20 = 0$$

$$9v_1 - 6v_2 = -40$$

$$2(v_2 - v_1) + 4v_a + v_2 + (v_2 - 5 - v_1)4 = 0$$

$$2v_2 - 2v_1 - 4v_a + v_2 + 4v_2 - 20 - 4v_1 = 0$$

$$v_a = 0.25 \text{ (S)} = 0 \text{ of } \left[ \frac{v_1 + 5 - v_2}{4} \right]$$

$$v_a = v_1 - v_2 + 5$$

~~$$2v_2 - 2v_1 - 4v_a$$~~

$$2v_2 - 2v_1 - 4[v_1 - v_2 + 5] + v_2 + 4v_2 - 20 - 4v_1$$

$$2v_2 - 2v_1 - 4v_1 + 4v_2 - 20 + v_2 + 4v_2 - 20 - 4v_1 = 0$$

$$-10v_1 + 11v_2 = 40 \quad \text{--- (2)}$$

$$v_1 = -0.897 \text{ volts}$$

$$v_2 = 2.8205 \text{ volts}$$

$$v_a = v_1 - v_2 + 5$$

$$= -0.897 - 2.805 + 5$$

$$v_a = 1.2821 \text{ volts}$$

### MISSION

Provide quality and contemporary education, in the domain of Electronics and communication and related fields, which enable collaborative ventures with industries and research organizations. Emphasis laid on creating innovative teaching-learning processes that motivate self-learning. by imparting quality education embedded with discipline & national honor.

### VISION

To create a rich intellectual potential implanted with multidisciplinary knowledge, human values and professional ethics among the aspirant of becoming Engineers and technologies, so as to unlock their imagination and discover their potential.

### OBJECTIVES

1. To impart good technical knowledge to the students.
2. To produce Excellent Engineers in Electronics & Communication fields.
3. To fulfil the needs of the society in the various fields related to Electronics and Communication engineering.
4. To bring post-graduate program in the diverse field of electronics and communication Engineering.
5. To upgrade the facilities in Research & Development Centre of the department with the use of modern aids.
6. To organize training programs / workshops for upgrading staff performance.
7. To establish Industry-Institute Interaction.
8. To publish technical papers in National / International journals and conferences.

### GOALS (Short Term):

1. Modernizing the Laboratories with new software & state-of-the art hardware in tune with the latest technological developments.
2. To obtain Quality certification from an agency of reputed.
3. Teaching Aids: LCD Projector, Smart Boards.
4. Promoting Faculty Development Programmes.
5. Conducting the need based training programs for Faculty & Students.
6. To improve the pass percentage 2-5% compared to previous year.

### GOALS (Long Term):


1. To start additional P.G. Programmes in Electronic and Communication engineering discipline.
2. To enter into understanding with globally renowned universities for special programmes in emerging technologies.
3. Promoting Industry - Institute interaction through projects and R & D work.

### Unit III :- Network theorems :- I

- Superposition theorem.
- Reciprocity theorem.
- Millman's theorem.

To apply any theorem, the network as to full fill the following two properties...

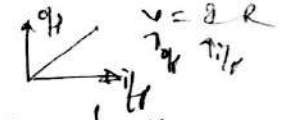1) Linearity :- An element is said to be linear if the excitation to response characteristic is linear.




2) Bilaterality :- The response remains the same for the both the polarities of the input excitation.

### Superposition theorem :- (SPT)

Statement :- In Any linear bilateral netw having two or more sources the total response in any part of the network will be equal to the algebraic sum of response due to each source acting alone at a time.


Note :- → all the ideal voltage sources are eliminated from the netw by shorting the sources, all the ideal current sources are eliminated by opening the sources (OC) and don't disturb the dependent source present in the netw.

Example:

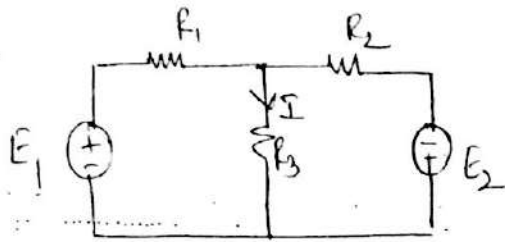

I - total response

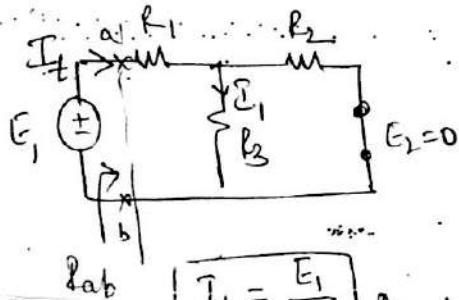Step 1: with  $E_1$  alone.  $E_2 = 0V$  (short ckt)



$$I_{T1} = \frac{E_1}{R_{ab}} \text{ Amperes}$$


$$R_{ab} = R_1 + R_2 \parallel R_3 = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

using branch current method

$$I_1 = I_{T1} \cdot \frac{R_2}{R_2 + R_3}$$

$$I_1 = \left( \frac{R_2}{R_2 + R_3} \right) \cdot \left( \frac{E_1}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} \right) \text{ Amperes}$$

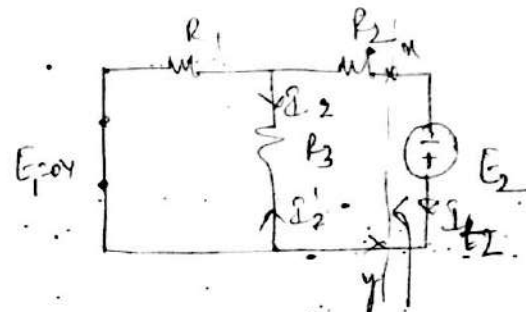Step 2: with  $E_2$  alone ( $E_1 = 0V$  @ short ckt).



$$I_{T2} = \frac{E_2}{R_{ba}} \text{ A}$$

$$R_{ba} = R_2 + R_1 \parallel R_3 = R_2 + \frac{R_1 R_3}{R_1 + R_3}$$

using branch current method

$$I_2' = I_{T2} \left( \frac{R_1}{R_1 + R_3} \right)$$

$$I_2' = \frac{E_2}{R_{ba}} \left( \frac{R_1}{R_1 + R_3} \right)$$

$$I_2' = \frac{E_2}{\left( R_2 + \frac{R_1 R_3}{R_1 + R_3} \right)} \left( \frac{R_1}{R_1 + R_3} \right) \text{ Amperes}$$

$$I_2 = -I_2'$$

$$\Rightarrow \text{Total response } I = I_1 + I_2$$

$$\Rightarrow I = I_1 - I_2' \text{ Amperes}$$




## 2 Reciprocity theorem:

In any linear bilateral network consisting of only one source, the ratio of the Excitation to response remains unchanged even after interchanging their positions.

(a) [In a single source also the positions of the source and response can be interchanged]

Example:

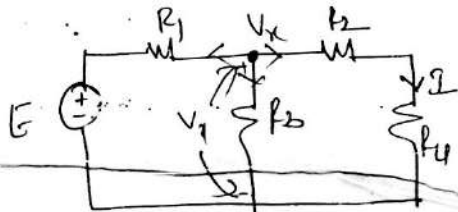

E - Excitation / Source / input

I - response

$$\boxed{\frac{E}{I} = \text{Constant } (k_1)}$$

$$\text{Kcl @ } \frac{V_x - E}{R_1} + \frac{V_x}{R_3} + \frac{V_x}{R_2 + R_4} = 0$$


$$V_x \left[ \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2 + R_4} \right] = \frac{E}{R_1}$$

$$V_x = \frac{E}{R_1} \times \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2 + R_4}\right)}$$

$$\boxed{I = \frac{V_x}{R_2 + R_4}} \quad \frac{E}{I} = \left[ R_1 \left( \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2 + R_4} \right) (R_2 + R_4) \right] \quad \leftarrow (a)$$

$$\therefore \frac{E}{I} = \frac{E}{\left(\frac{V_x}{R_2 + R_4}\right)} = \frac{E}{V_x} (R_2 + R_4) = k_1$$

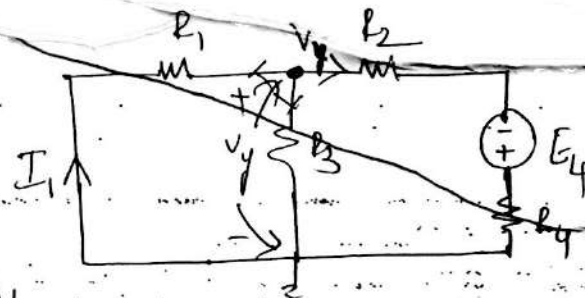Interchanging the positions of source and response



$$\frac{V_y}{R_1} + \frac{V_y}{R_3} + \frac{(V_y + E_4)}{R_2 + R_4} = 0$$

$$V_y \left[ \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2 + R_4} \right] = -\frac{E}{R_2 + R_4}$$

$$V_y = \frac{-E}{(R_2 + R_4)} \times \frac{1}{\left[\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2 + R_4}\right]}$$

$$I_1 = \frac{-V_y}{R_1} = - \frac{E}{R_1 (R_2 + R_4) \left[\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2 + R_4}\right]}$$


$$k_1 = \frac{E}{I_1} = (R_2 + R_4) R_1 \left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_2 + R_4}\right)$$

$$\Rightarrow k_1 = \frac{E}{I_1} = \frac{E}{I_1}$$

eqn (a) = eqn (b)

∴ Reciprocity theorem is verified.

8) Verify reciprocity theorem

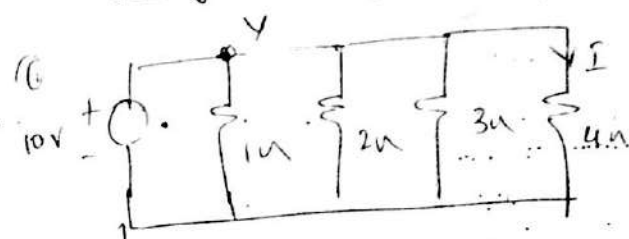


Sol:  $V = 10V$  — excitation (a) if.

$$I = \frac{V}{4} \text{ — response (a) if.}$$

$$I = \frac{10}{4} = \frac{5}{2} = 2.5 \text{ Amperes}$$

$$\frac{I}{V} = \frac{2.5}{10} = 25V \leftarrow (a)$$


interchangeable if & o/p is

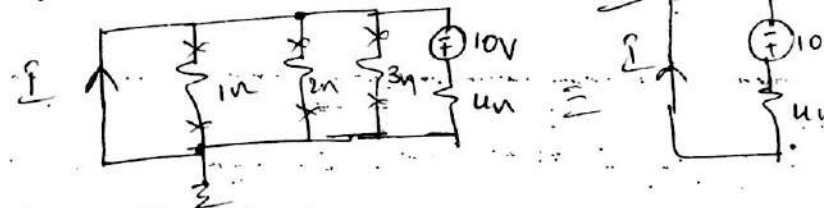

$$I = \frac{10}{4} = 2.5 \text{ Amperes}$$

$$\Rightarrow \frac{I}{V} = \frac{2.5}{10} = 25V \leftarrow (b)$$

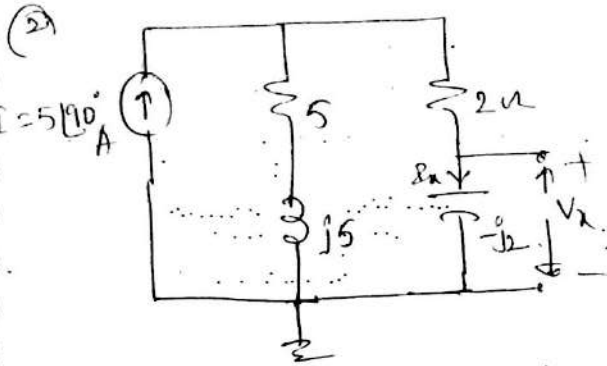eqn (a) = eqn (b) ∴ reciprocity theorem is verified.



Sol: i/p  $I = 5\angle 90^\circ$  A

o/p  $V_x \leftarrow$  w/o i/p

$$V_x = 2i_x \quad (i_x)$$

using BCM

$$I_x = 5\angle 90^\circ \left[ \frac{5 + j5}{(5 + j5)(2 - j2)} \right]$$

$$= 5\angle 90^\circ \times 0.9284 \angle 21.8014$$

$$I_x = 4.642 \angle 117.8014 \text{ Amp} \quad \checkmark$$

ratio of o/p to i/p  $\Rightarrow V_x = I_x [-j2]$


$$= 4.642 \angle 117.8014 \times [-j2] = 9.284 \angle 21.8014 \text{ volt}$$

$$\text{o/p } \boxed{V_x = 9.284 \angle 21.8014} \text{ volt}$$

ratio of o/p to i/p  $= \frac{V_x}{I} = \frac{9.284 \angle 21.8014}{5\angle 90^\circ}$

$$= 1.8568 \angle -68.198 \quad \checkmark \quad \text{a}$$

step interchange the i/p & o/p

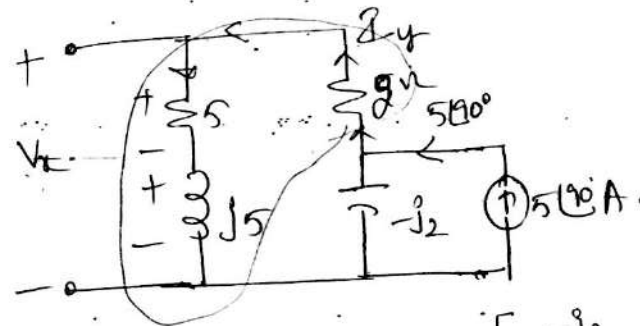

using VDR

$$I_y = 5\angle 90^\circ \left[ \frac{-j2}{(7 + j5)(j2)} \right]$$

$$= 5\angle 90^\circ \times 0.2626 \angle -113.139^\circ$$

$$I_y = 1.313 \angle -23.139^\circ \text{ Amp} \quad \checkmark$$

$$V_x = I_y [5 + j5] = 1.313 \angle -23.139^\circ [5 + j5]$$


$$V_x = 9.284 \angle 21.8014 \text{ volt}$$

$$\therefore \frac{V_x}{I} = \frac{9.284 \angle 21.8014}{5 \angle 90^\circ} = \frac{9.284 \angle 21.8}{5 \angle 90} \leftarrow (b)$$

$$= 1.8568 \angle -68.198$$

$$eqn (a) = eqn (b)$$

in AC circuit theorem is verified.

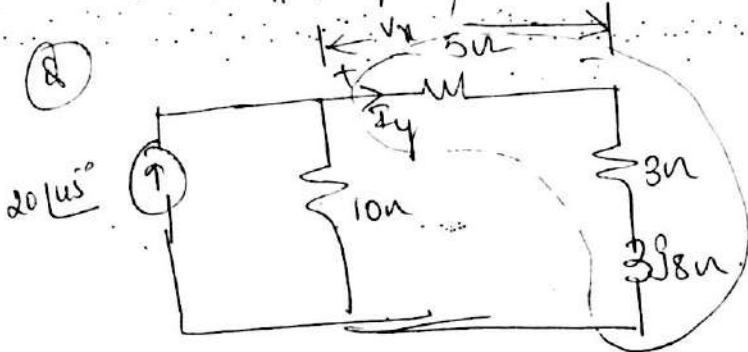

using VDR  $I = 20 \mu S \text{ A} \leftarrow \text{if}$

$$V_x = I_y \cdot 5 \text{ volt} \leftarrow \text{if}$$

$$I_y = 20 \mu S \left[ \frac{10}{10 + 5 + 3 + j8} \right]$$

$$= 20 \mu S \times 0.5076 \angle -23.96$$


$$I_y = 10.1534 \angle 21.037 \text{ Amperes}$$

$$V_x = I_y \times 5 = 50.767$$

$$V_x = 50.767 \angle 21.037 \text{ volt}$$

$$\frac{V_x}{I} = \frac{50.767 \angle 21.037}{20 \mu S} = 2.538 \angle -23.963 \leftarrow (a)$$

step 2 interchange if to if

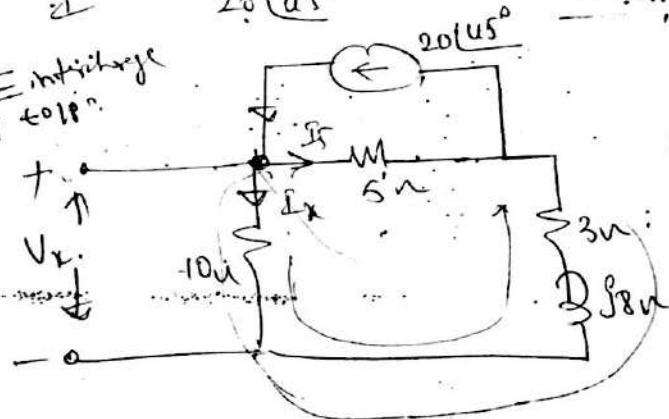

$$V_x = I_x \times 10 \text{ volt}$$

using VDR  $I_x = 20 \mu S \left[ \frac{5}{5 + 10 + 3 + j8} \right]$

$$= 20 \mu S \times 0.2538 \angle -23.962$$

$$I_x = 5.0767 \angle 21.037 \text{ Amperes}$$

$$V_x = 10 I_x = 10 \times 5.0767 \angle 21.037$$

$$V_x = 50.767 \angle 21.037 \text{ volt}$$


$$\frac{V_x}{I} = 2.538 \angle -23.963 \leftarrow (b) \quad eqn (a) = eqn (b) \text{ reciprocal theorem}$$

## Millman's theorem (Parallel generator theorem)
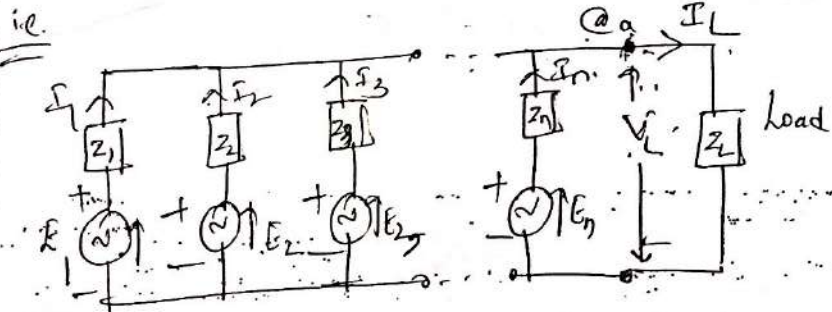
### Statement

When ever a set of practical voltage sources working in parallel feeding into a common load; A common terminal voltage of the combination is given by

$$V = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3 + \dots + E_n Y_n}{Y_1 + Y_2 + Y_3 + \dots + Y_n + Y_L}$$



At node 'a'  $I_1 + I_2 + I_3 + \dots + I_n = I_L$

$$\left(\frac{E_1 - V}{Z_1}\right) + \left(\frac{E_2 - V}{Z_2}\right) + \left(\frac{E_3 - V}{Z_3}\right) + \dots + \left(\frac{E_n - V}{Z_n}\right) = \frac{V}{Z_L}$$

$$(E_1 - V) Y_1 + (E_2 - V) Y_2 + (E_3 - V) Y_3 + \dots + (E_n - V) Y_n = V Y_L$$

$$E_1 Y_1 + E_2 Y_2 + E_3 Y_3 + \dots + E_n Y_n - V(Y_1 + Y_2 + Y_3 + \dots + Y_n) = V Y_L$$

$$E_1 Y_1 + E_2 Y_2 + E_3 Y_3 + \dots + E_n Y_n = V[Y_1 + Y_2 + Y_3 + \dots + Y_n + Y_L]$$

$$V_L = \frac{E_1 Y_1 + E_2 Y_2 + \dots + E_n Y_n}{Y_1 + Y_2 + Y_3 + \dots + Y_n + Y_L} \text{ volt}$$



note: if  $Y_L = 0$

ie. No-load with  $Y_L = 0$ .

$$V_{\text{No-load}} = \frac{E_1 Y_1 + E_2 Y_2 + \dots + E_n Y_n}{Y_1 + Y_2 + Y_3 + \dots + Y_n} \quad Y_L = 0$$

note: In the above case if the polarity of the source  $E_2$  are reverse then  $E_2$  is replaced by  $-E_2$  in the expression of  $V_L$ .

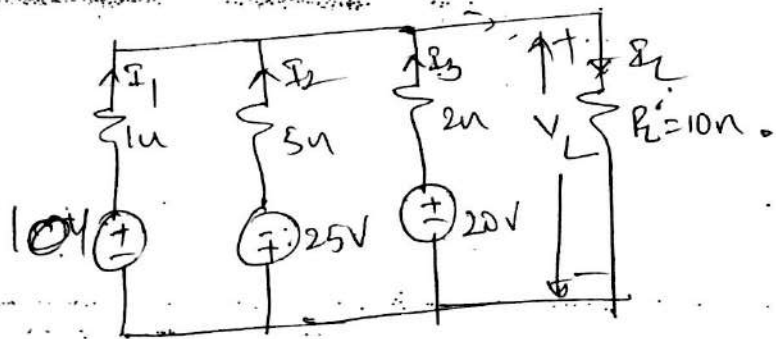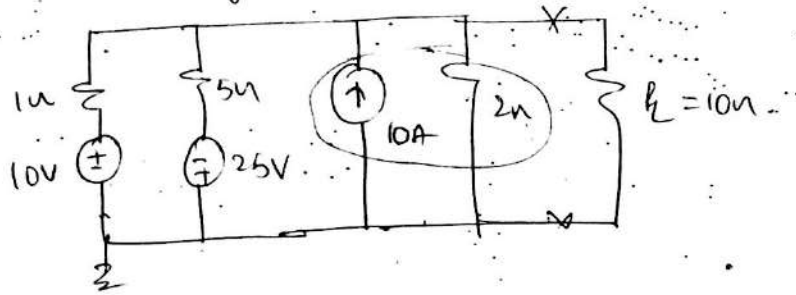8) Find the power delivered by the load resistance  $R_L$  and current supplied by each source in the ckt shown using millman's theorem.



$$V_L = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3}{Y_1 + Y_2 + Y_3 + Y_L}$$

$$= \frac{10(\frac{1}{1}) + (-25)(\frac{1}{5}) + 20(\frac{1}{2})}{(\frac{1}{1}) + (\frac{1}{5}) + (\frac{1}{2}) + (\frac{1}{10})} = 8.33 \text{ volts}$$

$$P_{R_L} = \frac{V^2}{R_L} = \frac{(8.33)^2}{10} = \underline{\underline{6.944 \text{ W}}}$$

$$I_1 = \frac{E_1 - V}{R_1} = \frac{10 - 8.33}{1} = \underline{\underline{1.67 \text{ A}}}$$

$$I_2 = \frac{E_2 - V}{R_2} = \frac{-25 - 8.33}{5} = \underline{\underline{-6.66 \text{ A}}}$$

$$I_3 = \frac{E_3 - V}{R_3} = \frac{20 - 8.333}{2} = \underline{\underline{5.835 \text{ A}}}$$

check

$$I_L = \frac{V}{R_L} = \frac{8.333}{10} = \underline{\underline{0.833 \text{ A}}}$$



$$= I_1 + I_2 + I_3$$

$$I_L = I_1 + I_2 + I_3$$

The Homogeneity principle


of in the principle obeyed by the all linear n/w's.

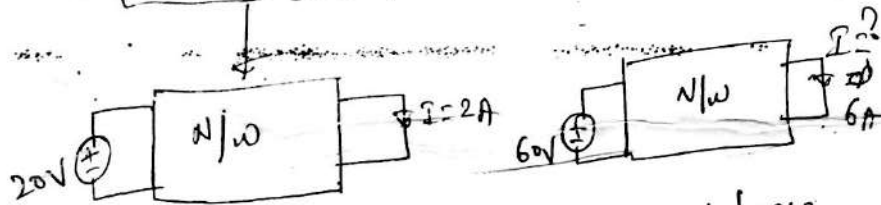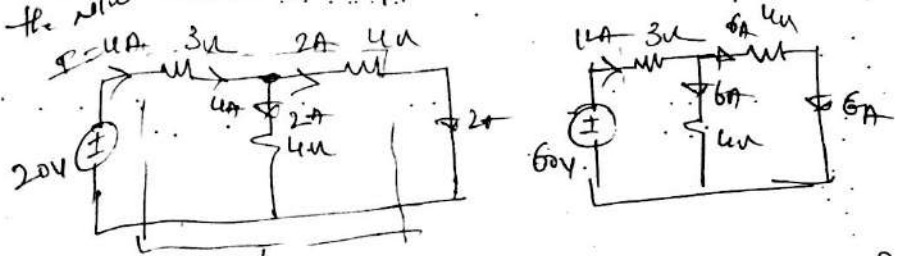Defn - In a linear n/w if the excitation is multiplied with a constant (k) then the response in all the other branches of the n/w are also multiplied with the same constant (k).



→ So, here the excitation is  $\times 3$  and hence in the responses also.

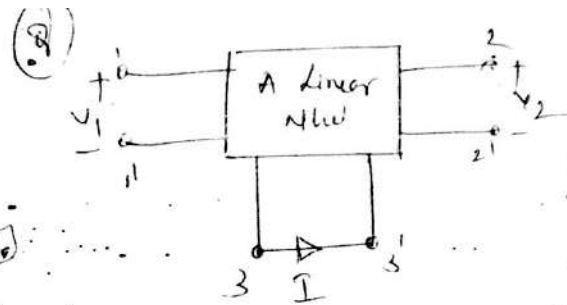Note: When Multiple sources are present then the SPT is applied first and later the homogeneity principle.



$V_1$	$V_2$	$I$
2V	0V	0.5A
0V	5V	-1A

If  $V_1 = 10V$  and  $V_2 = -5V$  then  $I = ?$

Solu: Using SPT  $I = k_1 V_1 + k_2 V_2$

~~2V 0.5A~~  $0.5 = k_1(2) \Rightarrow k_1 = 0.25$

$k_2(5) = -1 \Rightarrow k_2 = -1/5$

$\Rightarrow I = k_1 V_1 + k_2 V_2$

$I = 0.25 V_1 - 1/5 V_2$

$I = 0.25(10) - 1/5(-5)$

$= \frac{10}{4} + 1 = 2.5 + 1 = 3.5$

$I = 3.5$  Amps

(8) In the ckt shown


i)  $I_3 = 1.5A$  when  $V_a = 20V$  and  $V_b = 0$ . Find  $I_3 = ?$   
 $V_a = 50V + V_b = 0$

Find  $I_3$

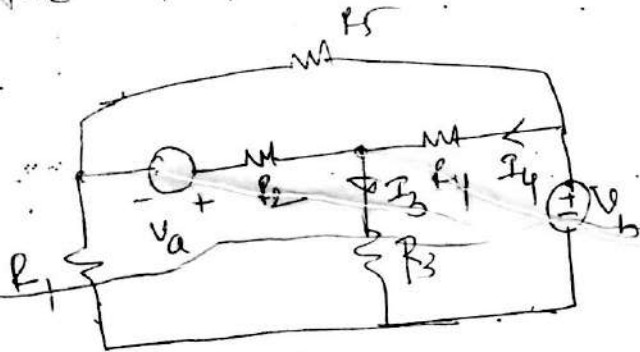ii)  $I_4 = 2A$  when  $V_a = 20V$  and  $V_b = 50V$

~~$I_4 = -1$  when  $V_a = 50V + V_b = 20V$~~

Find  $I_4$  if  $V_a = 30V$  &  $V_b = 100V$



Soln: using SPT

(1)

$$I_3 = k_1 V_a + k_2 V_b$$

given  $I_3 = 1.5A$ ;  $V_a = 20 + V_b = 0$

$$1.5 = k_1(20) + k_2(0)$$

$$\Rightarrow k_1 = \frac{1.5}{20} = \frac{15}{200} = 0.075$$

$\Rightarrow V_a = 50V$ ;  $V_b = 20V$   $I_3 = ?$

$$I_3 = k_1 V_a + k_2 V_b$$

$$I_3 = 0.075(50) + k_2(20) = \underline{\underline{3.75A}}$$

10

(9)

$$I_4 = k_3 V_a + k_4 V_b$$

$$\text{① } 2 = k_3(20) + k_4(50)$$

$$-1 = k_3(50) + k_4(20)$$

$$k_3 = -0.0428, \quad k_4 = 0.05714$$

$$\Rightarrow I_4 = k_3 V_a + k_4 V_b$$

$$I_4 = -0.0428 V_a + 0.05714 V_b$$

$$= -0.0428(30) + 0.05714(100)$$

$$\boxed{I_4 = 1.043A}$$



## Module 1: Basic Circuit Concepts

**Network:** Any interconnection of network or circuit elements (R, L, C, Voltage and Current sources).

**Circuit:** Interconnection of network or circuit elements in such a way that a closed path is formed and an electric current flows in it.

**Active Circuit elements** deliver the energy to the network (Voltage and Current sources)

**Passive Circuit elements** absorb the energy from the network (R, L and C).

**Active elements:**

**Ideal Voltage Source** is that energy source whose terminal voltage remains constant regardless of the value of the terminal current that flows. Fig.1a shows the representation of Ideal voltage source and Fig.1b, it's V-I characteristics.

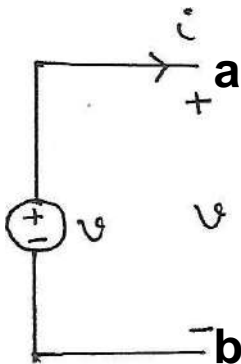


Fig.1a: Ideal Voltage source Representation

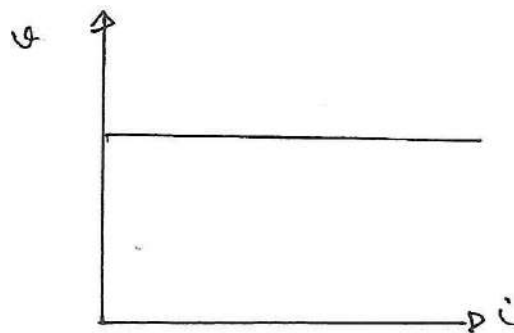


Fig. 1b: V-I characteristics

**Practical Voltage source:** is that energy source whose terminal voltage decreases with the increase in the current that flows through it. The practical voltage source is represented by an ideal voltage source and a series resistance called internal resistance. It is because of this resistance there will be potential drop **within the source and with the increase in terminal current or load current, the drop across resistor increases, thus**

reducing the terminal voltage. Fig.2a shows the representation of practical voltage source and Fig.2b, it's V-I characteristics.

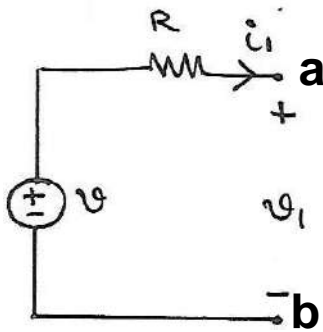


Fig. 2a: Practical Current Source

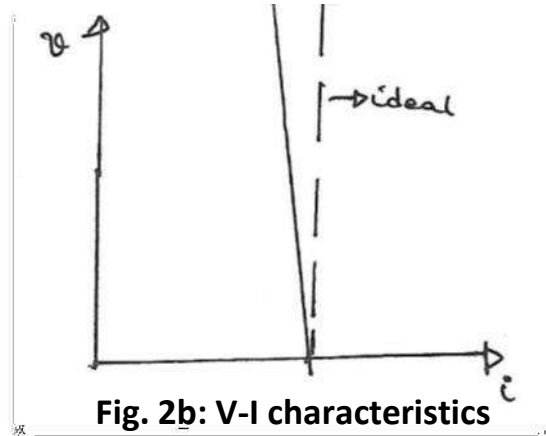


Fig. 2b: V-I characteristics

Here,  $i_1 = i - v_1/R$  ..... (2)

**Dependent or Controlled Sources:** These are the sources whose voltage/current depends on voltage or current that appears at some other location of the network. We may observe 4 types of dependent sources.

- i) Voltage Controlled Voltage Source (VCVS)
- ii) Voltage Controlled Current Source (VCCS)
- iii) Current Controlled Voltage Source (CCVS)
- iv) Current Controlled Current Source (CCCS)

Fig.3a, 3b, 3c and 3d represent the above sources in the same order as listed.

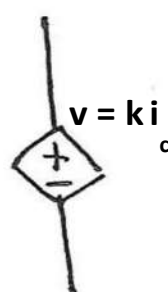
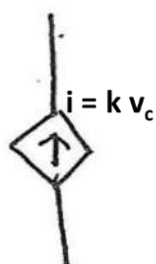
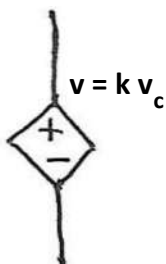


Fig. 3 a) VCVS


b) VCCS

c) CCVS

d) CCCS

### Kirchhoff's Voltage Law (KVL)

It states that algebraic sum of all branch voltages around any closed path of the network is equal to zero at all instants of time. Based on the law of conservation of energy.

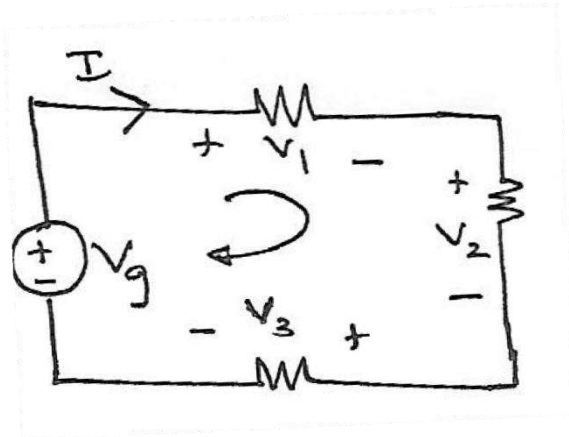

**Fig. 4: Example illustrating KVL**


Applying KVL clockwise,  $+V_1 + V_2 + V_3 - V_g = 0$  ..... (3)

$\Rightarrow V_g = V_1 + V_2 + V_3$  ..... (4), indicative of energy delivered

= energy absorbed

### Kirchhoff's Current Law (KCL)

The algebraic sum of branch currents that leave a node of a network is equal to zero at all instants of time. Based on the law of conservation of charge.

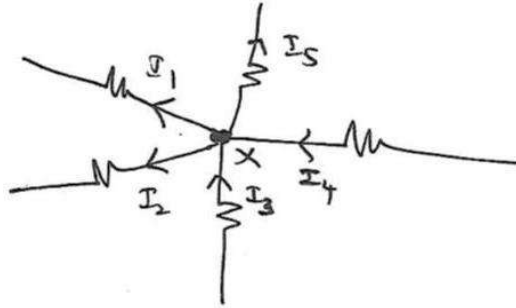

**Fig. 5: Example illustrating KCL**

Applying KCL at node X,  $+ I_1 + I_2 - I_3 - I_4 + I_5 = 0$  ..... (5)


=>  $I_3 + I_4 = I_1 + I_2 + I_5$  ..... (6), indicative of sum of incoming currents

= sum of outgoing currents at a node.


**Source Transformation**

Source Transformation involves the transformation of voltage source to its equivalent current source and vice-versa.

Consider a voltage source with a series resistance R, in Fig. 6a and a current source with the same resistance R connected across, in Fig.6b.

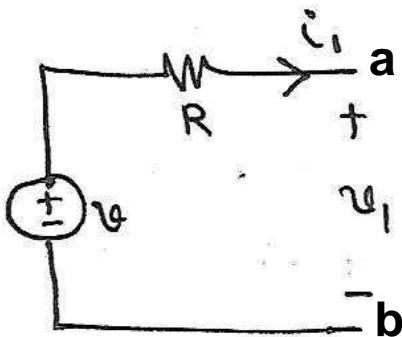

**Fig.6a Voltage Source**

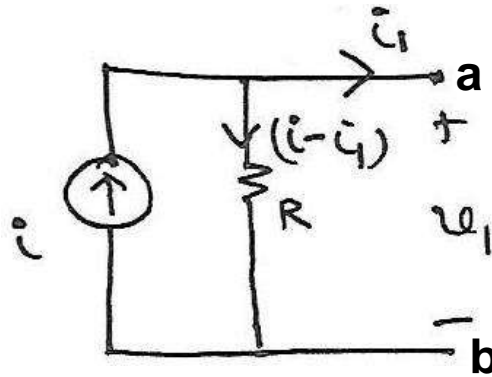

**Fig.6b Current Source**

The terminal voltage and current relationship in the case of voltage source is;

$$v_1 = v - i_1 R \text{ ..... (7)}$$

The terminal voltage and current relationship in the case of current source is;

$$i_1 = i - v_1 / R, \text{ which can be written as, } v_1 = i R - i_1 R \dots\dots (8)$$

If the voltage source above has to be equivalently transformed to or represented by, a current source then the terminal voltages and currents have to be same in both cases.

This means eqn. (7) should be equal to eqn. (8). This implies,  $v = i R$  or  $i = v / R \dots(9)$ . If eqn.(9) holds good, then the voltage source above can be equivalently transformed to or represented by, the current source shown above and vice-versa.

### Problems:

- 1) For the network shown below in Fig.7, find the current through  $2\Omega$  resistor, using source transformation technique.



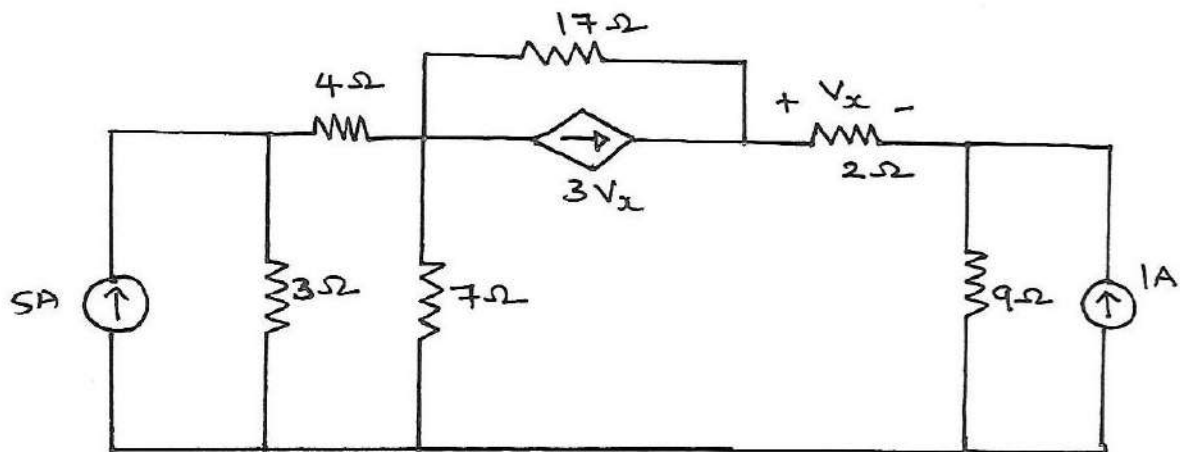


Fig.7

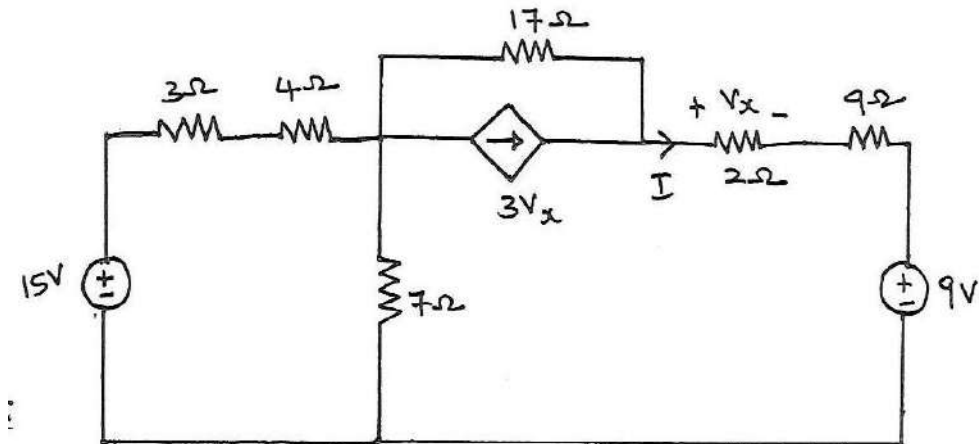
**Solution:** In the given circuit, Converting 5A source to voltage source so that resistor  $4\Omega$  comes in series with source resistor  $3\Omega$  and equivalent of them can be found. Also converting 1A source to voltage source, we obtain the circuit as below;



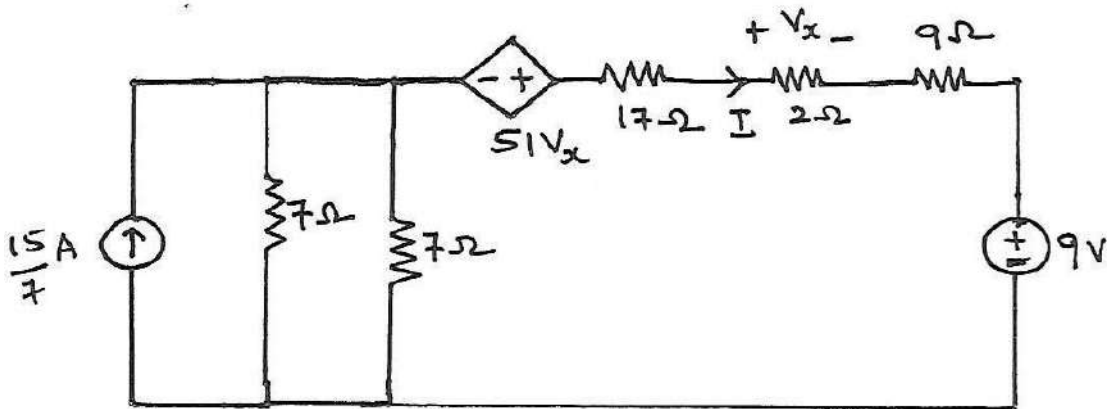Converting 15V source above to current source and converting  $3V_x$  dependent current source to dependent voltage source, we get the following;



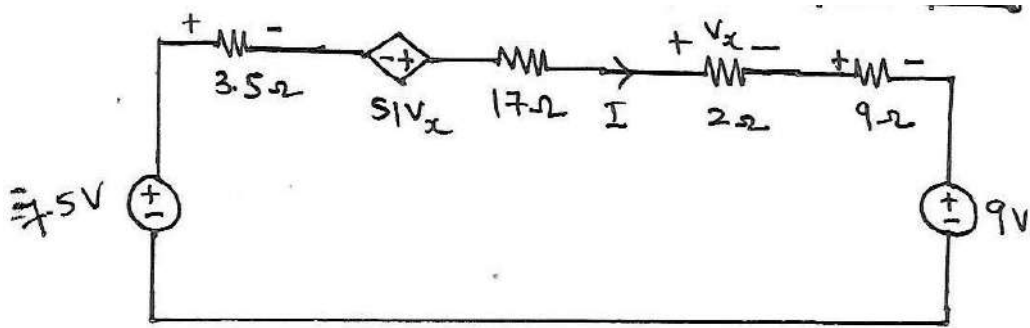Taking equivalent of the parallel combination of  $7\Omega$  resistors and converting  $15/7$  A current source to voltage source, we get as shown below;



Applying KVL to the loop above clockwise, we get;

$$3.5 I - 5I V_x + 17 I + 2I + 9I + 9 - 7.5 = 0$$

From the circuit above,  $V_x = 2I$ , substitute in above eqn, then we get;

$$-70.5 I = -1.5$$

$$\Rightarrow I = 0.02127 \text{ A} = 21.27 \text{ mA}$$

- 2) Represent the network shown below in Fig.8, by a single voltage source in series with a resistance between the terminals A and B, using source transformation techniques


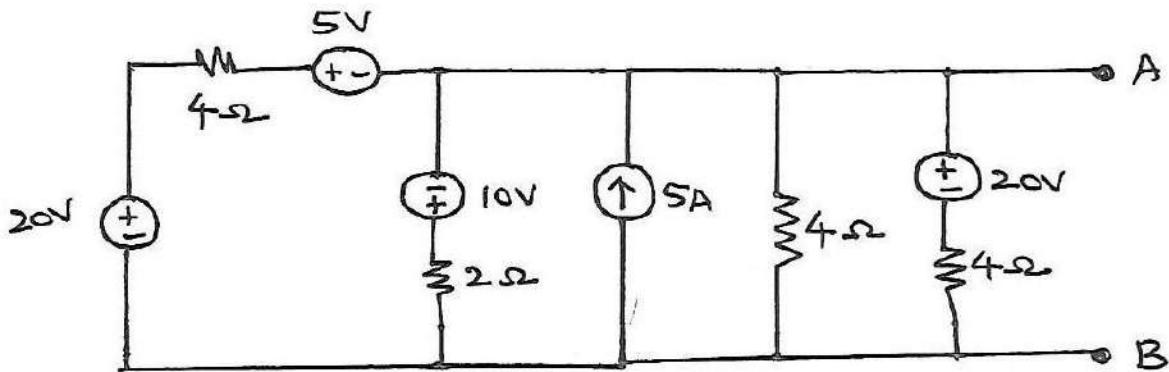


Fig.8

**Solution:** In the circuit above, 5V and 20 V sources are present in series arm and they are series opposing.

So, the sources are replaced by single voltage source which is the difference of two (as they are opposing, if series aiding then sum has to be considered). The polarity of the resulting voltage source will have same as that of higher value voltage source. Multiple current sources in parallel, can be added if they are in same direction and if they are in opposite direction, then difference is taken and resulting source will have same direction as that of higher one.

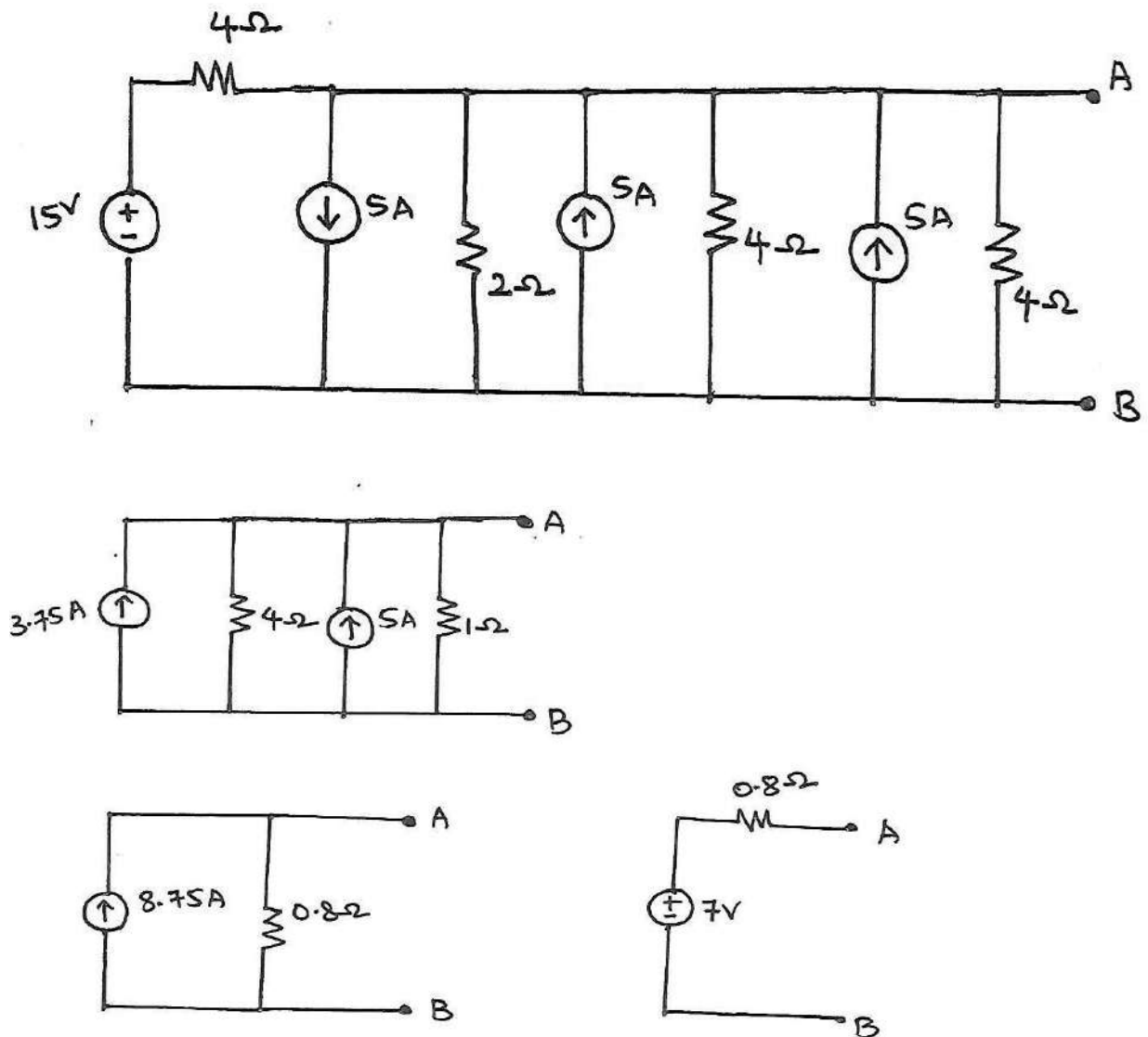Taking source transformation, such that we get all current sources in parallel and all resistances in parallel, between the terminals. This leads to finding of equivalent current source and equivalent resistance between A-B. The source transformation leads to single voltage source in series with a resistance. These are shown below;





### Illustration of Mesh Analysis:

3) Find the mesh currents in the network shown in fig.9

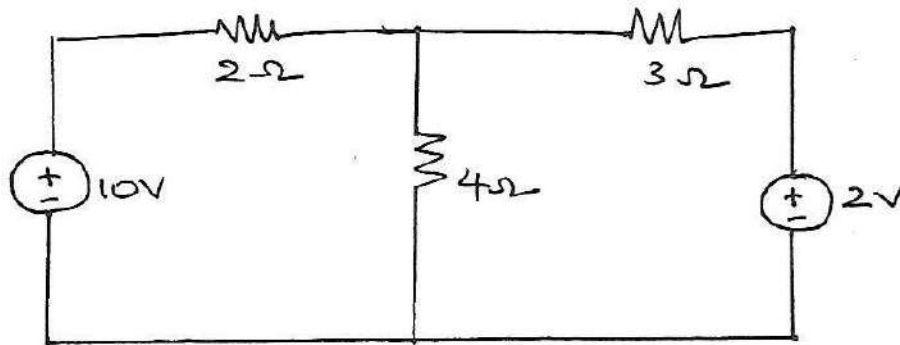



Fig.9

We identify two meshes; 10V-2 $\Omega$ -4  $\Omega$  called as mesh 1 and 3 $\Omega$ -2V-4  $\Omega$  called as mesh2. We consider  $i_1$  to flow in mesh1 and  $i_2$  to flow in mesh2. Their directions are always considered to be clockwise. If they are in opposite direction in actual, we get negative values when we calculate them, indicative of actual direction to be opposite.

10V-2 $\Omega$  branch only belongs to mesh1 and so current through it is  $i_1$  and 3 $\Omega$ -2V branch only belongs to mesh2 and so current through it is always  $i_2$ . Also, 4 $\Omega$  belongs to both meshes and so, the current through it will be the resultant of  $i_1$  and  $i_2$ . These are shown below;

Next we will apply KVL to each of the meshes; As a result, In this case, we get two equations in terms of  $i_1$  and  $i_2$  and when we solve them we get  $i_1$  and  $i_2$ . And when we know the mesh current values, we can find the response at any point of network.

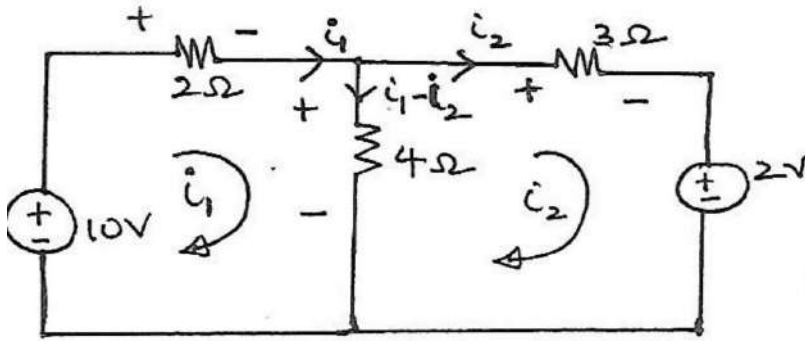The polarities of the potential drops across passive circuit elements are based on the directions of the current that flows through them



Applying KVL to mesh1;

$$+2 i_1 + 4 (i_1 - i_2) - 10 = 0$$

$$\Rightarrow +6 i_1 - 4 i_2 = 10 \dots\dots (1)$$

Applying KVL to mesh2;

$$+3 i_2 + 2 - 4 (i_1 - i_2) = 0$$

Above equation can be rewritten as

$$+3 i_2 + 2 + 4 (i_2 - i_1) = 0$$

$$\Rightarrow -4 i_1 + 7 i_2 = -2 \dots\dots (2)$$

Also observing the bold equations above, we may say that easily the potential drops across passive circuit elements can be considered to take +ve signs. From now onwards, we will not specifically identify polarities of potential drops across **passive circuit elements**. They are considered to take positive signs. For the case of shared element, like 4Ω above, which is shared between mesh1 and mesh2, the potential drop across it, is considered to be  $+4(i_1 - i_2)$ , when we apply KVL to mesh1 and  $+4(i_2 - i_1)$ , when we apply KVL to mesh2. Now eqn1 and eqn2 above can be represented in matrix form as shown;

$$\begin{bmatrix} 6 & -4 \\ -4 & 7 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 10 \\ -2 \end{bmatrix}$$

Using cramer's rule;

$$\Delta = \begin{vmatrix} 6 & -4 \\ -4 & 7 \end{vmatrix} = 26$$

$$\Delta i_1 = \begin{vmatrix} 10 & -4 \\ -2 & 7 \end{vmatrix} = 62$$

$$\Delta i_2 = \begin{vmatrix} 6 & 10 \\ -4 & -2 \end{vmatrix} = 28$$


$$\Rightarrow i_1 = \Delta i_1 / \Delta = 2.384 \text{ A}$$

$$\Rightarrow i_2 = \Delta i_2 / \Delta = 1.076 \text{ A}$$


As already told, if we know the mesh current values, we can find the response at any point of network. And so,  $V_x$  and  $I_x$  identified, can be easily obtained using the mesh currents.


$$I_x = -i_2 = -1.076 \text{ A}$$

$$V_x = 3i_2 = 3.228 \text{ A}$$

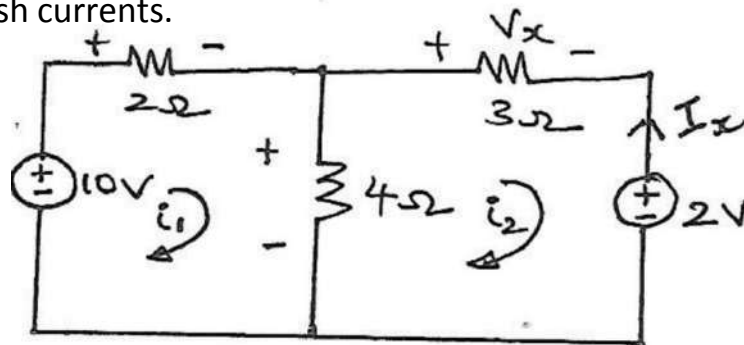

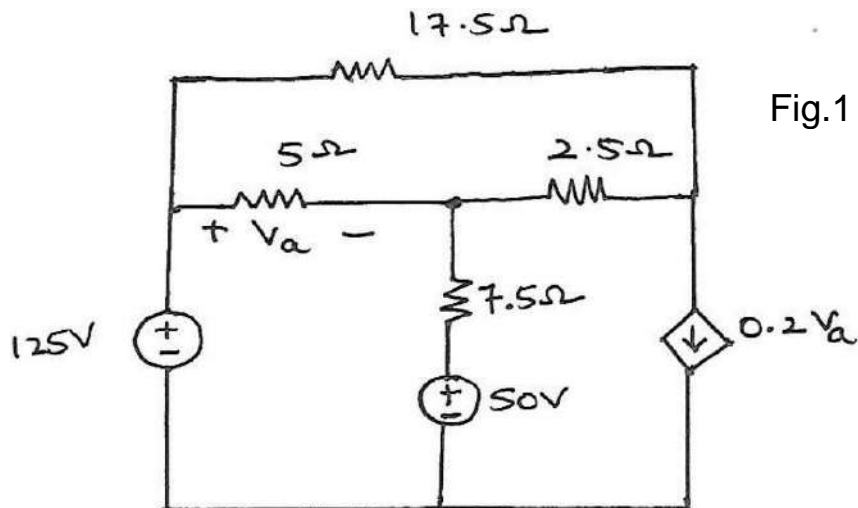- 4) Find the power delivered or absorbed by each of the sources shown in the network in Fig.10. Use mesh analysis



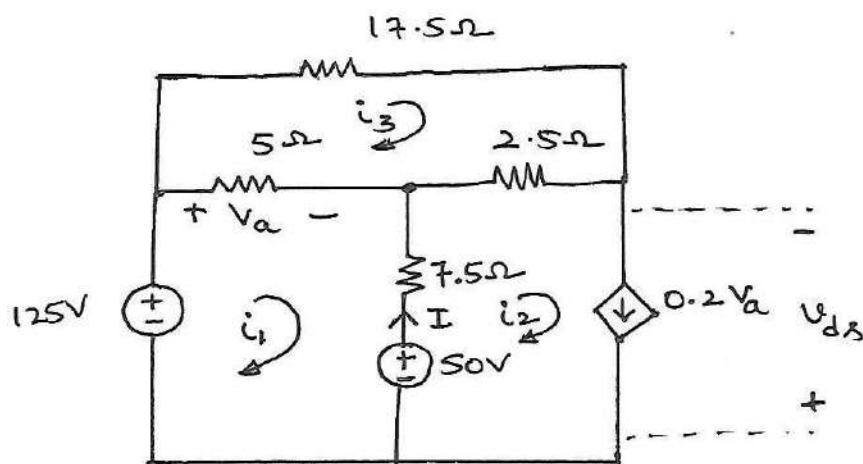

**Solution:-**

Power delivered by 125 V source,  $P_{125} = 125 i_1$

Power delivered by 50V source,  $P_{50} = 50 I = 50 (i_2 - i_1)$

**Power delvd. by dependent current source,  $P_{ds} = (0.2V_a) (v_{ds}) = (i_1 - i_3) (v_{ds})$**

**{Because  $V_a = 5 (i_1 - i_3)$ }**

From the circuit;  $V_a = 5 (i_1 - i_3)$

Also;  $i_2 = 0.2 V_a = i_1 - i_3$  (it is as good as specifying the value of  $i_2$  or we can say we have obtained equation from mesh2, so no need of applying KVL to mesh2)

Applying KVL to mesh1;

$$5 (i_1 - i_3) + 7.5(i_1 - i_2) + 50 - 125 = 0$$

$12.5 i_1 - 7.5 i_2 - 5 i_3 = 75$ ; substituting  $i_2 = i_1 - i_3$ ; we have;

$$5 i_1 + 2.5 i_3 = 125 \dots\dots (1)$$

Applying KVL to mesh3;

$$17.5 i_3 + 2.5 (i_3 - i_2) + 5(i_3 - i_1) = 0$$

$-5 i_1 - 2.5 i_2 + 25 i_3 = 0$ ; substituting  $i_2 = i_1 - i_3$ ; we have;

$$-7.5 i_1 + 27.5 i_3 = 0 \dots\dots (2)$$

Solving (1) and (2), we get;  $i_1=13.2$  A and  $i_3=3.6$  A

So,  $i_2=i_1 - i_3 = 13.2 - 3.6 = 9.6$  A

$$P_{125} = 125 i_1 = 125 (13.2) = 1650 \text{ W (power delivered)}$$

$P_{50} = 50 I = 50 (i_2 - i_1) = 50 (9.6 - 13.2) = -180$  W, here negative value of power delivered is the indicative of the fact that power is actually absorbed by 50V source.

To find  $v_{ds}$  in the network shown, we apply KVL to the outer loop  
 $17.5\Omega \rightarrow 0.2V_a \rightarrow 125V;$

$+17.5 i_3 - v_{ds} - 125 = 0$  {when **applying KVL, the potential drop across passive circuit element is taken as, + (resistance or impedance value) x (that particular current which is in alignment with KVL direction), if clockwise direction is considered, then clockwise current)}**

$$\Rightarrow v_{ds} = - 62V$$

$$P_{ds} = (0.2 V_a)(v_{ds}) = (i_1 - i_3) v_{ds} = - 595.2W \Rightarrow \text{Dependent source absorbs power of } 595.2 \text{ W}$$

- 5) Find the power delivered by dependent source in the network shown in Fig.11. Use mesh analysis


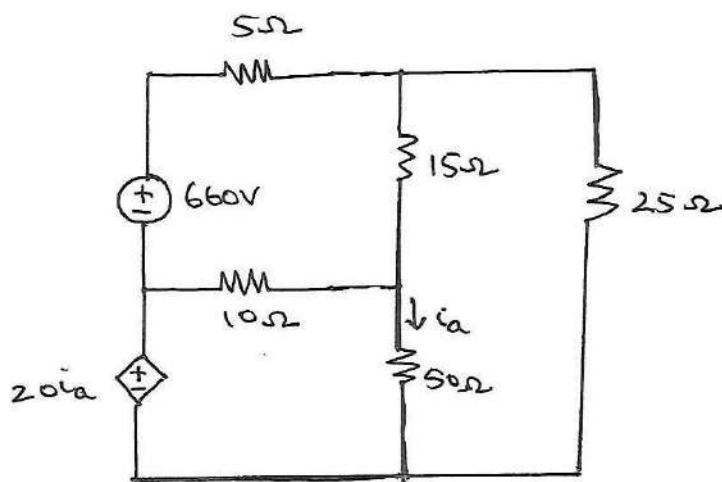


Fig.11

**Solution:-**

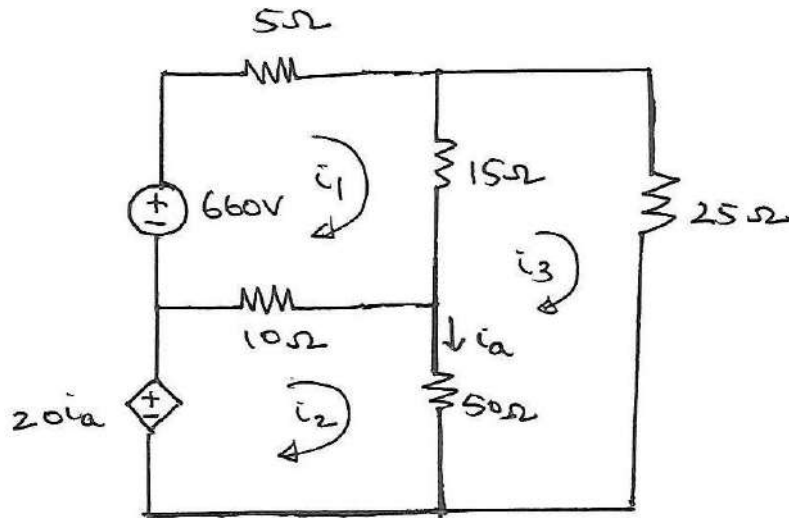

From the circuit,

$$i_a = i_2 - i_3$$

Power delivered by dependent source,  $P_{ds} = (20 i_a) (i_2) = 20 (i_2 - i_3) i_2$

**Apply KVL to mesh1**

$$5 i_1 + 15 (i_1 - i_3) + 10 (i_1 - i_2) - 660 = 0$$

$$30 i_1 - 10 i_2 - 15 i_3 = 660 \dots\dots (1)$$

**Apply KVL to mesh2**

$$10 (i_2 - i_1) + 50 (i_2 - i_3) - 20 i_a = 0$$

$$10 (i_2 - i_1) + 50 (i_2 - i_3) - 20 (i_2 - i_3)$$

$$-10 i_1 + 40 i_2 - 30 i_3 = 0 \dots\dots (2)$$

**Apply KVL to mesh3**

$$25 i_3 + 50 (i_3 - i_2) + 15 (i_3 - i_1) = 0$$

$$-15 i_1 - 50 i_2 + 90 i_3 = 0 \dots\dots (3)$$

**Solving (1), (2) and (3), we get  $i_2 = 27$  A and  $i_3 = 22$  A**

**$P_{ds} = (20) (i_2 - i_3) i_2 = 20(5)27 = 2700$ W, power delivered.**

## AC Circuits

These circuits consist L and C components along with R. Here we consider the excitation of the circuits by sinusoidal sources. Consider an AC circuit shown below;

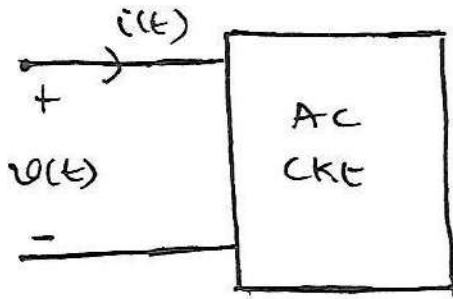


Fig.12

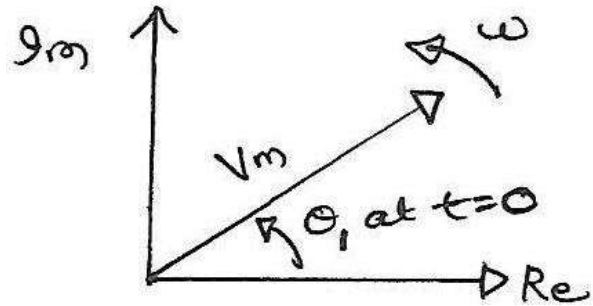


Fig.13

Let the applied voltage,  $v(t) = V_m \sin(\omega t + \theta_1)$ , the circuit current that flows is  $i(t)$  and is given as;  $i(t) = I_m \sin(\omega t + \theta_2)$ . These two sinusoidal quantities can be represented by phasors; a phasor is a rotating vector in the complex plane. This is shown in Fig.13, which is a voltage phasor. The phasor has a magnitude of  $V_m$  and rotates at an angular frequency of  $\omega$  with time.

The voltage phasor is given by  $V_m \angle \theta_1$  (Also referred as polar form of phasor). The rectangular form is  $V_m \cos \theta_1 + j V_m \sin \theta_1$ .

Similarly, the current phasor is given by  $I_m \angle \theta_2$  (Also referred as polar form of phasor). The rectangular form is  $I_m \cos \theta_2 + j I_m \sin \theta_2$ .

The ratio of voltage phasor to the current phasor is called as impedance.  $Z = (V_m \angle \theta_1) / (I_m \angle \theta_2) = (V_m/I_m) \angle (\theta_1 - \theta_2) = (V_m/I_m) \angle \theta$

The impedance although a complex quantity but is not a phasor, as with respect to time, the angle of impedance do not change

- If the AC circuit above is represented equivalently by single resistance, then  $Z = (V_m \angle \theta_1) / (I_m \angle \theta_1)$  {since in resistance there is no phase difference between voltage and current and so  $\theta_2 = \theta_1$ }.

So,  $Z = (V_m/I_m) \angle 0^\circ$

$$= (V_m/I_m) \cos 0^\circ + j (V_m/I_m) \sin 0^\circ$$

$$= V_m/I_m = R.$$

- If the AC circuit above is represented equivalently by single inductance, then  $Z = (V_m \angle \theta_1) / (I_m \angle (\theta_1 - 90^\circ))$  { since in inductance, current lags the voltage in phase by  $90^\circ$  }

$$\text{So, } Z = (V_m/I_m) \angle 90^\circ$$

$$= (V_m/I_m) \cos 90^\circ + j (V_m/I_m) \sin 90^\circ$$

$$= j (V_m/I_m)$$

$= j\omega L$  {in inductance, the ratio of peak value of voltage to peak value of current is always the reactance which is given by  $\omega L$ }. Now we can say, any inductance of  $L$  henry can be equivalently represented by impedance of  $j\omega L$  Ohms.

- If the AC circuit above is represented equivalently by single capacitance, then  $Z = (V_m \angle \theta_1) / (I_m \angle (\theta_1 + 90^\circ))$  { since in capacitance, current leads the voltage in phase by  $90^\circ$  }

$$\text{So, } Z = (V_m/I_m) \angle -90^\circ$$

$$= (V_m/I_m) \cos 90^\circ - j (V_m/I_m) \sin 90^\circ$$

$$= -j (V_m/I_m)$$

$$= -j(1/\omega C)$$

$= -j/\omega C$  {in capacitance, the ratio of peak value of voltage to peak value of current is always the reactance which is given by  $1/\omega c$ . Now we can say, any capacitance of  $C$  farad can be equivalently represented by impedance of  $-j/ \omega C$  Ohms.



- 6) Find the current through the capacitor in the circuit shown in Fig.14.  
Use mesh Analysis.


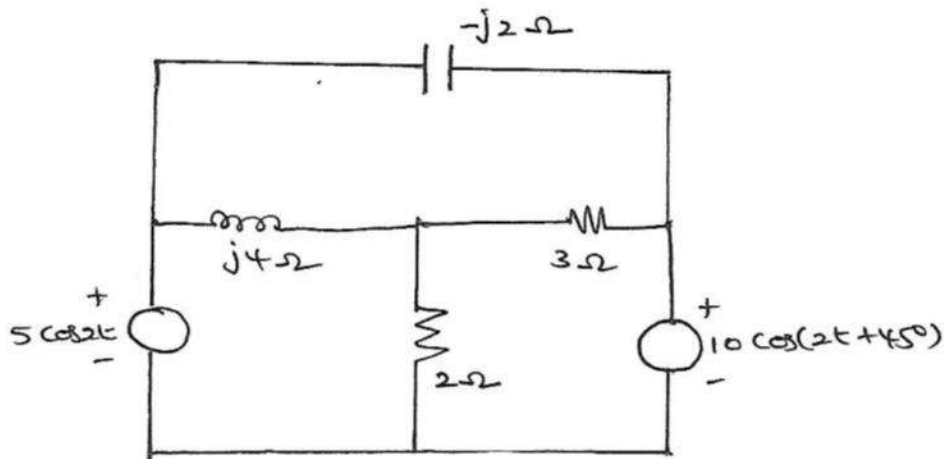


Fig.14

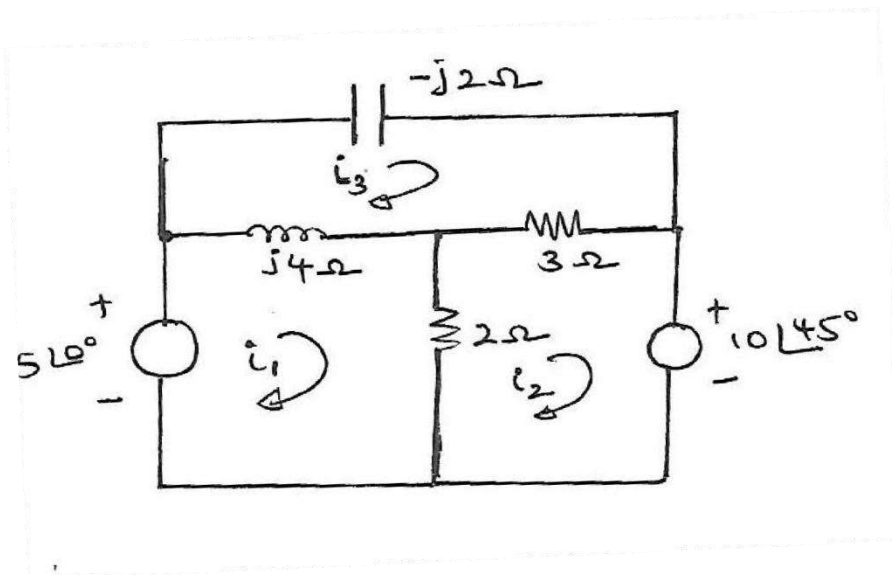**Solution:**

The sources are represented by phasors. The mesh currents are identified. The current through the capacitor is  $i_3$ . So,  $i_3$  needs to be found using mesh analysis.



Apply KVL to mesh1;

$$j4 (i_1 - i_3) + 2 (i_1 - i_2) - (5 \angle 0^\circ) = 0$$

$$(2+j4) i_1 - 2 i_2 - j4 i_3 = 5 \dots\dots(1)$$

Apply KVL to mesh2;

$$3 (i_2 - i_3) + (10 \angle 45^\circ) + 2 (i_2 - i_1) = 0$$

$$-2 i_1 + 5 i_2 - 3 i_3 = -(10 \angle 45^\circ) = -7.07 - j 7.07 \dots\dots(2)$$

Apply KVL to mesh3;

$$-j2 i_3 + 3 (i_3 - i_2) + j4 (i_3 - i_1) = 0$$

$$-j4 i_1 - 3 i_2 + (3+j2) i_3 = 0 \dots\dots (3)$$

Mesh equations in matrix form;

$$\begin{matrix} 2+j4 & -2 & -j4 & i_1 \\ -2 & 5 & -3 & i_2 \\ -j4 & -3 & 3+j2 & i_3 \end{matrix} = \begin{matrix} 5 \\ -7.07 - j 7.07 \\ 0 \end{matrix}$$

Using Cramer's rule to find  $i_3$ .

$$\Delta = \begin{vmatrix} 2+j4 & -2 & -j4 \\ -2 & 5 & -3 \\ -j4 & -3 & 3+j2 \end{vmatrix}$$

$$= (2+j4)[5(3+j2)-9] + 2[-2(3+j2)- (-3)(-j4)] -j4[6+j20]$$

$$= 40-j12$$

$$\Delta i_3 = \begin{vmatrix} 2+j4 & -2 & 5 \\ -2 & 5 & -7.07-j7.07 \end{vmatrix}$$

$-j4$        $-3$        $0$

$$\begin{aligned}
&= (2 + j4)[+3(-7.07 - j 7.07)] + 2[+j4(-7.07-j7.07)] + 5[6+ j 20] \\
&= 128.98 - j83.82
\end{aligned}$$

$$\begin{aligned}
\text{Therefore, } i_3 &= \Delta i_3 / \Delta = (128.98 - j83.82) / (40 - j12) \\
&= 3.535 - j1.035 \\
&= 3.68 \angle -16.31^\circ \text{ A.}
\end{aligned}$$

The above result represents the phasor of capacitor current. From this we can easily write the steady state expression of capacitor current, as,

$$i_3(t) = 3.68 \cos(2t - 16.31^\circ) \text{ A}$$

### **Node analysis**

Here, we identify nodes of the given network and consider one node as ground node, which is considered to be zero potential point. We then identify the voltage at each of the remaining nodes which is nothing but potential difference between a node of interest and ground node, with ground node as reference. Node analysis involves the computation of node voltages, and when once these are found, we can find the response at any point of network.

Illustration

7) Find the node voltages in the network shown in Fig.15;


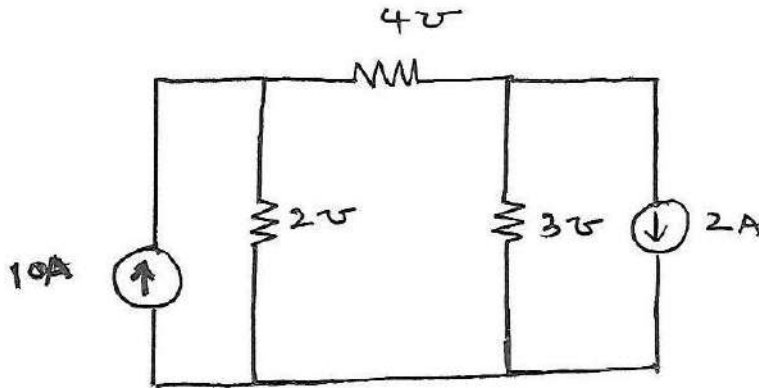


Fig.15

Solution:

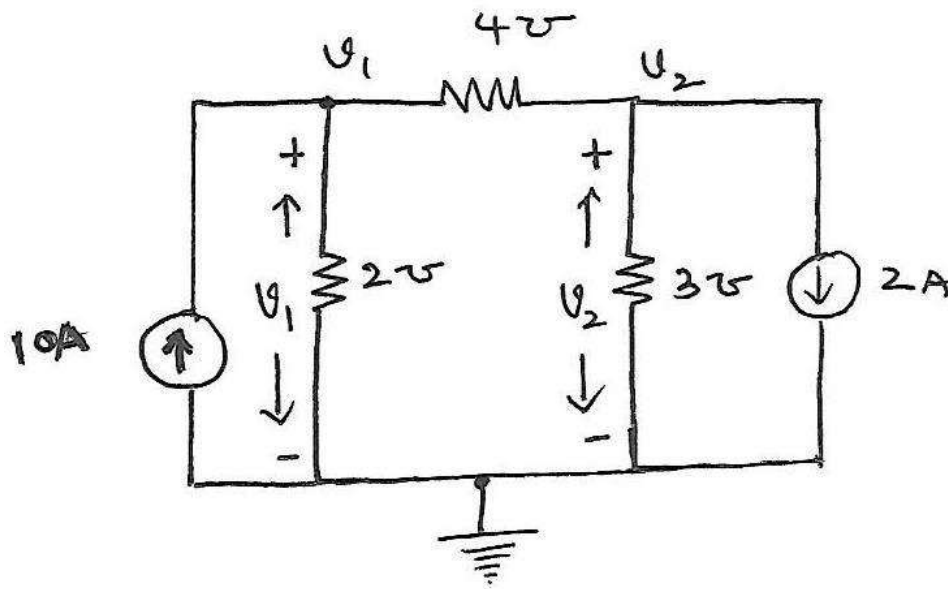There are 3 nodes in the network. The bottom node is selected as ground node. The voltage at node1 is identified as  $v_1$  and it is the potential difference between the node1 and the ground, with ground as reference. The voltage at node2 is identified as  $v_2$  and it is the potential difference between node2 and the ground, with ground as reference.



Recall KCL statement that “the algebraic sum of branch currents leaving a node of a network is zero at all instants of time”.

Apply KCL at node1;

$$-10 + 2v_1 + 4(v_1 - v_2) = 0$$

$$\Rightarrow 6v_1 - 4v_2 = 10 \dots\dots(1)$$

Apply KCL at node2;

$$+4(v_2 - v_1) + 3v_2 + 2 = 0$$

$$\Rightarrow -4v_1 + 7v_2 = -2 \dots\dots(2)$$

Node equations in Matrix form

$$\begin{pmatrix} 6 & -4 \\ -4 & 7 \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \end{pmatrix} = \begin{pmatrix} 10 \\ -2 \end{pmatrix}$$

Using Cramer’s rule;

$$\Delta = \begin{vmatrix} 6 & -4 \\ -4 & 7 \end{vmatrix} = 26$$

$$\Delta v_1 = \begin{vmatrix} 10 & -4 \\ -2 & 7 \end{vmatrix} = 62$$

$$\Delta v_2 = \begin{vmatrix} 6 & 10 \\ -4 & -2 \end{vmatrix} = 28$$

$$v_1 = \Delta v_1 / \Delta = 62/26$$

$$v_1 = 2.384V$$

$$v_2 = \Delta v_2 / \Delta = 28/26$$

$$v_2 = 1.076V$$

### Node Analysis Contd.

8) Use Node analysis to find the voltage  $V_x$  in the circuit shown in Fig.

16


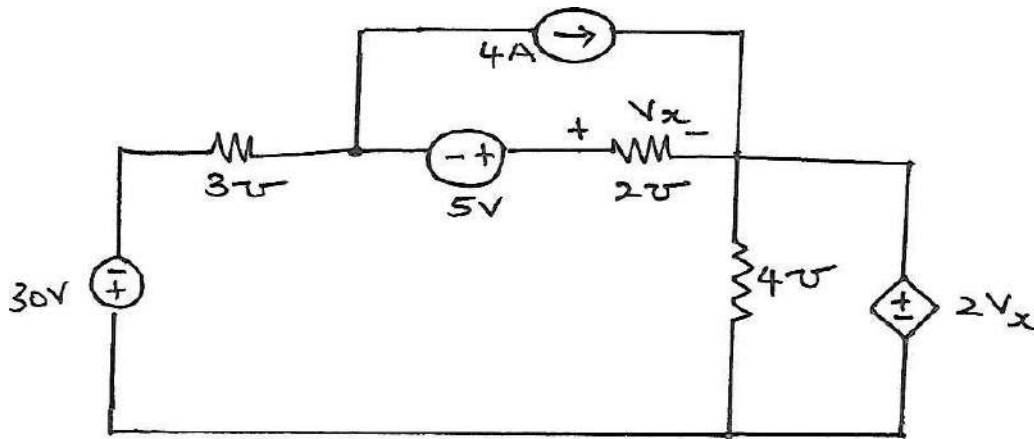


Fig.16

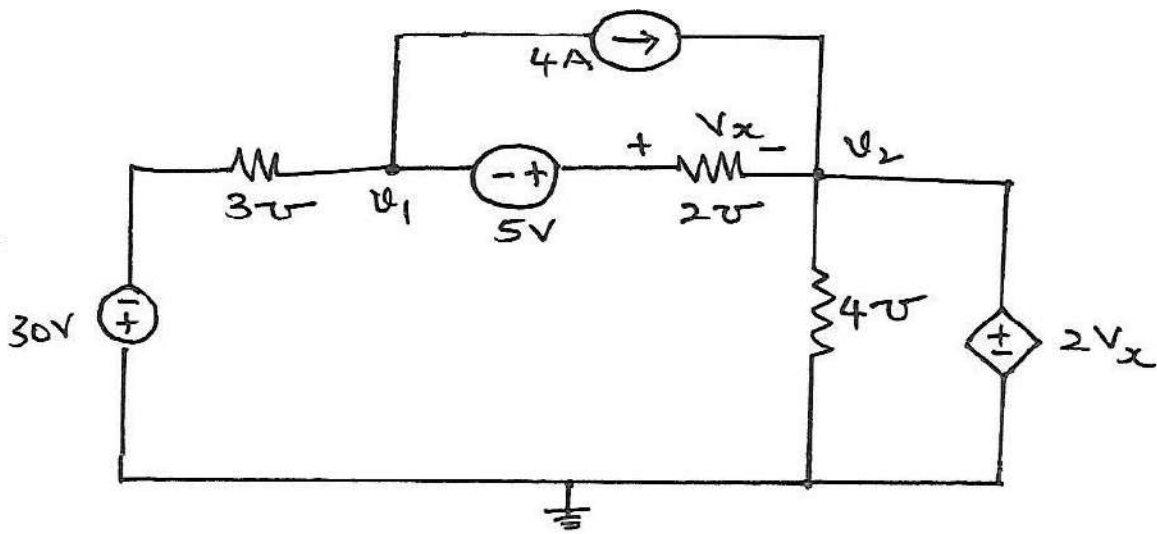The ground node and other nodes with their voltages are identified as shown;



Although that point where two circuit elements join is referred as node (like 30V and 3 mho joining point above), we do not consider voltage there or apply KCL, because it will simply contribute for redundancy, as without considering the above, still the solution can be obtained. Therefore, we consider voltages or apply KCL to those nodes where three or more circuit elements join.

From the circuit;  $V_x = v_1 + 5 - v_2$  and  $v_2 = 2V_x$

$$v_2 = 2 (v_1 + 5 - v_2)$$

$\Rightarrow 2 v_1 - 3 v_2 = -10$  ..... (1), now we have an equation expressing  $v_2$  or an equation associated with node 2. So no need of applying KCL at node2.

$\Rightarrow$  Apply KCL at node1;

$$3 (v_1 - (-30)) + 4 + 2( v_1 + 5 - v_2) = 0$$

$$\Rightarrow 5 v_1 - 2 v_2 = -104$$
 ..... (2)

$\Rightarrow$  Solving (1) and (2), we get;

$$\Rightarrow v_1 = -26.545V \text{ and } v_2 = -14.363V$$

$\Rightarrow$  Therefore,  $V_x = v_1 + 5 - v_2$

$$\Rightarrow -26.545 + 5 + 14.363 = -7.182 \text{ V.}$$

9) Find the power delivered by dependent source using node analysis in the circuit shown in Fig. 17.


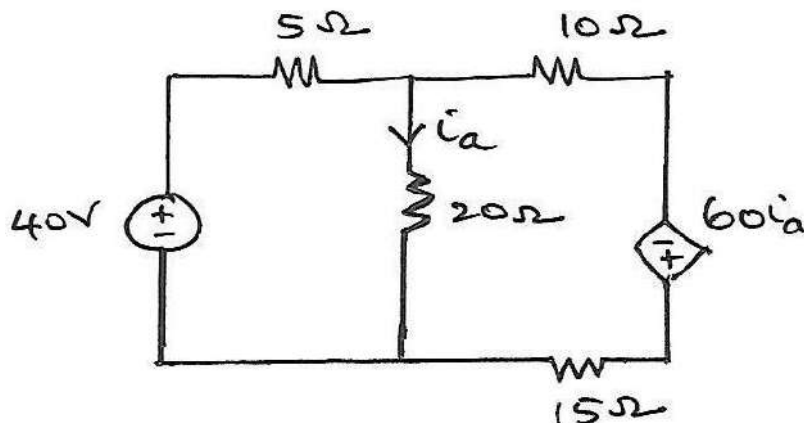


Fig.17

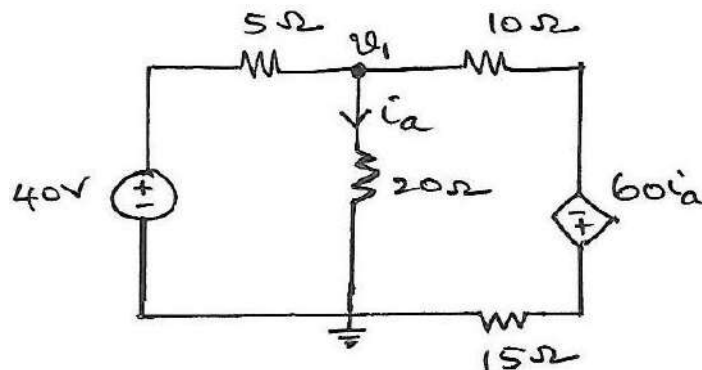

Solution: Identify ground node and other node with its voltage as shown;



From the circuit;

$$i_a = v_1/20 \text{ and}$$

$$P_{ds} = (60 i_a) \times (\text{current that comes out of +ve polarity of } 60i_a)$$

$$= (60 i_a) [(v_1 - (-60i_a))/(10 + 15)]$$

$$= (60 i_a) (v_1 + 60 i_a)/25$$

10) Find the current  $i_1$  in the network shown in Fig. 18. Use node Analysis.


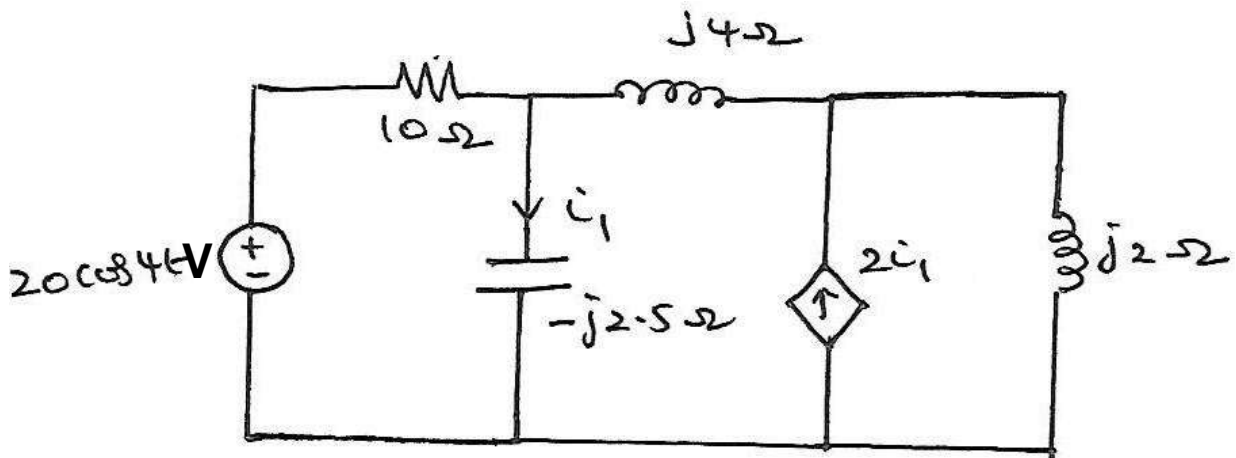


Fig.18

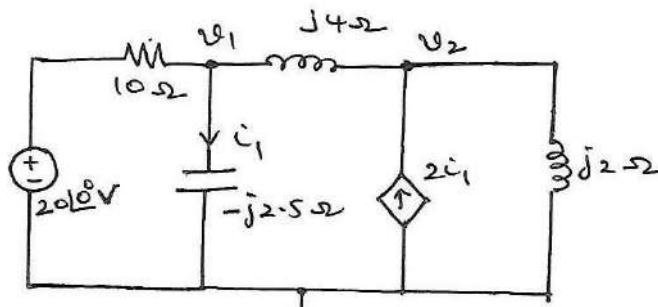Identify ground node and other node voltages as shown. Also writing source using phasor representation.



From the circuit;  $i_1 = v_1 / (-j2.5)$

Apply KCL at node 1;

$$v_1 / (-j2.5) + (v_1 - (20\angle 0^\circ)) / 10 + (v_1 - v_2) / j4 = 0$$

$$\Rightarrow j 0.4 v_1 + 0.1 v_1 - j 0.25 v_1 + j 0.25 v_2 = 2$$

$$\Rightarrow (0.1 + j 0.15) v_1 + j 0.25 v_2 = 2 \dots\dots(1)$$

Apply KCL at node 2;

$$-2i_1 + v_2 / j2 + (v_2 - v_1) / j4 = 0$$

$$\Rightarrow -2(v_1 / (-j2.5)) + v_2 / j2 + (v_2 - v_1) / j4 = 0$$

$$\Rightarrow -j 0.8 v_1 - j 0.5 v_2 - j 0.25 v_2 + j 0.25 v_1 = 0$$

$$\Rightarrow -j 0.55 v_1 - j 0.75 v_2 = 0 \dots\dots\dots (2)$$

Using Cramer's rule;

$$\Delta = \begin{vmatrix} 0.1 + j 0.15 & j 0.25 \\ -j 0.55 & -j 0.75 \end{vmatrix} = (0.1 + j 0.15)(-j 0.75) - 0.25(0.55) = -0.025 - j 0.075$$

$$\Delta v_1 = \begin{vmatrix} 2 & j 0.25 \\ 0 & -j 0.75 \end{vmatrix} = -j 1.5$$

$$v_1 = \Delta v_1 / \Delta = (-j 1.5) / (-0.025 - j 0.075) = 18 + j 6 = 18.97 \angle 18.43^\circ \text{ V}$$


$$\text{Therefore, } i_1 = v_1 / (-j 2.5) = -2.4 + j 7.2 = 7.58 \angle 108.43^\circ \text{ A.}$$

$$i_1(t) = 7.58 \cos (4t + 108.43^\circ) \text{ A}$$

### Concept of Supermesh:

Supermesh concept is considered whenever a current source appears in common to two meshes.

Consider the Network Below;

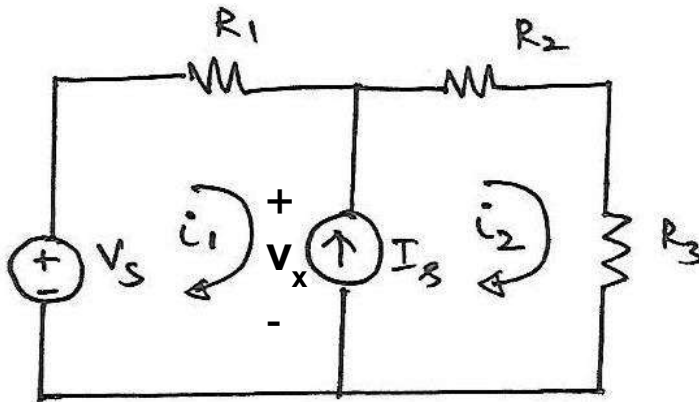

**Fig.19**

To know the advantage of applying supermesh concept; first consider usual way;

Applying KVL to mesh 1;

$$R_1 i_1 + v_x - V_s = 0$$

$$R_1 i_1 + v_x = V_s \dots\dots(1)$$

Applying KVL to mesh 2;

$$(R_2 + R_3)i_2 - v_x = 0$$

$$v_x = (R_2 + R_3)i_2 \dots\dots(2)$$

Substituting (2) in (1), we get;

$$R_1 i_1 + (R_2 + R_3)i_2 = V_s \dots\dots(3)$$

Also from the circuit;


$$i_2 - i_1 = I_s$$

$$\Rightarrow i_2 = I_s + i_1 \dots\dots(4)$$

⇒ Substituting (4) in (3) we get,  $i_1$ ;

⇒ Substituting  $i_1$  in (4), we get  $i_2$ .

Applying the concept of supermesh;

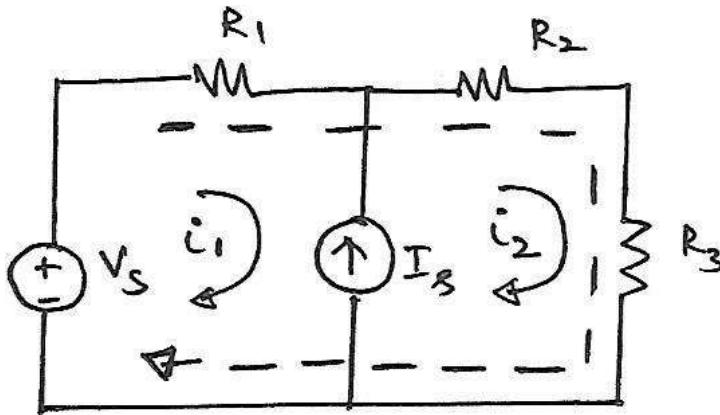

Here, after identifying a current source common to two meshes; we first write constraint equation which relates corresponding mesh currents and the current source value.

$$i_2 - i_1 = I_s$$

$$\text{Or } i_2 = I_s + i_1 \dots (1)$$

We then club those two meshes and call it as supermesh; shown by dashed lines in the figure; Now we apply KVL to supermesh;

$$R_1 i_1 + R_1 i_2 + R_3 i_2 - V_s = 0$$

$R_1 i_1 + (R_1 + R_3) i_2 = V_s \dots (2)$ , this equation is exactly the same as (3) in previous case. In this case, it was easily obtained thus reducing the steps. Now, substituting (1) in (2), we get  $i_1$ . Then substituting  $i_1$  in (1) we get  $i_2$ . Therefore, mesh currents were easily obtained using supermesh concept.

11) Use mesh analysis to find  $V_x$  in the circuit shown in fig. 20


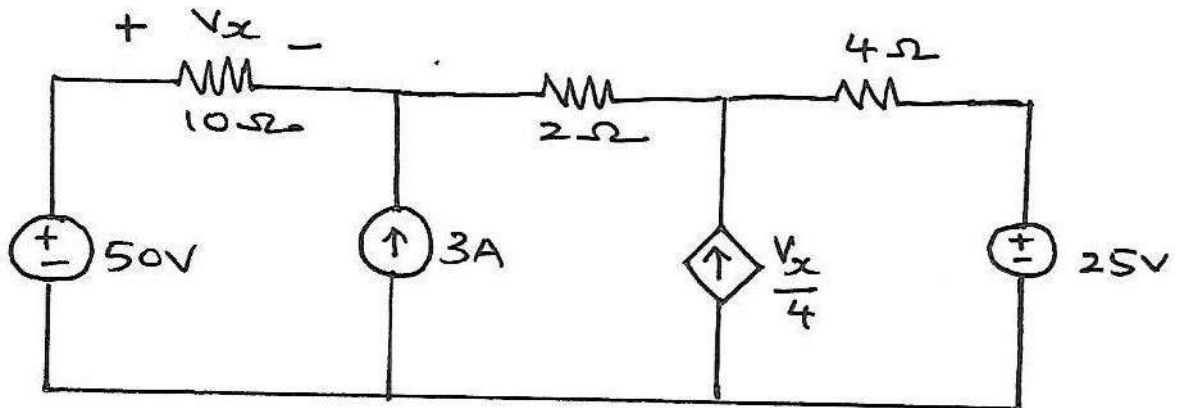


Fig.20

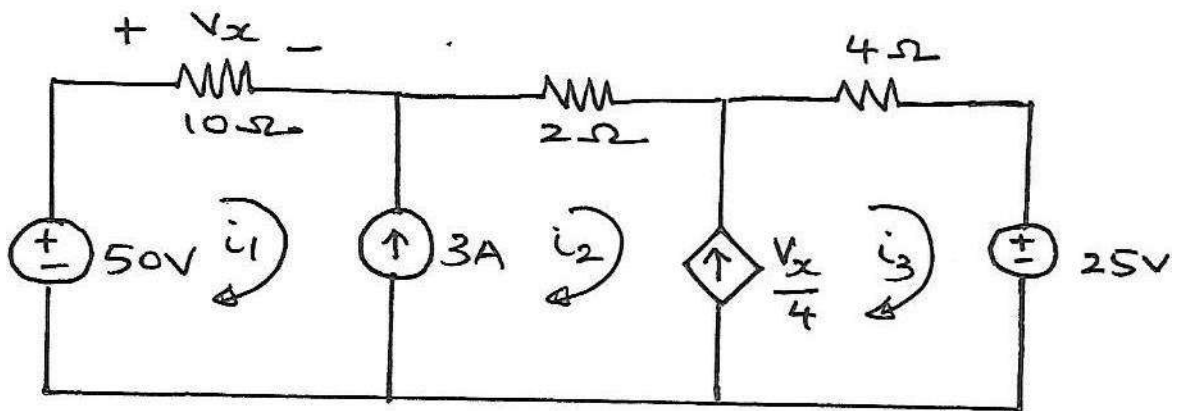

**Solution:** From the circuit;  $V_x = 10i_1$

Identifying 3A and  $V_x/4$  current sources appearing in common to mesh-1&2 and mesh-2&3 respectively; the constraint equations are written as;  $i_2 - i_1 = 3$

$$\Rightarrow i_2 = 3 + i_1 \quad \text{Also } i_3 - i_2 = V_x/4,$$

$$\text{wkt, } V_x = 10i_1$$

Substituting in above equation we get  $i_3 - i_2 = 10i_1/4$ , wkt  $i_2 = 3 + i_1$   
substituting this  $\Rightarrow 4i_3 - 4(3 + i_1) - 10i_1 = 0$

$$-14i_1 + 4i_3 = 12 \dots\dots(1)$$

Apply KVL to supermesh

formed by  $10\Omega \rightarrow 2\Omega \rightarrow 4\Omega \rightarrow 25V \rightarrow 50V \rightarrow 10\Omega$

$$10 i_1 + 2 i_2 + 4 i_3 + 25 - 50 = 0$$

$$\Rightarrow 10 i_1 + 2 i_2 + 4 i_3 = 25$$

$$\Rightarrow 10 i_1 + 2 (3+i_1) + 4 i_3 = 25$$


$$\Rightarrow 12 i_1 + 4 i_3 = 19 \dots\dots (2)$$

$\Rightarrow$  Solving (1) and (2), we get  $i_1 = 0.2692$  A and  $i_3 = 3.9423$  A

$$\Rightarrow i_2 = 3+i_1 = 3.2692$$
 A.


$$\Rightarrow V_x = 10 i_1 = 2.692$$
 V

12) Find  $v_x$  in the circuit shown in fig. 21, using mesh analysis;

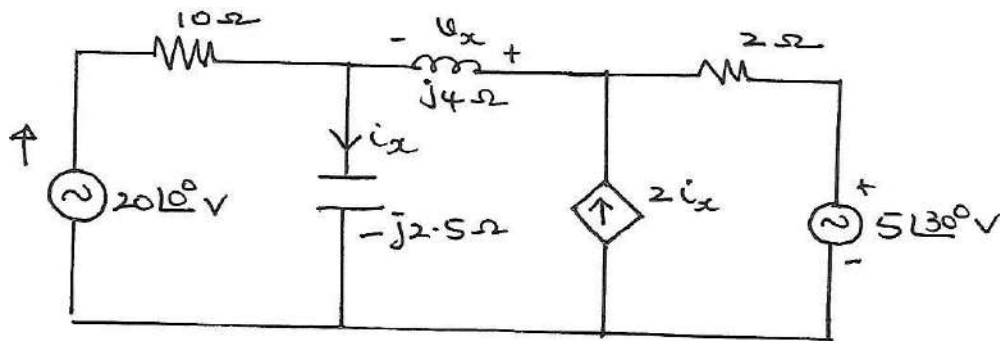

**Fig.21**

Solution:-

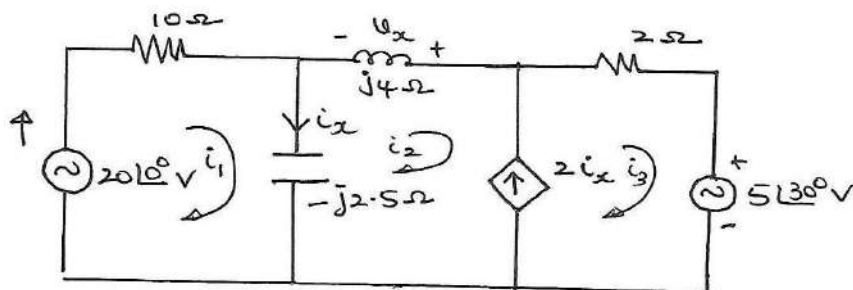

From the circuit;  $v_x = -j4 i_2$

$$i_x = i_1 - i_2$$

$i_3 - i_2 = 2 i_x$  (current source  $2i_x$  appears in common to two meshes)

$$i_3 - i_2 = 2(i_1 - i_2)$$

$$i_3 = 2i_1 - i_2$$

Apply KVL to mesh 1;

$$10 i_1 - j 2.5(i_1 - i_2) - (20 \angle 0^\circ) = 0$$

$$(10 - j2.5) i_1 + j 2.5 i_2 = 20 \dots\dots\dots(1)$$

Apply KVL to supermesh formed by

$$j4\Omega \rightarrow 2\Omega \rightarrow 5 \angle 30^\circ \rightarrow -j2.5 \Omega \rightarrow j4\Omega, \text{ we have,}$$

$$j4 i_2 + 2 i_3 + (5 \angle 30^\circ) - j 2.5 (i_2 - i_1) = 0$$

wkt  $i_3 = 2i_1 - i_2$ , subs in above eqn;

$$j4 i_2 + 2 (2i_1 - i_2) + (5 \angle 30^\circ) - j2.5 (i_2 - i_1) = 0$$

$$(4 + j2.5) i_1 + (-2 + j1.5) i_2 = -(5 \angle 30^\circ) = -4.33 - j2.5 \dots\dots\dots(2)$$

Using cramer's rule;

$$\Delta = \begin{vmatrix} 10 - j2.5 & j2.5 \\ 4 + j2.5 & -2 + j1.5 \end{vmatrix} = (10 - j2.5)(-2 + j1.5) - j2.5(4 + j2.5) = -10 + j10$$

$$\Delta i_2 = \begin{vmatrix} 10 - j2.5 & 20 \\ 4 + j2.5 & -4.33 - j2.5 \end{vmatrix} = (10 - j2.5)(-4.33 - j2.5) - 20(4 + j2.5) = -129.55 - j64.175$$

$$i_2 = \Delta i_2 / \Delta = (-129.55 - j64.175) / (-10 + j10)$$

$$i_2 = 3.268 + j9.686$$

$$i_2 = 10.22 \angle 71.35^\circ \text{ A}$$

$$\text{Therefore, } v_x = -j4 i_2 = 38.74 - j13.07 = 40.89 \angle -18.64^\circ \text{ V}$$

**Concept of Supernode:**

Supernode concept is applied whenever a voltage source appears in common to two nodes.

Consider the network below;


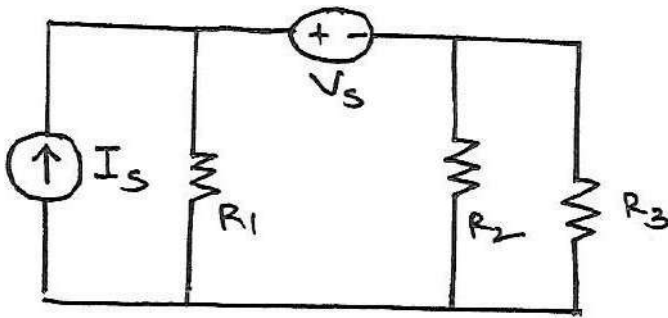


Fig.22

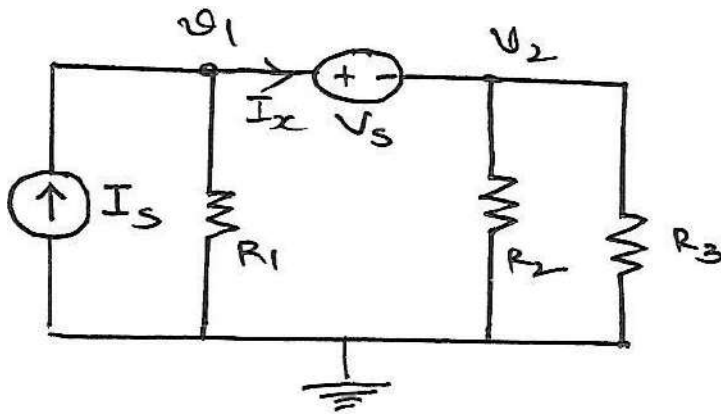To illustrate the advantage of supernode concept; we first find the node voltages of the network by the usual way;



Apply KCL at node 1;

$$v_1/R_1 - I_s + I_x = 0$$

$$v_1/ R_1 + I_x = I_s \dots\dots (1)$$

Apply KCL at node 2;



$$v_2 / R_2 + v_2 / R_3 - I_x = 0$$

$$v_2 / R_2 + v_2 / R_3 = I_x \dots\dots(2)$$

Subs (2) in (1), we get;

$$v_1 / R_1 + v_2 / R_2 + v_2 / R_3 = I_s \dots\dots (3)$$

Also from the circuit;  $v_1 - v_2 = V_s$

$$\Rightarrow v_1 = V_s + v_2 \dots\dots (4)$$

Substituting (4) in (3) will give the value of  $v_2$

Substituting the value of  $v_2$  in (4) will give the value of  $v_1$ .


**Applying the concept of supernode;**

After identifying the voltage source appearing in common to two nodes;

We first write constraint equation; which relates the voltage source value with the corresponding node voltages; here it is;  $v_1 - v_2 = V_s$

$$v_1 = v_2 + V_s \dots\dots (1)$$

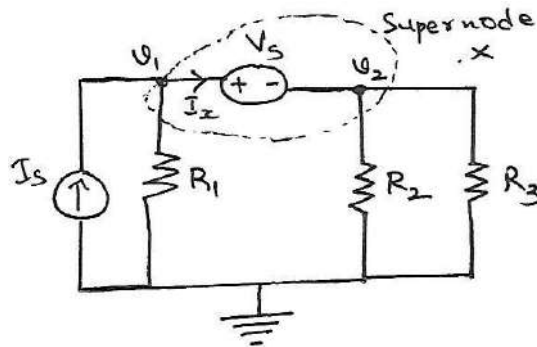After this, we club the corresponding nodes to become one node and call it as a supernode. Then we apply KCL to supernode. Here, we apply KCL at supernode X as shown;



$$v_1 / R_1 - I_s + v_2 / R_2 + v_2 / R_3 = 0$$

$$v_1 / R_1 + v_2 / R_2 + v_2 / R_3 = I_s \dots\dots(2)$$

The above equation is same as eqn 3 in previous method, but the above equation was easily obtained in just one step. Therefore, when a voltage

source is appearing in common to two nodes, it is always advantageous to consider the concept of supermesh.

Now, substituting (1) in (2), we get  $v_2$ .

Substituting  $v_2$  in (2) we get  $v_1$ .

13) Find  $i_a$  and  $v_a$  in the network shown in fig. 23 using node analysis.


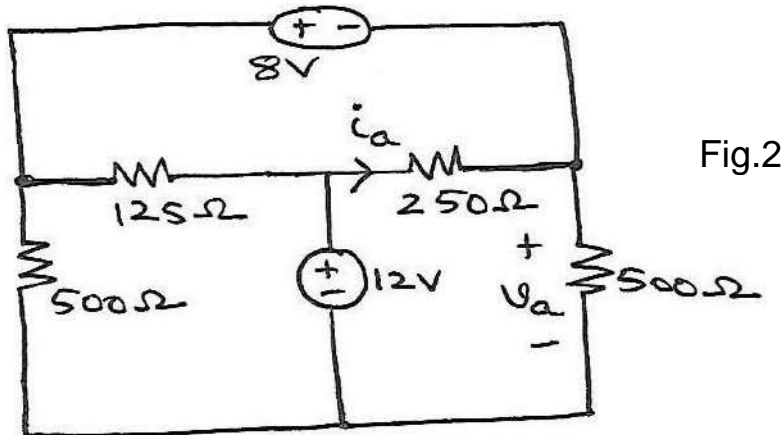


Fig.2

Solution:-

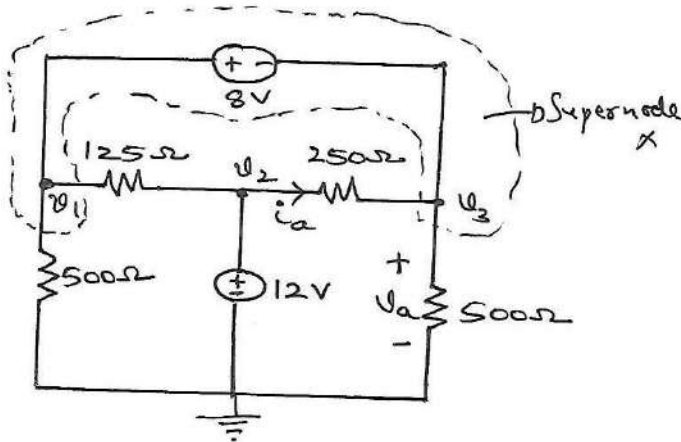

From the circuit;  
 $i = \frac{(v_2 - v_3)}{250}$   
 $v_1 = v_3$

Also;  $v_2 = 12\text{ V}$

$$v_1 - v_3 = 8$$

$$\Rightarrow v_1 = 8 + v_3$$

Apply KCL at supernode X;

$$v_1/500 + (v_1 - v_2)/125 + (v_3 - v_2)/250 + v_3/500 = 0$$

$$v_1 + 4v_1 - 4v_2 + 2v_3 - 2v_2 + v_3 = 0$$

$$5v_1 - 6v_2 + 3v_3 = 0$$

Substituting  $v_1 = 8 + v_3$  in above equation, we get;  $5(8+v_3) - 6v_2 + 3v_3 = 0$

$$-6v_2 + 8v_3 = -40$$

Wkt  $v_2 = 12 \text{ V}$

Therefore,  $v_3 = (-40 + 6(12))/8 = 4 \text{ V}$

Now,  $i_a = (v_2 - v_3)/250 = 0.032 = 32 \text{ mA}$ .

$$v_a = v_3 = 4 \text{ V}.$$

14) Find all the node voltages in the network shown in fig.24


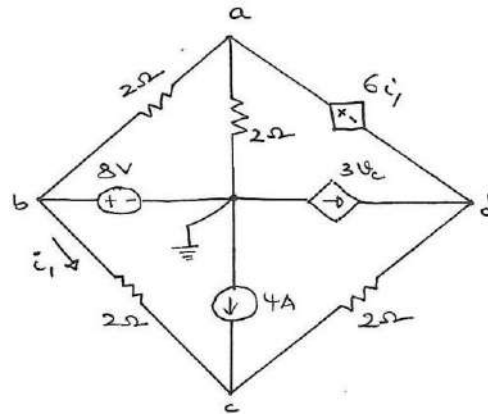


Fig.2

Solution:

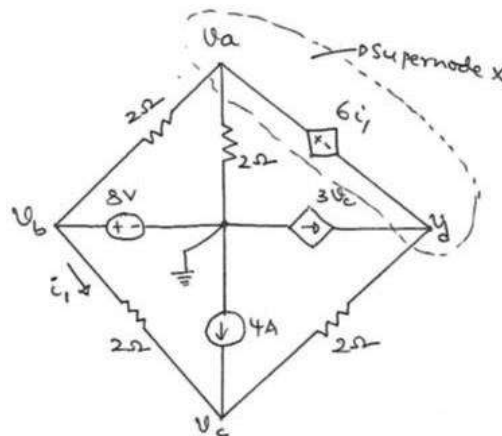

From the circuit;

$$v_b = 8 \text{ V}$$

$$\text{Also, } v_a - v_d = 6 i_1$$

$i_1 = (v_b - v_c)/2$  subs in above eqn. we get;

$$v_a - v_d = 6 (v_b - v_c) / 2$$

$$\Rightarrow 2v_a - 2v_d = 6 v_b - 6 v_c$$

$$\Rightarrow 2v_a + 6v_c - 2v_d = 6 v_b = 6(8) = 48 \dots\dots\dots(1)$$

Apply KCL at supernode X as shown;

$$(v_a - v_b)/2 + v_a/2 - 3v_c + (v_d - v_c)/2 = 0$$

$$(v_a - 8)/2 + v_a/2 - 3v_c + (v_d - v_c)/2 = 0$$

$$\Rightarrow v_a - 8 + v_a - 6 v_c + v_d - v_c = 0$$

$$\Rightarrow 2v_a - 7v_c + v_d = 8 \dots\dots\dots(2)$$

Apply KCL at node C

$$-4 + (v_c - v_d)/2 + (v_c - v_b)/2 = 0$$


$$\Rightarrow -8 + v_c - v_d + v_c - v_b = 0$$

$$\Rightarrow 2v_c - v_d = v_b + 8 = 16 \dots\dots\dots(3)$$


Solving (1),(2) and (3), we get;  $v_a = 9.142V$  ,  $v_c = -1.142 V$  ,  $v_d = -18.28V$

and  $v_b = 8V$  (given)

**Star- delta ( $\Delta$ ) and delta ( $\Delta$ ) to star transformations**

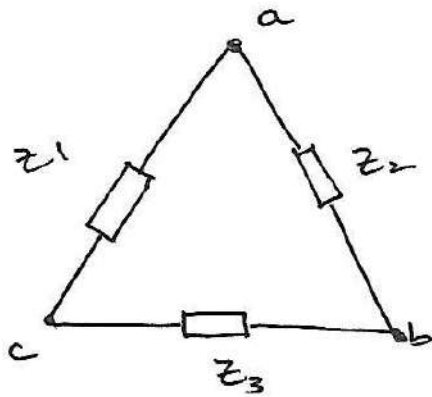

**Fig25a delta arrangement**

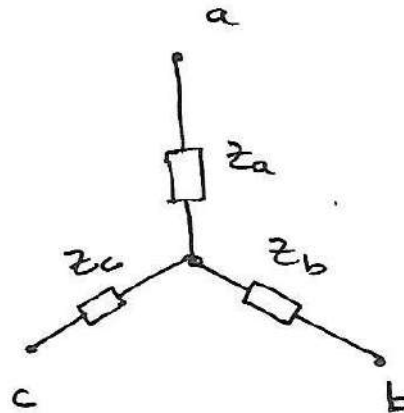

**Fig.25b Star arrangement**

(The positions of  $Z_1$ ,  $Z_2$  and  $Z_3$  should be noted.  $Z_1$  will appear between a and c; from there, going clockwise we see  $Z_2$  and  $Z_3$ . The positions of  $Z_a$ ,  $Z_b$  and  $Z_c$  should be noted.  $Z_a$  connected to vertex-a and centroid.  $Z_b$  connected to vertex-b and centroid.  $Z_c$  connected to vertex-c and centroid.)

Consider the above arrangements are equivalent; then;

$$Z_{ac} = Z_1(Z_2 + Z_3) / (Z_1 + Z_2 + Z_3) = Z_a + Z_c \dots \dots \dots (1)$$

Also,

$$Z_{ab} = Z_2(Z_3 + Z_1) / (Z_1 + Z_2 + Z_3) = Z_a + Z_b \dots \dots \dots (2)$$

$$Z_{bc} = Z_3(Z_1 + Z_2) / (Z_1 + Z_2 + Z_3) = Z_b + Z_c \dots \dots \dots (3)$$

Eqn. (1) – Eqn.(3)

$$(Z_1 Z_2 - Z_2 Z_3) / (Z_1 + Z_2 + Z_3) = Z_a - Z_b \dots \dots \dots (4)$$

$$\text{Solving (2) and (4), we get, } Z_a = Z_1 Z_2 / (Z_1 + Z_2 + Z_3) \dots \dots \dots (5)$$

Substituting (5) in (2), solving for  $Z_a$ , we get;

$$Z_b = Z_2 Z_3 / (Z_1 + Z_2 + Z_3) \dots \dots \dots (6)$$

Substituting (5) in (1), solving for  $Z_c$ , we get;

$$Z_c = Z_1 Z_3 / (Z_1 + Z_2 + Z_3) \dots\dots\dots (7)$$

Consider

$$Z_a Z_b + Z_b Z_c + Z_a Z_c = (Z_1 Z_2^2 Z_3 + Z_1 Z_2 Z_3^2 + Z_1^2 Z_2 Z_3) / (Z_1 + Z_2 + Z_3)^2$$

$$Z_a Z_b + Z_b Z_c + Z_a Z_c = Z_1 Z_2 Z_3 / (Z_1 + Z_2 + Z_3) \dots\dots\dots (8)$$

Eqn(8) /  $Z_b$  gives

$$Z_1 = (Z_a Z_b + Z_b Z_c + Z_a Z_c) / Z_b \dots\dots\dots (9)$$

Eqn(8) /  $Z_c$  gives

$$Z_2 = (Z_a Z_b + Z_b Z_c + Z_a Z_c) / Z_c \dots\dots\dots (10)$$

Eqn(8) /  $Z_a$  gives

$$Z_3 = (Z_a Z_b + Z_b Z_c + Z_a Z_c) / Z_a \dots\dots\dots (11)$$

15) Reduce the network shown in fig.26 to a single resistor between terminals a-b.


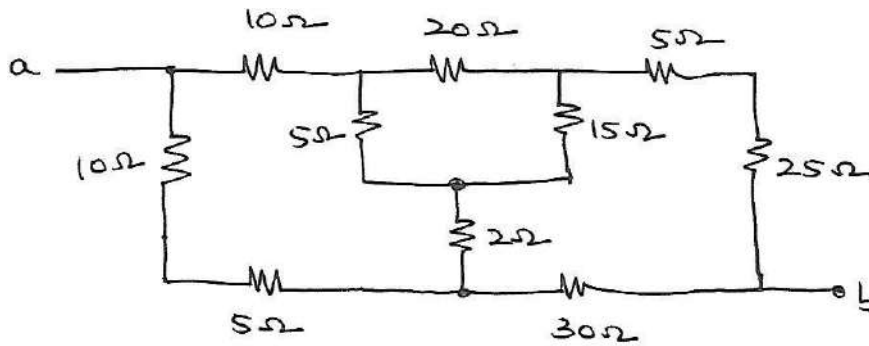


Fig.26

Solution:-

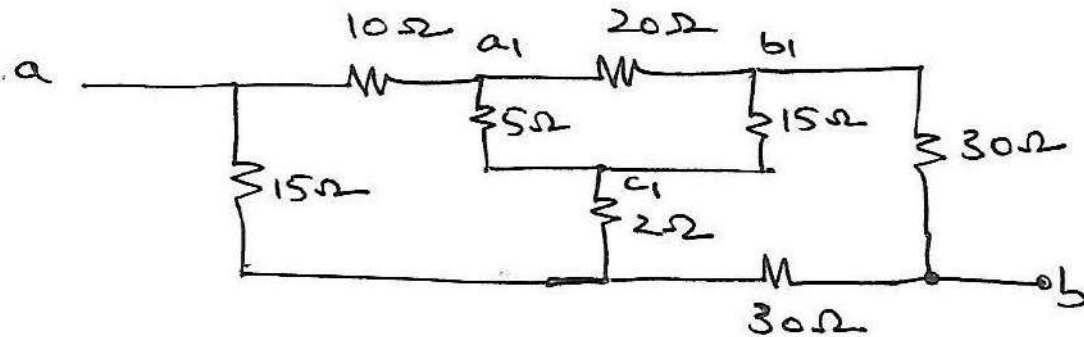

From the network above, we observe,  $10\Omega$  and  $5\Omega$  are in series and also  $5\Omega$  and  $25\Omega$  are in series. Therefore they are equivalently replaced by  $15\Omega$  and  $30\Omega$  as shown.

Identifying delta between the vertices  $a_1$ - $b_1$ - $c_1$ ;

We have  $R_1 \rightarrow R_2 \rightarrow R_3$

as,  $5\Omega \rightarrow 20\Omega \rightarrow 15\Omega$


Corresponding star will have;

$$R_a = R_1 R_2 / (R_1 + R_2 + R_3) = 100/40 = 2.5\Omega \text{ (resistance connected to vertex } a_1)$$


$$R_b = R_2 R_3 / (R_1 + R_2 + R_3) = 300/40 = 7.5\Omega \text{ (resistance connected to vertex } b_1)$$

$$R_c = R_1 R_3 / (R_1 + R_2 + R_3) = 75/40 = 1.875\Omega \text{ (resistance connected to vertex } c_1)$$

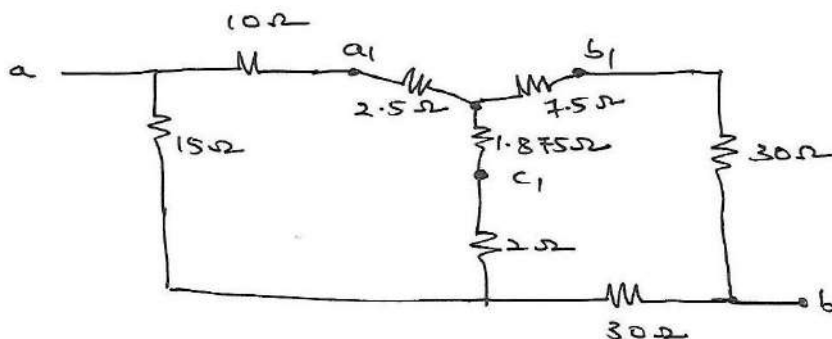After replacing delta elements by corresponding star elements;



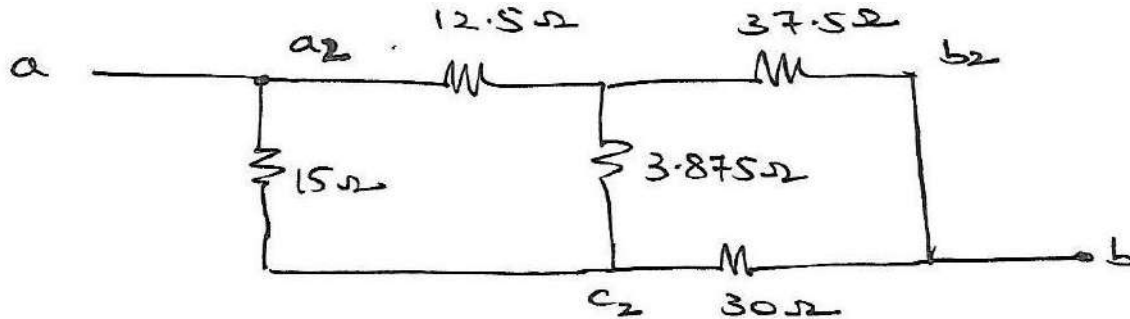10Ω and 2.5 Ω appear in series. 30Ω and 7.5Ω appear in series. 2Ω and 1.875Ω appear in series. They are replaced by their equivalent resistances.



Identifying star between the vertices a2-b2-c2;

We have  $R_a \rightarrow R_b \rightarrow R_c$

as,  $12.5\Omega \rightarrow 37.5\Omega \rightarrow 3.875\Omega$

Corresponding delta will have;

$$R_1 = (R_a R_b + R_b R_c + R_a R_c) / R_b$$

$$= [(12.5)(37.5) + (37.5)(3.875) + (3.875)(12.5)] / 37.5$$

$$= 662.5 / 37.5 = 17.66 \Omega \text{ (resistance connected b/n vertex a2 and c2)}$$


$$R_2 = (R_a R_b + R_b R_c + R_a R_c) / R_c$$

$$= 662.5 / 3.875 = 170.96 \Omega \text{ (resistance connected b/n vertex a2 and b2)}$$

$$R_3 = (R_a R_b + R_b R_c + R_a R_c) / R_a$$

$$= 662.5 / 12.5 = 53 \Omega \text{ (resistance connected b/n vertex b2 and c2)}$$

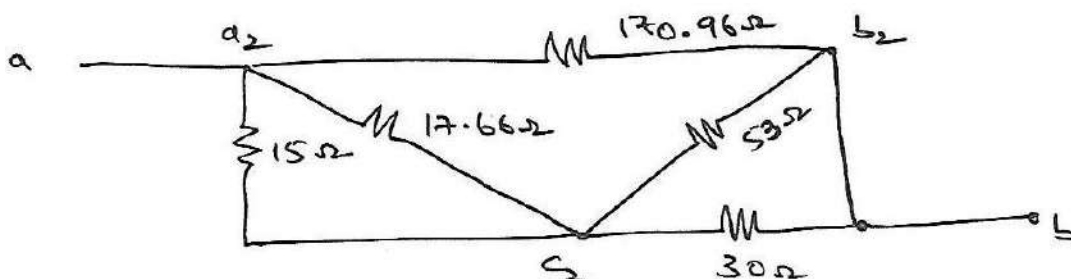
After replacing star elements by corresponding delta elements;






$$15 \parallel 17.66 = 8.11 \Omega$$

$$53 \parallel 30 = 19.15 \Omega$$

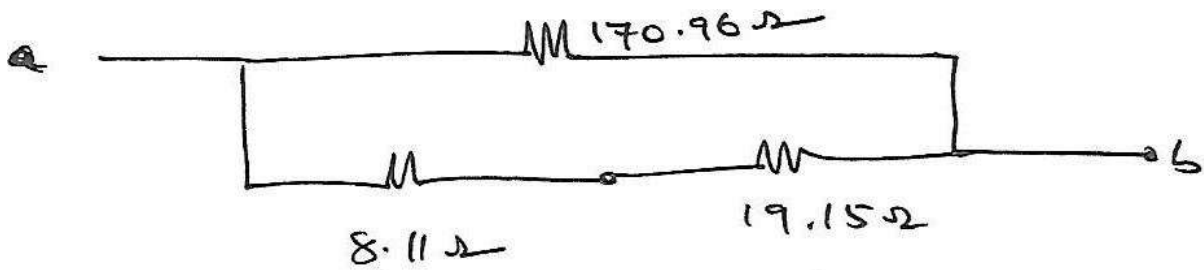
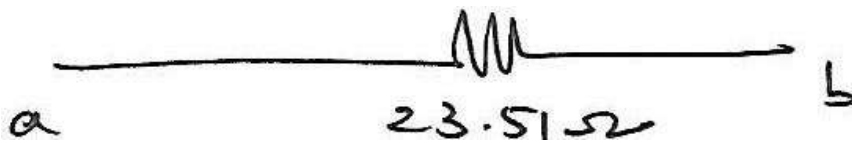
$$\text{Therefore, } R_{ab} = (19.15 + 8.11) \parallel 170.96 = 23.51 \Omega$$



Q16) Find the current  $I$  in the network shown in fig.27, by reducing the network to contain a source and a single series impedance.


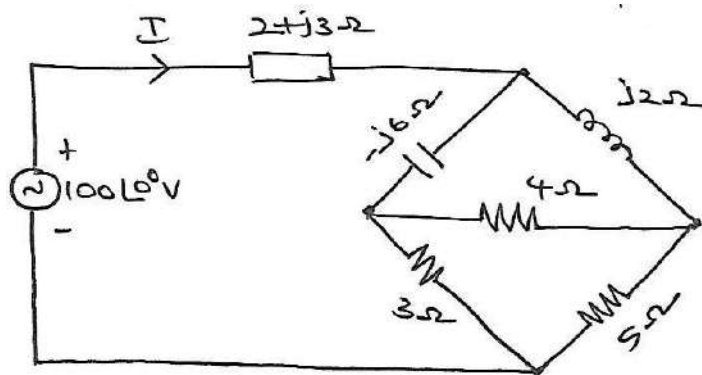


Fig.27

Solution:-

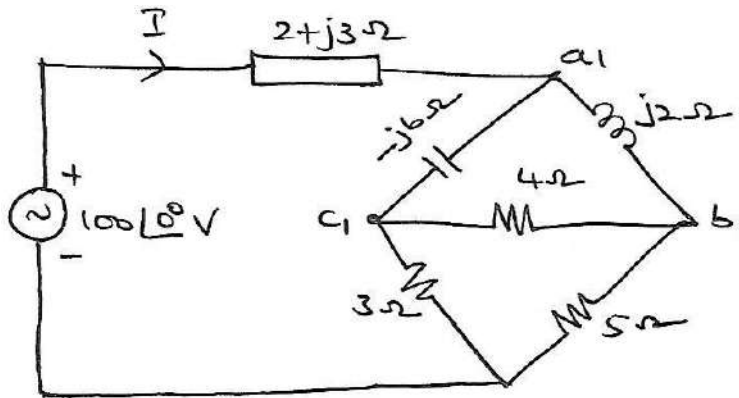

Identifying delta between the vertices a1-b1-c1;

We have  $Z_1 \rightarrow Z_2 \rightarrow Z_3$

as,  $-j6\Omega \rightarrow j2\Omega \rightarrow 4\Omega$

Corresponding star will have;

$$Z_a = Z_1 Z_2 / (Z_1 + Z_2 + Z_3) = (-j6)(j2) / (4-j4) = 1.5 + j1.5\Omega$$

(Impedance connected to vertex a1)


$$Z_b = Z_2 Z_3 / (Z_1 + Z_2 + Z_3) = (j2)(4) / (4-j4) = -1 + j\Omega$$

(Impedance connected to vertex b1)


$$Z_c = Z_1 Z_3 / (Z_1 + Z_2 + Z_3) = (-j6)(4) / (4-j4) = 3-j3\Omega$$

(Impedance connected to vertex c1)

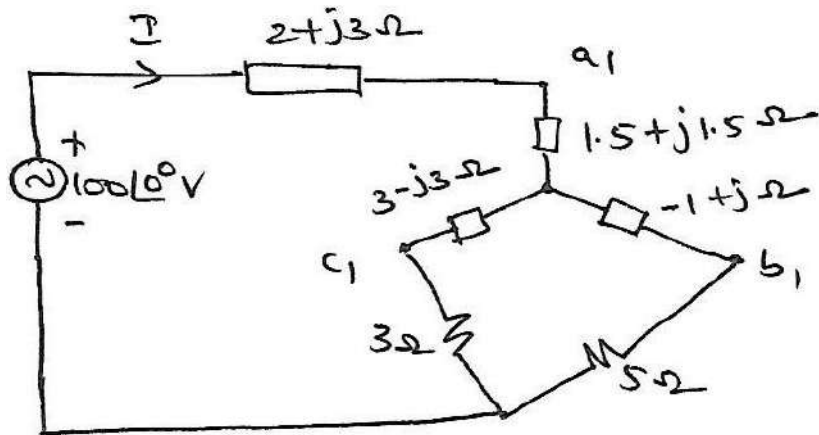
After replacing delta elements by corresponding star elements;



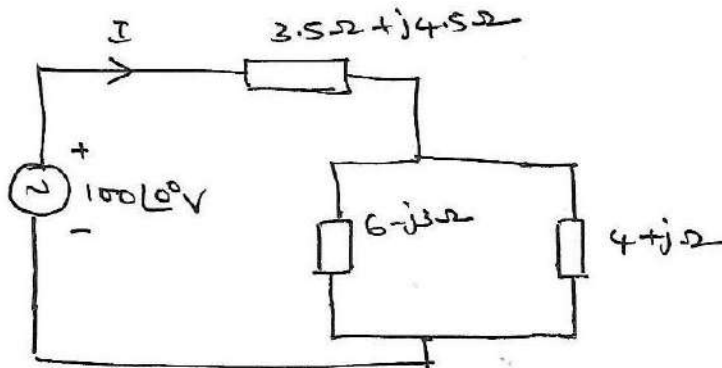The series impedances are replaced by equivalent impedances


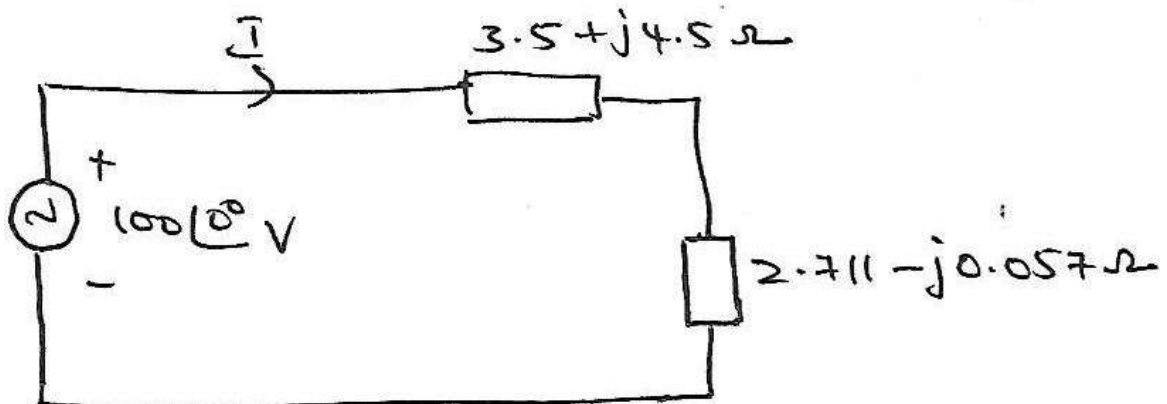
$$(6-j3) // (4+j) = 2.711 - j 0.057 \Omega$$




The single series impedance value,  $Z = (3.5 + j4.5) + (2.711 - j 0.057)$

$$Z = 6.211 + j 4.443 \Omega$$


Therefore,  $I = 100/Z = 100/(6.211 + j4.443) = 13.09 \angle -35.57^\circ \text{ A}$

## Additional Problems and Solutions

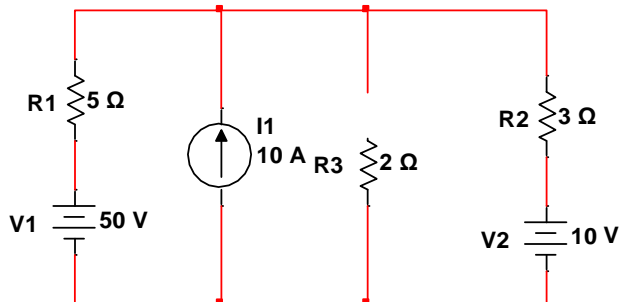
- 1) Using source transform, find the power delivered by the 50V source in the circuit shown:-



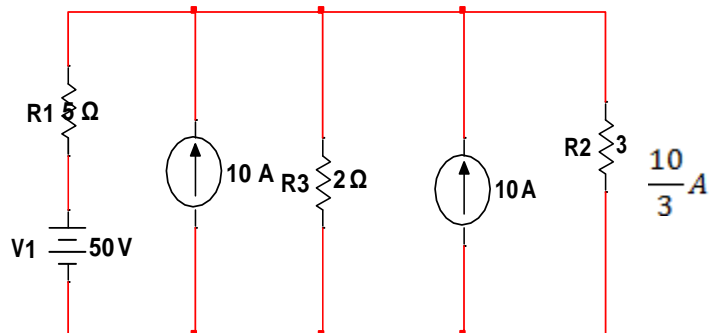
**Solution:** - Using source transformation for the pair V2 and R2, we get,



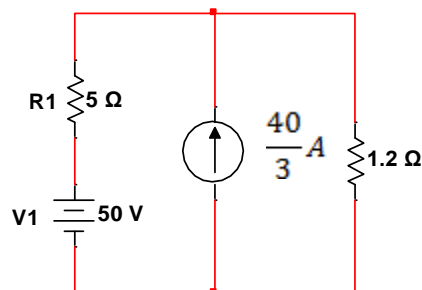Adding the parallel current sources and obtaining equivalent resistance of R3 and R2, we have,



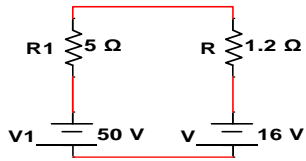
Converting the current source back to voltage source,



If  $I$  is the current in the circuit,  $I = \frac{50-16}{6.2} = 5.48A$

Therefore Power delivered by 50V source is  $P = I \times 50 = 5.48 \times 50 = 274.19W$ .

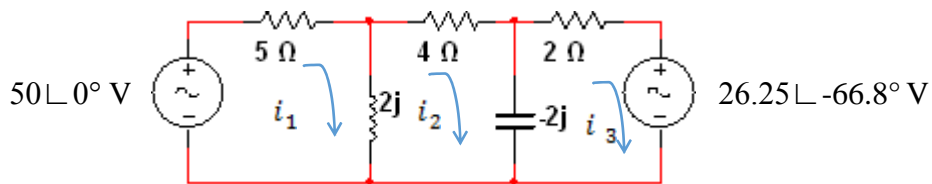2) Find the current through  $4\Omega$  in the network shown:



**Solution:** - Applying KVL to mesh 1 (mesh with  $i_1$ )

$$5i_1 + 2j(i_1 - i_2) - 50 = 0$$

$$\Rightarrow (5 + 2j)i_1 - (2j)i_2 = 50$$

Applying KVL to mesh 2

$$4i_2 - 2j(i_2 - i_3) + 2j(i_2 - i_1) = 0$$

$$\Rightarrow (-2j)i_1 + (4)i_2 + 2j(i_2 - i_1) = 0$$

Applying KVL to mesh 3

$$(2j)i_3 + (26.25 \angle -66.8^\circ) - (2j)(i_3 - i_2) = 0$$

$$\Rightarrow (2 - 2j)i_3 + (2j)i_2 = (26.25 \angle -66.8^\circ) - 10.39 + (24.12j)$$

Matrix form


$$\begin{bmatrix} 5 + 2j & -2j & 0 \\ -2j & 4 & j - 2 \\ 0 & 2j & 2 - 2j \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \\ -10.39 + 24.12j \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 5 + 2j & -2j & 0 \\ -2j & 4 & 2j \\ 0 & 2j & 2 - 2j \end{vmatrix} = 84 - 24j$$

$$\Delta i_2 = \begin{vmatrix} 5 + 2j & 50 & 0 \\ -2j & 0 & 2j \\ 0 & -10.39 + 24.12j & 2 - 2j \end{vmatrix} = 399.64 + 400.38j$$

$$i_2 = \frac{\Delta i_2}{\Delta} = 6.47 \quad \text{A}$$

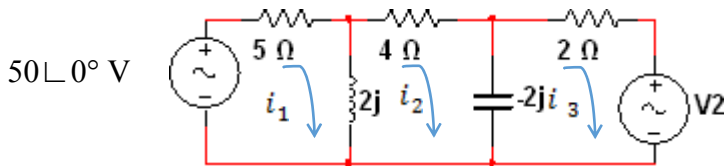3) Find the value of V2 if the current through 4Ω is zero.



**Solution:** - Given  $i_2=0$

Applying KVL to mesh 3 (mesh with  $i_3$ ), we get

$$2i_3 + V2 - 2j(i_3) = 0$$

$$\Rightarrow V2 = (-2 + 2j)i_3$$

Applying KVL to mesh 2,

$$4i_2 - 2j(i_2 - i_3) + 2j(i_2 - i_1) = 0$$

$$\Rightarrow i_3 = i_1$$


Applying KVL to mesh 1,

$$5i_1 + 2j(i_1) = 50$$

$$\Rightarrow i_1 = 9.28 \angle -21.8^\circ \text{ A} = i_3$$

$$\text{Therefore, } V2 = i_3(-2 + 2j) = 26.26 \angle 113.19^\circ \text{ V}$$

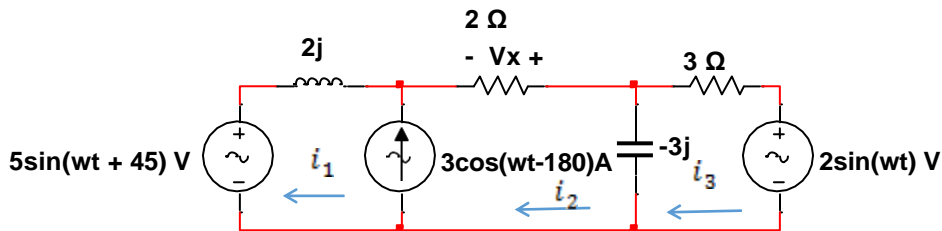4) Find  $V_x$  using mesh analysis for the circuit shown



**Solution:** - From the circuit  $V_x = -2i_2$

$$\text{Applying concept of super mesh, } i_2 - i_1 = 3 \angle -90^\circ$$

$$\text{Therefore, } i_1 = -3 \angle -90^\circ + i_2$$

Remove the arm of the current source and apply kvl,

$$(2j)i_1 - V_x - (3j)(i_2 - i_3) - 5 \angle 45^\circ = 0$$

$$\Rightarrow (2 - j)i_2 + (3j)i_3 = 9.535 + j3.535$$

Applying KVL to mesh with  $i_3$   
 $(3 - 3j)i_3 + (3j)i_2 = -2$

$$\text{Therefore } \Delta = \begin{vmatrix} 2 - j & j3 \\ j3 & 3 - j3 \end{vmatrix} = 12 - 9j$$


$$\Delta i_2 = \begin{vmatrix} 9.535 + j3.535 & j3 \\ -2 & 3 - j3 \end{vmatrix} = 39.21 - j12$$

$$i_2 = \frac{\Delta i_2}{\Delta} = 2.73 \angle 19.85^\circ \text{ A}$$

$$V_x = -2(2.73 \angle 19.85^\circ) \text{ v}$$

$$\text{Therefore, } V_x = 5.49 \angle -160.15^\circ \text{ V}$$

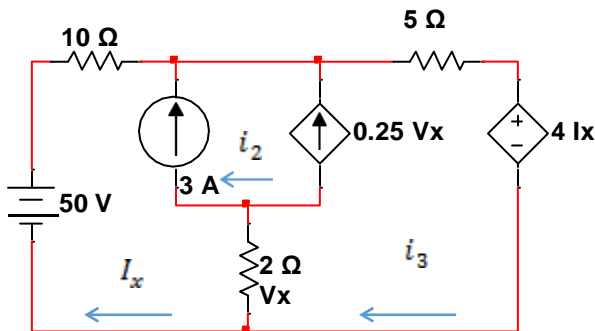5) Find  $V_x$  and  $I_x$  in the circuit shown using mesh analysis



**Solution:** - From the circuit  $V_x = 2(I_x - i_3) \dots (1)$

Also from the circuit  $i_2 - I_x = 3 \dots (2)$ ;  $i_3 - i_2 = 0.25 V_x \dots (3)$

Substituting equations 1 and 2 in 3, we get

$$6(i_3 - I_x) = 12 \Rightarrow i_3 - I_x = 2 \dots (4)$$


Removing the arm containing common current source and applying KVL, we get

$$14I_x + 5i_3 = 50 \dots (5)$$

Solving equations 4 and 5, we get  $I_x = 2.1 \text{ A}$


Therefore,  $V_x = -4 \text{ V}$ .

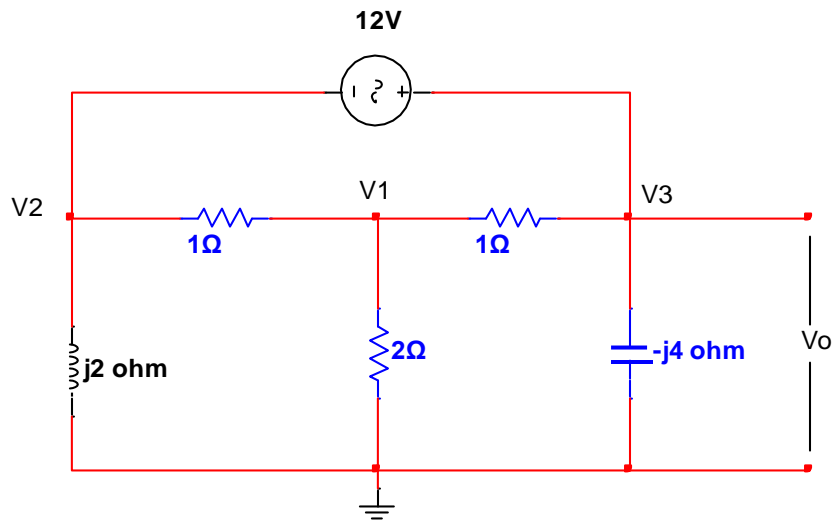6) Use node analysis to find  $V_0$  in the circuit shown below



From the circuit,
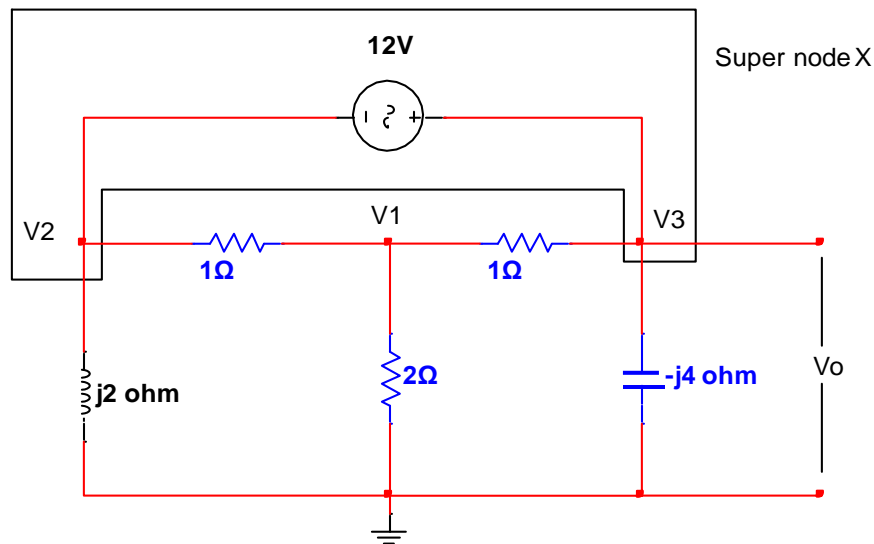
$$V_0 = V_3; V_0 - V_2 = 12V \text{ ---- (1);}$$



Applying KCL to super node X,

$$\Rightarrow \frac{V_2}{j2} + \frac{V_2 - V_1}{1} + \frac{V_0 - V_1}{1} + \frac{V_0}{-j4} = 0$$

$$\Rightarrow \frac{-jV_2}{2} + V_2 - V_1 + V_0 - V_1 + \frac{jV_0}{4} = 0$$

$$\Rightarrow -2jV_2 + 4V_2 - 4V_1 + 4V_0 - 4V_1 + jV_0 = 0$$



$$\Rightarrow (4 + j)V_0 - 8V_1 + (4 - j2)(V_0 - 12) = 0 \text{ (From(1))}$$

$$\Rightarrow 4V_0 + jV_0 - 8V_1 + 4V_0 - j2V_0 - 48 + j24 = 0$$

$$\Rightarrow (8 - j)V_0 - 8V_1 = 48 - j24 \text{ -----(2)}$$

Applying KCL at  $V_1$ ,

$$\Rightarrow \frac{V_1}{2} + \frac{V_1 - V_0}{1} + \frac{V_1 - V_2}{1} = 0$$

$$\Rightarrow V_1 + 2V_2 - 2V_0 + 2V_1 - 2V_2 = 0$$

$$\Rightarrow -2V_0 + 5V_1 - 2V_2 = 0$$

$$\Rightarrow -2V_0 + 5V_1 - 2(V_0 - 12) = 0$$

$$\Rightarrow -4V_0 + 5V_1 = -24 \text{ -----(3)}$$

Using Cramer's rule,

$$\Delta = \begin{vmatrix} 8 - j & -8 \\ -4 & 5 \end{vmatrix}$$

$$\Delta = 5(8 - j) - 32$$

$$\Delta = -5j + 8$$

$$\Delta V_0 = \begin{vmatrix} 48 - j24 & -8 \\ -24 & 5 \end{vmatrix}$$

$$\Delta V_0 = (48 - j24)5 - 192$$


$\Delta$

$$V_0 = \frac{\Delta V_0}{\Delta} = \frac{(48 - j24)5 - 192}{-5j + 8}$$

$$\therefore V_0 = 13.69V @ -36.19^\circ$$

W.K.T,

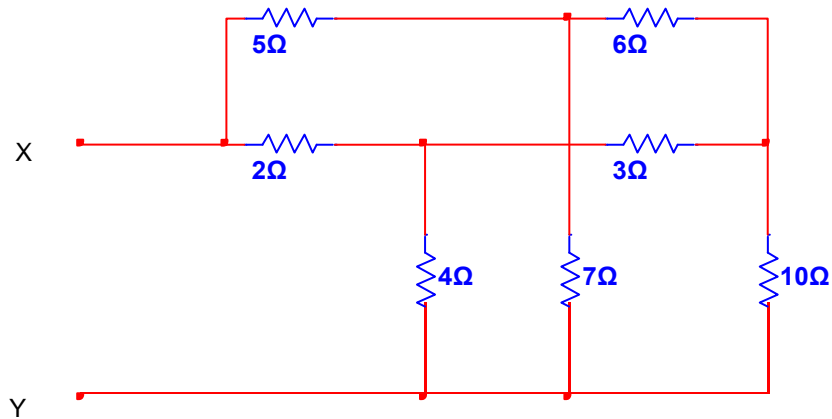7) Find the equivalent resistance between the terminals X and Y



Solution:-

Star 1:-  $R_a = 2; R_b = 3; R_c = 4;$

Corresponding Delta will have,

$$R_1 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_b}$$

$$\therefore R_1 = 8.66 \Omega$$

Similarly,

$$R_2 = \frac{26}{4} = 6.5 \Omega$$

$$R_3 = \frac{26}{3} = 13 \Omega$$

Now consider star 2:-  $R_a = 5; R_b = 6; R_c = 7;$

Corresponding Delta will have,


$$R_1 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_b}$$

$$\therefore R_1 = 17.8 \Omega$$


Similarly,

$$R_2 = \frac{107}{7} = 15.28 \Omega$$

$$R_3 = \frac{107}{5} = 21.4 \Omega$$

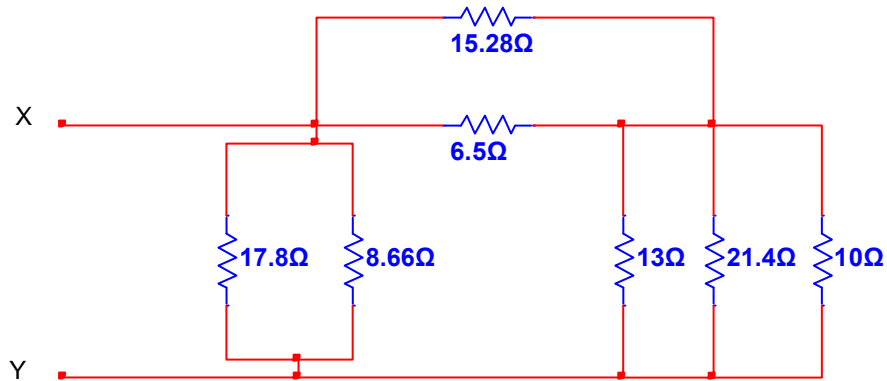


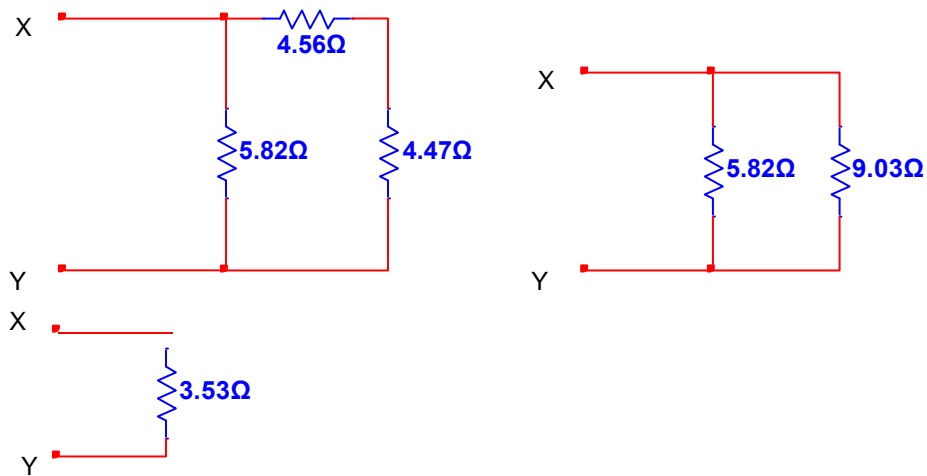This circuit can be reduced now using parallel and series combination of resistors as show below.



Therefore the equivalent resistance between X & Y = 3.53 Ω

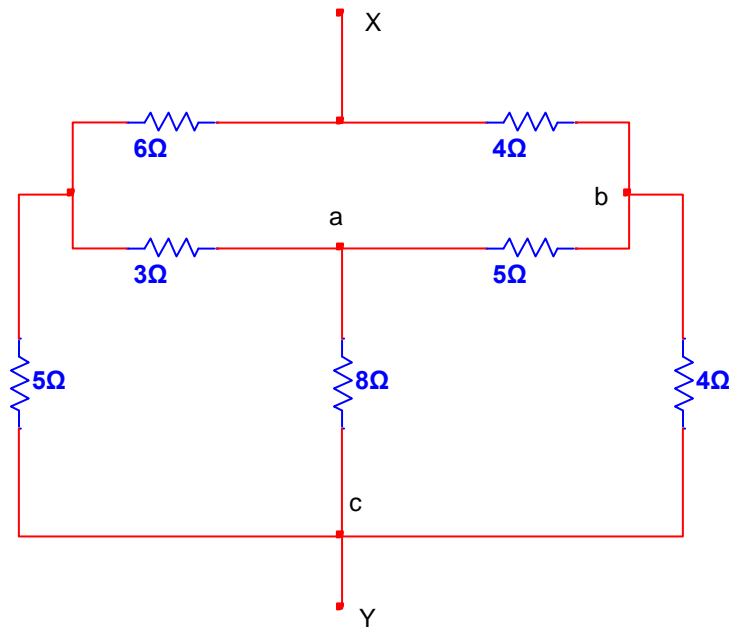
8) Determine the equivalent resistance between the terminals X & Y



Solution:

Consider the Delta  $R_1 = 8$ ;  $R_2 = 5$ ;  $R_3 = 4$ ;

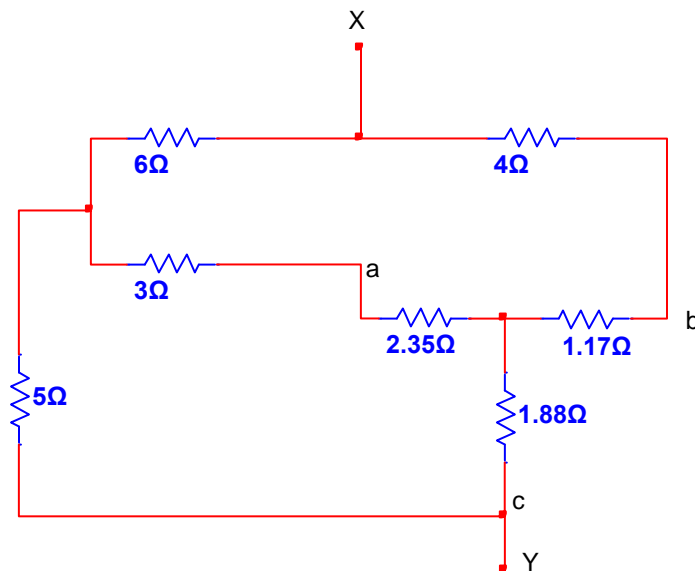It can be replaced with the circuit shown below



$$\text{Where, } R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$


$$\therefore R_a = 2.35\Omega$$

Similarly,

$$R_b = 1.17\Omega$$

$$R_c = 1.88\Omega$$

The above circuit can be written as,

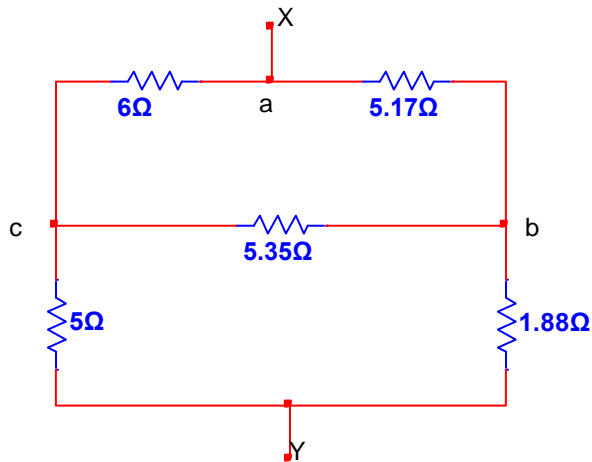



Consider the Delta,  $R_1 = 6$ ;  $R_2 = 5.17$ ;  $R_3 = 5.35$ ;

$$\therefore R_a = 1.877\Omega$$

$$\therefore R_b = 1.674\Omega$$

$$\therefore R_c = 1.94\Omega$$

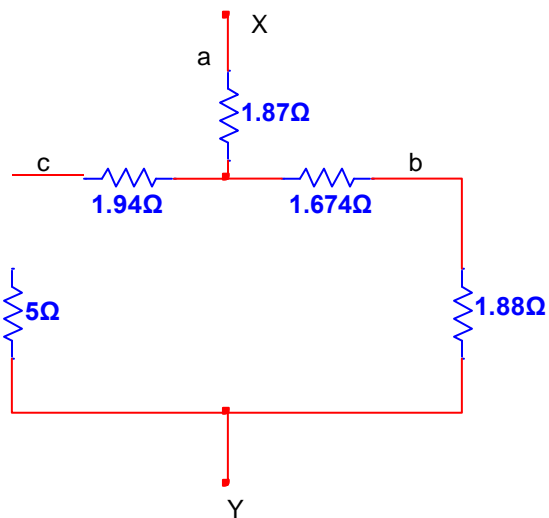

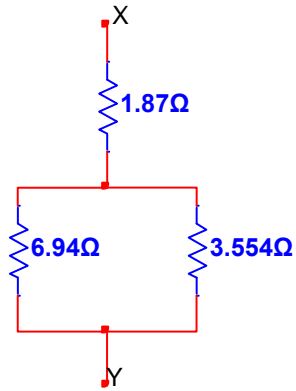

X




Y


Therefore the equivalent resistance between X & Y =  $4.22\Omega$

## Source Shifting:


(i) Voltage Source Shifting:-

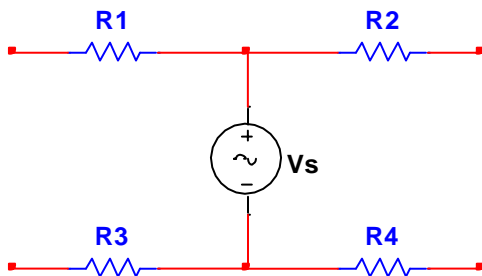


The above circuit can be written as,

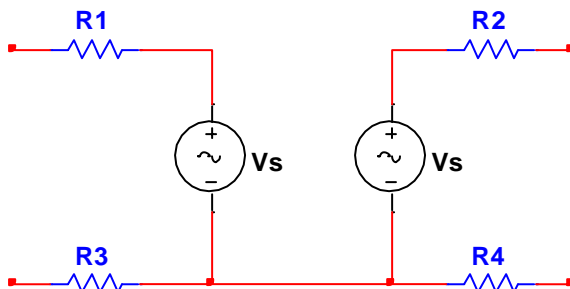


Which is equivalent to,

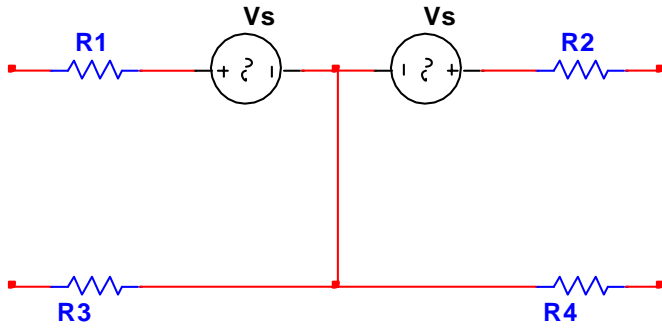

**(ii) Current Source Shifting:-**

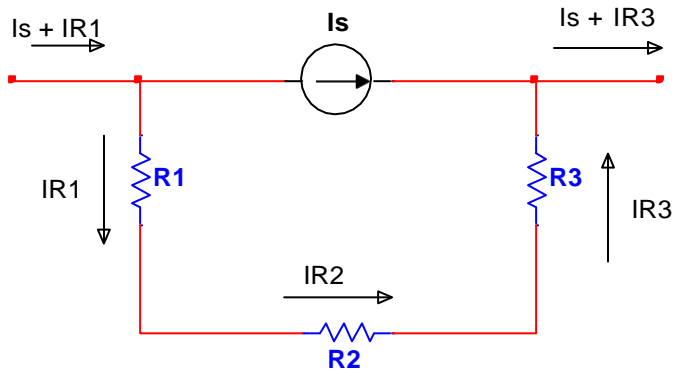


The above circuit can be redrawn as,

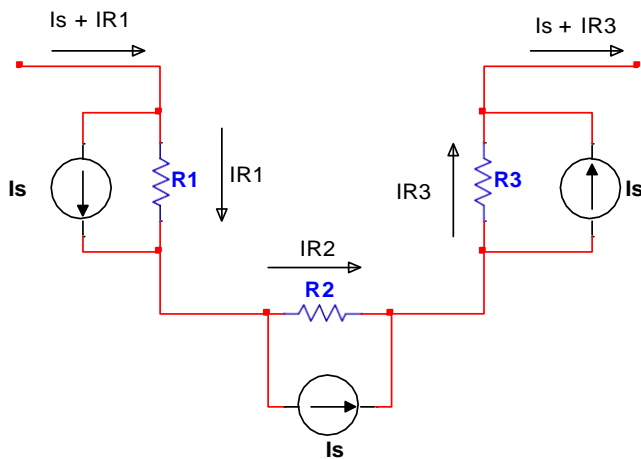


Problems on Source Shifting & Source Transformation:-

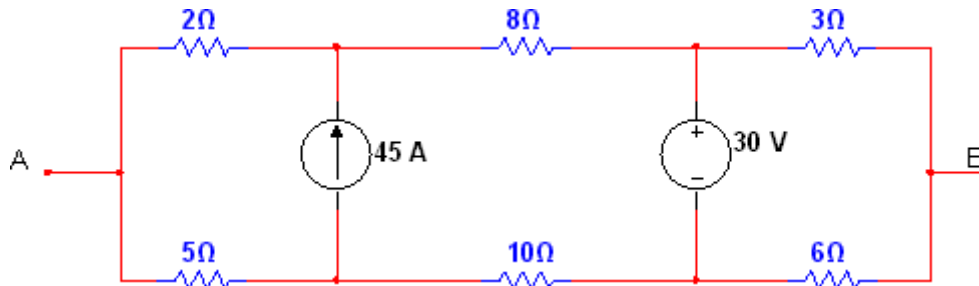- 1) Reduce the network shown to a single voltage source in series with a resistance using source shifting and source transformation.




Solution:-

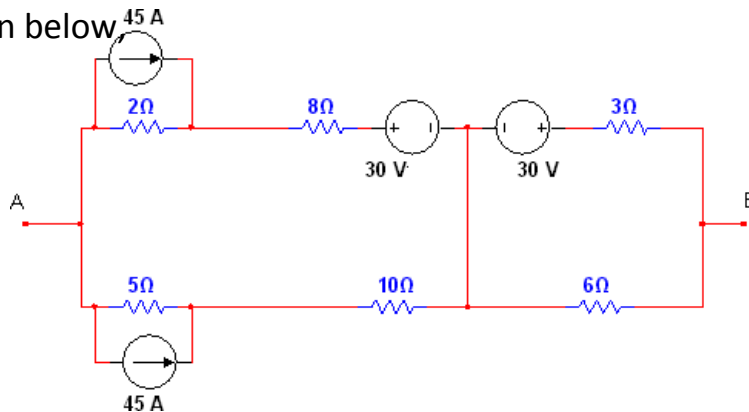Use Source shifting property on both the sources and rewrite the circuit as shown below




Now using Source transformation we get,


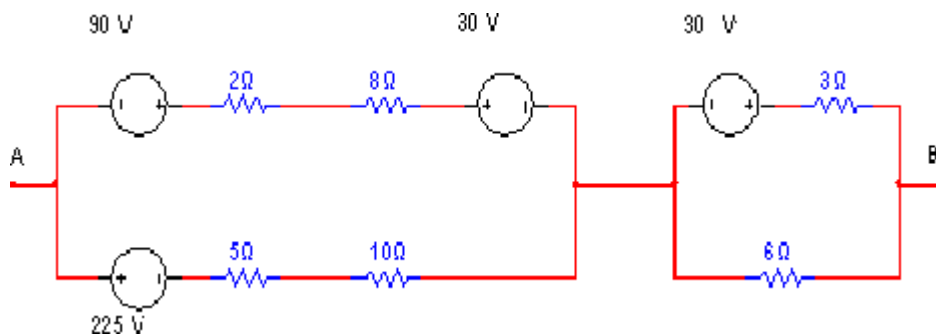


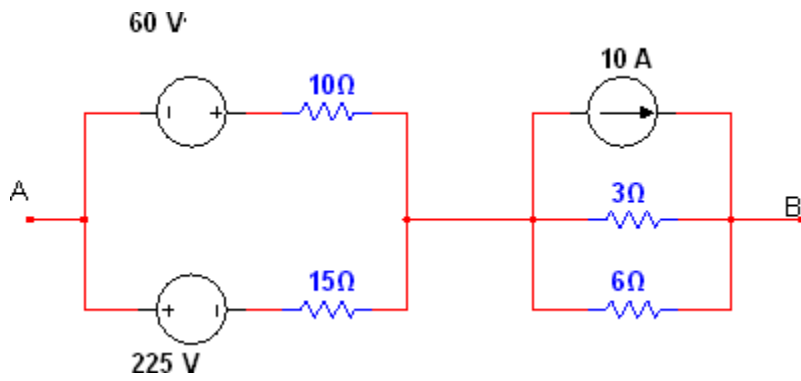
After simplifying the above circuit and applying Source transformation again, we get,





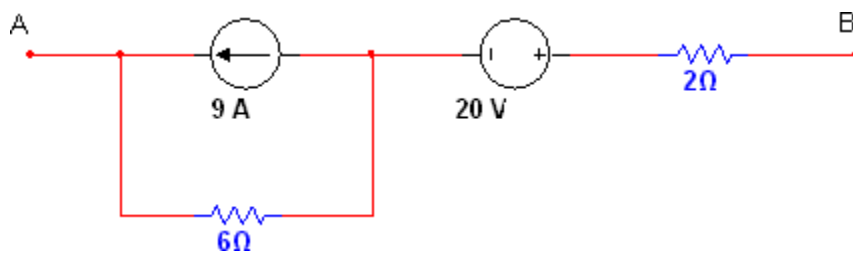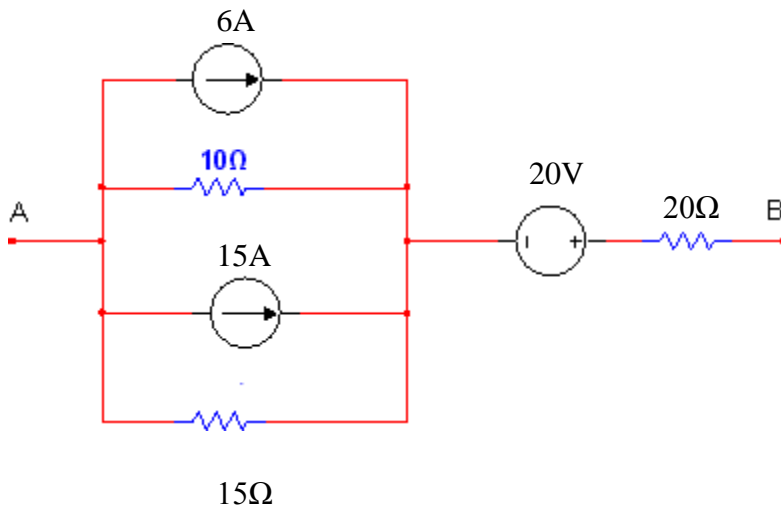
Which can be further simplified using Source transformation yet again,



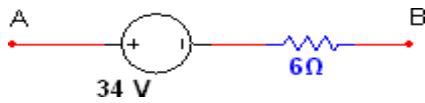





2) Find the voltage across the capacitor of  $20\Omega$  reactance of the network.

20 V

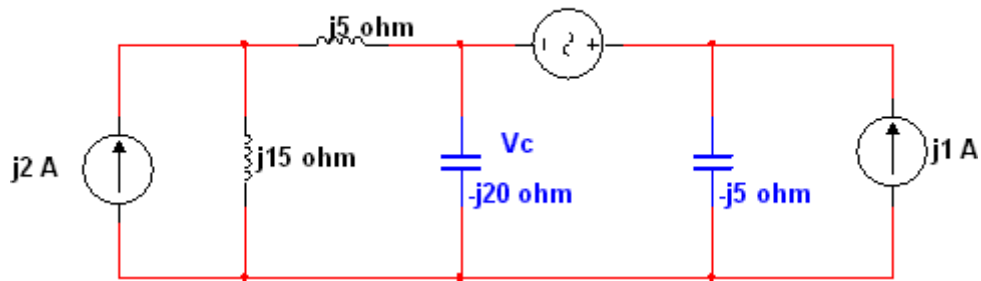

Solution:- Using Source Transformation,

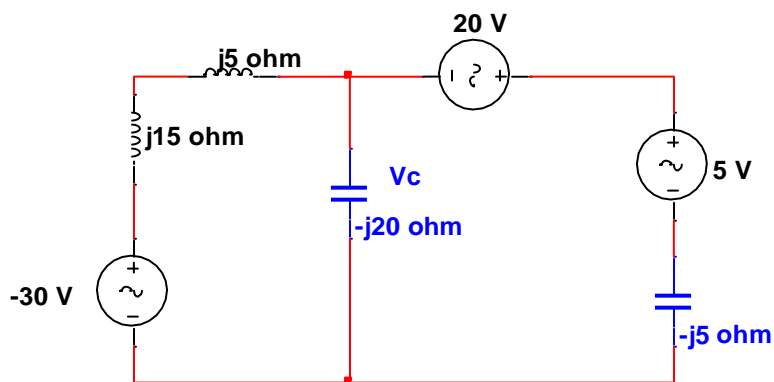

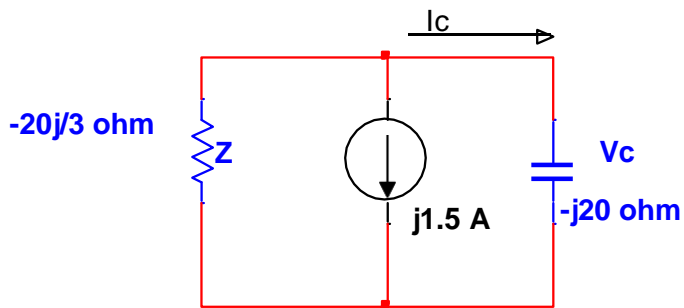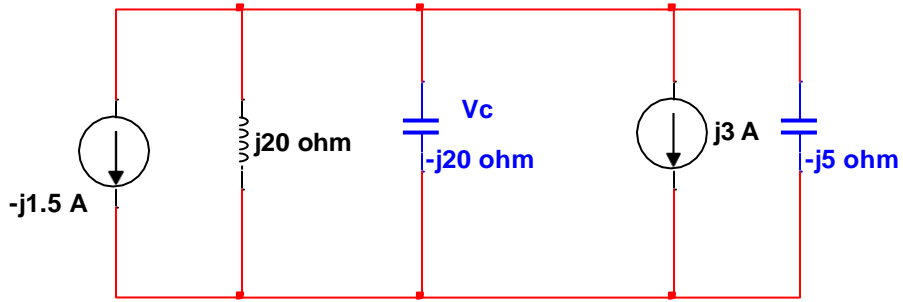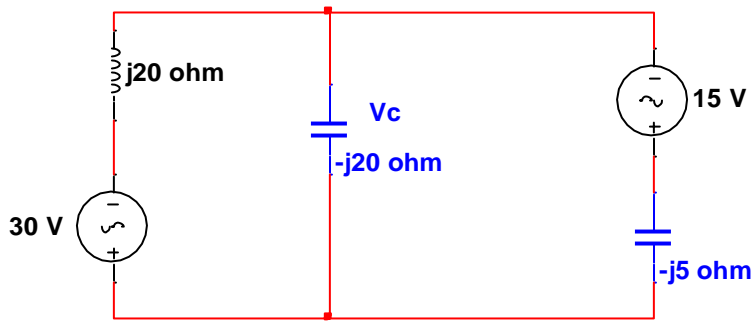

From the above circuit,

$$I_c = \frac{(-j1.5)(-j6.67)}{(-j26.67)}$$

$$\therefore I_c = -j(0.375) \text{ A}$$

$$\therefore V_c = I_c(-j20)$$

$$\therefore V_c = -7.5 \text{ V}$$

## NETWORK ANALYSIS (18EC32)

### Syllabus:-


#### **Module -2**

**Network Theorems:** Superposition, Millman's theorems, Thevenin's and Norton's theorems, Maximum Power transfer theorem

- Unit 4 → Thevenin's theorem ✓
- Norton's theorem ✓
- Maximum power transfer theorem.
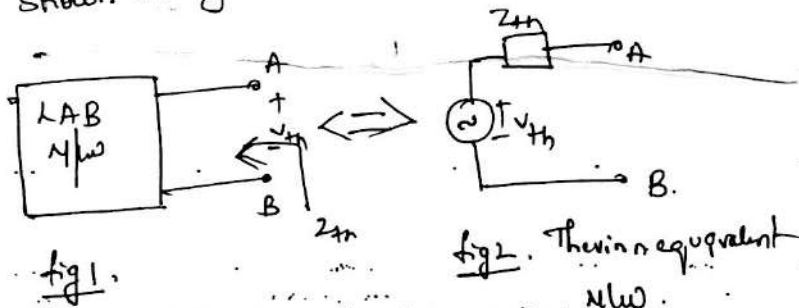
### Thevenin's theorem

→ Any linear, active, bilateral network with two output terminals A and B as shown in fig 1. can be represented by an equivalent voltage source  $V_{th}$  in series with an equivalent impedance  $Z_{th}$  b/w the terminals A-B as shown in fig 2.



where  $V_{th}$  is the Thevenin's voltage which is the open circuit voltage measured across the terminals A-B; and  $Z_{th}$  is the Thevenin's equivalent impedance which is the total impedance measured across the open circuit terminals A-B with all the internal sources set to zero. [voltage source (SC), current source (OC)].

### Norton's theorem

Any linear, bilateral, active network with two output terminals A and B as shown in fig. can be represented by an equivalent current source  $I_N$  in parallel with an equivalent impedance  $Z_N$  b/w the terminals A-B as in fig.

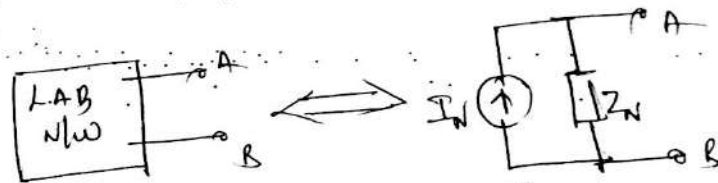



fig. Norton's equivalent circuit.

where  $I_N$  is a Norton's equivalent current which is the circuit current through A-B; and  $Z_N$  is Norton's impedance ( $Z_{th}$ ) which is the equivalent impedance measured across the open circuit terminals with all the internal sources said to be zero. [v.s. → SC, c.s. → OC].


Q

Case 9

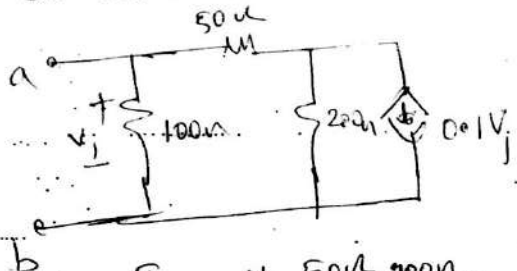Get the Thevenin and Norton equivalent across AB.



soln:

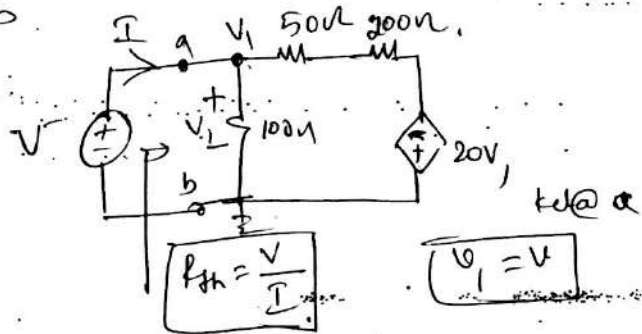

$$P_{th} = \frac{V}{I}$$

$$\frac{V}{I} = V$$

Nodal

$$-I + \frac{V}{100} + \frac{V + 20V}{250} = 0$$


$$V = v_1$$

$$\frac{V}{100} + \frac{V}{250} + \frac{20V}{250} = I$$


$$\Rightarrow \frac{V}{I} = P_{th} = \frac{1}{\frac{1}{100} + \frac{21}{250}} = 10.6 \mu$$




$$V_{th} = 20V + I_N \cdot 10.6 \mu$$

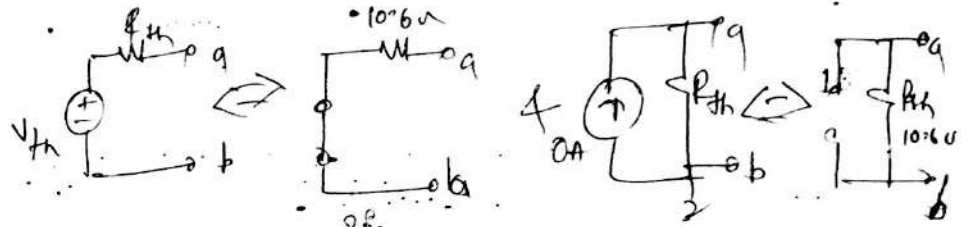

2)

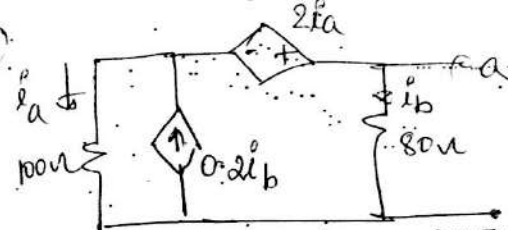

soln:

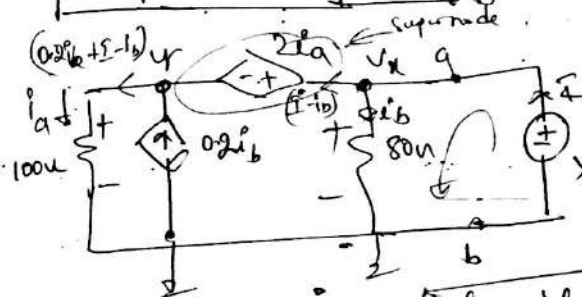

$$i_a = I - 0.8i_b$$

$$I = i_a + 0.8i_b$$

$$V = 80i_b$$

$$V = 80V$$

$$V_x = V_y = 80V$$

$$V_{th} = 20V, I_N = 0A, R_{th} = \frac{V}{I}$$


$$V_x - V_y = 2i_a \text{ and } i_a = \frac{V_y}{100}$$

$$V_x - V_y = 2 \left( \frac{V_y}{100} \right) \text{ --- (1)}$$

$$V = 2 \left[ \frac{1}{50} + 1 \right] V_y = \frac{51}{50} V_y$$

$$100i_a + 2i_a - 80i_b = 0 \Rightarrow 102i_a = 80i_b$$

Step 1, find  $V_{th}$ .

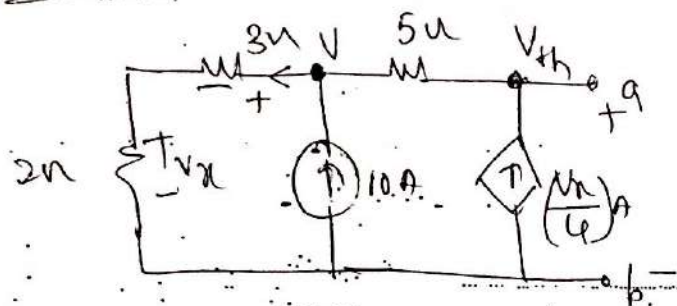

$$V_x = V_{2\Omega} = I_{2\Omega} \cdot 2 = \left(\frac{V-0}{3+2}\right) \cdot 2$$

$$V_x = \frac{2}{5}V \text{ with}$$

⇒ Nodal

$$\frac{V}{5} - 10 + \frac{V - V_{th}}{5} = 0$$

$$2V - V_{th} = 50 \rightarrow \textcircled{1}$$

⇒ Nodal

$$\frac{V_{th} - V}{5} - \frac{V_x}{4} = 0$$

$$\frac{V_{th} - V}{5} - \frac{2V}{5 \times 4} = 0$$


$$5V_{th} - 5V - 10V = 20$$

$$V = \frac{2}{3}V_{th} \rightarrow \textcircled{2}$$

$$V - \frac{2}{3}V_{th} = 0 \rightarrow \textcircled{1a}$$

solving  $\textcircled{1}$  &  $\textcircled{2a}$   $V_{th} = 150 \text{ Volts}$

Step 2: find  $I_{sc}$

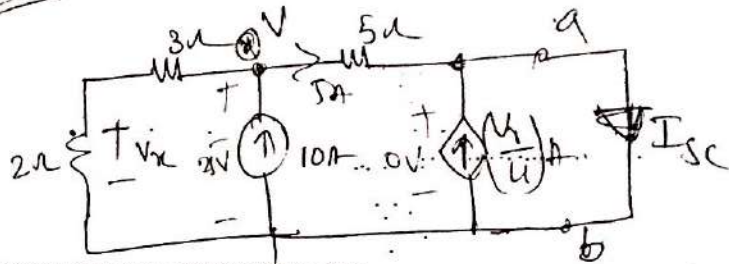

kill @ a

$$\frac{V}{5} - 10 + \frac{V}{5} = 0$$


$$V = 25 \text{ Volts} \quad (V_x = 10 \text{ Volts})$$

$$I_{sc} = \frac{25}{5} = 5A$$


$$I_{sc} = 5 + \frac{V_x}{4} = 5 + \frac{10}{4}$$

$$= \frac{15}{2}A$$
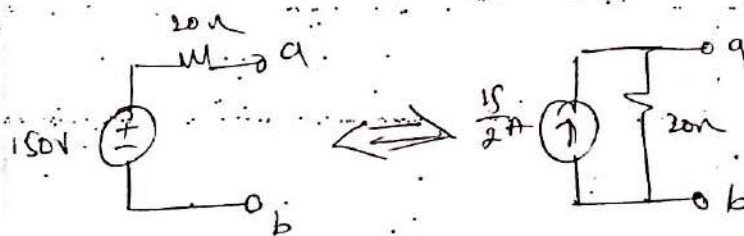
$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{150}{(15/2)} = 20\Omega$$





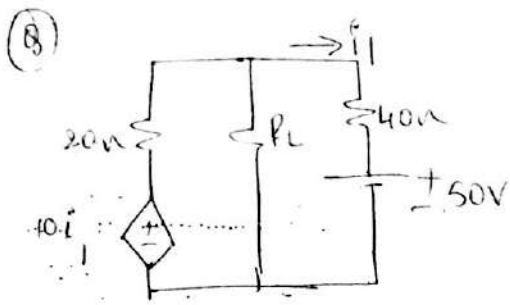


Get the thevenin + Norton equivalent across the RL

Soln

$$R_{th} = \frac{V_{th}}{I_N} = \frac{V_{th}}{I_{sc}}$$

Step 1 (for  $V_{th} = ?$ )

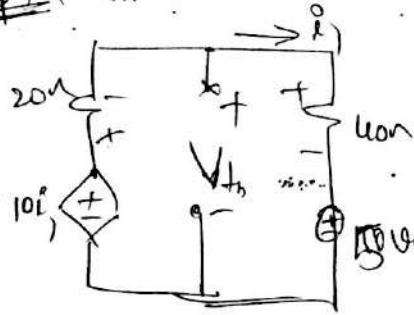

$$10i_1 - 20i_1 - 40i_1 + 50 = 0$$

$$-50i_1 = -50$$


$$i_1 = 1A$$

$$i_1 = -1A$$

$$V_{th} = 40(1) + 50$$

$$V_{th} = 90 \text{ Volts}$$

Step 2

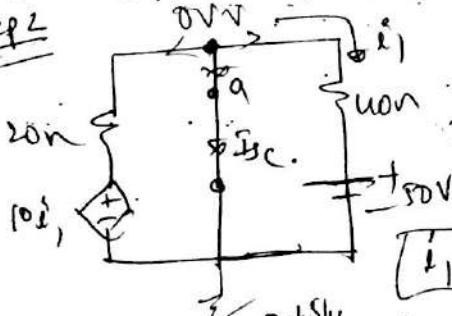

$$\frac{V - 10i_1}{2} + I_{sc} + \frac{V - 50}{40} = 0$$

$$i_1 = \frac{V - 50}{40}$$


$$V = 0 \text{ Volts}$$

$$I_1 = -5/4 A$$

$$\frac{0 + 5/4}{20} = \frac{5}{80} A$$

$$\frac{5}{80} + I_{sc} - 5/4 = 0$$

$$I_{sc} = 5/4 - 5/80$$

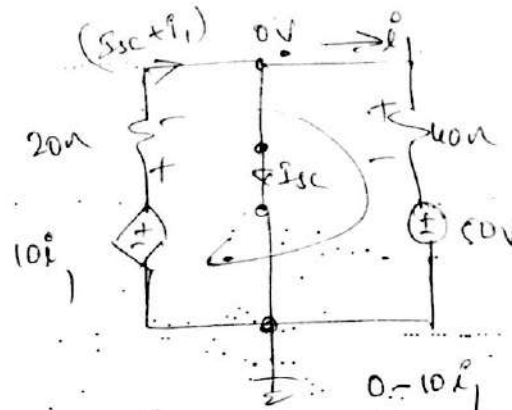

$$\frac{0 - 10i_1}{20} + I_{sc} + i_1 = 0$$

$$I_{sc} = ?$$

$$i_1 = \frac{0 - 50}{40} = -5/4 A$$

$$10i_1 - 20(I_{sc} + i_1) - 40(i_1) - 50 = 0$$


$$10(-5/4) - 20(I_{sc} - 5/4) - 40(-5/4) - 50 = 0$$

$$-\frac{50}{4} - 20I_{sc} + \frac{100}{4} + \frac{200}{4} - 50 = 0$$

$$I_{sc} = 5/8 = 0.625 \text{ Amps}$$

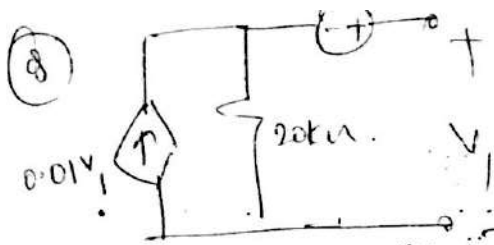
$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{90}{5/8} = \frac{80}{5} = 16 \Omega$$





Soln:  $V_{th} = V_1 = ?$   $I_d = I_{sc} = ?$

$$R_{th} = \frac{V_{th}}{I_{sc}}$$

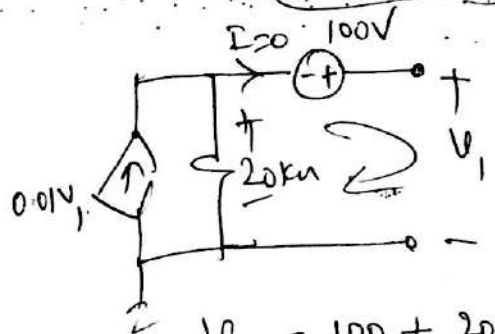


$$V_1 = 100 + 20k(0.01V_1)$$

$$V_1 - 20k(0.01)V_1 = 100$$

$$V_1 = \frac{100}{[1 - 20k(0.01)]} = -0.502512mV$$



$$V_1 = V_{th} = -502.512mV$$

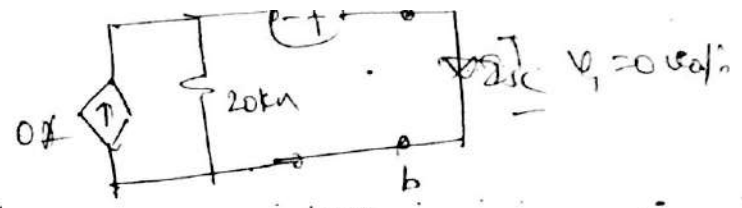


$$I_{sc} = \frac{100}{20k}$$


$$I_{sc} = 5mA$$
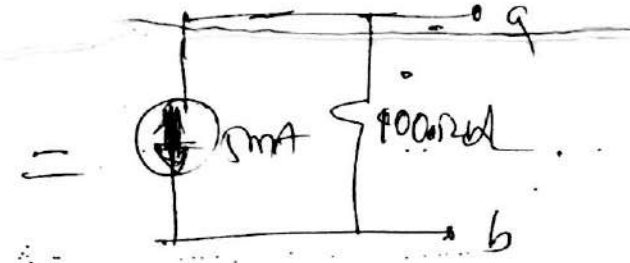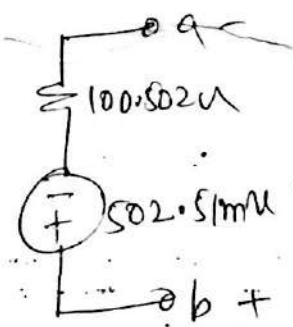
$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{-502.512mV}{5mA} = -100.502\Omega$$



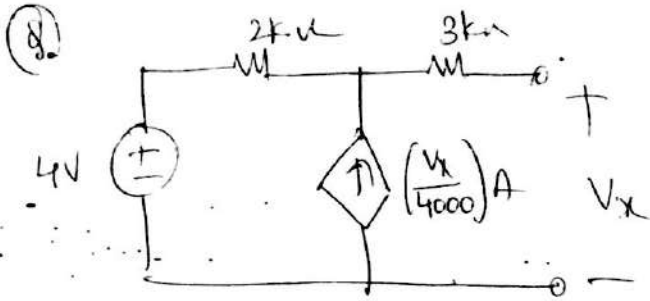


Solusi

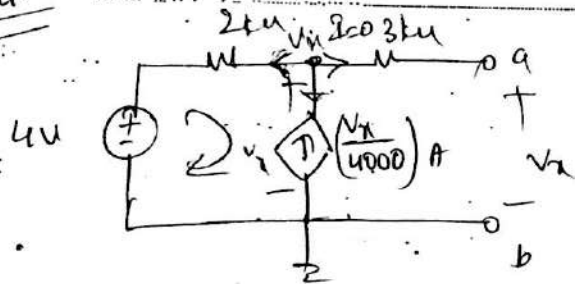


$$\frac{V_x - 4}{2k} - \frac{V_x}{4000} = 0$$
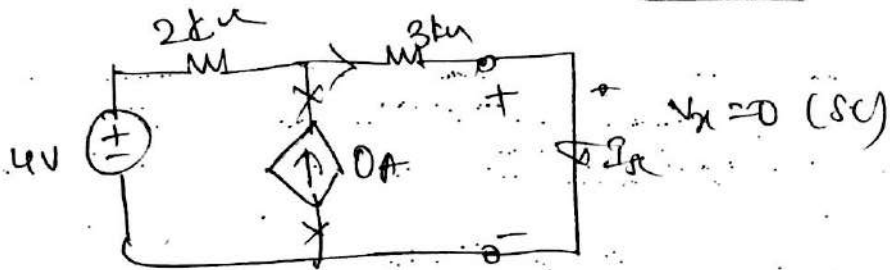
$$V_x = 8 \text{ volt} \Rightarrow V_{th} = 8 \text{ volt}$$





$$I_{sc} = \frac{4}{2k + 3k} = \frac{4}{5k} = \frac{4}{5} \text{ mA}$$
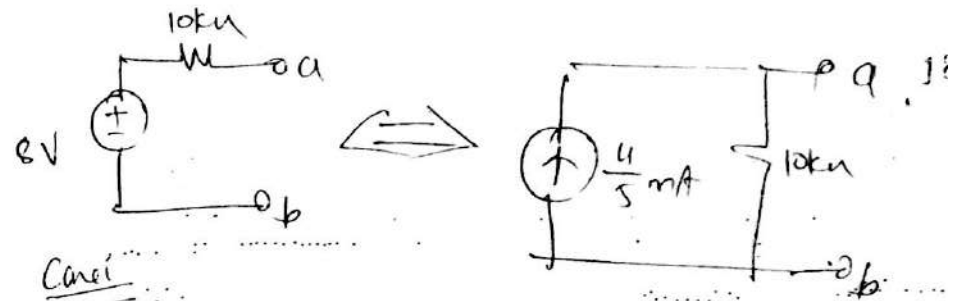
$$P_{th} = \frac{V_{th}}{I_{sc}} = \frac{8}{(4/5 \text{ mA})} = 10 \text{ k}\Omega$$




Consi

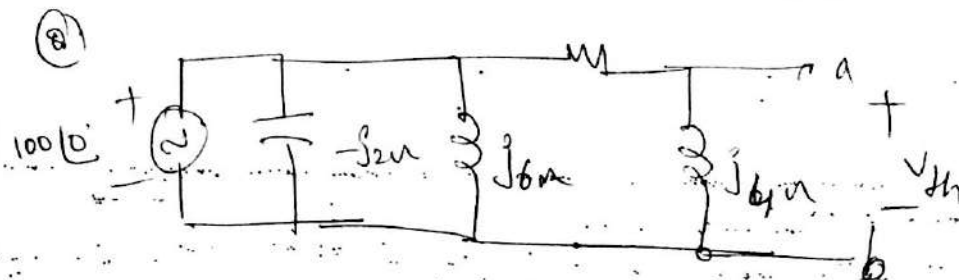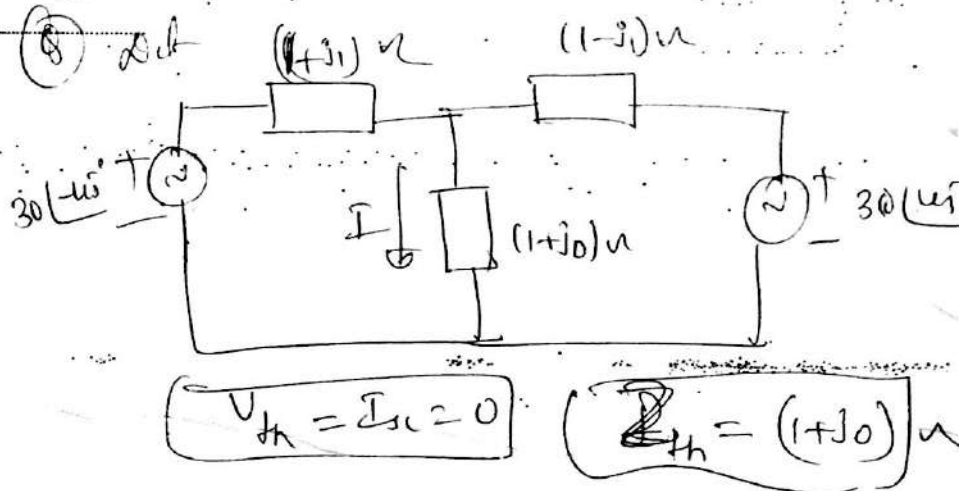

$$V_{th} = I_6 (3 - j4) \text{ volt}$$

$$Z_{th} = (3 \parallel j4)$$

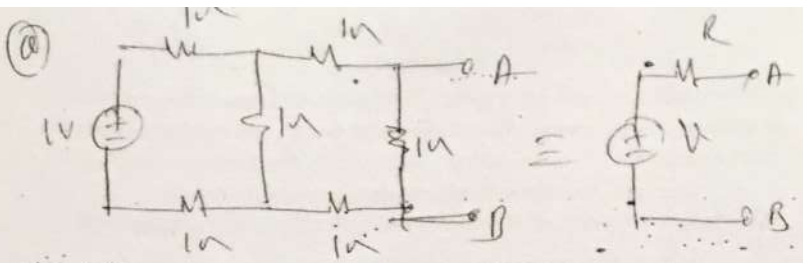

$V = \frac{1}{11} \text{ volt}$

$R_{th} = \frac{8}{11} \Omega$

### MISSION

Provide quality and contemporary education, in the domain of Electronics and communication and related fields, which enable collaborative ventures with industries and research organizations. Emphasis laid on creating innovative teaching-learning processes that motivate self-learning, by imparting quality education embedded with discipline & national honor.

### VISION

To create a rich intellectual potential implanted with multidisciplinary knowledge, human values and professional ethics among the aspirant of becoming Engineers and technologies, so as to unlock their imagination and discover their potential.

### OBJECTIVES

1. To impart good technical knowledge to the students.
2. To produce Excellent Engineers in Electronics & Communication fields.
3. To fulfil the needs of the society in the various fields related to Electronics and Communication engineering.
4. To bring post-graduate program in the diverse field of electronics and communication Engineering.
5. To upgrade the facilities in Research & Development Centre of the department with the use of modern aids.
6. To organize training programs / workshops for upgrading staff performance.
7. To establish Industry-Institute Interaction.
8. To publish technical papers in National / International journals and conferences.

### GOALS (Short Term):


1. Modernizing the Laboratories with new software & state-of-the art hardware in tune with the latest technological developments.
2. To obtain Quality certification from an agency of reputed.
3. Teaching Aids : LCD Projector, Smart Boards.
4. Promoting Faculty Development Programmes.
5. Conducting the need based training programs for Faculty & Students.
6. To improve the pass percentage 2-5% compared to previous year.

### GOALS (Long Term):

1. To start additional P.G. Programmes in Electronic and Communication engineering discipline.
2. To enter into understanding with globally renowned universities for special programmes in emerging technologies.
3. Promoting Industry - Institute interaction through projects and R & D work.
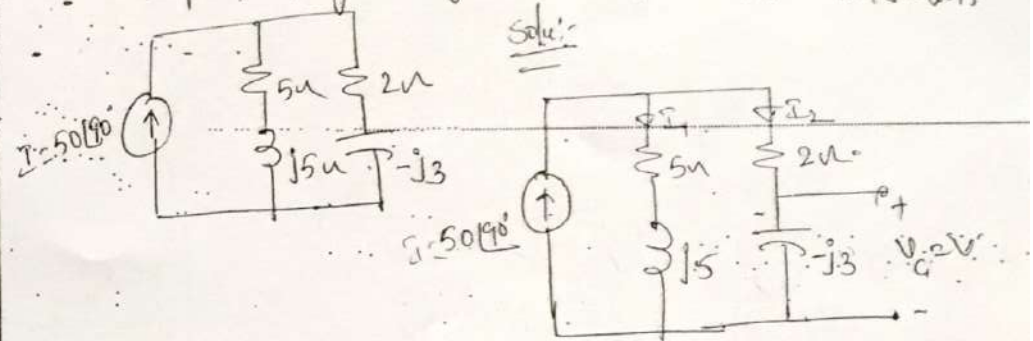
## Problem on Reciprocity theorem

- ① Verify reciprocity theorem for the netw shown in fig. 1  
 Response being voltage across the capacitor  
 6m. De/Jan 2015



using BCM

$$I_2 = \frac{I \times Z_1}{Z_1 + Z_2}$$

$$I_2 = \frac{50 \angle 90^\circ [5 + j5]}{(5 + j5 + 2 - j3)} = \frac{48564 \angle 119.05^\circ \text{ Amp-ohm}}{48.564 \angle 119.05^\circ}$$


$$V = V_c = I_2 (-j3) = 48564 \angle 119.05^\circ \times (-j3)$$

$$V = 145569 \angle 29.05^\circ \text{ volt} = 145.569 \angle 29.05^\circ \text{ volt}$$

the ratio of  $\frac{I}{V} = \frac{50 \angle 90^\circ}{145.569 \angle 29.05^\circ} = 0.3431 \angle 60.94^\circ$

Now interchange the source & response.

ie

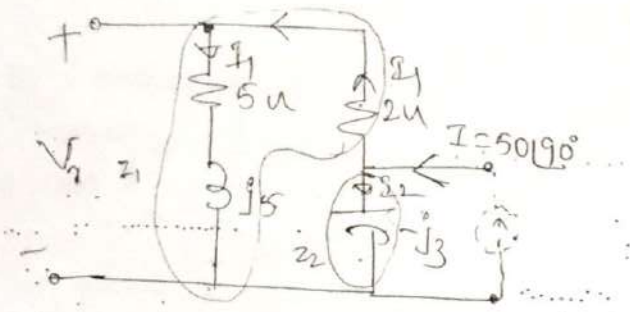

using BCM 
$$I_1 = \frac{I_0 Z_2}{Z_1 + Z_2}$$

$$Z_1 = (5 + j5) = (7 + j5) \mu$$

$$Z_2 = -j3 \mu$$

$$I_1 = \frac{50 \angle 90^\circ \cdot [-j3]}{7 + j5 - j3} = 20.604 \angle -15.945 \text{ Amp-}\mu$$

$$V_1 = I_1 \cdot [5 + j5] = 20.604 \angle -15.945 \times (5 + j5)$$

$$V = 145 \angle 29.05 \text{ volts}$$


$$\frac{I}{V} = \frac{50 \angle 90^\circ}{145 \angle 29.05} = 0.34431 \angle 60.94 \leftarrow \textcircled{2}$$

eq 1 = eq 2


∴ Reciprocity theorem is verified.

2) State and prove reciprocity theorem (6m) Dec 14/Jan 15. Sh. ref. notes.

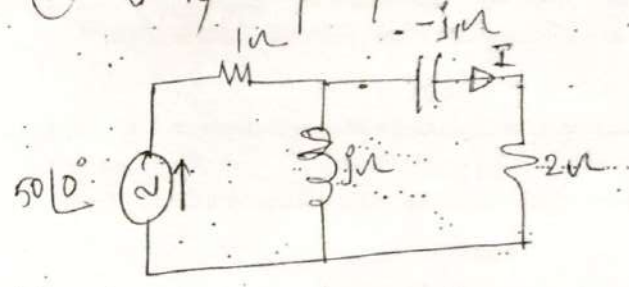3) Verify reciprocity theorem for the ckt shown in fig.



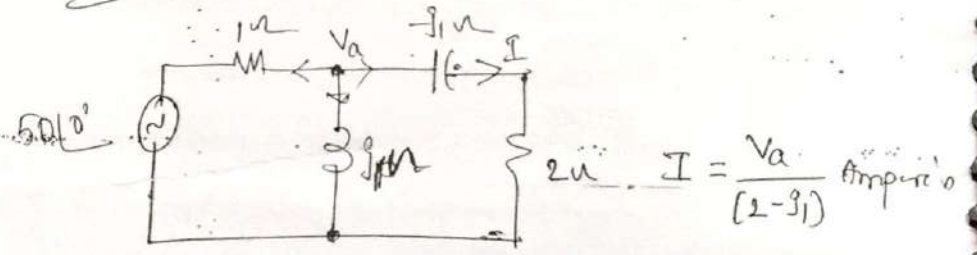Sol:  $V = 50 \angle 0^\circ$  ← i/p  $I \leftarrow$  o/p (response)



KVL @ a 
$$\frac{V_a - 50 \angle 0^\circ}{1} + \frac{V_a}{j1} + \frac{V_a}{2 - j1} = 0$$



$$V_a [1 + (j1)^{-1} + (2 - j1)^{-1}] = 50 \angle 0^\circ$$

$$V_a = \frac{50 \angle 0^\circ}{1.6124 \angle -29.74} = 31.008 \angle 29.744$$

$$V_a = 31.008 \angle 29.744 \text{ volt}$$
 and  $\frac{50 \angle 0^\circ}{13.867 \angle 56.30} = \frac{V}{I}$

$$\Rightarrow I = \frac{V_a}{(2 - j1)} = \frac{31.008 \angle 29.744}{(2 - j1)} = 13.867 \angle 56.30 \text{ Amp-}\mu$$

Now interchange the i/p and o/p's.

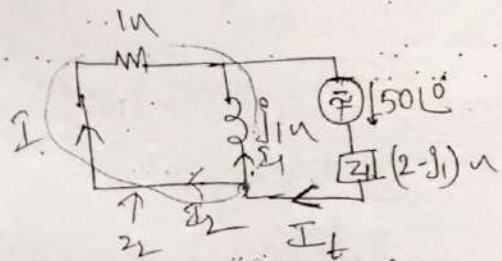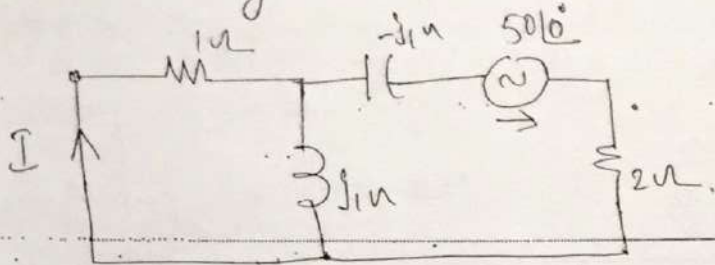

$$Z_2 = 1 \parallel j_1 = \frac{j_1}{(1+j_1)} = (0.5 + j0.5) \Omega$$

$$Z_T = Z_1 + Z_2 = (2-j1) + (0.5 + j0.5) = (2.5 - j0.5) \Omega$$

$$I = \frac{50 \angle 0^\circ}{Z_T} = \frac{50 \angle 0^\circ}{(2.5 - j0.5)} = 19.6116 \angle 11.309^\circ \text{ Amperes}$$

using BCM

$$I = \frac{I_1 \cdot (j_1)}{(1+j_1)} = \frac{19.6116 \angle 11.309^\circ \times (j_1)}{(1+j_1)}$$

$$I = 13.867 \angle 56.309^\circ \text{ Amperes}$$


$$\frac{V}{I} = \frac{50 \angle 0^\circ}{13.867 \angle 56.309^\circ} = 3.605 \angle -56.309^\circ \leftarrow \textcircled{2}$$

Reciprocity theorem is satisfied.

(4) State and prove reciprocity theorem. (5m). Jan 2004 (5m)

Soln - repeated question.

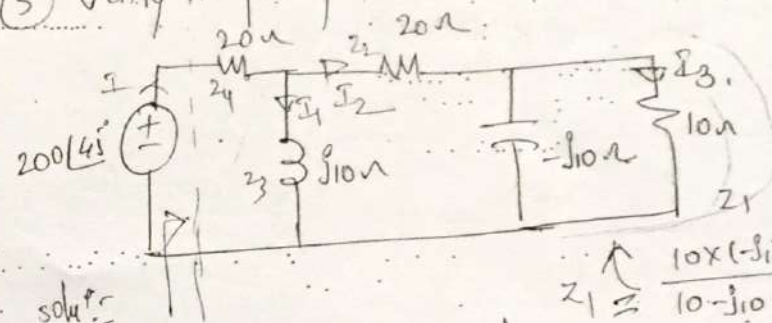(5) Verify reciprocity theorem for the value of fig. with response.



Soln

$$Z_4 = 20$$

$$Z_1 = \frac{10 \times (-j10)}{10 - j10} = (5 - j5) \Omega$$

$$(Z_1 + Z_2) = 20 + (5 - j5) = (25 - j5) \Omega$$

$$Z_3 \parallel (Z_2 + Z_1)$$

$$= \frac{(25 - j5) \times j10}{25 - j5 + j10}$$


$$= (3.8461 + j9.23) \Omega$$

$$Z_T = Z_4 + [Z_3 \parallel (Z_2 + Z_1)]$$

$$= 20 + (3.8461 + j9.23) = (23.8461 + j9.23) \Omega$$

$$I = \frac{V}{Z_T} = \frac{200 \angle 45^\circ}{(23.8461 + j9.23)} = 7.82 \angle 23.83^\circ \text{ Amperes}$$
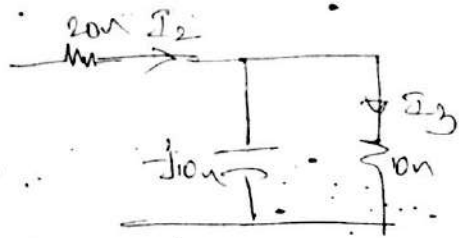
$$I_2 = \frac{I [Z_3]}{[Z_3 + (Z_2 \parallel Z_1)]} = \frac{7.82 \angle 23.83^\circ (j10)}{[j10 + 25 - j5]} = 3.067 \angle 102.52^\circ \text{ Amperes}$$




$$I_3 = \frac{I_2 (-j10)}{(-j10 + 10)} = \frac{3.067 \angle 102.52^\circ (-j10)}{(10 - j10)}$$

$$I_3 = 2.169 \angle 57.52^\circ \text{ Ampere}$$

$$\frac{V}{I_3} = \frac{200 \angle 45^\circ}{2.169 \angle 57.52^\circ} = 92.195 \angle -12.52^\circ$$

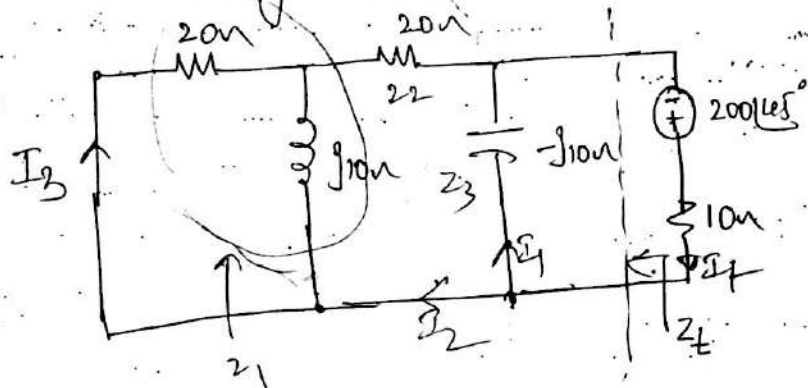Now interchange the i/p and o/p.  $\leftarrow \textcircled{V}$



$$Z_1 = 20 \parallel j10 = (4 + j8) \Omega$$

$$Z_1 + Z_2 = 4 + j8 + 20 = (24 + j8) \Omega$$

$$(Z_1 + Z_2) \parallel Z_3 = Z_4 = (24 + j8) \parallel (-j10) = (4.1379 - j9.7)$$

$$I_t = \frac{200 \angle 45^\circ}{(10 + Z_4)} = \frac{200 \angle 45^\circ}{(10 + 4.1379 - j9.65)}$$

$$I_t = 11.682 \angle 79.33^\circ \text{ Ampere}$$

$$I_2 = \frac{I_t (Z_3)}{(Z_1 + Z_2 + Z_3)} = \frac{11.682 \angle 79.33^\circ (-j10)}{24 + j8 + (-j10)}$$

$$I_2 = 4.8507 \angle 174.09^\circ \text{ Ampere}$$

$$I_3 = \frac{I_2 (j10)}{20 + j10} = \frac{4.8507 \angle 174.09^\circ (-j10)}{20 + j10}$$

$$I_3 = 2.169 \angle -12.52^\circ \text{ Ampere} = 2.169 \angle 57.52^\circ$$


$$\frac{V}{I_3} = \frac{200 \angle 45^\circ}{2.169 \angle 57.52^\circ} = 92.195 \angle -12.52^\circ$$

$\textcircled{V} = \textcircled{I}$  Reciprocity theorem is verified.



In the <sup>single</sup> Superposition Current source shown by the voltage  $V_x$  interchange the Current source and Resulting voltage  $V_x$ , in the Reciprocity theorem verified? (6m)

5/5 2013.

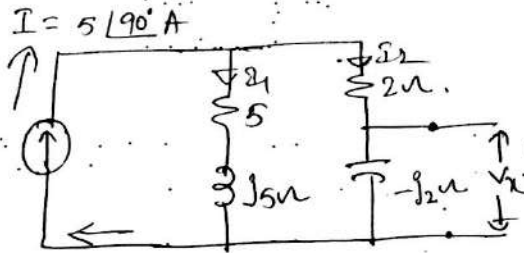

Sol<sup>n</sup> i/p  $I = 5∠90^\circ A$  o/p  $V_x = V_n$

Repeated question by to Q no. 1

Dec-Jan 2015

$$I_2 = \frac{5∠90^\circ [5+j5]}{[5+j5] + [2-j2]} = \frac{4.642 \angle 111.8^\circ}{2.707 \angle 135^\circ} \text{ Amperes}$$


$$V_2 = I_2 (-j2) = \frac{4.642 \angle 111.8^\circ}{2.707 \angle 135^\circ} (-j2)$$

$$V_x = 3.835 \angle 145^\circ \text{ volts} \quad 9.284 \angle 210.8 \text{ Volts}$$

$$\frac{I}{V_x} = \frac{5∠90^\circ}{3.835 \angle 145^\circ} = 0.414 \angle -55^\circ \quad \leftarrow \text{2}$$

$$\frac{I}{V_x} = \frac{5∠90^\circ}{9.284 \angle 210.8} = 0.5385 \angle 68.19 \quad \leftarrow \text{1}$$

Now interchange the i/p and o/p n.

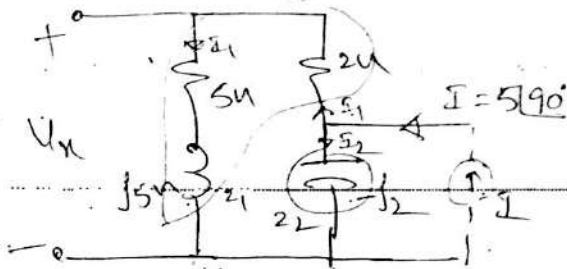

$$I_1 = 8$$

$$V_x = I_1 (5+j5) \text{ volts}$$

$$I_1 = \frac{I Z_2}{Z_1 + Z_2} = \frac{5∠90^\circ [-j2]}{(7+j5) - j2}$$

$$I_1 = 1.313 \angle -23.198 \text{ Amperes}$$


$$V_x = I_1 (5+j5) = 1.313 \angle -23.198 (5+j5)$$

$$V_x = 9.284 \angle 210.814 \text{ Amperes}$$

$$\frac{I}{V_x} = \frac{5∠90^\circ}{9.284 \angle 210.814} = 0.5385 \angle 68.19 \quad \leftarrow \text{1}$$

eq<sup>n</sup> 1 = eq<sup>n</sup> 2 ∴ Reciprocity theorem is verified

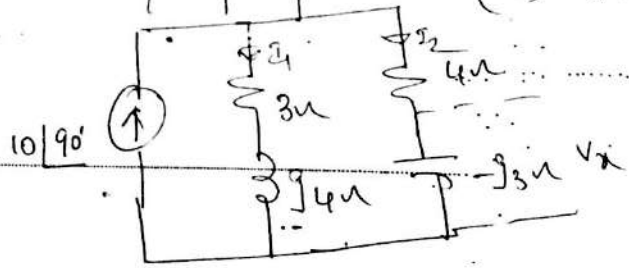7) Det Voltage  $V_x$  in the ckt shown in fig. hence  
Verify reciprocity theorem. (6m) Jun 2012.



Solu:  $I = 10∠90^\circ$  A ← i/p      $V_x = I_2(-j3)$  ← o/p


$$I_2 = \frac{10∠90^\circ [3+j4]}{[3+j4] + [4-j3]} = 7.0071∠135^\circ \text{ Ampere}$$

$$V_x = I_2(-j3) = 7.0071∠135^\circ (-j3)$$

$$V_x = 21.0213∠45^\circ \text{ volt}$$

$$\frac{I}{V_x} = \frac{10∠90^\circ}{21.0213∠45^\circ} = 0.47714∠45^\circ \leftarrow \textcircled{1}$$

also interchange the i/p and o/p n.

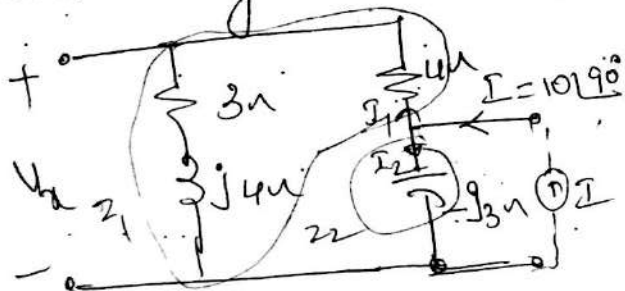

$$I_1 = \frac{I \cdot Z_2}{Z_1 + Z_2} = \frac{10∠90^\circ [-j3]}{[4+3+j4] + [-j3]}$$

$$I_1 = 4.2426∠-80.130^\circ \text{ Ampere}$$


$$V_x = I_1(3+j4) = 4.2426∠-80.130^\circ [3+j4]$$

$$V_x = 21.0213∠45^\circ \text{ volt}$$

$$\frac{I}{V_x} = \frac{10∠90^\circ}{21.0213∠45^\circ} = 0.47714∠45^\circ \leftarrow \textcircled{2}$$

Eq<sup>n</sup> ① = Eq<sup>n</sup> ② ∴ Reciprocity theorem is verified.

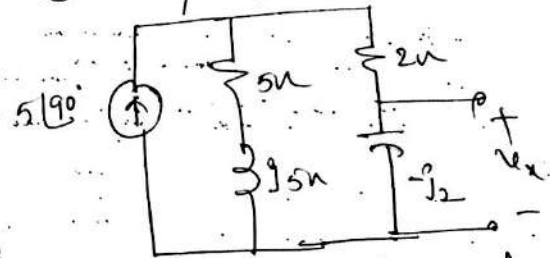8) Verify reciprocity theorem for the ckt. shown in fig.  
Dec 2012. (6m)




Solu: repeated question. refer (Q.7)

Q7 Find  $i_x$  and hence verify reciprocity theorem for the network shown in fig.

Shown in fig.


(8m)

J/J 2014

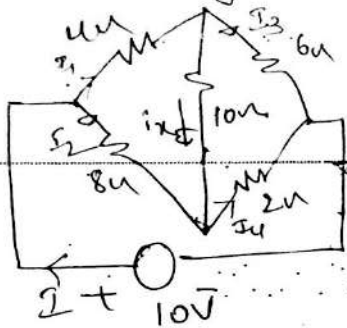

Soln: i/p  $V = 10$  volts o/p  $i_x = ?$

Q8

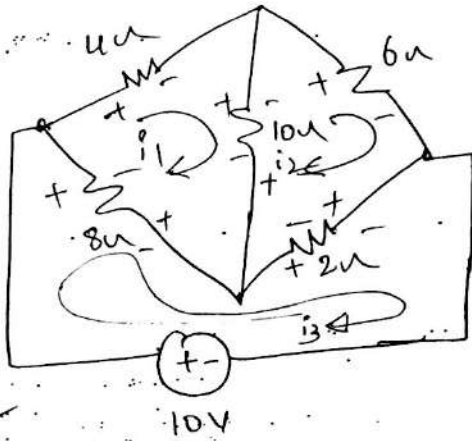

Soln

Loop 1

$$-4i_1 - 10(i_1 - i_2) - 10(i_1 - i_3) = 0$$

$$-4i_1 - 10i_1 + 10i_2 - 8i_1 + 8i_3 = 0$$

$$-22i_1 + 10i_2 + 8i_3 = 0 \quad \leftarrow (1)$$

Loop 2

$$-10(i_2 - i_1) - 6i_2 - 2(i_2 - i_3) = 0$$

$$-10i_2 + 10i_1 - 6i_2 - 2i_2 + 2i_3 = 0$$

$$10i_1 - 18i_2 + 2i_3 = 0 \quad \leftarrow (2)$$

Loop 3

$$10 - 8(i_3 - i_1) - 2(i_3 - i_2) = 0$$

$$10 = 8(i_3 - i_1) + 2(i_3 - i_2)$$

$$10 = 8i_3 - 8i_1 + 2i_3 - 2i_2$$

$$-8i_1 - 2i_2 + 10i_3 = 10 \quad \leftarrow (3)$$

Soln by eq (1), (2), (3)  $i_1 = 1.171$  Ampere


$$i_2 = 0.8857 \text{ Ampere}$$

$$i_3 = 2.0142 \text{ Ampere}$$

o/p  $i_x = (i_1 - i_2) = 1.171 - 0.8857 = 0.2853 \text{ Ampere}$

$$\frac{V}{i_x} = \frac{10}{0.2853} = 35.05 \quad \leftarrow (1)$$

Now interchange the positions of i/p and o/p.

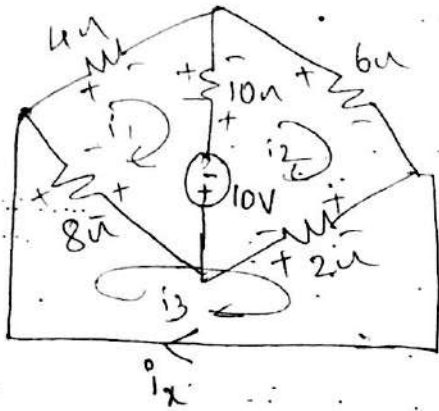

Loop 1

$$-4i_1 - 10(i_1 - i_2) + 10 - 8(i_1 - i_3) = 0$$

$$-4i_1 - 10i_1 + 10i_2 + 10 - 8i_1 + 8i_3 = 0$$

$$-22i_1 + 10i_2 + 8i_3 = -10 \quad \leftarrow \textcircled{1}$$

Loop 2

$$-10 - 10(i_2 - i_1) - 6i_2 - 2(i_2 - i_3) = 0$$

$$-10 - 10i_2 + 10i_1 - 6i_2 - 2i_2 + 2i_3 = 0$$

$$10i_1 - 18i_2 + 2i_3 = 10 \quad \leftarrow \textcircled{2}$$

Loop 3

$$-8(i_3 - i_1) - 2(i_3 - i_2) = 0$$

$$-8i_3 + 8i_1 - 2i_3 + 2i_2 = 0$$

$$8i_1 + 2i_2 - 10i_3 = 0 \quad \leftarrow \textcircled{3}$$

Solving eq<sup>n</sup> ①, ②, ③

$$i_1 = 0.428 \text{ A}, \quad i_2 = -0.2857 \text{ A}, \quad i_3 = 0.2857 \text{ A}$$


$$i_3 = i_a = 0.2853 \text{ Ampere}$$

$$\frac{V}{i_3} = \frac{10}{0.2853} = 35.05 \quad \leftarrow \textcircled{?}$$

eq<sup>n</sup> ① = eq<sup>n</sup> ② ∴ Reciprocity theorem is verified

⑩ State and explain the reciprocity theorem. (5m) Jan 2013  
 sol<sup>n</sup> repeated question.



Millman's theorem:-

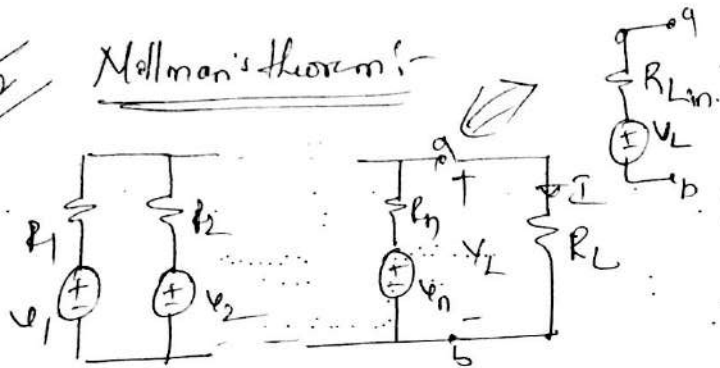

$$V_L = \frac{v_1 Y_1 + v_2 Y_2 + v_3 Y_3 + \dots + v_n Y_n}{Y_1 + Y_2 + Y_3 + \dots + Y_n} \text{ volt/n}$$

$$R_{L'n} = \frac{1}{Y_1 + Y_2 + Y_3 + \dots + Y_n}$$

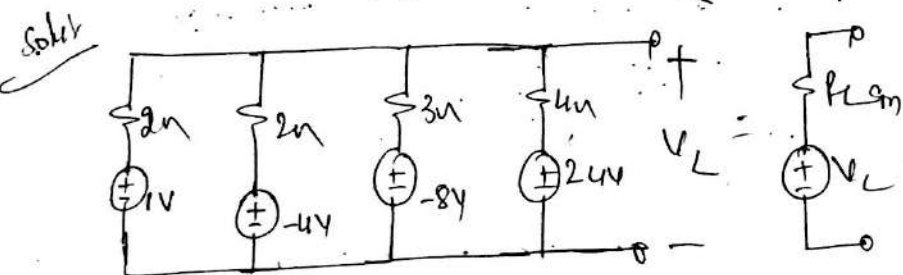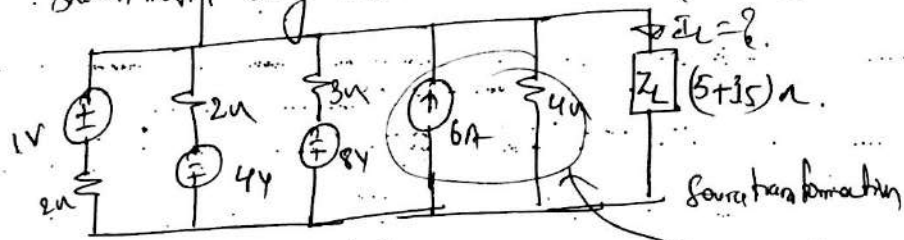(Q1) Find the current through the load impedance  $Z_L$  for the circuit shown in fig. using millman's theorem. 6m. (Jen 2015)



$$I_L = \frac{V_L}{(Z_L + R_{L'n})} \text{ Amp/n}$$


$$V_L = \frac{v_1 Y_1 + v_2 Y_2 + v_3 Y_3 + v_4 Y_4}{Y_1 + Y_2 + Y_3 + Y_4}$$

$$V_L = \frac{1(2)^{-1} + (-4)(2)^{-1} + (-8)(3)^{-1} + (24)(4)^{-1}}{2^{-1} + 2^{-1} + 3^{-1} + 4^{-1}}$$

$$V_L = 1.15789 \text{ volt/n}$$


$$R_{L'n} = \frac{1}{Y_1 + Y_2 + Y_3 + Y_4} = \frac{1}{(2^{-1} + 2^{-1} + 3^{-1} + 4^{-1})}$$

$$R_{L'n} = 0.6315 \Omega$$

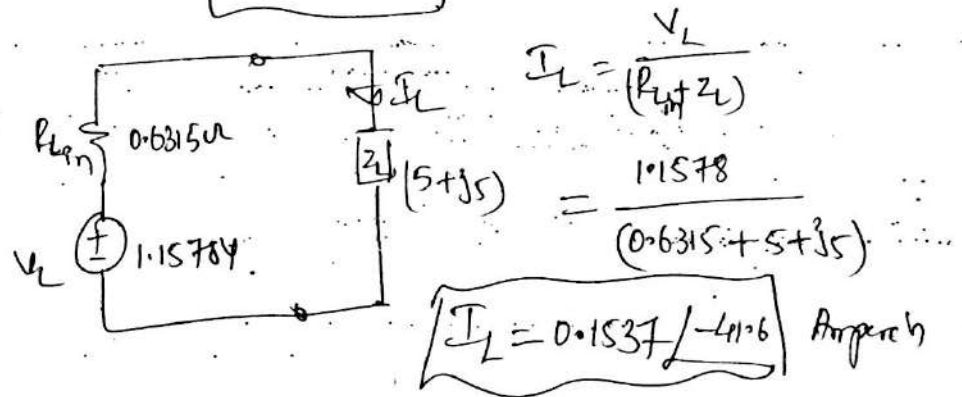


3

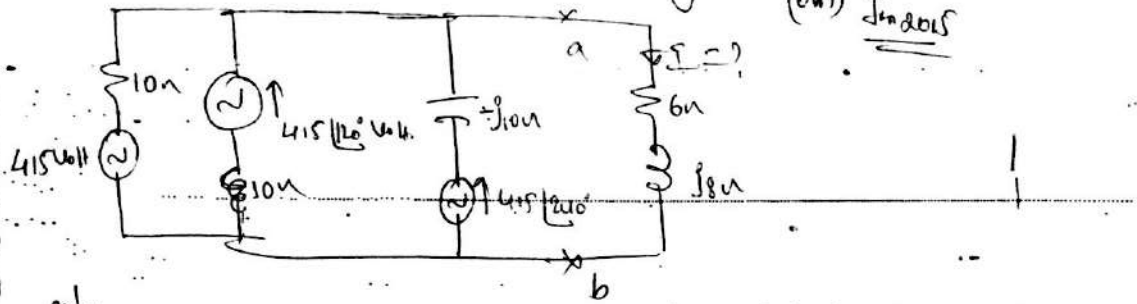For the ckt shown in fig. find Current 'I' using millman's theorem. (6m)  $I_{ind}$



Solu

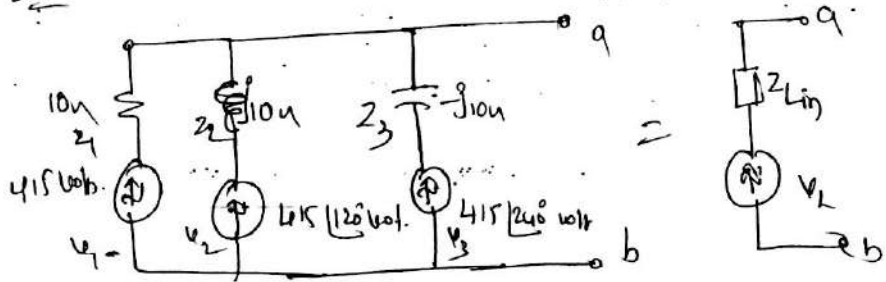


$$V_L = \frac{V_1 Y_1 + V_2 Y_2 + V_3 Y_3}{Y_1 + Y_2 + Y_3}$$

$$V_L = \frac{415(10)^{-1} + 415 \angle 120^\circ (310)^{-1} + 415 \angle 240^\circ (-j10)^{-1}}{(10)^{-1} + (310)^{-1} + (-j10)^{-1}}$$

$$V_L = 1133.80 \angle 0^\circ \text{ volt}$$

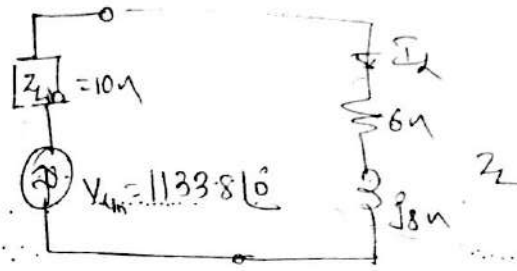
$$Z_L = \frac{1}{Y_1 + Y_2 + Y_3} = \frac{1}{10^{-1} + (j10)^{-1} + (-j10)^{-1}} = 10 \Omega$$




$$I_2 = \frac{V_{Th}}{Z_{L1} + Z_L} = \frac{1133.8 \angle 0^\circ}{10 + 6 + j5}$$


$$I_2 = 63.381 \angle -26^\circ \text{ amp}$$

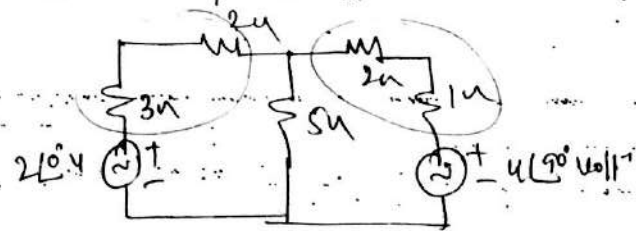4 Find the power delivered by the 5Ω resistor in the circuit shown in fig. and find the current supplied by each source. use millman's principle. (8m)



Solu Qu. write the ckt

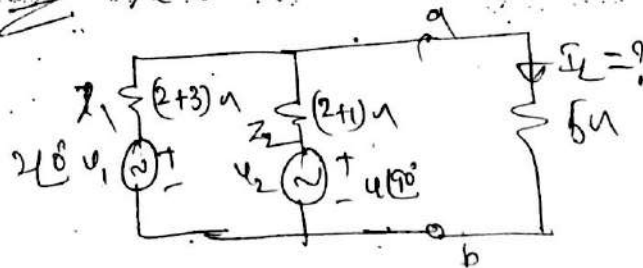

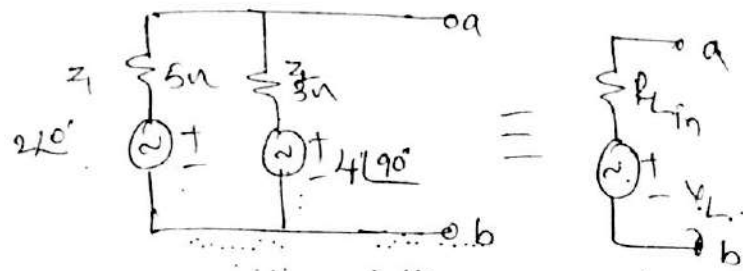


$$V_L = \frac{V_1 Y_1 + V_2 Y_2}{Y_1 + Y_2}$$

$$V_L = \frac{2\angle 0^\circ (5)^{-1} + 4\angle 90^\circ (3)^{-1}}{5^{-1} + 3^{-1}}$$

$$V_L = 1.3920 \angle 73.30^\circ \text{ Volts}$$

$$R_{L_{in}} = \frac{1}{Y_1 + Y_2} = \frac{1}{5^{-1} + 3^{-1}}$$

$$R_{L_{in}} = 1.875 \Omega$$

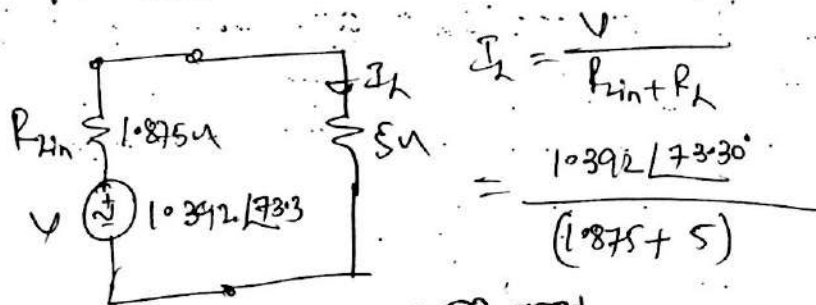


$$I_L = \frac{V}{R_{L_{in}} + R_L} = \frac{1.392 \angle 73.3^\circ}{(1.875 + 5)}$$

$$I_L = 0.202 \angle 73.3^\circ \text{ Amperes}$$

$$P_{L_{abn}} = |I_L|^2 \times R_L = [(0.202)^2 \times 5] = (0.202)^2 \times 5$$

$$P_{L(abn)} = 0.2049 \text{ Watts}$$

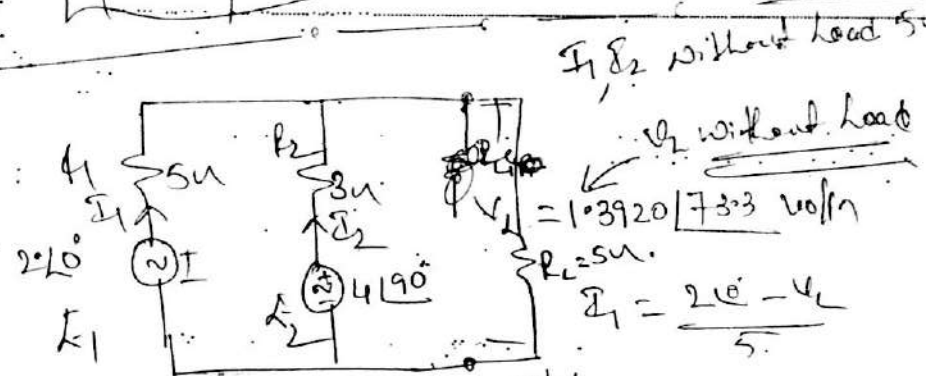

$$I_1 = \frac{2\angle 0^\circ - 1.392 \angle 73.3^\circ}{5} = 0.416 \angle -39.804^\circ \text{ A}$$

$$I_2 = \frac{4\angle 90^\circ - 1.392 \angle 73.3^\circ}{5} = 0.8988 \angle 98.53^\circ \text{ A}$$


$$V_L = \frac{V_1 Y_1 + V_2 Y_2}{Y_1 + Y_2 + Y_L} = \frac{2\angle 0^\circ (5)^{-1} + 4\angle 90^\circ (3)^{-1}}{5^{-1} + 3^{-1} + 5^{-1}} = 1.8982 \angle 73.30^\circ \text{ Volts}$$

$$I_1 = \frac{V_1 - V_L(\text{with load})}{R_1} = \frac{2\angle 0^\circ - 1.8982 \angle 73.30^\circ}{5} = 0.465 \angle -51.33^\circ \text{ Amperes}$$

$$I_2 = \frac{V_2 - V_L(\text{with load})}{R_2} = \frac{4\angle 90^\circ - 1.8982 \angle 73.3^\circ}{3} = 0.719 \text{ Amperes}$$

5) Using Millman's theorem find the current through  $10\Omega$


Question shown in fig. a

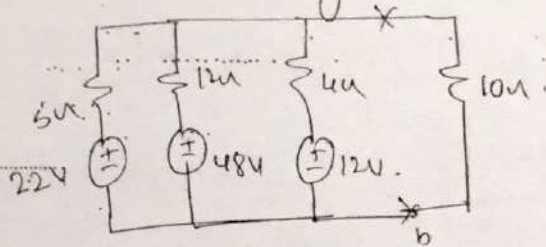

Jan 2014

(7m)

Soln:

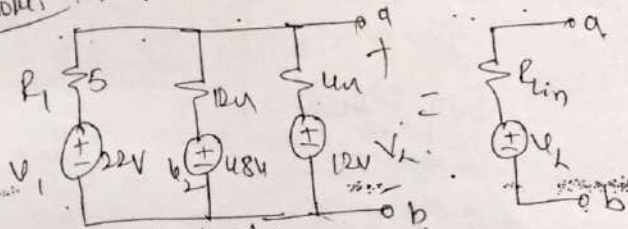


without load

$$V_L = \frac{V_1 Y_1 + V_2 Y_2 + V_3 Y_3}{Y_1 + Y_2 + Y_3}$$

$$V_L = \frac{22(5^{-1}) + (48)(12^{-1}) + 12(4^{-1})}{5^{-1} + 12^{-1} + 4^{-1}}$$


$$V_L = 21.375 \text{ volt}$$
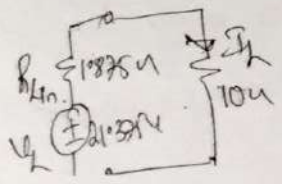
$$R_L = \frac{1}{5^{-1} + 12^{-1} + 4^{-1}} = \frac{1}{Y_1 + Y_2 + Y_3} = 1.875 \Omega$$



$$I_2 = \frac{V_L}{R_{L_{in}} + 10} = \frac{21.375}{1.875 + 10} = 1.8 \text{ A}$$

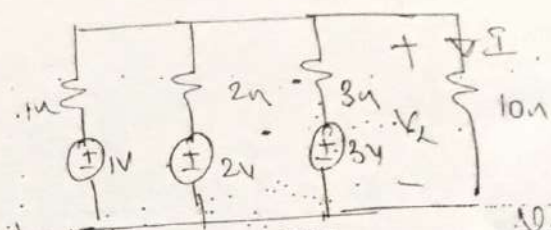6) Find the load current  $I$  in the ckt of fig by using Millman's theorem. (6m) J/S 2013. 13



2nd method


$$V_L = \frac{V_1 Y_1 + V_2 Y_2 + V_3 Y_3}{Y_1 + Y_2 + Y_3 + Y_L}$$

$$V_L = \frac{1(1^{-1}) + 2(2^{-1}) + 3(3^{-1})}{1^{-1} + 2^{-1} + 3^{-1} + 10^{-1}} = 1.5517 \text{ volt}$$

$$I = \frac{V_L}{10} = \frac{1.5517}{10} = 0.15517 \text{ Ampere}$$


6) State and explain millman's theorem. (04m) J/S 2013.

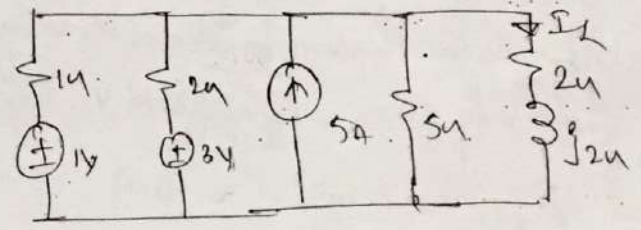7) Det. Load current  $I_2$  in the ckt shown in fig using millman's theorem. (6m) June 2012.





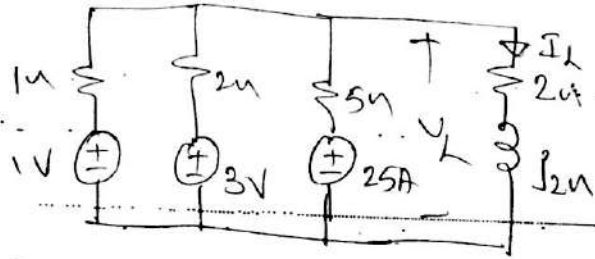Soln: <sup>Practical</sup> Convert Current source to practical voltage source.



$V_L$  with load is given by


$$V_L = \frac{V_1 Y_1 + V_2 Y_2 + V_3 Y_3}{Y_1 + Y_2 + Y_3 + Y_L}$$

$$= \frac{1(1)^{-1} + 3(2)^{-1} + 25(5)^{-1}}{1^{-1} + 2^{-1} + 5^{-1} + (2+j2)^{-1}}$$


$$= 3.8149 \angle 7.305^\circ \text{ Volt}$$

$$I_L = \frac{V_L}{(2+j2)} = \frac{3.8149 \angle 7.305^\circ}{(2+j2)} = 1.3487 \angle -37.69^\circ \text{ Ampere}$$

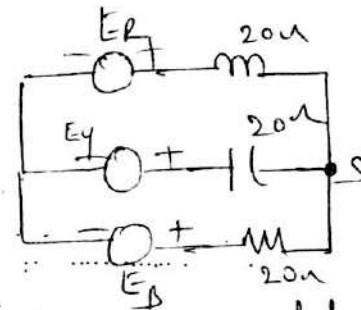⑧ Use millman's theorem to determine the voltage  $V_S$  of the a/c shown in fig. given  $E_R = 230 \angle 0^\circ \text{ V}$ ,  $E_Y = 230 \angle -120^\circ \text{ V}$   
 $E_B = 230 \angle 120^\circ \text{ V}$  (6m)



Soln: Rewrite the ckt

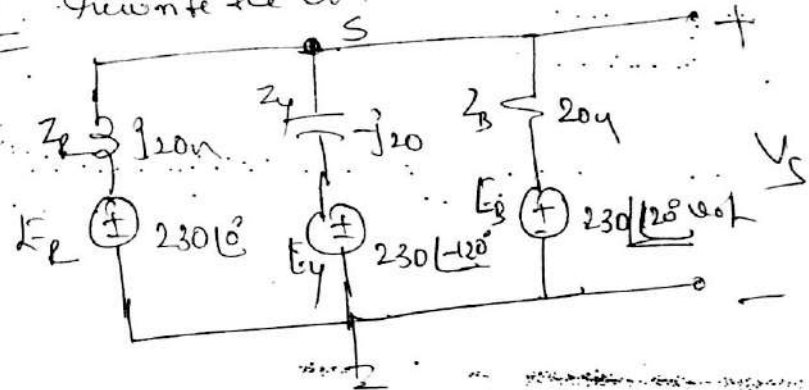


$$V_S = \frac{E_R Y_R + E_Y Y_Y + E_B Y_B}{Y_R + Y_Y + Y_B}$$

$$V_S = \frac{230 \angle 0^\circ (j20)^{-1} + 230 \angle -120^\circ (-j20)^{-1} + 230 \angle 120^\circ (20)^{-1}}{(j20)^{-1} + (-j20)^{-1} + (20)^{-1}}$$

$$V_S = 168.371 \angle -60^\circ \text{ Volt}$$

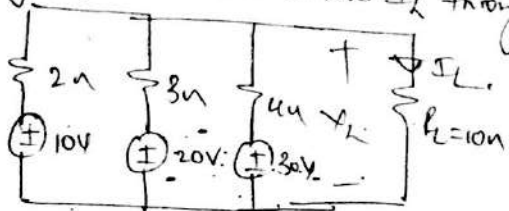9) Using millman's theorem find  $I_L$  through  $R_L$  for this circuit (6m) 5/5 2014



Soln:  $V_L$  with load

$$V_L = \frac{V_1 Y_1 + V_2 Y_2 + V_3 Y_3}{Y_1 + Y_2 + Y_3 + Y_L}$$


$$V_L = \frac{10 \times 2^{-1} + 20 \times 3^{-1} + 30 \times 4^{-1}}{2^{-1} + 3^{-1} + 4^{-1} + 10^{-1}}$$

$$V_L = 16.197 \text{ Volt}$$

$$I_L = \frac{V_L}{10} = 1.6197 \text{ Ampere}$$

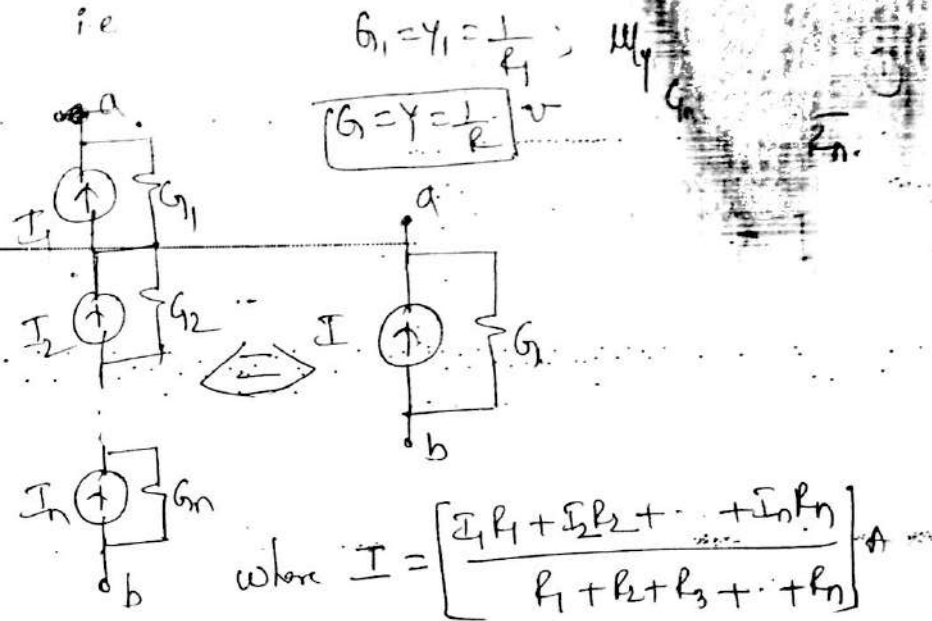10) State and prove millman's theorem for current sources in series. (6m) Jan 2013


Statement If 'n' practical current sources having internal conductance @ admittance which can be replaced by a single current source  $I$  in parallel with an equivalent conductance @ admittance.



$$\text{and } G = \frac{1}{R_1 + R_2 + R_3 + \dots + R_n}$$

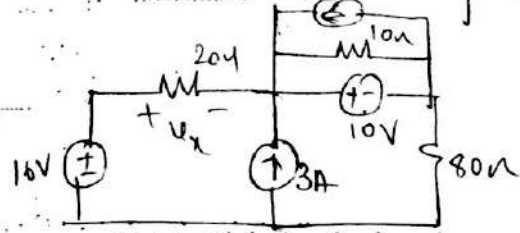
### 3 Superposition theorem:-

① Find  $V_x$  using Superposition theorem for the network shown  
 1.5A in fig. (8m)  $I_{80\Omega}$




Soln:- Step 1. 16V acting alone: make other source to zero  
 i.e. open circuit all current source & short circuit

the voltage sources.


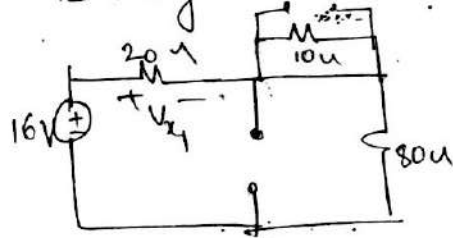


using V.D.R

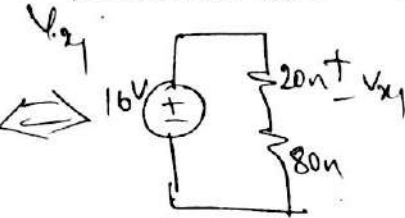


$$V_{x1} = \frac{16}{(20+80)} \times 20 = \underline{\underline{3.2 \text{ volt}}}$$

Step 2 10V acting alone

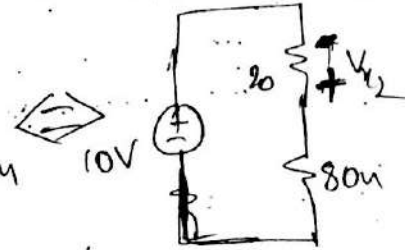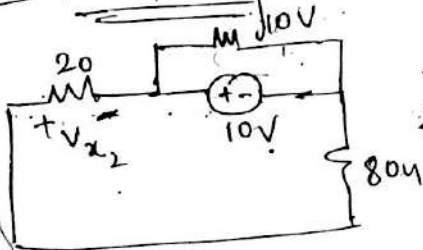

$$V_{x2} = -\frac{10}{(20+80)} \times 20 = \underline{\underline{-2 \text{ volt}}}$$


Step 3 :- 3A source alone

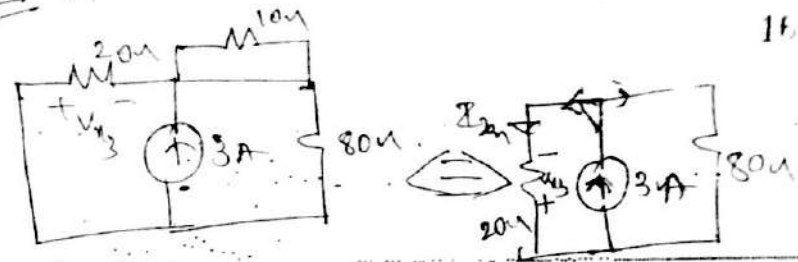

$$I_{80\Omega} = \frac{3 \times 80}{(20+80)} = \underline{\underline{2.4 \text{ Amp}}}$$

$$V_{x3} = -20 \times 2.4 = \underline{\underline{-48 \text{ Volt}}}$$


Step 4 - 1.5A source alone

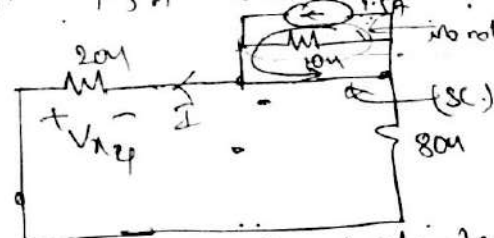

due to short circuit no current flows in 20Ω resistor  
 $V_{x4} = 0 \text{ volt}$  using SP

$$V_a = V_{x1} + V_{x2} + V_{x3} + V_{x4} \\ = 3.2 - 2 - 48 + 0 = \underline{\underline{-46.8 \text{ volt}}}$$

Verification using nodal method

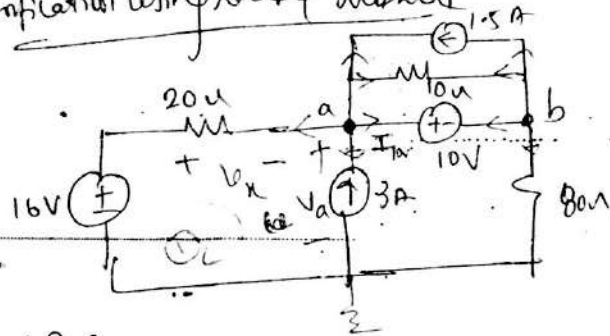

Let  $V_a$

$$\frac{V_a - 16}{20} + \frac{V_a - V_b}{10} - 1.5 - 3 + I_{10} = 0$$

$V_a = 10$  Volts ← (a)  
 $V_b - V_a = -10$

Let  $V_b$

$$\frac{V_b - 10}{10} + 1.5 + \frac{V_b}{80} - I_{10} = 0$$

$$20V_a - \left(\frac{16}{20}\right) + 1.5 = 4.5 + I_{10} = 0$$

$$20V_a + I_{10} = 4.3 \leftarrow (1)$$

$$-1 + 1.5 + \frac{V_b}{80} - I_{10} = 0$$

$$80V_b - I_{10} = -0.5 \leftarrow (2)$$

$$(1) + (2) \quad 20V_a + 80V_b = 3.8 \leftarrow (b)$$

Solve eq (a) and (b).

$$V_a - V_b = 10$$

$$20V_a + 80V_b = 3.8$$

$$V_a = 62.8 \text{ Volts}$$

$$V_b = 52.8 \text{ Volts}$$


Let loop

$$16 - V_x - V_a = 0$$


$$V_x = 16 - V_a = 16 - 62.8 = -46.8 \text{ Volts}$$

$V_x = -46.8$  Volts hence verified



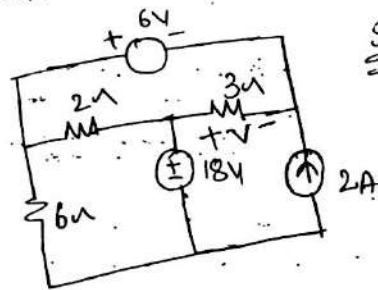
(2) Find the voltage 'V' across 3 ohm resistor using Superposition theorem for the circuit shown in the fig.




Soln:

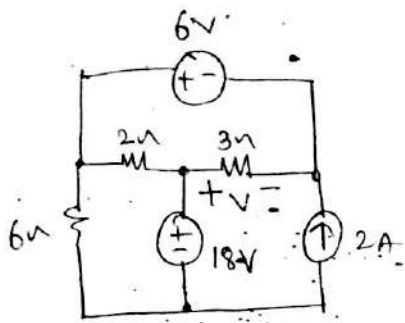

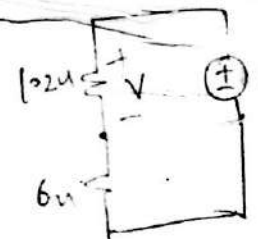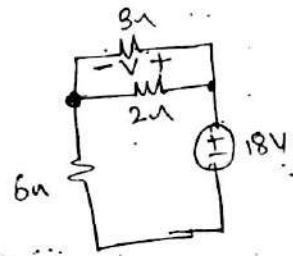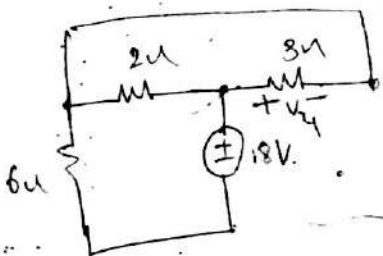Soln. Step 1. 18V source alone  $V \Rightarrow V_1$



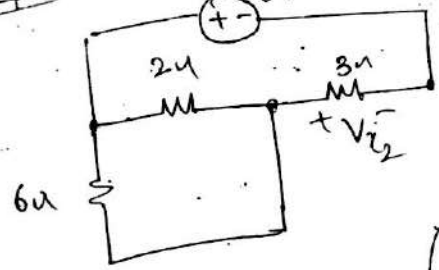
Step 2 6V source active alone  $V \Rightarrow V_2$



$$V_1 = \frac{18}{(1+2+6)} = 3 \text{ volts}$$

$$V_2 = \frac{6}{(1+2)} \times 3 = 4 \text{ volts}$$

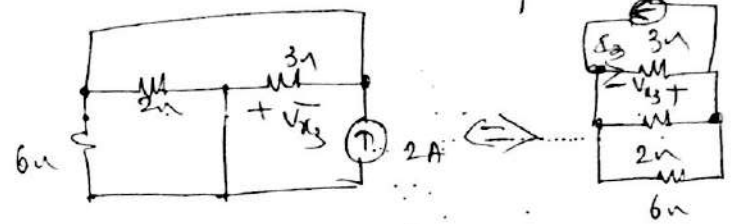Step 3. 2A current source active alone.  $V \Rightarrow V_3$




$$I_3 = \frac{2 \cdot (2 \parallel 6)}{3 + 2 \parallel 6} = \frac{2 \times 1.5}{3 + 1.5}$$

$$I_3 = 0.666 \text{ A} = \frac{2}{3} \text{ A}$$

$$V_3 = -I_3 \times 3 = -2 \text{ volts}$$

$$V = V_1 + V_2 + V_3 = 3 + 4 - 2 = 5 \text{ volts}$$

Verification by mesh analysis

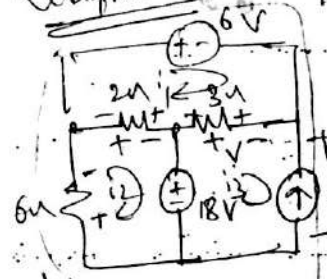

Identified loop  $V_1 = 5 \text{ volts}$

$$V = 3(i_3 + i_2) \text{ Volt?}$$

$$= 3[-2 + 2.5] = 1.5 \text{ Volt}$$

$$-6i_2 - 2(i_2 - i_1) - 18 = 0$$

$$-6i_2 - 2i_2 + 2i_1 = 18$$

$$2i_1 - 8i_2 = 18 \quad \text{--- (1)}$$

$$18 - 3(i_3 - i_1) - V_2 = 0 \quad \text{--- (2)}$$

$$18 - 3i_3 + 3i_1 - V_2 = 0$$

$$+3i_1 - 3i_3 = V_2 + 18 \quad \text{--- (2)}$$

$$6 + 2(i_1 - i_2) + 3(i_1 - i_3) = 0$$

$$2i_1 - 2i_2 + 3i_1 - 3i_3 = -6 \Rightarrow 5i_1 - 2i_2 - 3i_3 = -6 \quad \text{--- (3)}$$

$$5i_1 - 2i_2 = 0 \quad \text{--- (4)}$$

but to  
 answer  

$$V_2 + 6 + 6$$

$$V_2 = -6$$

$$3i_1 - 3i_3 + 6i_1$$


$$3i_1 + 6i_1 - 3i_3$$

$$9i_1 - 3i_3 = -21$$

$$3i_1 - i_3 = -7$$

$$i_1 = -1 \text{ A}$$

$$i_2 = -2.5 \text{ A}$$

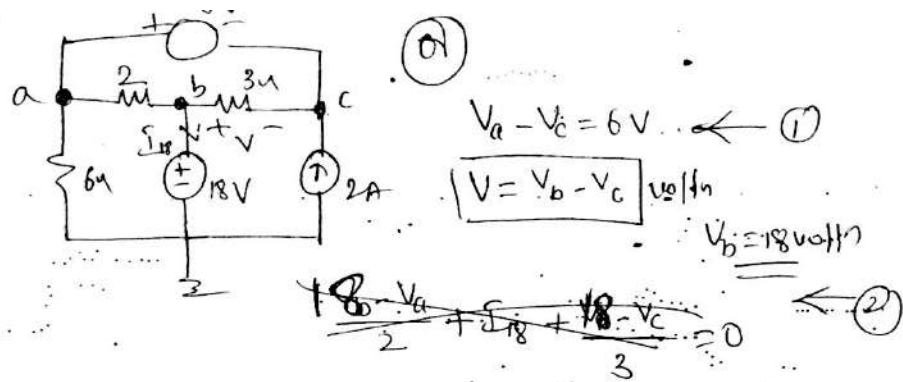


$$\frac{V_a}{6} + \frac{V_a - 18}{2} + \frac{V_c - 18}{3} - 2 = 0$$

$$[6^{-1} + 2^{-1}]V_a + 3^{-1}V_c = \left(\frac{18}{2} + \frac{18}{3} + 2\right)$$

$$V_a = 19 \text{ volt}, \quad V_c = 13 \text{ volt}$$


$$V = V_b - V_c = 18 - 13 = 5 \text{ volt} \quad \text{Verified}$$

Step 1. 5V source active alone.

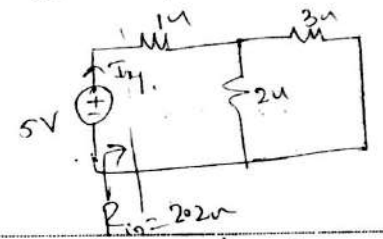

$$I_{x1} = \frac{5}{2.2} = 2.2727 \text{ Amps}$$

Step 2. 10V source active alone.

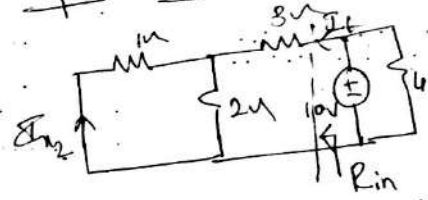


$$R_{in} = 3 + \parallel 2 = 3.666 \Omega$$

$$I_t = \frac{10}{R_{in}} = \frac{10}{3.666} = 2.7227 \text{ A}$$

$$I_{x2} = - \left[ \frac{2.7227 \times 2}{1 + 2} \right] = -1.01818 \text{ A}$$

Step 3. 1A source active alone.

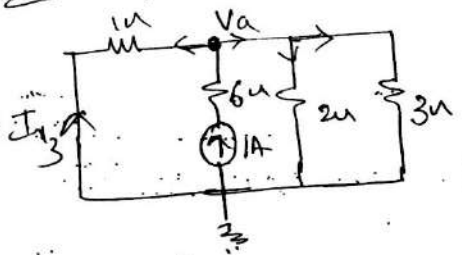

$$\frac{V_a}{1} + \frac{V_a}{2} + \frac{V_a}{3} - 1 = 0$$

$$V_a = 0.5454 \text{ volt}$$

$$I_{x3} = \frac{-V_a}{1} = -0.5454 \text{ Amps}$$


Using SPT

$$I_{x} = I_{x1} + I_{x2} + I_{x3}$$

$$= 2.2752 - 1.0188 - 0.5454$$

$$I_x = 0.5479 \text{ Amps}$$

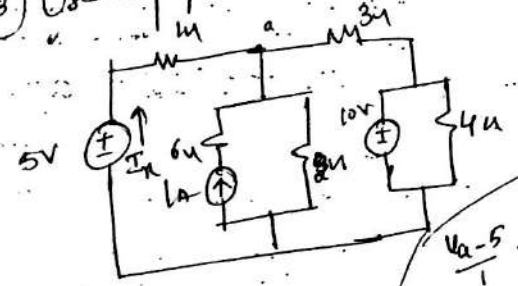(3) Use Superposition theorem to find  $I_x$  of the circuit shown in fig.




$$\frac{V_a - 5}{1} + \frac{V_a - 10}{3} + \frac{V_a}{2} - 1 = 0$$


$$V_a = 5.0901 \text{ A}$$

$$I_x = 5$$

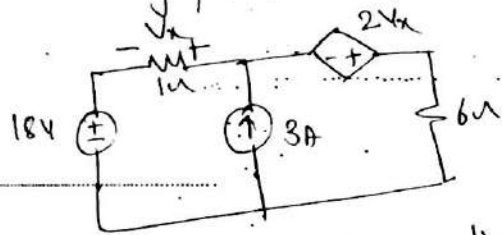④ Calculate the current in the  $6\Omega$  resistor of the circuit shown in fig using principle of superposition. (6m) J/J 2014



Soln: Step 1: 18V Source active alone

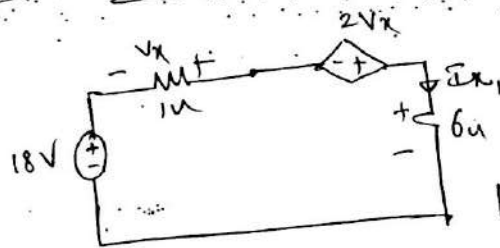

using KVL


$$18 + V_x + 2V_x - 6I_{x1} = 0$$

but  $V_x = -I_{x1}$   
 $V_x = -I_{x1}$

$$18 - I_{x1} - 2I_{x1} - 6I_{x1} = 0$$

$$18 = +9I_{x1} \Rightarrow \boxed{I_{x1} = 2} \text{ Ampere's}$$

Step 2: 3A Source active alone

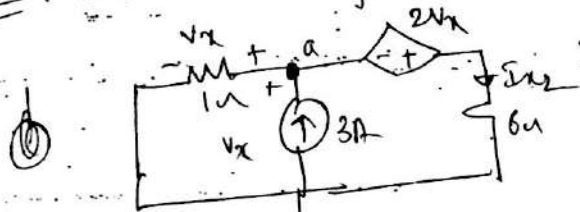

KVL @ a

$$\frac{V_x}{1} - 3 + \frac{V_x + 2V_x}{6} = 0$$


$$I_{x2} = \frac{V_x + 2V_x}{6} = \frac{2+4}{6} = 1A$$

$$\Rightarrow \boxed{V_x = 2} \text{ volts}$$

using SPT the current through  $6\Omega$  resistor is 2A

$$I_x = I_{x1} + I_{x2} = 2 + 1 = \underline{\underline{3A}}$$

Verification:

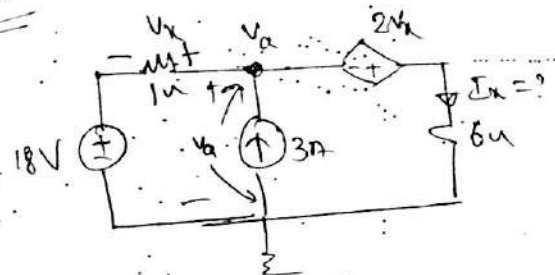

$$\frac{V_a - 18}{1} - 3 + \frac{V_a + 2V_x}{6} = 0$$

$$[1+6^{-1}]V_a + (\frac{1}{3})V_x = (3+18) \leftarrow (1)$$

$$18 + V_x - V_a = 0$$


$$\Rightarrow -V_a + V_x = -18 \leftarrow (2)$$

$$V_a = 18 \text{ volts} \quad V_x = 0 \text{ volts}$$



$$\Rightarrow I_x = \frac{V_a + 2V_x}{6} = \frac{18+0}{6} = \underline{\underline{3A}}$$

Verified

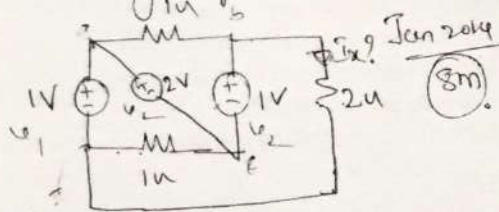
5) Find the Current through  $2\Omega$  resistor in the Nlw shown in fig. using Superposition theorem.




Step 1:  $V_1 = 1V$  Source alone

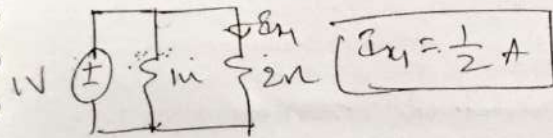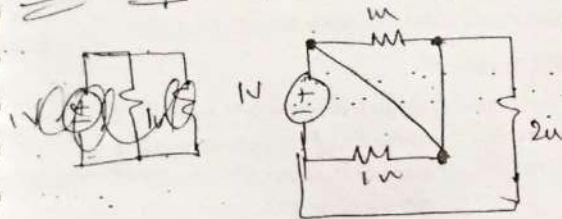

Step 2:  $V_2 = 2V$  Source alone

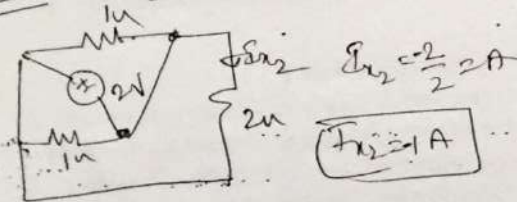

Step 3:  $V_3 = 1V$  source alone

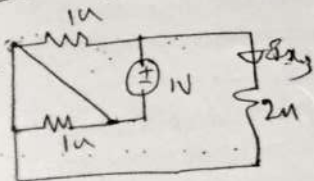

$I_{23} = \frac{1}{2} A$

Ans:  $I = I_1 + I_2 + I_3 = 0.5 + 1 + 0.5 = 2A$

$V_a = 1V \leftarrow (1)$   $V_b - V_c = 1V \leftarrow (2)$

$\frac{V_b - V_c}{1} + \frac{V_c}{2} + \frac{V_b}{1} = 0$

$2V_b + 0.5V_c = -1 \leftarrow (3)$

$V_a - V_c = 2V \leftarrow (4)$

$\therefore V_c = 2V \leftarrow V_a = 1V \text{ volt}$

$V_c = 1 - 2 = -1 \text{ Volt}$

$V_b = 1 + V_c = 1 - 1 = 0 \text{ volt}$

$I_2 = \frac{V_b - V_c}{2} = 0A$

Verified

### PROGRAMME EDUCATIONAL OBJECTIVES (PEOs)

- PEO1: To educate to be a Electronics and Communication Engineering graduate with an ability to pursue higher studies in global scenario.
- PEO2: To educate the learners to be highly competent Electronics and Communication Engineers with in-depth knowledge in the engineering fundamentals and chosen domain.
- PEO3: To impart the knowledge to the students to be able to function in a team with varied professional background or fields of Engineering and Technology to be able to meet the challenges of competitive field.
- PEO4: To enable the Electronics and communication engineering graduates in a truly professional way with ethical approach in solving and serving the needs of the society with humane approach.
- PEO5: To motivate the Electronic and communication engineering graduates to keep abreast with modern ever changing engineering and technologies and applications to evolve with innovative solutions and to build a carrier of their own with leadership qualities.

### PROGRAMME OUTCOMES

- a) An ability to apply knowledge of mathematics, science, and engineering,
- b) An ability to design and conduct experiments, as well as to analyze and interpret data,
- c) An ability to design a system, components, or process to meet desired needs within realistic constraints such as economic, environmental, social, political, ethical, health and safety, manufacturability, and sustainability,
- d) An ability to function on multidisciplinary teams,
- e) An ability to identify, formulate, and solve engineering problems,
- f) An understanding of professional and ethical responsibility,
- g) An ability to communicate effectively,
- h) The board education necessary to understand the impact of engineering solutions in a global, economic, environmental, and societal context,
- i) A recognition of the need for and an ability to engage in life-long learning,
- j) A knowledge of contemporary issues, and
- k) An ability to use the techniques, skills, and modern engineering tools necessary for engineering practice.
- l) Knowledge of advanced mathematics, including differential equations, linear algebra, complex variables, an probability and statistics, including applications to electronics and communication engineering.




## Theorem 1: Norton's Theorem

### Statement :

Norton's Theorem states that a linear two terminal network can be replaced by an equivalent circuit consisting of a current  $I_N$  in parallel with a resistor  $R_N$ , where

- $R_N$  is the equivalent resistance at the terminals when the independent sources are turned off
- $I_N$  is short circuit current through the terminals.

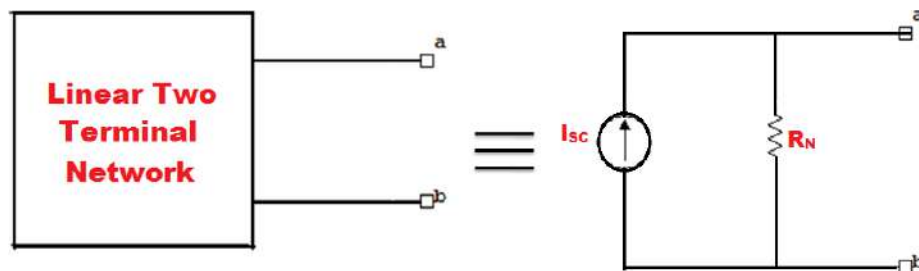If the circuit consists of the dependent sources the Norton's resistance has to be found out as  $R_N = V_{oc} / I_{sc}$




There can be two types of problems,

1. To find the Norton's equivalent circuit across the open circuit terminals
2. To find a voltage or a current in the circuit by Norton's Theorem.
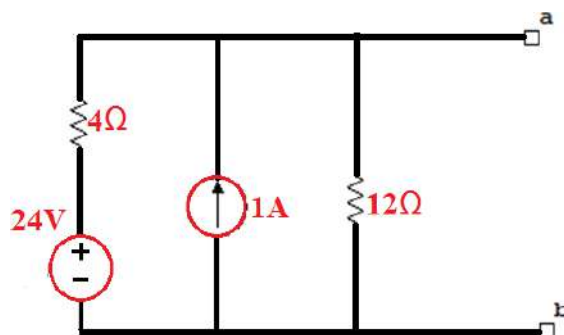
### Problems:

P1. Find the Norton's equivalent circuit across the terminals a-b




Solution:

Steps to find out the Norton's Resistance  $R_N$  :

Step 1: Turn off the independent sources

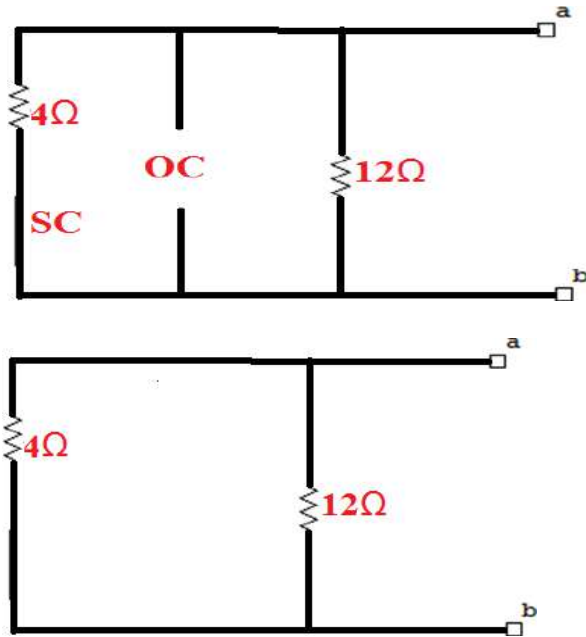(open-circuit the current source and short-circuit the voltage source)



Step 2: Find the equivalent resistance looking into the open circuit terminals


$$R_N = 12 \times 4 / 12 + 4$$

$$R_N = 3 \Omega$$


Steps to find out the Norton's Current  $I_N$  (Short circuit current):

Step 1: Short circuit the open circuit terminals and mark the  $I_{SC}$  as shown.

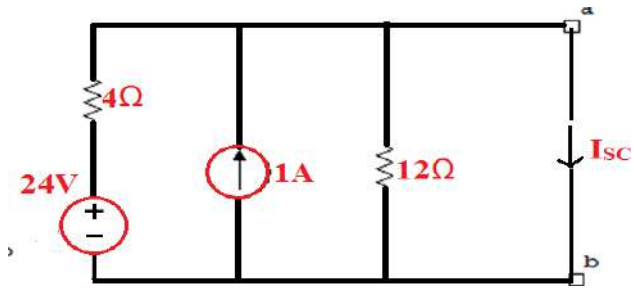Step 2: Find the short circuit current by a suitable technique



By Node Analysis:

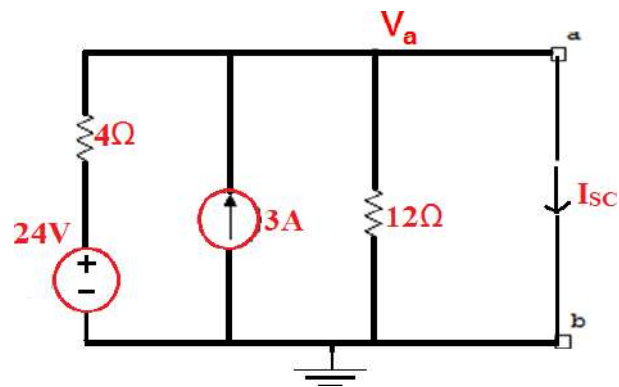


Applying KCL at node a :

$$\frac{V_a - 24}{4} + \frac{V_a}{12} + I_{sc} = 3$$


Substituting  $V_a = 0$  V in the above equation implies

$$I_{sc} = 9 \text{ A}$$

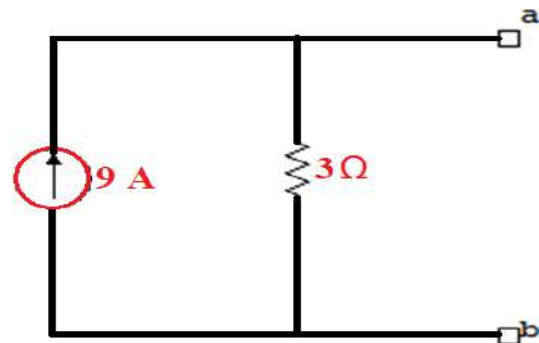Therefore the Norton's equivalent circuit across terminals a-b is



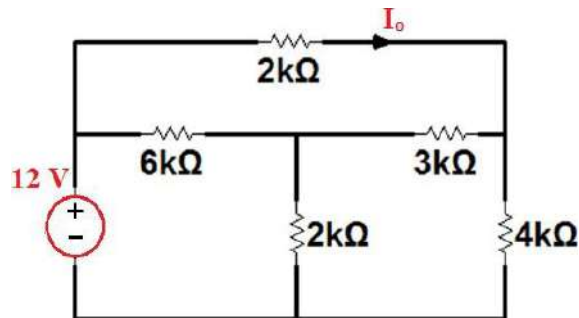P2. Find  $I_0$  in the network shown, using Norton's Theorem




Solution:

Step 1: Separate the branch through which  $I_0$  is flowing


Step 2: Find the Norton's equivalent network across the open circuit terminals

Step 3: Connect the branch separated, back to the Norton's equivalent circuit to find  $I_0$

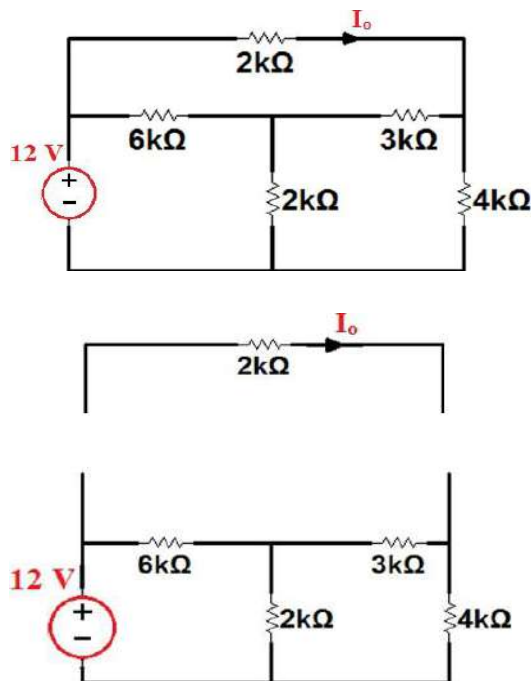
Step 1: Separate the branch through which  $I_0$  is flowing



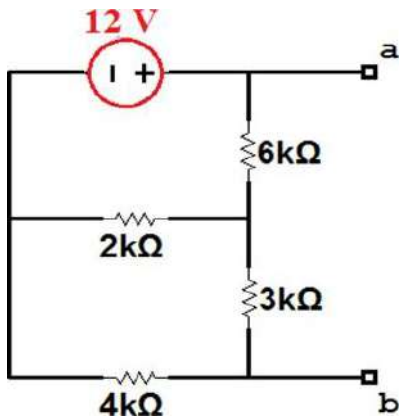Step 2: Find the Norton's equivalent network across the open circuit terminals a-b



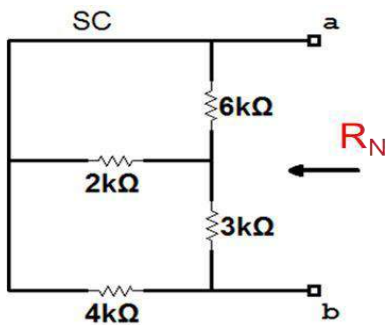
Find the  $R_N$  across the open circuit terminals a-b by short-circuiting 12 V source



$$R_N = [ (6\text{ K} \parallel 2\text{ K}) + 3\text{ K} ] \parallel 4\text{ K}$$

$$\underline{R_N = 2.12\text{ K}\Omega}$$

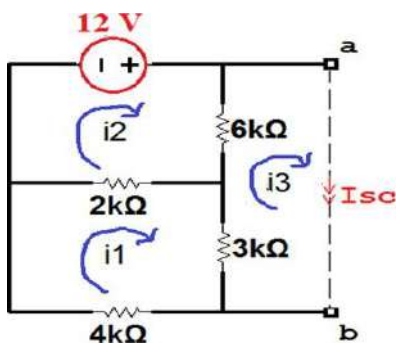Find the  $I_{SC}$  or  $I_N$  through terminals a-b by short-circuiting a-b as shown



By Mesh Analysis:

Mark  $i_1, i_2, i_3$  as shown

KVL to Mesh 1:

$$4K i_1 + 2K(i_1 - i_2) + 3K(i_1 - i_3) = 0$$

$$9K i_1 - 2K i_2 - 3K i_3 = 0 \dots\dots\dots \text{Eq1}$$

KVL to mesh 2:

$$-12 + 6K(i_2 - i_3) + 2K(i_2 - i_1) = 0$$

$$-2K i_1 + 8K i_2 - 6K i_3 = 12 \dots\dots\dots \text{Eq2}$$

KVL to mesh 3:

$$3K(i_3 - i_1) + 6K(i_3 - i_2) = 0$$


$$-3K i_1 - 6K i_2 + 9K i_3 = 0 \dots\dots\dots \text{Eq3}$$

Solving Eq1, Eq2 and Eq3 we have,



$$i_1 = 3\text{mA}, i_2 = 6\text{mA}, i_3 = 5\text{mA}$$

$$\underline{I_{sc} = i_3 = 5\text{mA}}$$

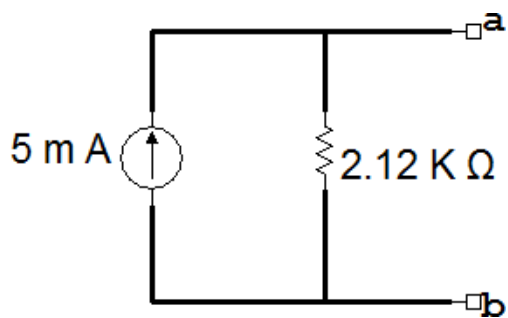Therefore the Norton's equivalent circuit across terminals a-b is



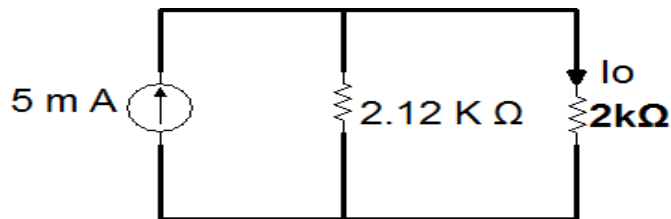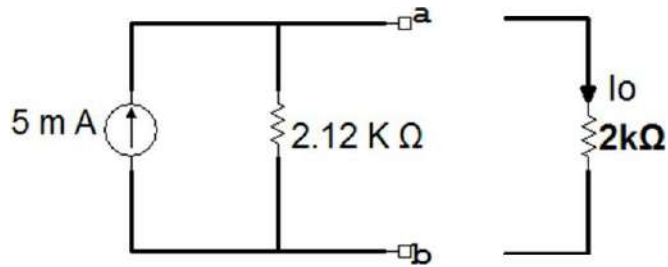
Step 3: Connect the branch separated, back to the Norton's equivalent circuit to find  $I_0$



By Current Division Method

$$I_o = \frac{5\text{ m} \times 2.12\text{ K}}{2\text{ K} + 2.12\text{ K}} = 2.57\text{ mA}$$

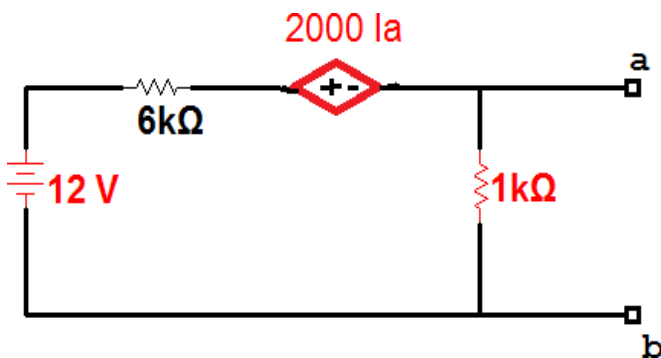P3. Find the Norton's Equivalent network across the terminals a-b




Solution:

Since the network consists of the dependent source (Dependant sources cannot be turned off) the Norton's resistance has to be found out as


$$R_N = V_{oc} / I_{sc}$$

Step 1: To find out  $I_{sc}$  ( $I_N$ )

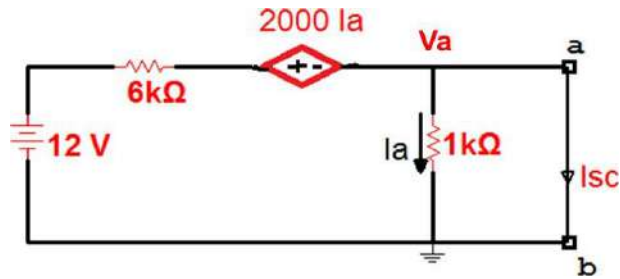Short Circuit the terminals a-b and mark  $I_{sc}$  as shown




$V_a = I_a = 0$

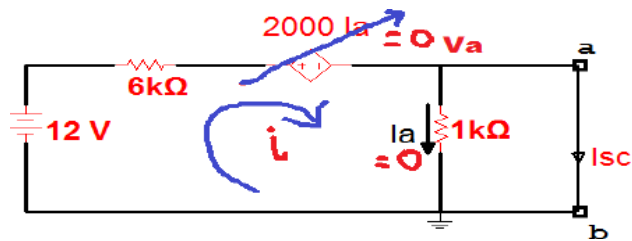

Since  $V_a$  is connected to ground through short circuit terminals a-b  $V_a=0$ .

Hence the circuit gets reduced to...

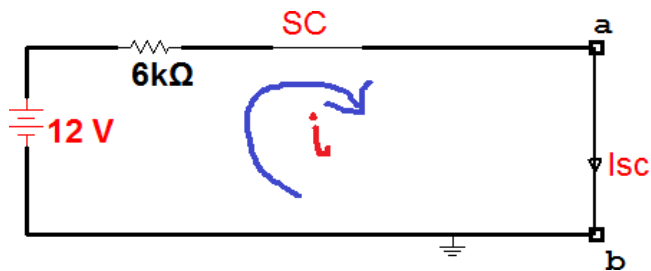


KVL:  $-12 + 6K i = 0$

$i = 12/6K = 2 \text{ m A}$

$I_{SC} = i = 2 \text{ m A}$

Step 2: To find out  $V_{OC}$

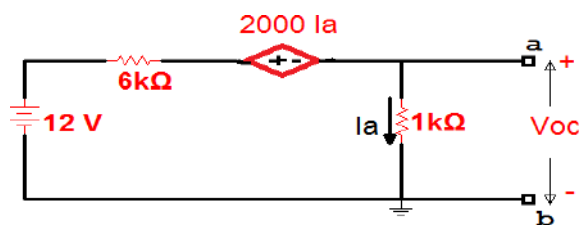



KCL at node a:

$$\frac{V_{oc} + 2000I_a - 12}{6K} + \frac{V_{oc}}{1K} = 0$$


$$2000 I_a + 7 V_a = 12$$

Substituting  $I_a = \frac{V_{oc}}{1K}$

$$\underline{V_{oc} = 4/3 \text{ V}}$$

$$\text{Therefore } R_N = V_{oc} / I_{sc} = 667 \Omega$$

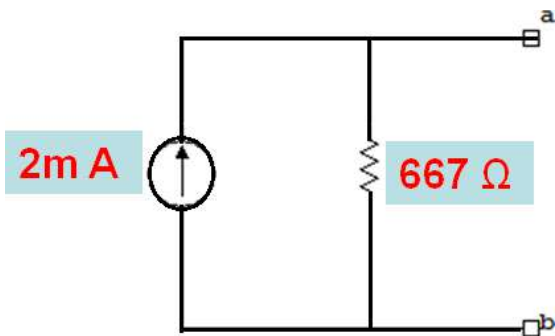Therefore Norton's equivalent circuit across the terminals a-b is given by



## Theorem 2: Thevenin's Theorem


Definition :

Thevenin's Theorem states that a linear two terminal network can be replaced by an equivalent network consisting of an Voltage  $V_T$  in series with a resistor  $R_T$  , where

- $R_T$  is the equivalent resistance at the terminals when the independent sources are turned off
- $V_T$  is open circuit voltage across the terminals.

If the circuit consists of the dependent sources the Norton's resistance has to be found out as  $R_T = V_{oc} / I_{sc}$

P1. Find  $V_O$  by Thevenin's Theorem

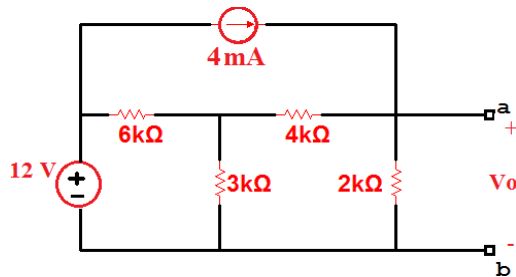


Solution:

Step 1: Remove resistor  $2K \Omega$  from the circuit across which  $V_O$  is dropping


Step 2: Find the Thevenin's network across the open circuit terminals a-b

Step 3: Connect  $2K \Omega$  (Disconnected in Step 1) across the open circuit terminals a-b and find  $V_O$ .


Circuit can be visualized as,

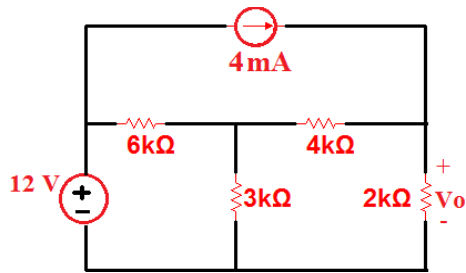

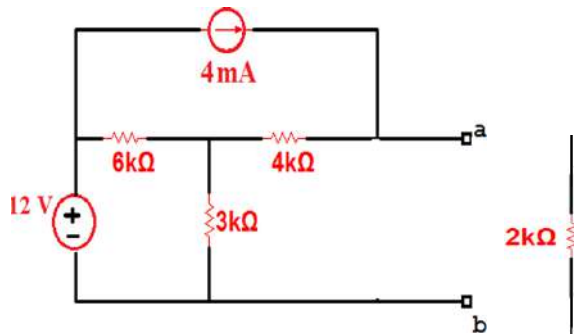Step 1: Remove resistor  $2\text{k}\Omega$  from the circuit across which  $V_O$  is dropping and mark terminals a-b




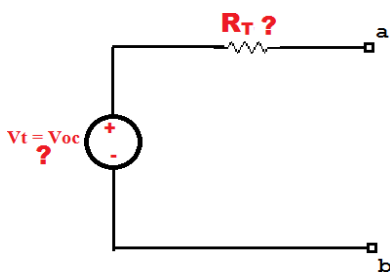Step 2: Find the Thevenin's network across the open circuit terminals a-b



To find  $V_{OC}$ :

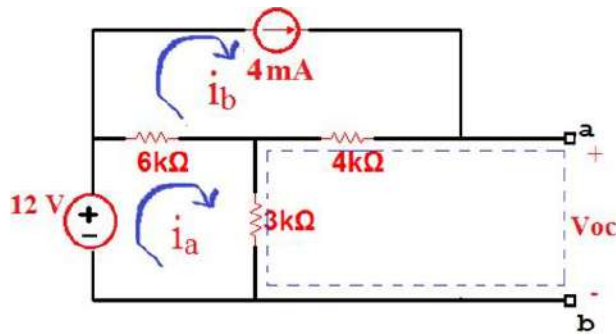Mark  $V_{OC}$  across the open circuit terminals as shown:



Mark Mesh currents  $i_a$  and  $i_b$ :

By Observation:

$$I_a = 4 \text{ mA}$$

Applying KVL to Mesh 1:

$$-12 + 6K(i_a - i_b) + 3K i_a = 0$$

$$9K i_a - 6K i_b = 12$$

$$\text{Sub. } I_a = 4 \text{ mA,}$$

$$I_b = 4 \text{ mA}$$

To find  $V_{oc}$  apply KVL along the dotted path:


$$-3K I_a - 4K I_b + V_{oc} = 0$$

Sub.  $I_a$  and  $I_b$ ,

$$V_{oc} = 28 \text{ V}$$

To find  $R_T$  :


Deactivate the independent sources

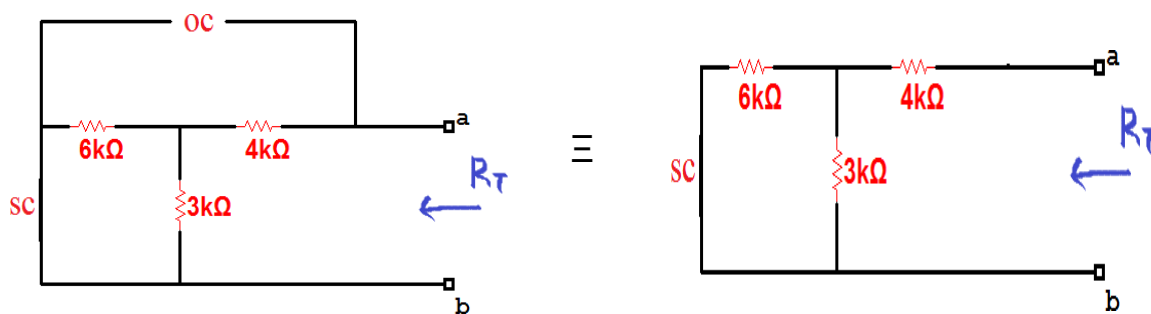

$$R_T = (6K \parallel 3K) + 4K$$


$$R_T = 6K$$

Therefore the Thevenini's network is

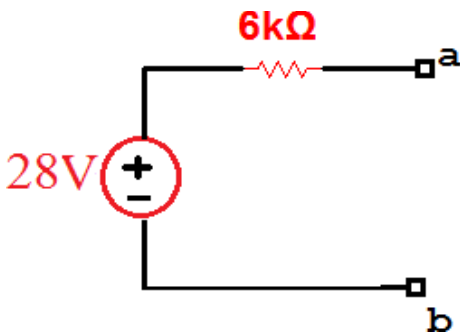

Step 3: To find  $V_O$

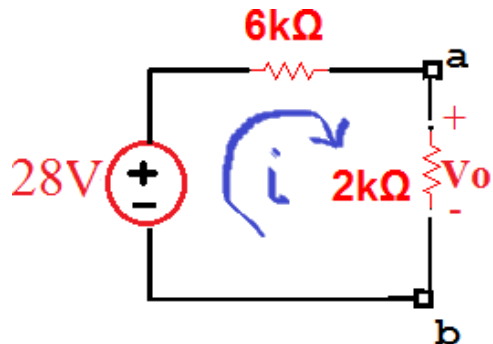Now connect 2 K  $\Omega$  across a-b to find  $V_O$




KVL gives,

$$-28 + 6K i + 2K i = 0$$

$$i = 28/8K = 3.5 \text{ mA}$$

$$V_O = 2K i = 7 \text{ V}$$

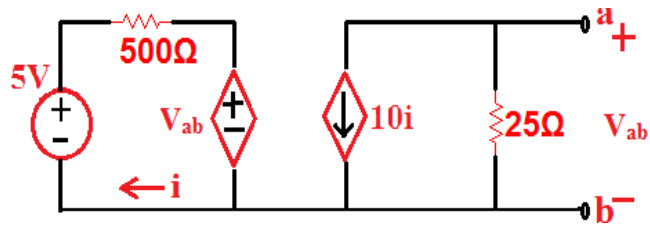P2. Find the Thevenin's Equivalent circuit across terminals a-b




Solution:

Since the dependant sources are involved  $R_T$  is given by

$$R_T = V_{oc} / I_{SC}$$

Step 1: To find  $V_{OC}$

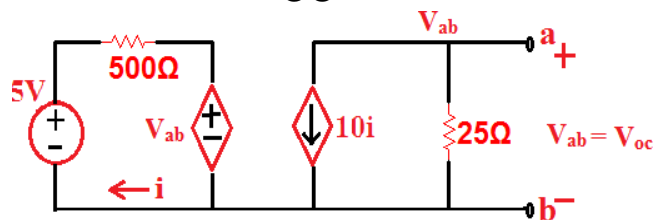

Applying KVL to LHS part:

$$-5 + 500 i + V_{ab} = 0$$

$$500 i + V_{ab} = 5$$

Applying KCL to RHS part:

$$10 i + V_{ab} / 25 = 0$$


$$250 i + V_{ab} = 0$$

Solving equations we have

$i = 0.02 \text{ A}$	$V_{ab} = -5 \text{ V}$
----------------------	-------------------------

$V_{oc} = V_{ab} = -5 \text{ V}$
----------------------------------

Step 2: To find  $I_{SC}$

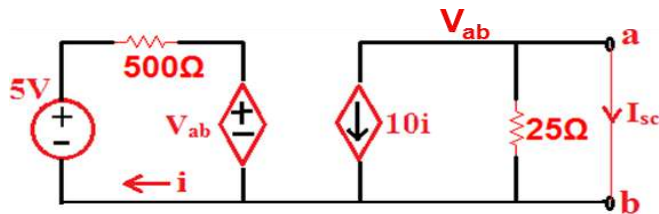


Short circuit terminals a-b and mark  $I_{SC}$  as shown

Mark  $V_{ab}$

Since  $V_{ab}$  is connected to ground through a-b,  $V_{ab} = 0$

Since  $25\ \Omega$  is in parallel with a short,  $25\ \Omega$  is redundant

Therefore the circuit reduces to,

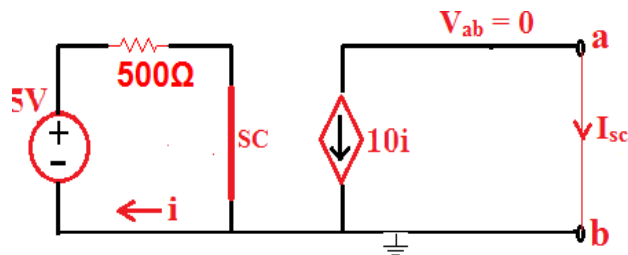

From LHS part, KVL gives

$$-5 + 500 i = 0$$

From RHS part,

$$I_{SC} = -10i$$


and sub.  $i = 0.01\text{ A}$

$$I_{SC} = -0.1\text{ A}$$


Therefore  $R_T = V_{OC} / I_{SC} = -5 / -0.1$

$$R_T = 50 \Omega$$

Therefore the Thevenin's network is,

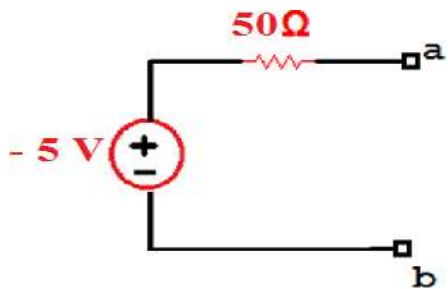

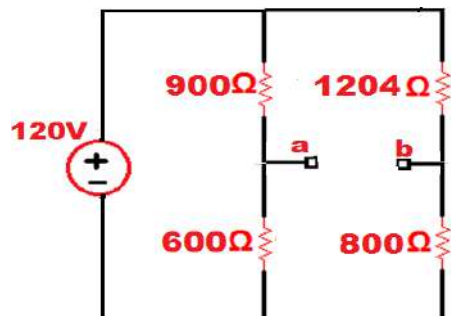
P3. Find the Thevenin's Equivalent network across terminals a-b



Solution:

Step1: To find Mark  $V_{OC}$  ( $V_T$ ) across terminals a-b

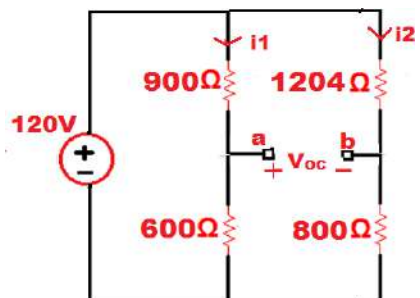Mark the branch currents  $i_1$  and  $i_2$  as shown





Applying KVL to mesh 1

$$-120 + 900 i_1 + 600 i_1 = 0$$


$$i_1 = 0.08 \text{ A}$$

Applying KVL to mesh 2

$$-120 + 1204 i_2 + 800 i_2 = 0$$

$$i_2 = 0.05988 \text{ A}$$

To find  $V_{OC}$ :

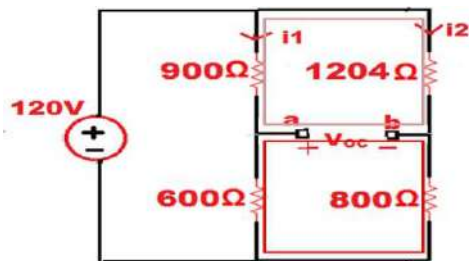


Applying KVL along the pink path

$$- 900 i_1 + 1204 i_2 - V_{OC} = 0$$


$$V_{OC} = 0.095 \text{ V}$$

Step 2: To find  $R_T$

Turning off 120 V source

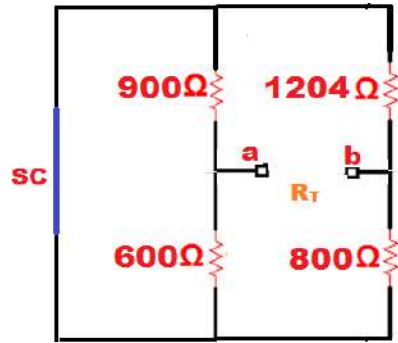


which can be visualized as

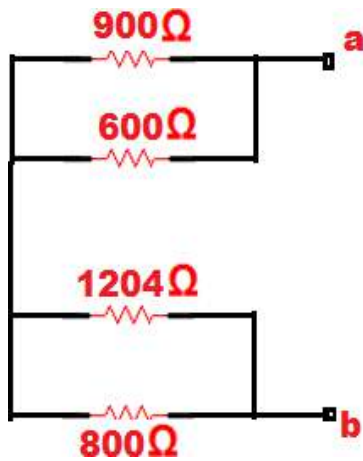

$$R_T = (900 \parallel 600) + (1204 \parallel 800)$$

$$R_T = 840.638 \Omega$$

Therefore Thevenin's network is

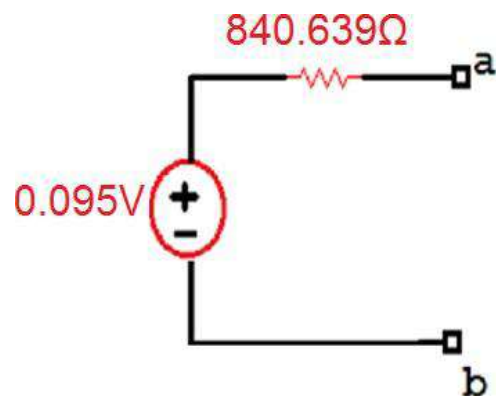

Summary:


1. Thevenin's network is a Voltage in series with a resistor
2. Thevenin's voltage is  $V_{OC}$  across the terminals
3. Thevenin's resistance and Norton's resistance are the same.
4. Thevenin's and Norton's equivalent networks can be obtained by source transformation.

### Theorem 3: Maximum Power Transfer Theorem

There are three cases to be considered in this

1. AC circuits with Impedance ( $Z_L$ ) as load
2. AC circuits with purely resistive load ( $R_L$ )
3. DC circuits with resistive load ( $R_L$ )


Conditions for Maximum Power Transfer :

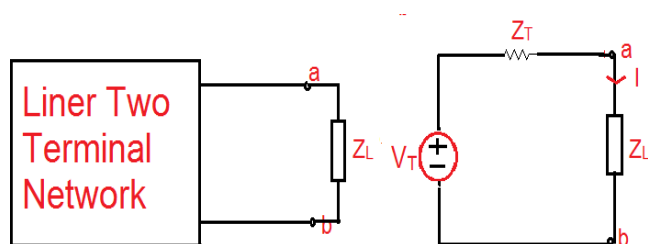

where,

$$Z_T = R_T + j X_T$$

$$Z_L = R_L + j X_L$$

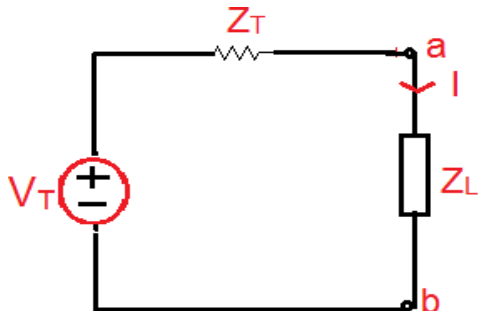

KVL to closed path:

$$-V_T + Z_T I + Z_L I = 0$$

$$I = \frac{V_T}{Z_T + Z_L} = \frac{V_T}{(R_T + jX_T) + (R_L + jX_L)}$$

The average power delivered to the load is

$$P = \frac{1}{2} |I|^2 R \quad \dots\dots\dots \textcircled{1}$$

$$I^2 = \frac{V_T^2}{[(R_T + jX_T) + (R_L + jX_L)]^2}$$

$$I^2 = \frac{V_T^2}{[(R_T + R_L) + j(X_T + X_L)]^2}$$

$$|I|^2 = \frac{|V_T|^2}{[\sqrt{(R_T + R_L)^2 + (X_T + X_L)^2}]^2}$$

Substituting in equation in 1

$$P = \frac{R_L}{2} \frac{|V_T|^2}{(R_T + R_L)^2 + (X_T + X_L)^2}$$

For this P to be  $P_{Max}$  we can vary two parameters

–  $R_L$  and  $X_L$  in the load impedance.

Mathematically it can be done by differentiating  $P$  with respect to  $R_L$  and  $X_L$  partially and equating it to zero respectively.

i.e,

$$\frac{\partial P}{\partial R_L} = 0 \quad \text{and} \quad \frac{\partial P}{\partial X_L} = 0$$

Performing  $\frac{\partial P}{\partial R_L} = 0$  results in

$$(R_T + R_L)^2 + (X_T + X_L)^2 - 2R_L(R_T + R_L) = 0$$

This implies

$$R_L = \sqrt{R_T^2 + (X_T + X_L)^2} \quad \dots\dots\dots \textcircled{2}$$

Performing  $\frac{\partial P}{\partial X_L} = 0$  results in

$$X_L = -X_T \quad \dots\dots\dots \textcircled{3}$$

Substituting  $\textcircled{3}$  in  $\textcircled{2}$

$$R_L = R_T \quad \dots\dots\dots \textcircled{4}$$

From equations 3 and 4

$$Z_L = R_L + j X_L = R_T - j X_T$$

$$Z_L = Z_T^*$$

If the Load  $Z_L$  is purely resistive then

$$X_L = 0 \text{ and } Z_L = R_L$$

Substituting  $X_L = 0$  in 2


$$R_L = \sqrt{R_T^2 + X_T^2} \dots\dots\dots 5$$

$$R_L = |Z_T| \dots\dots\dots 6$$

Equations 4 , 5 and 6 are the conditions for which the maximum power would be transferred to the load.


Highlights:

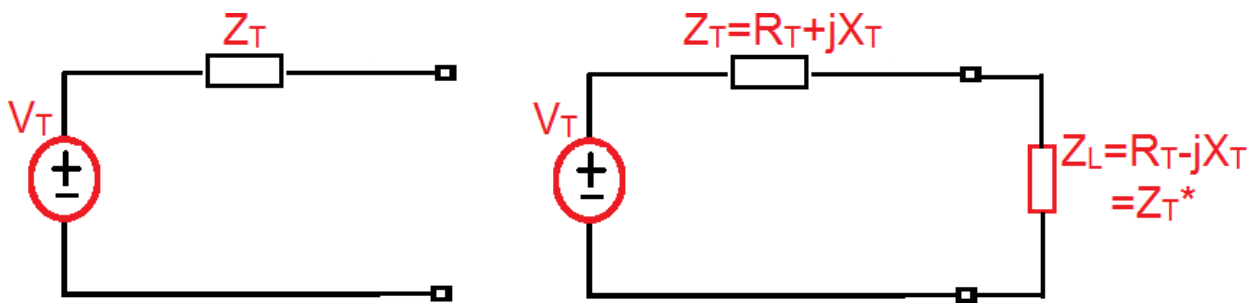1. AC circuits with Impedance ( $Z_L$ ) as load




$$P_{\max} = |i|^2 R_L$$

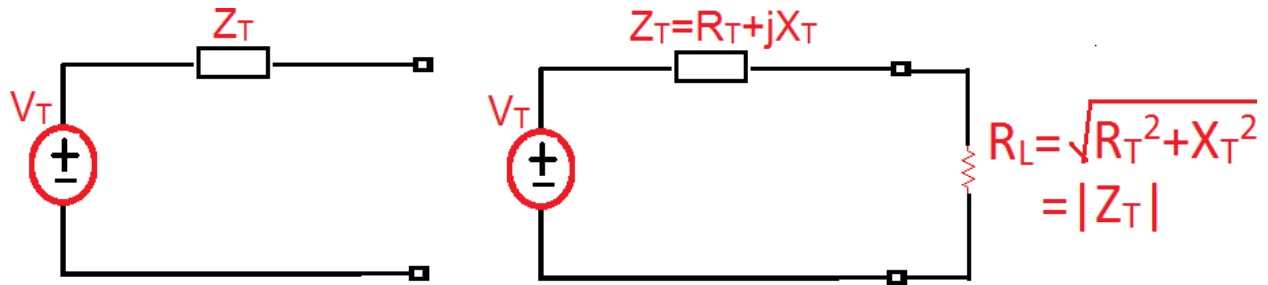2. AC circuits with Pure Resistive ( $R_L$ ) load




$$P_{\max} = |i|^2 R_L$$

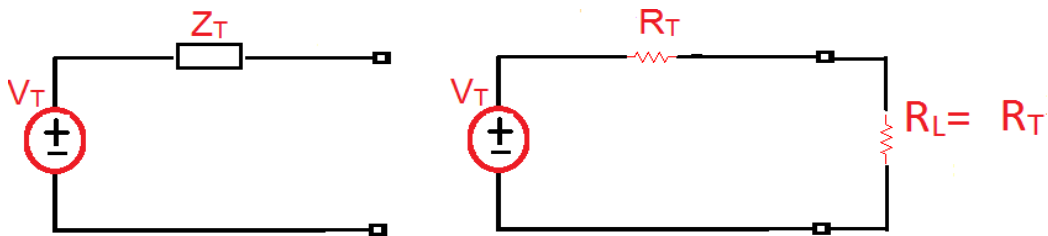3. DC circuits with Resistor ( $R_L$ ) as the load



$$P_{\max} = i^2 R_L$$

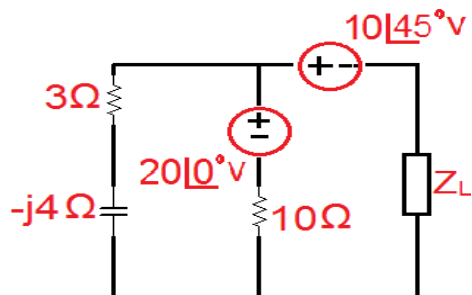P1. Calculate the value of  $Z_L$  for maximum power transfer and also calculate the maximum power.



Solution:


Step1. Remove the Impedance  $Z_L$

Step2. Find the Thevenin's equivalent network across the terminals a-b

Step3. Connect  $Z_L = Z_T^*$  across the terminals a-b for the maximum power transfer.

Step4. Find  $P_{\max} = |I|^2 R_L$

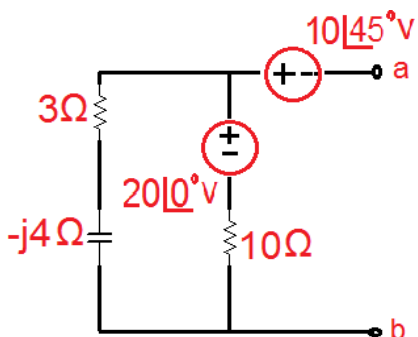
Step1. Remove the Impedance  $Z_L$  and mark terminals a-b



Step2. Find the Thevenin's equivalent network across the terminals a-b.

To find Thevenin's Impedance  $Z_T$ :

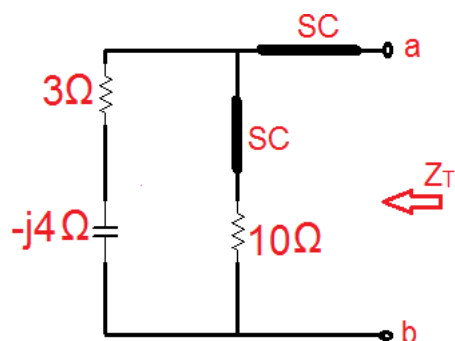Deactivating the independent sources we have,





$$Z_T = 10 \parallel (3 - j4)$$

$$Z_T = 2.97 - j 2.16 \Omega$$

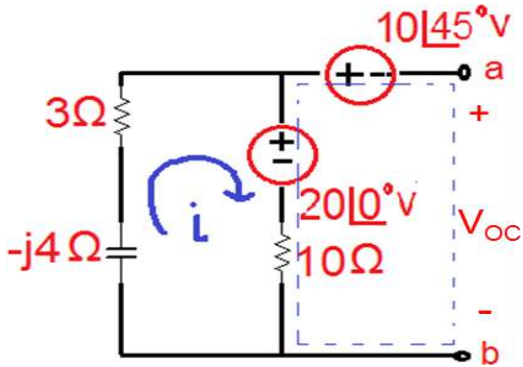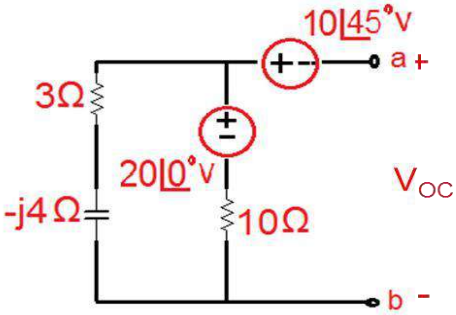To find Thevenin's Voltage  $V_T$  or  $V_{OC}$ :





KVL implies:

$$(3-j4) i + 20 + 10 i = 0$$

$$i = -1.405 - j 0.432$$

KVL along the dotted path to find  $V_{OC}$ :


$$- 10 i - 20 + 10 \angle 45 + V_{OC} = 0$$

Substituting  $i$


$$V_T = -1.121 - j 1.391$$

$$= 11.44 \angle -95.62 \text{ V}$$

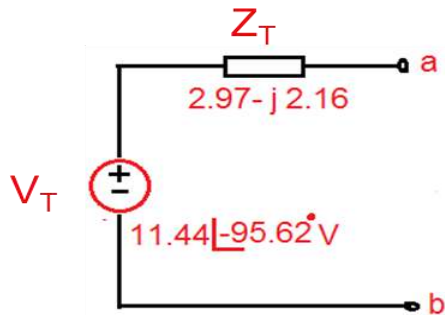Therefore Thevenin's equivalent network is



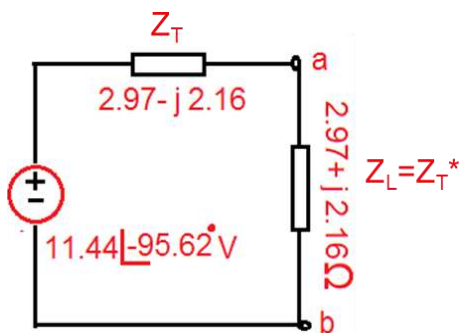Step 3. Connect  $Z_L = Z_T^*$  across the terminals a-b to find the maximum power transfer.



KVL implies:

$$-11.44 \angle -95.62^\circ + (2.9729)i + (2.9729)i = 0$$

$$i = -0.185 - j 1.916 \text{ A}$$

$$i = 1.925 \angle -95.62^\circ \text{ A}$$


Step 4. To find  $P_{\max}$

$$P_{\max} = |i|^2 R_L$$

$$= (1.925)^2 \times 2.9729$$

$$P_{\max} = 11 \text{ Watts}$$

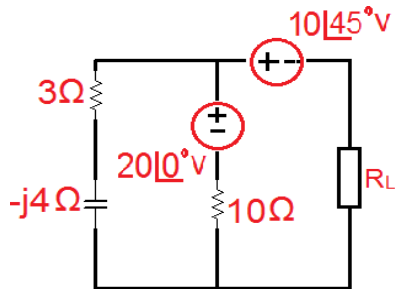P2. Calculate the value of  $R_L$  for maximum power transfer and also calculate the maximum power.



Solution:


Step1. Remove the Impedance  $Z_L$

Step2. Find the Thevenin's equivalent network across the terminals a-b

Step3. Connect  $Z_L = |Z|$  across the terminals a-b for the maximum power transfer.

Step4. Find  $P_{\max} = |I|^2 R_L$

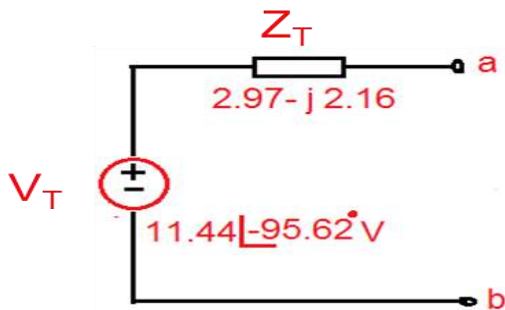
From Step1 and Step2 (Refer P1), the Thevenin's equivalent is



Step3. Connect  $R_L = |Z|$  across the terminals a-b to find the maximum power transfer.

$$R_L = |Z_T| = \sqrt{(2.97)^2 + (2.16)^2}$$

$$R_L = 3.675 \Omega$$

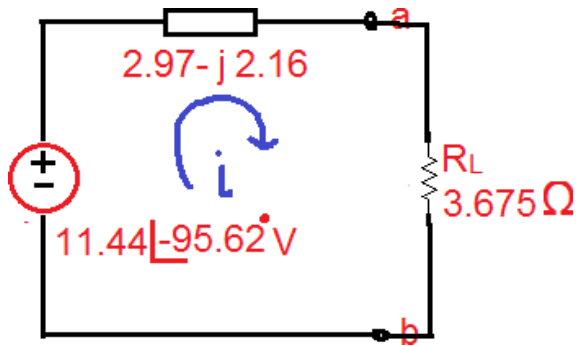

KVL implies

$$-11.44 \angle -95.62 + (2.97 - j 2.16) i + 3.675 i = 0$$

$$i = 1.6377 \angle -77.62 \text{ A}$$


Step 4. To find  $P_{\max}$

$$P_{\max} = |i|^2 R_L$$

$$= (1.6377)^2 \times 3.675$$


$$P_{\max} = 9.85 \text{ W}$$

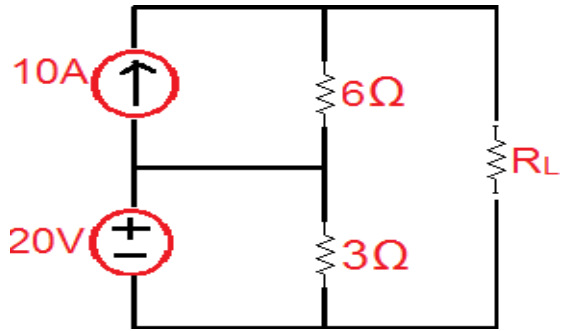P3. Find the  $R_L$  across the load for which maximum power will be transferred to the load and hence find the maximum power




Solution:

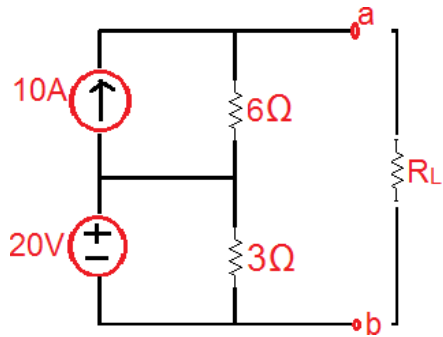Step 1: Remove the resistor  $R_L$  and mark terminals a-b as shown



Step 2: Find the Thevenin's network across the terminals a-b

To find  $V_{oc}$ :

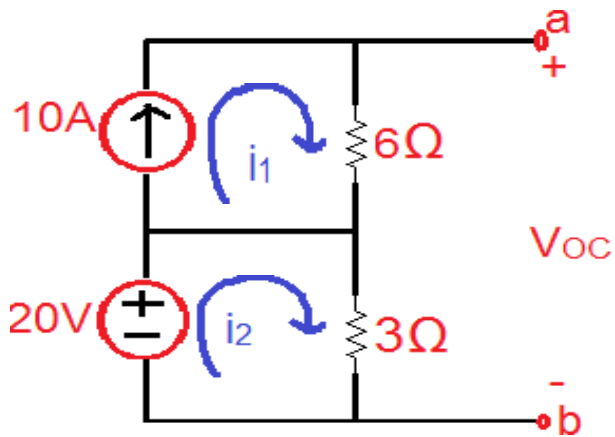


By observation:

$$i_1 = 10 \text{ A}$$

KVL to mesh 2:

$$-20 + 3 i_2 = 0$$

$$i_2 = 20/3 \text{ A}$$

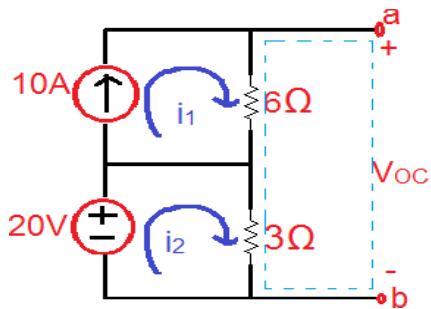

$$- 3i_2 - 6i_1 + V_{oc} = 0$$


KVL along the dotted path

$$V_{oc} = 6 i_1 + 3 i_2$$


Substituting  $i_1$  and  $i_2$

$$V_T = V_{oc} = 80 \text{ V}$$

To find  $R_T$ :

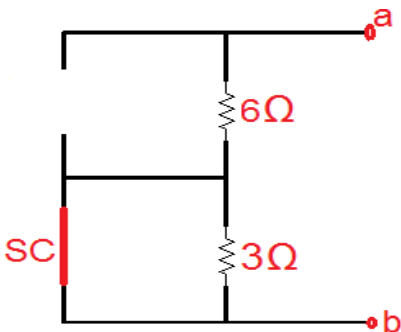


which can be visualized as

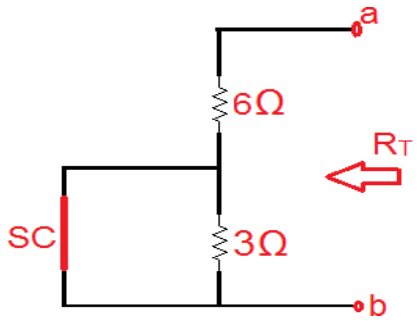

Since  $3\ \Omega$  is in parallel with the short, it is redundant.


Therefore  $R_T = 6\ \Omega$

Therefore Thevenin's network is

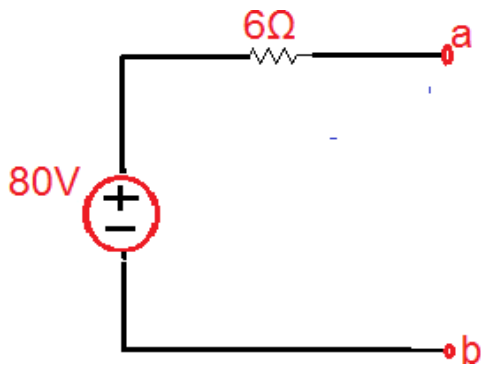

Step 3: To find  $P_{\max}$

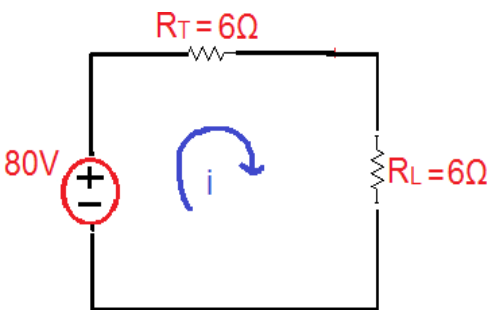Connect  $R_L = R_T$  across the terminals a-b



KVL implies:

$$-80 + 6i + 6i = 0$$

$$i = 20/3 \text{ A}$$

$$P_{\max} = i^2 R_L = (20/3)^2 \times 6 = 266.66 \text{ W}$$

Summary:

1. Maximum power transfer theorem is the extension of Thevenin's theorem.
2. The conditions for Maximum power to be transferred to the load are
  - i) For AC circuits if load is impedance then  $Z_L = Z_T^*$
  - ii) For AC circuits if load is purely resistive then  $R_L = |Z_T|$
  - iii) For DC circuits  $R_L = R_T$
3. Power is always a real entity and therefore for power calculations always real part of  $Z_L$  (i.e.,  $R_L$ ) is used.




## Theorem 4: Superposition Theorem

### Statement:

In any Linear circuit containing multiple independent sources, a current or a voltage at any point in the circuit can be calculated as algebraic sum of Individual contributions of each source when acting alone.
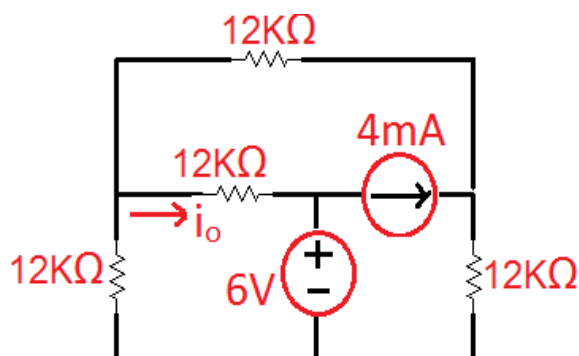
### Problems:

P1. Find  $i_o$  by Super position theorem.



Solution:

$$\text{Let } i_o = i_{o1} + i_{o2}$$

where,



$i_{o1}$  is the contribution of 6 V source when acting alone and

$i_{o2}$  is the contribution of 4mA source when acting alone
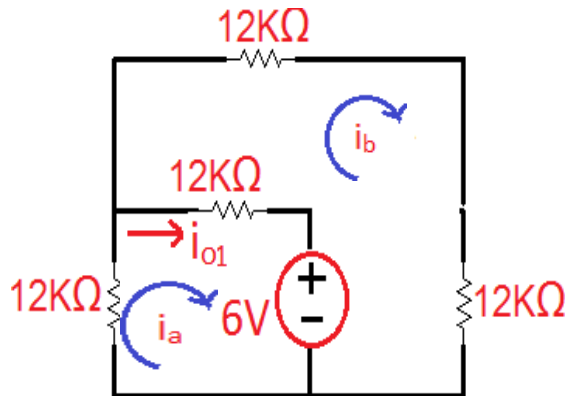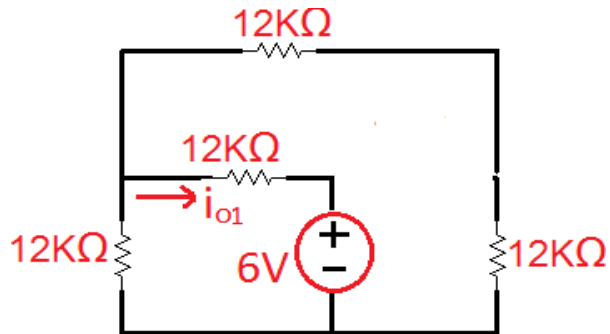
### Steps:

Step 1 : To find  $i_{o1}$  which is the contribution of 6 V acting alone

Deactivating the 4mA source the circuit becomes



Applying KVL to mesh 1:

$$12K i_a + 12K (i_a - i_b) + 6 = 0$$

$$24K i_a - 12K i_b = -6 \dots\dots\dots \text{Eq1}$$

Applying KVL to mesh 2:

$$12K (i_b - i_a) + 12K i_b + 12K i_b - 6 = 0$$

$$-12K i_a + 36K i_b = 6 \dots\dots\dots \text{Eq2}$$

Solving equations Eq1 and Eq2,


$$i_a = -0.2 \text{ mA}$$

$$i_b = 0.1 \text{ mA}$$

$$\mathbf{i_{o1} = i_a - i_b = -0.3 \text{ mA}}$$

Step 2 : To find  $i_{o2}$  which is the contribution of 4mA source acting alone

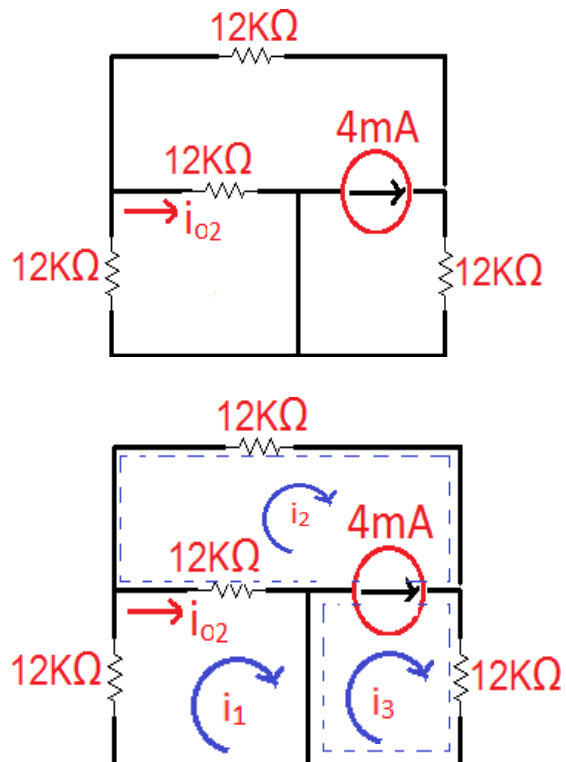Deactivating the 6 V source the circuit becomes



Constraint equation:

$$i_3 - i_2 = 4\text{mA}$$

Applying KVL to mesh 1:

$$12\text{K } i_1 + 12\text{K } (i_1 - i_2) = 0$$

$$24\text{K } i_1 - 12\text{K } i_2 = 0$$

Applying KVL to Supermesh:

$$12\text{K} (i_2 - i_1) + 12\text{K } i_2 + 12\text{K } i_3 = 0$$

$$-12\text{K } i_1 + 24\text{K } i_2 + 12\text{K } i_3 = 0$$

Applying KVL to mesh 1:

$$12K i_1 + 12K (i_1 - i_2) = 0$$

$$24K i_1 - 12K i_2 = 0$$

Solving equations 1, 2 and 3

$$i_1 = -0.8 \text{ mA}; i_2 = -1.6 \text{ mA}; i_3 = 2.4 \text{ mA}$$

$$i_{o2} = i_1 - i_2 = \mathbf{0.8 \text{ mA}}$$

Step 3 : To find  $i_o$


By Super Position Theorem,

$$i_o = i_{o1} + i_{o2}$$

$$i_o = -0.3 \text{ m} + 0.8 \text{ m}$$

$$i_o = \mathbf{0.5 \text{ m A}}$$

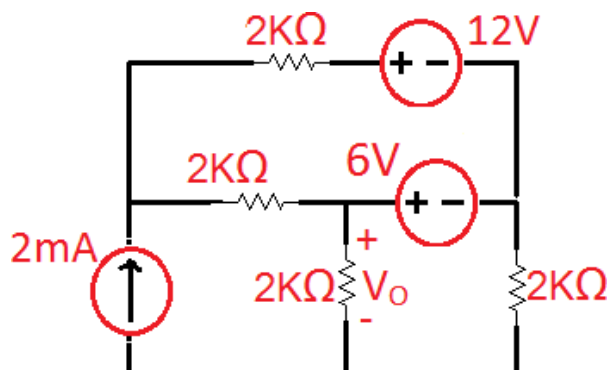P2. Find  $V_o$  by Super position theorem.



Solution:

$$\text{Let } V_0 = V_{01} + V_{02} + V_{03}$$

where,


$V_{01}$  is the contribution of 12V source when acting alone

$V_{02}$  is the contribution of 6V source when acting alone

$V_{03}$  is the contribution of 2mA source when acting alone

Step 1: To find  $V_{01}$

Deactivate 6V and 2mA sources

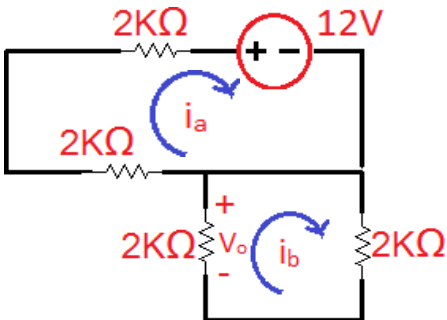

KVL to mesh2:


$$2\text{K } i_b + 2\text{K } i_b = 0$$

$$i_b = 0$$

$$V_{01} = -2\text{K } i_b = 0\text{V}$$

Step 2: To find  $V_{02}$

Deactivate 12V and 2mA sources

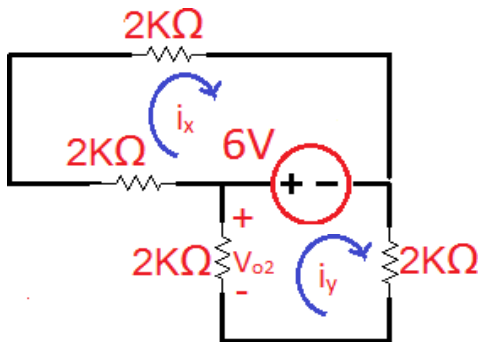

KVL to mesh2:



$$2K i_y + 6 + 2K i_y = 0$$

$$i_y = -1.5\text{mA}$$

$$V_{O2} = -2K i_y = 3\text{V}$$

Step 3: To find  $V_{o3}$

Deactivate 12V and 6V sources

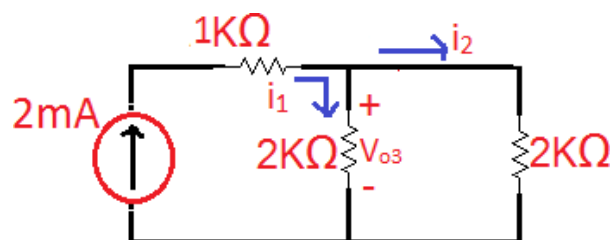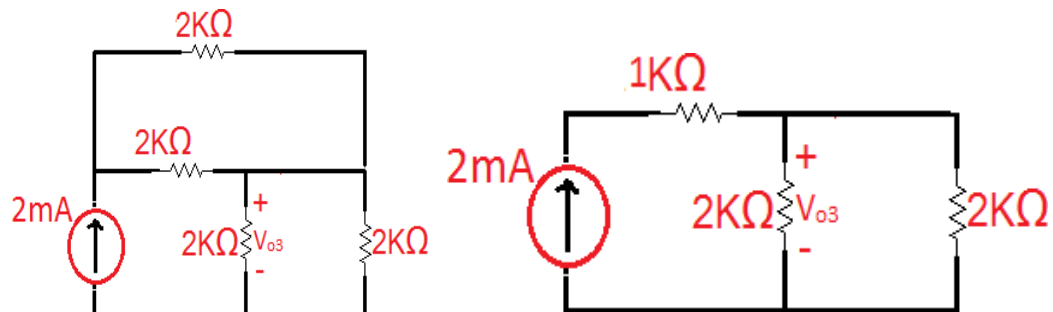

$$i_1 = i_2 = 1\text{mA}$$

$$V_{O3} = 2K i_1 = 2\text{V}$$

Step 4:


By Super position Theorem

$$V_0 = V_{01} + V_{02} + V_{03}$$

$$V_0 = 0 + 3 + 2$$

$$V_0 = 5 \text{ V}$$

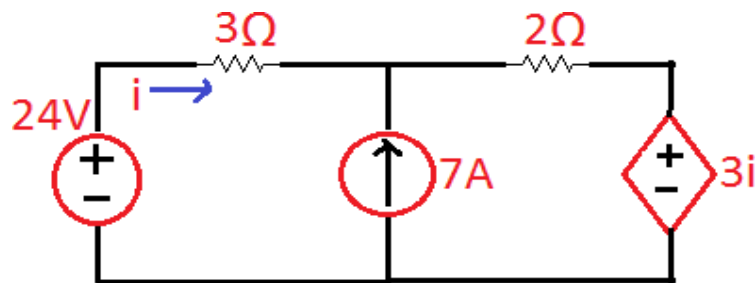P3. Find  $i$  by Super position theorem.



Solution:

$$\text{Let } i = i_1 + i_2$$

where,


$i_1$  is the contribution of 24V source when acting alone

$i_2$  is the contribution of 7A source when acting alone

The dependant voltage source cannot be deactivated - keep it as it is.

Step 1: To find  $i_1$

Deactivate 7A source

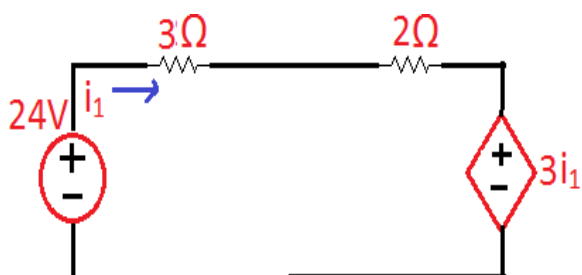



Applying KVL:

$$-24 + 3 i_1 + 2 i_1 + 3 i_1 = 0$$

$$i_1 = 3 \text{ A}$$

Step 2: To find  $i_2$

Deactivate 24V source

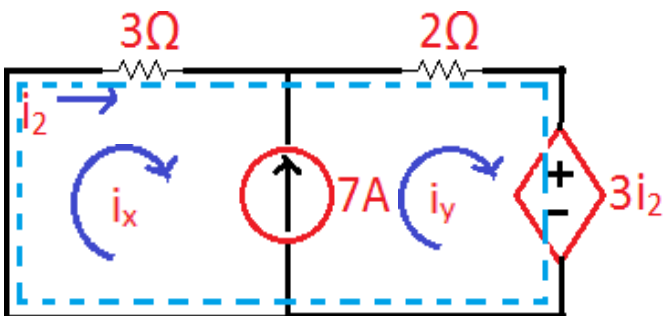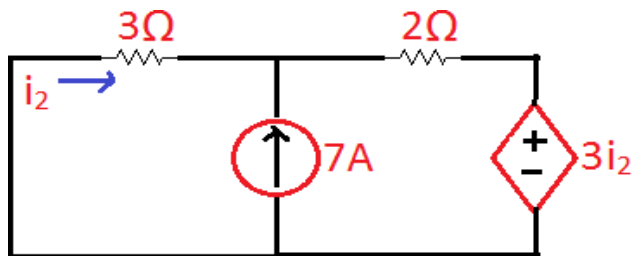

Constraint equation:

$$-i_x + i_y = 7\text{A}$$

KVL to Supermesh:

$$3 i_x + 2 i_y + 3 i_2 = 0$$

Sub.  $i_2 = i_x$

$$3 i_x + 2 i_y + 3 i_x = 0$$

$$6 i_x + 2 i_y = 0$$

Solving the equations

$$-i_x + i_y = 7\text{A}$$



$$6 i_x + 2 i_y = 0$$

Implies,

$$i_x = -1.75 \text{ A and } i_y = 5.25 \text{ A}$$

$$i_2 = i_x = -1.75 \text{ A}$$

Step 3:

By Super position Theorem

$$i = i_1 + i_2$$

$$i = 3 - 1.75$$

$$i = 1.25 \text{ A}$$

Summary:

1. Superposition theorem is applicable to circuits with multiple independent sources only.
2. Dependant sources can be present.
3. At a time only one independent source should be acting, which gives its individual contribution.
4. Algebraic summation of the individual contributions gives the actual current/voltage in a circuit.
5. It is as good as cutting down complex problems into simpler ones.

# **NETWORK ANALYSIS (18EC32)**

## **Syllabus:-**

**Module -3**

**Transient Behavior and initial conditions**

## Initial Conditions


Any electrical n/w consists of Vg sources, current sources, L & C.

When such n/w are to be analysed, the integro-differential eqns are written & solved.

General soln to such eqn consists of 2 parts.

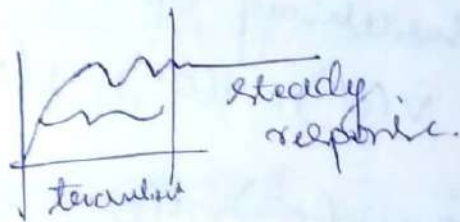- i) Complementary fun  $\rightarrow$  general soln
- ii) particular integral  $\rightarrow$  particular soln

Any response consists of initial state transient response & steady state response



Complementary fun is soln of homogeneous eqn which also represent the response of the system.

Transient response depends on type, value & arrangement of elements in the n/w.

Complementary fun is general soln of homogeneous eqn & particular integral is the particular soln of non homogeneous eqn.

while solving eqn of  $n^{\text{th}}$  order,

we come across  $n$  no of constants in the

Complementary fn, which are to be evaluated

to get ~~particular~~ exact soln. To evaluate these

constants,  $n$  no of initial conditions are required.

The initial conditions of n/w are the conditions prevailing in the elements of the n/w at the time of closing the switch at  $t=0$ .

In a switching opn,  $t=0$  is taken as ref. The initial conditions in n/w may be the voltages across the various elements, currents through them or charges existing on them at time of switching opn i.e. at  $t=0$ .

Immediately before the switching opn, these quantities are referred to as  $v(0^-)$ ,  $i(0^-)$ ,  $q(0^-)$  at  $t=0^-$ .

Immediately after switching opn, these quantities are referred to as  $v(0^+)$ ,  $i(0^+)$ ,  $q(0^+)$  at  $t=0^+$ .

~~Knowing these values of  $v(0^-)$ ,  $i(0^-)$ ,  $q(0^-)$ ,~~

The initial conditions in a n/w depends on the past history of the n/w prior to  $t=0^-$  and n/w structure at  $t=0^+$  just after switching.

They also depend on the nature of elements in the n/w.




The knowledge of initial values of one or more derivative of response, are helpful in anticipating the form of response, thus we can check the soln.

Knowing the values of  $V_g$  & currents of elements at  $t=0^-$ , finding these values at  $t=0^+$ , constitutes the evaluation of initial conditions

Conditions

Initial conditions of element.

Resistor

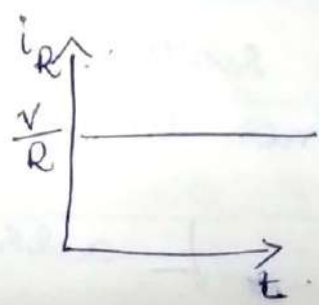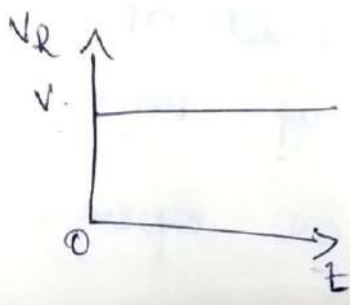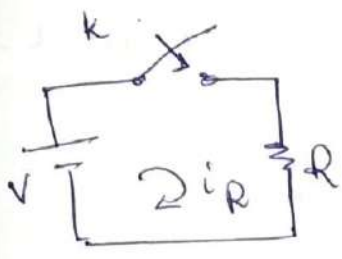

In Resistor, current &  $V_g$ s are related by

$$V = iR$$

when a step response of  $V$   $V_g$  is applied to Resistor

by closing switch at  $t=0$ ,

the current ~~is~~ is also a step function & is given by  $I = \frac{V}{R}$ .


The waveform of current is same as w/f of  $V_g$  i.e

Current through  $R$  changes instantaneously, if

$V_g$  changes instantaneously.

||| by the  $V_g$  across resistor also changes instantaneously when the current through it changes instantaneously

## The inductor:

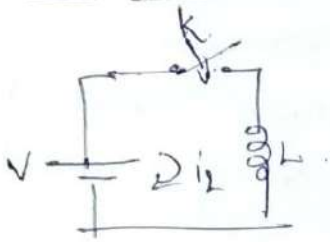

Current through inductor does not change instantaneously.


When switch is closed at  $t=0$ , if inductor does not have any initial current at  $t=0^+$ ,

i.e.  $L$  acts as open ckt.

But at  $t=0^-$ , if the inductor has initial current  $I_0$ . Then at  $t=0^+$ , current in inductor continues to be  $I_0$ , inductor acts as a current source of  $I_0$  ampere.
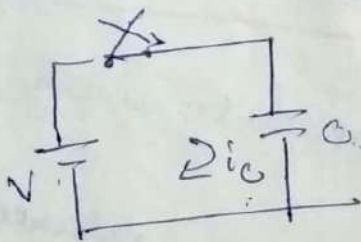
## The Capacitor:

$$C = \frac{Q}{V} \Rightarrow V = \frac{Q}{C}$$




The  $V_C$  across the  $C$  cannot change instantaneously. When uncharged capacitor is connected to a DC  $V_C$  source  $V$  by closing switch  $K$  at  $t=0$ , when there is no charge on  $C$ ,  $V_C$  across it is zero & hence acts as short ckt.

If capacitor has initial charge of  $Q_0$  counts at  $t=0^-$ , then at  $t=0^+$ , the capacitor is equivalent to  $V_C$  source of  $V = \frac{Q_0}{C}$ .


Primary  
Initial  
Cond.

Initial Conditions

Condition of element at  $t = 0^-$

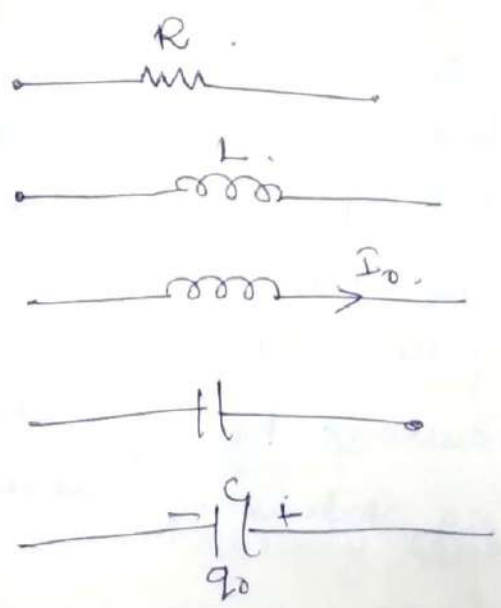

Condition of element at  $t = 0^+$

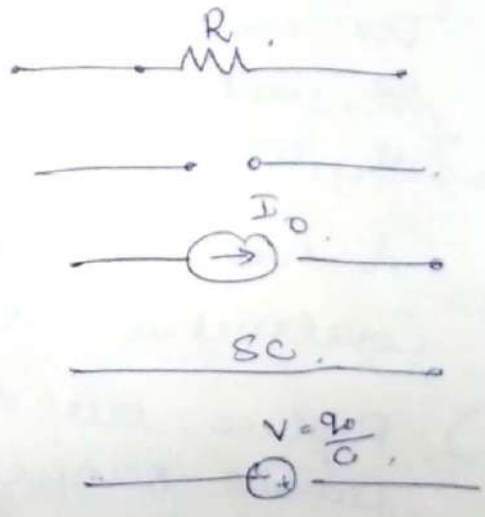

There are some exceptions to the initial conditions of the elements. They are:

1. When the impulse  $v_q$  is applied to an inductance, its current changes instantaneously.
2. When an impulse current is applied to a capacitor, its  $v_q$  changes  $\int A \cdot \frac{1}{C}$  instantaneously.

Procedure for finding initial conditions:

There is no unique procedure to be followed for to find the initial conditions.

It is like a game of chess, strategy is chosen depending on other opposite party move. Here the procedure depends on the particular  $np$  being considered.

general procedure is as follows:

1. Initial values of voltages & currents before switch at  $t=0^-$  can be found directly from the schematic diagram of given circuit.
2. For each value element of the n/w, we must find out, what happens to element at  $t=0^+$  i.e. after closing the switch.
3. A new equivalent n/w at  $t=0^+$  is constructed as per following rules.
  - a) Replace all the inductors by open ckt & current source having value of current flowing at  $t=0^-$ .
  - b) Replace all the capacitors by short ckt or Vg source of  $v = \frac{q_0}{C}$ , if there is any initial charge.
  - c) Resistors are left in the n/w without any change.
4. From n/w at  $t=0^+$ , first initial values of Vg & currents are solved. Then their derivatives are found.

VI relations of n/w elements

~~R~~  $R \rightarrow v(t) = R i(t) \quad \text{and} \quad i(t) = \frac{v(t)}{R}$

$L \rightarrow v(t) = L \frac{di(t)}{dt} \quad \& \quad i(t) = \frac{1}{L} \int_0^t v(t) dt$

$= \frac{1}{L} \int_0^t v(t) dt + i_L(0^-)$

$C \rightarrow v(t) = \frac{1}{C} \int_0^t i(t) dt \quad \& \quad i(t) = \frac{C dv(t)}{dt}$


$v(t) = \frac{1}{C} \int_0^t i(t) dt + v_C(0^-)$

$C = \frac{Q}{V}$   
 $V = \frac{Q}{C} = \frac{I t}{C}$




Final Conditions in a n/w. i.e at  $t = \infty$ .

(4)

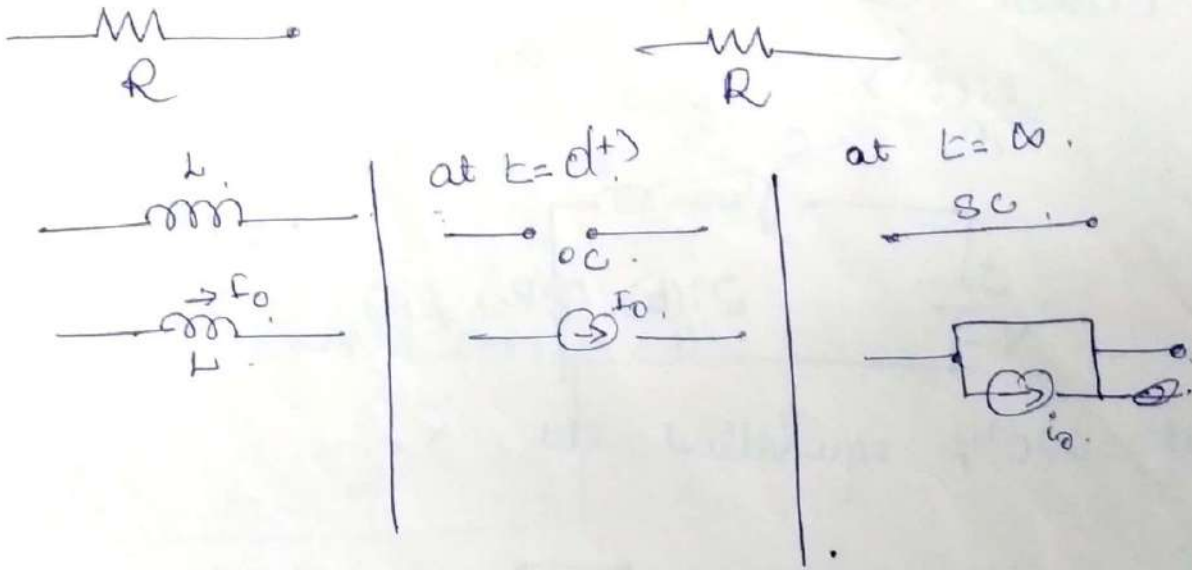

$$V = L \frac{di}{dt}$$

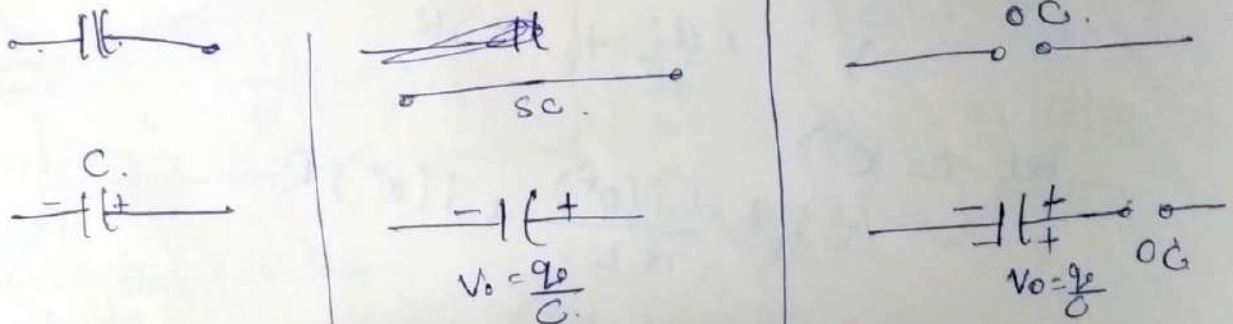
Under steady state condition  $\frac{di}{dt} = 0$ .  
 This means  $v = 0$  & hence  $L$  acts as short ckt at  $t = \infty$ .  
 uncharged &  $v = 0 \Rightarrow sr$



$$I(t) = C \frac{dV(t)}{dt}$$


Under steady state.  $\frac{dV(t)}{dt} = 0$  i.e at  $t = \infty$ ,  $i(t) = 0$ .  
 i.e capacitor acts as an open ckt.

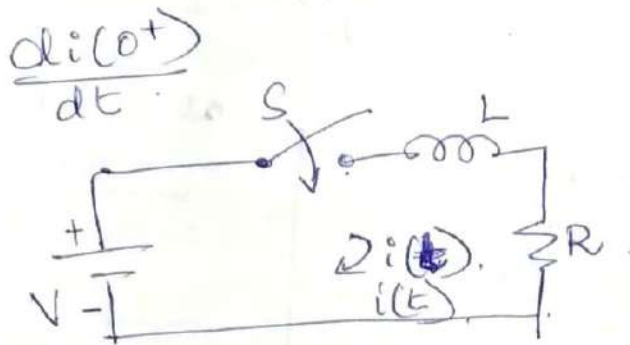4. For the n/w shown below, switch  $S$  closed at  $t=0$ , find the conditions  $i(0^+)$



$$V = L \frac{di}{dt} + iR$$

at  $t=0^+$ , equivalent ckt is

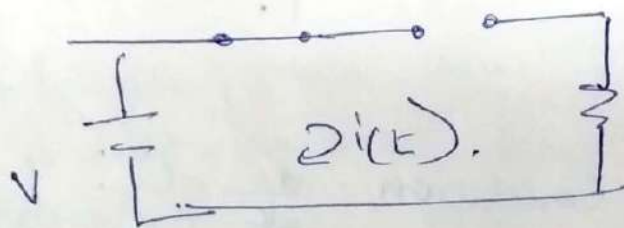

$$i(0^+) = 0$$

KVL to given loop.

$$V = L \frac{di}{dt} + i(t)R$$

at  $t=0^+$

$$V = L \frac{di(0^+)}{dt} + i(0^+)R$$

$$V = L \frac{di(0^+)}{dt}$$

$$\frac{di(0^+)}{dt} = \frac{V}{L}$$


For the ckt shown.

(5)

$V = 10V, R = 10\Omega, L = 1H, C = 10\mu F$

&  $V_C(0) = 0$  find

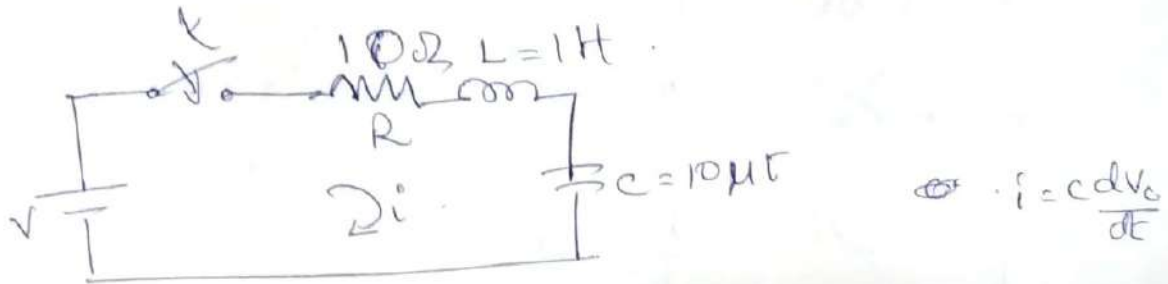
$i(t^+), \frac{di}{dt}(t^+)$  and  $\frac{d^2i}{dt^2}(t^+)$ .



switch is closed at  $t = 0$

$V = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt$  (1)

At  $t = 0^+$ .

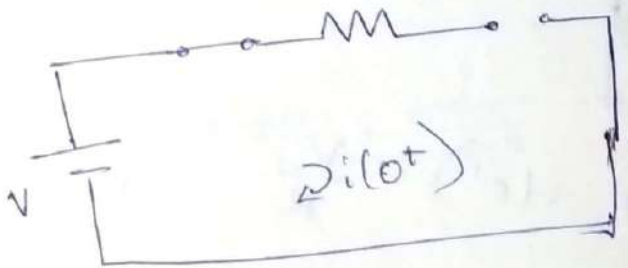

$\therefore i(0^+) = 0$

at  $t = 0^+$ .

~~$V = R i(0^+) +$~~

~~$V = R i(0^+) + L \frac{di(0^+)}{dt} + \frac{1}{C} \int i(0^+) dt$~~

KVL to this loop

$V = R i(0^+) + L \frac{di(0^+)}{dt}$

$V = 0 + L \frac{di(0^+)}{dt}$

$\frac{di(0^+)}{dt} = \frac{V}{L} = \frac{10}{1} = 10 A/sec.$

Differentiating (1)

$\frac{d}{dt} (R \frac{di(0^+)}{dt} + L \frac{d^2i(0^+)}{dt^2} + \frac{1}{C} i(0^+)) = 0$

$10 \times 10 + L \frac{d^2i(0^+)}{dt^2} + \frac{1}{C} (0) = 0$


$\frac{d^2i(0^+)}{dt^2} = \frac{-100}{L} = \frac{-100}{1} = -100 A/sec^2$

$\therefore V \neq 0$

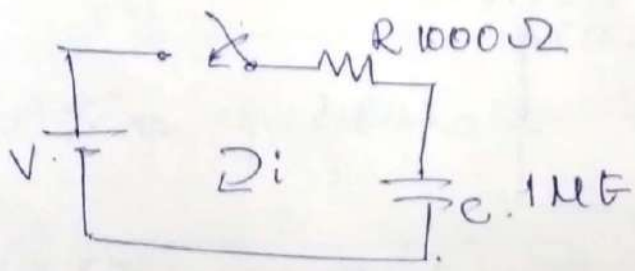3) in the n/w shown, the switch k is closed at  $t=0$ , with capacitor uncharged.

Find the values for  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  at  $t=0^+$ , for the element values as follows.

$V = 100V$ ,  $R = 1000\Omega$  and  $C = 1\mu F$




when closed at  $t=0$ ,

$$V = iR + \frac{1}{C} \int i dt$$

n/w at  $t = 0^+$ .

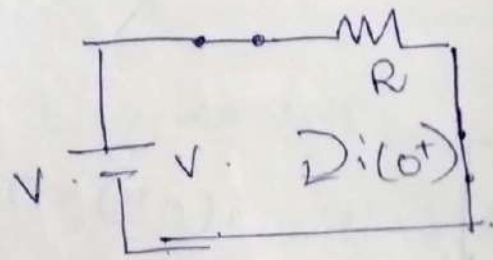$C \rightarrow$  uncharged  $\rightarrow V_C = 0 \rightarrow SC$ .



$$V = iR$$

$$V = i(0^+) R \Rightarrow i(0^+) = \frac{V}{R} = \frac{100}{1000} = 0.1A$$

diff (1)

$$R \frac{di(0^+)}{dt} + \frac{1}{C} i(0^+) = 0 \quad \text{--- (2)}$$

$$R \frac{di(0^+)}{dt} + \frac{1}{0.000001} (0.1) = 0$$

$$\frac{di(0^+)}{dt} = - \frac{0.1 \times 10^6}{R}$$

$$\frac{di(0^+)}{dt} = - \frac{0.1 \times 10^6}{1000} = -0.1 \times 10^3$$

$$= -1 \times 10^2$$


$$= -100 A/sec$$

diff (2)

$$R \frac{d^2i(0^+)}{dt^2} + \frac{1}{C} \frac{di(0^+)}{dt} = 0$$


$$\frac{d^2i(0^+)}{dt^2} = - \frac{\frac{1}{C} \frac{di(0^+)}{dt}}{R} = \frac{-100}{10^3} = \frac{100}{10^3} = 10^{-1} = 0.1 A/sec^2$$

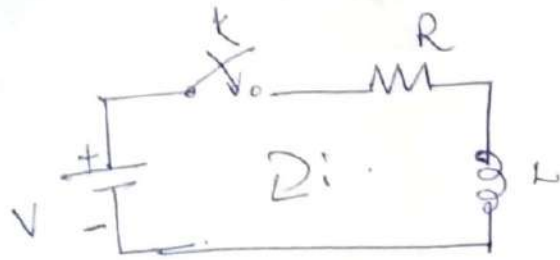In the n/w shown,  $K$  is closed at  $t=0$ , with zero current in the inductor. Find  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t=0^+$ , if  $R=10\Omega$ ,  $L=1H$  and  $V=100V$ .



$$V = iR + L \frac{di}{dt} \quad \text{--- (1)}$$

at  $t=0^+$

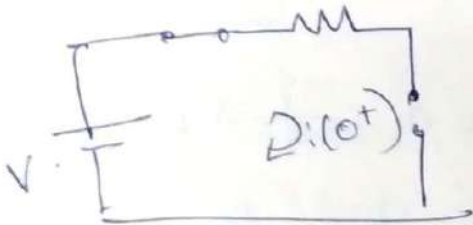

$$i(0^+) = 0$$

diff (1)

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} = V - iR$$

$$\frac{di}{dt} = \frac{V - i(0^+)R}{L}$$

$$= \frac{100}{1}$$

$$= 100 \text{ A/sec.}$$

diff (1)



$$R \frac{di(0^+)}{dt} + L \frac{d^2i(0^+)}{dt^2} = 0$$

$$10 \times 100 + 1 \frac{d^2i(0^+)}{dt^2} = 0$$

$$\frac{d^2i(0^+)}{dt^2} = -1000 \text{ A/sec}^2$$

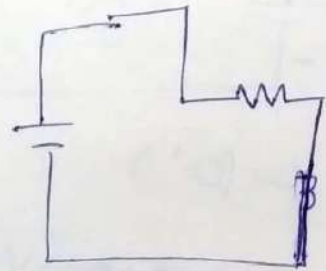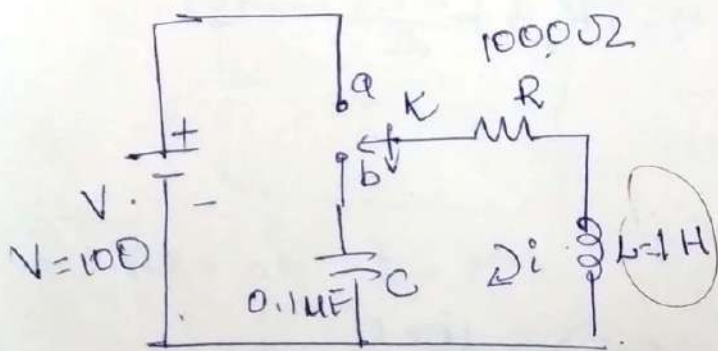5) For the circuit shown,  $k$  is changed from position  $a$  to  $b$  at  $t=0$ . Solve for  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  at  $t=0^+$ .

If  $R = 1000 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 0.1 \mu\text{F}$  and  $V = 100 \text{ V}$ . Assume that capacitor is initially uncharged.




when switch  $k$  is at position  $a$ .  $\rightarrow L \rightarrow \text{sc}$ .

$$i(0^-) = \frac{V}{R} = \frac{100}{1000} = 0.1 \text{ A}$$

$$i(0^+) = 0.1 \text{ A}$$

when  $k$  is changed from  $a$  to  $b$ ,

$$i(0^+) = 0.1 \text{ A}$$

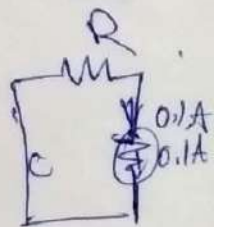

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0$$

$$Ri(0^+) + L \frac{di(0^+)}{dt} + \frac{1}{C} \int i(0^+) dt = 0$$

$$Ri(0^+) + L \frac{di(0^+)}{dt} + V_C(0^+) = 0$$

$$Ri(0^+) + L \frac{di(0^+)}{dt} = 0$$

$$\frac{di(0^+)}{dt} = \frac{-R \times 0.1}{L} = \frac{-1000 \times 0.1}{1} = -100 \text{ A/sec}$$

initially uncharged  $C \rightarrow \text{sc}$ .

diff (1)

$$R \frac{di(t)}{dt} + L \frac{d^2i}{dt^2} + \frac{1}{C} i = 0$$

$$1000 \times (-100) + L \frac{d^2i(t)}{dt^2} + \frac{i(t)}{C} = 0$$

$$-10^5 + L \frac{d^2i(t)}{dt^2} + \frac{0.1}{0.1 \times 10^{-6}} = 0$$


$$\frac{d^2i(t)}{dt^2} = 10^5 - 1 \times 10^{-1} \times 10^7$$

$$= 10^5 - 10^6$$

$$= -9 \times 10^5 \text{ A/sec}^2$$

$$\frac{1000000}{100000} = \frac{1000000}{900000}$$

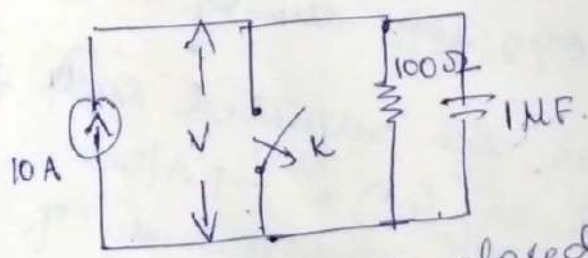6) In the circuit shown in fig. Switch k is opened at  $t=0$ . find the values of  $V$ ,  $\frac{dV}{dt}$  and  $\frac{d^2V}{dt^2}$  at  $t=0^+$ .




$i = C \frac{dV}{dt}$

$$10 + \frac{V}{100} + C \frac{dV}{dt} = 0$$


$$\frac{V}{100} + C \frac{dV}{dt} = -10 \quad \text{--- (1)}$$

When switch is closed, all the current flows through the switch, & capacitor is not charged.

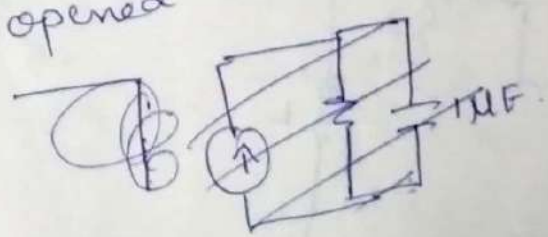$\therefore V_C(0^-) = 0 = V_C(0^+)$   
when opened



at  $t=0^+$

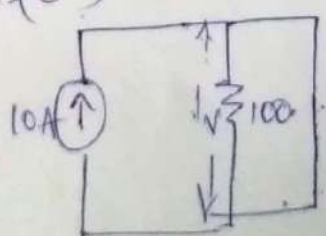

$V(0^+) = 0$  ( $\because$  sc)

$$\frac{v(0^+)}{100} + c \frac{dv(0^+)}{dt} = 10$$

$$0 + c \frac{dv(0^+)}{dt} = 10$$

$$\frac{dv(0^+)}{dt} = \frac{10}{c} = \frac{10}{10^{-6}} = 10^7 \text{ V/sec}$$

diff (1)

$$\frac{dv}{dt} + c \frac{d^2v}{dt^2} = 0$$

$$\frac{10^7 \text{ s}}{10^2} + c \frac{d^2v}{dt^2} = 0$$

$$c \frac{d^2v}{dt^2} = -10^5$$

$$\frac{d^2v}{dt^2} = \frac{-10^5}{c} = \frac{-10^5}{10^{-6}} = -10^{11} \text{ V/sec}^2$$


7

In the N/w shown, the switch is opened at  $t=0$ , after the N/w has attained the steady state with the switch closed.

a) Find an expression for the  $V_g$  across the switch at  $t=0^+$ .

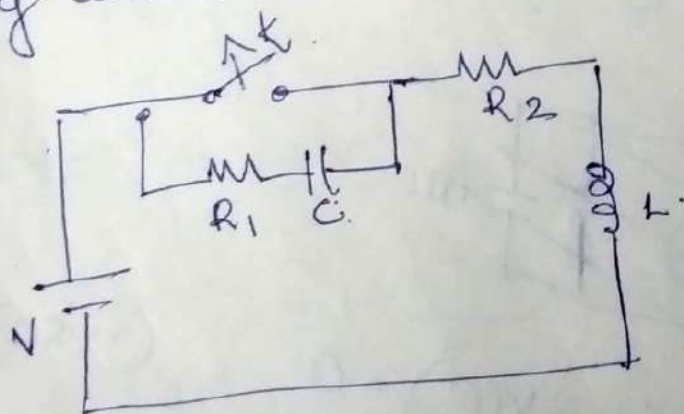
b) If the parameters are adjusted such that  $i(0^+) = 1 \text{ A}$  and  $\frac{di}{dt}(0^+) = -1 \text{ A/sec}$ .

What is the value of the derivative of the  $V_g$  across the switch?






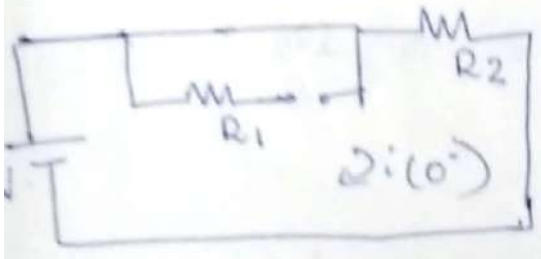
when k is closed, steady state attained  
 $L$  acts as SC &  $C$  act as OC



$$i(0^-) = \frac{V}{R_2} = i(0^+)$$

& capacitor is uncharged,  
 $v_c(0^-) = 0 = v_c(0^+)$

when k is opened

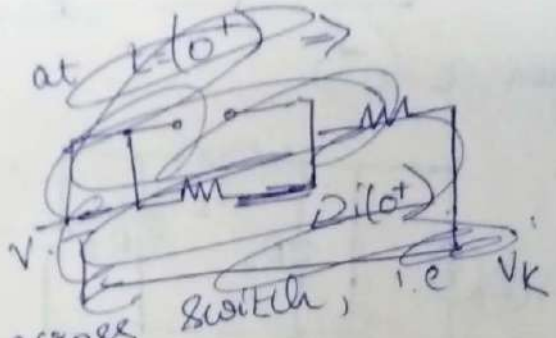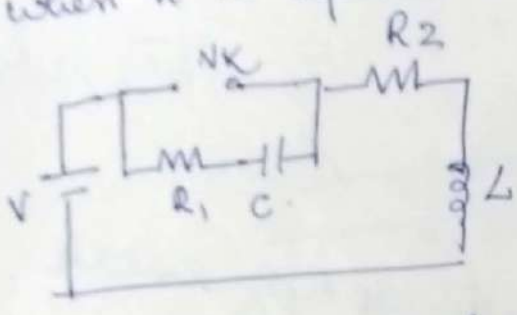

They ask to find  $v_k$  across switch, i.e.  $v_k$

$$v_k = i(t)R_1 + \frac{1}{C} \int i dt. \quad \text{--- (1)}$$

at  $t=0^+$   $v_k = i(0^+)R_1 + v_c(0^+)$

$$v_k = i(0^+)R_1$$

$$v_k = \frac{V}{R_2} \cdot R_1 =$$

$$v_k = V \frac{R_1}{R_2}$$


$$\frac{dv_k}{dt} = \frac{di}{dt} R_1 + \frac{i}{C}$$

$$\frac{dv_k(0^+)}{dt} = R_1(-1) + \frac{V}{C}$$


$$\frac{dv_k}{dt} = -R_1 + \frac{V}{C}$$

$$\frac{dv_k}{dt} = \frac{1}{C} - R_1$$

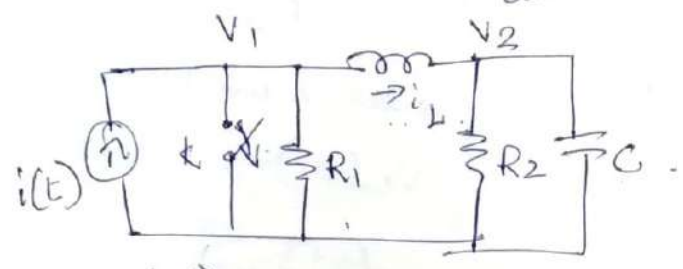8) The n/w shown in fig has 2 independent pairs. If the switch  $k$  is opened at  $t=0$ , find the following quantities at  $t=0^+$ ,  
 i)  $V_1$  ii)  $V_2$  iii)  $\frac{dV_1}{dt}$  & iv)  $\frac{dV_2}{dt}$ .



when  $t=0^+$

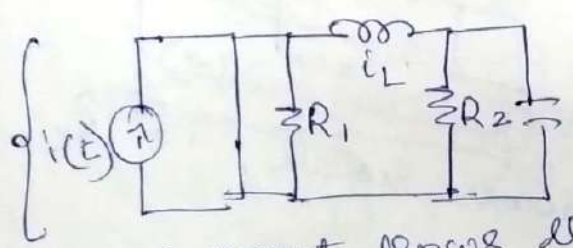


all current flows through closed switch.

hence  $i_L(0^-) = 0$   ~~$i_L(0^+)$~~ :  $V_C(0^-) = 0$   
 $\therefore i_L(0^+) = 0$  &  $V_C(0^+) = 0$   
 $\therefore V_2(0^+) = 0$

when switch  $k$  is opened at  $t=0$ ,

at node

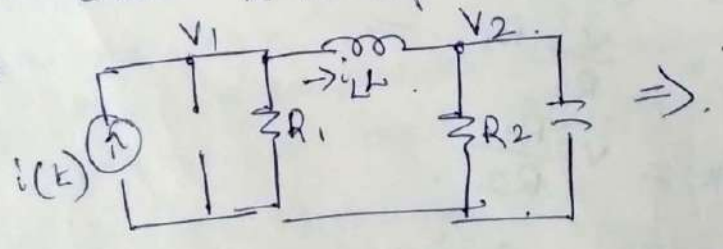

at node  $V_1$   $-i(t) + \frac{V_1}{R_1} + i_L = 0$  ①

$i(t) = \frac{V_1}{R_1} + i_L(0^+)$

$i(0^+) = \frac{V_1(0^+)}{R_1} + 0$

$\therefore V_1(0^+) = R_1 [i(0^+)]$  ②

At node  $v_2$ .

(9)

$$-i_L + \frac{v_2}{R_2} + C \frac{dv_2}{dt} = 0 \quad \text{--- (3)}$$

$$\text{at } t=0^+ \quad -i_L(0^+) + \frac{v_2(0^+)}{R_2} + C \frac{dv_2(0^+)}{dt} = 0.$$

$$0 + 0 + C \frac{dv_2(0^+)}{dt} = 0$$

$$\Rightarrow \frac{dv_2(0^+)}{dt} = 0.$$

diff (1)

$$\text{eqn (1)} \quad i(t) = \frac{v_1}{R_1} + i_L(t)$$

$$\frac{di(t)}{dt} = \frac{1}{R_1} \frac{dv_1(t)}{dt} + \frac{di_L(t)}{dt} = 0.$$

$$\frac{di}{dt} = -d$$

$$\frac{di(t)}{dt} = \frac{1}{R} \frac{dv_1}{dt} + \frac{di_L}{dt}$$

$$\frac{di(0^+)}{dt} = \frac{1}{R} \frac{dv_1(0^+)}{dt} + \frac{R_1 i(0^+)}{L}$$

$$\frac{1}{R} \frac{dv_1(0^+)}{dt} = \left[ \frac{di(0^+)}{dt} - \frac{R_1 i(0^+)}{L} \right]$$

$$\frac{dv_1(0^+)}{dt} = R_1 \left[ \frac{di(0^+)}{dt} - \frac{R_1 i(0^+)}{L} \right]$$

$$v = L \frac{di_L}{dt}$$

$$\therefore i_L = \frac{1}{L} (v_1 - v_2) d$$

$$\frac{di_L}{dt} = \frac{v_1 - v_2}{L}$$


$$\frac{di_L(0^+)}{dt} = \frac{1}{L} [v_1 - v_2]$$

$$= \frac{1}{L} [R_1 i(0^+) - 0] - \frac{R_1 i(0^+)}{L}$$

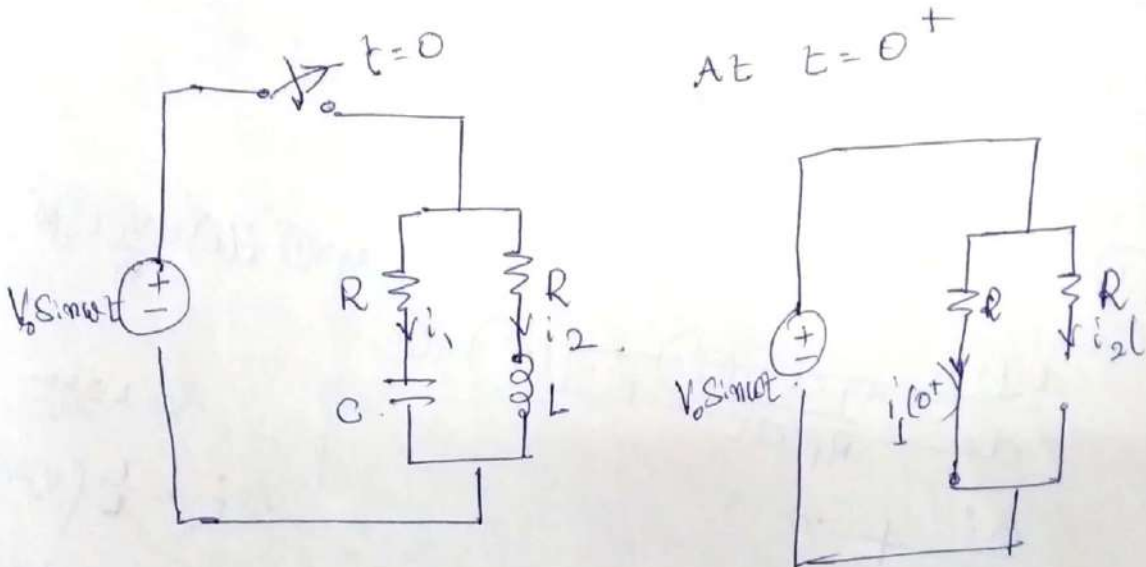9) In the ckt shown. the switch K is at  $t=0$ . S.T. at  $t=0^+$

$$\frac{di_1}{dt} = \frac{V_0}{R} \left[ \omega \cos \omega t - \frac{\sin \omega t}{RC} \right] \quad \&$$

$$\frac{di_2}{dt} = \frac{V_0 \sin \omega t}{L}$$



$$i_1(0^+) = \frac{V_0 \sin \omega t}{R} \quad i_2(0^+) = 0$$

writing loop eqn for  $i_1$

$$V_0 \sin \omega t = i_1 R + \frac{1}{C} \int i_1 dt \quad \text{--- (1)}$$

loop eqn for  $i_2$

$$V_0 \sin \omega t = i_2 R + L \frac{di_2}{dt} \quad \text{--- (2)}$$

diff (1)

$$R \frac{di_1}{dt} + \frac{i_1}{C} = V_0 (\cos \omega t) \omega$$

$$R \frac{di_1(0^+)}{dt} + \frac{i_1(0^+)}{C} = V_0 \omega \cos \omega t$$

$$R \frac{di_1(0^+)}{dt} = V_0 \omega \cos \omega t - \frac{i_1(0^+)}{C}$$

$$= V_0 \omega \cos \omega t - \frac{V_0 \sin \omega t}{RC}$$

$$\frac{di_1(0^+)}{dt} = \frac{V_0}{R} \left[ \omega \cos \omega t - \frac{\sin \omega t}{RC} \right]$$


diff (2)

$$V_0 \omega \cos \omega t = \frac{di_2}{dt} R + L \frac{di_2}{dt}$$

$$\frac{di_2}{dt} = \frac{1}{L} \left[ V_0 \sin \omega t - i_2(0^+) R \right] = \frac{V_0 \sin \omega t}{L}$$

In the n/w shown. Switch  $k$  is closed at  $t=0$ .  
The n/w being initially unenergized.

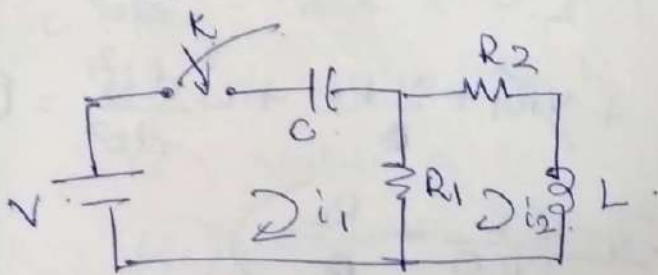find  $i_1(t^+)$ ,  $i_2(t^+)$ ,  $\frac{di_1(t^+)}{dt}$ ,  $\frac{di_2(t^+)}{dt}$ ,  $\frac{d^2i_1(t^+)}{dt^2}$




$$V = \frac{1}{C} \int i_1 dt + R_1 (i_1 - i_2) \quad \text{--- (1)}$$

$$R_1 (i_2 - i_1) + R_2 i_2 + L \frac{di_2}{dt} = 0$$

$$-R_1 i_1 + i_2 (R_1 + R_2) + L \frac{di_2}{dt} = 0 \quad \text{--- (2)}$$

at  $t=0^+$ ,

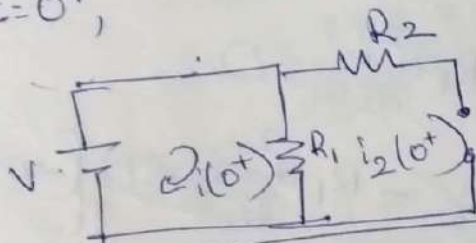

$$i_1(t^+) = \frac{V}{R_1} \quad \& \quad i_2(t^+) = 0$$

from (2)

$$-R_1 i_1(t^+) + i_2(t^+) (R_1 + R_2) + L \frac{di_2(t^+)}{dt} = 0$$

$$-R_1 \frac{V}{R_1} + 0 + L \frac{di_2(t^+)}{dt} = 0$$

$$L \frac{di_2(t^+)}{dt} = V \Rightarrow \boxed{\frac{di_2(t^+)}{dt} = \frac{V}{L}}$$

diff (1)

$$0 = \frac{i_1(t^+)}{C} + \frac{di_1(t^+)}{dt} R_1 - R_1 \frac{di_2(t^+)}{dt} = 0 \quad \text{--- (3)}$$

$$= \frac{V}{R_1 C} + \frac{di_1(t^+)}{dt} R_1 - R_1 \frac{V}{L} = 0$$

$$\frac{di_1(t^+)}{dt} R_1 = +V \left( \frac{R_1}{L} - \frac{1}{R_1 C} \right) \Rightarrow \frac{di_1(t^+)}{dt} = \frac{V}{R_1} \left( \frac{R_1}{L} - \frac{1}{R_1 C} \right)$$

diff eqn (2).

$$-R_1 \frac{di_1}{dt} + R_1 \frac{di_2}{dt} + R_2 \frac{di_2}{dt} + L \frac{di_2^2}{dt^2} = 0$$

$$-R_1 \left[ \frac{V}{R_1} \left( \frac{R_1}{L} - \frac{1}{R_1 C} \right) \right] + R_1 \left( \frac{V}{L} \right) + R_2 \frac{V}{L} + L \frac{di_2^2}{dt^2} = 0$$

$$-V \left( \frac{R_1}{L} - \frac{1}{R_1 C} \right) + \frac{V}{L} (R_1 + R_2) + L \frac{di_2^2}{dt^2} = 0$$

$$-\frac{V}{L} \left( R_1 - \frac{L}{R_1 C} \right) + \frac{V}{L} (R_1 + R_2) + L \frac{di_2^2}{dt^2} = 0$$

$$-VR_1 + \frac{VL}{R_1 C} + VR_1 + \frac{VR_2}{L} + L^2 \frac{di_2^2}{dt^2} = 0$$

$$L^2 \frac{di_2^2}{dt^2} = -\frac{V}{L} \left( \frac{L}{R_1 C} + \frac{R_2}{L} \right)$$

$$\frac{di_2^2}{dt^2} = -\frac{V}{L^2} \left( \frac{L}{R_1 C} + \frac{R_2}{L} \right)$$

$$= -V \left[ \frac{1}{R_1 C} + \frac{R_2}{L^2} \right]$$

diff eqn (3).

$$\frac{1}{C} \frac{di_1}{dt} + R_1 \frac{d^2 i_1}{dt^2} - R_1 \frac{d^2 i_2}{dt^2} = 0$$

$$\frac{1}{C} \left( \frac{V}{L} - \frac{V}{R_1^2 C} \right) + R_1 \frac{d^2 i_1}{dt^2} - R_1 \frac{d^2 i_2}{dt^2} = \left[ (-V) \left( \frac{1}{R_1 C} + \frac{R_2}{L} \right) \right]$$

$$\left\{ \begin{aligned} \frac{1}{C} \left( \frac{V}{L} - \frac{V}{R_1^2 C} \right) + R_1 \frac{d^2 i_1}{dt^2} + R_1 V \left( \frac{1}{R_1 C} + \frac{R_2}{L} \right) &= 0 \\ R_1 \frac{d^2 i_1}{dt^2} &= - \left( \frac{V}{LC} - \frac{VR_1 R_2}{L^2} \right) - \frac{V}{CL} + \frac{V}{R_1^2 C^2} \end{aligned} \right.$$


$$= -\frac{2V}{LC} - \frac{VR_1 R_2}{L^2} + \frac{V}{R_1^2 C^2}$$

$$\frac{d^2 i_1}{dt^2} = \frac{1}{R_1} \left[ \frac{1}{C} \left( \frac{V}{R_1^2 C} - \frac{V}{L} \right) - VR_1 \left( \frac{1}{R_1 C} + \frac{R_2}{L} \right) \right]$$

(12)


For the ckt shown. Switch  $K$  is closed at  $t=0$ , connecting the battery to an energized n/w. Determine.

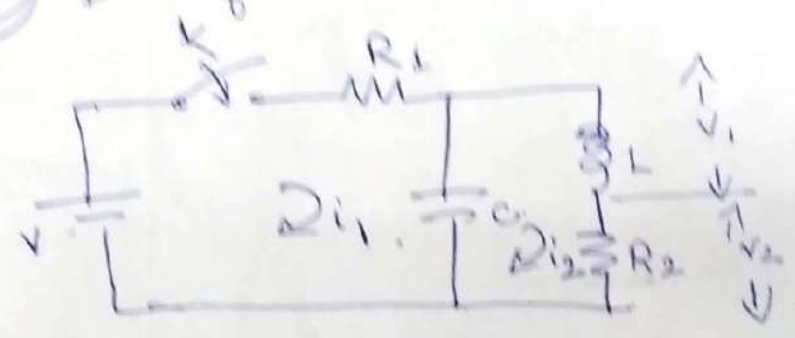- i)  $V_1$  and  $V_2$  at  $t=0^+$  &  $t=\infty$ .
- ii) ESB of second derivative of  $V_1$  &  $V_2$  at  $t=0^+$ .



at  $t=0^+$

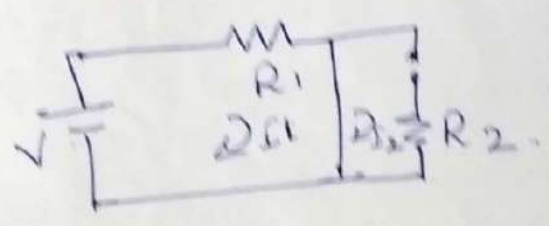$i_2(0^+) = 0$      $L \rightarrow \text{OC}$   
 $C \rightarrow \text{SC}$



$i_1(0^+) = \frac{V}{R_1}$

$\theta \quad V_1 + V_2 = 0$  but  $V_2(0^+) = 0 \quad \therefore i_2(0^+) = 0$   
 $\therefore V_1 = 0 \Rightarrow V_1(0^+) = 0$


At  $t=\infty$ ,  $L \rightarrow \text{SC}$      $C$  acts as OC.

$V_1(\infty) = 0$      $V_2(\infty) = \frac{V}{R_1 + R_2} R_2$

In the ckt shown. the capacitor is initially uncharged, switch k is closed at time  $t=0$ .

The initial value of current is found to be 25mA through CRO. The transient disappears (reduces 2% of its initial value) after a time 0.1 sec.   
 By classical method   
 By Determine

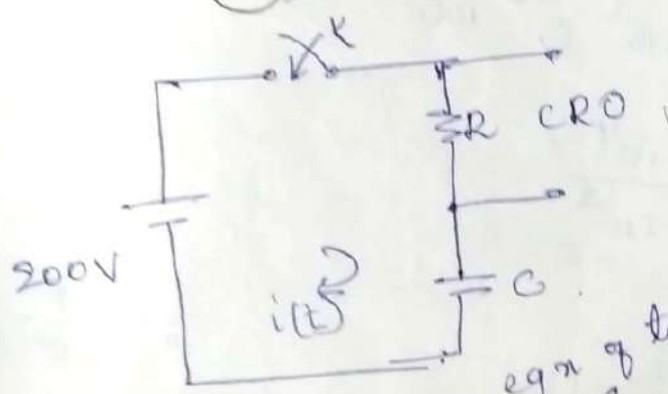- i) the value of R
- ii) value of C
- iii) expression for the current  $i(t)$  for  $t > 0$ .



when k is closed at  $t=0$ ,  $200 = iR + \frac{1}{C} \int i dt$  (1)

diff (1).  $\left(\frac{di}{dt} R + \frac{i}{C}\right) = 0$ .  $(R \frac{di}{dt} + \frac{i}{C}) = 0$

solving  $\text{soln}$  of eqn of type  $(RS + \frac{1}{C}) i = 0 \Rightarrow RS + 1 = 0$

$(RSC + 1) = 0$  &  $S = -\frac{1}{RC}$

$i = k e^{st} \Rightarrow i = k e^{-t/RC}$  where k is constant

At  $t(0^+)$   $i(0^+) = 25 \text{ mA}$  (given)  $e^0 = 1$   
 $25 \text{ m} = k e^{-0/RC} = k$

$k = 25 \text{ mA}$

$i = 25 \times 10^{-3} e^{-t/RC}$

~~$i(0^+) = \dots$~~



At  $t=0^+$ ,  $C \rightarrow sc$ . (given)

$$i(0^+) = \frac{V}{R} = \frac{200}{R} = 25 \text{ mA}$$

$$\textcircled{a} \quad \frac{200}{R} = 25 \text{ mA} \Rightarrow R = \frac{200}{25 \text{ mA}} = 8000 \Omega$$

$$R = 8 \text{ k}\Omega$$

After 0.1 sec

$$i = 2\% \text{ of initial } V.$$

$$= \frac{2}{100} \times 25 \times 10^{-3}$$

$$\frac{2}{100} \times 25 \times 10^{-3} = k e^{-t/RC}$$

$$\textcircled{a} \quad 5 \times 10^{-4} = 25 \times 10^{-3} e^{-0.1/RC}$$

$$e^{-0.1/RC} = \frac{5 \times 10^{-4}}{25 \times 10^{-3}}$$

$$e^{-0.1/RC} = \frac{1}{50}$$

$$e^{-t} = \frac{1}{e^t}$$

$$\textcircled{a} \quad \frac{1}{e^{0.1/RC}} = \frac{1}{50}$$

$$\textcircled{a} \quad e^{0.1/RC} = 50$$

$$\frac{0.1}{RC} = \ln(50) = 3.91$$

$$\frac{0.1}{RC} = 3.91$$

$$RC = \frac{0.1}{3.91} = 0.0256$$

$$C = \frac{0.0256}{R} = \frac{0.0256}{8 \text{ k}} = 3.195 \mu\text{F}$$

# **NETWORK ANALYSIS (18EC32)**

## **Syllabus:-**

**Module -4**

**Laplace Transform and its Applications**

## Laplace transformation

$$\mathcal{L}[f(t)] = F(s) = \int_0^{\infty} f(t) e^{-st} dt$$

where  $s = \sigma + j\omega$  is a complex number.


provided  $\int_0^{\infty} |f(t)| e^{-\sigma t} dt < \infty$  for real +ve  $\sigma$ .

$s = \sigma + j\omega$  is a complex number.

### Laplace transform of standard functions

1. unit step function

$$f(t) = u(t)$$

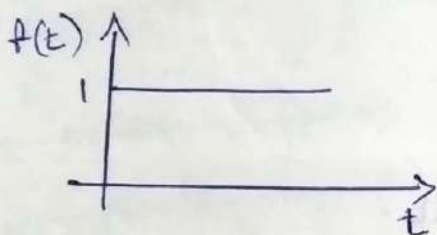

$$u(t) = 1 \text{ for } t \geq 0 \\ = 0 \text{ for } t < 0$$

$$\begin{aligned} \mathcal{L}[u(t)] &= \int_0^{\infty} 1 \cdot e^{-st} dt = \left[ \frac{e^{-st}}{-s} \right]_0^{\infty} = -\frac{1}{s} \left[ e^{-st} \right]_0^{\infty} \\ &= -\frac{1}{s} \left[ e^{-\infty} - e^{-0} \right] = -\frac{1}{s} [0 - 1] \\ &= \frac{1}{s} \end{aligned}$$

$$\boxed{\mathcal{L}[u(t)] = \frac{1}{s}}$$

2.  $f(t) = e^{at}$  where  $a$  is constant.

$$\begin{aligned} \mathcal{L}[e^{at}] &= \int_0^{\infty} e^{at} e^{-st} dt = \int_0^{\infty} e^{-(s-a)t} dt = \left[ \frac{-1}{(s-a)} e^{-(s-a)t} \right]_0^{\infty} \\ &= \frac{-1}{s-a} \left[ e^{-\infty} - e^{-0} \right] = \frac{-1}{s-a} [0 - 1] = \frac{1}{s-a} \end{aligned}$$

$$\boxed{\mathcal{L}[e^{at}] = \frac{1}{s-a}}$$

384.  $f(t) = \sin \omega t$  and  $f(t) = \cos \omega t$

$$\mathcal{L}[e^{i\omega t}] = \mathcal{L}[\cos \omega t + j \sin \omega t]$$

$$= \frac{1}{s - j\omega} \times \frac{s + j\omega}{s + j\omega}$$

$$= \frac{s}{s^2 + \omega^2} + j \frac{\omega}{s^2 + \omega^2}$$

$$\left. \begin{aligned} e^{at} &= \frac{1}{s-a} \\ j\omega t &= \frac{1}{s-j\omega} \end{aligned} \right\}$$

$$\mathcal{L}[\sin \omega t] = \frac{\omega}{s^2 + \omega^2}$$

$$\mathcal{L}[\cos \omega t] = \frac{s}{s^2 + \omega^2}$$

5.  $f(t) = t^n$

$$\mathcal{L}[t^n] = \int_0^{\infty} t^n e^{-st} dt$$

$$= \left[ t^n \frac{e^{-st}}{-s} \right]_0^{\infty} - \int_0^{\infty} \left( \frac{e^{-st}}{-s} \right) n \cdot t^{n-1} dt$$

$$= t^n (0 - 0) + \frac{n}{s} \int_0^{\infty} t^{n-1} e^{-st} dt$$

$$= \frac{n}{s} \mathcal{L}[t^{n-1}]$$

$$= \frac{n}{s} \frac{(n-1)}{s} \mathcal{L}[t^{n-2}]$$

$$= \frac{n}{s} \frac{(n-1)}{s} \frac{(n-2)}{s} \dots \frac{2}{s} \frac{1}{s} \mathcal{L}[t^{n-n}]$$

$$= \frac{n}{s} \frac{(n-1)}{s} \frac{(n-2)}{s} \dots \frac{2}{s} \frac{1}{s} \frac{1}{s}$$

$$\mathcal{L}[t^n] = \frac{n!}{s^{n+1}}$$

(2)

$$\mathcal{L}[t^{(n-1)}] = \frac{(n-1)!}{s^{(n-1)+1}} = \frac{(n-1)!}{s^n}$$

$$\mathcal{L}[t^3] = \frac{3!}{s^4}$$

$$\mathcal{L}[t^2] = \frac{2!}{s^3}$$

$t^n f(t)$

$$\mathcal{L}[f(t)] = F(s) = \int_0^{\infty} f(t) e^{-st} dt$$

$$\mathcal{L}[f'(t)] = F'(s) = \int_0^{\infty} (-t) f(t) e^{-st} dt = \mathcal{L}[-t f(t)]$$

$$\mathcal{L}[f''(t)] = F''(s) = \int_0^{\infty} t^2 f(t) e^{-st} dt = \mathcal{L}[t^2 f(t)]$$

$$\mathcal{L}[f^{(n)}(t)] = F^{(n)}(s) (-1)^n = \int_0^{\infty} t^n f(t) e^{-st} dt$$

$$\boxed{\therefore \mathcal{L}[t^n f(t)] = (-1)^n F^{(n)}(s)}$$

$$7) f(t) = \sinh \omega t$$

$$\mathcal{L}[\sinh \omega t] = \mathcal{L}\left[\frac{e^{\omega t} - e^{-\omega t}}{2}\right]$$

$$= \frac{1}{2} \left[ \frac{1}{s-\omega} - \frac{1}{s+\omega} \right] = \frac{1}{2} \left[ \frac{s+\omega - s+\omega}{s^2 - \omega^2} \right] = \frac{1}{2} \left[ \frac{2\omega}{s^2 - \omega^2} \right]$$

$$\boxed{\mathcal{L}[\sinh \omega t] = \frac{\omega}{s^2 - \omega^2}}$$

$$8) f(t) = \cosh \omega t$$

$$\mathcal{L}[\cosh \omega t] = \mathcal{L}\left[\frac{e^{\omega t} + e^{-\omega t}}{2}\right] =$$

$$= \frac{1}{2} \left[ \frac{1}{s-\omega} + \frac{1}{s+\omega} \right] = \frac{1}{2} \left[ \frac{2s}{s^2 + \omega^2} \right]$$

$$\boxed{\mathcal{L}[\cosh \omega t] = \frac{s}{s^2 + \omega^2}}$$

9] Laplace transform of derivatives

$$\mathcal{L}[f'(t)] = \int_0^{\infty} f'(t) e^{-st} dt = \left[ e^{-st} f(t) \right]_0^{\infty} - \int_0^{\infty} f(t) e^{-st} (-s) dt$$

$$= -f(\infty) + s \int_0^{\infty} f(t) e^{-st} dt$$

$$= sF(s) - f(0^-)$$

In general

$$\mathcal{L}[f^n(t)] = s^n F(s) - s^{n-1} f(0^-) - s^{n-2} f'(0^-) - \dots - f^{(n-1)}(0^-)$$

### Laplace transform of integrals

$$\mathcal{L} \left[ \int_0^t f(t) dt \right] = \int_0^\infty \left[ \int_0^t f(t) dt \right] e^{-st} dt$$

$$= \left[ -\frac{e^{-st}}{s} \int_0^t f(t) dt \right]_0^\infty + \int_0^\infty \frac{f(t) e^{-st}}{s} dt$$

(1st term x derivative of 2nd term)

$$= 0 + \frac{F(s)}{s}$$

If the integral has the limits  $-\infty$  to  $t$  instead of  $0$  to  $t$ , then

$$\int_{-\infty}^t f(t) dt = \int_{-\infty}^{0^-} f(t) dt + \int_{0^-}^t f(t) dt$$

The first term on the right hand is const. and can be represented as  $f(-\infty)$  or  $f(0^-)$

$$\mathcal{L} \left[ \int_{-\infty}^t f(t) dt \right] = \mathcal{L} \left[ f(0^-) + \int_{0^-}^t f(t) dt \right] = \frac{f(0^-)}{s} + \frac{F(s)}{s}$$

If  $f(t)$  is a current, then  $f(0^-)$  represents the initial charge  $q(0^-)$ . If  $f(t)$  is a voltage, then  $f(0^-)$  represents flux linkages  $\psi(0^-) = Li(0^-)$ .

$$f(0^-) \Rightarrow \begin{matrix} i(t) & \rightarrow & \text{initial charge } q(0^-) \\ v(t) & \rightarrow & \text{flux linkage } \psi(0^-) = Li(0^-) \end{matrix}$$



11. property of linearity:

$F(s) \rightarrow f(t)$  then

$$\mathcal{L}[k f(t)] = k \mathcal{L}[f(t)] = k F(s) \text{ where}$$

12. property of Superposition

If  $F_1(s), F_2(s), \dots, F_n(s)$  are the Laplace transform of  $f_1(t), f_2(t), \dots, f_n(t)$  then

$$\mathcal{L}[f_1(t) + f_2(t) + \dots + f_n(t)] = F_1(s) + F_2(s) + \dots + F_n(s)$$

Inverse Laplace transform

$$f(t) = \mathcal{L}^{-1}[F(s)]$$

$$f(t) = \frac{1}{2\pi j} \int_{\sigma_1 - j\infty}^{\sigma_1 + j\infty} F(s) e^{st} dt$$

}  $\rightarrow$  Not used

Complex inverse integral

If  $F(s)$  is not in standard form for which  $f(t)$  can be readily found, it must be converted into the std form and then its inverse is found.

The uniqueness property of Laplace transformation i.e. no two different functions have the same Laplace transformation, helps to find  $f(t)$  for given  $F(s)$ .

procedure for to use Laplace transformation

- 1. The integro differential equations are written for given n/w.
- 2. on applying LT, the transformed eqns are written, inserting the initial conditions to them.
- 3. The transformed eqns are manipulated algebraically, such that they are in std form for which inverse LT can be found.
- 4. The inverse LT of these eqns give required soln.

First shifting theorem:

If  $F(s)$  is LT of  $f(t)$  then

$$\mathcal{L}[e^{-at} f(t)] = F(s+a)$$

ex:  $\mathcal{L}[\sin \omega t] = \frac{\omega}{s^2 + \omega^2}$ ,  $\mathcal{L}[e^{-at} \sin \omega t] = \frac{\omega}{(s+a)^2 + \omega^2}$

Second shifting theorem:

If  $\mathcal{L}[f(t)] = F(s)$  then  $\mathcal{L}[f(t-a) u(t-a)] = e^{-as} F(s)$  → shifted.

ex:  $\mathcal{L}[t u(t)] = \frac{1}{s^2}$   $\therefore \mathcal{L}[(t-a) u(t-a)] = e^{-as} \frac{1}{s^2}$

Convolution theorem:

If  $F_1(s)$  and  $F_2(s)$  are Laplace transforms of  $f_1(t)$  and  $f_2(t)$  respectively then

$$\begin{aligned} \mathcal{L}\left[\int_0^t f_1(\tau) f_2(t-\tau) d\tau\right] &= \mathcal{L}\left[\int_0^t f_1(t-\tau) f_2(\tau) d\tau\right] \\ &= \mathcal{L}\left[f_1(t) * f_2(t)\right] = F_1(s) F_2(s) \end{aligned}$$

i.e. LT of convolution of 2 fun = product of 2 functions

### Initial value theorem:

This theorem helps us to find the initial value of function  $f(t)$  directly from the transformed function  $F(s)$ .

Statement: If  $f(t)$  and  $f'(t)$  are Laplace transform then the behaviour of  $f(t)$  in the neighbourhood  $t=0^-$  corresponds to the behaviour of  $SF(s)$  in the neighbourhood of  $S=\infty$ .

$$i.e. \lim_{t \rightarrow 0^-} f(t) = \lim_{S \rightarrow \infty} SF(s)$$

### Final value theorem:

This theorem helps us to find the final value function  $f(t)$  directly from transformed function.

$$i.e. \lim_{t \rightarrow \infty} f(t) = \lim_{S \rightarrow 0} SF(s)$$

Laplace transform of periodic functions :-

$f(t)$  be a periodic function with  $T$  as period.

Let  $f_1(t), f_2(t), f_3(t) \dots$  represent the first, second, third, ... etc cycles of the periodic wave. Then

$$\begin{aligned}
 f(t) &= f_1(t) + f_2(t) + f_3(t) + \dots \\
 &= f_1(t) + f_1(t-T)u(t-T) + f_1(t-2T)u(t-2T) \\
 &\quad + f_1(t-3T)u(t-3T) + \dots
 \end{aligned}$$

Then  $F(s) = F_1(s) + e^{-sT} F_1(s) + e^{-2sT} F_1(s) + e^{-3sT} F_1(s) + \dots$

$$= F_1(s) [ 1 + e^{-sT} + e^{-2sT} + e^{-3sT} + \dots ]$$

$$= F_1(s) [ 1 - e^{-sT} ]^{-1}$$


$$F(s) = \frac{F_1(s)}{1 - e^{-sT}}$$

Transformed N/w's :

For solving electrical N/w's using LT, it is necessary for us to know the transformed equivalents of all the elements present in the N/w, considering initial values on them.

The elements  $\rightarrow R, L, C$ .

1) Resistance :

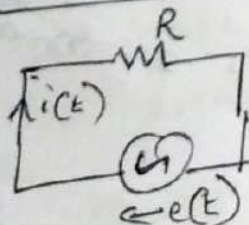


$$i(t) = \frac{e(t)}{R}$$


$$\text{or } I(s) = \frac{E(s)}{R}$$

then transformed n/w is

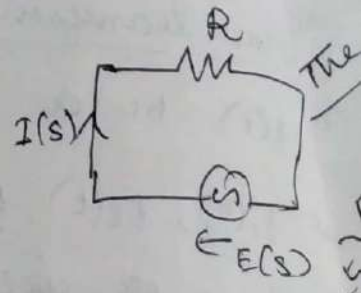we can observe that, Resistance remains unchanged in the transformed n/w.



2) The inductance:

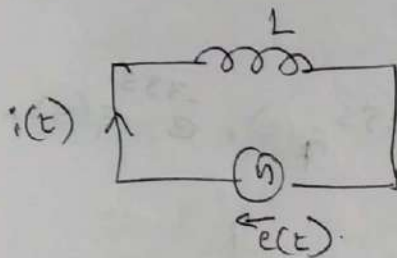


$$e(t) = L \frac{di}{dt}$$

$$E(s) = L [sI(s) - i(0^-)]$$

$$E(s) - LsI(s) + Li(0^-) = 0$$

$$I(s) = \frac{E(s) + Li(0^-)}{Ls} \quad \text{--- (1)}$$

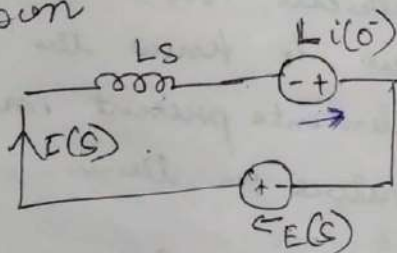
The transformed ckt satisfying eqn 1 is ~~shown~~ shown



eqn (1) can be written as


$$I(s) = \frac{E(s)}{Ls} + \frac{i(0^-)}{s} \quad \text{--- (2)}$$

The transformed ckt for eqn 2 may be

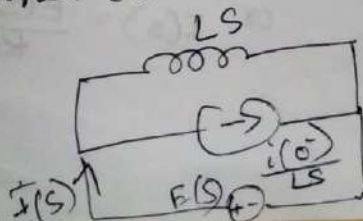

The capacitance:
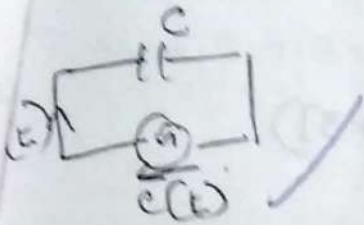
$$C = \frac{q}{V} = q \cdot CV \quad (7)$$



$$i(t) = C \frac{d v(t)}{dt}$$

$$I(s) = C [sE(s) - v_c(0^-)]$$


$$= CsE(s) - Cv_c(0^-)$$

$$I(s) = \frac{E(s)}{1/Cs} - Cv_c(0^-) \quad (1)$$

$$E(s)Cs = I(s) + Cv_c(0^-) \quad I(s) = \frac{1}{Cs} I(s) - Cv_c(0^-)$$

initial \$V\_q\$ on the capacitor.

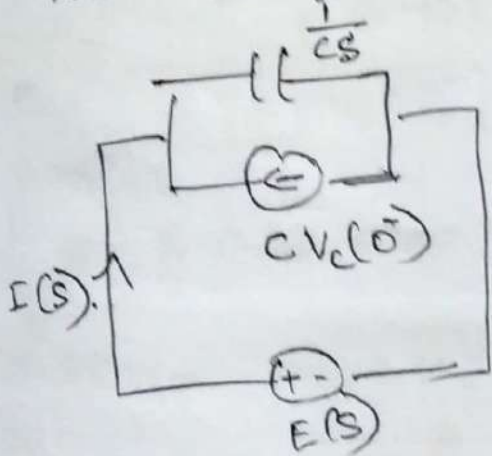The transformed circuit satisfying eqn (1) is




eqn (1) can also be written

$$E(s) = \frac{I(s)}{Cs} + \frac{v_c(0^-)}{s}$$


$$I(s) + Cv_c(0^-) = \frac{E(s)}{1/Cs}$$

$$\frac{I(s)}{Cs} + \frac{v_c(0^-)}{s}$$

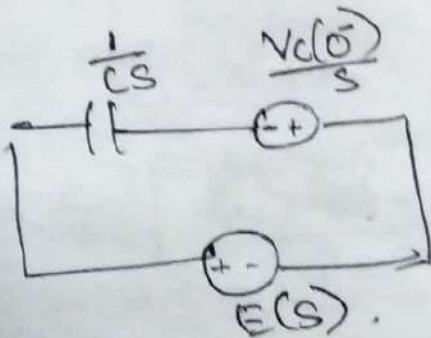
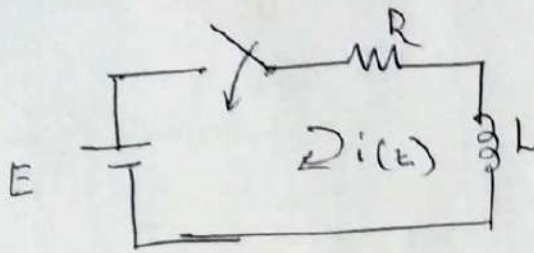
# Laplace transformation.

For the ckt shown, find an expression for  $i(t)$ , when the switch  $k$  is closed at  $t=0$ .



When  $k$  is closed at  $t=0$ .

$$L \frac{di}{dt} + Ri = E$$

$$L [sI(s) - i(0^-)] + RI(s) = \frac{E}{s}$$

$$i(0^-) = i(0^+) = 0$$

$$I(s) [LS + R] = \frac{E}{s}$$

$$I(s) = \frac{E}{s(LS + R)} = \frac{E}{sL(s + \frac{R}{L})}$$

$$= \frac{E}{L} \cdot \frac{1}{s(s + \frac{R}{L})}$$

$$= \frac{E}{R} \cdot \frac{1}{s \cdot \frac{R}{L}}$$

$$= \frac{E}{L} \left[ \frac{A}{s} + \frac{B}{s + \frac{R}{L}} \right]$$

$$= \frac{E}{L} \left[ \frac{L/R}{s} - \frac{L/R}{s + R/L} \right]$$

$$= \frac{E}{L} \left[ \frac{L}{R} - \frac{L}{R} e^{-\frac{R}{L}t} \right]$$


$$i(t) = \frac{E}{R} \left[ 1 - e^{-\frac{R}{L}t} \right]$$

$$\frac{A}{s} + \frac{B}{s + R/L}$$

$$A = \left( \frac{1}{s + R/L} \right)_{s=0} \quad A \Rightarrow L/R$$

$$B = \left( \frac{1}{s} \right)_{s=-R/L} \quad B \Rightarrow -$$

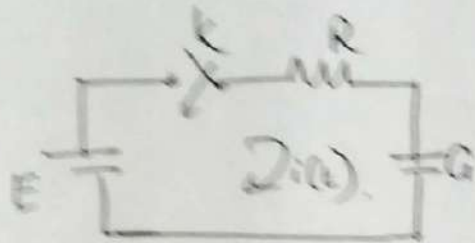2) For the circuit shown, find an expression for  $i(t)$ , when the switch  $K$  is closed at  $t=0$ . Assume that there is no initial charge on the capacitor.



when switch  $K$  is closed at  $t=0$ .

$$Ri + \frac{1}{C} \int i dt = E$$

on taking LT

$$R I(s) + \left[ \frac{I(s)}{Cs} - \frac{0}{s} \right] = \frac{E}{s}$$

$$I(s) \left[ R + \frac{1}{Cs} \right] = \frac{E}{s}$$

$$I(s) = \frac{E}{s \left( R + \frac{1}{Cs} \right)} = \left( \frac{E}{sR + \frac{1}{C}} \right)$$

$$= \frac{E}{R \left( s + \frac{1}{CR} \right)} = \frac{E}{R} \left( \frac{1}{s + \frac{1}{CR}} \right)$$

$$= \frac{E}{R} \left( \frac{1}{s + \frac{1}{CR}} \right)$$

$$i(t) = \frac{E}{R} e^{-t/RC}$$


$$C = \frac{Q}{V}$$

$$Q = CV$$



3

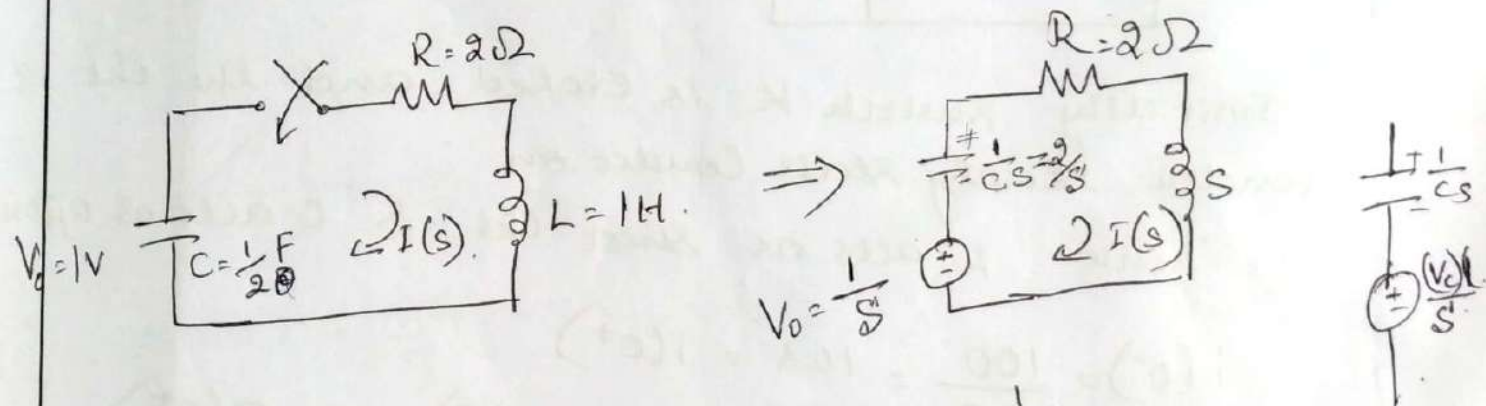3) In the ckt shown in fig, if the capacitor is initially charged to 1V, find an expression for  $i(t)$  when the switch K is closed at  $t=0$ .



$$R I(s) + S I(s) + \frac{2}{s} I(s) = \frac{1}{s}$$

$$I(s) \left( R + S + \frac{2}{s} \right) = \frac{1}{s}$$

$$I(s) \frac{sR + s^2 + 2}{s} = \frac{1}{s}$$


$$I(s) = \frac{1}{s^2 + sR + 2}$$

$$R = 2 \Omega$$

$$I(s) = \frac{1}{s^2 + 2s + 2} = \frac{1}{(s+1)^2 + 1}$$

$$i(t) = e^{-t} \sin t$$

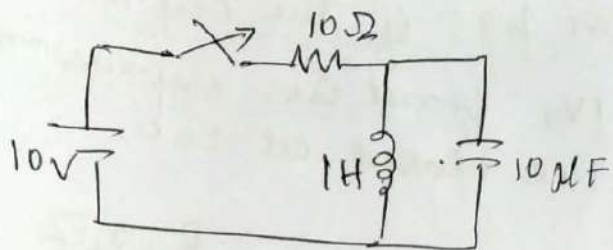In the ckt shown, the switch K is closed and the steady state is reached. At  $t=0$ , the switch is opened. Find the expression for the current in the inductor using Laplace transform.



Initially switch  $k$  is closed and the ckt is under steady state condition.

∴ hence  $L$  acts as short ckt &  $C$  acts as open ckt

$$i(0^-) = \frac{100}{10} = 10A = i(0^+)$$

$$V_c(0^-) = 0 = V_c(0^+) \quad \therefore q(0^-) = 0 = q(0^+)$$

when  $k$  is opened.

$$L \frac{di}{dt} + \frac{1}{C} \int i dt = 0.$$

$$L [s I(s) - i(0^-)] + \frac{1}{Cs} \left[ \frac{I(s)}{s} + \frac{V_c(0^-)}{s} \right] = 0$$

$$Ls I(s) - Li(0^-) + \frac{I(s)}{Cs} = 0.$$

$$Ls I(s) - 10L + \frac{I(s)}{10\mu F s} = 0.$$

$$I(s) \left[ s - 10 + \frac{10^5}{s} \right] = 10$$

$$sI(s) + \frac{I(s)}{10^{-5} s} = 10$$

$$I(s) \left[ s + \frac{10^5}{s} \right] = 10.$$


$$I(s) \left[ \frac{s^2 + 10^5}{s} \right] = 10.$$

$$I(s) = \frac{10s}{s^2 + 10^5} = \frac{10s}{s^2 + (10^{\frac{5}{2}})^2}$$


$$I(t) = 10 \cos 10^{\frac{5}{2}} t$$

out pages

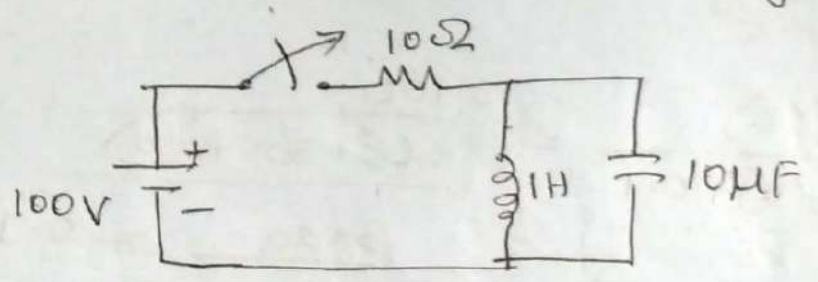In the n/w shown, switch k is closed and steady state is reached. At  $t=0$ , the switch is opened, Find the expression for the current in the inductor using Laplace transform.



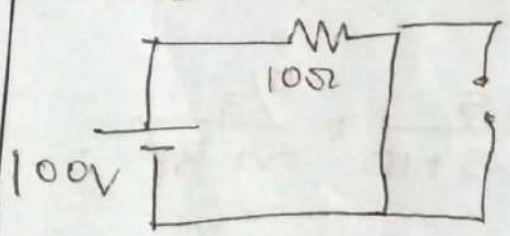when k is closed, the ckt is under steady state condition.  $L$  acts as SC &  $C \rightarrow O.C$ .  
 $t = 0^-$




$$i(0^-) = i(0^+) = \frac{100}{10} = 10A.$$

$$V_L(0^-) = 0 = V_C(0^+)$$

$$q(0^-) = 0 = q(0^+)$$

when k is opened

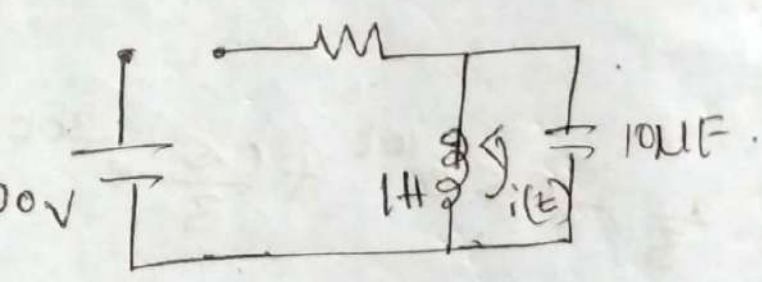

$$L \frac{di}{dt} + \frac{1}{C} \int i dt = 0.$$

Taking L.T

$$L [s I(s) - i(0^-)] + \frac{1}{C} \left[ \frac{I(s)}{s} - \frac{q(0^-)}{s} \right] = 0.$$

$$1 [s I(s) - 10] + \frac{1}{10 \times 10^{-6}} \left[ \frac{I(s)}{s} \right] = 0.$$

$$I(s) \left[ s + \frac{10^5}{s} \right] = 10.$$

$$I(s) = \frac{10}{s + \frac{10^5}{8}} = \frac{10s}{s^2 + 10^5}$$


25

(17)

$$= \frac{10s}{s^2 + (10^{5/2})^2}$$

$$i(t) = 10 \cos 10^{5/2} t$$

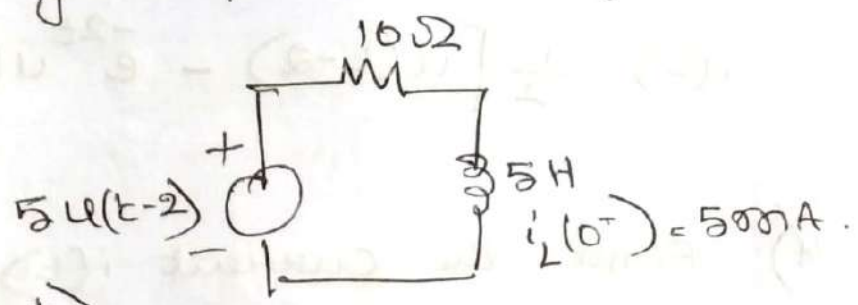Determine the response current  $i(t)$  in the ckt shown using Laplace transform



$$i_L(0^-) = 500\text{mA} = i_L(0^+)$$

$$10 I(s) + 4 [s I(s) - i(0^+)] = \frac{5e^{-2s}}{s}$$

$$10 I(s) + 5 (s I(s)) - 5 \times 5 = \frac{5e^{-2s}}{s}$$

$$I(s) [10 + 5s] - 25 = \frac{5e^{-2s}}{s}$$

$$I(s) = \frac{5e^{-2s}}{s} + 25 \times 10^{-3}$$

$$= \frac{5e^{-2s} + (25 \times 10^{-3})s}{10 + 5s}$$

$$= \frac{5e^{-2s} + 5 \times 10^{-3}s}{5(2 + s)}$$

$$= \frac{e^{-2s} + 5 \times 10^{-3}s}{s(s+2)}$$

$$= \frac{e^{-2s}}{s(s+2)} + \frac{5 \times 10^{-3}}{(s+2)}$$

$$= e^{-2s} \left[ \frac{A}{s} + \frac{B}{s+2} \right] + \frac{5 \times 10^{-3}}{s+2}$$

$$= e^{-2s} \left[ \frac{1/2}{s} - \frac{1/2}{s+2} \right] + \frac{5 \times 10^{-3}}{s+2}$$


$$A = \frac{1}{s+2} \Big|_{s=0} = \frac{1}{2}$$

$$B = \frac{1}{s} \Big|_{s=-2} = -\frac{1}{2}$$

$$= \frac{1}{2} e^{-2s} \left[ \frac{1}{s} - \frac{1}{s+2} \right] + \frac{5 \times 10^{-3}}{s+2}$$

$$i(t) = \frac{1}{2} \left[ u(t-2) - e^{-2t} u(t-2) \right] + 5 \times 10^{-3} e^{-2t} u(t)$$

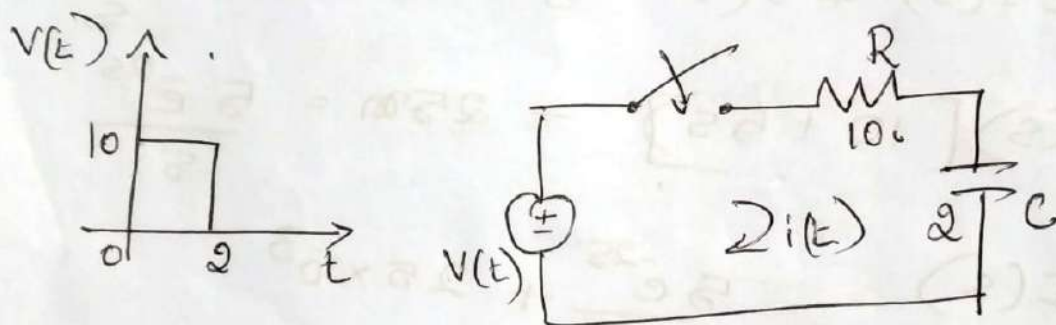4) Find the current  $i(t)$  assuming zero initial conditions, when switch  $k$  is closed at  $t=0$ . The excitation  $V(t)$  is pulse magnitude 10V and duration of 2sec. Consider  $R=10\Omega$   $C=2F$ .



$$V(t) = 10u(t) - 10u(t-2) = 10[u(t) - u(t-2)]$$

$$\left[ R I(s) + \frac{1}{C} \left[ \frac{I(s)}{s} + \frac{V_C(0^-)}{s} \right] \right] = V(s)$$

$$\left[ 10 I(s) + \frac{1}{2} \frac{I(s)}{s} \right] = 10 \left[ \frac{1}{s} - \frac{e^{-2s}}{s} \right]$$

$$I(s) \left[ 10 + \frac{1}{2s} \right] = 10 \left[ \frac{1}{s} - \frac{e^{-2s}}{s} \right]$$


$$I(s) \left[ \frac{20s+1}{2s} \right] = 10 \left( \frac{1-e^{-2s}}{s} \right)$$

$$I(s) = \frac{20(1-e^{-2s})}{1+20s}$$



$$= \frac{20(1 - e^{-2s})}{20(s + \frac{1}{20})} = \frac{1}{s + \frac{1}{20}} - \frac{e^{-2s}}{s + \frac{1}{20}}$$

$$i(t) = e^{-\frac{1}{20}t} u(t) - e^{-\frac{1}{20}(t-2)} u(t-2)$$

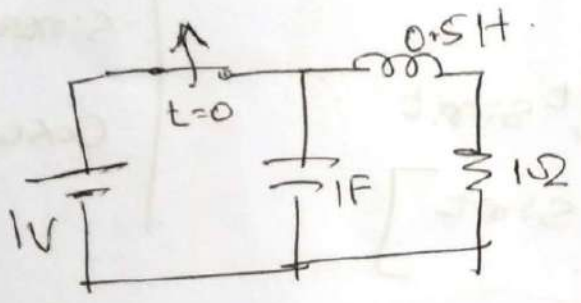5) The n/w shown in fig was in steady state before  $t=0^+$ . The switch is opened at  $t=0$ . Find  $i(t)$  for  $t>0$  using L.T.



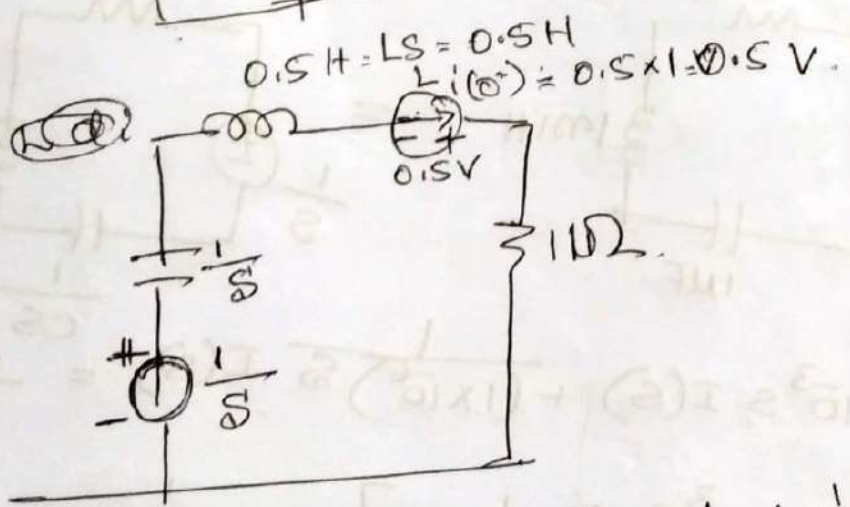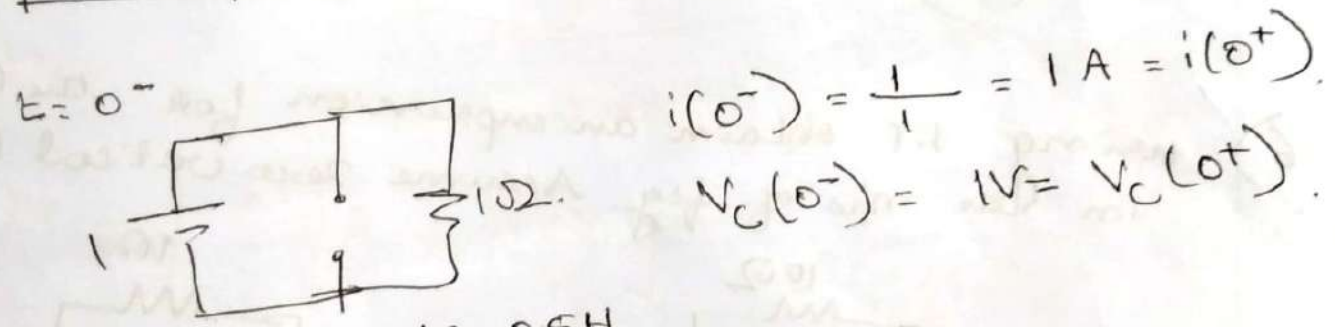steady  $C \rightarrow O.C$   
 $L \rightarrow S.C$



$$0.5 I(s) - 0.5 + I(s) - \frac{1}{s} + \frac{1}{s} I(s) = 0$$

$$I(s) \left[ 0.5 + 1 + \frac{1}{s} \right] = \frac{1}{s} + 0.5$$

$$I(s) = \frac{\frac{1}{s} + \frac{1}{2}}{1 + \frac{1}{s} + \frac{1}{2}s} = \frac{\frac{s+2}{2s}}{\frac{2s+2+s^2}{2s}}$$

30

$$= \frac{s+2}{s^2+2s+2}$$

$$= \frac{(s+1)+1}{(s+1)^2+1}$$

$$= \frac{s+1}{(s+1)^2+1} + \frac{1}{(s+1)^2+1}$$



$$i(t) = e^{-t} \cos t + e^{-t} \sin t$$

$$i(t) = e^{-t} [\cos t + \sin t]$$

$$\text{S: } \frac{\omega}{s^2 + \omega^2}$$

$$\text{CoS } \omega t = \frac{s}{s^2 + \omega^2}$$

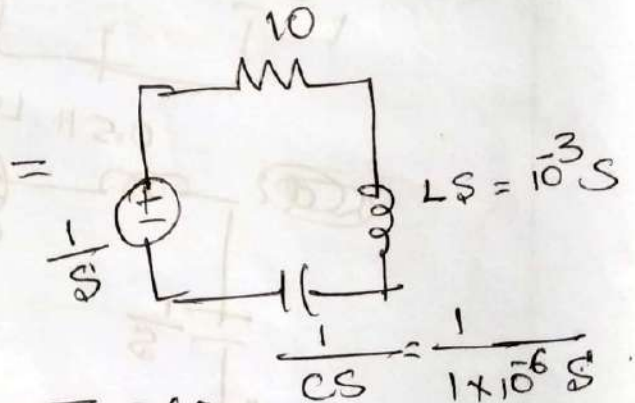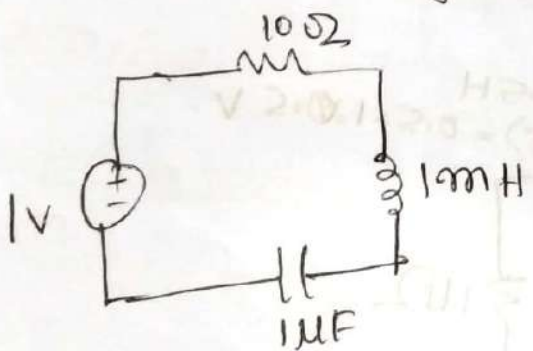6) using LT obtain an expression for the current  $i(t)$  in the n/w of fig. Assume zero critical conditions



$$10 I(s) + 10^3 s I(s) + \frac{1}{(1 \times 10^{-6}) s} I(s) = \frac{1}{s}$$

$$I(s) \left[ 10 + 10^3 s + \frac{1}{10^{-6} s} \right] = \frac{1}{s}$$

$$I(s) \left[ \frac{10^{-5} s + 10^9 s^2 + 1}{10^{-6} s} \right] = \frac{1}{s}$$



$$I(s) \left[ \frac{10^6 (10^3 s + 10^9 s^2 + 1)}{s} = \frac{1}{s} \right]$$

$$= I(s) \left[ 10s + 10^3 s^2 + 10^6 \right] = 1$$

$$I(s) = \frac{1}{10s + 10^3 s^2 + 10^6} \times \frac{10^3}{10^3}$$

$$= \frac{10^3}{s^2 + 10^4 s + 10^9}$$

$$= \frac{1000}{s^2 + 10,000s + 10^9}$$

$$= \frac{1000}{(s+5000)^2 + 31225^2} \times \frac{(31225)}{(31225)}$$


$10^9 s^2$   
 $5000s \quad 5000s = 10,000$

$$= 0.032 \times \frac{31225}{(s+5000)^2 + 31225^2}$$

$10^9 - (5000)^2 = 31225^2$

$$i(t) = 0.032 e^{-5000t} \sin 31225t$$

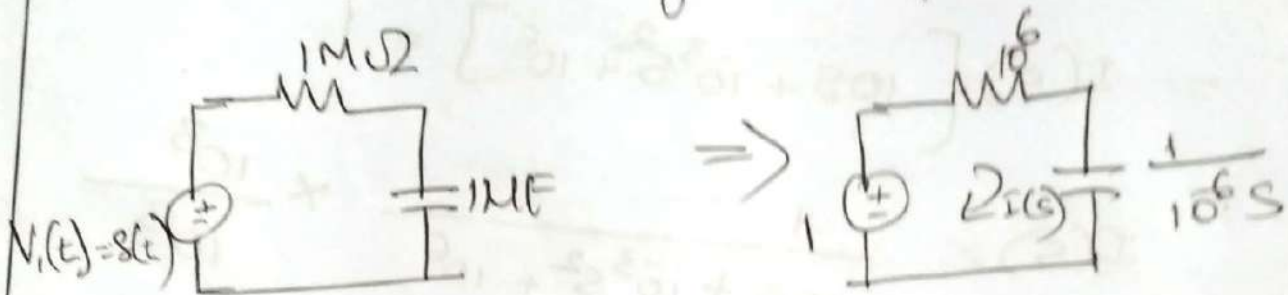7) For an critically damped n/w of shown. Obtain expression for the current  $i(t)$  use Laplace transform. Given  $V_i(t) = 8t$



$$\left[ 10^6 + \frac{1}{10^{-6} S} \right] I(s) = 1$$

$$\left[ \frac{S + 1}{10^6 S} \right] I(s) = 1$$

$$I(s) = 10^6 \left( \frac{S}{S+1} \right)$$

$$= 10^6 \left[ \frac{S+1-1}{S+1} \right]$$


$$= 10^6 \left[ 1 - \frac{1}{S+1} \right]$$

impulse =  $8(t)$


$$i(t) = 10^6 [ 8(t) - e^{-t} ]$$

①

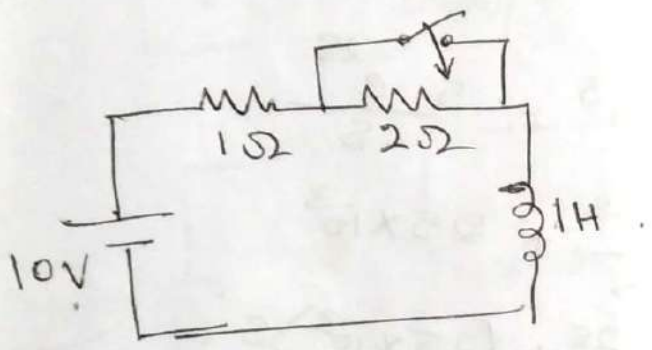The battery  $V_g$  10V is applied for a steady state period with switch  $k$  open. Obtain the complete expression for the current  $i$  after closing the switch  $k$ . Use L.T.




$t = 0^-$

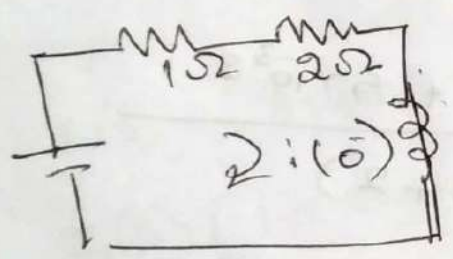

$L \rightarrow \infty C$

$i(0^-) = \frac{10A}{3} = i(0^+)$

$t = 0^+$

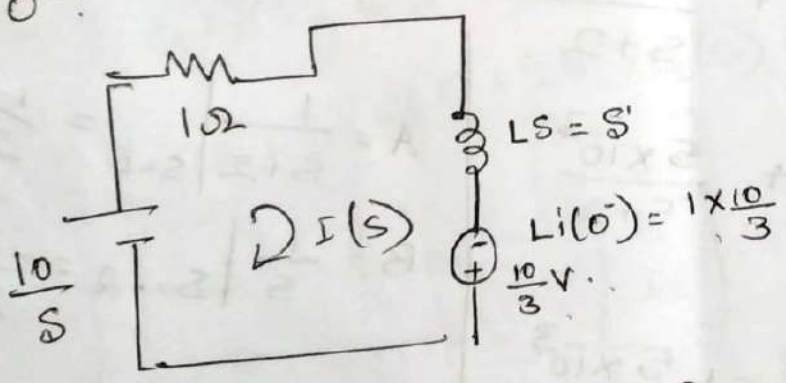

$$\frac{10}{s(s+1)} = \frac{A}{s} + \frac{B}{s+1}$$

$$A = \frac{10}{s+1} \Big|_{s=0} = 10$$

$$B = \frac{10}{s} \Big|_{s=-1} = -10$$

$I(s) + s I(s) - \frac{10}{3} = \frac{10}{s}$



$I(s)[1+s] = \frac{10}{s} + \frac{10}{3} = \frac{30+10s}{3s}$

$I(s) = \frac{30+10s}{3s(s+1)} = \frac{30}{3s(s+1)} + \frac{10s}{3s(s+1)}$

$= \frac{10}{s(s+1)} + \frac{10/3}{s+1}$

$\frac{10}{s} + \frac{10}{s+1} + \frac{10/3}{s+1} \Rightarrow 10u(t) - 10e^{-t}u(t)$

a) solve for  $i_L(t)$  using L.T.

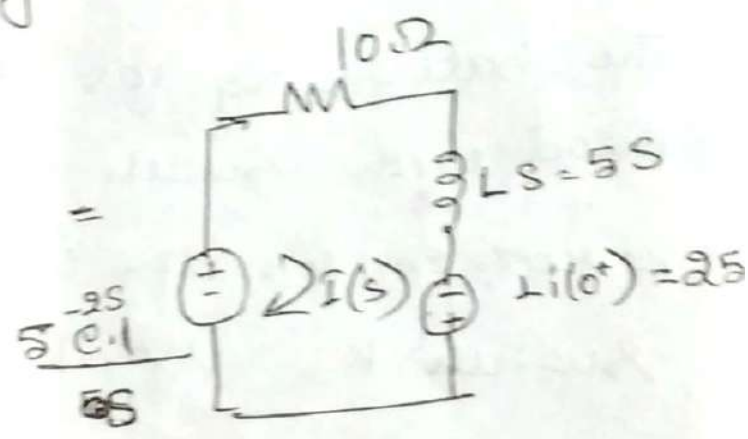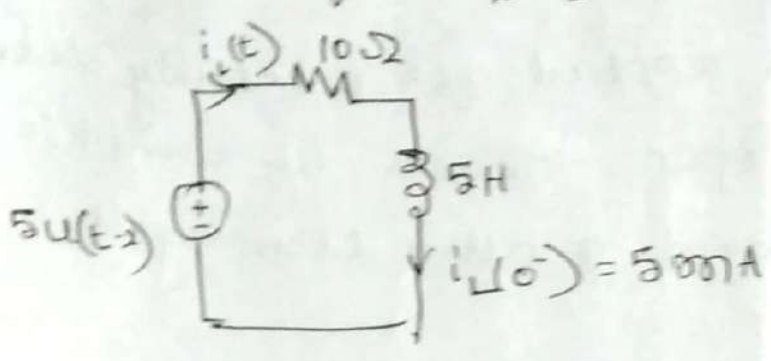

$$10 I(s) + 5s I(s) - 25 \times 10^{-3} = \frac{5 e^{-2s}}{s}$$

$$I(s) [10 + 5s] = \frac{5 e^{-2s}}{s} + 25 \times 10^{-3}$$

$$= \frac{5 e^{-2s} + (25 \times 10^{-3})s}{s(10 + 5s)}$$

$$= \frac{5 e^{-2s} + 5 \times 10^{-3} s}{s(s+2)}$$

$$= \frac{e^{-2s}}{s(s+2)} + \frac{5 \times 10^{-3}}{s+2}$$

$$= e^{-2s} \left[ \frac{A}{s} + \frac{B}{s+2} \right] + \frac{5 \times 10^{-3}}{s+2}$$



$$A = \frac{1}{s+2} \Big|_{s=0} = \frac{1}{2}$$

$$B = \frac{1}{s} \Big|_{s=-2} = -\frac{1}{2}$$

$$I(s) = e^{-2s} \left[ \frac{1/2}{s} - \frac{1/2}{s+2} \right] + \frac{5 \times 10^{-3}}{s+2}$$

$$i_L(t) = \frac{1}{2} [u(t-2) - e^{-(t-2)} u(t-2)] + 5 \times 10^{-3} e^{-2t} u(t)$$

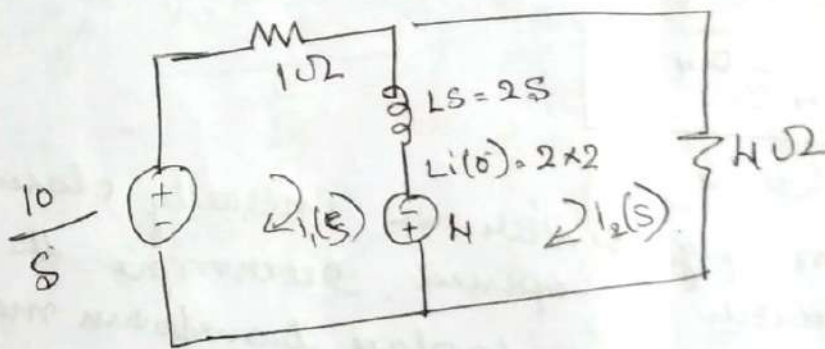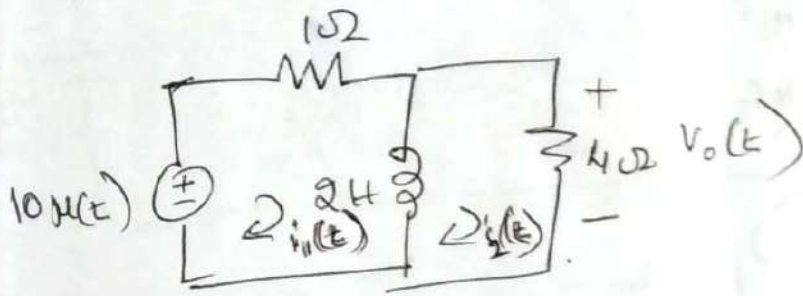For the ckt shown in fig, the switch is closed at  $t=0$ , The initial current through the inductance is 2A. Obtain the expression for  $V_o(t)$  for  $t>0$ .



$$10/s + 2s(I_1(s) - I_2(s)) - 4 = 10/s$$

$$I_1(s) [1 + 2s] - 2s I_2(s) = 10/s + 4 = \frac{10 + 4s}{s} \quad (1)$$

$$4I_2(s) + 4 + 2s(I_2(s) - I_1(s)) = 0$$

$$-2s I_1(s) + (4 + 2s) I_2(s) = -4 \quad (2)$$

$$\begin{bmatrix} 1 + 2s & -2s \\ -2s & 4 + 2s \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{10 + 4s}{s} \\ -4 \end{bmatrix}$$

$$\Delta = (1 + 2s)(4 + 2s) - 4s^2$$

$$= 4 + 8s + 2s + 4s^2 - 4s^2 = 4 + 10s$$

$$I_2 = \frac{\begin{bmatrix} 1 + 2s & \frac{10 + 4s}{s} \\ -2s & -4 \end{bmatrix}}{\Delta} = \frac{(1 + 2s)(-4) + 2s \frac{(10 + 4s)}{s}}{\Delta}$$

$$= \frac{-4 - 8s + 20 + 8s}{\Delta} = \frac{16}{\Delta}$$

$$\bar{I}_2 = \frac{16}{\Delta} = \frac{16}{4 + 10s} = \frac{16}{10(s + \frac{4}{10})}$$

$$= \frac{1.6}{s + 0.4}$$


$$= 1.6 e^{-0.4t}$$

$$V_o(t) = 4 \times i_2(t)$$


$$= 4 \times 1.6 e^{-(0.4)t}$$

$$V_o(t) = 6.4 e^{-0.4t}$$

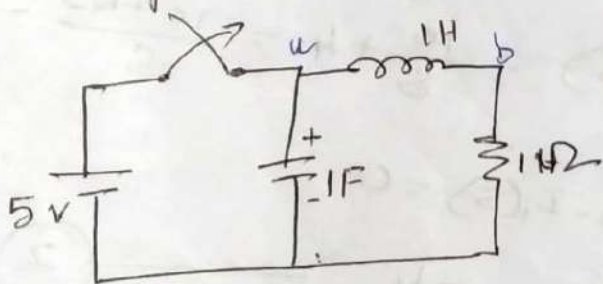4] In the ckt shown in fig switch is initially closed. After steady state, the switch is opened. Determine the nodal vgs  $V_a(t)$  and  $V_b(t)$  using Laplace transform method.




At  $t = 0^-$

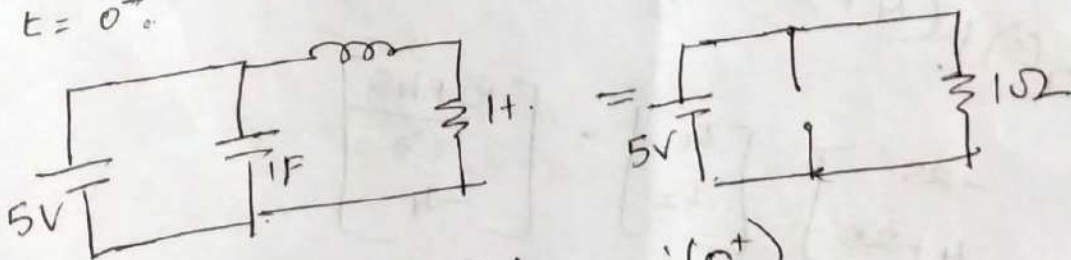

$$i(0^-) = \frac{5}{1} = 5 \text{ A} = i(0^+)$$

$$V_c(0^-) = 5 \text{ V} = V_c(0^+)$$

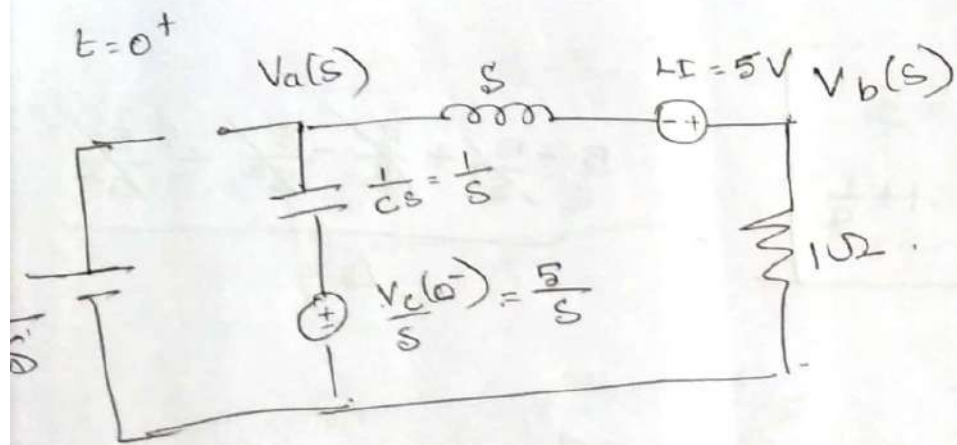

$$\frac{V_a(s)}{s} + \frac{V_a - \frac{5}{s}}{\frac{1}{s}} + \frac{V_a - V_b + 5}{s} = 0$$

$$s(V_a - \frac{5}{s}) + \frac{1}{s}(V_a - V_b) + \frac{5}{s} = 0 \quad \text{--- (1)}$$

$$(s + \frac{1}{s})V_a - \frac{1}{s}V_b = 5 - \frac{5}{s}$$

$$\frac{V_b}{1} + \frac{V_b - V_a - 5}{s} = 0 \quad \text{--- (2)}$$

$$-\frac{1}{s}V_a + (1 + \frac{1}{s})V_b = \frac{5}{s}$$

$$\begin{bmatrix} s + \frac{1}{s} & -\frac{1}{s} \\ -\frac{1}{s} & 1 + \frac{1}{s} \end{bmatrix} \begin{bmatrix} V_a(s) \\ V_b(s) \end{bmatrix} = \begin{bmatrix} 5 - \frac{5}{s} \\ \frac{5}{s} \end{bmatrix}$$

$$\Delta = (s + \frac{1}{s})(1 + \frac{1}{s}) - \frac{1}{s^2}$$

$$= \frac{(s^2 + 1)}{s} \left(\frac{s+1}{s}\right) - \frac{1}{s^2}$$

$$= \frac{s^3 + s + s^2 + 1}{s^2} - \frac{1}{s^2}$$

$$= s + \frac{1}{s} + 1 + \frac{1}{s^2} - \frac{1}{s^2} = \boxed{\frac{s^2 + s + 1}{s}}$$

$$V_a(s) = \frac{\begin{bmatrix} 5 - \frac{5}{s} & -\frac{1}{s} \\ \frac{5}{s} & 1 + \frac{1}{s} \end{bmatrix}}{\Delta} = \frac{5 - \frac{5}{s} + \frac{5}{s} - \frac{5}{s^2} + \frac{5}{s^2}}{\Delta}$$

$$= \frac{5}{\frac{s^2 + s + 1}{s}} = \frac{5s}{s^2 + s + 1}$$

$$= \frac{5s}{\left(s + \frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2} \quad \left| \begin{array}{l} s^2 + \frac{1}{4} + s + 1 - \frac{1}{4} \\ = (s+1)^2 + \left(\frac{3}{4}\right) \end{array} \right.$$

$$= 5 \frac{s + \frac{1}{2} - \frac{1}{2}}{\left(s + \frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2}$$

$$= 5 e^{-\frac{1}{2}t} \cos$$

$$= 5 \left[ \frac{\left(s + \frac{1}{2}\right) - \frac{\sqrt{3}}{2} \times \frac{1}{\sqrt{3}}}{\left(s + \frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2} \right]$$

$$\frac{s}{s^2 + a^2} = \cos at$$

$$\frac{a}{s^2 + a^2} = \sin at$$

$$= 5 e^{-\frac{1}{2}t} \cos \frac{\sqrt{3}}{2}t - e^{-\frac{1}{2}t} \cdot \frac{1}{\sqrt{3}} \sin \frac{\sqrt{3}}{2}t$$

~~$$= 5 \left[ e^{-\frac{1}{2}t} \cos \frac{\sqrt{3}}{2}t - \frac{1}{\sqrt{3}} \sin \frac{\sqrt{3}}{2}t \right]$$~~

$$V_a(t) = 5 e^{-\frac{1}{2}t} \left[ \cos \frac{\sqrt{3}}{2}t - \frac{1}{\sqrt{3}} \sin \frac{\sqrt{3}}{2}t \right]$$



$$V_b(s) = \left[ \frac{s + \frac{1}{s} \quad \sqrt{5} - \frac{\sqrt{5}}{s}}{\Delta} \right] = \frac{5 + \frac{5}{s^2} + \frac{1}{s} \left( \sqrt{5} - \frac{\sqrt{5}}{s} \right)}{\Delta}$$

$$= \frac{5 + \cancel{\frac{5}{s^2}} + \frac{\sqrt{5}}{s} - \cancel{\frac{\sqrt{5}}{s^2}}}{\Delta} = \frac{5s + \sqrt{5}}{\Delta}$$

$$= \frac{5s + \sqrt{5}}{s} = \frac{5(s+1)}{s^2 + s + 1}$$


$$= \frac{5(s+1)}{\left(s + \frac{1}{2}\right)^2}$$

$$= \frac{5 \left\{ \frac{\left(s + \frac{1}{2}\right) + \frac{1}{2} \cdot \frac{\sqrt{3} \times \frac{1}{\sqrt{3}}}{\left(s + \frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2} \right\}}{\left(s + \frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2}$$

$$= 5 \left[ e^{-\frac{1}{2}t} \cos \frac{\sqrt{3}}{2}t + \frac{1}{\sqrt{3}} e^{-\frac{1}{2}t} \sin \frac{\sqrt{3}}{2}t \right]$$

$$V_b(s) = 5e^{-\frac{1}{2}t} \left[ \cos \frac{\sqrt{3}}{2}t + \frac{1}{\sqrt{3}} \sin \frac{\sqrt{3}}{2}t \right]$$


unit step function.

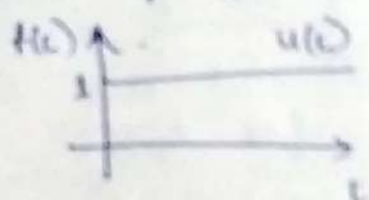


$$u(t) = \begin{cases} 1 & \text{for } t \geq 0 \\ 0 & \text{for } t < 0. \end{cases}$$

$$\mathcal{L}[u(t)] = \int_{0^-}^{\infty} 1 \cdot e^{-st} \cdot dt = \left[ \frac{1}{s} e^{-st} \right]_0^{\infty} = \frac{1}{s}$$

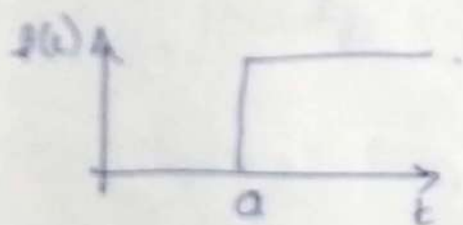
$$\boxed{\mathcal{L}[u(t)] = \frac{1}{s}}$$


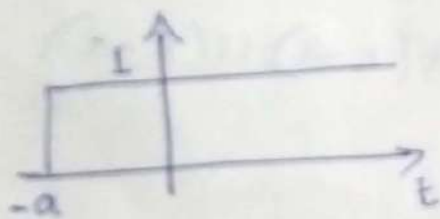
$$u(t-a) = \begin{cases} 1 & \text{for } t \geq a \\ 0 & \text{for } t < a. \end{cases}$$



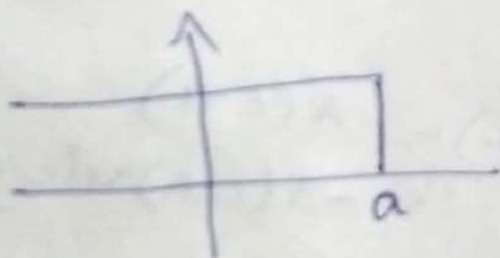
$$u(t+a) = \begin{cases} 1 & \text{for } t \geq -a \\ 0 & \text{for } t < -a. \end{cases}$$



$$u(-(t-a)) = u(a-t) = \begin{cases} 1 & \text{for } t < a \\ 0 & \text{for } t \geq a. \end{cases}$$

## unit ramp functions:

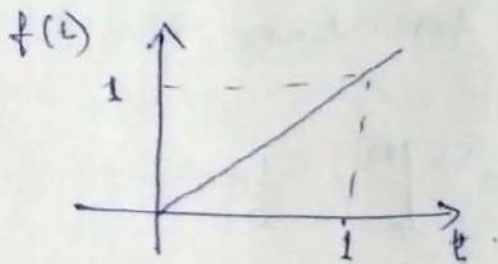


$$\gamma(t) = \begin{cases} t & \text{for } t \geq 0 \\ 0 & \text{for } t < 0 \end{cases}$$


$$\mathcal{L}[\gamma(t)] = \mathcal{L}[t] = \frac{1}{s^2}$$

if slope is  $\frac{y}{x}$   $A t = A[A t] = \frac{A}{s^2}$ .

Shifted versions of ramp

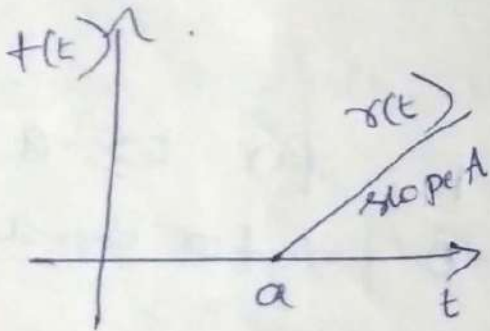
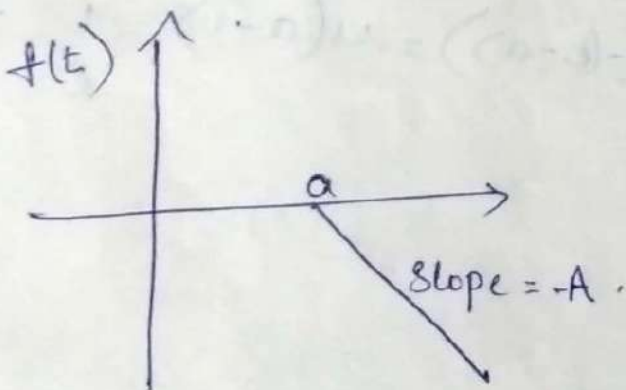
$$\begin{aligned} \gamma(t) &= A(t-a) \\ &= A(t-a)u(t-a) \end{aligned}$$




$$\begin{aligned} \gamma(t) &= -A(t-a) \\ &= -A(t-a)u(t-a) \end{aligned}$$

Gate function:

The gate fun helps to determine the Laplace transform of discrete periodic functions.

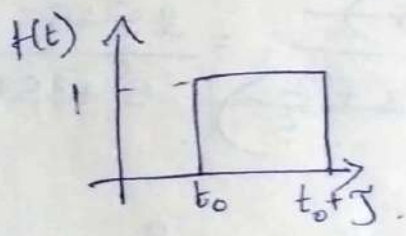Gate fun has height 1 and a period of  $T$ .  
it starts at  $t=t_0$  & ends at  $t=t_0+T$   
 $T \rightarrow$  period of gate fun.




$$g_{t_0}(t) = u(t-t_0) - u[t-(t_0+T)]$$

$$G_{t_0}(s) = e^{-t_0 s} \frac{1}{s} - e^{-(t_0+T)s} \frac{1}{s}$$
$$= \frac{e^{-t_0 s}}{s} [1 - e^{-Ts}]$$



$$t_0=0, G_0(s) = \frac{1}{s} (1 - e^{-Ts})$$

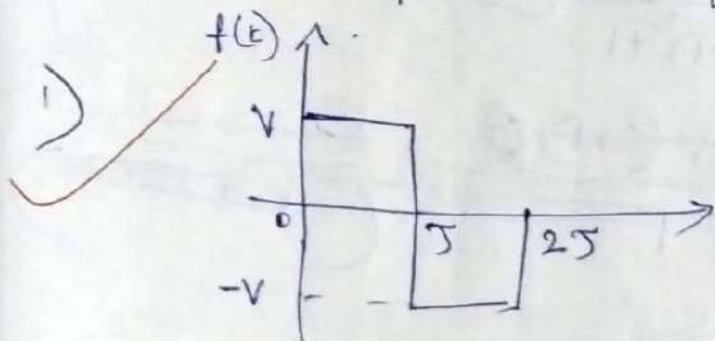Find Laplace transform of following signal



$$\begin{aligned}
 f_1(t) &= V u(t) - 2V u(t-T) + V u(t-2T) \\
 &= \frac{V}{s} - 2V e^{-sT} \frac{1}{s} + V e^{-2sT} \frac{1}{s} \\
 &= \frac{V}{s} (1 - 2e^{-sT} + e^{-2sT})
 \end{aligned}$$

$$F(s) = \frac{V}{s} [(1 - e^{-sT})^2]$$

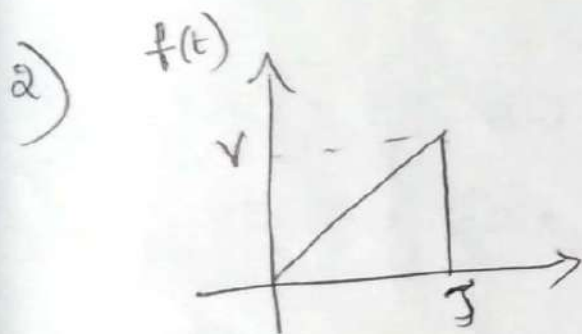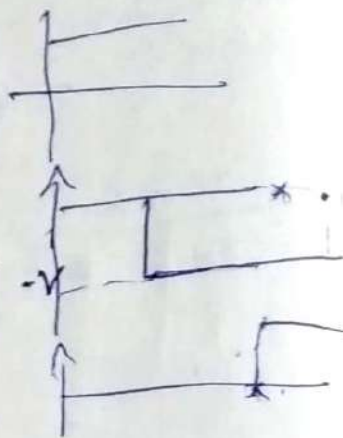


$f(t) \stackrel{\text{unit}}{=} t$  slope  $\frac{V}{T}$

$$f(t) = \frac{V}{T} t - \frac{V}{T} (t-T) u(t-T) - V u(t-T)$$



$$= \frac{V}{T} t u(t) - \frac{V}{T} (t-T) u(t-T) - V u(t-T)$$
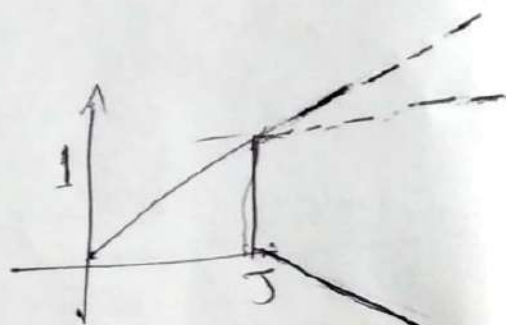
$$F(s) = \frac{V}{T} \frac{1}{s^2} - \frac{V}{T} e^{-sT} \frac{1}{s^2} - V e^{-sT} \frac{1}{s}$$



$$\begin{aligned}
 f(t) &= t - (t-T) u(t-T) - V u(t-T) \\
 &= t - (t-T) u(t-T) - V u(t-T)
 \end{aligned}$$

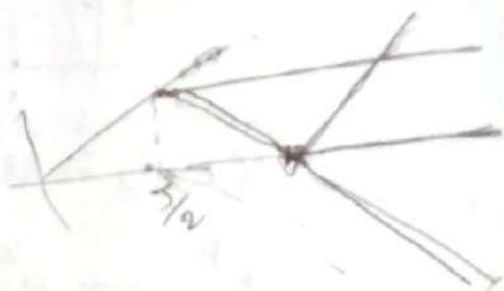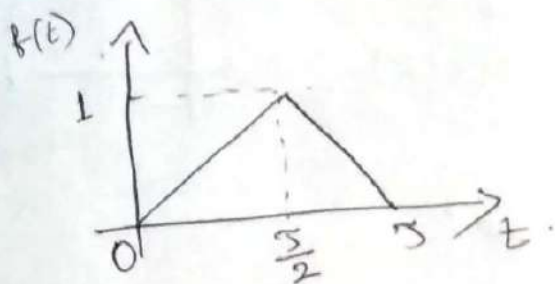For the w/f shown in fig write Laplace transform.



$$f(t) = \delta(t) - \delta\left(t - \frac{3}{2}\right) - \delta\left(t - \frac{3}{2}\right) + \delta(t - 3)$$

$$= \delta(t) - 2\delta\left(t - \frac{3}{2}\right) + \delta(t - 3)$$



$$= \text{slope } t - \text{slope} \cdot 2 \left(t - \frac{3}{2}\right) + \text{slope}(t - 3)$$

$$= \frac{1}{3}t - 2 \cdot \frac{1}{3} \left(t - \frac{3}{2}\right) + \frac{1}{3/2}(t - 3)$$

$$= \frac{2}{3}t - \frac{4}{3} \left(t - \frac{3}{2}\right) + \frac{2}{3}(t - 3)$$

$$= \frac{2}{3}t u(t) - \frac{4}{3} \left(t - \frac{3}{2}\right) u\left(t - \frac{3}{2}\right) + \frac{2}{3}(t - 3) u(t - 3)$$

3)

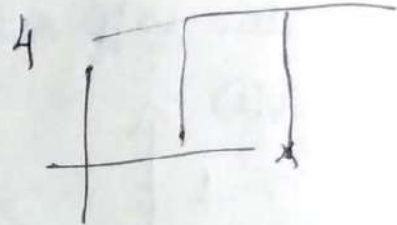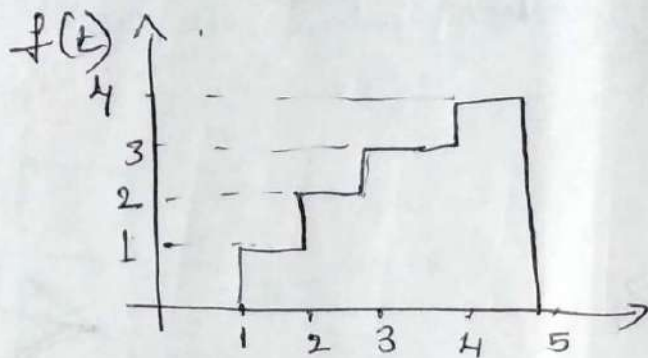


$$f(t) = u(t-1) + u(t-2) + u(t-3) + u(t-4) - 4u(t-5)$$

$$F(s) = e^{-1s} \frac{1}{s} + e^{-2s} \frac{1}{s} + e^{-3s} \frac{1}{s} + e^{-4s} \frac{1}{s} - 4e^{-5s} \frac{1}{s}$$

$$= \frac{1}{s} \left[ e^{-s} + e^{-2s} + e^{-3s} + e^{-4s} - 4e^{-5s} \right]$$

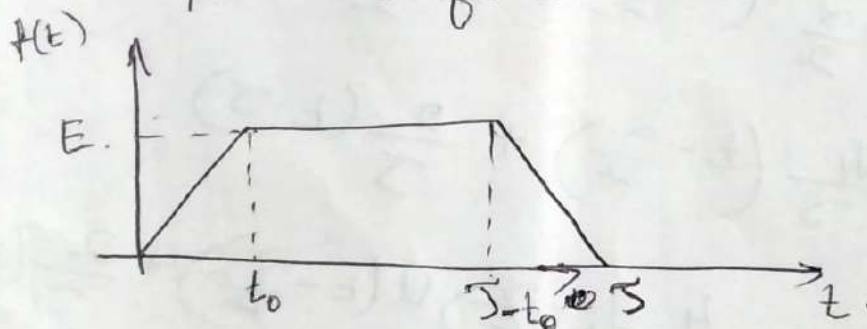4) write the eqn for the waveform and find its Laplace transform.



$$f(t) = \delta(t) - \delta(t-t_0) - \delta(t-(t_0+s)) + \delta(t-s)$$

$$f(t) = t - t(t-t_0) - (t-(t_0+s)) + (t-s)$$



$$f(t) = \frac{E}{t_0} t - \frac{E_0}{t_0} (t-t_0) - \frac{E_0}{t_0} [t-(s-t_0)] + \frac{E_0}{t_0} (t-s)$$

$$= \frac{E}{t_0} t u(t) - \frac{E_0}{t_0} (t-t_0) u(t-t_0) - \frac{E_0}{t_0} [t-(s-t_0)] u(t-(s-t_0)) + \frac{E_0}{t_0} (t-s) u(t-s)$$

$$= \frac{E_0}{t_0} \cdot \frac{1}{s^2} - \frac{E_0}{t_0} e^{-t_0 s} \frac{1}{s^2} - \frac{E_0}{t_0} e^{-(s-t_0)s} \frac{1}{s^2} + \frac{E_0}{t_0} e^{-3s} \frac{1}{s^2}$$

$$= \frac{E_0}{t_0 s^2} [1 - e^{-t_0 s} - e^{-(s-t_0)s} + e^{-3s}]$$

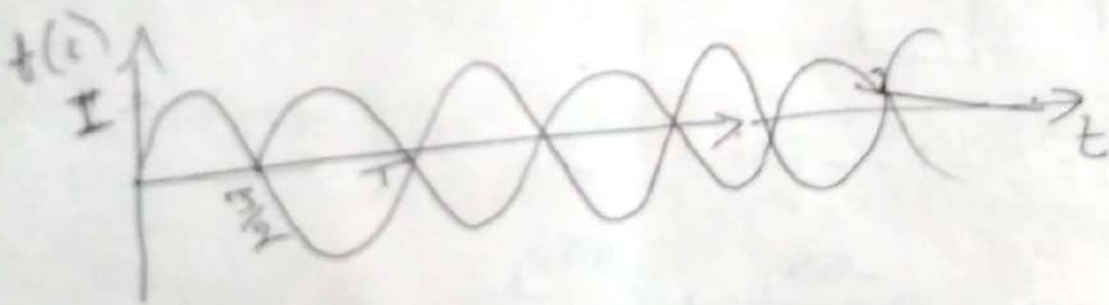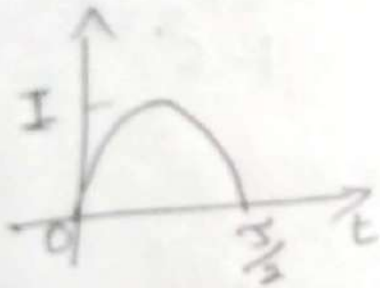write the eqn for sinusoidal waveform shown & find its Laplace transform.



$$\omega = 2\pi f = \frac{2\pi}{T}$$


$$f(t) = I \sin\left(\frac{2\pi}{T} t\right) u(t) + I \sin\left(\frac{2\pi}{T} (t - \frac{3}{2})\right) u(t - \frac{3}{2})$$

$$= I \frac{\frac{2\pi}{T}}{s^2 + \left(\frac{2\pi}{T}\right)^2} + I e^{-\frac{3}{2}s} \left( \frac{\frac{2\pi}{T}}{s^2 + \left(\frac{2\pi}{T}\right)^2} \right)$$

$$F(s) = I \frac{\frac{2\pi}{T}}{s^2 + \left(\frac{2\pi}{T}\right)^2} [1 + e^{-\frac{3}{2}s}]$$




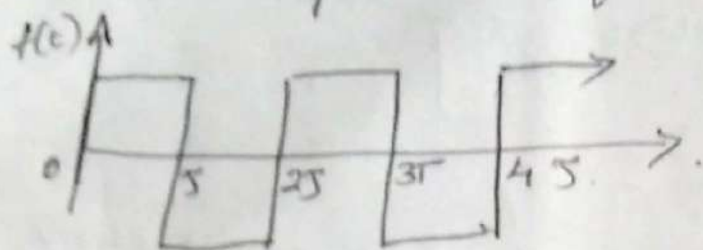6) For the rectangular waveform shown write down the Laplace transform equation.



whenever there is a periodic fun.
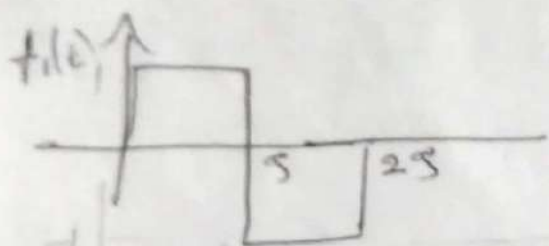
$$\text{Laplace transform } F(s) = \frac{F_1(s)}{1 - e^{-2Ts}}$$



$$f_1(t) = u(t) - 2u(t-T) + u(t-2T)$$




$$F_1(s) = \frac{1}{s} - 2e^{-Ts} \frac{1}{s} + e^{-2Ts} \frac{1}{s}$$

$$= \frac{1}{s} [1 - 2e^{-Ts} + e^{-2Ts}]$$

$$= \frac{1}{s} (1 - e^{-Ts})^2$$




$$F(s) = \frac{F_1(s)}{1 - e^{-2Ts}}$$
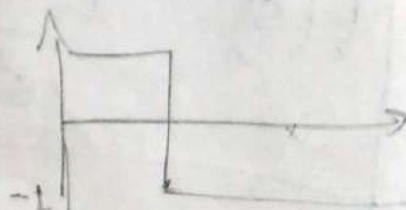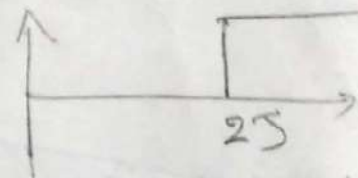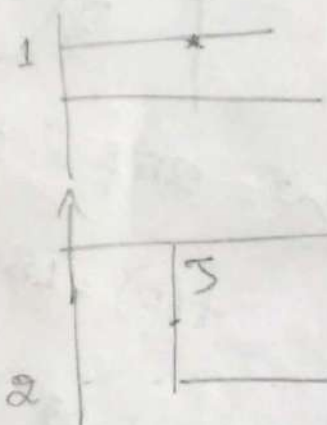
$$= \frac{1(1 - e^{-Ts})^2}{s(1 - e^{-2Ts})}$$



①

# 1) waveform Synthesis:

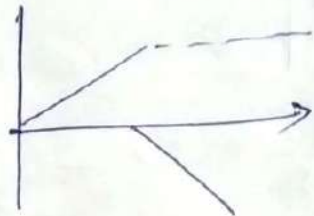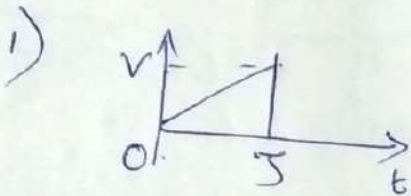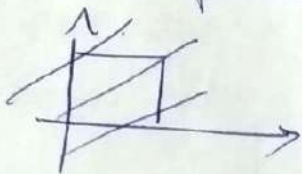

$$f(t) = v(t) - v(t-T) - u(t-T)$$

$$f(t) = \frac{v}{T} t - \frac{v}{T} (t-T) - v u(t-T)$$




$$= \frac{v}{T} t u(t) - \frac{v}{T} (t-T) u(t-T) - v u(t-T)$$

$$F(s) = \frac{v}{T} \frac{1}{s^2} - \frac{v}{T} e^{-Ts} \frac{1}{s^2} - v e^{-Ts} \frac{1}{s}$$

$$= \frac{v}{Ts^2} [1 - e^{-Ts}] - v \frac{e^{-Ts}}{s}$$

$$= \frac{v}{Ts^2} [1 - e^{-Ts} - Ts e^{-Ts}]$$
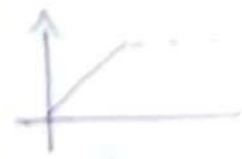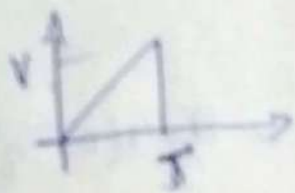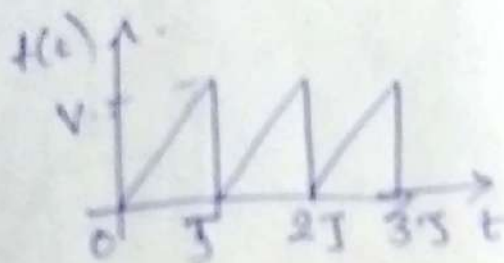
$$F(s) = \frac{v}{Ts^2} [1 - (1+Ts)e^{-Ts}]$$





$$f_1(t) = \frac{V}{T} \gamma(t) - \frac{V}{T} \gamma(t-T)$$

$$F_1(s) = \frac{V}{Ts^2} [1 - (1+Ts)e^{-Ts}]$$

$$F(s) = \frac{F_1(s)}{1 - e^{-Ts}}$$

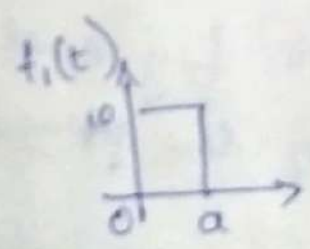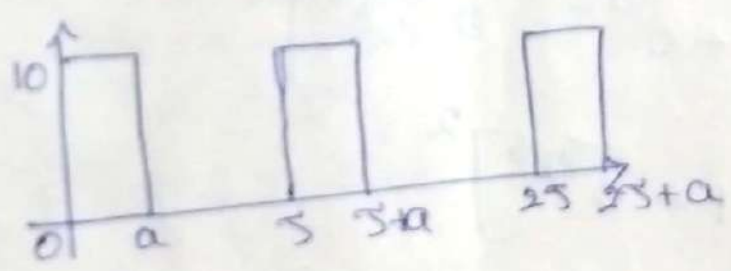For the rectangular pulse shown in fig write the eqn and find its Laplace transform.





$$f_1(t) = 10u(t) - 10u(t-a)$$

$$F_1(s) = 10 \frac{1}{s} - 10e^{-as} \frac{1}{s}$$

$$= \frac{10}{s} [1 - e^{-as}]$$
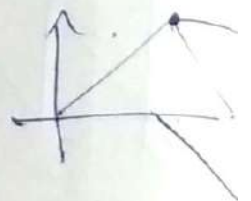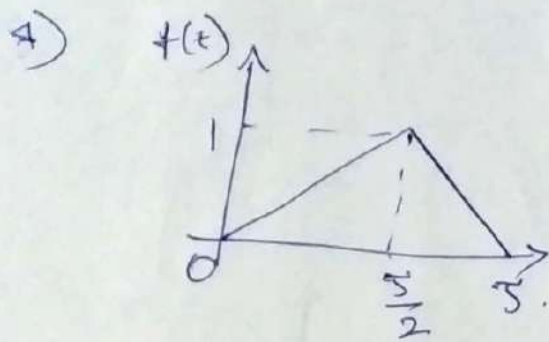
$$F(s) = \frac{F_1(s)}{1 - e^{-Ts}} = \frac{10}{s} \left[ \frac{1 - e^{-as}}{1 - e^{-Ts}} \right]$$



$$f(t) = \frac{1}{3/2} \gamma(t) - \frac{2}{5} \gamma(t - 3/2) - \frac{2}{5} \gamma(t - 5) + \frac{2}{5} \gamma(t - 5)$$

$$= \frac{2}{5} t - \frac{2}{5} (t - 3/2) - \frac{2}{5} (t - 3/2) + \frac{2}{5} (t - 5)$$

$$f(t) = \frac{2}{5} t - \frac{4}{5} (t - 3/2) + \frac{2}{5} (t - 5)$$


$$= \frac{2}{5} t u(t) - \frac{4}{5} (t - 3/2) u(t - 3/2) + \frac{2}{5} (t - 5) u(t - 5)$$

$$F(s) = \frac{2}{5} \cdot \frac{1}{s^2} - \frac{4}{5} e^{-3/2 s} \frac{1}{s^2} + \frac{2}{5} e^{-5s} \frac{1}{s^2}$$

$$= \frac{2}{5 s^2} \left[ 1 + e^{-5s} - 2 e^{-3/2 s} \right]$$

$$F(s) = \frac{2}{5 s^2} \left[ 1 - e^{-3/2 s} \right]^2$$


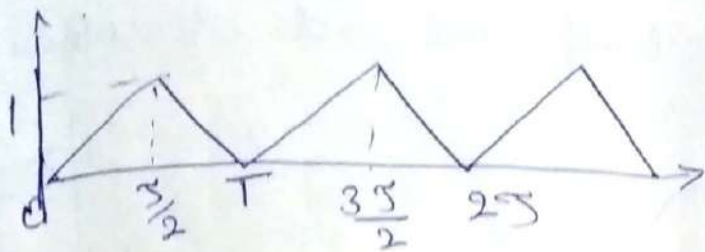
5] Synthesize the w/f shown in fig and find the Laplace transform of the periodic waveform.



$$F(s) = \frac{F_1(s)}{1 - e^{-Ts}}$$

$$= \frac{\frac{2}{3s^2} \left[ 1 - e^{-\frac{3s}{2}} \right]^2}{1 - e^{-Ts}}$$

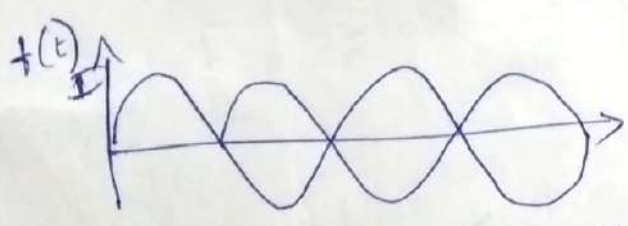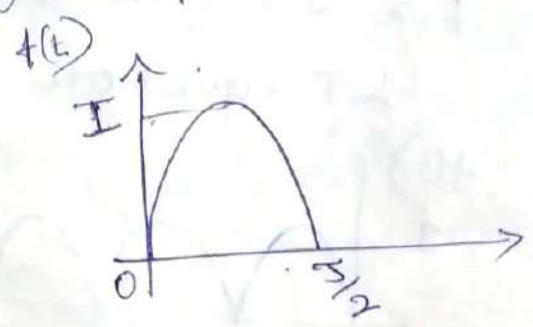write the equation for the sinusoidal waveform and find its Laplace transform



$$f(t) \Rightarrow \omega = 2\pi f = \frac{2\pi}{T}$$


$$f(t) = I \sin \omega t + I \sin \omega(t - T/2)$$

$$f(t) = I \sin \frac{2\pi}{T} t u(t) + I \sin \frac{2\pi}{T} (t - T/2) u(t - T/2)$$

$$F(s) = I \frac{\frac{2\pi}{T}}{s^2 + \left(\frac{2\pi}{T}\right)^2} + I e^{-\frac{sT}{2}} \frac{\frac{2\pi}{T}}{s^2 + \left(\frac{2\pi}{T}\right)^2}$$

$$= I \frac{\frac{2\pi}{T}}{s^2 + \left(\frac{2\pi}{T}\right)^2} \left[ 1 + e^{-\frac{sT}{2}} \right]$$

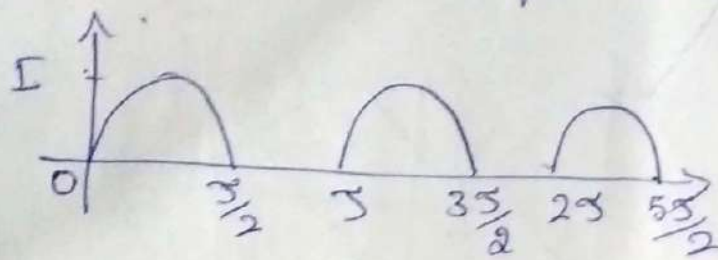
7) Find the LT for half rectified sine wave



$$F(s) = \frac{F_1(s)}{1 - e^{-\gamma s}} = I \cdot$$

$$= I \frac{\frac{2\pi}{\gamma}}{s^2 + \left(\frac{2\pi}{\gamma}\right)^2} \left[ \frac{1 + e^{-\frac{\gamma}{2}s}}{1 - e^{-\gamma s}} \right]$$

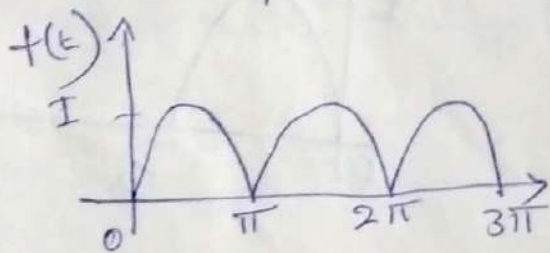8) For the full rectified waveform, find the LT equation.




$$F(s) = \frac{F_1(s)}{1 - e^{-\gamma s}}$$

$$\gamma = 2\pi$$

$$\therefore F_1(s) = \frac{I}{s^2 + 1} (1 + e^{-\pi s})$$

$$F(s) = \frac{I}{(s^2 + 1)} \frac{(1 + e^{-\pi s})}{(1 - e^{-\pi s})}$$
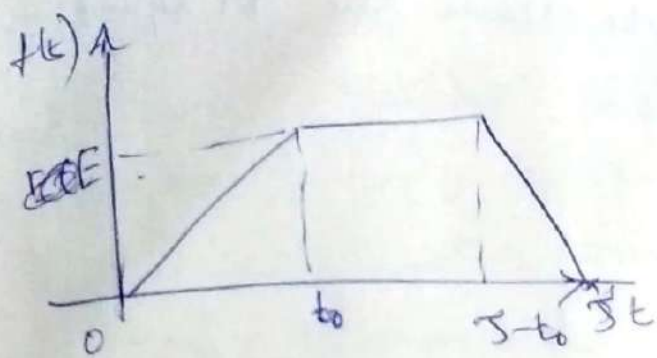
$$= \frac{I}{s^2 + 1} \coth \frac{\pi s}{2}$$



$$f(t) = \frac{E}{t_0} \gamma(t) - \frac{E}{t_0} \gamma(t-t_0) - \frac{E}{t_0} \gamma(t-(S-t_0)) + \frac{E}{t_0} \gamma(t-S)$$

$$= \frac{E}{t_0} t - \frac{E}{t_0} (t-t_0) - \frac{E}{t_0} (t-(S-t_0)) + \frac{E}{t_0} (t-S)$$

$$= \frac{E}{t_0} t u(t) - \frac{E}{t_0} (t-t_0) u(t-t_0) - \frac{E}{t_0} [t-(S-t_0)] u(t-(S-t_0)) + \frac{E}{t_0} (t-S) u(t-S)$$

$$= \frac{E}{t_0} \frac{1}{s^2} - \frac{E}{t_0} e^{-t_0 s} \frac{1}{s^2} - \frac{E}{t_0} e^{-(S-t_0)s} \frac{1}{s^2} + \frac{E}{t_0} e^{-Ss} \frac{1}{s^2}$$


$$= \frac{E}{t_0 s^2} \left[ 1 - e^{-t_0 s} - e^{-(S-t_0)s} + e^{-Ss} \right]$$

$$= \frac{E_0}{t_0 s^2} \left[ 1 - e^{-t_0 s} + e^{-Ss} (1 - e^{t_0 s}) \right]$$


$$= \frac{E_0}{t_0 s^2} \left[ 1 - e^{-t_0 s} \right]$$

$\frac{E}{s}$

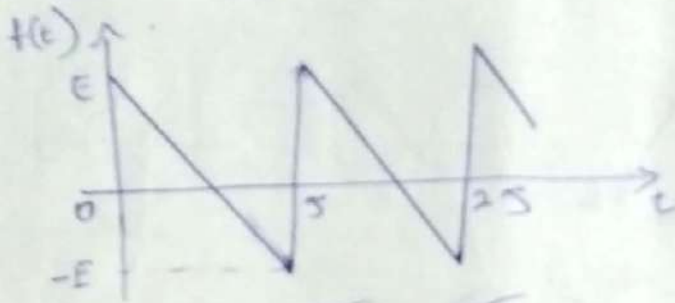10) For the w/f shown, write down the LT of



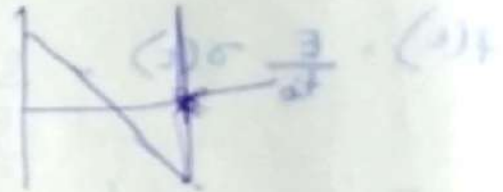~~$$f(t) = -\frac{E}{\frac{3}{2}}t + \frac{E}{\frac{3}{2}}(t-\tau)$$~~



$$f(t) = E u(t) - \frac{E}{\frac{3}{2}}t + \frac{E}{\frac{3}{2}}(t-\tau) + E u(t-\tau)$$



$$= E u(t) - \frac{2E}{3}t + \frac{2E}{3}(t-\tau) + E u(t-\tau)$$

$$F_1(s) = E \cdot \frac{1}{s} - \frac{2E}{3} \cdot \frac{1}{s^2} + \frac{2E}{3} e^{-s\tau} \frac{1}{s^2} + E \cdot e^{-s\tau} \frac{1}{s}$$

$$= \frac{E}{s} (1 + e^{-s\tau}) - \frac{2E}{3s^2} (1 - e^{-s\tau})$$

~~2nd~~


$$F(s) = \frac{F_1(s)}{1 - e^{-s\tau}}$$

$$= \frac{E(1+e^{-s\tau})}{s(1-e^{-s\tau})} - \frac{2E}{3s^2}$$

$$F(s) = -\frac{2E}{3s^2} + \frac{E}{s} \coth\left(\frac{s\tau}{2}\right)$$



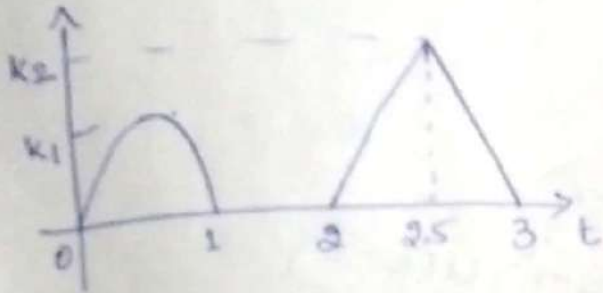11) The w/f shown in fig is sinusoidal in the interval  $t=0$  to  $t=1$  and is an isosceles triangle from  $t=2$  to  $t=3$ . For all other  $t$ ,  $v=0$ . Write the expression for  $v(t)$ , using step, ramp and sine functions and find its Laplace transform.



$$f_1(t) = k_1 \sin \omega t + k_1 \sin \omega(t-1)$$

$$\omega = 2\pi f = \frac{2\pi}{T} = \frac{2\pi}{2} = \pi \text{ rad/sec}$$

$$= k_1 \sin \pi t u(t) + k_1 \sin \pi(t-1) u(t-1)$$

$$F_1(s) = k_1 \frac{\pi}{s^2 + \pi^2} + k_1 e^{-s} \frac{\pi}{s^2 + \pi^2}$$

$$f_2(t) = \frac{k_2}{0.5} \gamma(t-2) - \frac{k_2}{0.5} \gamma(t-2.5) - \frac{k_2}{0.5} \gamma(t-2.5)$$

$$+ \frac{k_2}{0.5} \gamma(t-3)$$

$$= \frac{k_2}{0.5} (t-2) u(t-2) - \frac{2}{0.5} k_2 (t-2.5) u(t-2.5)$$



$$+ \frac{k_2}{0.5} (t-3) u(t-3)$$

$$= 2k_2 (t-2) u(t-2) - 4k_2 (t-2.5) u(t-2.5) + 2k_2 (t-3) u(t-3)$$

$$F_2(s) = 2k_2 \frac{e^{-2s}}{s^2} - 4k_2 e^{-2.5s} \frac{1}{s^2} + 2k_2 e^{-3s} \frac{1}{s^2}$$

$$F(s) = F_1(s) + F_2(s)$$

12) Find LT of periodic signal  $x(t)$

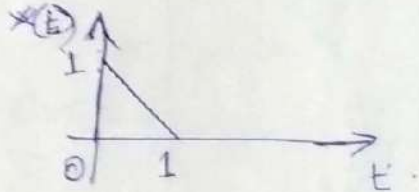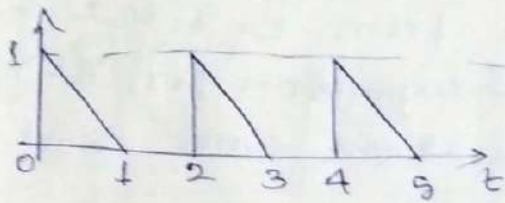

$$f_1(t) = u(t) - x(t) + x(t-1)$$

$$f_1(t) = u(t) - t u(t) + (t-1) u(t-1)$$

$$F_1(s) = \frac{1}{s} - \frac{1}{s^2} + e^{-s} \frac{1}{s^2}$$



$$= \frac{1}{s} - \frac{1}{s^2} [1 + e^{-s}] = \frac{s - 1 + e^{-s}}{s^2}$$

$$= \frac{s - 1 + e^{-s}}{s^2}$$

here  $s=2$

$$F(s) = \frac{F_1(s)}{1 - e^{-s}} = \frac{s - 1 + e^{-s}}{s^2(1 - e^{-s})}$$

13) Find LT

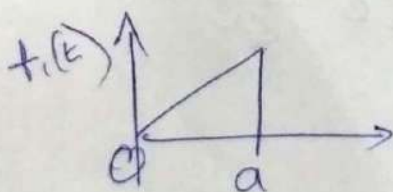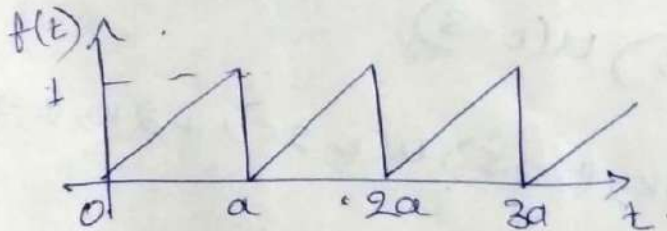

$$f_1(t) = x(t) - x(t-a) - u(t-a)$$

$$= t - (t-a) - u(t-a)$$

$$= \frac{1}{a} t u(t) - \frac{1}{a} (t-a) u(t-a) - u(t-a)$$

$$F_1(s) = \frac{1}{as^2} - \frac{1}{a} e^{-as} \frac{1}{s^2} - e^{-as} \frac{1}{s}$$

$$F_1(s) = \frac{1}{as^2} (1 - e^{-as}) - e^{-as} \frac{1}{s}$$


$$F(s) = \frac{F_1(s)}{1 - e^{-as}}$$

$$= \mathcal{L}^{-1} \{ a \cdot \dots \}$$

$$= \frac{F_1(s)}{1 - e^{-as}}$$

$$F(s) = \frac{1}{as^2} - \frac{e^{-as}}{s(1 - e^{-as})}$$

14]. Find LT.

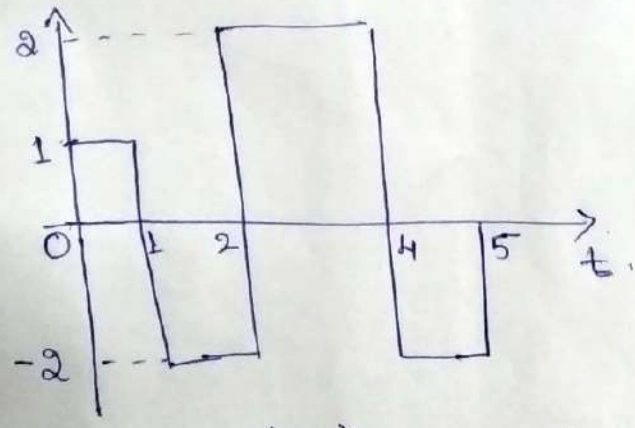

$$f(t) = u(t) - 3u(t-1) + 4u(t-2) - 4u(t-4) - 2u(t-5)$$

$$F(s) = \frac{1}{s} \left[ 1 - 3e^{-s} + 4e^{-2s} - 4e^{-4s} - 2e^{-5s} \right]$$

$$F(s) = \frac{1}{s} \left[ 1 - 3e^{-s} + 4e^{-2s} - 4e^{-4s} - 2e^{-5s} \right]$$

# **NETWORK ANALYSIS (18EC32)**

## **Syllabus:-**

Module -5

❖ **Two Port Network Parameters**

❖ **Resonance**

## Introduction

Electrical n/w consists of passive and active elements.

To energise a passive n/w, the n/w needs to be connected to an energy source.

Two terminals are provided for the passive n/w which may be represented as a box, and to these terminals the energy source is connected.

If only one pair of terminals available for internal connections, the n/w is termed as one port n/w.

If 2 pairs of terminals are available,  $\rightarrow$  2 port n/w.  
one of them is called  $\rightarrow$  i/p port.  
o/p port.

The  $v$  &  $i$  at the 2 ports are interrelated and these relationships are expressed in terms of n/w parameters.

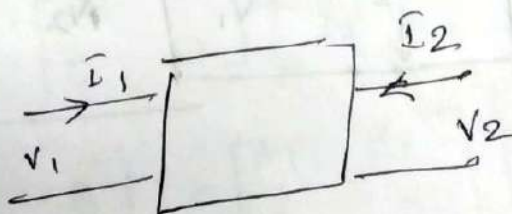


Fig. 7.1(a)

### 7.3 Open-circuit Impedance Parameters (z parameters):

The defining equations for these parameters are:

$$z_{11} I_1 + z_{12} I_2 = V_1 \quad \dots (7.7)$$

$$z_{21} I_1 + z_{22} I_2 = V_2 \quad \dots (7.8)$$

By putting  $I_1 = 0$  or  $I_2 = 0$  in the above equations, we get

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \dots (7.9)$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \quad \dots (7.11)$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad \dots (7.10)$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \dots (7.12)$$

$z_{11}$ ,  $z_{12}$ ,  $z_{21}$  and  $z_{22}$  are called *open-circuit impedance parameters*, as they are obtained by putting  $I_1 = 0$  or  $I_2 = 0$  i.e. by open-circuiting the two ports alternately.

For reciprocal or bilateral networks,  $z_{12} = z_{21}$ .

The equivalent network of a two-port network in terms of  $z$  parameters is as shown in Fig. 7.1(b).

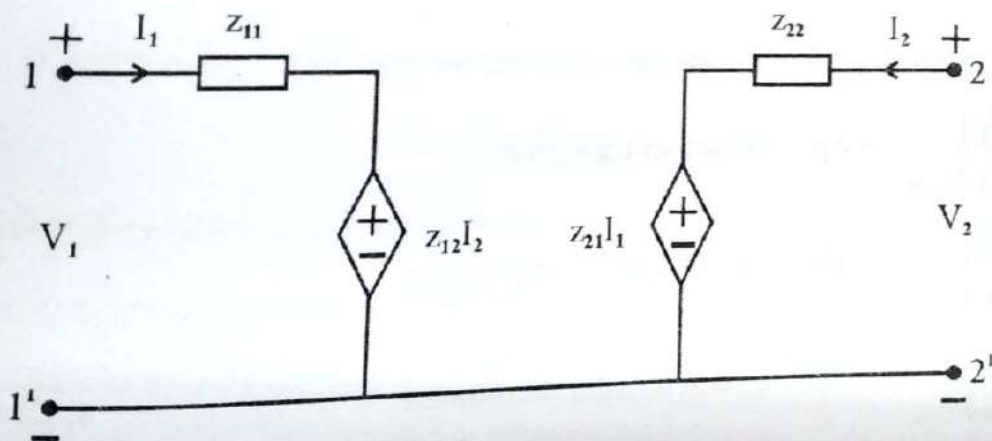


Fig. 7.1(b)

2) Short circuited admittance parameters.  $V = EY$   
 $I = EY$

$I_1, I_2$  dependent,  $V_1, V_2 \rightarrow$  independent  
 $I_1, I_2 \rightarrow$  dependent.

$$I_1 = f_1(\underbrace{V_1, V_2}_{in})$$

$$I_2 = f_2(V_1, V_2)$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \Rightarrow \text{i/p admittance with o/p port shorted}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} \Rightarrow \text{Transfer admittance with i/p port short circuited.}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} \Rightarrow \text{Transfer admittance with o/p port short circuited.}$$


$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} \Rightarrow \text{output admittance with i/p port short circuited.}$$



$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{cases} I_1 = Y_{11}V_1 + Y_{12}V_2 \\ I_2 = Y_{21}V_1 + Y_{22}V_2 \end{cases}$$

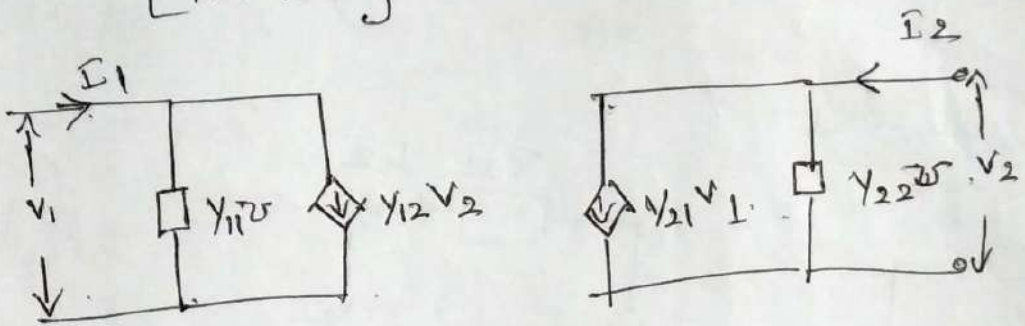where  $\Delta Y = Y_{11}Y_{22} - Y_{12}Y_{21}$




Hybrid Parameters (h parameters)  
 independent -  $V_1, I_2$   
 dependent  $V_2, I_1$   
 i/p voltage, o/p current

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$

- $h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$  → i/p impedance with o/p port short cktd.
- $h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$  → Reverse  $V_g$  gain with i/p port open cktd.
- $h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$  → Forward current gain with o/p port short cktd.
- $h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$  → o/p admittance with i/p port open cktd.

$$\Delta = h_{11}h_{22} - h_{21}h_{12}$$
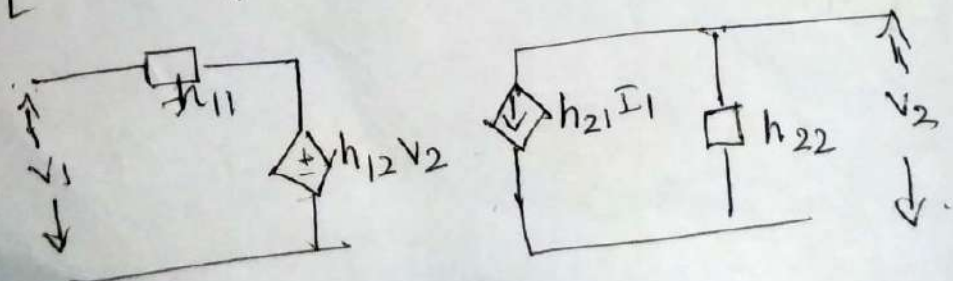
$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$



# Transmission parameters (T)

Gives relation b/w  $V_1$  & current at one port to the  $V_2$  & current at the other port.

$V_1, I_1$  dependent,  $V_2, I_2$  independent.

$$V_1 = AV_2 - BI_2$$
$$I_1 = CV_2 - DI_2$$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0}$$

$\downarrow \frac{1}{A} = \frac{V_2}{V_1} \Big|_{I_2=0} \Rightarrow$  Forward  $V_1$  gain  $n$  with o/p port open circuited.

$$-B = \frac{V_1}{I_2} \Big|_{V_2=0}$$

$-\frac{1}{B} = \frac{I_2}{V_1} \Big|_{V_2=0} \rightarrow$  Transfer conductance port short ckted. with o/p

$$C = \frac{I_1}{V_2} \Big|_{I_2=0}$$



$\frac{1}{C} = \frac{V_2}{I_1} \Big|_{I_2=0} \Rightarrow$  Transfer impedance with o/p port open circuited.

$$-D = \frac{I_1}{I_2} \Big|_{V_2=0}$$

$-\frac{1}{D} = \frac{I_2}{I_1} \Big|_{V_2=0} \Rightarrow$  Forward current gain with o/p port short ckted.

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

$$\Delta T = AD - BC$$

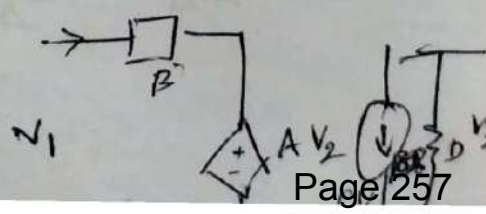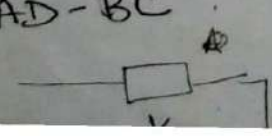

## Relationship b/w Z and Y parameters:

Z parameters

$$\begin{cases} V_1 = Z_{11} I_1 + Z_{12} I_2 & \text{--- (1)} \\ V_2 = Z_{21} I_1 + Z_{22} I_2 & \text{--- (2)} \end{cases}$$

Y parameters

$$\begin{cases} I_1 = Y_{11} V_1 + Y_{12} V_2 & \text{--- (3)} \\ I_2 = Y_{21} V_1 + Y_{22} V_2 & \text{--- (4)} \end{cases}$$

from (3) & (4), express  $V_1$  & compare with (1) & (2)

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{aligned} V_1 &= \frac{\begin{bmatrix} I_1 & Y_{12} \\ I_2 & Y_{22} \end{bmatrix}}{\Delta Y} = \frac{Y_{22} I_1 - Y_{12} I_2}{\Delta Y} \\ V_1 &= \frac{Y_{22} I_1}{\Delta Y} - \frac{Y_{12} I_2}{\Delta Y} \end{aligned} \quad \text{--- (5)}$$

Compare (1) & (5)

$$Z_{11} = \frac{Y_{22}}{\Delta Y} \quad Z_{12} = -\frac{Y_{12}}{\Delta Y}$$

$$\begin{aligned} V_2 &= \frac{\begin{bmatrix} Y_{11} & I_1 \\ Y_{21} & I_2 \end{bmatrix}}{\Delta Y} = \frac{Y_{11} I_2 - Y_{21} I_1}{\Delta Y} \\ &= -\frac{Y_{21} I_1}{\Delta Y} + \frac{Y_{11} I_2}{\Delta Y} \end{aligned} \quad \text{--- (6)}$$

Comp eqn (2) & (6)

$$Z_{21} = -\frac{Y_{21}}{\Delta Y} \quad Z_{22} = \frac{Y_{11}}{\Delta Y}$$

Relation b/w  $Z$  and  $h$  parameter.

$V_1, I_2, I_1, V_2$

$$h \text{ parameter } \begin{cases} V_1 = h_{11} I_1 + h_{12} V_2 & \text{--- (1) --- (3)} \\ I_2 = h_{21} I_1 + h_{22} V_2 & \text{--- (2) --- (4)} \end{cases}$$

& ~~2~~

$$Z \text{ parameters } \begin{cases} V_1 = Z_{11} I_1 + Z_{12} I_2 & \text{--- (A) --- (1)} \\ V_2 = Z_{21} I_1 + Z_{22} I_2 & \text{--- (B) --- (2)} \end{cases}$$

from (2)

$$h_{22} V_2 = I_2 - h_{21} I_1$$

$$V_2 = \frac{I_2}{h_{22}} - \frac{h_{21}}{h_{22}} I_1$$

$$V_2 = -\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \quad \text{--- (5)}$$

Compare (2) & (5)

$$Z_{21} = -\frac{h_{21}}{h_{22}}, \quad Z_{22} = \frac{1}{h_{22}}$$

Subst. eqn (5) in (3)

$$V_1 = h_{11} I_1 + h_{12} \left( -\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \right)$$

$$= I_1 \left( h_{11} - \frac{h_{12} h_{21}}{h_{22}} \right) + \frac{h_{12}}{h_{22}} I_2 \quad \text{--- (6)}$$

Compare eqn (6) & (1)

$$Z_{11} = h_{11} - \frac{h_{12} h_{21}}{h_{22}} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} = \frac{\Delta h}{h_{22}}$$

$$Z_{12} = -\frac{h_{12}}{h_{22}}$$

## Relation b/w $Z$ and $T$ parameters

$$\begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 & \text{--- (1)} \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 & \text{--- (2)} \end{aligned}$$

$T$  parameters.

$$V_1 = A V_2 - B I_2 \quad \text{--- (3)}$$

$$I_1 = C V_2 - D I_2 \quad \text{--- (4)}$$

from eqn (4).

$$C V_2 = I_1 + D I_2$$

$$V_2 = \frac{1}{C} I_1 + \frac{D}{C} I_2 \quad \text{--- (5)}$$

Compare (5) & (2)

$$Z_{21} = \frac{1}{C} \quad Z_{22} = \frac{D}{C}$$

Subst (5) in eqn (3)

$$V_1 = A \left( \frac{1}{C} I_1 + \frac{D}{C} I_2 \right) - B I_2$$

$$V_1 = \frac{A}{C} I_1 + I_2 \left( \frac{AD}{C} - B \right) \quad \text{--- (6)}$$

Compare (1) & (6)

$$\begin{aligned} Z_{11} &= \frac{A}{C} & Z_{12} &= \frac{AD}{C} - B \\ & & &= \frac{AD - BC}{C} \\ & & &= \frac{\Delta T}{C} \end{aligned}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

Summary:

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{Y_{22}}{\Delta Y} & -\frac{Y_{12}}{\Delta Y} \\ -\frac{Y_{21}}{\Delta Y} & \frac{Y_{11}}{\Delta Y} \end{bmatrix} = \begin{bmatrix} \frac{\Delta h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ -\frac{h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{bmatrix} = \begin{bmatrix} \frac{A}{C} & \frac{\Delta T}{C} \\ \frac{1}{C} & \frac{D}{C} \end{bmatrix}$$

Relation b/w  $Y$  parameters & other type of parameters. (5)

$Z$  parameters  $\rightarrow$   $Z$   
 $h$   
 $T$

$Z$  parameters  $\rightarrow$

$$\begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)} \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)} \end{aligned}$$

$V_1, V_2 \rightarrow$  depend  
 $I_1, I_2 \rightarrow$  independent

$Y$  parameters  $\rightarrow$

$$\begin{aligned} I_1 &= Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (3)} \\ I_2 &= Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (4)} \end{aligned}$$

$I_1, I_2 \rightarrow$  depend  
 $V_1, V_2 \rightarrow$  independent

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \Delta Z = Z_{11} Z_{22} - Z_{21} Z_{12}$$

$$I_1 = \frac{\begin{vmatrix} V_1 & Z_{12} \\ V_2 & Z_{22} \end{vmatrix}}{\Delta Z} = \frac{V_1 Z_{22} - V_2 Z_{12}}{\Delta Z}$$

$$I_1 = \frac{Z_{22}}{\Delta Z} V_1 - \frac{Z_{12}}{\Delta Z} V_2 \quad \text{--- (5)}$$

Comparing (3) & (5).

$$Y_{11} = \frac{Z_{22}}{\Delta Z}, \quad Y_{12} = -\frac{Z_{12}}{\Delta Z}$$

$$I_2 = \frac{\begin{vmatrix} Z_{11} & V_1 \\ Z_{21} & V_2 \end{vmatrix}}{\Delta Z} = \frac{Z_{11} V_2 - Z_{21} V_1}{\Delta Z}$$

$$\begin{aligned} I_2 &= \frac{Z_{11}}{\Delta Z} V_2 - \frac{Z_{21}}{\Delta Z} V_1 \\ &= -\frac{Z_{21}}{\Delta Z} V_1 + \frac{Z_{11}}{\Delta Z} V_2 \end{aligned}$$

$$Y_{21} = -\frac{Z_{21}}{\Delta Z}, \quad Y_{22} = \frac{Z_{11}}{\Delta Z}$$

$Y$  and  $h$  parameters.

$$Y.P. \begin{cases} I_1 = Y_{11} V_1 + Y_{12} V_2 & \text{--- (1)} \\ I_2 = Y_{21} V_1 + Y_{22} V_2 & \text{--- (2)} \end{cases}$$

$$h \text{ par} \begin{cases} V_1 = h_{11} I_1 + h_{12} V_2 & \text{--- (3)} \\ I_2 = h_{21} I_1 + h_{22} V_2 & \text{--- (4)} \end{cases}$$

from (3)

$$h_{11} I_1 = V_1 - h_{12} V_2$$

$$I_1 = \frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2 \quad \text{--- (5)}$$

Compare (1) & (5)

$$Y_{11} = \frac{1}{h_{11}} \quad Y_{12} = -\frac{h_{12}}{h_{11}}$$

Subs (5) in (4)

$$\begin{aligned} I_2 &= h_{21} \left( \frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2 \right) + h_{22} V_2 \\ &= \frac{h_{21}}{h_{11}} V_1 + \left( -\frac{h_{21} h_{12}}{h_{11}} + h_{22} \right) V_2 \end{aligned}$$

$$I_2 = \frac{h_{21}}{h_{11}} V_1 + \left( h_{22} + \frac{h_{21} h_{12}}{h_{11}} \right) V_2 \quad \text{--- (6)}$$

Compare (2) & (6)

$$Y_{21} = \frac{h_{21}}{h_{11}} \quad Y_{22} = \left( \frac{h_{11} h_{22} - h_{21} h_{12}}{h_{11}} \right) V_2$$

$$Y_{21} = \frac{h_{21}}{h_{11}} \quad Y_{22} = \frac{\Delta h}{h_{11}}$$

Y in terms of T parameters

Y para

$$\begin{cases} I_1 = Y_{11}V_1 + Y_{12}V_2 & \text{--- (1)} \\ I_2 = Y_{21}V_1 + Y_{22}V_2 & \text{--- (2)} \end{cases}$$

T parameters

$$\begin{cases} V_1 = AV_2 - BI_2 & \text{--- (3)} \\ I_1 = CV_2 - DI_2 & \text{--- (4)} \end{cases}$$

Rewrite eqn (3)

$$BI_2 = AV_2 - V_1$$

$$I_2 = \frac{A}{B}V_2 - \frac{1}{B}V_1$$

$$I_2 = -\frac{1}{B}V_1 + \frac{A}{B}V_2 \quad \text{--- (5)}$$

$$\therefore \boxed{Y_{21} = -\frac{1}{B}} \quad \boxed{Y_{22} = \frac{A}{B}}$$

Subst (5) in (4)

$$I_1 = CV_2 - D \left( -\frac{1}{B}V_1 + \frac{A}{B}V_2 \right) \quad \left[ \begin{matrix} A & B \\ C & D \end{matrix} \right] \cdot AD(BC)$$

$$= \left( C - \frac{DA}{B} \right) V_2 + \frac{D}{B}V_1$$

$$= \left( \frac{BC - AD}{B} \right) V_2 + \frac{D}{B}V_1$$

$$= -\left( \frac{AD - BC}{B} \right) V_2 + \frac{D}{B}V_1$$

$$I_1 = \frac{D}{B}V_1 - \left( \frac{\Delta T}{B} \right) V_2$$

$$\therefore \boxed{Y_{11} = \frac{D}{B}} \quad \boxed{Y_{12} = -\frac{\Delta T}{B}}$$



# Relation b/w h. parameters & other eq. parameters

$$h \rightarrow \frac{V}{I}$$

$$Z \begin{cases} V_1 = Z_{11} I_1 + Z_{12} I_2 & \text{--- (1)} \\ V_2 = Z_{21} I_1 + Z_{22} I_2 & \text{--- (2)} \end{cases}$$

$$h \begin{cases} V_1 = h_{11} I_1 + h_{12} V_2 & \text{--- (3)} \\ I_2 = h_{21} I_1 + h_{22} V_2 & \text{--- (4)} \end{cases}$$

rewriting eqn (2)

$$Z_{22} I_2 = V_2 - Z_{21} I_1$$

$$I_2 = \frac{1}{Z_{22}} V_2 - \frac{Z_{21}}{Z_{22}} I_1$$

$$I_2 = -\frac{Z_{21}}{Z_{22}} I_1 + \frac{1}{Z_{22}} V_2 \quad \text{--- (5)}$$

comp

(4) & (5)

$$\boxed{h_{21} = -\frac{Z_{21}}{Z_{22}}} \quad \boxed{h_{22} = \frac{1}{Z_{22}}}$$

sub eqn (5) in (1)

$$V_1 = Z_{11} I_1 + Z_{12} \left( -\frac{Z_{21}}{Z_{22}} I_1 + \frac{1}{Z_{22}} V_2 \right)$$

$$= \left( Z_{11} - \frac{Z_{12} Z_{21}}{Z_{22}} \right) I_1 + \frac{Z_{12}}{Z_{22}} V_2$$

$$V_1 = \left( \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{22}} \right) I_1 + \frac{Z_{12}}{Z_{22}} V_2 \quad \text{--- (6)}$$

$$V_1 = \left( \frac{\Delta Z}{Z_{22}} \right) I_1 + \frac{Z_{12}}{Z_{22}} V_2$$

$$\boxed{h_{11} = \frac{\Delta Z}{Z_{22}}} \quad \boxed{h_{12} = \frac{Z_{12}}{Z_{22}}}$$

Relat. on  $\mathbb{N}$   $T \rightarrow \left. \begin{matrix} 2 \\ 2 \\ n \end{matrix} \right\}$

(1)

$h \rightarrow y$ .

$$y \left\{ \begin{aligned} I_1 &= Y_{11} V_1 + Y_{12} V_2 && \text{--- (1)} \\ I_2 &= Y_{21} V_1 + Y_{22} V_2 && \text{--- (2)} \end{aligned} \right.$$

$$h \left\{ \begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 && \text{--- (3)} \\ I_2 &= h_{21} I_1 + h_{22} V_2 && \text{--- (4)} \end{aligned} \right.$$

Rewriting eqn (1)

$$Y_{11} V_1 = I_1 - Y_{12} V_2,$$

$$V_1 = \frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2. \text{--- (5)}$$

Compare (3) & (5)

$h_{11} = \frac{1}{Y_{11}}$	$h_{12} = -\frac{Y_{12}}{Y_{11}}$
-----------------------------	-----------------------------------

Subst. (5) in (2)

$$I_2 = Y_{21} \left( \frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2 \right) + Y_{22} V_2.$$

$$I_2 = \frac{Y_{21}}{Y_{11}} I_1 + \left( Y_{22} - \frac{Y_{21} Y_{12}}{Y_{11}} \right) V_2. \text{--- (6)}$$

Compare (4) & (6)

$$h_{21} = \frac{Y_{21}}{Y_{11}} \quad h_{22} = \frac{\Delta Y}{Y_{11}}$$

h and T.

$$h \begin{cases} V_1 = h_{11} I_1 + h_{12} V_2 & \text{--- (1)} \\ I_2 = h_{21} I_1 + h_{22} V_2 & \text{--- (2)} \end{cases}$$

$$T \begin{cases} V_1 = A V_2 - B I_2 & \text{--- (3)} \\ I_1 = C V_2 - D I_2 & \text{--- (4)} \end{cases}$$

~~Rewrite eqn (3)~~

$$\text{--- } B I_2 = V_1 - A V_2$$

$$I_2 = \frac{1}{B} V_1 - \frac{A}{B} V_2 \quad \text{--- (5)}$$

Rewrite eqn (4)

$$D I_2 = C V_2 - I_1$$

$$I_2 = \frac{C}{D} V_2 - \frac{1}{D} I_1$$

$$I_2 = -\frac{1}{D} I_1 + \frac{C}{D} V_2 \quad \text{--- (5)}$$

Compare (2) & (5)

$$h_{21} = -\frac{1}{D} \quad h_{22} = \frac{C}{D}$$

Sub eqn (5) in (3)

$$V_1 = A V_2 - B \left( -\frac{1}{D} I_1 + \frac{C}{D} V_2 \right)$$

$$V_1 = \left( A - \frac{BC}{D} \right) V_2 + \frac{B}{D} I_1$$

$$V_1 = \frac{B}{D} I_1 + \left( \frac{AD - BC}{D} \right) V_2$$

$$V_1 = \frac{B}{D} I_1 + \frac{\Delta T}{D} V_2 \quad \text{--- (6)}$$

(1) & (6):

$$h_{11} = \frac{B}{D}$$

$$h_{12} = \frac{\Delta T}{D}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = AD - BC$$

Series Connection of two ports!

cascade connection of two port networks.

(show that resultant ABCD matrix of cascade connection is the product of individual ABCD matrix).

The transmission parameters A, B, C and D are useful in describing two-port n/w's which are connected in cascade.

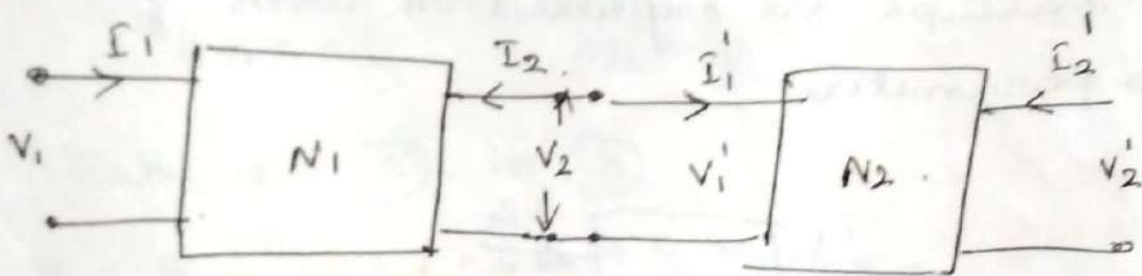


Fig shows 2 port n/w's connected in cascade. In the cascade connection the o/p port of the first network becomes the i/p port of the second n/w.

Here  $I_1' = -I_2$ .

Let  $A_1, B_1, C_1, D_1$  be the transmission parameters of n/w  $N_1$

and  $A_2, B_2, C_2$  and  $D_2$  be the transmission parameters of the n/w  $N_2$

W.K.T ABCD parameters are given as

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

Expressing this in matrix form for  $N_1$ .

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} \quad \text{--- (1)}$$

$$\begin{bmatrix} V_1' \\ I_1' \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix} \quad \text{--- (2)}$$

since  $V_1' = V_2$  &  $I_1' = -I_2$ .

$$\begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix} \quad \text{--- (3)}$$

put (3) in (1).

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix}$$

$$\text{hence } \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$


This eqn shows that the resultant ABCD matrix of cascade connection is the product of individual ABCD matrices.

Two ports are said to be connected in cascade, if o/p port of one is i/p port for the second.

This connection is also called as Tandem connection. This can be conveniently studied by ABCD parameters.
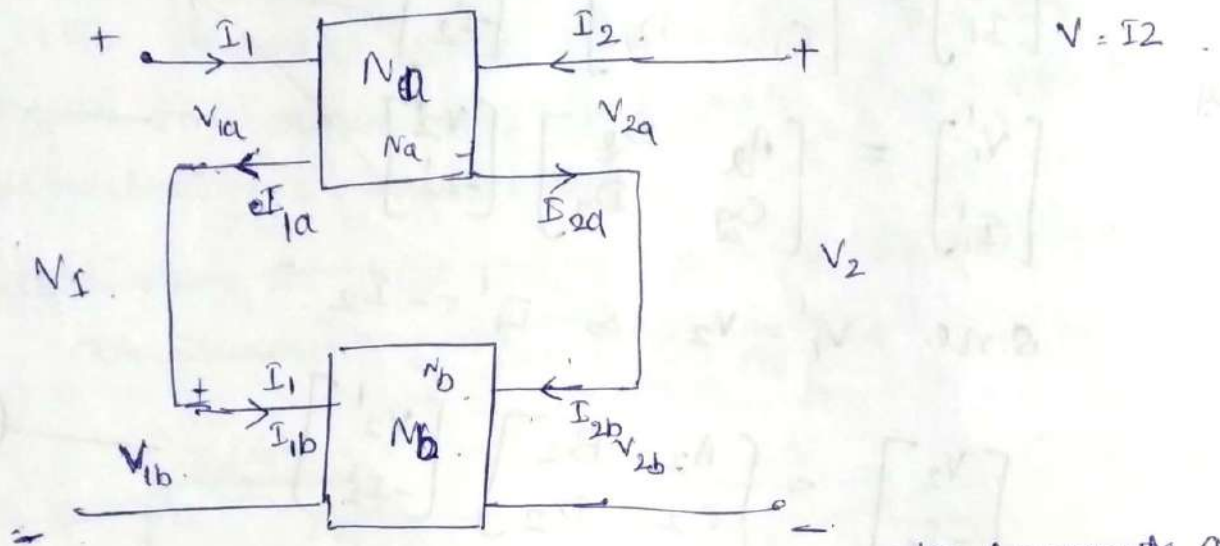
## Series Connection of 2 ports:

Two two port networks  $N_a$  and  $N_b$  are said to be connected in series if corresponding ports are connected in series.



In this connection, the i/p & o/p currents at the corresponding ports are forced to be the same. The overall port  $V$ 's are equal to the sum of the corresponding port  $V$ 's of the individual 2 ports.

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} + \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix}$$

$$\begin{aligned} V_1 &= V_{1a} + V_{1b} \\ V_2 &= V_{2a} + V_{2b} \\ &= \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} + \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix} \end{aligned}$$

$$= \begin{bmatrix} Z_{11a} & Z_{12a} \\ Z_{21a} & Z_{22a} \end{bmatrix} \begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} + \begin{bmatrix} Z_{11b} & Z_{12b} \\ Z_{21b} & Z_{22b} \end{bmatrix} \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix}$$


But  $I_{1a} = I_{1b} = I_1$  &  $I_{2a} = I_{2b} = I_2$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11a} + Z_{11b} & Z_{12a} + Z_{12b} \\ Z_{21a} + Z_{21b} & Z_{22a} + Z_{22b} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


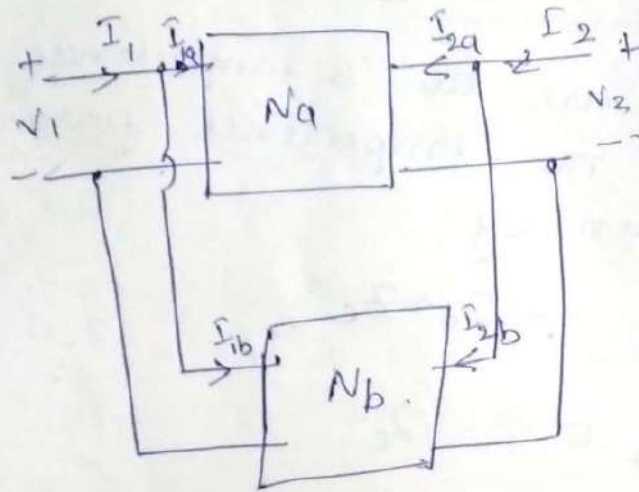
## parallel Connection of 2 ports:

Two 2 port n/w's are said to be connected in parallel, if the corresponding ports are connected in parallel as shown in fig.



In this connection the i/p & o/p v/s of the corresponding ports are forced to be the same. The overall port currents are equal to the sum of the corresponding port currents at the individual 2 ports.


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} + \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix}$$

$$= \begin{bmatrix} Y_{11a} & Y_{12a} \\ Y_{21a} & Y_{22a} \end{bmatrix} \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} + \begin{bmatrix} Y_{11b} & Y_{12b} \\ Y_{21b} & Y_{22b} \end{bmatrix} \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix}$$

But  $V_{1a} = V_{1b} = V_1$  &  
 $V_{2a} = V_{2b} = V_2$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11a} + Y_{11b} & Y_{12a} + Y_{12b} \\ Y_{21a} + Y_{21b} & Y_{22a} + Y_{22b} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

T section repn of 2 port n/w.

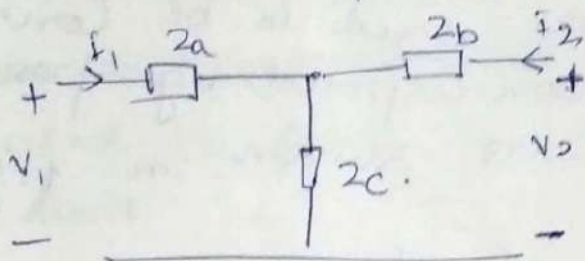

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$Z_a$ ,  $Z_b$  &  $Z_c$  are the 3 impedances connected as a T n/w. The impedance parameters for the n/w are given by.

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = Z_a + Z_c$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = Z_c$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = Z_c$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = Z_b + Z_c$$

$$Z_a I_1 + Z_c (I_1 + I_2) = V_1$$

$$Z_a I_1 + Z_c I_1 = V_1$$

$$Z_a I_1 + Z_c I_1 = V_1$$

$$(Z_a + Z_c) I_1 = V_1$$

$$V_2 = Z_b I_2 + Z_c (I_1 + I_2)$$

$$V_1 = I_1 Z_c$$

$$V_2 = I_2 Z_c + I_2 Z_b$$

$$\frac{V_2}{I_2} = ?$$

[T] T in terms of Z

$$A = \frac{Z_{11}}{Z_{21}}$$

$$B = \frac{\Delta Z}{Z_{21}}$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

$$C = \frac{1}{Z_{12}}$$

$$D = \frac{Z_{22}}{Z_{21}}$$

$$A = \frac{Z_{11}}{Z_{21}} = \frac{Z_a + Z_c}{Z_c} = 1 + \frac{Z_a}{Z_c} = 1 + Z_a Y_c$$

$$B = \frac{\Delta Z}{Z_{21}} = \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{21}} = \frac{(Z_a + Z_c)(Z_b + Z_c) - Z_c^2}{Z_c}$$

$$\frac{Z_a Z_b + Z_c Z_b + Z_a Z_c + Z_c^2 - Z_c^2}{Z_c}$$

$$= Z_a + Z_b + \frac{Z_a Z_b}{Z_c}$$

$$= Z_a + Z_b + Z_a Z_b Y_c$$

$$C = \frac{1}{Z_{12}} = \frac{1}{Z_c} = Y_c$$

$$D = \frac{Z_{22}}{Z_{21}} = \frac{Z_b + Z_c}{Z_c} = 1 + \frac{Z_b}{Z_c} = 1 + Z_b Y_c$$

Conversely

$$A = 1 + z_a Y_c \Rightarrow A - 1 = z_a Y_c = z_a C$$

$$\therefore z_a = \frac{A-1}{C}$$

$$D = 1 + z_b Y_c$$

$$D - 1 = z_b Y_c = z_b C$$

$$\therefore z_b = \frac{D-1}{C}$$

$$\& z_c = \frac{1}{Y_c} = C$$

⊙

⊙

To show that  $AD - BC = 1$

$$AD - BC = (1 + z_a Y_c)(1 + z_b Y_c) - (z_a + z_b + z_a z_b Y_c)$$

$$= 1 + z_a Y_c + z_b Y_c - z_a Y_c + z_b Y_c - z_a z_b Y_c$$

$$= 1 + \cancel{z_a z_b Y_c} + \cancel{z_a z_b Y_c}$$

$$= 1$$


(2)

$$C = \frac{1}{z_b} = Y_c$$

Reciprocal & Symmetrical n/w's:

Reciprocal n/w:-

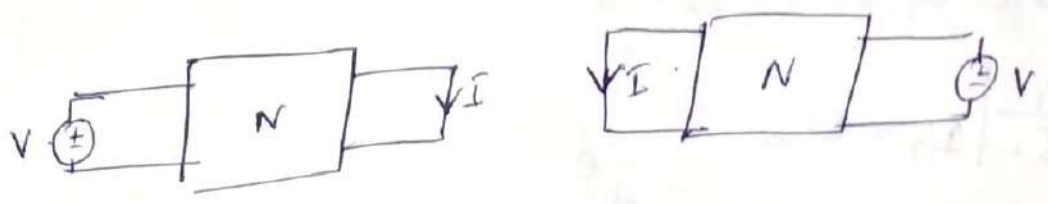Any 2 port n/w in which, the ratio of response to the excitation remains constant, when the positions of excitation & response are interchanged. Such n/w is called a reciprocal n/w.



$Z_{12} = Z_{21}$   
 $Y_{12} = Y_{21}$



Symmetrical n/w's:

A 2 port n/w is said to be symmetrical if n/w characteristics are not changed whenever the 2 ports are interchanged. The condition for symmetry in terms of Z parameters

$Z_{11} = Z_{22}$


in terms of Y parameters

$Y_{11} = Y_{22}$

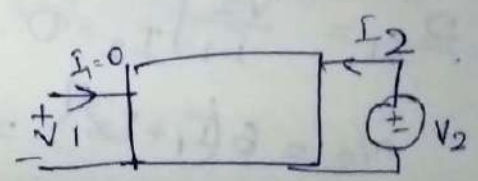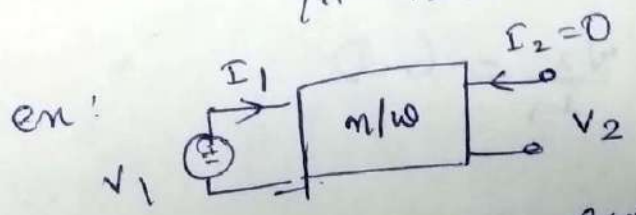

if impedance measured at one port is equal to the impedance measured at the other port with the remaining port open ckted.

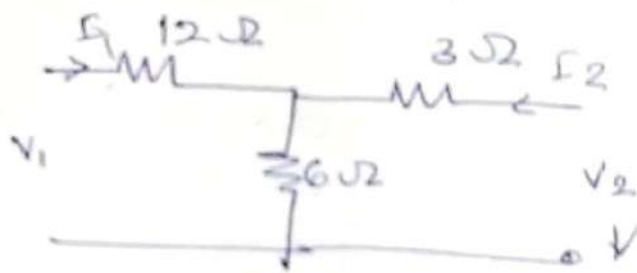1. Find the 2 parameters for the circuit shown.



$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$V_1 = 12I_1 + 6(I_1 + I_2)$$

$$V_1 = 18I_1 \Rightarrow \frac{V_1}{I_1} = 18\Omega$$

$$\boxed{Z_{11} = 18\Omega}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$V_1 = 12I_2 + 6(I_2)$$

$$V_1 = 6I_2 \Rightarrow \frac{V_1}{I_2} = 6\Omega$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$V_2 = 6(I_1) \Rightarrow \frac{V_2}{I_1} = 6\Omega$$


$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

$$V_2 = 3I_2 + 6(I_2)$$

$$V_2 = 9I_2 \Rightarrow \frac{V_2}{I_2} = 9\Omega$$

Z parameters:


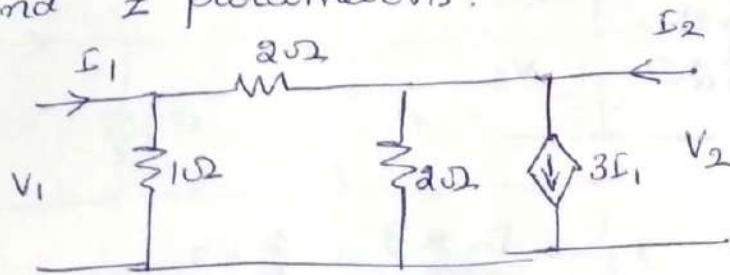
1) The n/w shown in fig contains controlled current source. Find Z parameters.



$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad \& \quad Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

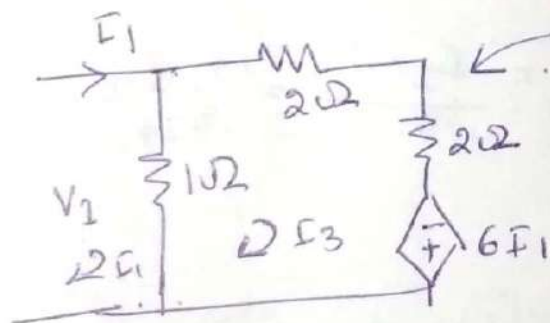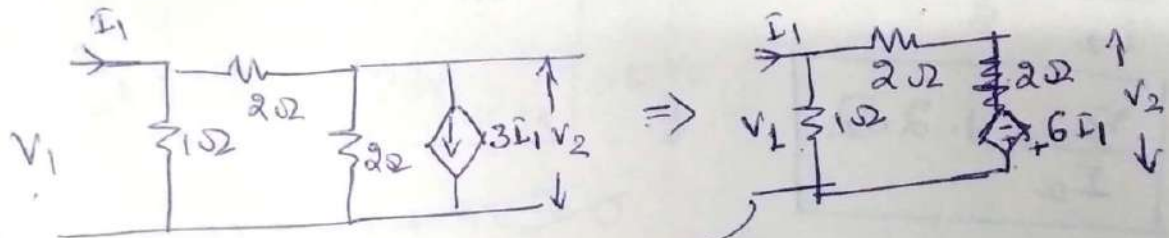

$$V_1 = 1(I_1 - I_3)$$

$$\& \quad 4I_3 - 6I_1 + I_3 - I_1 = 0$$

$$V_1 = I_1 - \frac{7}{5} I_1$$

$$5I_3 = 7I_1$$


$$I_3 = \frac{7}{5} I_1$$

$$V_1 = -\frac{2}{5} I_1$$

$$\frac{V_1}{I_2} = -\frac{2}{5} = -0.4 \Omega$$

$$\frac{V_1}{I_2} = -0.4 \Omega$$

$$6 \quad Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} \quad \& \quad Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

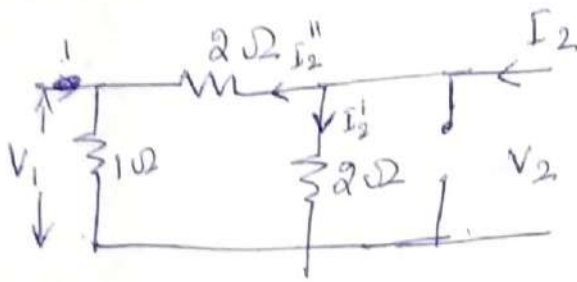

$$V_2 = 2 I_2'$$

$$\& \quad I_2' = \frac{I_2 \times 3}{5} = \frac{3}{5} I_2$$

$$= 2 \frac{3}{5} I_2$$

$$V_2 = \frac{6}{5} I_2$$

$$\frac{V_2}{I_2} = \frac{6}{5} = 1.2$$

$$\boxed{\frac{V_2}{I_2} = 1.2 \Omega}$$

$$V_1 = 1 I_2''$$

$$V_1 = \frac{2}{5} I_2$$

$$\frac{V_1}{I_2} = \frac{2}{5}$$


$$\boxed{\frac{V_1}{I_2} = 0.4 \Omega}$$

$$I_2'' = \frac{I_2 \times 2}{5} = \frac{2}{5} I_2$$

(2)

Find 2 parameters for the n/w shown which contains a controlled V<sub>g</sub> source.

31

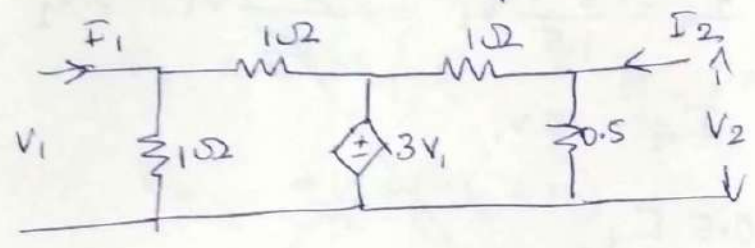


$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

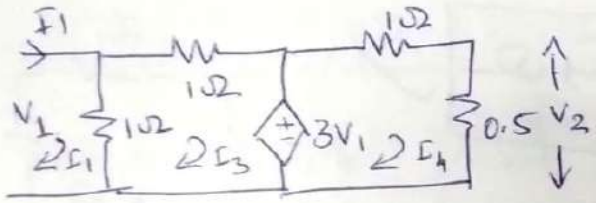

$$V_1 = (I_1 - I_3) \cdot 10 + I_3 \cdot 10 + 3V_1 = 0$$

(1) loop

$$V_1 = I_1 - I_3$$

(1)

$$-I_1 + I_3 + I_3 + 3V_1 = 0 \Rightarrow -I_1 + 2I_3 + 3V_1 = 0$$

(2) loop

$$2I_3 = -3V_1 + I_1$$

$$I_3 = -\frac{3}{2} V_1 + \frac{1}{2} I_1 \quad (2)$$

sub (2) in (1)

$$V_1 = I_1 - \left(-\frac{3}{2} V_1 + \frac{1}{2} I_1\right)$$

$$V_1 = I_1 + \frac{3}{2} V_1 - \frac{1}{2} I_1$$

$$V_1 - \frac{3}{2} V_1 = \frac{1}{2} I_1$$

$$-\frac{1}{2} V_1 = \frac{1}{2} I_1$$

$$\boxed{\frac{V_1}{I_1} = -1 \Omega}$$



3<sup>rd</sup> loop

32  
12

$$1.5 I_4 - 3V_1 = 0.$$

$$1.5 I_4 = 3V_1.$$

$$I_4 = \frac{3}{1.5} V_1 = \frac{3}{\frac{3}{2}} V_1 = 2V_1$$

$$I_4 = 2V_1$$

$$V_2 = 0.5 I_4$$

$$V_2 = 0.5 (2V_1)$$


$$V_2 = V_1.$$

$$\Delta \quad V_1 = -I_1$$

$$V_2 = -I_1$$

$$\boxed{\frac{V_2}{I_1} = -1 \Omega} \quad \checkmark$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} \quad \& \quad Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

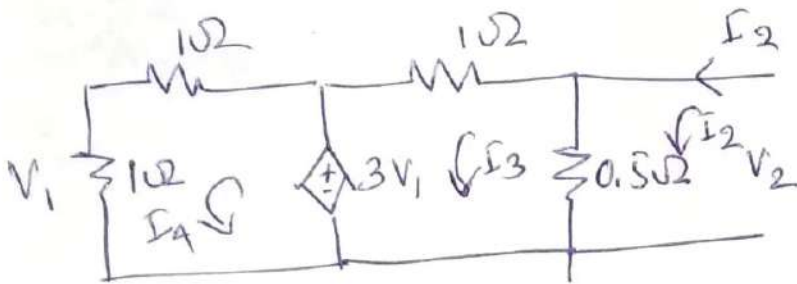

$$V_1 = I_4$$

$$2I_4 - 3V_1 = 0 \Rightarrow 2I_4 - 3I_4 = 0 \Rightarrow I_4 = 0$$

$$\therefore I_4 = V_1 = 0$$

$$I_3 + 3V_1 + 0.5(I_3 - I_2) = 0$$

$$I_3 + 3V_1 + 0.5I_3 - 0.5I_2 = 0$$

$$1.5I_3 = 0.5I_2 \Rightarrow I_3 = \frac{0.5}{1.5} I_2$$

$$I_3 = \frac{1/2}{3/2} I_2$$

$$I_3 = \frac{1}{3} I_2$$

$$\boxed{Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = \frac{I_4}{I_2} = 0}$$

$$V_2 = 0.5 (I_2 - I_3)$$


$$8 \quad V_2 = 0.5 \left[ I_2 - \frac{1}{3} I_2 \right]$$

$$V_2 = \frac{1}{2} \left[ \frac{2}{3} I_2 \right]$$

$$\boxed{\frac{V_2}{I_2} = \frac{1}{3} \Omega} \quad \checkmark$$

then solve:

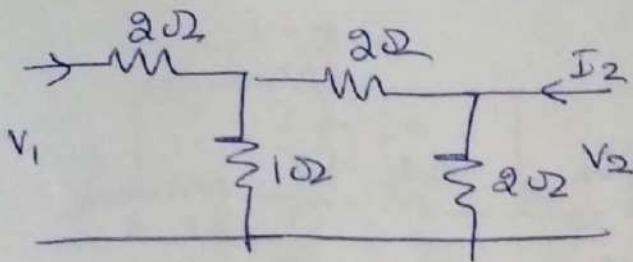Determine the 2 parameters of ckt shown. (4)




29

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

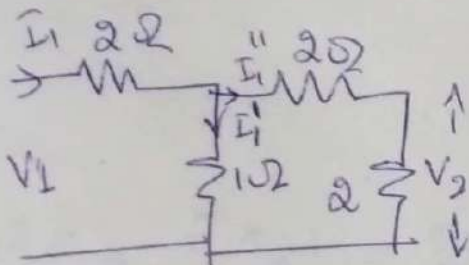

$$V_1 = 2I_1 + I_1'$$

$$I_1' = \frac{I_1 \times 4}{5} = \frac{4I_1}{5}$$

$$V_1 = 2I_1 + \frac{4}{5}I_1$$

$$V_1 = \frac{14}{5}I_1$$

$$\frac{V_1}{I_1} = \frac{14}{5} \Omega \checkmark$$

$$\frac{V_1}{I_1} = 2.8 \Omega$$

$$V_2 = 2I_1''$$

$$I_1'' = \frac{I_1 \times 1}{5} = \frac{1}{5}I_1$$


$$V_2 = 2 \times \frac{1}{5}I_1 = \frac{2}{5}I_1$$

$$\frac{V_2}{I_1} = \frac{2}{5} \Omega \checkmark$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

30

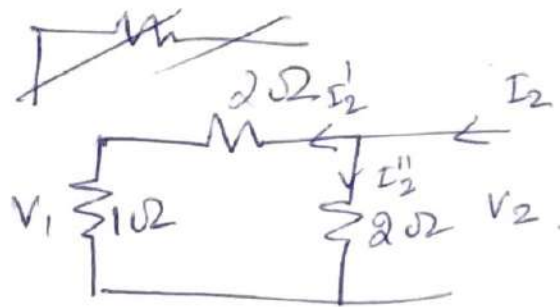

$$V_1 = I_2'$$

$$I_2' = \frac{I_2 \times 2}{5} = \frac{2}{5} I_2$$

$$V_1 = \frac{2}{5} I_2$$

$$\boxed{\frac{V_1}{I_2} = \frac{2}{5} \Omega}$$

$$V_2 = 2 I_2''$$

$$\& \quad I_2'' = \frac{I_2 \times 3}{5} = \frac{3}{5} I_2$$


$$V_2 = 2 \frac{3}{5} I_2$$

$$V_2 = \frac{6}{5} I_2$$

$$\boxed{\frac{V_2}{I_2} = \frac{6}{5} \Omega}$$

Find Z parameters for the n/w shown


11

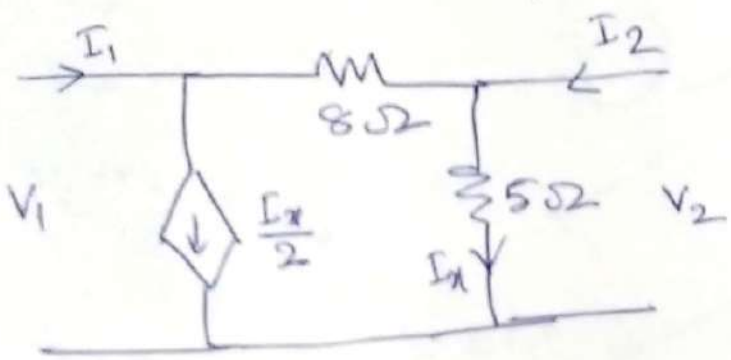

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

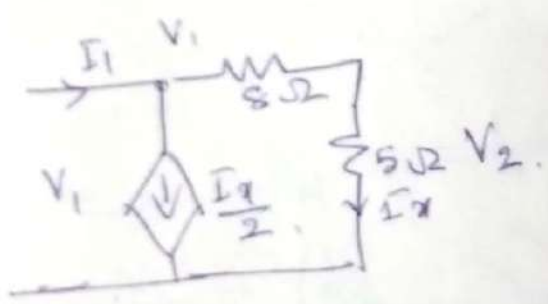

$$I_x = I_1 - \frac{I_x}{2} \Rightarrow I_x + \frac{I_x}{2} = I_1$$

$$\frac{3I_x}{2} = I_1$$

$$I_x = \frac{2}{3} I_1$$

$$V_1 = (8 + 5) I_x$$

$$V_1 = 13 I_x$$

$$V_1 = 13 \left( \frac{2}{3} \right) I_1$$

$$V_2 = 5 I_x$$

$$V_2 = 5 \left( \frac{2}{3} \right) I_1$$


$$V_2 = \frac{10}{3} I_1$$

$$\boxed{\frac{V_1}{I_1} = \frac{26}{3} \Omega}$$

$$\boxed{\frac{V_2}{I_1} = \frac{10}{3} \Omega}$$

$$Z_{11} = Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

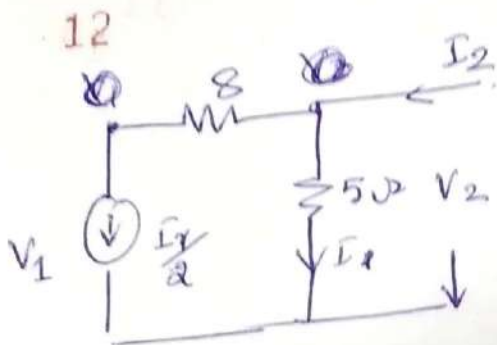

$$I_x = I_2 - \frac{I_x}{2} \Rightarrow$$

$$I_x + \frac{I_x}{2} = I_2$$


$$\frac{3I_x}{2} = I_2 \Rightarrow I_x = \frac{2}{3} I_2$$

$$V_2 = 5 I_x$$

$$V_2 = 5 \cdot \frac{2}{3} I_2$$

$$V_2 = \frac{10}{3} I_2$$
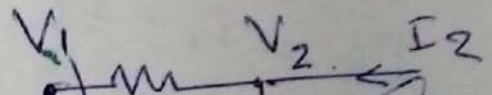
$$\boxed{\frac{V_2}{I_2} = \frac{10}{3} \Omega}$$



$$\frac{V_2}{I_2} = \frac{10}{3} \quad \checkmark$$

$$V_2 = \frac{10}{3} I_2 \quad \text{--- (1) } \checkmark$$

$$\frac{V_1 - V_2}{8} + \frac{I_2}{2} = 0 \quad \checkmark$$

$$\frac{V_1}{8} - \frac{V_2}{8} + \frac{I_2}{2} = 0 \quad \checkmark$$

25



$$\frac{V_1}{8} - \frac{\frac{10}{3} I_2}{8} + \frac{\frac{2}{3} I_2}{2} = 0 \quad \checkmark$$

$$\frac{V_1}{8} - \frac{10}{24} I_2 + \frac{2}{6} I_2 = 0 \quad \checkmark$$


$$\frac{V_1}{8} - \frac{5}{12} I_2 + \frac{1}{3} I_2 = 0$$

$$\frac{V_1}{8} = I_2 \left[ \frac{5}{12} - \frac{1}{3} \right]$$


$$\frac{V_1}{8} = I_2 \left[ \frac{5-4}{12} \right]$$

$$\frac{V_1}{8} = \frac{1}{12} I_2$$
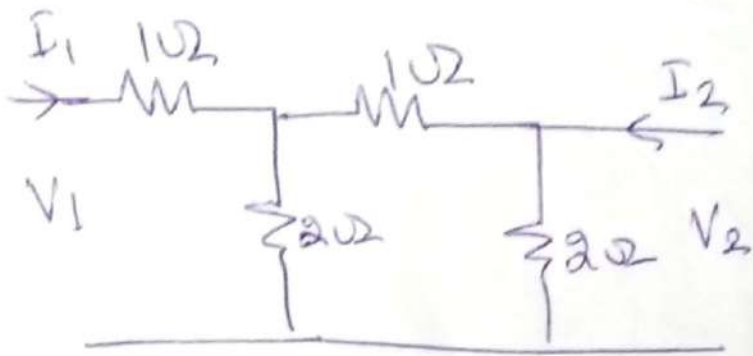
$$\left[ \frac{V_1}{I_2} = \frac{8}{12} = \frac{2}{3} \Omega \right] \quad \checkmark$$



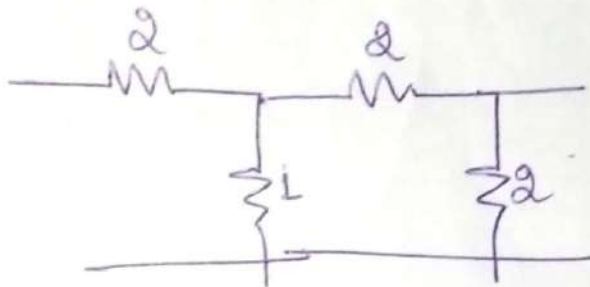ans: 
$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} \frac{11}{5} & \frac{4}{5} \\ \frac{4}{5} & \frac{6}{5} \end{bmatrix}$$



$$z_{11} = \frac{14}{5} \quad z_{12} = \frac{2}{5} \Omega$$

$$z_{21} = \frac{2}{5} \Omega \quad z_{22} = \frac{6}{5} \Omega$$

## Y parameters

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$I_1 = \frac{V_1 - V_3}{1}$$

$$I_1 = V_1 - \frac{6}{11}V_3$$

$$I_1 = \frac{5}{11}V_1$$

$$\boxed{\frac{I_1}{V_1} = \frac{5}{11}}$$



$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$I_2 = \frac{V_2 - V_3}{3}$$

$$I_2 = 0 - \frac{6}{11}V_1$$

$$3I_2 = -\frac{6}{11}V_1$$
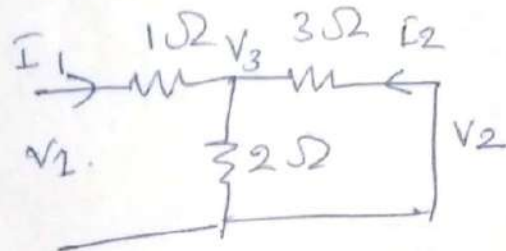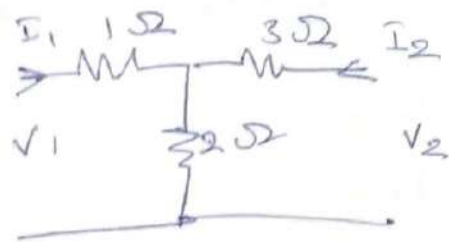
$$\boxed{\frac{I_2}{V_1} = -\frac{2}{11}}$$



$$\frac{V_3 - V_1}{1} + \frac{V_3}{2} + \frac{V_3 - V_2}{3} = 0$$

$$\left(\frac{6}{6} + \frac{1}{2} + \frac{1}{3}\right)V_3 = V_1$$

$$\left(\frac{6+3+2}{6}\right)V_3 = V_1$$

$$\frac{11}{6}V_3 = V_1$$

$$V_3 = \frac{6}{11}V_1$$

$$I_2 = \frac{V_2 - V_3}{3} = \text{⊖}$$

$$Y_{12} = \frac{\bar{I}_1}{V_2} \Big|_{V_1=0}$$

$$\bar{I}_1 = \frac{V_1 - V_3}{1\Omega}$$

$$\bar{I}_1 = -V_3$$

$$\bar{I}_1 = -\frac{2}{11}V_2$$

$$\frac{\bar{I}_1}{V_2} = -\frac{2}{11}$$

$$\bar{I}_1 = -\frac{2}{11}V_2$$

$$\frac{\bar{I}_1}{V_2} = -\frac{2}{11}$$

$$Y_{22} = \frac{\bar{I}_2}{V_2} \Big|_{V_1=0}$$

$$\bar{I}_2 = \frac{V_2 - V_3}{3\Omega}$$


$$\bar{I}_2 = \frac{V_2 - \frac{2}{11}V_2}{3} = \frac{11V_2 - 2V_2}{11 \times 3} = \frac{9V_2}{33}$$

$$3\bar{I}_2 = \frac{9}{11}V_2$$

$$33\bar{I}_2 = 9V_2$$

$$\frac{\bar{I}_2}{V_2} = \frac{9}{33} = \frac{3}{11}$$

$$Y_{22} = \frac{\bar{I}_2}{V_2} \Big|_{V_1=0}$$

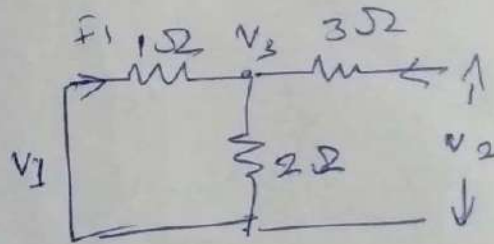

$$\frac{V_3}{2} + \frac{V_3 - V_2}{3} - \bar{I}_1 = 0$$

$$\left(\frac{1}{2} + \frac{1}{3}\right)V_3 = \frac{V_2}{3} + \bar{I}_1$$

$$\left(\frac{3+2}{6}\right)V_3 = \frac{V_2}{3} + \frac{V_1 - V_3}{1}$$

$$\frac{5}{2}V_3 = V_2$$

$$V_3 = \frac{2}{5}V_2$$


$$\left(\frac{1}{2} + \frac{1}{3} + 1\right)V_3 = \frac{V_2}{3}$$

$$\left(\frac{3+2+6}{6}\right)V_3 = \frac{V_2}{3}$$

$$\frac{11}{2}V_3 = V_2$$

$$V_3 = \frac{2}{11}V_2$$
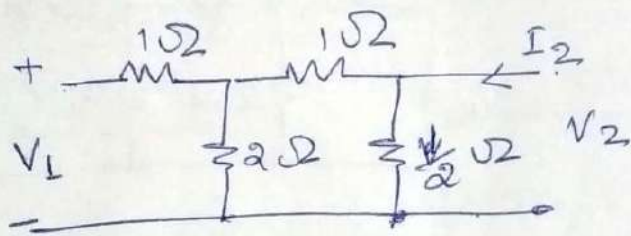
$$\frac{\bar{I}_2}{V_2} = \frac{9}{33} = \frac{3}{11}$$



$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$


$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \quad Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$I_1 = \frac{V_1 - V_3}{1}$$

$$I_1 = V_1 - \frac{2}{5}V_1$$

$$I_1 = \frac{3}{5}V_1$$
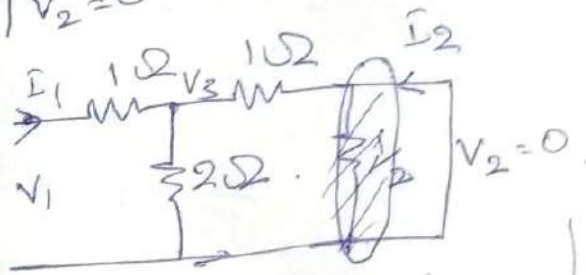
$$\frac{I_1}{V_1} = \frac{3}{5} \text{ A/V}$$



$$\frac{V_3}{2} + \frac{V_3 - V_2}{1} + \frac{V_3 - V_1}{1} = 0$$

$$\left(\frac{1}{2} + 1 + 1\right)V_3 - V_2 - V_1 = 0$$

$$\frac{5}{2}V_3 = V_1$$

$$V_3 = \frac{2}{5}V_1$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$I_2 = \frac{V_2 - V_3}{1} = 0 - \frac{2}{5}V_1$$

$$\boxed{\frac{I_2}{V_1} = -\frac{2}{5} \text{ A/V}}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$


$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

$$I_1 = \frac{V_1 - V_3}{1}$$

$$I_1 = -\frac{2}{5}V_2$$

$$\frac{I_1}{V_2} = -\frac{2}{5} \text{ A/V}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}, \quad I_2 = \frac{V_2 - V_3}{1}$$

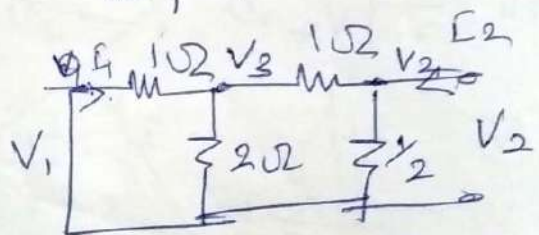


$$\frac{V_3}{2} + \frac{V_3 - V_2}{1} + \frac{V_3 - V_1}{1} = 0$$

$$\left(\frac{1}{2} + 1 + 1\right)V_3 = V_2$$

$$\frac{5}{2}V_3 = V_2$$

$$V_3 = \frac{2}{5}V_2$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

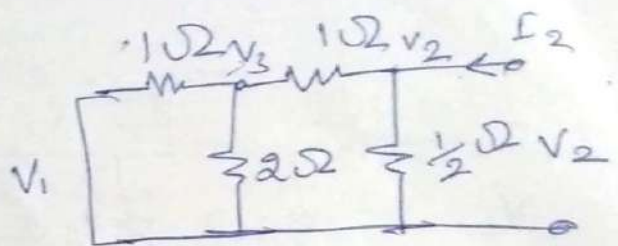

Kcl at node ②

$$\frac{V_2 - V_3}{1 \Omega} + \frac{V_2}{\frac{1}{2} \Omega} - I_2 = 0$$

$$V_2 + 2V_2 - V_3 - I_2 = 0$$

$$3V_2 - \frac{2}{5}V_2 - I_2 = 0$$


$$\frac{13}{5}V_2 = I_2$$

$$\frac{I_2}{V_2} = \frac{5}{13} \text{ V}$$

$$V_3 = \frac{2}{5}V_2$$

Learn notes

Find Y parameters

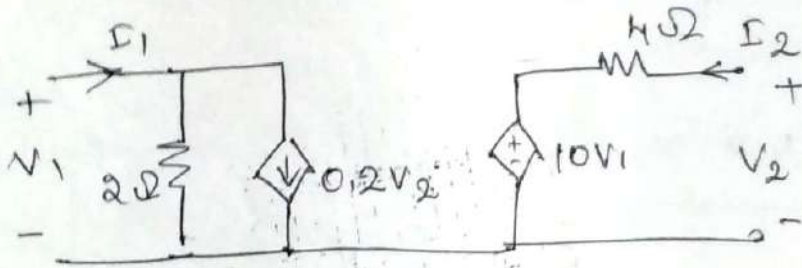


$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

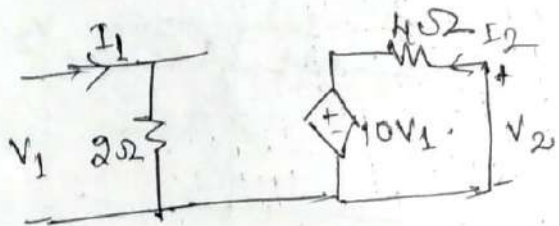


$$V_1 = 2I_1 \Rightarrow \frac{I_1}{V_1} = \frac{1}{2} = \boxed{0.5 \text{ S}}$$

$$4I_2 + 10V_1 = 0 \Rightarrow 4I_2 = -10V_1 \Rightarrow \frac{I_2}{V_1} = -\frac{10}{4}$$

$$\boxed{Y_{21} = -2.5 \text{ S}}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

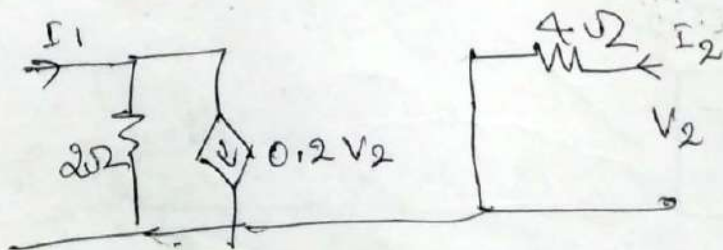


$$4I_2 = V_2 \Rightarrow \frac{I_2}{V_2} = \frac{1}{4} = \boxed{0.25 \text{ S}}$$

~~$$2I_1 = V_1 \text{ and } V_1 = 2 \times 0.2V_2$$~~

$$I_1 = 0.2V_2 \Rightarrow \boxed{\frac{I_1}{V_2} = 0.2 \text{ S}}$$

4) Y parameters ?


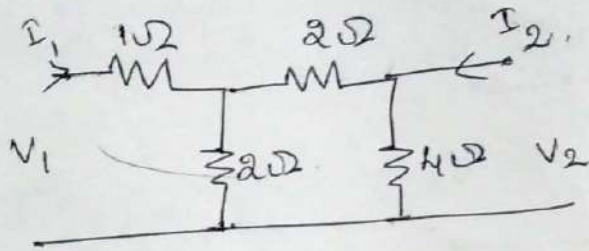


$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

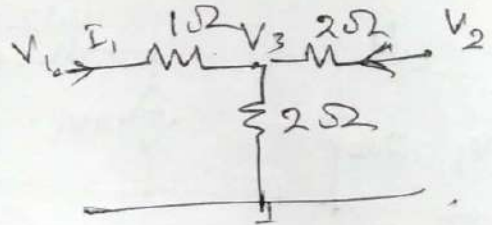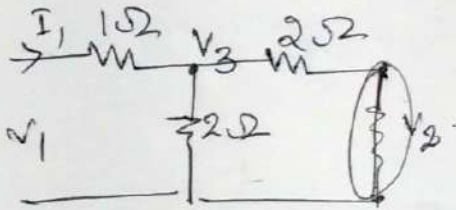

~~$V_1 = V_3$~~   $I_1 = \frac{V_1 - V_3}{1}$

$$\frac{V_3 - V_1}{1} + \frac{V_3}{2} + \frac{V_3 - V_2}{2} = 0$$

$$I_1 = V_1 - \frac{1}{2}V_1 = \frac{1}{2}V_1$$

$$\left(1 + \frac{1}{2} + \frac{1}{2}\right) V_3 = V_1$$

$$2V_3 = V_1$$

$$V_3 = \frac{1}{2}V_1$$

$$Y_{11} = \frac{I_1}{V_1} = \frac{1}{2} \text{ S}$$

$$I_2 = \frac{\frac{V_1}{2} - V_3}{2} = \frac{-\frac{1}{2}V_1}{2} = -\frac{1}{4}V_1$$


$$\frac{I_2}{V_1} = -\frac{1}{4} \text{ S}$$



(7)

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

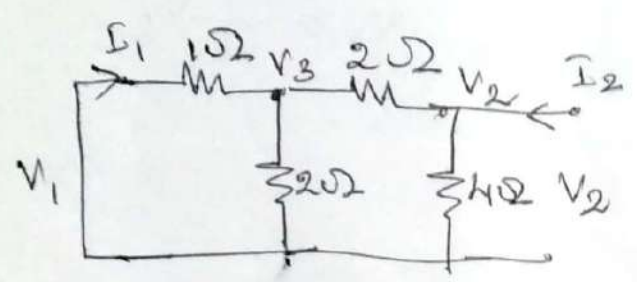

$$I_1 = \frac{V_1 - V_3}{1} = -V_3$$

$$I_1 = -\frac{1}{4} V_2$$


$$\boxed{\frac{I_1}{V_2} = -\frac{1}{4} \Omega}$$

$$\frac{V_3}{1} + \frac{V_3}{2} + \frac{V_3 - V_2}{2} = 0$$

$$\left(1 + \frac{1}{2} + \frac{1}{2}\right) V_3 = \frac{1}{2} V_2$$

$$2 V_3 = \frac{1}{2} V_2$$

$$V_3 = \frac{1}{4} V_2$$

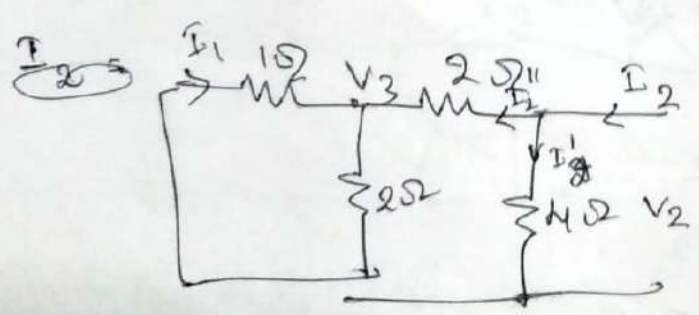

next page.

$$\frac{V_2 - V_3}{2} + \frac{V_2}{4} - I_2 = 0.$$

$$\frac{3}{4}V_2 - \frac{1}{2}V_3 = I_2$$

$$V_3 = \frac{1}{4}V_2$$


$$\frac{3}{4}V_2 - \frac{1}{2} \cdot \frac{1}{4}V_2 = I_2$$

$$\frac{3}{4}V_2 - \frac{1}{8}V_2 = I_2$$

$$\left(\frac{3}{4} - \frac{1}{8}\right)V_2 = I_2$$

$$\left(\frac{6-1}{8}\right)V_2 = I_2$$
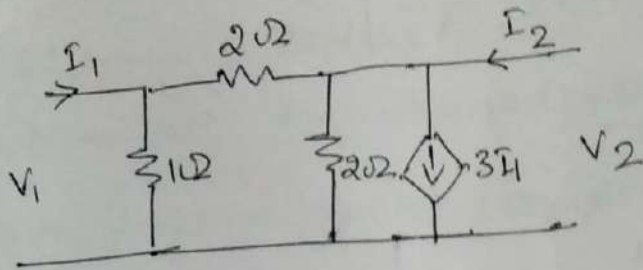
$$\Rightarrow \boxed{\frac{I_2}{V_2} = \frac{5}{8} \text{ } \Omega}$$





$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

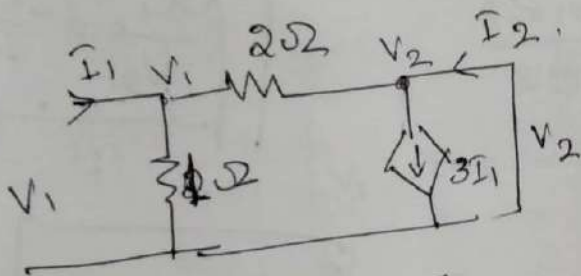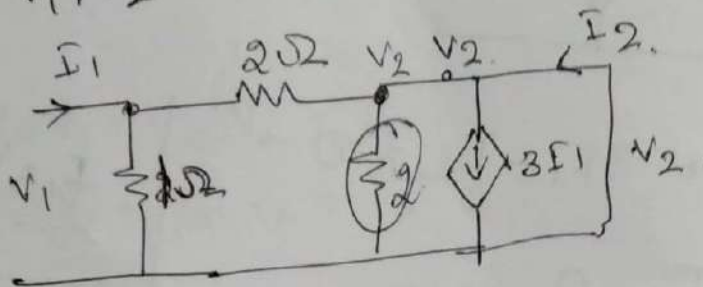

$$-I_1 + \frac{V_1}{1} + \frac{V_1 - V_2}{2} = 0$$

$$-I_1 + \frac{3}{2}V_1 = 0$$

$$I_1 = \frac{3}{2}V_1 \Rightarrow$$

$$\boxed{\frac{I_1}{V_1} = \frac{3}{2}}$$

$$\frac{V_2 - V_1}{2} + \frac{V_2}{2} + 3I_1 - I_2 = 0$$

$$-\frac{V_1}{2} + 3\left(\frac{3}{2}V_1\right) - I_2 = 0$$



$$-\frac{1}{2}V_1 + \frac{9}{2}V_1 - I_2 = 0$$

$$\frac{4}{2}V_1 = I_2$$

$$\boxed{\frac{I_2}{V_1} = 2}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

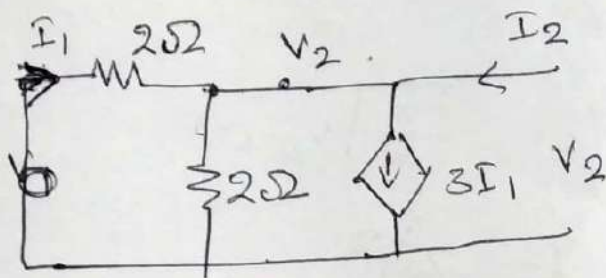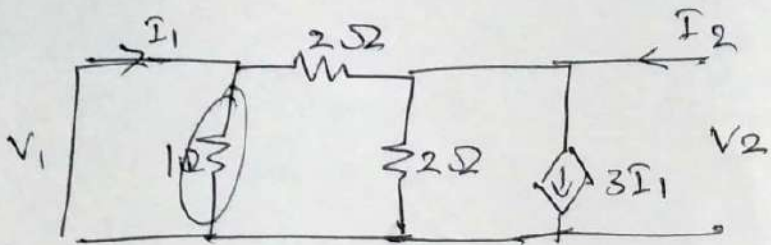

$$\frac{V_2}{2} + \frac{V_2 - V_1}{2} + 3I_1 - I_2 = 0$$

$$V_2 + 3I_1 - I_2 = 0$$

$$V_2 + 3\left(-\frac{1}{2}V_2\right) - I_2 = 0$$

$$V_2 - \frac{3}{2}V_2 = I_2$$

$$-\frac{1}{2}V_2 = I_2 \Rightarrow$$

$$\boxed{\frac{I_2}{V_2} = -\frac{1}{2}}$$

$$I_1 = \frac{V_1 - V_2}{2} = -\frac{1}{2}V_2$$

$$\boxed{\frac{I_1}{V_2} = -\frac{1}{2}}$$

(Jan 2015 6M) ⑥

3) Following short circuit currents and voltages are obtained experimentally for a two port n/w.

i. with output short circuited,  $I_1 = 5 \text{ mA}$ ,  $I_2 = -0.3 \text{ mA}$   
&  $V_1 = 25 \text{ V}$ .

ii) with i/p short circuited,  $I_1 = -5 \text{ mA}$ ,  $I_2 = 10 \text{ mA}$ ,  
 $V_2 = 30 \text{ V}$

Determine y parameters

$$Y_{11}V_1 + Y_{12}V_2 = I_1$$

$$Y_{21}V_1 + Y_{22}V_2 = I_2$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{5 \times 10^{-3}}{25} = 0.2 \times 10^{-3} \text{ S}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{-0.3 \times 10^{-3}}{25} = -0.012 \times 10^{-3} \text{ S}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = -0.01667 \times 10^{-3} \text{ S}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = 0.333 \times 10^{-3} \text{ S}$$

4) The z parameters of a two port n/w are  $Z_{11} = 20 \Omega$ ,  
 $Z_{22} = 30 \Omega$ ,  $Z_{12} = Z_{21} = 10 \Omega$ . Find y and ABCD  
parameters of the n/w.

y in terms of z.

ABCD in terms of z.

$$Y_{11} = \frac{Z_{22}}{\Delta Z} = \frac{Z_{22}}{Z_{11}Z_{22} - Z_{12}Z_{21}} = \frac{30}{20 \times 30 - 10 \times 10} = \frac{30}{500} \text{ S}$$

$$Y_{22} = \frac{Z_{11}}{\Delta Z} = \frac{20}{500} = 0.04 \text{ S}$$

$$Y_{12} = -\frac{Z_{12}}{A_2} = \frac{-10}{500} = -0.01 \text{ V} = Y_{21}$$

$$ii) \quad A = \frac{Z_{11}}{Z_{21}} = \frac{20}{10} = 2.$$

$$B = -\frac{A_2}{Z_{21}} = -\frac{500}{10} = -50 \Omega$$

$$C = \frac{1}{Z_{11}} = \frac{1}{10} = 0.1 \text{ V}.$$

$$D = \frac{Z_{22}}{Z_{21}} = 3.$$

For the network shown in Fig.7.14, find y and z parameters. (Karnataka University)

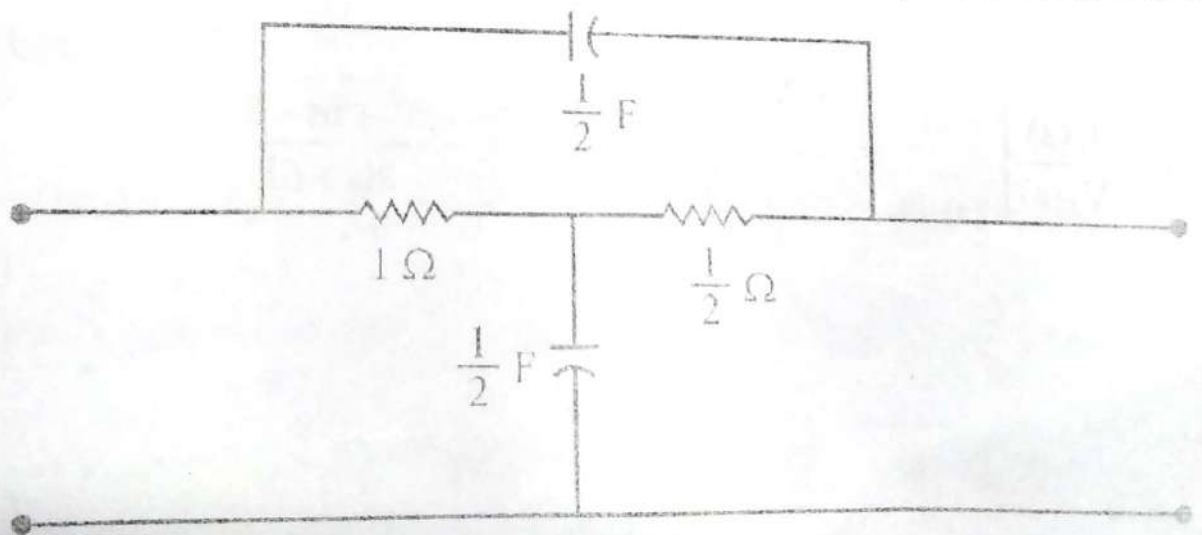


Fig. 7.14

**Solution:**

The transformed network is as shown in Fig.1.

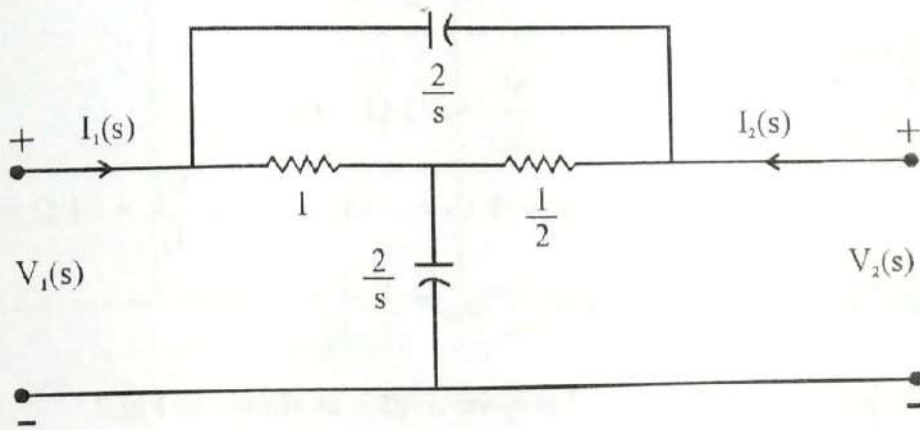


Fig. 1

Converting the star network into delta and simplifying, the network in Fig.1 can be written as in Fig.2.

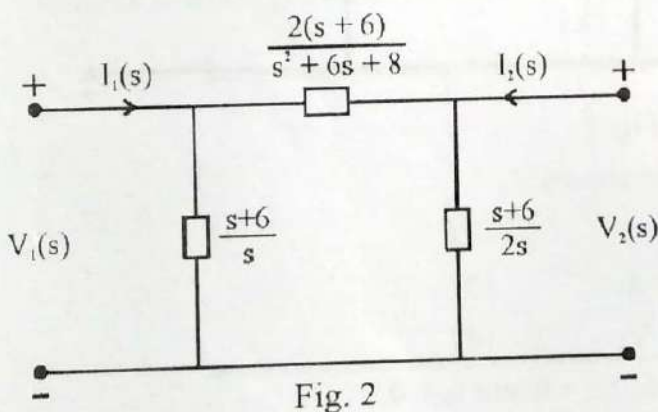


Fig. 2

$$y_{11}(s) = \left. \frac{I_1(s)}{V_1(s)} \right|_{V_2(s)=0}$$

$$= \frac{s^2 + 6s + 8}{2(s+6)} + \frac{s}{s+6} = \frac{s^2 + 8s + 8}{2(s+6)}$$

$$y_{21}(s) = \left. \frac{I_2(s)}{V_1(s)} \right|_{V_2(s)=0}$$

$$= \frac{-V_1(s) \frac{s^2 + 6s + 8}{2(s+6)}}{V_1(s)} = -\frac{s^2 + 6s + 8}{2(s+6)}$$

$$y_{22}(s) = \left. \frac{I_2(s)}{V_2(s)} \right|_{V_1(s)=0} = \frac{s^2 + 6s + 8}{2(s+6)} + \frac{2s}{s+6} = \frac{s^2 + 10s + 8}{2(s+6)}$$

$$y_{12}(s) = \left. \frac{I_1(s)}{V_2(s)} \right|_{V_1(s)=0} = \frac{-V_2(s) \frac{s^2 + 6s + 8}{2(s+6)}}{V_2(s)} = -\frac{s^2 + 6s + 8}{2(s+6)}$$



7.12 Define Z parameters. Determine Z parameters for the network shown in Fig. 7.22. (June/July 2011) (10 marks)

Soln.:  $Z_{11}I_1 + Z_{12}I_2 = V_1$  ,  $Z_{21}I_1 + Z_{22}I_2 = V_2$

$$\therefore Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = 0, \quad Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = 0, \quad Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

Converting the star network of 1 Ω, 2 Ω and 5 Ω into delta and simplifying further, the N.W in fig. 7.22 may be written as in Fig. 1.

When  $I_2 = 0$

$$Z_{11} = \frac{V_1}{I_1} = \frac{17 \times \left( \frac{51}{32} + 17 \right)}{\frac{17}{2} + \frac{51}{32} + 17} = \frac{10,115}{1,734} = \frac{35}{6} \Omega$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{17 \times \left( \frac{51}{32} + \frac{17}{2} \right)}{17 + \frac{51}{32} + \frac{17}{2}} = \frac{19}{3} \Omega$$

$$\text{When } I_2 = 0, \quad I_{17\Omega} = \frac{I_1 \times \frac{17}{2}}{\frac{17}{2} + \frac{51}{32} + 17} = \frac{17}{867} I_1 = \frac{272}{867} I_1$$

$$\therefore V_2 = 17 \times I_{17\Omega} = 17 \times \frac{272}{867} I_1, \quad \therefore Z_{21} = \frac{V_2}{I_1} = \frac{17 \times 272}{867} = \frac{16}{3} \Omega = Z_{12}$$

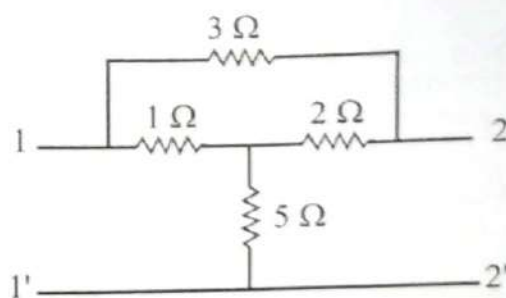


Fig. 7.22

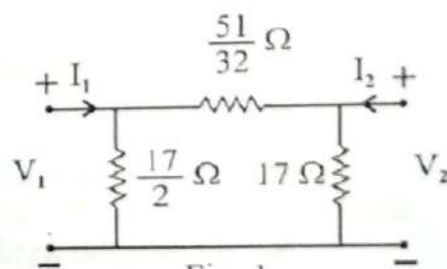


Fig. 1

Fig. 7.32

2 Find the y parameters for the network shown in Fig. 7.33 (Karnataka University)

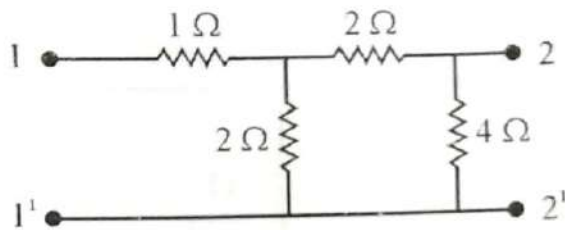


Fig. 7.33

3 Find z parameters for the network shown in Fig. 7.34. (Mysore University)

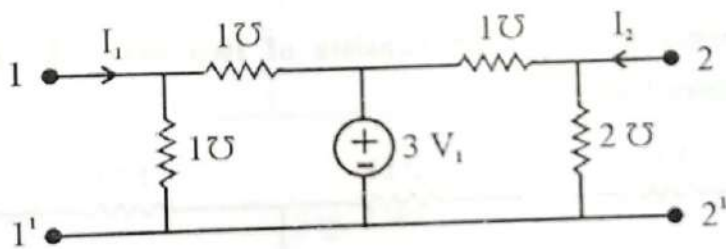


Fig. 7.34

4 Find y parameters for the network shown in Fig. 7.35. (Kuvempu University)

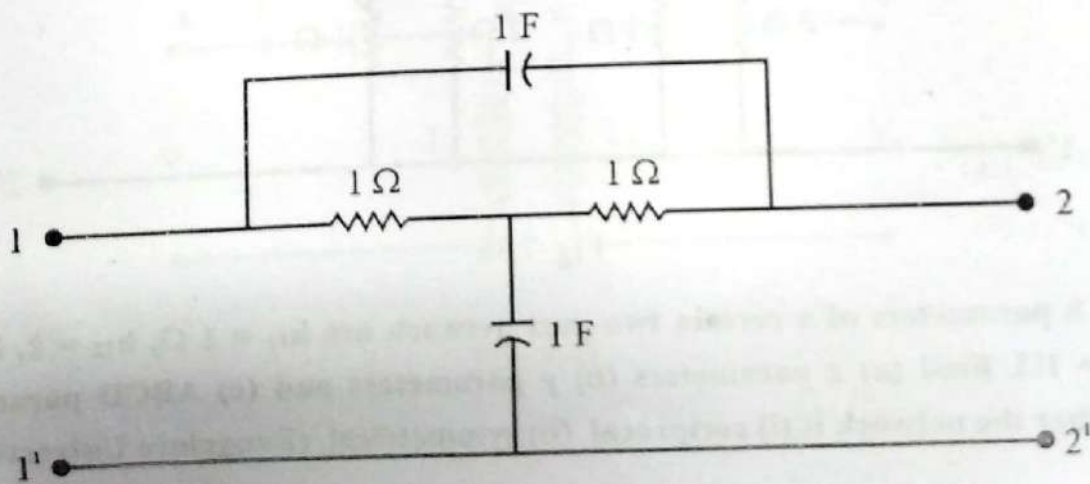


Fig. 7.35

7.2  $y_{11} = 0.5 \text{ } \Omega$ ,  $y_{12} = y_{21} = -0.25 \text{ } \Omega$ ,  $y_{22} = 0.625 \text{ } \Omega$

7.3  $z_{11} = z_{21} = -1 \text{ } \Omega$ ,  $z_{12} = 0 \text{ } \Omega$ ,  $z_{22} = \frac{1}{3} \text{ } \Omega$

7.4  $y_{11}(s) = y_{22}(s) = \frac{s^2 + 3s + 1}{s + 2}$ ,  $y_{12}(s) = y_{21}(s) = -\frac{s^2 + 2s + 1}{s + 2}$

1


h parameters:  $V_1, I_2$  depend

①

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

1) Find h parameters of the n/w shown.

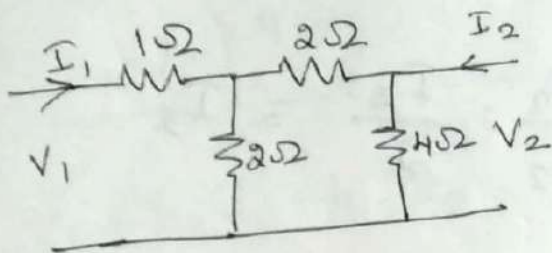


$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

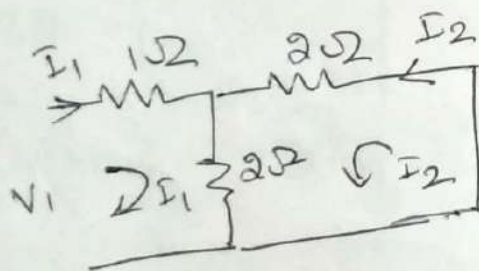

$$V_1 = I_1 + 2(I_1 + I_2)$$

$$V_1 = 3I_1 + 2I_2$$

$$V_1 = 3I_1 + 2\left(-\frac{I_1}{2}\right)$$

$$V_1 = 3I_1 - I_1$$

$$V_1 = 2I_1$$

$$\boxed{\frac{V_1}{I_1} = 2 \Omega}$$

$$4I_2 + 2I_1 = 0$$

$$I_1' = \frac{I_1 \times 2}{4} = \frac{I_1}{2}$$


$$I_1' = I_1'' = \frac{I_1}{2}$$

$$I_2 = -\frac{I_1}{2}$$

$$\therefore \boxed{\frac{I_2}{I_1} = -\frac{1}{2}}$$

$I_1'$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} \quad \& \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

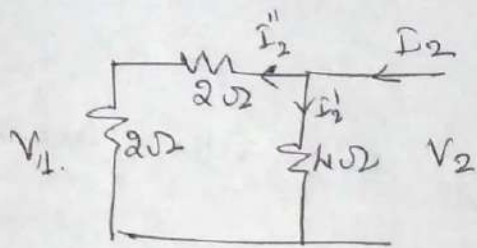

$$I_2'' = \frac{I_2 \times 4}{4 + 4} = \frac{4I_2}{8} = \frac{I_2}{2} = I_2'$$

$$V_2 = 4I_2'$$

$$V_2 = 4 \frac{I_2}{2} = 2I_2$$

$$\boxed{\frac{I_2}{V_2} = \frac{1}{2}}$$


$$V_2 = 4I_2'$$

$$V_1 = 2I_2''$$

$$\frac{V_1}{V_2} = \frac{2I_2''}{4I_2'} = \frac{2 \times \frac{I_2}{2}}{4 \times \frac{I_2}{2}} = \frac{1}{2}$$

$$\boxed{\frac{V_1}{V_2} = \frac{1}{2}}$$

Find  $h$

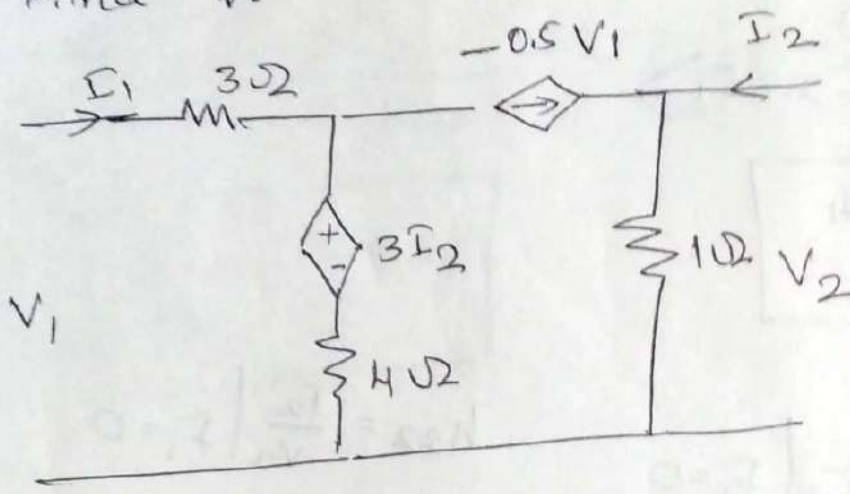


$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

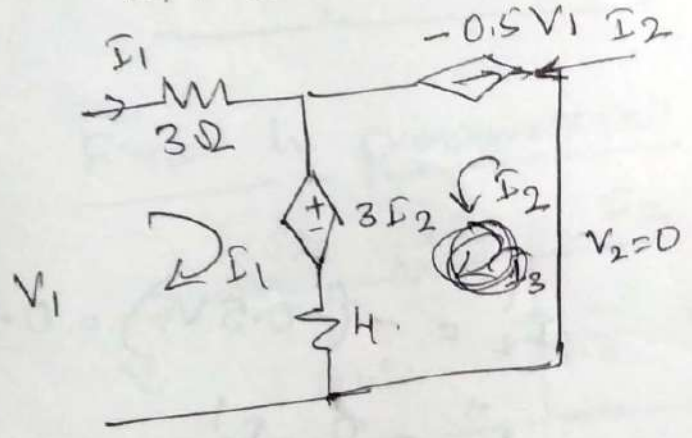

$$I_2 = (-0.5 V_1) = 0.5 V_1$$

$$3 I_1 + 3 I_2 + 4(I_1 + I_2) = V_1$$

$$7 I_1 + 7 I_2 = V_1$$

$$7 I_1 + 7(0.5 V_1) = V_1$$

$$7 I_1 + 3.5 V_1 = V_1$$

$$7 I_1 = V_1 - 3.5 V_1 = -2.5 V_1$$

$$\frac{V_1}{I_1} = \frac{-7}{2.5} = -2.8 \Omega$$

$$\boxed{\frac{V_1}{I_1} = -2.8 \Omega}$$


$$I_2 = 0.5 V_1$$

$$I_2 = 0.5(-2.8 I_1)$$

$$\boxed{\frac{I_2}{I_1} = -1.4}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

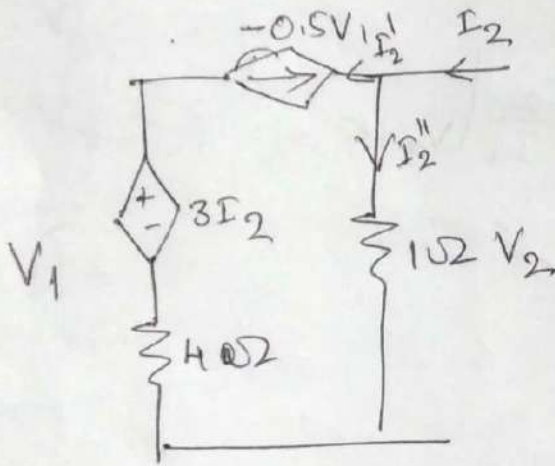

$$V_1 = 3I_2 + 4I_2'$$

$$V_1 = 3I_2 + 4(0.5V_1)$$

$$V_1 = 3I_2 + 2V_1$$

$$-3I_2 = V_1$$

$$I_2' = -(-0.5V_1) = 0.5V_1$$

$$I_2'' = I_2 - I_2'$$

$$= I_2 - 0.5V_1$$

$$V_2 = I_2''$$

$$V_2 = I_2 - 0.5V_1$$

$$V_2 = I_2 - 0.5(-3I_2)$$

$$V_2 = I_2 + 1.5I_2$$


$$V_2 = 2.5I_2$$

$$\boxed{\frac{I_2}{V_2} = \frac{1}{2.5} = 0.4}$$


$$\frac{V_1}{V_2} = \frac{-3I_2}{2.5I_2} = -\frac{3}{2.5} = \frac{-300}{250} = -1.2$$

$$\frac{V_1}{V_2} = -1.2$$

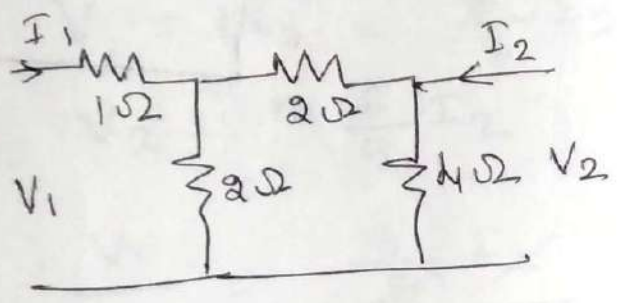3) done Find h parameters of the n/w shown.



3) Find h parameters!

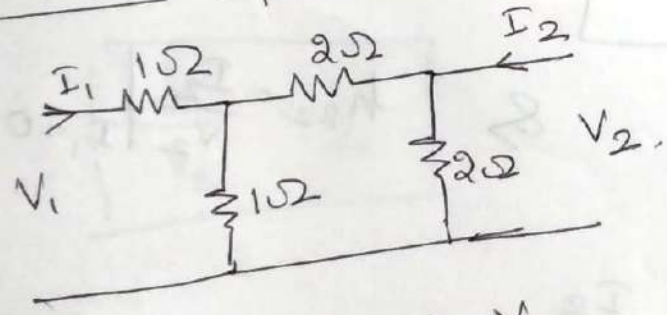


$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$



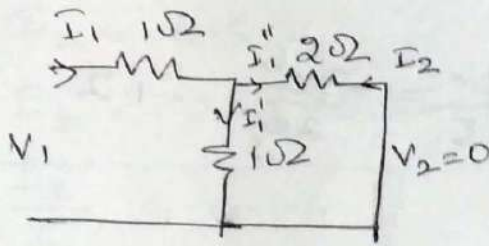

$$I_1'' = \frac{I_1 \times 1}{3} = \frac{1}{3} I_1$$

$$\& I_2 = -I_1'' = -\frac{1}{3} I_1$$

$$I_1' = \frac{I_1 \times 2}{3} = \frac{2}{3} I_1$$

$$\boxed{\frac{I_2}{I_1} = -\frac{1}{3}}$$


$$V_1 = I_1 + I_1'$$

$$V_1 = I_1 + \frac{2}{3} I_1$$

$$V_1 = \frac{5}{3} I_1$$

$$\boxed{\frac{V_1}{I_1} = \frac{5}{3} \Omega}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} \quad \& \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

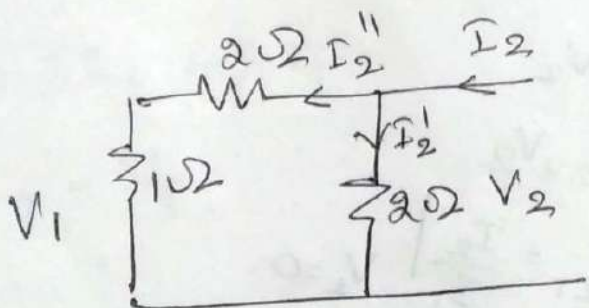

$$I_2' = \frac{I_2 \times 3}{3+2} = \frac{3}{5} I_2$$

$$I_2'' = \frac{I_2 \times 2}{5} = \frac{2}{5} I_2$$

$$V_2 = 2 I_2'$$

$$V_2 = 2 \times \frac{3}{5} I_2$$

$$V_2 = \frac{6 I_2}{5}$$

$$\boxed{\frac{I_2}{V_2} = \frac{5}{6} \text{ } \mathcal{U}}$$


$$V_1 = 1 I_2'' = \frac{3}{5} I_2$$

$$V_2 = \frac{6}{5} I_2$$

$$\frac{V_1}{V_2} = \frac{\frac{3}{5} I_2}{\frac{6}{5} I_2} = \frac{1}{2}$$


$$\boxed{\frac{V_1}{V_2} = \frac{1}{2}}$$

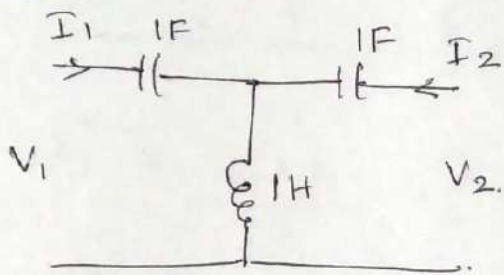4] Determine h parameters after writing transform




$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

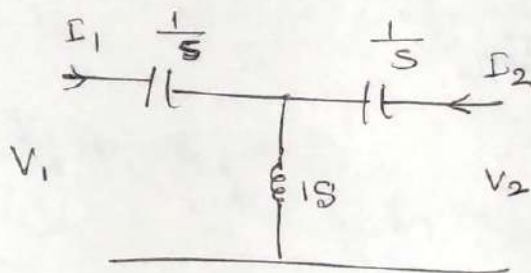

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} \quad h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

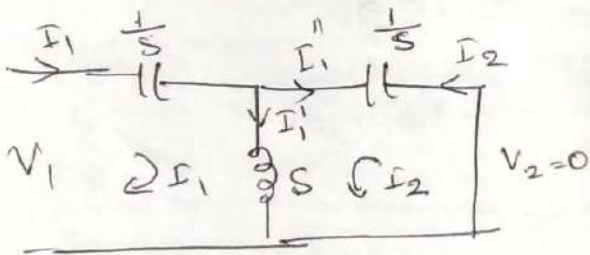

$$I_1'' = -I_2$$

$$I_1' = \frac{I_1 \times \frac{1}{s}}{s + \frac{1}{s}} = \frac{I_1}{s^2 + 1} = \frac{I_1}{1 + s^2}$$

$$I_1'' = \frac{I_1 \times s}{s + \frac{1}{s}} = \frac{I_1 \cdot s \cdot s}{1 + s^2} = \frac{s^2 I_1}{1 + s^2}$$

$$V_1 = \frac{1}{s} I_1 + s I_1'$$

$$= \frac{1}{s} I_1 + \frac{s I_1}{1 + s^2} = \left[ \frac{1 + s^2 + s^2}{(1 + s^2)s} \right] I_1$$


$$\boxed{\frac{V_1}{I_1} = \frac{1 + 2s^2}{s(1 + s^2)}} \quad \Omega$$

$$I_1'' = -I_2$$

$$\frac{s^2 I_1}{1+s^2} = -I_2$$

$$\boxed{\frac{I_2}{I_1} = -\left(\frac{s^2}{1+s^2}\right)}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} \quad \& \quad h_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

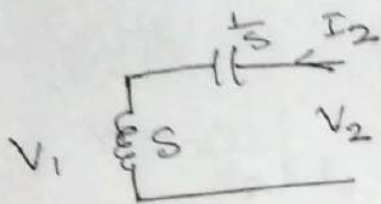

$$V_2 = \left(s + \frac{1}{s}\right) I_2 = \left(\frac{1+s^2}{s}\right) I_2$$

$$\boxed{\frac{I_2}{V_2} = \frac{s}{1+s^2}}$$

$$V_1 = s I_2$$

$$V_2 = \left(\frac{1+s^2}{s}\right) I_2$$


$$\frac{V_1}{V_2} = \frac{s I_2}{\left(\frac{1+s^2}{s}\right) I_2} = \frac{s^2}{1+s^2}$$

$$\boxed{\frac{V_1}{V_2} = \frac{s^2}{1+s^2}}$$

5

①

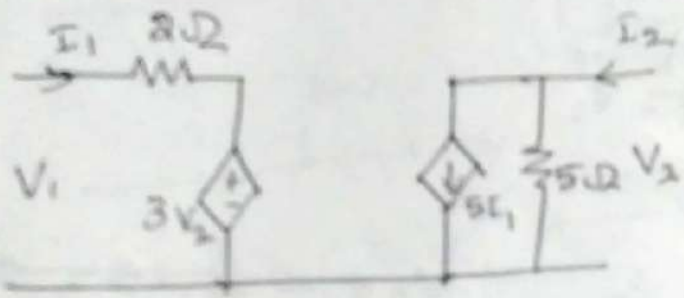
1. Determine the transmission parameters for the n/w shown in fig



$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} \quad C = \frac{I_1}{V_2} \Big|_{I_2=0}$$

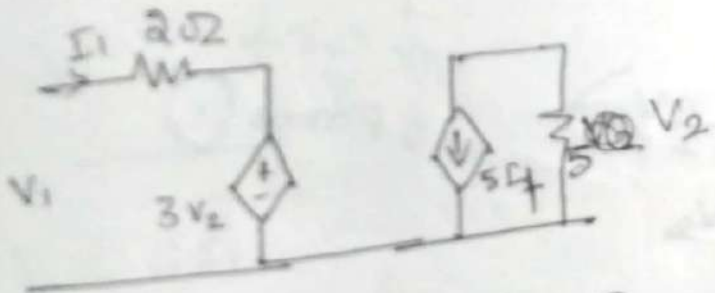

$$V_2 = -5I_1 \times 5 \Rightarrow \frac{25I_1}{5} = \frac{I_1}{5} \Rightarrow \boxed{\frac{I_1}{V_2} = -\frac{1}{25}}$$


$$V_1 = 2I_1 + 3V_2$$

$$V_1 = 2\left(-\frac{1}{25}V_2\right) + 3V_2$$

$$V_1 = -\frac{2}{25}V_2 + 3V_2$$

$$V_1 = \frac{73}{25}V_2$$
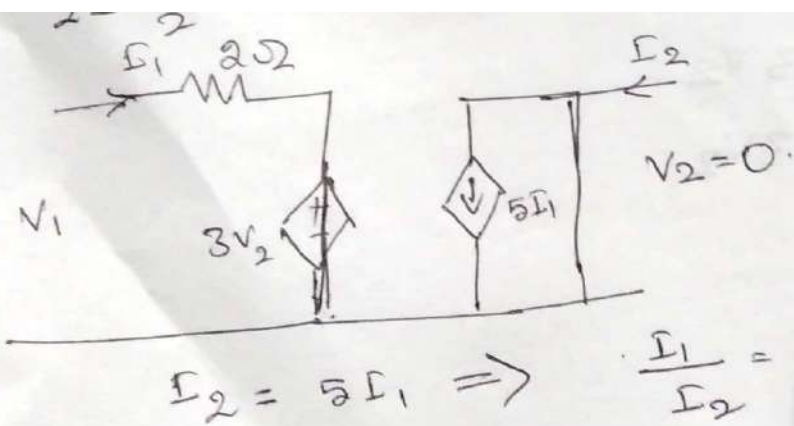
$$\boxed{\frac{V_1}{V_2} = \frac{73}{25}}$$



$$I_2 = 5I_1 \Rightarrow$$

$$\frac{I_1}{I_2} = \frac{1}{5} \Rightarrow$$

$$\boxed{\frac{I_1}{-I_2} = -\frac{1}{5}}$$


$$V_1 = 2I_1 \Rightarrow V_1 = 2\left(\frac{1}{5}\right)I_2 = \frac{2}{5}I_2 \Rightarrow$$

$$\frac{V_1}{I_2} = \frac{2}{5}$$

$$\boxed{\frac{V_1}{-I_2} = -\frac{2}{5}}$$

2) Find ABCD parameters:

2

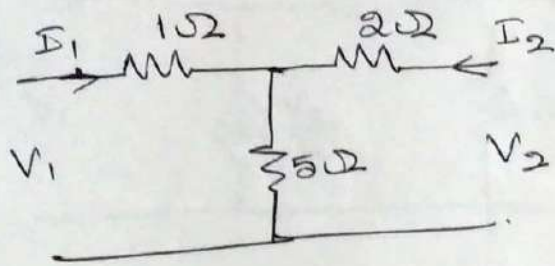


$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

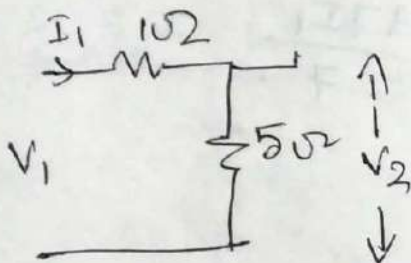

$$V_1 = 6I_1$$

$$V_2 = 5I_1$$


$$\boxed{\frac{V_1}{V_2} = \frac{6}{5}}$$

$$V_2 = 5I_1$$

$$\boxed{\frac{I_1}{V_2} = \frac{1}{5}}$$

$$-B = \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

$$-D = \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

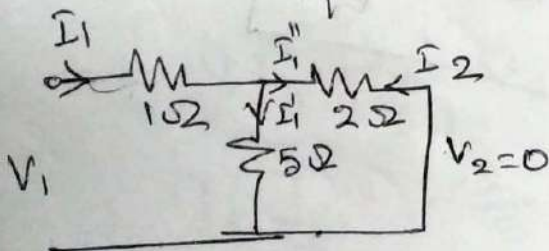

$$I_1'' = -I_2$$

$$I_1' = \frac{I_1 \times 2}{7} = \frac{2I_1}{7}$$

$$I_1'' = \frac{I_1 \times 5}{7} = \frac{5I_1}{7}$$

$$I_1'' = -I_2$$

$$\frac{5I_1}{7} = -I_2$$

$$\frac{I_1}{I_2} = -\frac{7}{5}$$

$$-D = -\frac{7}{5}$$

$$D = \frac{7}{5}$$

$$V_1 = I_1 + 5I_1'$$

$$V_1 = I_1 + 5\left(\frac{2I_1}{7}\right) = \frac{17I_1}{7}$$

$$V_1 = \frac{17I_1}{7}$$

$$V_1 = \frac{17}{7} \left(-\frac{7}{5}\right) I_2$$

$$V_1 = -\frac{17}{5} I_2$$

$$-B = \frac{V_1}{I_2} = -\frac{17}{5} \Omega$$

$$B = \frac{17}{5}$$


$$\frac{V_1}{I_2} = -\frac{17}{5}$$

$$-B = -\frac{17}{5}$$

$$B = \frac{17}{5}$$



3) Find transmission parameters:

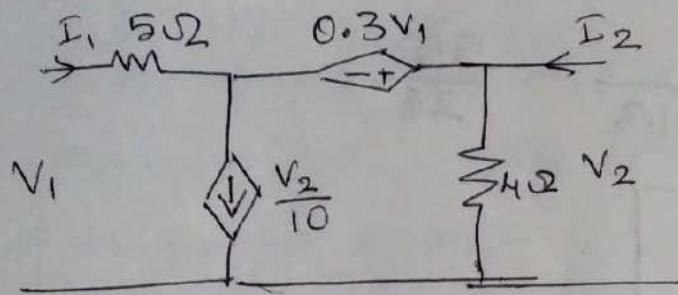


$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

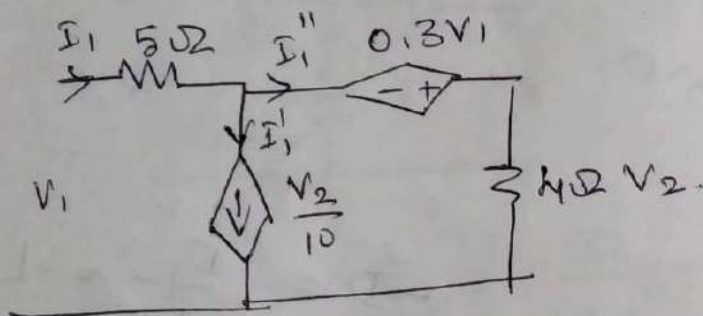

$$I_1' = \frac{V_2}{10} \quad \& \quad I_1'' = I_1 - \frac{V_2}{10}$$

$$5I_1 - 0.3V_1 + 4I_1'' = V_1$$

$$5I_1 + 4\left(I_1 - \frac{V_2}{10}\right) = V_1 + 0.3V_1$$

$$5I_1 + 4I_1 - \frac{2}{5}V_2 = 1.3V_1$$

$$9I_1 - \frac{2}{5}V_2 = 1.3V_1$$

$$9\left(\frac{7V_2}{20}\right) - \frac{2}{5}V_2 = 1.3V_1$$

$$\frac{63V_2}{20} - \frac{2}{5}V_2 = 1.3V_1$$

$$\left(\frac{63-8}{20}\right)V_2 = 1.3V_1$$

$$\frac{55}{20}V_2 = 1.3V_1$$

$$V_2 = 4I_1''$$

$$V_2 = 4\left(I_1 - \frac{V_2}{10}\right)$$

$$V_2 = 4I_1 - \frac{2}{5}V_2$$

$$V_2 + \frac{2}{5}V_2 = 4I_1$$

$$\frac{7V_2}{5} = 4I_1$$

$$\frac{V_2}{I_1} = \frac{20}{7}$$

$$\boxed{\frac{I_1}{V_2} = \frac{7}{20}}$$


$$\frac{55}{20} V_2 = 1.3 V_1$$

$$\frac{V_1}{V_2} = \frac{55}{20 \times 1.3} = \frac{55}{26}$$

$$\boxed{\frac{V_1}{V_2} = \frac{55}{26}}$$

$$-B = \frac{V_1}{I_2} \Big|_{V_2=0}$$

$$-D = \frac{I_1}{I_2} \Big|_{V_2=0}$$

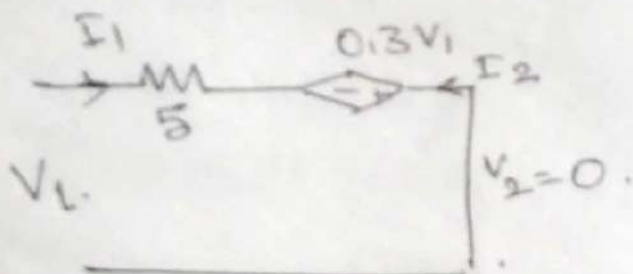

$$I_1 = -I_2$$

$$-D = \frac{I_1}{I_2} = -1$$

$$V_1 = 5I_1 - 0.3V_1$$

$$V_1 = -5I_2 - 0.3V_1$$

$$V_1 + 0.3V_1 = -5I_2$$


$$1.3V_1 = -5I_2$$

$$\frac{V_1}{I_2} = \frac{-5}{1.3}$$

$$\boxed{B = \frac{5}{1.3} = \frac{50}{13} \Omega}$$

$$\boxed{D = 1}$$

Find transmission parameters.

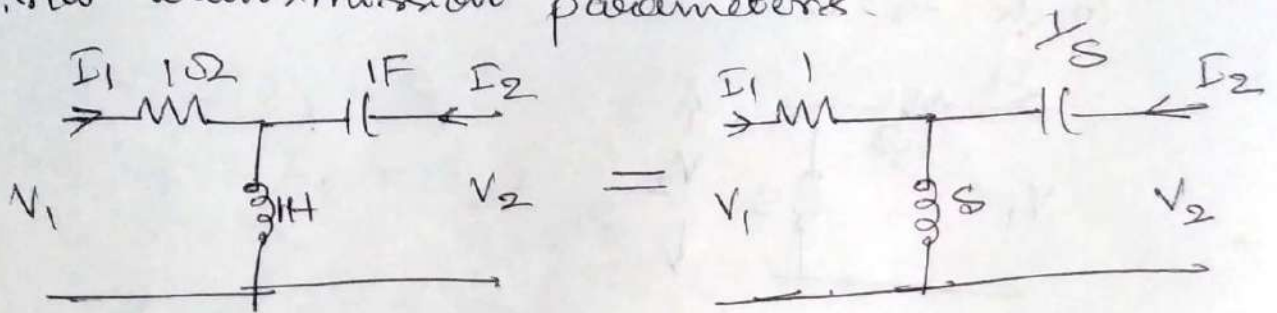


$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

With  $I_2 = 0$

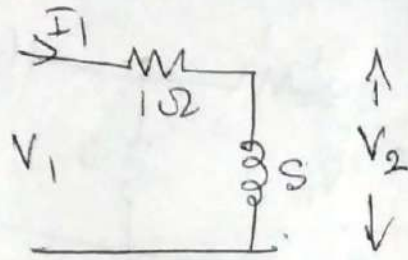

$$V_1 = (1 + s) I_1$$

$$V_2 = s I_1$$


$$\boxed{\frac{V_1}{V_2} = \left( \frac{1 + s}{s} \right)}$$

$$V_2 = s I_1$$

$$\boxed{\frac{I_1}{V_2} = \frac{1}{s}}$$

$$-B = \frac{V_1}{I_2} \Big|_{V_2=0}$$

$$-D = \frac{I_1}{I_2} \Big|_{V_2=0}$$

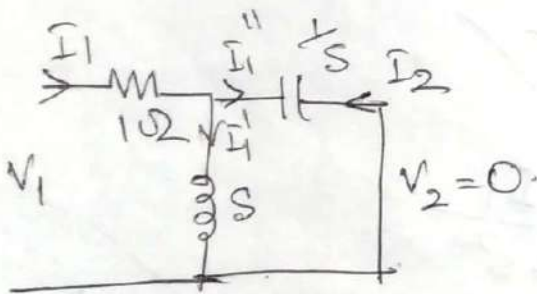

$$I_1'' = -I_2$$

$$I_1'' = \frac{I_1 \times s}{s + \frac{1}{s}} = \frac{s I_1 \cdot s}{(s^2 + 1)} = \frac{s^2 I_1}{(1 + s^2)} = -I_2$$

$$I_1' = \frac{I_1 \times \frac{1}{s}}{s + \frac{1}{s}} = \left( \frac{I_1}{1 + s^2} \right)$$

$$\frac{I_1}{I_2} = - \left( \frac{1 + s^2}{s^2} \right)$$

$$\boxed{D = \frac{1 + s^2}{s^2}}$$

$$V_1 = I_1 + sI_1'$$


$$V_1 = I_1 + s \frac{I_1}{(1+s^2)}$$

$$V_1 = \frac{(1+s^2+s)}{1+s^2} I_1$$

$$V_1 = \left( \frac{1+s+s^2}{1+s^2} \right) \left( \frac{1+s^2}{s^2} \right) I_2$$

$$\boxed{\frac{V_1}{I_2} = \frac{1+s+s^2}{s^2}}$$

5] Determine ABCD parameters.

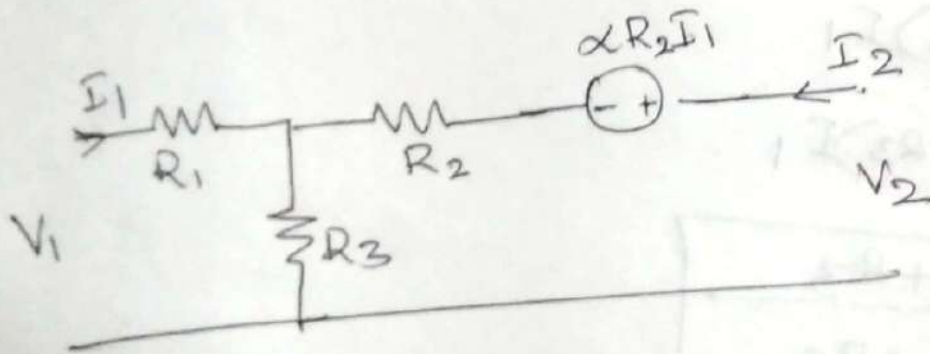


$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0}$$

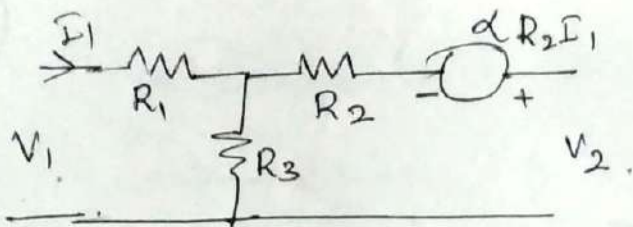

~~$$-\alpha R_2 I_1 + V_2$$~~

$$-\alpha R_2 I_1 + V_2 - I_1 R_3 = 0.$$

$$I_1 (-\alpha R_2 - R_3) = -V_2$$

$$-I_1 (\alpha R_2 + R_3) = -V_2$$

$$\boxed{\frac{I_1}{V_2} = \frac{1}{\alpha R_2 + R_3}}$$

$$V_1 = I_1 R_1 + I_1 R_3 = I_1 (R_1 + R_3)$$


$$V_1 = (R_1 + R_3) I_1$$

$$V_2 = (\alpha R_2 + R_3) I_1$$

$$\boxed{\frac{V_1}{V_2} = \frac{R_1 + R_3}{\alpha R_2 + R_3}}$$

$$-B = \frac{V_1}{I_2} \Big|_{V_2=0}$$

$$\rightarrow -D = \frac{I_1}{I_2} \Big|_{V_2=0}$$

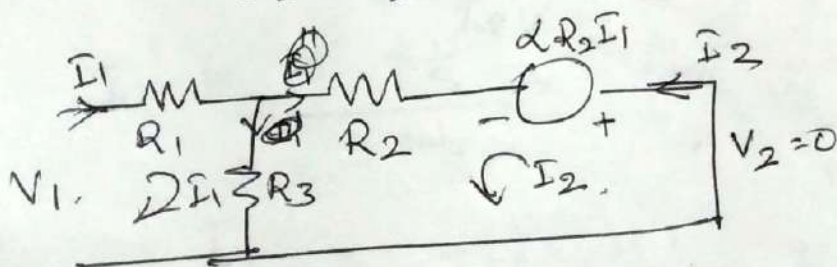

$$\boxed{I_1 = -I_2}$$

## Resonant circuits

### Series & parallel resonance frequency response of series & parallel circuits & factors Bandwidth

Resonance is a phenomenon which takes place in ac circuits

- very imp especially in field of comm.  
ex: Radio Rx has the ability to select certain desired freq, transmitted by station. ~~The~~ & rejects all other unwanted frequencies transmitted by the other station. Such a selection of required freq & rejection of unwanted freq is based on the principle of resonance.

Resonance is a phenomenon in which applied  $V_g$  and resulting current are in phase  
OR

Ac ckt is said to be under resonance if it exhibits unity <sup>power</sup> factor condition. [ $\cos 0 = 1$ ]

The resonance condition can be achieved either by keeping the n/w elements constant & by varying freq  
OR

keeping freq constant & varying freq dependent elements

A resonant ckt must have an inductance & capacitance. The resistance will be always present either due to lack of ideal elements or due to the resistance itself.

When resonance occurs, energy absorbed by one reactive element is exactly equal to the energy by the other reactive element, within the system.  $f \rightarrow$


The total apparent power is simply the average power dissipated by the reactive element. The average power is  $P = I^2 R$

The average power absorbed by the system will also be max at resonance.

2 Two types:

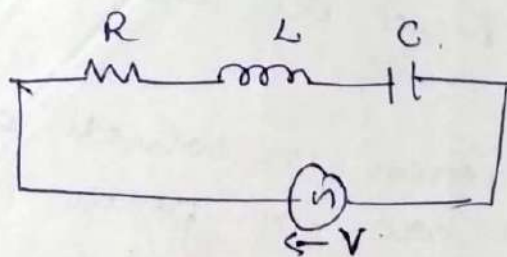1. Series Resonant circuit
2. parallel Resonant ckt.

Series Resonant circuit: R, L, C connected in series across alternating  $V_s$  of varying freq



$$\begin{aligned}
 Z &= (R + jX_L - jX_C) \\
 &= R + j\omega L - j\frac{1}{\omega C} \\
 &= R + j\left(\omega L - \frac{1}{\omega C}\right)
 \end{aligned}$$

at resonance  $Z = R$ ,  $\omega \rightarrow \omega_0$

$$\omega_0 L - \frac{1}{\omega_0 C} = 0 \Rightarrow \omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$2\pi f_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$



$f_r \rightarrow$  Resonant freq.

At resonance, current through ckt is maximum.

$\Delta$  is given by

$$I_r = \frac{E}{R} = I_m.$$

$$I = \frac{V}{R + j(X_c - X_L)}$$

$$X_L = j\omega L$$


$$X_c = \frac{-j}{\omega C}$$

for less  $f_r$

For  $f_{\text{req}} < f_r$ ;

$$X_c > X_L \ \&$$

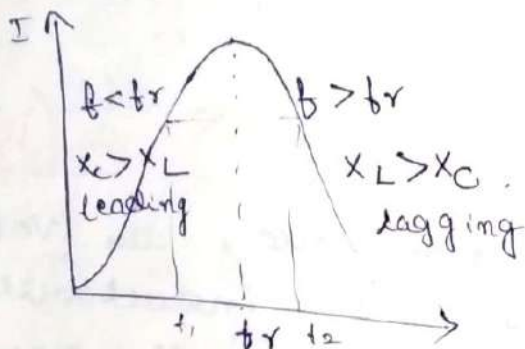For  $f_{\text{req}} > f_r$ ;  $X_L > X_c$ .



$X_c$  - Current leading  $V_g$


$X_L$  - Current lagging  $V_g$

Bandwidth

Defined as the range of frequencies over which the gain is equal to or greater than  $\frac{1}{\sqrt{2}} I_0$ .

( $I_0 \rightarrow$  max value of current)

$$\text{or Bandwidth} = f_2 - f_1.$$

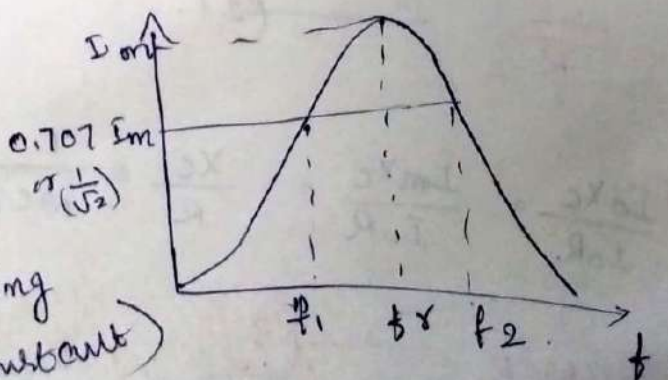

$f_1, f_2 \rightarrow$  cut off freq  
or  $\rightarrow$  band freq  
or  $\rightarrow$  half power freq.

keeping  $E$  constant

at resonance,  $P_m = I_m^2 R$

$$\text{or } f_1 \text{ or } f_2 \quad P = \left(\frac{I_m}{\sqrt{2}}\right)^2 R = \frac{I_m^2}{2} R = \frac{P_m}{2}$$

$\therefore f_1, f_2 \rightarrow$  half power frequencies

A ~~low~~ resonant ckt is always adjusted to select the band of frequencies lying b/w  $f_1$  &  $f_2$

Selectivity:

It is defined as the ratio of Resonant frequency to B.W

$$\text{i.e. } \boxed{\text{Selectivity} = \frac{f_0}{f_2 - f_1}}$$

Qs factor (Quality factor) or (Vg magnification)

During series resonance, the voltages across the reactive elements i.e. inductance & capacitance is many times more than the applied  $V_g$ .

i.e.  $Q \rightarrow$  ratio of  $V_g$  across inductor or capacitor to the applied  $V_g$ .

$$Q = Q_s = \frac{V_L}{V_0} \quad \text{or} \quad Q_s = \frac{V_C}{V} \quad \text{--- (1)}$$

$$Q_s = \frac{V_L}{V} = \frac{I_0 X_L}{I_0 R} = \frac{I_m X_L}{I_m R} = \frac{X_L}{R} = \frac{\omega_0 L}{R}$$

$$\text{i.e. } Q_s = \frac{\omega_0 L}{R} \quad \text{--- (2)}$$

also  ~~$V_L = I_0 X_L$~~

$$Q_s = \frac{V_C}{V} = \frac{I_0 X_C}{I_0 R} = \frac{I_m X_C}{I_m R} = \frac{X_C}{R} = \frac{1}{\omega_0 C R}$$

$$Q_s = \frac{1}{\omega_0 C R} \quad \text{--- (3)}$$

## Parallel resonance!

From (2) & (3)

$$\frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$$

Quality factor can also be defined as the ratio of inductive reactance or capacitive reactance to the resistance.

$$(2) \text{ & } (3) \quad Q_s = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$$

$$Q_s = \frac{1}{\omega_0^2 C L}$$

$$Q = \frac{X_L}{R}$$

$$\& \quad Q = \frac{X_C}{R}$$

$$X_C = \frac{1}{\omega_0 C}$$

$$Q = \frac{\omega_0 L}{R} \quad (5)$$

$$Q = \frac{1}{\omega_0 C R}$$

$$\omega_0 = \frac{1}{Q C R} \quad (4)$$

Substi (4) in (5)

$$Q = \frac{\frac{1}{Q C R} \cdot L}{R}$$


$$Q = \frac{L}{Q C R^2}$$

$$Q^2 = \frac{L}{R^2 C}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Basically a resonant ckt is freq select. i.e. the behaviour of reactive components change w variation in freq. So it is necessary to study variation of diff parameters with variation of freq.
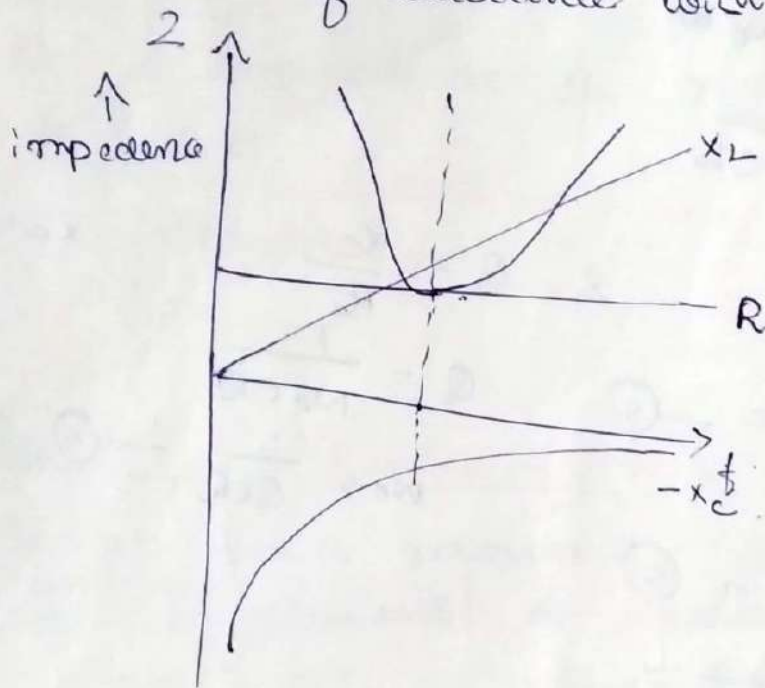
### 1. Variation of reactance with frequency.



$$X_L = f\omega L$$

$$f \uparrow \Rightarrow X_L = \uparrow$$

$$X_C = \frac{1}{\omega C}$$

$$f \uparrow \Rightarrow X_C \downarrow$$

R remains constant for all freq.


The inductive reactance  $X_L$  follows st. line.

$X_C$  follows hyperbolic curve.

At  $f_r$ ,  $X_L = X_C$  & The variation of  $Z$  is shown

at  $f_r$ ,  $I$  max  $\Rightarrow Z$  min.

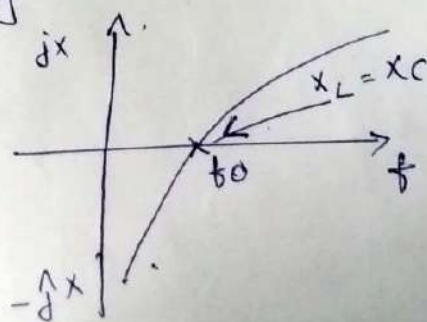for lower value  $f$ ,  $Z \uparrow$  due to increased value of  $X_C$   
 for higher value  $f$  ( $f > f_r$ )  $Z \uparrow$  due to increased value of  $X_L$



variation of impedance with freq.  
 $Z = R + j(X_L - X_C)$   
 $Z = R + j(\omega L - \frac{1}{\omega C})$



under resonance  $Z = R$ .

Current in series resonant ckt is given by

$$I = \frac{V}{|Z|} = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$



at resonance  $I = I_0$

$$I_0 = \frac{V}{R}$$

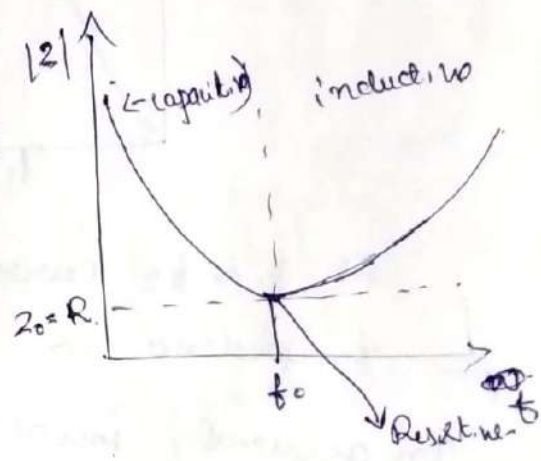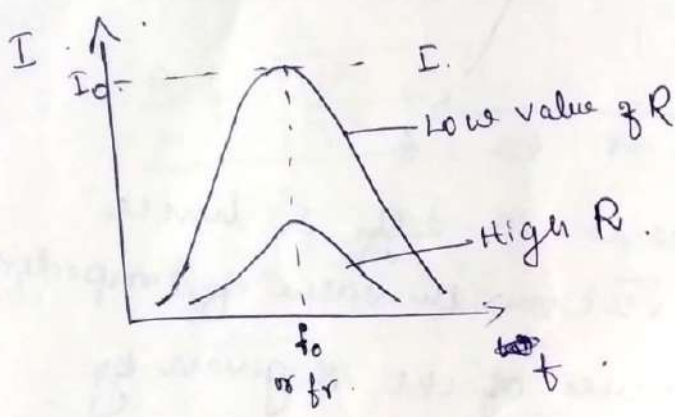

$$X_C = \frac{1}{\omega C} \quad X_L = \omega L$$


variation of current with freq

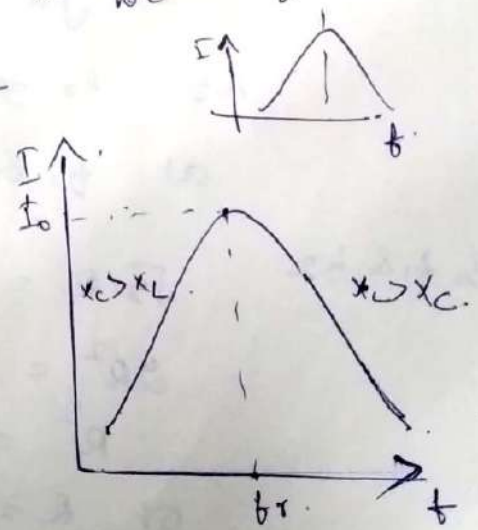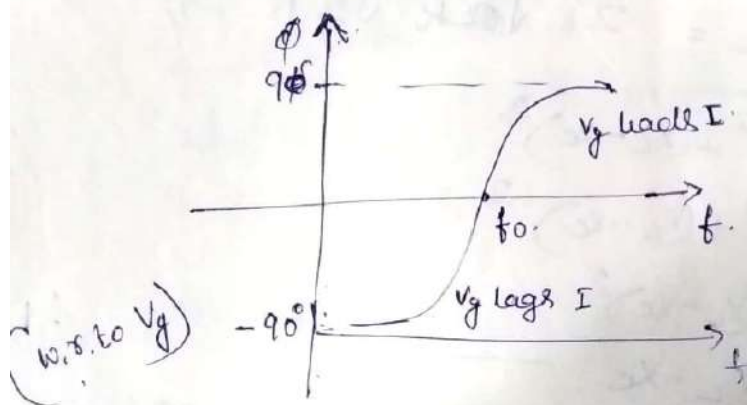

Considering phase

considering mag.

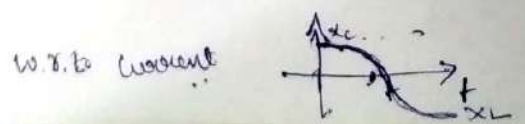$f > f_0 (f_r) \rightarrow$  inductive effect.




Expression for  $f_1$  &  $f_2$  :-  
 Relation b/w,  $f_1$ ,  $f_2$ ,  $f_r$ .

Expression for  $f_{max}$ ,  $I_{max}$ .

Expression for B.W

Expression for  $f_1$  &  $f_2$  & B.W

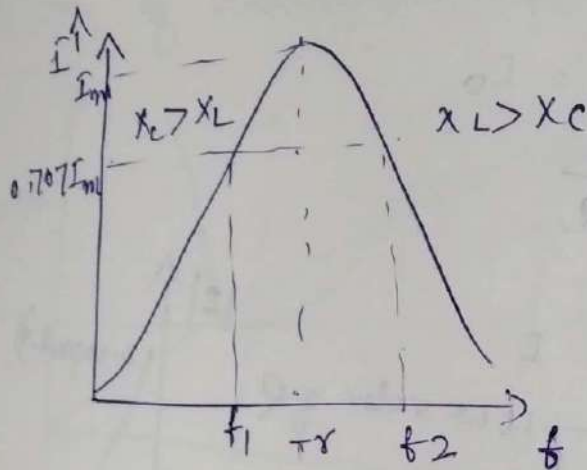

At  $f_1$  &  $f_2$  current is  $\frac{I_m}{\sqrt{2}}$  & hence impedance is  $\sqrt{2}$  times the value of impedance

In general, impedance of ckt is given by.

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

At  $f_r$   $Z_r = R$   $Z = \sqrt{2} Z_r$

at  $f_1$  &  $f_2$   $Z = \sqrt{2} R$

&  $f_1$  &  $f_2$

$$\sqrt{2} R = \sqrt{R^2 + (X_L - X_C)^2}$$

$$2R^2 = R^2 + (X_L - X_C)^2$$

$$R^2 = (X_L - X_C)^2$$

$$\text{or } R = X_L - X_C \quad \text{--- (1)}$$

At  $f_1$ ,  $X_C > X_L$ , eqn (1) can be written as  
 $R = X_C - X_L$

$$R = X_C - X_L$$

$$= \frac{1}{\omega_1 C} - \omega_1 L$$

$$R = \frac{1 - \omega_1^2 LC}{\omega_1 C}$$

$$R\omega_1 C = 1 - \omega_1^2 LC$$

$$\omega_1^2 LC + R\omega_1 C - 1 = 0$$

$$\omega_1^2 + \frac{R}{L}\omega_1 - \frac{1}{LC} = 0$$

$$\omega_1 = \frac{-R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - 4\left(-\frac{1}{LC}\right)}$$

$$= \frac{-R}{L} \pm \sqrt{\frac{R^2}{L^2} + \frac{4}{LC}}$$

$$\omega_1 = \frac{-R}{L} + \sqrt{\frac{R^2}{L^2} + \frac{4}{LC}}$$

$$\omega_1 = \frac{-R}{2L} + \frac{1}{2} \sqrt{\frac{R^2}{L^2} + \frac{4}{LC}}$$

$$\omega_1 = \frac{-R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

$$f_1 = \frac{1}{2\pi} \left[ \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right]$$

At  $t_2$ ,  $X_L > X_C$

at  $t_2$ ,

$$R = X_L - X_C$$

$$= \omega_2 L - \frac{1}{\omega_2 C}$$

$$R = \frac{\omega_2^2 LC - 1}{\omega_2 C}$$

$$\div LC \quad ax^2 + bx + c$$

$$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

discard

$$\omega_1 = \frac{-R}{L} - \sqrt{\frac{R^2}{L^2} + \frac{4}{LC}}$$

-ve sign  $\rightarrow$  -ve  $\omega$

$$\omega_2 RC = \omega_2^2 LC - 1$$

$$\omega_2^2 LC - \omega_2 RC - 1 = 0$$

$$\omega_2^2 - \omega_2 \frac{R}{L} - \frac{1}{LC} = 0$$

$\frac{1}{LC}$

$$\omega_2 = \frac{\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 + 4\left(\frac{1}{LC}\right)}}{2}$$

$$\omega_2 = \frac{\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} + \frac{4}{LC}}}{2}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$f_2 = \frac{1}{2\pi} \left[ \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right]$$

Bandwidth  $\therefore f_2 - f_1$

$$= \frac{1}{2\pi} \left\{ \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right\} - \left[ \frac{1}{2\pi} \left( -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right) \right]$$

$$= \frac{1}{2\pi} \left[ \frac{R}{2L} + \frac{R}{2L} \right]$$

$$= \frac{1}{2\pi} \cdot \frac{2R}{2L}$$

$$f_2 - f_1 = \frac{R}{2\pi L}$$

$$\frac{X_C}{R} = \frac{1}{\omega CR}$$

$$= \frac{1}{2\pi f CR}$$

$f =$

at resonance  $Q = Q_s = \frac{X_L}{R} = \frac{\omega L}{R}$

$$= \frac{2\pi f_r L}{R}$$

$$= \frac{2\pi f_r \frac{L}{R}}{R}$$

$$Q = \frac{f_r}{f_2 - f_1}$$

$$\frac{R}{2\pi L} = f_2 - f_1$$



$$Q = \frac{f_r}{f_2 - f_1}$$

Characterizes resonance  
B.W. relod.ve to its  
Central freq.

$$f_2 - f_1 = \frac{f_r}{Q}$$

$$B.W = f_2 - f_1 = \frac{f_r}{Q} = \frac{f_r}{Q_s}$$

$$f_2 - f_1 = \frac{R}{2\pi L}$$

$$f_2 - f_1 = \frac{f_r}{Q_s}$$

$$\frac{f_2 - f_1}{f_r} = \frac{1}{Q_s}$$

Sometimes  $\frac{f_2 - f_1}{f_r} \rightarrow$  is referred to as fractional

Relation b/w  $f_r, f_1$  &  $f_2$ :

The impedances of an RLC resonant ckt at  $f_1$  &  $f_2$  are given by

$$Z_1 = \sqrt{R^2 + (X_{C1} - X_{L1})^2}$$

magnitudes equal.

$$Z_2 = \sqrt{R^2 + (X_{L2} - X_{C2})^2}$$

But  $Z_1 = Z_2$

$$R^2 + (X_{C1} - X_{L1})^2 = R^2 + (X_{L2} - X_{C2})^2$$

$$X_{C1} - X_{L1} = X_{L2} - X_{C2}$$

$$X_{C1} + X_{C2} = X_{L1} + X_{L2}$$

$$\frac{1}{\omega_1 C} + \frac{1}{\omega_2 C} = \omega_1 L + \omega_2 L$$

$$\frac{1}{C} \left[ \frac{\omega_1 + \omega_2}{\omega_1 \omega_2} \right] = L (\omega_1 + \omega_2)$$

$$\omega_1 \omega_2 = \frac{1}{LC} \quad \text{--- (1)}$$

but  $f_0 = \frac{1}{2\pi\sqrt{LC}}$

$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \omega_0^2 = \frac{1}{LC}$

∴ from (1) & (2) (2)



$\omega_1 \omega_2 = \omega_0^2$

$\omega_0 = \sqrt{\omega_1 \omega_2}$

∴  $f_0 = \sqrt{f_1 f_2}$

i.e. resonant freq is geometric mean of half power frequencies.

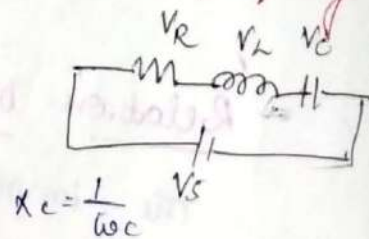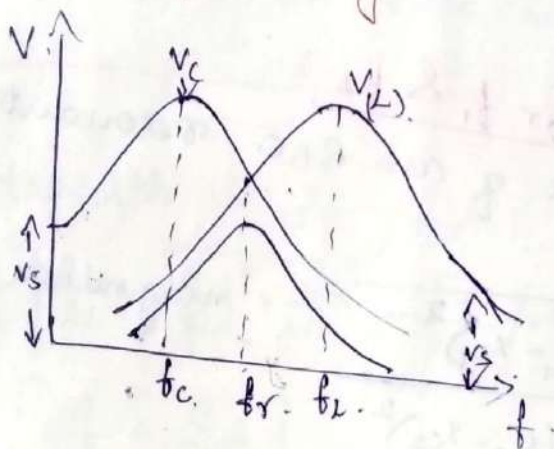Variation of Voltages across L & C with frequency



Initially at  $f=0 \Rightarrow C \rightarrow$  acts as open ckt & blocks current.

∴ Then across capacitor we have total i/p  $V_S$

As freq  $\uparrow$ , reactance of C  $\downarrow$  & that.

but freq  $\uparrow$ , reactance of L  $\uparrow$ .

SO  $X_C - X_L = \downarrow$  & current  $\uparrow$ .

As current  $\uparrow$ ,  $V_f$  across R  $V_R \uparrow$  & also both  $V_L$  &  $V_C \uparrow$ .

When frequency =  $f_r$ , Impedance  $Z=R$ ,  
 $\therefore$  Current is max  $\Rightarrow$  so  $V_R$  reaches max value.

As freq is still  $\uparrow$  above  $f_r$ ,  
 reactance of  $L \uparrow$  & reactance of  $C \downarrow$ .

& hence  $(X_L - X_C) \uparrow \Rightarrow$  Current  $\downarrow$ ,

$\Rightarrow$  so  $V_R \downarrow$  & also both  $V_C$  &  $V_L \downarrow$ .

As frequency becomes very high, both  $V_R$  &  $V_C$   
 value approaches zero while  $V_L$  value approaches  $V_s$ .

From the graph, it is clear that,  
 $V_C$  across  $C$  &  $V_L$  across  $L$  is not max at  $f_r$ .  
 At resonance  $V_L$  &  $V_C$  are equal in mag. but  
 opposite in phase

$V_C$  is max at freq  $f_C$  ( $f_C < f_r$ )  
 &  $V_L$  is max at freq  $f_L$  ( $f_L > f_r$ )

Frequencies for maximum  $V_C$  across  $C$  &  $V_L$  across  $L$

$f_{Cmax}$  is freq at which  $V_{Cmax}$  occurs &  
 $f_{Cmax} < f_r$  for which  $X_C > X_L$

$V \rightarrow$  supply  $V$

$$V_C = I X_C$$

$$V_C = \frac{V}{Z} \cdot \frac{1}{\omega C}$$

$$= \frac{V}{\sqrt{R^2 + (X_C - X_L)^2}} \cdot \frac{1}{\omega C}$$

$$V_c^2 = \frac{V^2}{R^2 + \left(\frac{1}{\omega C} - \omega L\right)^2} \times \frac{1}{\omega^2 C^2}$$

$$= \frac{V^2}{\omega^2 C^2 R^2 + \omega^2 C^2 \left(\frac{1}{\omega^2 C^2} + \omega^2 L^2 - 2\frac{L}{C}\right)}$$

$$= \frac{V^2}{\omega^2 C^2 R^2 + (1 + \omega^4 C^2 L^2 - 2\omega^2 LC)}$$

$$= \frac{V^2}{\omega^2 C^2 R^2 + (\omega^2 LC - 1)^2}$$

$V_c$  is max when  $\frac{dV_c^2}{d\omega} = 0$

$$\frac{dV_c^2}{d\omega} = \frac{d}{d\omega} \left[ \frac{V^2}{\omega^2 C^2 R^2 + (\omega^2 LC - 1)^2} \right]$$

$$= -V^2 \left\{ \frac{2\omega C^2 R^2 + 2\omega^3 C^2 L^2 - 4\omega LC}{(\omega^2 LC - 1)^2} \right\} = 0$$

$$2\omega C^2 R^2 + 4\omega^3 C^2 L^2 - 4\omega LC = 0$$

$$2\omega C (CR^2 + 2\omega^2 L^2 C - 2L) = 0$$

$$CR^2 + 2\omega^2 L^2 C - 2L = 0$$

$$2\omega^2 L^2 C - 2L + CR^2 = 0$$

$$\omega^2 - \frac{1}{2LC} + \frac{R^2}{2L^2} = 0$$

$$\omega^2 = \frac{1}{2LC} - \frac{R^2}{2L^2}$$

$$\omega = \sqrt{\frac{1}{2LC} - \frac{R^2}{2L^2}}$$

$$f_{\text{max}} = \frac{1}{2\pi} \sqrt{\frac{1}{2LC} - \frac{R^2}{2L^2}}$$

all

$$f_{L \max} = ?$$

$$f_{L \max} = \frac{1}{2\pi} \sqrt{\dots}$$

$$V_L = I X_L = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} \quad \omega L$$

$$= \frac{V \omega L}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$V_L = V$$

## Frequency deviation (s)

The frequency deviation of an R.L.C series ckt is defined as the ratio of the difference b/w operating frequency & resonant frequency to the resonant frequency

$$s = \frac{\omega - \omega_r}{\omega_r} = \frac{f - f_r}{f_r}$$

$\omega \rightarrow$  operating freq in rad/sec

$\omega_r \rightarrow$  resonant freq in rad/sec

$f \rightarrow$  operating frequency in Hz

$f_r \rightarrow$  resonant frequency in Hz

The impedance of an R.L.C series ckt is given by

$$Z = R + j(X_L - X_C)$$

$$= R + j\omega L - j \frac{1}{\omega C}$$

$$= R \left[ 1 + j \left( \frac{\omega L}{R} - \frac{1}{\omega C R} \right) \right]$$

$$= R \left[ 1 + j \left[ \frac{\omega_r L}{R} \cdot \frac{\omega}{\omega_r} - \frac{1}{\omega_r C R} \times \frac{\omega_r}{\omega} \right] \right]$$

$$= R \left[ 1 + j \left( Q_s \frac{\omega}{\omega_r} - Q_s \frac{\omega_r}{\omega} \right) \right]$$

$$= R \left[ 1 + j Q_s \left( \frac{\omega}{\omega_r} - \frac{\omega_r}{\omega} \right) \right]$$

$$= R \left[ 1 + j Q_s \left( 1 + s - \frac{1}{1+s} \right) \right]$$

$$= R \left[ 1 + j Q_s \left( \frac{1+s^2+2s-1}{1+s} \right) \right]$$

$$= R \left[ 1 + j Q_s s \left( \frac{2+s}{1+s} \right) \right]$$

$$Z = R \left[ 1 + j Q_s s \left( \frac{2+s}{1+s} \right) \right]$$

$$Q = \frac{\omega L}{R}$$

$$Q = \frac{1}{\omega C R}$$

$$s = \frac{\omega - \omega_r}{\omega_r}$$

$$s = \frac{\omega}{\omega_r} - 1$$

$$\frac{\omega}{\omega_r} = 1 + s$$

1) A series resonant ckt containing resonating  
 1000 kHz with effective value of Q as 100  
 having total value of resistance in ckt of 50 Ω  
 The applied  $V_g$  is 10 V. Calculate the  
 phase angle of current & impedance of the  
 at frequency 10 kHz below resonant freq.

$$f_r = 1000 \text{ kHz}$$

$$Q = 100$$

$$Z = R = 50 \Omega$$

$$V = 10 \text{ V}$$

$$I = \frac{V}{Z}$$

$$Z = R \left[ 1 + j Q \left( \frac{2 + s}{1 + s} \right) \right]$$

$$f = \frac{1000 \text{ k} - 10 \text{ k}}{990}$$

$$s = \frac{f - f_r}{f_r}$$

$$= \frac{990 \text{ k} - 1000 \text{ k}}{1000 \text{ k}}$$

$$= 50 \left[ 1 + j (100) \left( \frac{-0.01}{1 - 0.01} \right) \cdot \frac{2 - 0.01}{1 - 0.01} \right] = -0.99$$

$$= 50 \left[ 1 + j 2.010 \right] = -0.01$$

$$= 50 \angle$$

$$= 50 - 100.5 \angle$$

$$= 112.25 \angle -63.55 \Omega$$

$$I = \frac{V}{Z}$$

$$= \frac{10}{112.25 \angle -63.55}$$

$$= 0.0891 \angle 63.55$$

$$\text{Magnitude} = 0.0891$$

$$\phi = 63.55$$

i.e. current leads  $V_g$

i.e. below resonant freq.

is capacitive

is required that a series RLC circuit should operate at 1 MHz. Determine values of R, L & C B.W of ckt is 5 kHz and its impedance is 50  $\Omega$  at resonance.

$$B.W = 5 \text{ kHz} =$$

$$Z_0 = R = 50 \Omega$$

$$f_0 = 1 \text{ MHz} = 1 \times 10^6 \text{ Hz}$$

The impedance of series RLC ckt at resonance is given by

$$Z_0 = R$$

$$R = 50 \Omega$$

$$B.W = f_2 - f_1 = \frac{R}{2\pi L} = 5 \text{ kHz}$$

$$L = \frac{R}{2\pi(B.W)} = \frac{50}{2\pi(5000)} =$$

$$L = 1.5915 \text{ mH}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$


$$C = \frac{1}{(2\pi f_0)^2 L}$$

$$= \frac{1}{(2\pi \times 1 \times 10^6)^2 (1.5915 \times 10^{-3})}$$

$$= 15.9159 \text{ nF}$$



## Parallel Resonance!

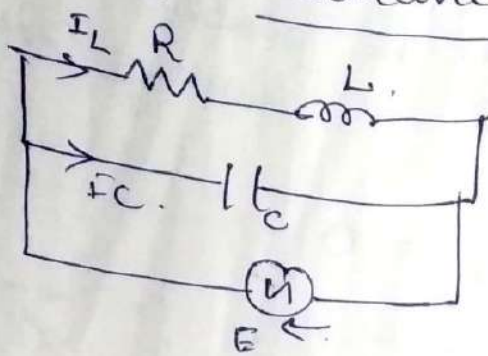

Consists of an inductive coil of resistance  $R$  & inductance  $L$  placed in parallel with  $C$  & connected to an alternating supply of  $V_g E$ .

The impedance of coil is

$$Z_L = R + j\omega L.$$

Admittance of coil is

$$Y_L = \frac{1}{Z_L} = \frac{1}{R + j\omega L} \times \frac{R - j\omega L}{R - j\omega L} = \frac{R - j\omega L}{R^2 + \omega^2 L^2}.$$

$$Z_C = -j \frac{1}{\omega C}$$

$$\& Y_C = \frac{1}{Z_C} = \frac{1}{-j \frac{1}{\omega C}} = \frac{\omega C}{-j} \times \frac{j}{j} = j\omega C.$$

Total admittance of  $CKL$  is

$$Y = Y_L + Y_C$$

$$= \frac{R - j\omega L}{R^2 + \omega^2 L^2} + j\omega C.$$

$$= \frac{R}{R^2 + \omega^2 L^2} + j \left( \omega C - \frac{\omega L}{R^2 + \omega^2 L^2} \right)$$

ckt at resonance  
 or admittance must be purely  
 impedance of ckt be purely  
 Conductance

$$\therefore \omega_r C - \frac{\omega_r L}{R^2 + \omega_r^2 L^2} = 0$$

$$\omega_r C = \frac{\omega_r L}{R^2 + \omega_r^2 L^2}$$

$$R^2 + \omega_r^2 L^2 = \frac{L}{C} \quad \text{--- (1)}$$

$$\omega_r^2 = \frac{\frac{L}{C} - R^2}{L^2} = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\omega_r = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

At resonance, admittance of ckt is purely conductance

$$Y_r = \frac{R}{R^2 + \omega_r^2 L^2} \quad \text{--- (2)}$$

from (1)

$$R^2 + \omega_r^2 L^2 = \frac{L}{C}$$

sub (1) in (2)

$$Y_r = \frac{R}{\frac{L}{C}} = \frac{RC}{L}$$

$$Y_r = \frac{RC}{L}$$

$$\therefore Z_r = \frac{L}{RC} \quad \text{--- dynamic resistance}$$


# Network Analysis

## parallel resonance

(1)

Resonance  $\rightarrow V_g$  &  $I$  in phase.

Here elements are connected in parallel.

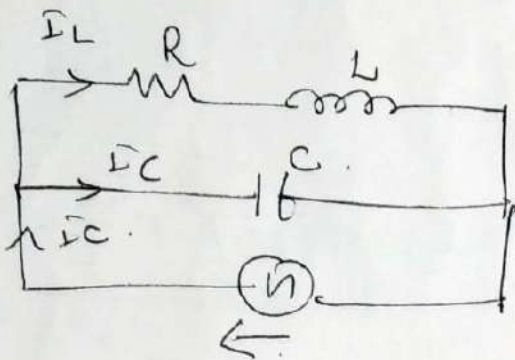

Impedance  $\rightarrow$  admittance  
 $R \rightarrow$  conductance  
 reactance  $\rightarrow$  susceptance.

practical practical resonant ckt

Consists of an inductive coil of resistance  $R$  & an inductance  $L$  placed in parallel with capacitance  $C$ . Connected to an alternating  $V_g$  of variable freq  $f$ .

Impedance of coil is

$$Z_L = R + j\omega L$$

Admittance of coil is

$$Y_L = \frac{1}{Z_L} = \frac{1}{R + j\omega L} \times \frac{R - j\omega L}{R - j\omega L} = \frac{R - j\omega L}{R^2 + \omega^2 L^2}$$

$$Z_C = -\frac{j}{\omega C}$$

$$Y_C = \frac{1}{Z_C} = \frac{\omega C}{-j} \times \frac{j}{j} = j\omega C$$

Total admittance of the coil is

$$Y = Y_L + Y_C$$

$$= \frac{R - j\omega L}{R^2 + \omega^2 L^2} + j\omega C$$

$$= \frac{R}{R^2 + \omega^2 L^2} + j \left( \frac{\omega C - \omega L}{R^2 + \omega^2 L^2} \right)$$

At resonance, impedance of ckt is purely resistive.  
 Admittance must be purely conductive.  
 $\therefore$  imaginary part is zero.

At resonance,

$$\omega_r C - \frac{\omega_r L}{R^2 + \omega_r^2 L^2} = 0$$

$$\omega_r C = \frac{\omega_r L}{R^2 + \omega_r^2 L^2} \Rightarrow \boxed{R^2 + \omega_r^2 L^2 = \frac{L}{C}}$$

$$\omega_r^2 L^2 = \frac{L}{C} - R^2$$

$$\omega_r^2 = \frac{\frac{L}{C} - R^2}{L^2} = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\omega_r = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\& \therefore \boxed{f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}}$$

At resonance, admittance of ckt is purely conductive.

$$Y_r = \frac{R}{R^2 + \omega_r^2 L^2}$$

$$Y_r = \frac{R}{\frac{L}{C}}$$

$$\therefore \text{from } \textcircled{1} \\ R^2 + \omega_r^2 L^2 = \frac{L}{C}$$


$$Y_r = \frac{RC}{L}$$

or  $\boxed{Z_r = \frac{L}{RC}} \Rightarrow \text{dynamic resistance.}$

Current at resonance is given by

$$I_r = \frac{E}{Z} = \frac{E \times 1}{\frac{L}{RC}} = \frac{E RC}{L}$$

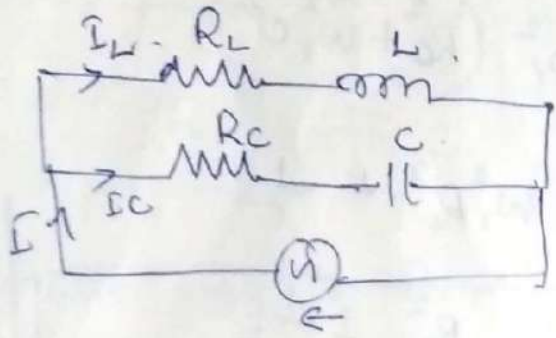parallel resonant ckt considering capacitance to have resistance



Consider a parallel ckt as shown.

$$Z_L = R_L + j\omega L$$

$$\therefore Y_L = \frac{1}{R_L + j\omega L} \times \frac{R_C + j\omega L}{R_C + j\omega L} = \frac{R_L - j\omega L}{R^2 + \omega^2 L^2}$$

$$Z_C = R_C - j \frac{1}{\omega C}$$

$$Y_C = \frac{1}{R_C - j \frac{1}{\omega C}} \times \frac{R_C + j \frac{1}{\omega C}}{R_C + j \frac{1}{\omega C}} = \frac{R_C + j \frac{1}{\omega C}}{R_C^2 + \frac{1}{\omega^2 C^2}}$$

Total admittance Y

$$Y = Y_L + Y_C = \frac{R_L - j\omega L}{R_L^2 + \omega^2 L^2} + \frac{R_C + j \frac{1}{\omega C}}{R_C^2 + \frac{1}{\omega^2 C^2}}$$

$$= \left( \frac{R_L}{R_L^2 + \omega^2 L^2} + \frac{R_C}{R_C^2 + \frac{1}{\omega^2 C^2}} \right) + j \left[ \frac{\frac{1}{\omega C}}{R_C^2 + \frac{1}{\omega^2 C^2}} - \frac{\omega L}{R_L^2 + \omega^2 L^2} \right]$$

At resonance,

Admittance of ckt is purely conductive.

∴ imaginary part is 0.

$$\therefore \frac{1}{\omega C} \frac{1}{R_C^2 + \frac{1}{\omega^2 C^2}} = \frac{\omega L}{R_L^2 + \omega^2 L^2}$$

$$\frac{R_L^2 + \omega_r^2 L^2}{\omega_r C} = \omega_r L \left( R_C^2 + \frac{1}{\omega_r^2 C^2} \right)$$

$$\frac{1}{LC} (R_L^2 + \omega_r^2 L^2) = \omega_r^2 \left( R_C^2 + \frac{1}{\omega_r^2 C^2} \right)$$

$$\frac{R_L^2}{LC} + \frac{\omega_r^2 L}{C} = \omega_r^2 R_C^2 + \frac{1}{C^2}$$

$$\boxed{\omega_r^2 \left( R_C^2 - \frac{L}{C} \right) = \frac{R_L^2}{LC} - \frac{1}{C^2}} \\ = \frac{1}{LC} \left( R_L^2 - \frac{L}{C} \right)$$

$$\therefore \omega_r^2 = \frac{\frac{1}{LC} \left( R_L^2 - \frac{L}{C} \right)}{R_C^2 - \frac{L}{C}}$$

$$\omega_r = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L^2 - \frac{L}{C}}{R_C^2 - \frac{L}{C}}}$$

$$\boxed{f_r = \frac{1}{2\pi \sqrt{LC}} \sqrt{\frac{R_L^2 - \frac{L}{C}}{R_C^2 - \frac{L}{C}}}}$$

Condition should be 0

$$\omega_r^2 \left( R_C^2 - \frac{L}{C} \right) = \frac{1}{LC}$$

$$R_C^2 - \frac{L}{C} = 0$$


$$\text{or } R_C^2 - \frac{L}{C} > 0$$

The admittance at resonance is purely conductive


$$Y_r = \frac{R_L}{R_L^2 + \omega_r^2 L^2} + \frac{R_C}{R_C^2 + \frac{1}{\omega_r^2 C^2}}$$

Current at resonance is given by
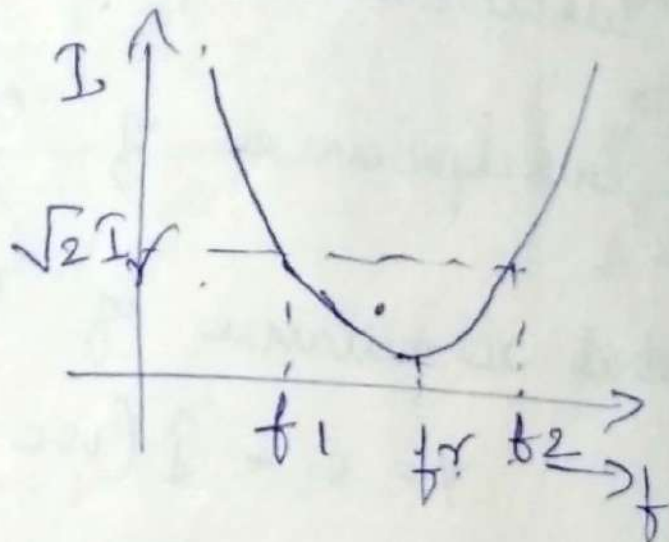
$$I_r = E Y_r = \frac{E}{Z} \\ = E \left[ \frac{R_L}{R_L^2 + \omega_r^2 L^2} + \frac{R_C}{R_C^2 + \frac{1}{\omega_r^2 C^2}} \right]$$




Q factor of a parallel resonant ckt.

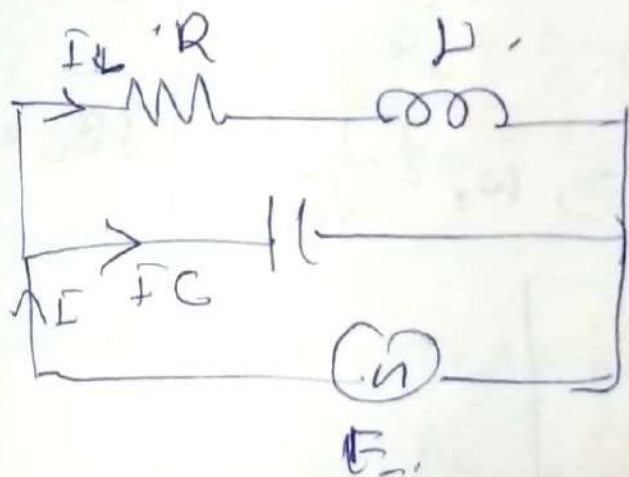

$V \angle -$   
 $L \rightarrow$

vector diagram is shown

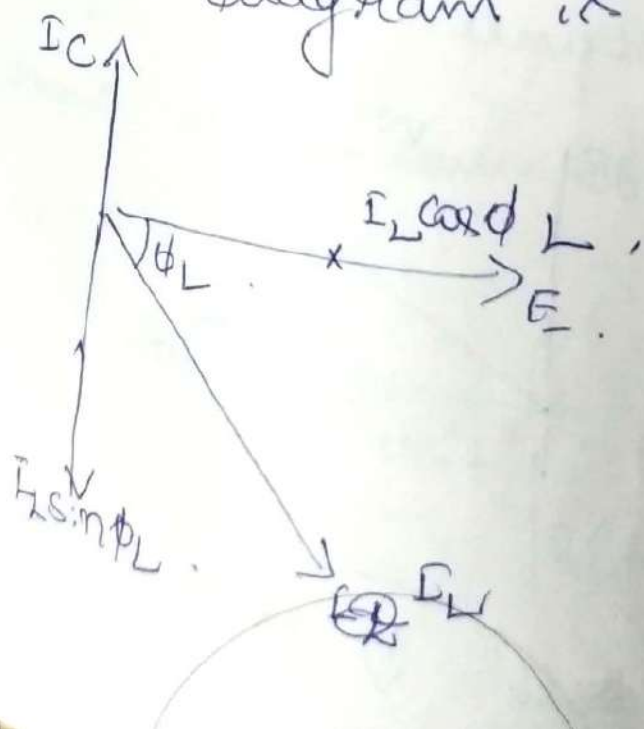

$I_L$  lags  $V$   
 $I_C$  leads  $V$   
 $Z = \sqrt{R^2 + (\omega L)^2}$   
 $\theta = \tan^{-1} \left( \frac{\omega L}{R} \right)$

Quality factor of a parallel resonant circuit

At resonance only reactive elements flow through 2 branches. ( $I_L \sin \phi_L$ ) through R-L branch &  $I_C$  through capacitance. These currents will be many times more than the total current at resonance.

The quality factor of parallel resonant ckt is defined as current magnification.

$$Q_p = \frac{\text{current through capacitor at resonance}}{\text{Total current at resonance}}$$

$$X_C = \frac{-j}{\omega C} \Rightarrow Y_C = \frac{\omega C}{-j} \times \frac{j}{j} = \dots$$

Reactance/susceptance

$$= \frac{I_C}{I_T}$$

$$= \frac{E Y_C}{E Y_2} = \frac{E Y_C}{E Y_2}$$

$$= \frac{E \omega C}{\frac{E R C}{R \omega L}} = \frac{\omega R C}{\frac{R C}{L}}$$

$$= \frac{\omega R C}{R} \cdot \frac{L}{R C}$$

$$= \frac{\omega L}{R}$$

$$= \frac{X_L}{R}$$

$$= Q_s$$

$$Y_r = \frac{R}{R^2 + \omega^2 L^2}$$

$$Y_r = \frac{R}{L^2/C}$$

$$Y_r = \frac{R C}{L}$$

$$\text{or } Z_r = \frac{L}{R C}$$

$$X_L = j \omega L$$

$$\frac{1}{X_L} = \frac{1}{j \omega L} \times \frac{j}{j} = \frac{j}{-j \omega L}$$

$$\frac{E Y_L}{E Y_2} = \frac{1}{\frac{R C}{L}}$$

∴ quality factor of series & parallel resonant ckt is same.



To derive  $f_1, f_2, \Rightarrow$  impedance of parallel RLC  
 is 0.707 times value of max impedance at  $\sqrt{2}$

freq deviation i.e.  $2 = \frac{R_L Q_0^2}{1 + f^2 2 Q_0^2}$  } deriv not required

$$s = \pm \frac{1}{2 Q_0}$$

~~$f_2 - f_1 = f$~~

frequency deviation  $\rightarrow$  ratio of diff b/w operating freq & resonant freq to that of  $f_r$

$$s = \frac{f - f_r}{f_r} = \pm \frac{1}{2 Q_0}$$

B.W of parallel ckt is given by

$$B.W = f_2 - f_1 = \frac{\text{resonant freq}}{\text{Quality factor}} = \frac{f_r}{Q_p}$$

$$\boxed{f_2 - f_1 = \frac{f_r}{Q_p}} \Rightarrow Q_p = \frac{f_r}{f_2 - f_1}$$

$$\text{Selectivity} = \frac{\text{Resonant freq}}{B.W} = \frac{f_r}{f_2 - f_1}$$

$$\boxed{\text{Selectivity} = \frac{f_r}{f_2 - f_1} = Q_p}$$

increases with

$$f_2 - f_1 = \frac{R}{\omega L}$$

$$Q = \frac{X_L}{R} = \frac{\omega L}{R} = \frac{2\pi f L}{R}$$

$$Q = \frac{f_r}{f_2 - f_1}$$

$$\boxed{Q = \frac{f_r}{B.W}}$$


So also,

$$I_L = Q_0 I$$

$$I_C = Q_0 I$$

Current through inductor & capacitor are  $Q$  times supplied current at antiresonance.

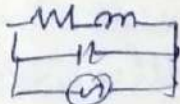Frequency of parallel resonance can be written in another form as follows



(5)

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$= \frac{1}{2\pi} \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{CR^2}{L}}$$

$\therefore =$

$$f_r = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{1}{Q^2}}$$

This eqn indicates that freq differs from that of series ckt with the same elements by a factor  $\sqrt{1 - \frac{1}{Q^2}}$ .

For high quality factor circuits, frequency of series & parallel ckt are almost same.

$$Q = \frac{\omega L}{R} = \frac{1}{\omega R C}$$

$$Q = \frac{1}{\omega R C} \Rightarrow \omega = \frac{1}{QR C}$$

$$Q = \frac{\omega L}{R} = \frac{1}{QR C} \cdot L$$

$$Q = \frac{RL}{QR C}$$


$$Q = \frac{L}{CR^2}$$

$$Q = \frac{L}{QR C}$$

$$Q = \frac{L}{QR^2 C}$$

$$Q^2 = \frac{L}{CR^2}$$

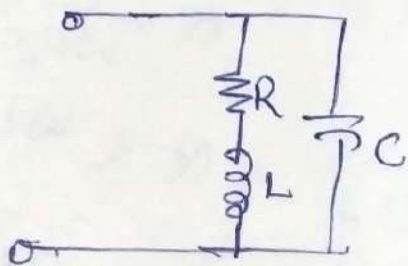In the ckt given below, an inductance having a Q of 5 is in parallel with a capacitor & a resistor. Determine the value of capacitance & at resonant freq of 500 rad/sec.



$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\text{or } f_r = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{1}{Q_0^2}}$$

$$(2\pi f_r)^2 = \frac{1}{LC} \sqrt{1 - \frac{1}{Q_0^2}}$$

$$(2\pi f_r)^2 = \frac{1}{LC} \left(1 - \frac{1}{Q_0^2}\right)$$

$$C = \frac{1}{(2\pi f_r)^2 \times L} \left(1 - \frac{1}{Q_0^2}\right)$$

$$= \frac{1}{(500)^2 \times 0.1} \left(1 - \frac{1}{5^2}\right)$$

$$= 38.4 \times 10^{-6} \text{ F}$$


$$\boxed{C = 38.4 \mu\text{F}}$$

$$Q = \frac{\omega L}{R} \Rightarrow R = \frac{\omega L}{Q}$$

$$R = \frac{100}{500 \times 0.1}$$

$$\boxed{R = 10 \Omega}$$

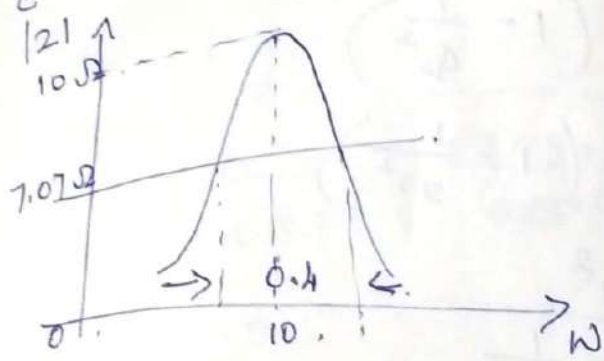Determine the R-L-C parallel ckt parameters whose response curve is as shown in fig. what are the new values of  $\omega_r$  and bandwidth if  $C$  is increased 4 times?



From fig.  $Z_r = 10\Omega$ .  $\omega_r = 10 \text{ rad/sec}$ .  
 $B.W = 0.4 \text{ rad/s}$ .

Cons. det  
 Sd parallel ckt

$$\therefore Z_r = \frac{L}{RC} = 10\Omega$$

$$Q_p = \frac{f_r}{BW} = \frac{\omega_r}{BW}$$

$$Q_p = \frac{10}{0.4} = 25$$

$$1) \boxed{Z_r = R(1 + Q_0^2)}$$

$$10 = R(1 + 25^2)$$

$$R = \frac{10}{1 + 25^2}$$

$$= 0.01597\Omega$$

$$Z_r = \frac{L}{RC}$$

$$10 = \frac{L}{RC} \Rightarrow \frac{L}{C} = R(10)$$

$$\Rightarrow \frac{L}{C} = (0.01597)(10)$$

$$\frac{L}{C} = 0.1597$$

$$B.W = \frac{f_r}{Q_p}$$

In den.

$$R^2 + \omega^2 L^2 = \frac{L}{C}$$

$$R^2 \left(1 + \frac{\omega^2 L^2}{R^2}\right) = \frac{L}{C}$$

$$R^2(1 + Q_0^2) = \frac{L}{C}$$

$$R(1 + Q_0^2) = \frac{L}{CR}$$

$$R(1 + Q_0^2) = 2$$

$$f_r = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{1}{Q_0^2}}$$

$$W_r = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{1}{Q_0^2}}$$

$$W_r^2 = \frac{1}{LC} \left(1 - \frac{1}{Q_0^2}\right)$$

$$(10)^2 = \frac{1}{LC} \left(1 - \frac{1}{25^2}\right)$$

$$\frac{1}{LC} = \frac{10^2}{1 - \frac{1}{25^2}}$$

$$\frac{1}{LC} = 100.16$$

$$LC = 9.984 \times 10^{-3} \quad \text{--- (2)}$$

$$\text{we have } \frac{L}{C} = 0.1597 \Rightarrow C = \frac{L}{0.1597} \quad \text{--- (3)}$$

$$\text{Sub (3) in (2)}$$

$$L \frac{L}{0.1597} = 9.984 \times 10^{-3}$$

$$L = 0.03993 \text{ H}$$

$$L = 39.93 \text{ mH}$$

from (3)

$$C = \frac{L}{0.1597} = 0.25 \text{ F}$$

$$L = 39.93 \text{ mH}$$

$$C = 0.25 \text{ F}$$

$$R = 0.01597$$

Now if  $C' = 4C = 4(0.25) = 1F$  used in the ckt. (7)

$$f_{r_{new}} = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{1}{Q_0^2}}$$

$$Q_0' = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$= \frac{1}{0.01597} \sqrt{\frac{39.93 \text{ mH}}{1F}}$$

$$= 12.51$$

$$f_r = \frac{1}{2\pi\sqrt{LC}} \left( \sqrt{1 - \frac{1}{Q_0^2}} \right)$$

$$W_{s_{new}} = \frac{1}{\sqrt{LC}} \left( \sqrt{1 - \frac{1}{Q_0^2}} \right)$$

$$= \frac{1}{\sqrt{39.93 \text{ mH} \times 1}} \left( \sqrt{1 - \frac{1}{(12.51)^2}} \right)$$

$$0.9967$$

$$= 4.988 \text{ rad/s}$$


$$W_r = \frac{1}{2\pi\sqrt{LC}}$$

$$W_r = \frac{1}{LC}$$

$$\therefore 5 \text{ rad/s}$$

$$B.W = \frac{W_r}{Q_0} = \frac{4.988}{12.51} = 0.399 \text{ rad/sec} \approx 0.4 \text{ rad/sec}$$

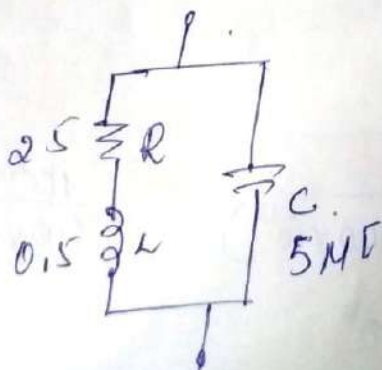3) If  $R = 25\Omega$ ,  $L = 0.5H$ ,  $C = 5\mu F$ . find  $W_r$ ,  $Q$  and bandwidth for the ckt shown.



$$W_r = \frac{1}{\sqrt{LC}}$$

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$W_r = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$= \sqrt{\frac{1}{0.5 \times 5 \times 10^{-6}} - \frac{(25)^2}{(0.5)^2}}$$

$$= 630.476 \text{ rad/sec.}$$


$$Q = \frac{WL}{R}$$

$$= \frac{630.476 \times 0.5 \text{ H}}{25}$$

$$= 12.6095$$

$\frac{1}{2}W_1$  B.W =  $\frac{W_r}{Q_0} = \frac{630.476}{12.6095} = 50 \text{ rad/sec.}$

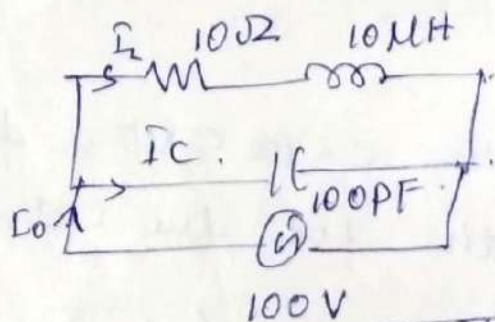For the parallel resonant ckt shown in fig find  $I_0$ ,  $I_L$ ,  $I_C$ ,  $f_0$  & dynamic resistance.



$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$


$$= \frac{1}{2\pi} \sqrt{\frac{1}{(10 \times 10^{-6})(100 \times 10^{-12})} - \frac{10^2}{(10 \times 10^{-6})^2}}$$

$$= \frac{1}{2\pi} 316067 \times 10^6$$

$$f_0 = 5.0298 \text{ MHz.}$$

A coil of R =  
k a capacitor  
= 50 Hz. A  
this ckt  
Comb n at  
total th  
applied

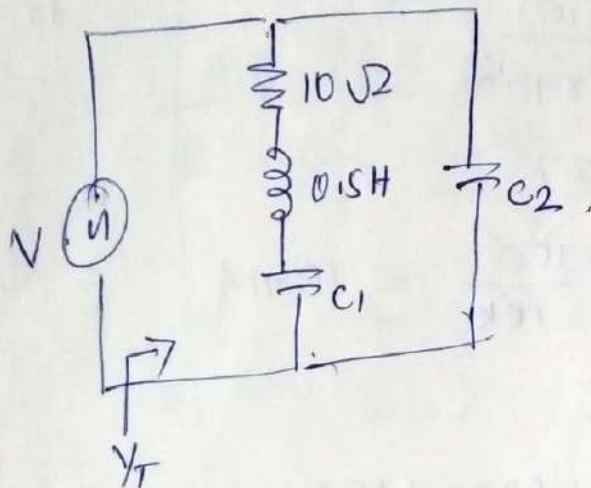A coil of  $R=10\Omega$  and  $L=0.5H$  is connected in series with a capacitor. The current is maximum when  $f=50Hz$ . A second capacitor is connected in parallel with this ckt. what capacitance must it have so that the combn acts like a non inductive resistor at  $100Hz$ . calculate the total current supplied in each case if the applied  $V_T$  is  $220V$ .



$$f_0 = 50Hz.$$

let us calculate  $C_1$  first,

$$f_0 = \frac{1}{2\pi\sqrt{LC_1}}$$

$$\sqrt{LC_1} = \frac{1}{2\pi f_0}$$

$$LC_1 = \frac{1}{(2\pi f_0)^2}$$

$$C_1 = \frac{1}{(2\pi f_0)^2 \times L}$$

$$= 20.258 \times 10^{-6} F$$

$$C_1 = 20.258 \mu F.$$



$$Z = \frac{L}{CR}$$

$$= \frac{10 \mu}{100 \mu \times 10}$$

$$= 10 \text{ k} \Omega$$

$$Q_0 = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$= \frac{1}{10} \sqrt{\frac{10 \times 10^{-6}}{100 \times 10^{-12}}}$$

$$= 31.6227$$


$$I_0 = \frac{V}{Z} = \frac{100}{10 \text{ k}} = 10 \text{ mA}$$

$$I_C = I_L = Q I$$

$$= 31.6227 \times 10 \text{ mA}$$

$$= 316.227 \text{ mA}$$

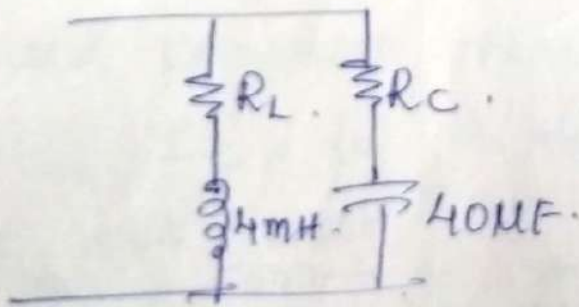Determine  $R_L$  and  $R_C$  for which circuit shown in figure resonate at all frequencies.



$$\frac{R_L^2 - \frac{L}{C}}{R_C^2 - \frac{L}{C}} = 1$$

$$R_L^2 - \frac{L}{C} = R_C^2 - \frac{L}{C}$$

$$R_L^2 = R_C^2$$

$$f_r = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{R_L^2 - \frac{L}{C}}{R_C^2 - \frac{L}{C}}}$$

$$R_L^2 - \frac{L}{C} = 0$$

$$R_L^2 = \frac{L}{C}$$

$$R_L = \sqrt{\frac{L}{C}}$$

$$= \sqrt{\frac{10 \times 10^{-6}}{40 \times 10^{-6}}}$$

$$= 10 \Omega$$

$$R_C = \sqrt{\frac{L}{C}}$$

$$R_C = 10 \Omega$$

$C_2$  is connected in parallel with the above circuit. (9)

Admittance

$$\begin{aligned}
 Y_T &= \frac{1}{R + j\left(\omega L - \frac{1}{\omega C_1}\right)} + \frac{1}{-j\omega C_2} \\
 &= \frac{1}{R + j\left(\omega L - \frac{1}{\omega C_1}\right)} + j\omega C_2 \\
 &= \frac{R - j\left(\omega L - \frac{1}{\omega C_1}\right)}{R^2 + \left(\omega L - \frac{1}{\omega C_1}\right)^2} + j\omega C_2 \\
 &= \frac{R}{R^2 + \left(\omega L - \frac{1}{\omega C_1}\right)^2} + j\left[\omega C_2 - \frac{\left(\omega L - \frac{1}{\omega C_1}\right)}{R^2 + \left(\omega L - \frac{1}{\omega C_1}\right)^2}\right]
 \end{aligned}$$

Above resonance, it must be purely resistive.

Hence susceptance should be 0.

At  $f = 100 \text{ Hz}$

$$\omega C_2 - \frac{\left(\omega L - \frac{1}{\omega C_1}\right)}{R^2 + \left(\omega L - \frac{1}{\omega C_1}\right)^2} = 0$$

$$\omega C_2 = \frac{\left(\omega L - \frac{1}{\omega C_1}\right)}{R^2 + \left(\omega L - \frac{1}{\omega C_1}\right)^2}$$

$$C_2 = \frac{\omega\left(L - \frac{1}{\omega^2 C_1}\right)}{\omega\left[R^2 + \left(\omega L - \frac{1}{\omega C_1}\right)^2\right]}$$

$$C_2 = \frac{0.5}{\frac{1}{(2\pi \times 100)^2 \times (20.2642 \times 10^{-6})}}$$

$$10^2 + \left(2\pi \times 100 \times 0.5 - \frac{1}{(2\pi \times 100 \times 20.2642 \times 10^{-6})}\right)^2$$

$$\frac{0.5 - 0.125}{(10)^2 + 55540.45}$$

$$= 6.7426$$

$$= 6.7397 \text{ MF}$$

with  $C_1$  only in series RLC ckt, max current given by

$$I_0 = \frac{V}{R} = \frac{220}{10} = 22 \text{ A}$$

with  $C_2$  in ckt, impedance at ckt resonance

$$Y = \frac{R}{R^2 + \left(\omega L - \frac{1}{\omega C_1}\right)^2}$$

$$Z = \frac{R^2 + \left(\omega L - \frac{1}{\omega C_1}\right)^2}{R}$$

$$= \frac{(10)^2 + \left[2\pi \times 100 \times 0.5 - \left(\frac{1}{(2\pi \times 100 \times 20.2642 \times 10^{-6})}\right)\right]^2}{10}$$

$$= \frac{100 + \left(314.2 - \frac{78.529}{\cancel{7852.97}}\right)^2}{10}$$


$$= \frac{\cancel{100} \cancel{56.833} \times 10^6}{\cancel{10}} = \frac{100 + 55540.82}{10}$$

$$= \cancel{5.683} \times 10^6 \Omega = 5.564 \times 10^3 \Omega$$

Max Current

$$I_0 = \frac{220}{Z_{\text{ar}}} = \frac{220}{5.564 \times 10^3} = 39.55 \text{ mA}$$

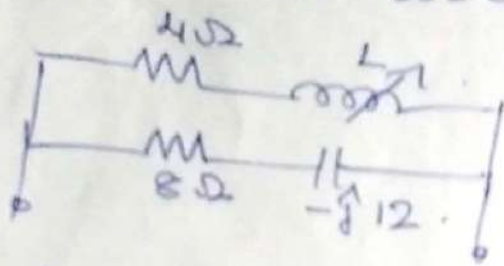Find the value of  $L$  for which given ckt resonates at  $\omega = 5000 \text{ rad/sec}$ . (10)



Total admittance of ckt is given by.

$$Y = \left[ \frac{1}{4 + jX_L} + \frac{1}{8 - j12} \right] V$$

$$= \frac{4 - jX_L}{16 + X_L^2} + \frac{8 + j12}{8^2 + 12^2}$$

$$= \left( \frac{4}{16 + X_L^2} + \frac{8}{8^2 + 12^2} \right) + j \left( \frac{12}{8^2 + 12^2} - \frac{X_L}{16 + X_L^2} \right)$$

At resonance, imaginary part is zero.

$$\frac{12}{8^2 + 12^2} - \frac{X_L}{16 + X_L^2} = 0$$

$$\frac{12}{8^2 + 12^2} = \frac{X_L}{16 + X_L^2}$$

$$\frac{3}{52} = \frac{X_L}{16 + X_L^2}$$

$$3X_L^2 + 48 = 52X_L$$

$$3X_L^2 - 52X_L + 48 = 0$$

$$X_L^2 - \frac{52}{3}X_L + 16 = 0$$

$$X_L = 16.36 \text{ or } 0.978$$

$$\text{or } \omega L = 16.36$$

$$\text{or } \omega L = 0.978$$

$$L = 3.27 \text{ mH}$$

$$L = 0.196 \text{ mH}$$

$$X_L = \frac{52 \pm \sqrt{\left(\frac{52}{3}\right)^2 - 4}}{2}$$

$$= \frac{52 \pm 15.377}{2}$$

$$= 16.355 \text{ or } 0.9$$

problems on series resonance  $Z = R \sqrt{1 + Q^2} \delta \left( \frac{2+s}{1+s} \right)$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$Q = \frac{V_L}{V} \text{ or } V_L = QV$$

$$f_0 = \sqrt{f_1 f_2}$$

$$Q = \frac{V_C}{V} \text{ or } V_C = QV$$

$$B.W = f_2 - f_1$$

$$Q = \frac{X_L}{R} = \frac{\omega_0 L}{R}$$

$$B.W = \frac{f_0}{Q}$$

$$Q = \frac{1}{\omega_0 C R}$$

$$B.W = \frac{R}{2\pi L}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$f_c = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

$$Q = \frac{f_0}{f_2 - f_1}$$

$$f_L = \frac{1}{2\pi \sqrt{LC - \frac{R^2 C^2}{2}}}$$

1. In a series RLC ckt driven with a sinusoidal a.c voltage source determine value of C required to achieve resonance in a ckt at 5kHz if value of resistance & inductance are  $2\Omega$  and  $1mH$  respectively.

$$R = 2\Omega \quad L = 1mH,$$

$$f_0 = 5kHz$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$V_L = I_0(jX_L)$$

$$\sqrt{LC} = \frac{1}{2\pi f_0}$$

$$= j \frac{V}{R} (\omega_0 L)$$

$$LC = \frac{1}{(2\pi f_0)^2}$$

$$= j(Q_0)V$$

$$C = \frac{1}{(2\pi f_0)^2 \times L}$$

$$V_C = I_0(-jX_C)$$

$$= \frac{V}{R} (-j/\omega C)$$

$$= 1.013 \times 10^{-6} F$$

$$= -jVQ_0$$

$$= 1.013 \mu F$$

A series RLC ckt consists of a resistance of  $1\text{ k}\Omega$  & an inductance of  $100\text{ mH}$  in series with a capacitance of  $10\text{ pF}$ . If  $100\text{ V}$  is applied as  $\text{r.m.s}$  across the combn determine

- i) resonant freq
- ii) max current in the ckt
- iii) Q factor of ckt
- iv) half-power frequencies

$$R = 1\text{ k}\Omega$$

$$L = 100\text{ m}$$

$$C = 10\text{ pF}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{100 \times 10^{-3} \times 10 \times 10^{-12}}}$$

$$= 159.13\text{ kHz}$$

$$i) I_0 = \frac{V}{R} = \frac{100}{1000} = 0.1\text{ A}$$

$$iii) Q_0 = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{1000} \sqrt{\frac{100\text{ m}}{10 \times 10^{-12}}} = 100$$

$$or Q = \frac{\omega L}{R} = \frac{2\pi f \times L}{R} = 100$$

iv)

iv)  $f_1$  &  $f_2$

$$f_1 = \frac{1}{2\pi} \left[ -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right]$$

$$f_2 = \frac{1}{2\pi} \left[ \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right]$$

$$\sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} = \sqrt{\left(\frac{1000}{2 \times 100 \times 10^{-3}}\right)^2 + \frac{1}{100 \times 10^{-3} \times 10 \times 10^{-12}}}$$

$$= 1000002.5$$


$$f_1 = \frac{1}{2\pi} \frac{R}{2L} = \frac{1000}{2 \times 100 \times 10^{-3}} = 5000$$

$$f_1 = \frac{1}{2\pi} \left[ -5000 + 1000002.5 \right]$$

$$= 158.339 \text{ kHz}$$

$$f_2 = \frac{1}{2\pi} \left[ 5000 + 1000002.5 \right] \quad \pi = 3.142$$

$$= 159.93 \text{ kHz}$$

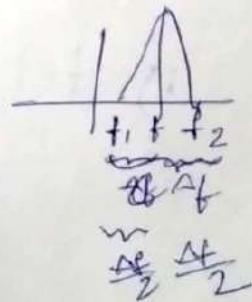

or B.W  $\Delta f = f_2 - f_1 = \frac{R}{2\pi L}$

$$\Delta f = \frac{R}{2\pi L}$$

$$\Delta f = \frac{R}{2\pi L} = \frac{1000}{2\pi \times 100 \times 10^{-3}} = 795.67 \text{ Hz}$$

$$= 1591.34 \text{ Hz}$$

$$f_1 = f_0 - \frac{\Delta f}{2} = 159.13 \text{ kHz} - 795.67 = 158.33 \text{ kHz}$$

$$f_2 = f_0 + \frac{\Delta f}{2} = 159.13 \text{ kHz} + 795.67 = 159.93 \text{ kHz}$$

In series RLC ckt with variable capacitance, the current is at max value with capacitance of 20  $\mu\text{F}$  and the current reduces 0.707 times of max value with capacitance of 30  $\mu\text{F}$ .

Find the values of R and L.

What is the B.W of ckt if supply  $V_g$  is  $20 \sin(6.28 \times 10^3)t$  Volts.

$$V = V_m \sin \omega t$$

$$\omega = 6.28 \times 10^3$$

~~f~~ This is tuning ckt  $\Rightarrow f_i = f_r$ .

$$f_r = \frac{\omega}{2\pi} = \omega = 2\pi f \Rightarrow f = \frac{\omega}{2\pi}$$

$$f_0 = f_r = \frac{6.28 \times 10^3}{2 \times \pi} = 1000 \text{ Hz}$$

$$f_0 = \frac{1}{2\pi \sqrt{LC}} \quad \text{at resonance } C = 20 \mu\text{F}$$

$$\sqrt{LC} = \frac{1}{2\pi f_0}$$

$$L = \frac{1}{(2\pi f_0)^2 C}$$

$$= \frac{1}{(2\pi \times 1000)^2 \times 20 \times 10^{-6}}$$

$$L = 1.2662 \text{ mH}$$



At half power freq current becomes 0.707 times

of its max value with  $C = 30 \mu F$  & ~~resistor~~ Resistance

at this stage reactance is given by

$$|X| = X_L - X_C = \left( \omega L - \frac{1}{\omega C} \right)$$

$$\omega L = 2\pi f_0 L = 2\pi \times 1000 \times 1.2662 \times 10^{-3} = 7.957 \Omega$$

$$\omega C = 2\pi f_0 C = 2\pi \times 1000 \times 30 \times 10^{-6} = \cancel{0.1885} \Omega$$

$$5.307 \Omega$$

$$|X| = \left( 7.957 - \frac{1}{0.1885} \right)$$

$$X = 2.652 \Omega$$

$$Z = R + jX =$$

$$\therefore \text{Resistance } R = X = 2.652 \Omega$$

At

$$Z = R + j(X_L - X_C)$$

At  $f_0$   $Z = R$

$$\text{at } f_1 = 2 = \sqrt{2}R$$

$$f_1 R = X_L - X_C$$

$$f_2 R = X_C - X_L$$


$$B.W = \frac{f_0}{Q_0} = \frac{f_0}{\frac{\omega_0 L}{R}} = 100$$

$$Q = \frac{\omega_0 L}{R} = \frac{7.957}{2.652} = 3$$

$$\therefore B.W = \frac{f_0}{Q} = \frac{1000 \pm 12}{3} = 333.33 \text{ Hz}$$

For the ckt shown. Determine the following

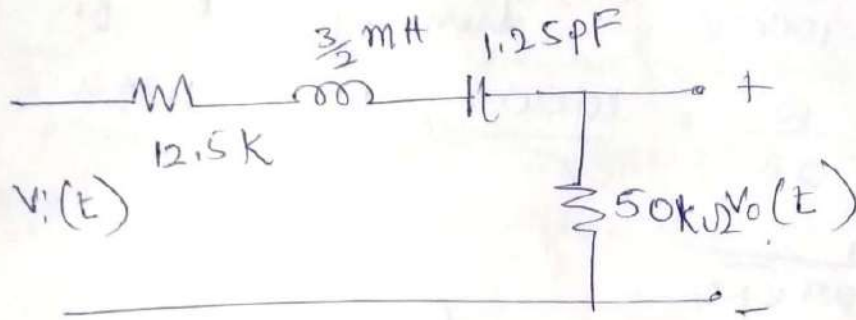- i)  $f_0$
- ii)  $Q$
- iii) Half power freq.
- iv) Bandwidth



$$\text{total } R = 12.5k + 50k = 62.5k$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{\frac{3}{2} \times 10^{-3} \times 1.25 \times 10^{-12}}}$$

$$= 3.675 \text{ MHz} = 3675049.454 = 36750.495 \times 10^3$$

$$Q = \frac{\omega L}{R} = \frac{2\pi f_0 L}{R} = \frac{2\pi f_0 L}{R} = 5.543$$

$$\text{or } B_0 = \frac{1}{R} \sqrt{\frac{L}{C}} =$$

$$B.W = \Delta f = f_2 - f_1 = \frac{f_0}{Q} = \frac{36750.495 \times 10^3}{5.543}$$

$$\Delta f = 6630.073 \text{ kHz}$$

~~$$\Delta f = 3315.037 \text{ kHz}$$~~

$$f_1 = f_0 - \frac{\Delta f}{2} = 33435.458 \times 10^3 = 33.435 \times 10^6$$

$$f_2 = f_0 + \frac{\Delta f}{2} = 40065.5 \text{ kHz} = 40.066 \text{ MHz}$$

6) A coil is connected in series with a variable capacitor across  $v(t) = 10 \cos 1000t$ . The capacitor is varying & current is max when  $C = 10 \mu F$ . when  $C = 12.5 \mu F$ , the current is 0.707 times the max value. Find  $L, R$  &  $Q$  of the coil.

$\omega = 1000 \text{ rad/s}$  tuning ckt  $f_1 = f_r$   
 $f_0 = \frac{\omega}{2\pi} = \frac{1000}{2\pi} = 159.134 \text{ Hz}$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

at  $f_0 \Rightarrow C = 10 \times 10^{-6}$

$$\sqrt{LC} = \frac{1}{2\pi f}$$

$$L = \frac{1}{(2\pi f)^2 \times C} = \frac{1}{(2\pi \times 159.134)^2 \times 10 \times 10^{-6}}$$

$L = 0.1 \text{ H}$

f. & b. 2.

$$R = \sqrt{X_L - X_C}$$

$$= \omega L - \frac{1}{\omega C}$$

$$\left\{ \begin{aligned} \omega L &= 1000 \times 0.1 = 100 \\ \omega C &= 1000 \times 12.5 \times 10^{-6} = 0.0125 \end{aligned} \right.$$

$$R = \left[ 100 - \frac{1}{0.0125} \right]$$

$$R = 20 \Omega$$

$$Q = \frac{\omega L}{R} = \frac{1000 \times 0.1}{20} = \frac{100}{20} = 5$$