

"An electric circuit (or) electric network is an inter-connection of electrical elements linked together in a closed path so that an electric current may continuously flow."

* "Charge is the quantity of electricity responsible for electric phenomena".

* The time rate of change constitutes an electric current

$$i(t) = \frac{dq(t)}{dt} \quad (\text{or}) \quad q(t) = \int_{-\infty}^t i(x) dx. \quad \text{C/Sec}$$

* "Current is the time rate of flow of electric charge past a given point".

* "Electrical Potential (Voltage) at any point in a charged conductor is defined as the work done to bring a unit charge from ∞ to that point."

The unit of voltage is volt (V). (or) (E)

$$V = \frac{dW}{dq} \quad \text{J/Coulomb}$$

* Power is defined as the rate at which, the work is done (W).

$$P = EI = \frac{E^2}{R} = I^2R$$

$$(\text{or}) \quad P = VI = \frac{V^2}{R} = I^2R$$

* Energy is the Capacity to do work (kWh or unit).

$$W = EIt = \frac{E^2 t}{R} = I^2 R t.$$

Elements of an Electric Circuit:-

Electric circuit consists of 2 types of elements.

- 1) Active elements (or) Sources.
- 2) Passive elements (or) Sinks.

1) Active elements:- "They are the elements of a ckt which possess energy of their own & can impart it to other elements of the ckt." [Independent Sources].


There are 2 types of active elements,

- i) Voltage Source
- ii) Current Source

i) "An ideal voltage source is one, which delivers energy to a load at a constant terminal voltage, irrespective of the current drawn by the load."

ii) "An ideal current source is one, which delivers energy with a constant current to the load, irrespective of the terminal voltage across the load."


* Symbolically

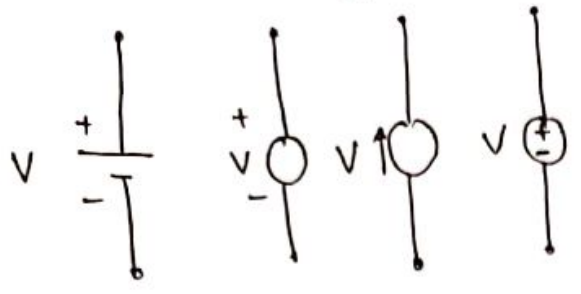


(a) Ideal D.C. Voltage Sources (Time Invariant SRCs)




(b) Ideal D.C. Current Sources.

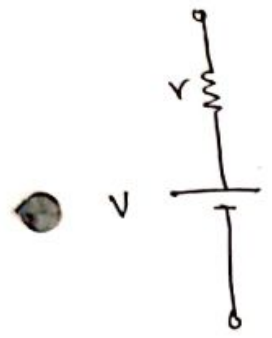


(c) Practical voltage source

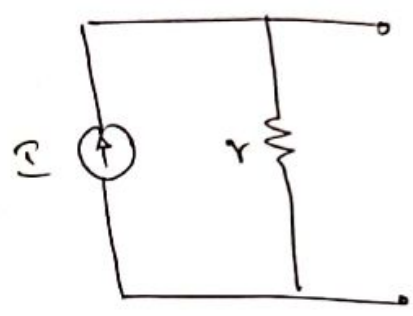


(d) Practical current source

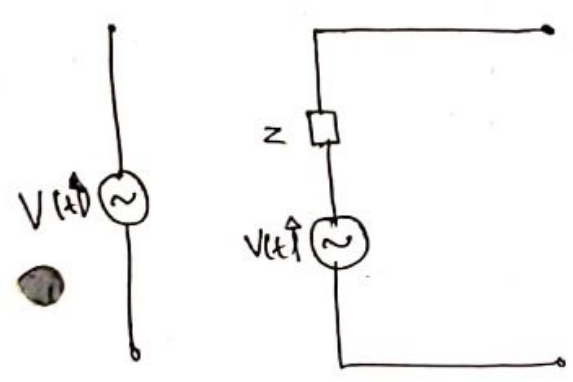

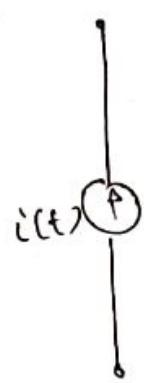
(e) Ideal & Practical a.c. voltage Sources. (Time variant SRCs)



* Dependent Sources.

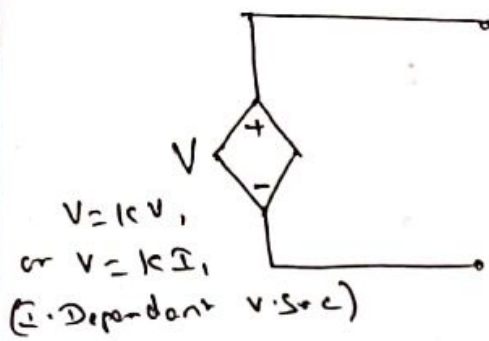

(a) Dependent Voltage Source

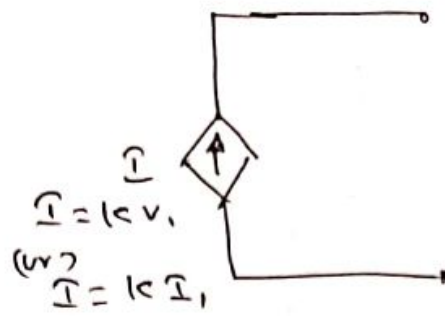

(b) Dependent Current Source

Dependent sources are special kinds of sources in which the source voltage (or) current depends upon a current (or) voltage elsewhere in the ckt.

2) Passive Elements:- "These are the elements of an electric circuit which do not pass energy of their own." They receive energy from the sources.

Eg:- Resistance, inductance & capacitance.

* Resistance is the property of a conductor by virtue of which it opposes (or) limits the flow of current through it, unit is ohm (Ω).

$$R = \frac{\rho l}{a}$$

ρ \rightarrow Resistivity

l \rightarrow length of conductor.

a \rightarrow Area of cross section.

* A pure inductance does not consume any power & the energy given to it is stored in the form of electromagnetic field & is given by

$$E = \frac{1}{2} L I^2 \text{ w sec}$$

I \rightarrow Current flowing through inductor.

3

* A pure capacitance does not consume any power & the energy given to it is stored in the form of electrostatic field & is given by

$$E = \frac{1}{2} CV^2$$

V → voltage applied across a Capacitor.


Ohm's Law:

" On temperature remaining constant, the current flowing through any conductor is directly proportional to the potential difference b/w the 2 ends of the conductor."

I ∝ V

$$I = \frac{V}{R}$$

$$V = IR$$

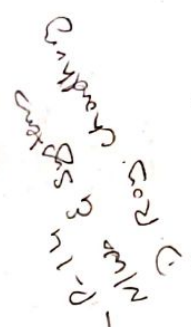

Definitions:-

- 1) Circuit Element: Any individual electric component (eg: R, C, L) with 2 terminals, by which it can be connected to other electric components.
- 2) Branch: A group of electric elements, usually in series & with 2 terminals
- 3) Potential & Independent: A hypothetical generator which maintains its value of potential independent of the o/p current. An a.c. source will be indicated by a circle enclosing a wavy line

4) Current Src (Independent): A generator which maintains its o/p current independent of the voltage across its terminals. It is indicated by a \odot enclosing an arrow for reference current direction.

5) Networks & Circuit: An electric n/w is any possible interconnection of electric ckt elements (or branches).

An electric ckt is a closed energized n/w. A n/w is not necessarily a ckt. Eg: T-n/w.

6) Lumped N/w: A n/w in which physically separate resistors, capacitors & inductors can be represented.

7) Distributed N/w: one in which resistors, capacitors & inductors cannot be electrically separated & individually isolated as separate elements.

Eg: Transmission line.

8) Passive n/w: A n/w containing ckt elements without any energy sources.

9) Active n/w: A n/w containing energy sources together with other ckt elements.

10) Linear element: A ckt element is linear if the relation b/w current and voltage involves a constant Co-efficient.

Eg: $V = Ri$, $V = L \frac{di}{dt}$, $V = \frac{1}{C} \int i dt$.

A linear n/w is one in which principle of Superposition holds. A non-linear n/w is one which is not linear.

4


11) Mesh & Loop: A set of branches forming a closed path, with the omission of any branch making the path open. Mesh must not have any other ckt inside it. Loop may have other loops (or) meshes inside it.

12) Node (or) junction: A terminal of any branch of a n/w common to 2 (or) more branches is known as a node. Voltage of any node w.r.t. gnd is the node voltage. Voltage b/w any pair of nodes is the node-pair voltage.


13) Vector & Phasor: Vector is generalized multidimensional quantity having both magnitude & direction. Phasor is a 2 dimensional vector used in electrical technology which relates to voltage & current.

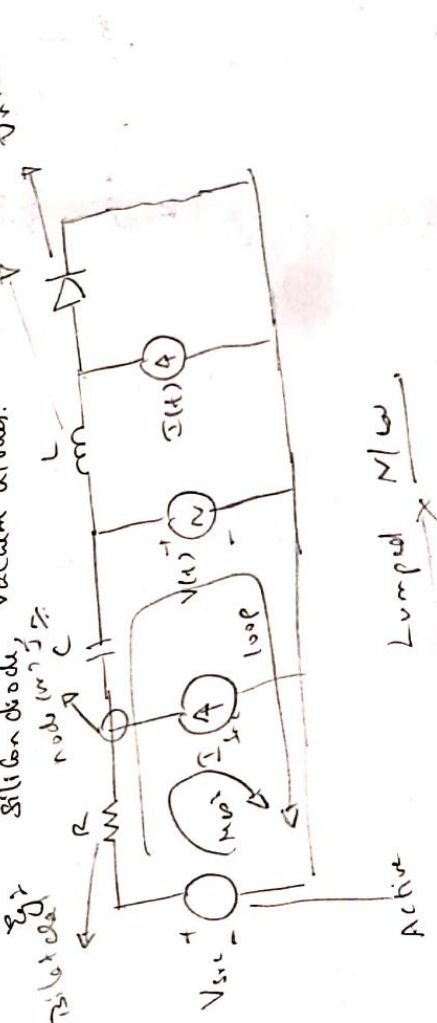14) Bilateral & unilateral element
 For A bilateral element, the same relation exists b/w voltage & current flowing in either direction.
 Eg:- voltage Src, current source

For an unilateral is one, in which the same relation does not (hold) exist b/w the voltage & current either direction.



Resistances in Series:-

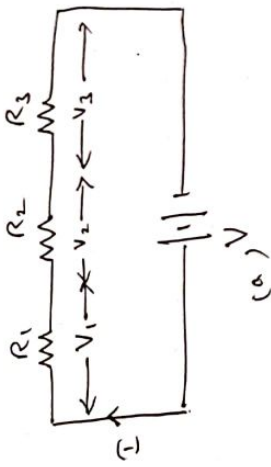

Let $R_1, R_2 \& R_3$ be 3 resistors connected in series. Let $V_1, V_2 \& V_3$ be their corresponding voltage drops respectively.

Let V be the total voltage applied & I be the current flowing through the circuit.

$$V = V_1 + V_2 + V_3$$


$$IR = IR_1 + IR_2 + IR_3$$

$$R = R_1 + R_2 + R_3 \quad \text{total resistance}$$

|||) With n resistor in series, the total resistance

$$is \quad R = R_1 + R_2 + \dots + R_n.$$

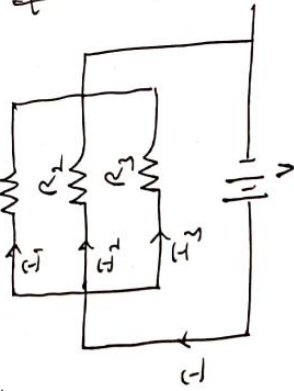Resistances in Parallel:- Let $I_1, I_2 \& I_3$ be the currents flowing through $R_1, R_2 \& R_3$ respectively



$$I = I_1 + I_2 + I_3$$

$$\therefore \frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$


$$\therefore \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Note: $R = \frac{R_1 R_2}{R_1 + R_2}$

5

Kirchhoff's Laws:

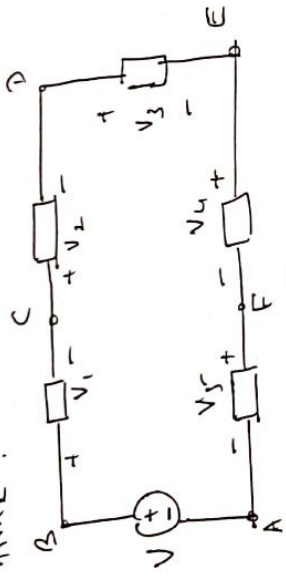(i) Kirchhoff's Voltage Law:
 "The algebraic sum of all branch voltages around any closed loop of a circuit is zero at all instants of time."




(a) Consider a electrical circuit with six nodes A, B, C, D, E & F as shown in figure

Applying KVL to the above circuit,

$$V - V_1 - V_2 - V_3 - V_4 - V_5 = 0$$

i.e. $\sum V = 0$

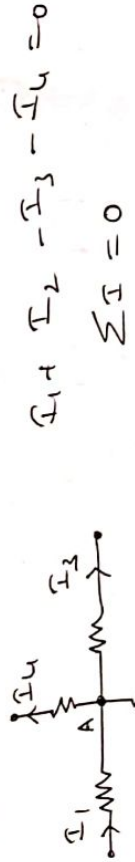
(ii) Kirchhoff's Current Law:
 "The algebraic sum of branch currents at a node is zero at all instants of time."



Note: Currents entering the node are taken as +ve & leaving the node as -ve.

$$I_1 + I_2 - I_3 - I_4 = 0$$

$$\sum I = 0$$

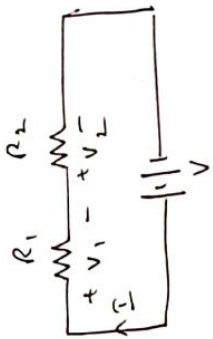

$$V = V_1 + V_2$$


$$V = V_1 + I R_2$$

$$V = V_1 + \frac{V R_2}{R}$$

$$V = V_1 + \frac{V R_2}{R_1 + R_2}$$

$$\therefore \boxed{V_1 = \frac{V R_1}{R_1 + R_2}}$$
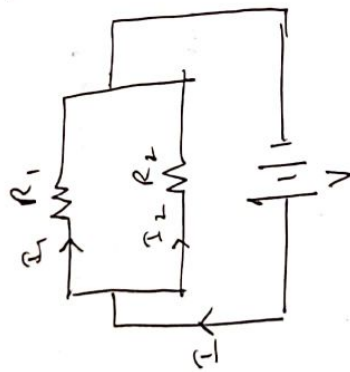
$$\boxed{V_2 = \frac{V R_2}{R_1 + R_2}}$$



$$I = I_1 + I_2$$

$$I = I_1 + \frac{V}{R_2}$$

$$I = I_1 + \frac{I R}{R_2}$$

$$I = I \left[1 - \frac{R}{R_2} \right]$$

$$I_1 = I \left[1 - \left[\frac{R_1 R_2}{R_1 + R_2} \right] / R_2 \right]$$


$$I_1 = I \left[\frac{R_1 + R_2 - R_1}{R_1 + R_2} \right]$$

$$\boxed{I_1 = \frac{I R_2}{R_1 + R_2}}$$

$$\boxed{I_2 = \frac{I R_1}{R_1 + R_2}}$$

6


Problem 1

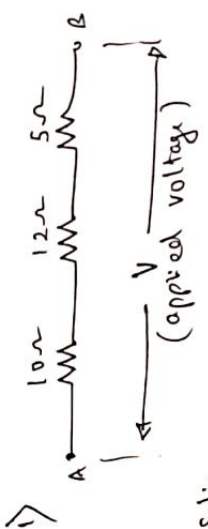


Sol: $R_s = R_1 + R_2 + R_3 = 10 + 12 + 5$

$R_s = 27\Omega$

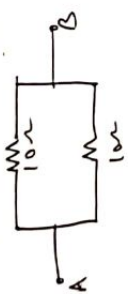2) Sol: $R_p = \frac{R_1 R_2}{R_1 + R_2} = \frac{10 \times 10}{10 + 10} = 5\Omega$



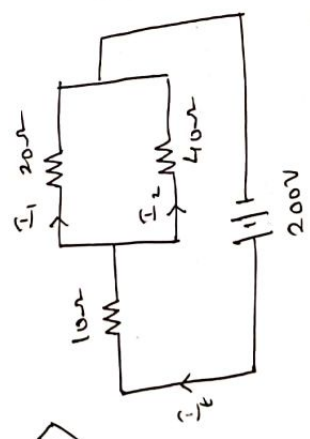3) Find the current in each resistance & voltage across 10Ω . Find also the Power consumed in all the resistances.



∴ net resistance is, $R_t = 10\Omega + \frac{20 \times 40}{20 + 40} = 23.33\Omega$

$\therefore I_t = \frac{V_t}{R_t} = \frac{200}{23.33} = 8.57A$

$I_1 = \frac{I_t \times 40}{20 + 40} = \frac{8.57 \times 40}{60} = 5.71A$

∴ $I_2 = \frac{8.57 \times 20}{20 + 40} = 2.86A$

$$V_{10\Omega} = I \times 10 = 8.57 \times 10 = 85.7 \text{ Volts}$$

$$P = VI = I^2 R$$


$$P_{10\Omega} = (8.57)^2 \times 10 = 734.449 \text{ W}$$

$$P_{20\Omega} = (5.71)^2 \times 20 = 652.082 \text{ W}$$

$$P_{40\Omega} = (2.86)^2 \times 40 = 327.184 \text{ W}$$

4) 3 resistors A, B & C are connected in 11th taking a total current of 12A from the supply. If $I_B = 2I_A$, $I_C = 3.5I_A$ & the total current power drawn is 3kW, Calculate

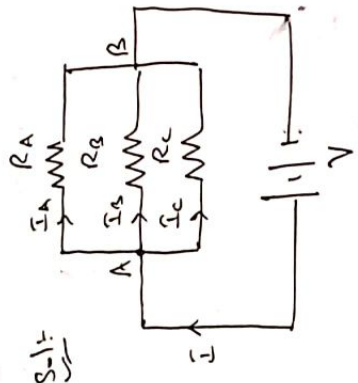- (a) Current drawn by each resistor.
- (b) Supply voltage
- (c) Power consumed by each resistor.



(a) Apply KCL at node A

$$I = I_A + I_B + I_C$$

$$12 = I_A + 2I_A + 3.5I_A$$

$$12 = I_A + 2I_A + 3.5(2I_A)$$

$$\therefore I_A = 1.2 \text{ A}$$

$$I_B = 2I_A = 2(1.2) = 2.4 \text{ A}$$

$$I_C = 3.5 I_B = 8.4 \text{ A}$$

(b) $P = VI$

$$V = \frac{P}{I} = \frac{3\text{K}}{12} = 250 \text{ V}$$

(c) ~~$P_A = 520 \text{ W}$~~

$$P = VI$$


$$P_A = VI_A = 300 \text{ W}$$

$$P_B = VI_B = 600 \text{ W}$$

$$P_C = VI_C = 2100 \text{ W}$$

5) In the ckt given find the voltage drop across 4Ω resistor & the supply voltage.

(7)

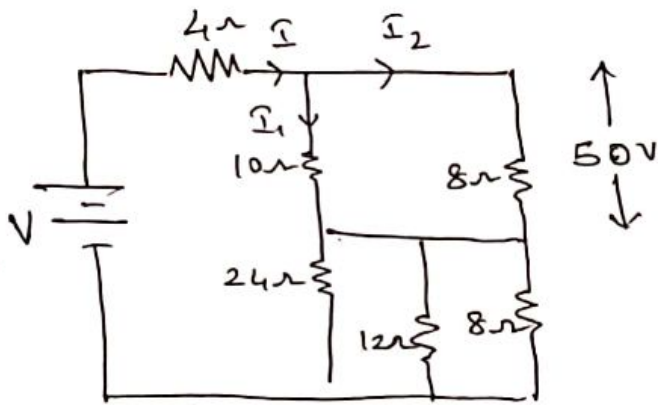

Let I , I_1 & I_2 be the currents flowing in the branches shown in fig.


$$I_1 = \frac{50}{10} = 5A$$

$$I_2 = \frac{50}{8} = 6.25A$$

$$I = I_1 + I_2 = 11.25A$$

$$V_{4\Omega} = 4I = 4 \times 11.25 = 45V //$$

$$R_T = (24 || 12 || 8) + (10 || 8) + 4$$

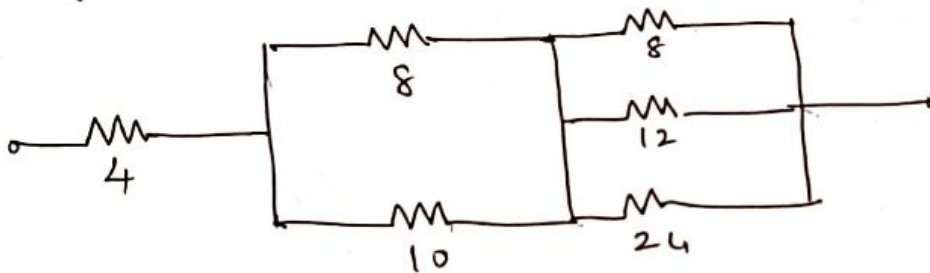

$$24 || 12 = \frac{24 \times 12}{24 + 12} = 8\Omega, \quad 8\Omega || 8\Omega = \frac{8 \times 8}{8 + 8} = 4\Omega$$


$$10 || 8 = \frac{10 \times 8}{10 + 8} = 4.44\Omega$$

$$R_T = 4 + 4.44 + 4 = 12.44\Omega$$

$$\therefore V = R_T I = 12.44 \times 11.25 = 140V //$$

6)

find the value of R.

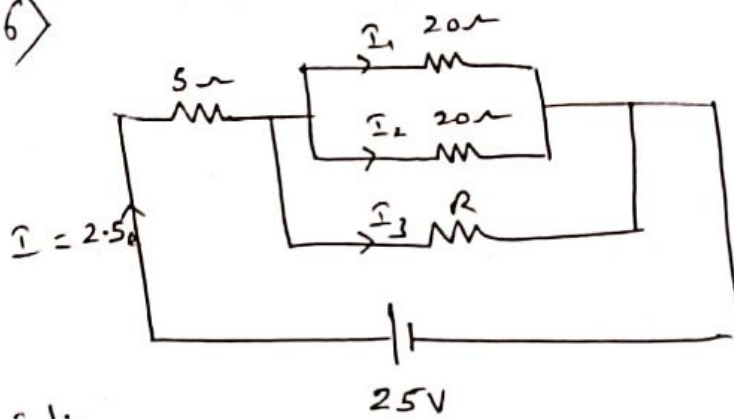

sol:

$$V_{5\Omega} = 2.5 \times 5 = 12.5$$

$$\text{Voltage across the combination} = 25 - 12.5 = 12.5 \text{ V}$$

$$I_1 = \frac{12.5}{20} = 0.625 \text{ A} = I_2$$


$$\text{But } I = I_1 + I_2 + I_3$$

$$2.5 = 0.625 + 0.625 + I_3$$

$$\therefore I_3 = 1.25 \text{ A}$$

$$\therefore R = \frac{12.5}{I_3} = \frac{12.5}{1.25} = 10 \Omega \quad \boxed{R = 10 \Omega}$$

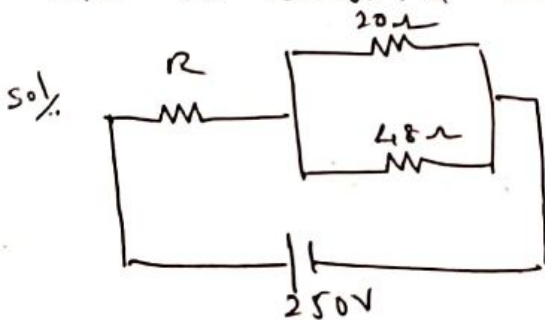7) A resistance R is connected in series with a parallel circuit comprising 20Ω & 48Ω . The total power dissipated in the circuit is 1000 W & the applied voltage is 250 V . Calculate R.



$$P = \frac{V^2}{R_t} = 1000$$

$$\frac{(250)^2}{R_t} = 1000$$


$$R_t = 62.5 \Omega$$

$$R_t = R + \frac{20 \times 48}{20 + 48} = 62.5$$


$$\therefore R = 48.38 \Omega \quad \boxed{R = 48.38 \Omega}$$

Source Transformations:

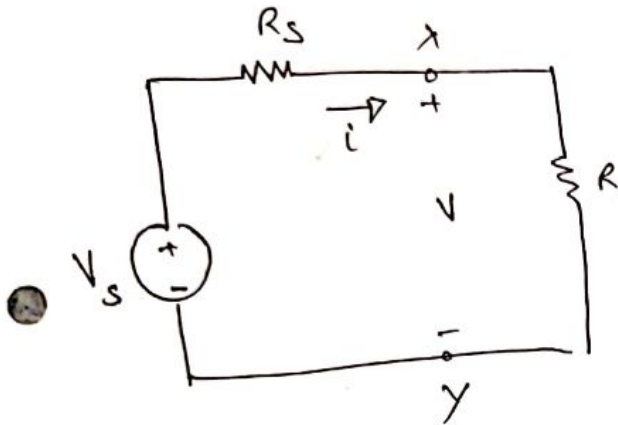- * Src transformation is a procedure which transforms one Src into another while retaining the terminal characteristics of the original Src
- * An Equivalent ckt is one whose terminal characteristics remain identical to those of the original ckt.



(a)

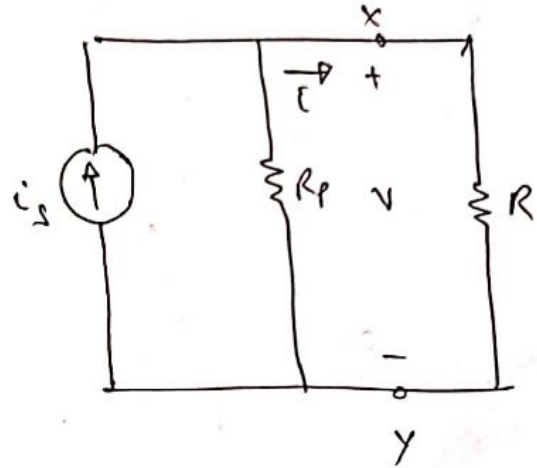

(b)

- * We want to transform the ckt in (a) to (b)
- * for all values of R both the ckt should have same characteristics b/w the terminal x & y.

* If $R=0$, i.e. $x-y$ short ckted.

In fig (a) $i = \frac{V_s}{R_s}$

In fig (b) the s.c current is i_s

$$\therefore i_s = \frac{V_s}{R_s} \quad \text{--- (1)}$$

* If $R = \infty$ i.e. $x-y$ open ckted

In fig (b) $V = i_s R_p$

In fig (a) the o.c. voltage is $V_s \therefore V_s = i_s R_p$ --- (2)

s.t. eq (1) & eq (2)

$$V_s = \left(\frac{V_g}{R_s} \right) R_p$$

$$\therefore R_s = R_p$$

* Applying KVL to fig (a)

$$V_s - iR_s - V = 0$$

$$V_s = iR_s + V$$

$$\frac{V_s}{R_s} = i + \frac{V}{R_s} \quad \text{--- (3)}$$

Applying KCL to fig (b)



$$i_s = i + \frac{V}{R_p} \quad \text{--- (4)}$$

Thus fig (a) & (b) are equivalent if,

$$i_s = \frac{V_s}{R_s} \quad \& \quad R_s = R_p$$


Note: 1) A current src i in ||k with a resistor R can be replaced by a voltage src of $V = iR$ in series with a resistor R .

2) Reverse is also true.

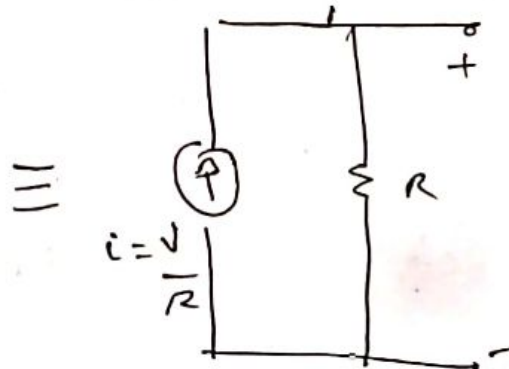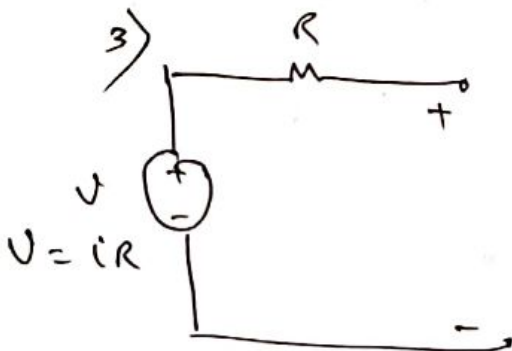


Problem 1

1)

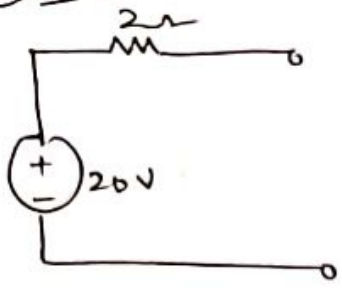


≡

Sol

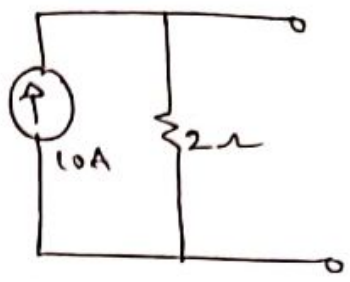


$$i = \frac{V}{R} = \frac{20}{2} = 10A$$

2)

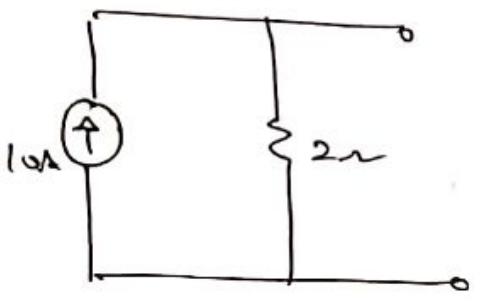


≡

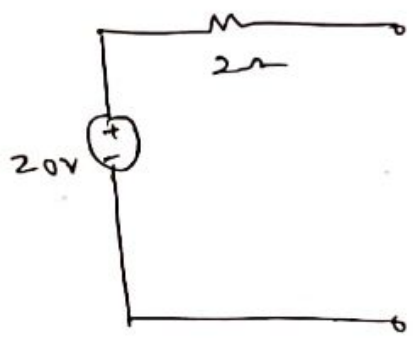


$$V = IR = 10 \times 2 = 20V$$


Note:

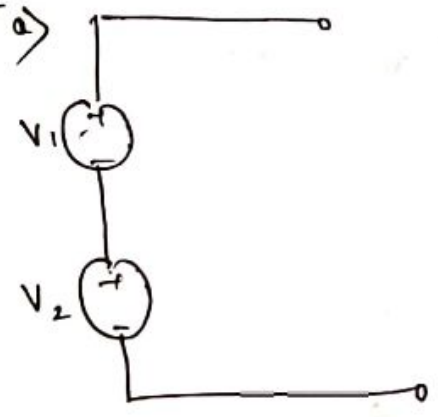


≡

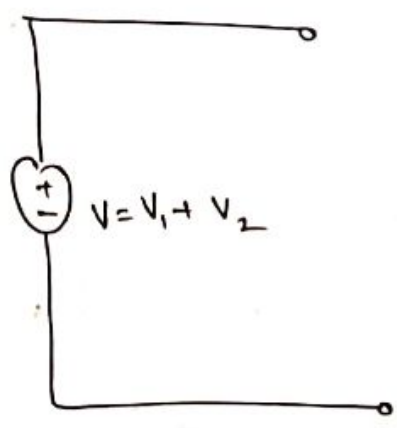


2)

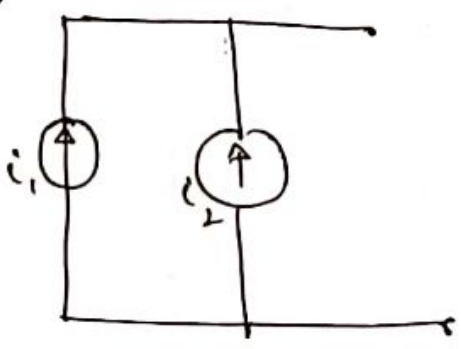


≡

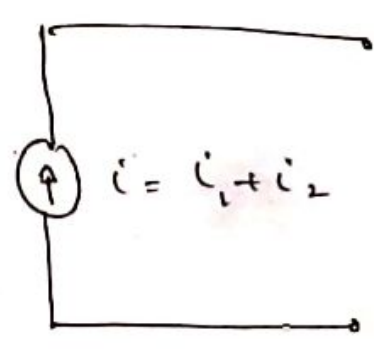


c)

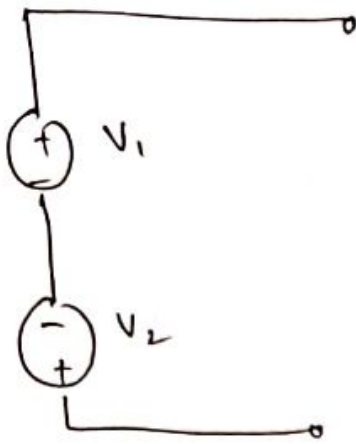


≡

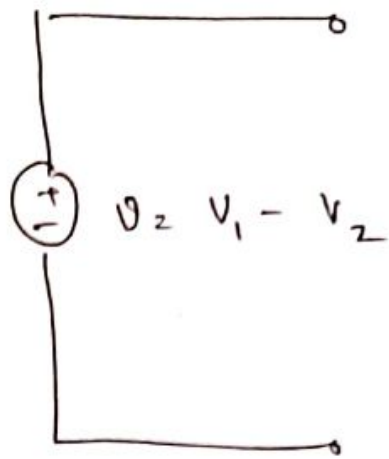


d)

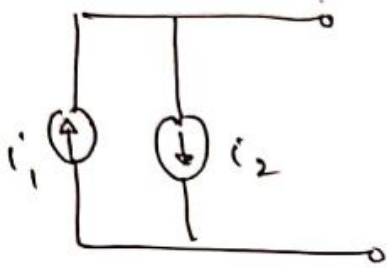


≡

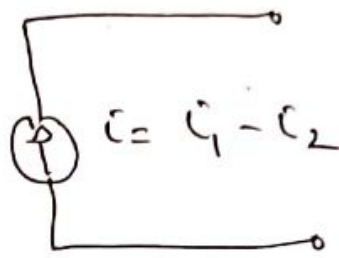


e)

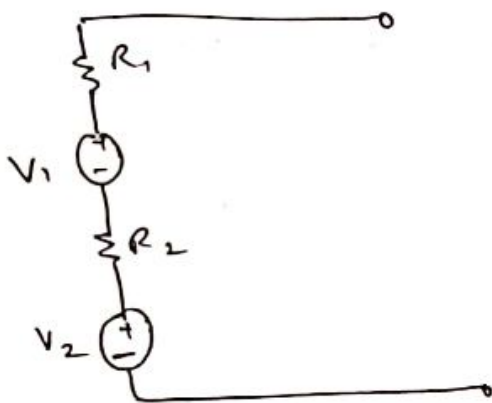


≡

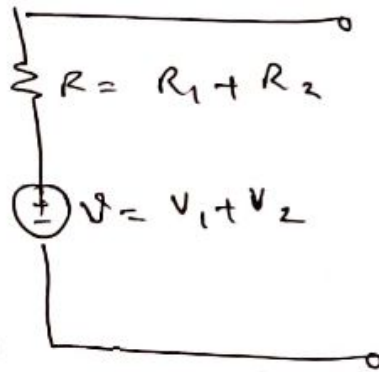


f)

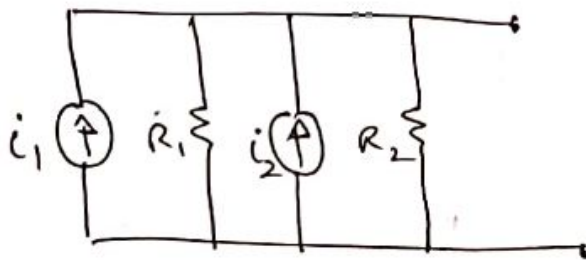


≡

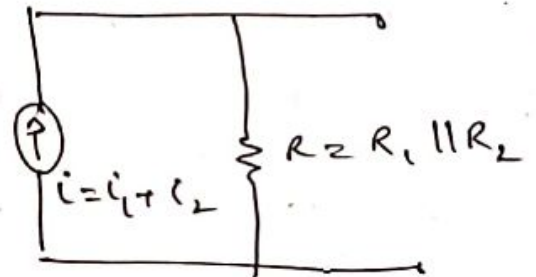


g)

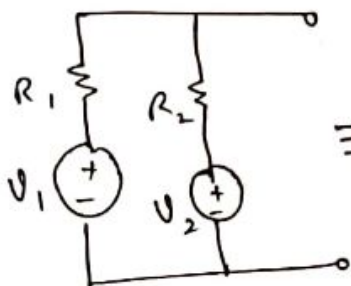


≡

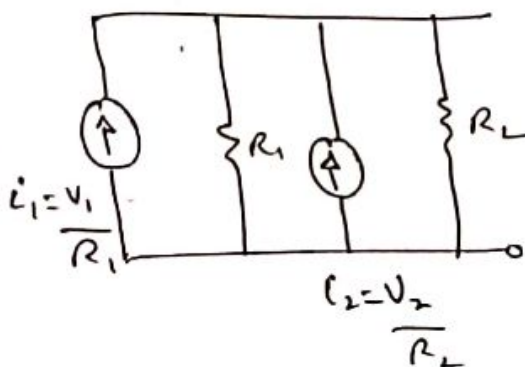

≡




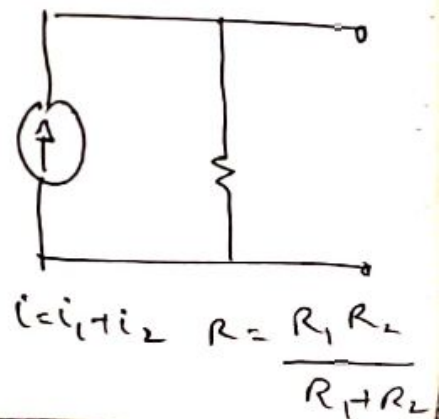












3

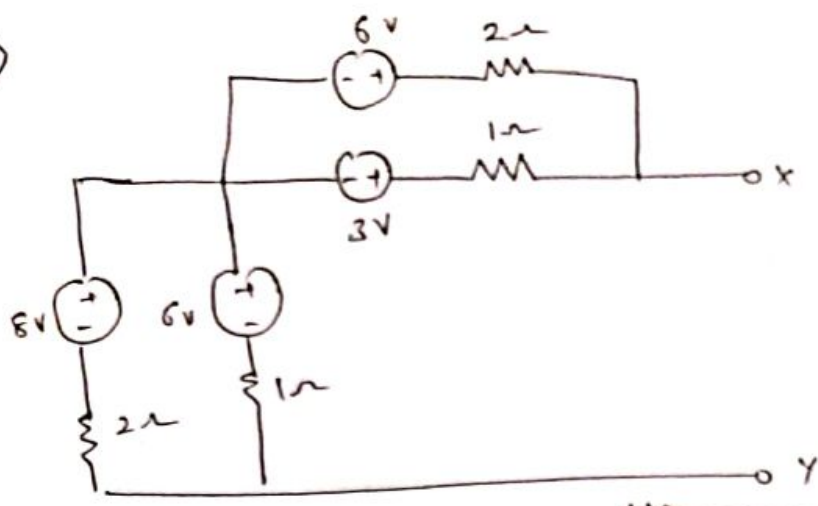

Reduce the circuit to a single voltage source & a resistor.


Sol/

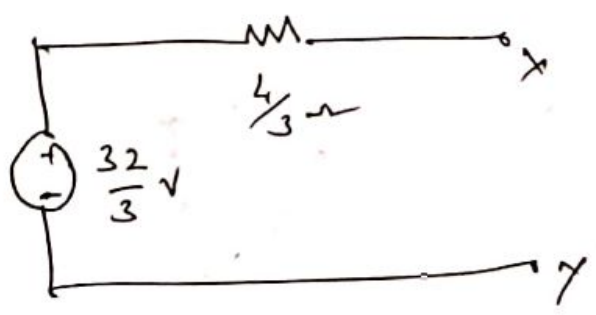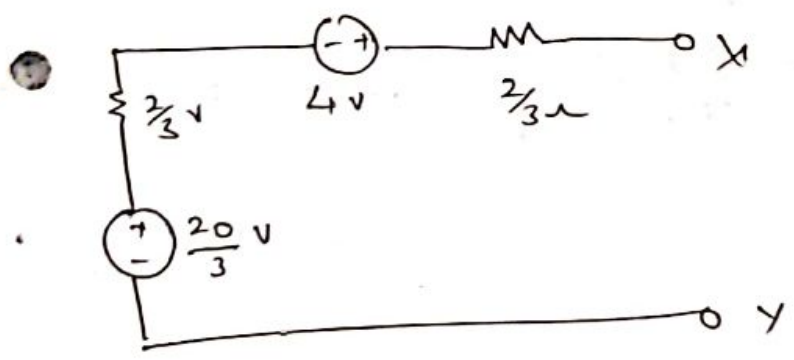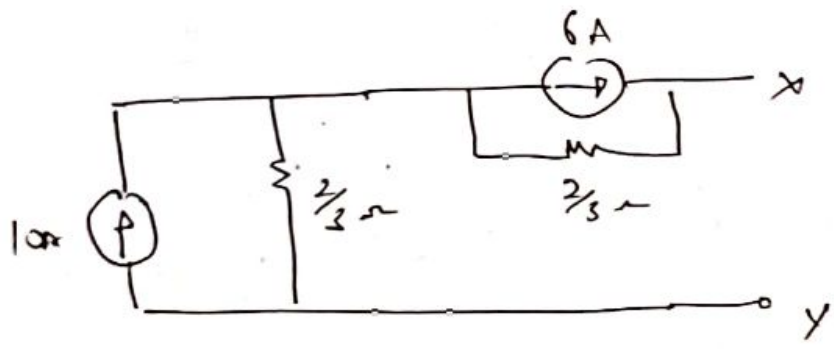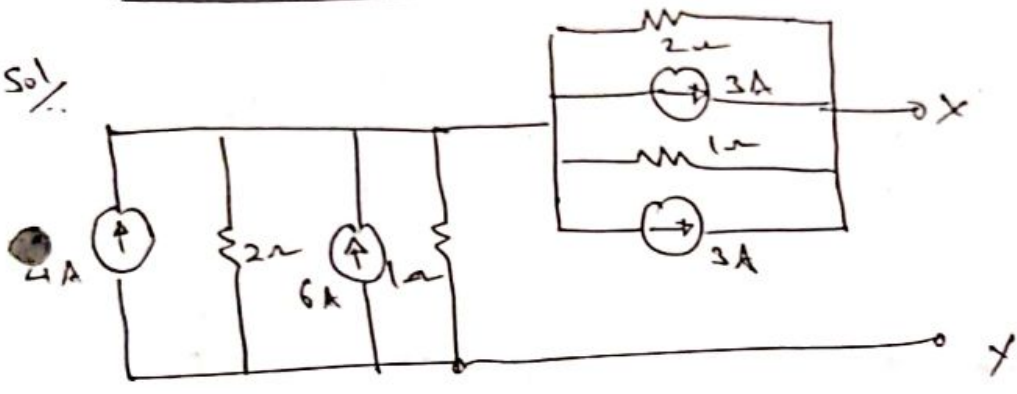

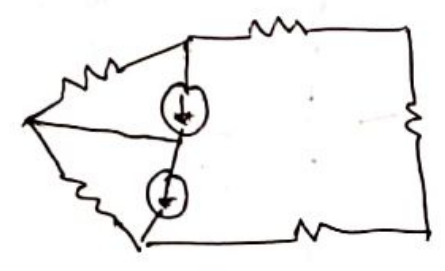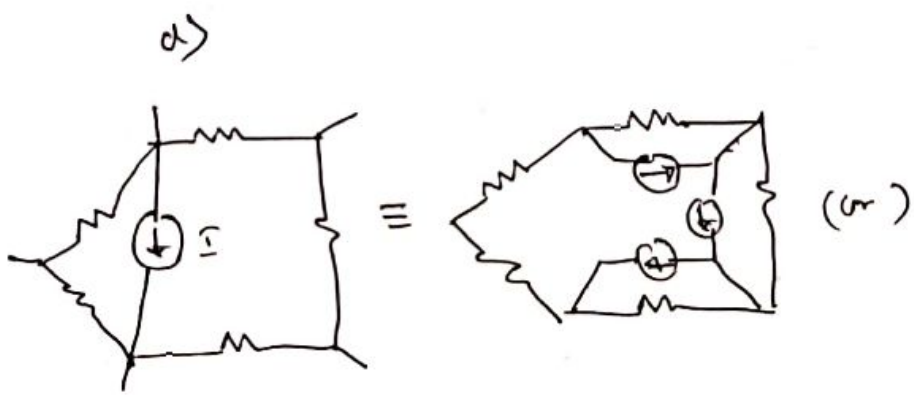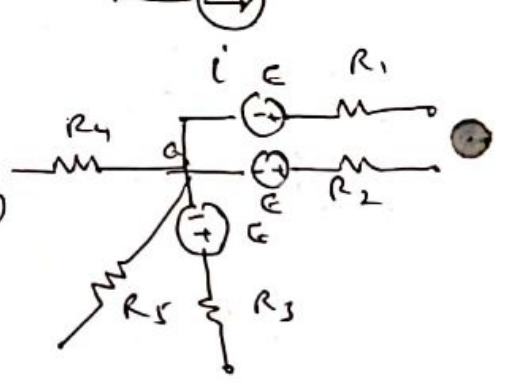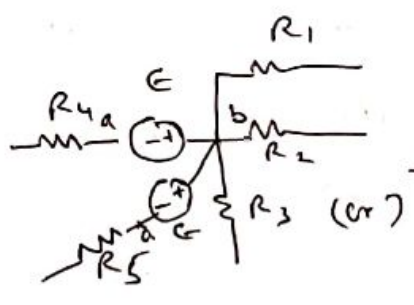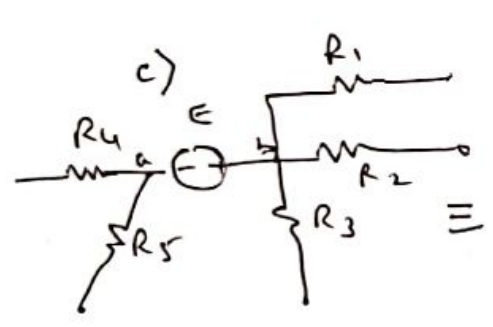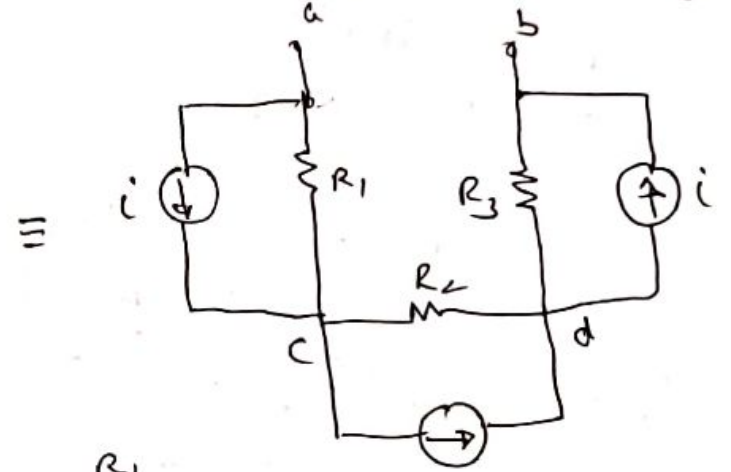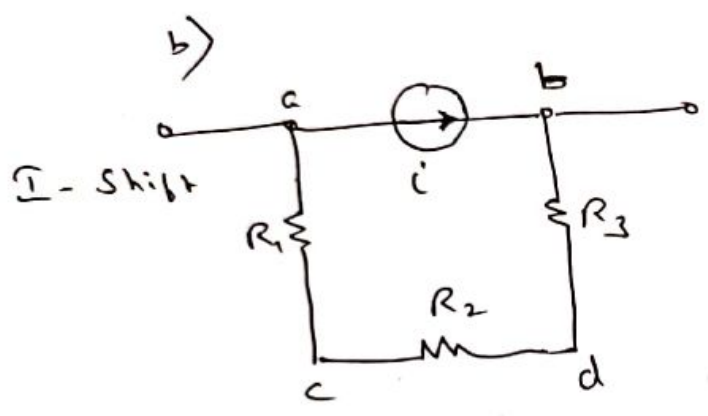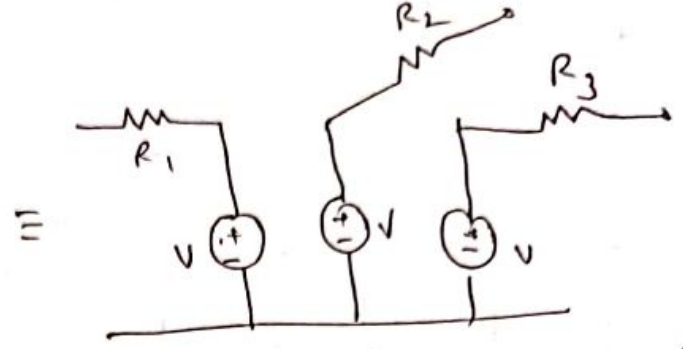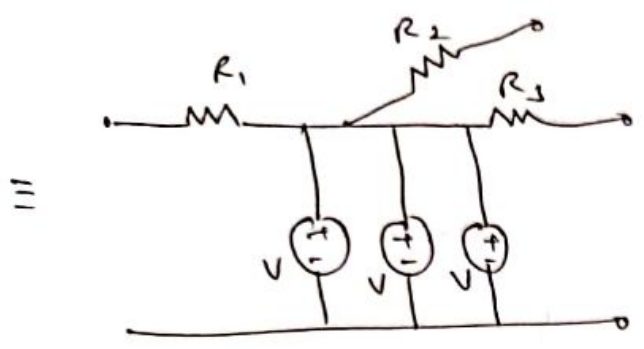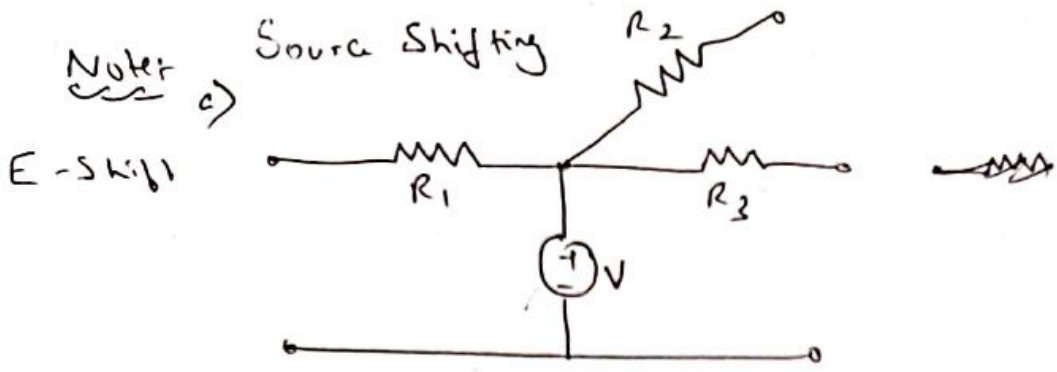


4) Reduce the cktng to a single current s-c & a single resistor in 11k to it.




(11) a

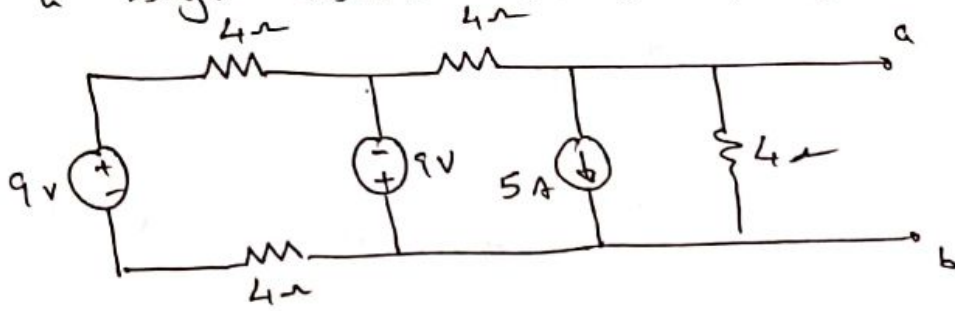


Sol

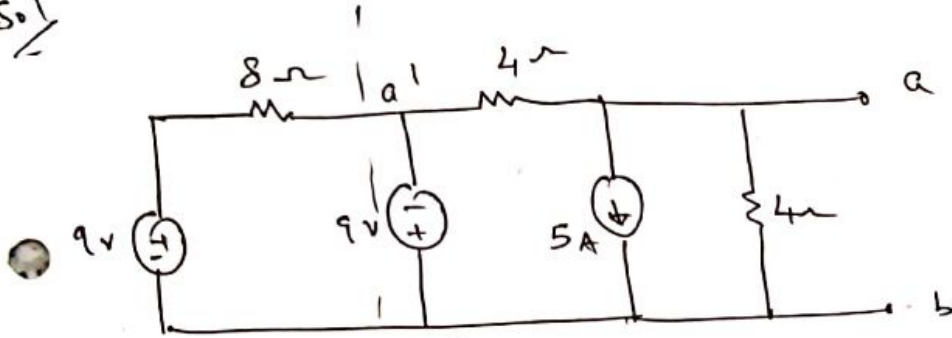

Dummy: it has no effect

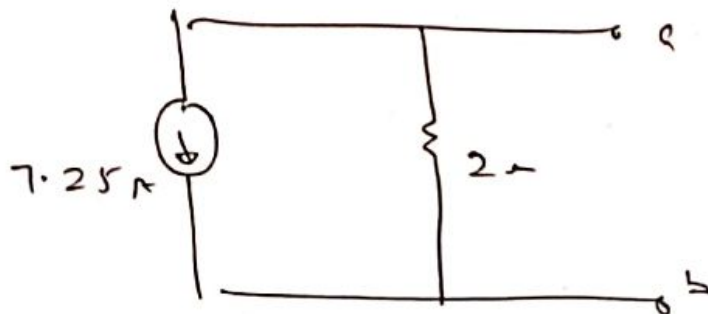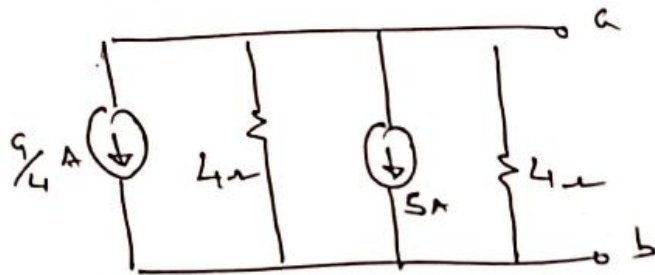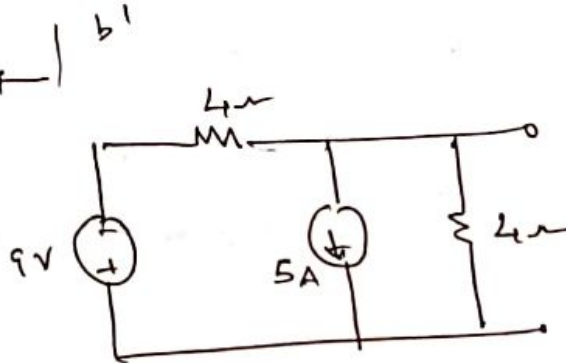


5)

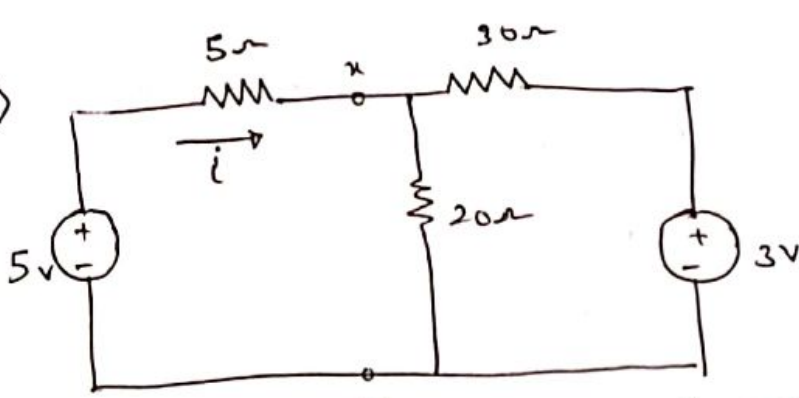

Find the current i , by reducing the ckt to the right to its simplest form.


Sol/

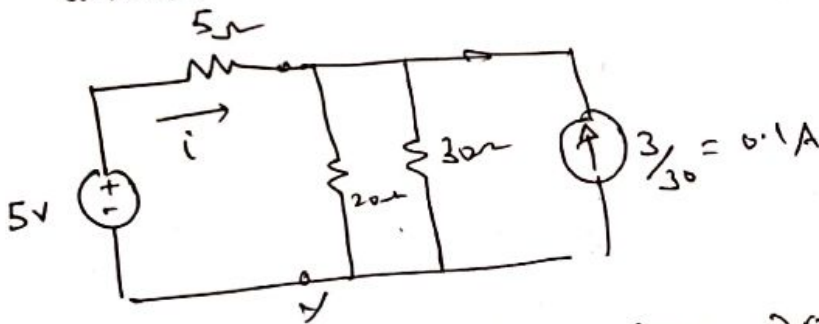Step 1: Transform 30Ω resistor & 3V src into a current src & a 11Ω resistance




Step 2: Reducing 11Ω resistors 20 & 30Ω, we have
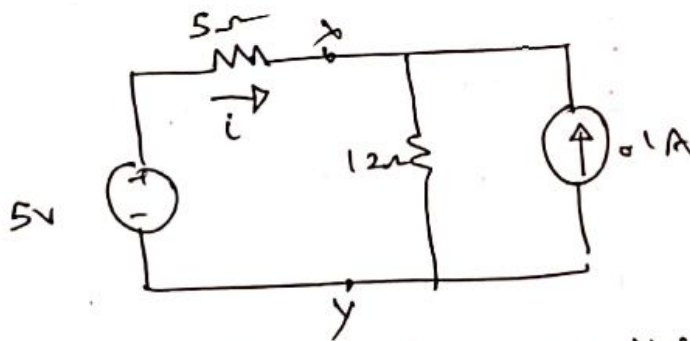
$$\frac{20 \times 30}{20 + 30} = 12\Omega$$



Step 3: Current src \rightarrow V. src

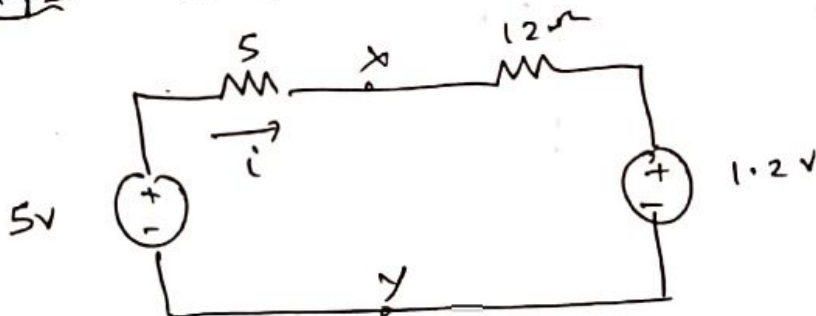


$$\text{KVL, } 5 - 5i - 12i - 1.2 = 0$$

$$\therefore i = 0.2235A$$

Src shifting


(11)

*

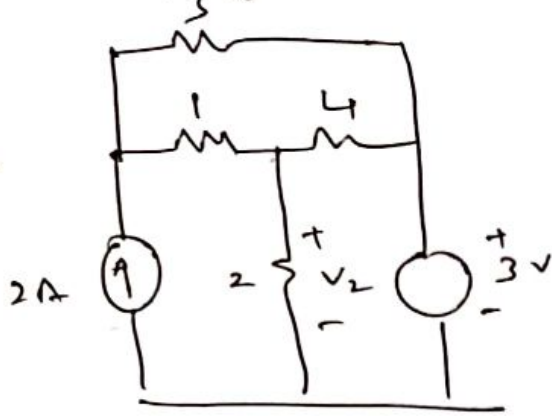

$$V_2 = 3V$$

*

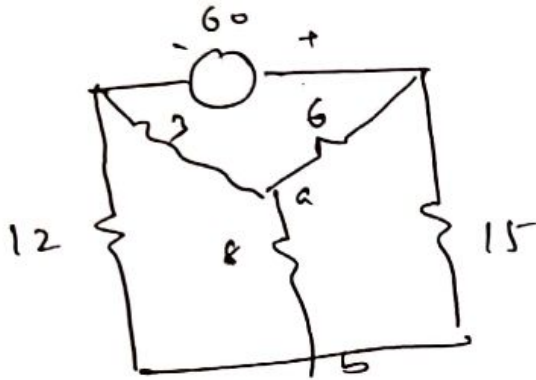

$$V_{ab} = 3.6V$$

Star-Delta Transformation

(2)

Delta to Star Transformation (Δ to Y) :-



(a) Delta Connection

(b) Star (or) Y Connection

Let R_{AB} , R_{BC} & R_{CA} be the 3 resistors connected in delta as shown in fig(a) & R_A , R_B & R_C be the 3 equivalent resistances connected in Star (Y) as shown in fig (b)

"Principle of conversion is that the equivalent resistance b/w the corresponding points in both the connections is same."

$\therefore R_A + R_B = R_{AB} || (R_{CA} + R_{BC})$

$R_A + R_B = \frac{R_{AB} (R_{CA} + R_{BC})}{R_{AB} + R_{CA} + R_{BC}} = \frac{R_{AB} (R_{CA} + R_{BC})}{\Sigma R_{AB}}$ (1)

Similarly $R_B + R_C = \frac{R_{BC} (R_{AB} + R_{CA})}{R_{AB} + R_{BC} + R_{CA}} = \frac{R_{BC} (R_{AB} + R_{CA})}{\Sigma R_{AB}}$ (2)

$R_C + R_A = \frac{R_{CA} (R_{AB} + R_{BC})}{\Sigma R_{AB}}$ (3)

① - ②

$$R_A - R_C = \frac{R_{AB} R_{CA} - R_{BC} R_{CA}}{\Sigma R_{AB}} \quad \text{--- (4)}$$

③ - ④

$$2 R_A = \frac{2 R_{AB} R_{CA}}{\Sigma R_{AB}} \quad \therefore R_A = \frac{R_{AB} R_{CA}}{\Sigma R_{AB}} \quad \text{--- (5)}$$

111b

$$R_B = \frac{R_{BC} R_{AB}}{\Sigma R_{AB}} \quad \text{--- (6)}$$
$$R_C = \frac{R_{BC} R_{CA}}{\Sigma R_{AB}} \quad \text{--- (7)}$$

Star to Δ Transformation:

for eq (5), (6) & (7) we can write

$$R_{AB} + R_{BC} + R_C R_A = \frac{R_{AB} R_{BC} R_{CA} (R_{AB} + R_{BC} + R_{CA})}{(\Sigma R_{AB})^2}$$



$$= R_{BC} \times \frac{R_{AB} R_{CA}}{\Sigma R_{AB}}$$

$$= R_{BC} \cdot R_A$$

111b

$$\therefore R_{BC} = R_B + R_C + \frac{R_{AB} R_C}{R_A}$$
$$R_{AB} = R_A + R_B + \frac{R_A R_B}{R_C}$$
$$R_{CA} = R_C + R_A + \frac{R_C R_A}{R_B}$$

Problems

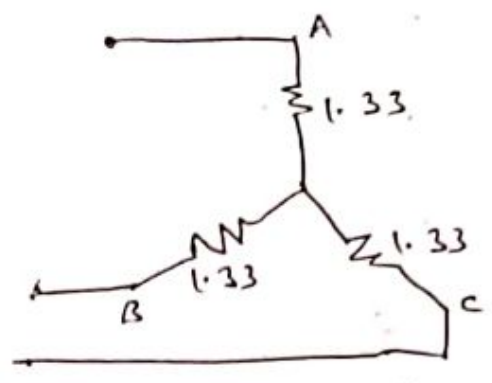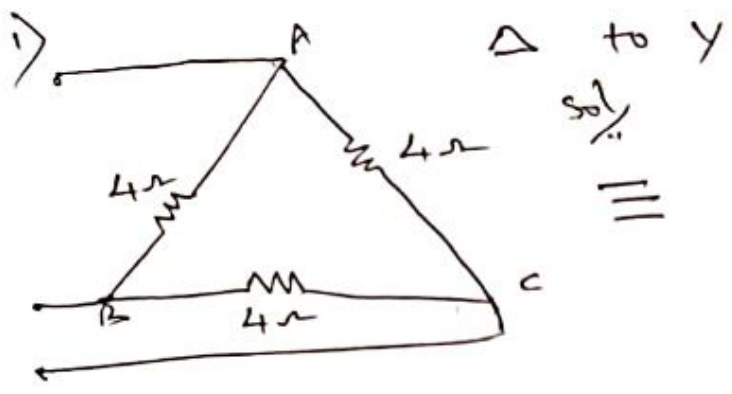


$$R_A = \frac{R_{AB} R_{CA}}{\sum R_{AB}} = \frac{4 \times 4}{4+4+4}$$



||| b

$$R_B = R_C = 1.33 \Omega$$


$$= 1.33 \Omega$$

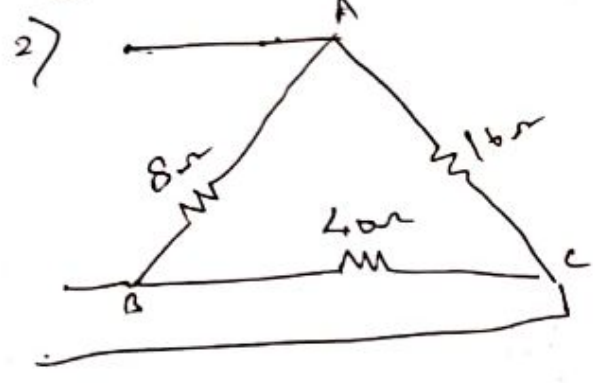

|||

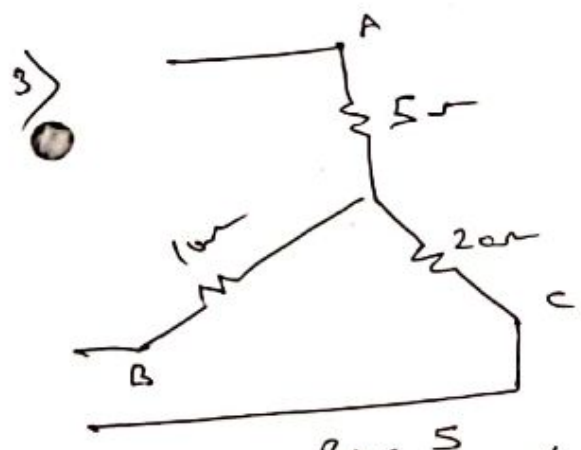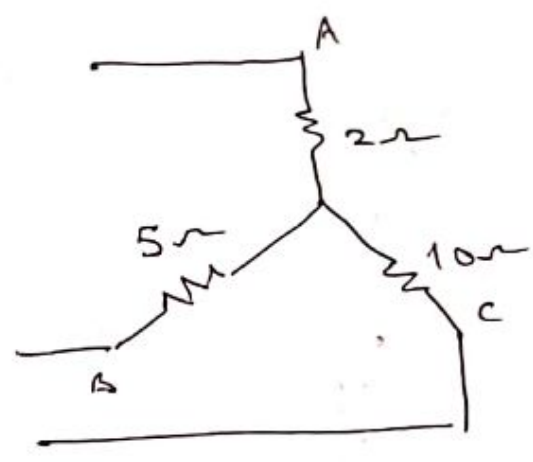


|||


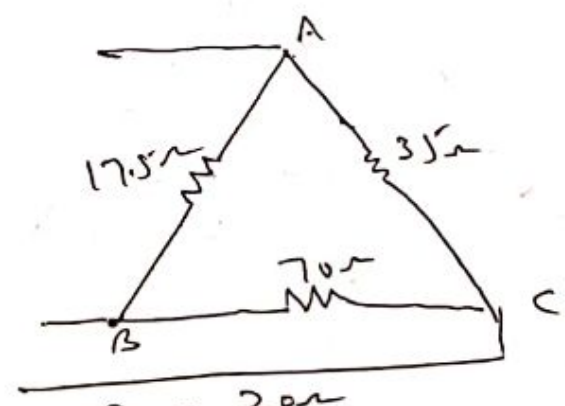


$$R_A = 5, R_B = 10, R_C = 20$$


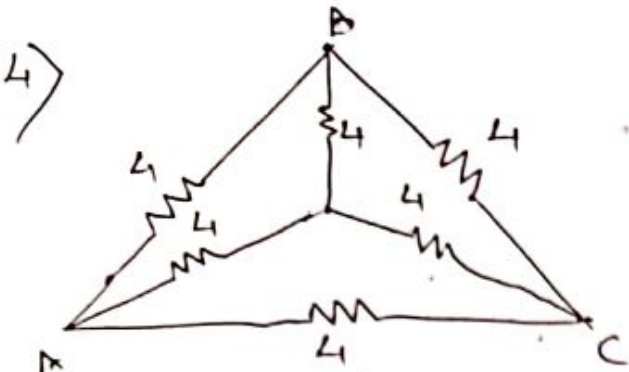
$$R_{AB} = R_A + R_B + \frac{R_A R_B}{R_C}$$



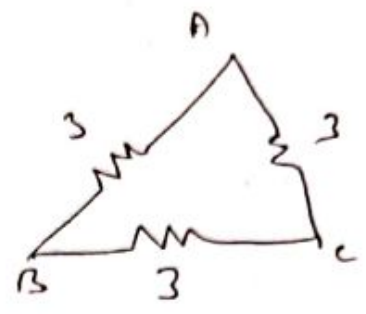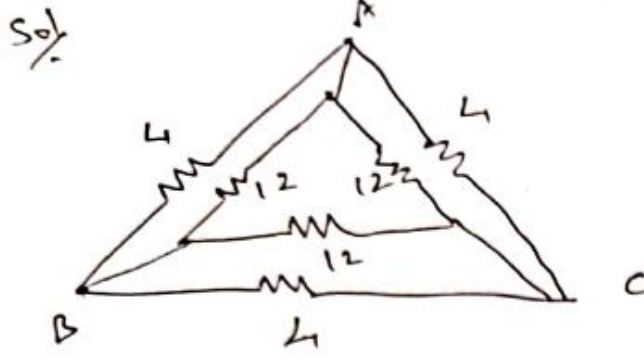Find the equivalent resistance
b/w A & B.



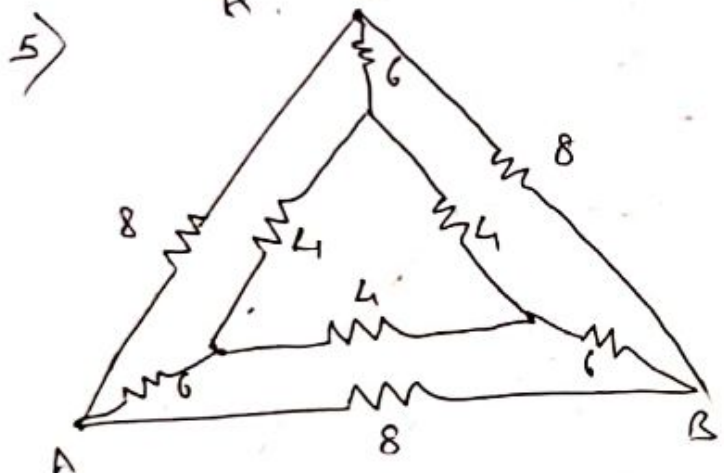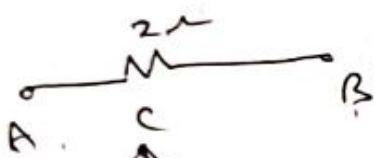
Req. equivalent resistance is $\frac{3 \times 6}{3+6} = 2 \Omega$



find the Resistance
b/w A & B


Sol. Ans: 3.913Ω

Find the resistance b/w A & B

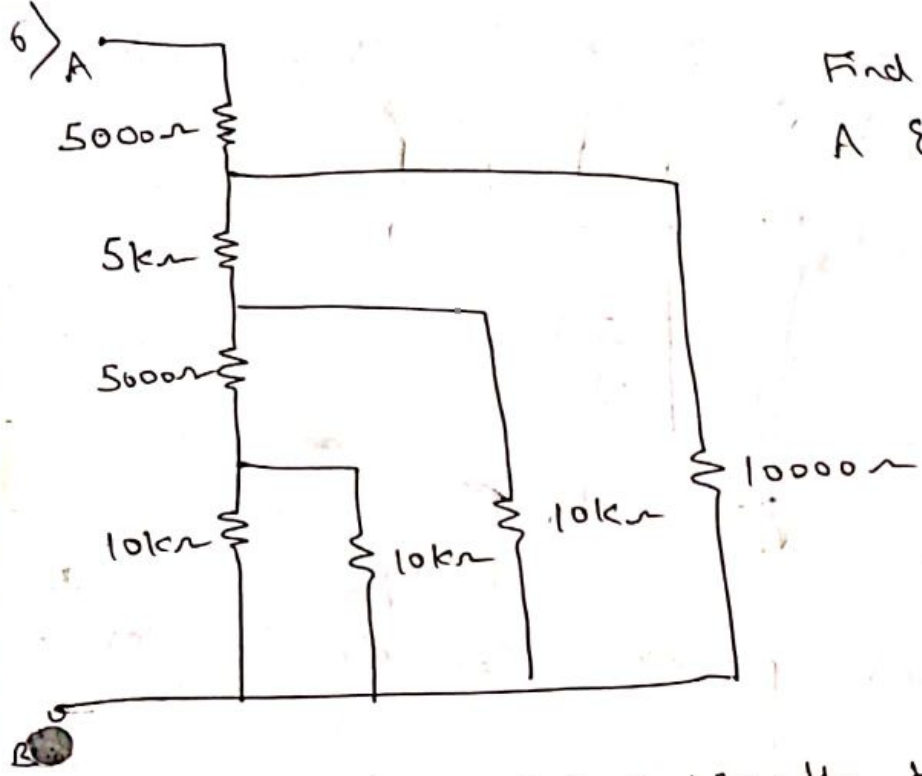


Ans: 10k

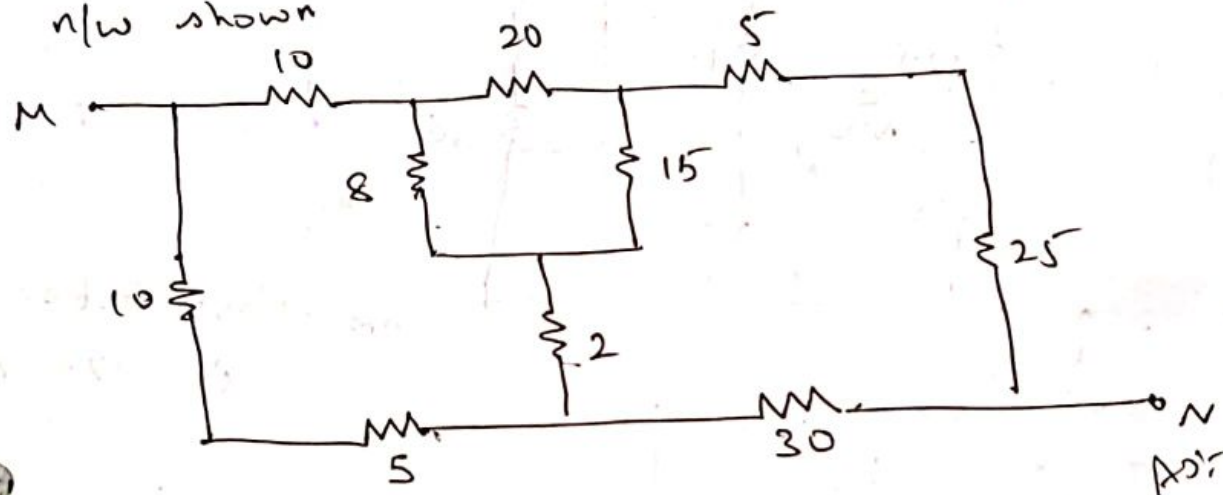7) Determine the resistance b/w the terminals M & N of the n/w shown




Ans: 23.1

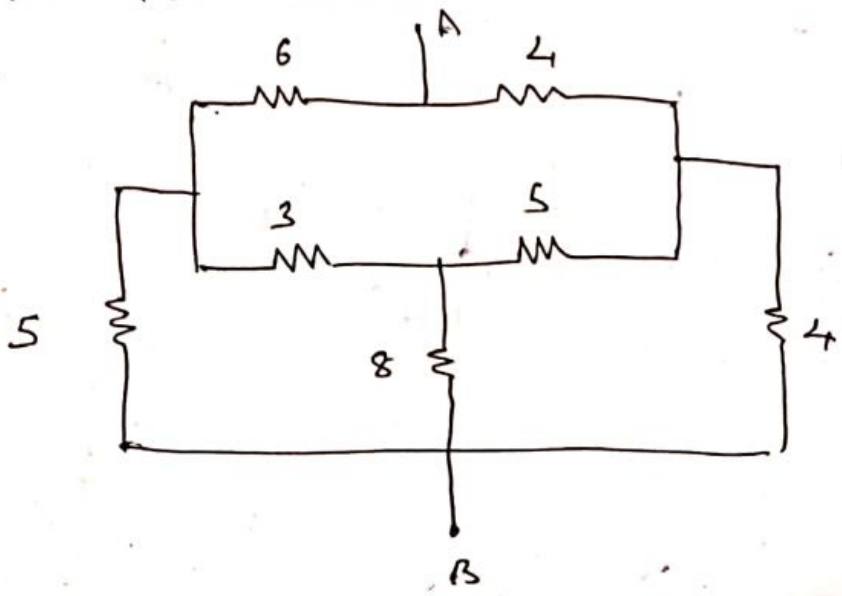8) Determine the resistance b/w the points A & B in the n/w shown




Ans: 4.3

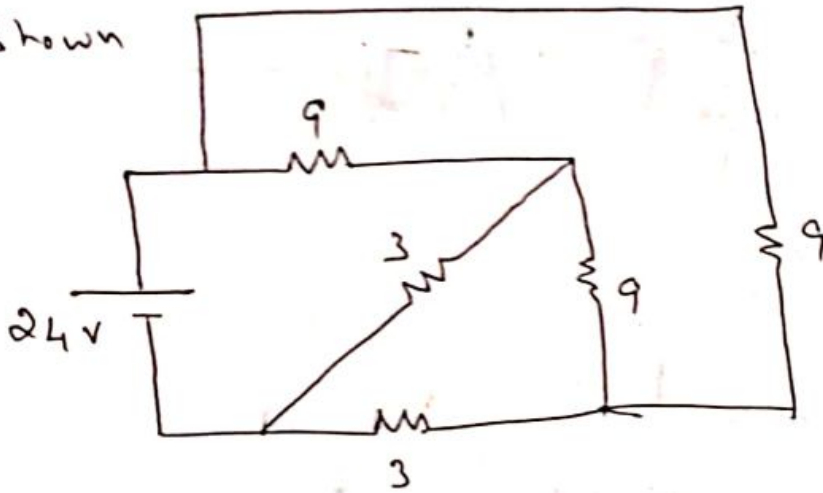9) Find the current supplied by the Src to the n/w shown





$i = 4A$

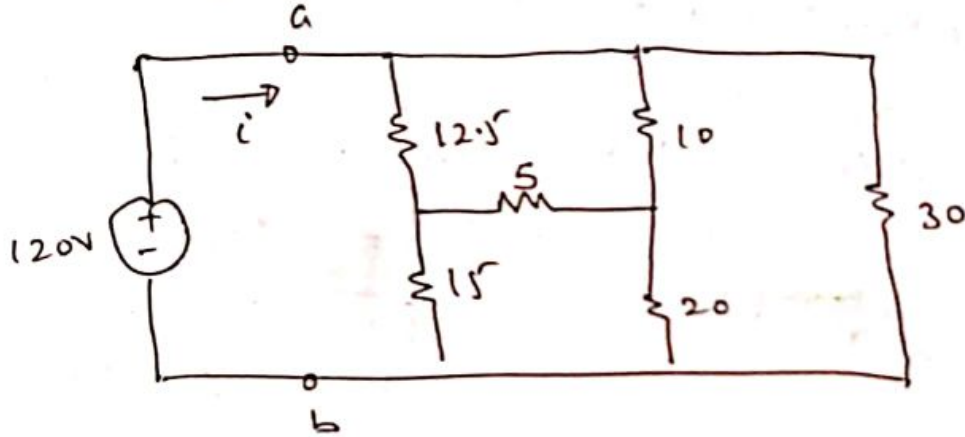10) Obtain the equivalent resistance R_{ab} for the circuit here find i




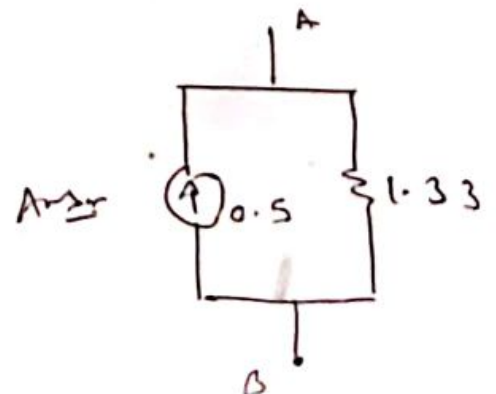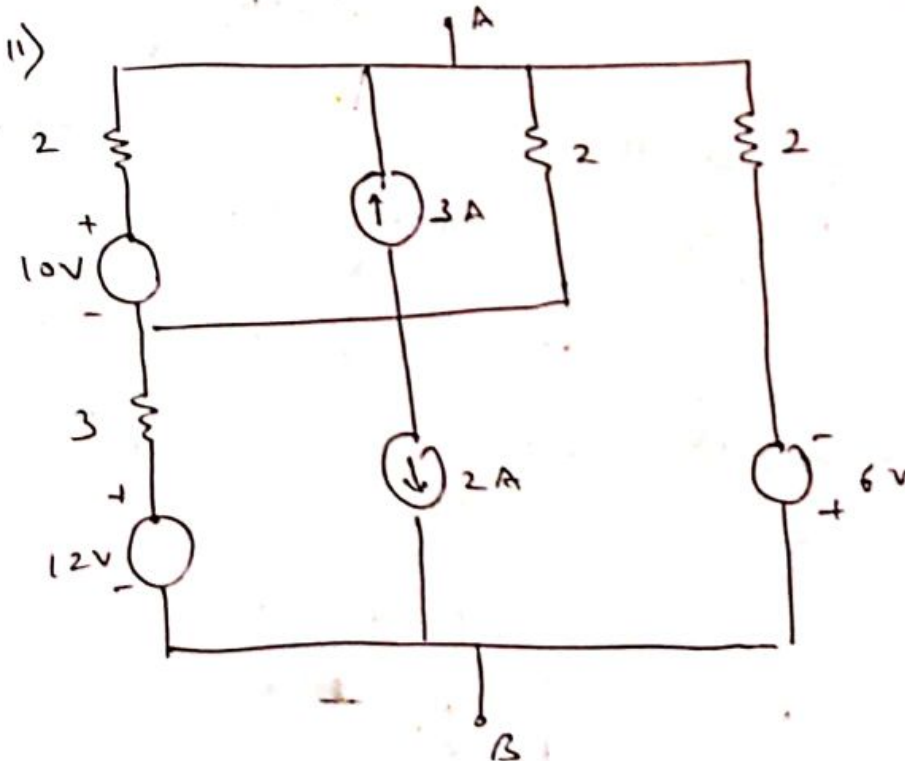Ans: $R_{ab} = 9.632 \Omega$
 $i = 12.458A$



Mesh Analysis with independent Voltage Src:

Consider the ckt,

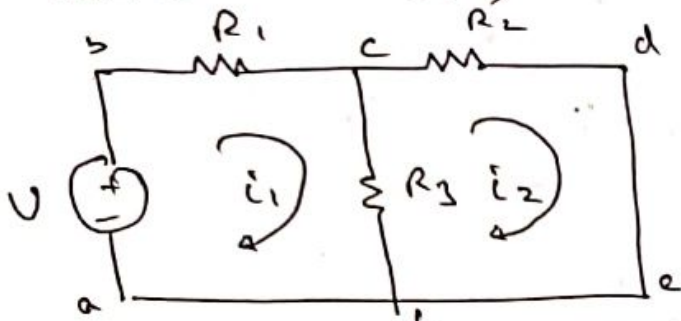


Applying KVL to each mesh,

Mesh 1: $V - i_1 R_1 - R_3 (i_1 - i_2) = 0$ — (1)

Mesh 2: $-i_2 R_2 - (i_2 - i_1) R_3 = 0$ — (2)

Once Mesh currents are known branch currents can be found out.

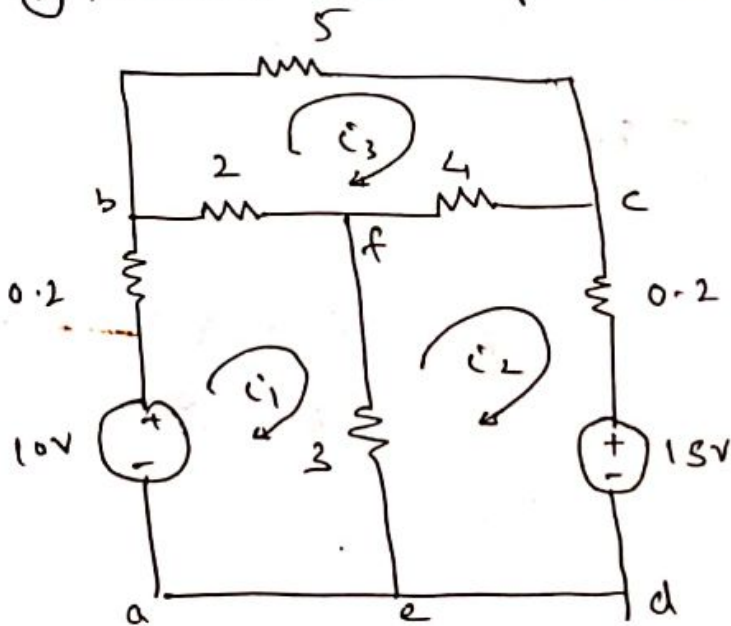Eg: (1) Determine the loop currents & all branch currents



Applying KVL to meshes,

Mesh 1: $10 - 0.2 i_1 - 2(i_1 - i_3) - 3(i_1 - i_2) = 0$

$5.2 i_1 - 3 i_2 - 2 i_3 = 10$ — (1)

Mesh 2: $-3(i_2 - i_1) - 4(i_2 - i_3) - 0.2 i_2 - 15 = 0$

$-3 i_1 + 7.2 i_2 - 4 i_3 = -15$ — (2)

$$\text{Mesh 3: } -5i_3 - 4(i_3 - i_2) - 2(i_3 - i_1) = 0$$

$$-2i_1 - 4i_2 + 11i_3 = 0 \quad \text{--- (3)}$$

$$\begin{bmatrix} 5 & -3 & -2 \\ -3 & 7 & -4 \\ -2 & -4 & 11 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ -18 \\ 0 \end{bmatrix}$$


using Cramer's rule,

$$i_1 = 0.11 \text{ A}$$

$$i_2 = -2.53 \text{ A}$$

$$i_3 = -0.9 \text{ A}$$

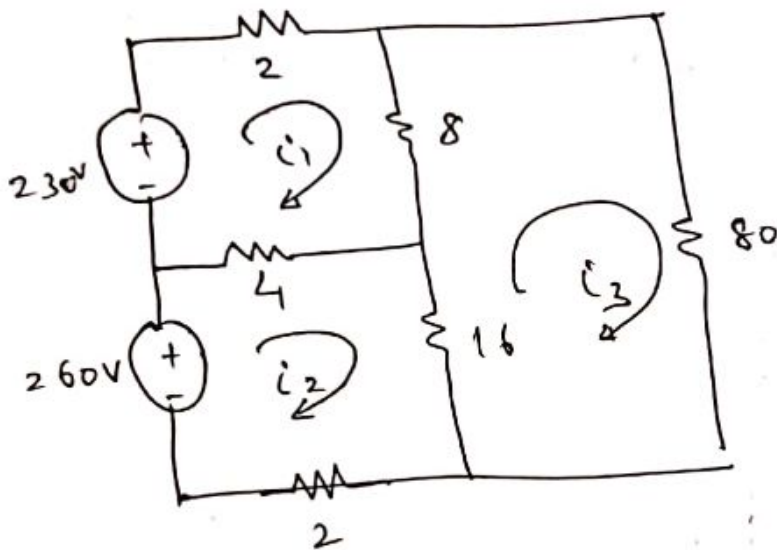
(2) Find the Power dissipated in the 80Ω resistor using Mesh Analysis



Ans: $i_3 = 5 \text{ A}$
 $P_{80} = 2000 \text{ W}$

Mesh Analysis with independent Current Src

16

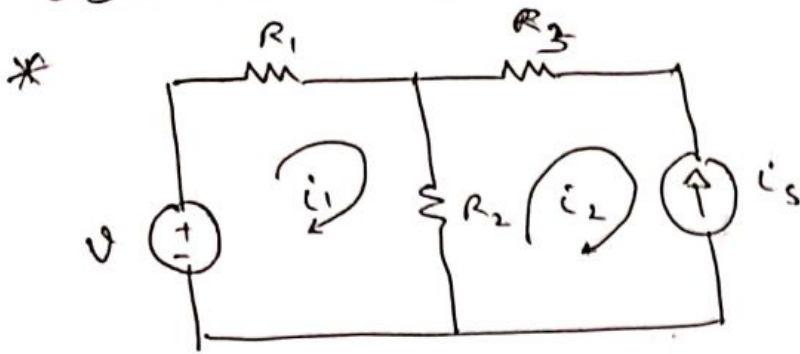

Applying KVL to Mesh 1,


$$V - i_1 R_1 - R_2 (i_1 - i_2) = 0$$

$$i_1 (R_1 + R_2) + i_2 R_2 = V \quad \text{--- (1)}$$

from Mesh 2, we have $i_2 = -i_s \quad \text{--- (2)}$

$$\therefore i_1 (R_1 + R_2) - i_s R_2 = V$$

$$i_1 = \frac{V - i_s R_2}{R_1 + R_2}$$

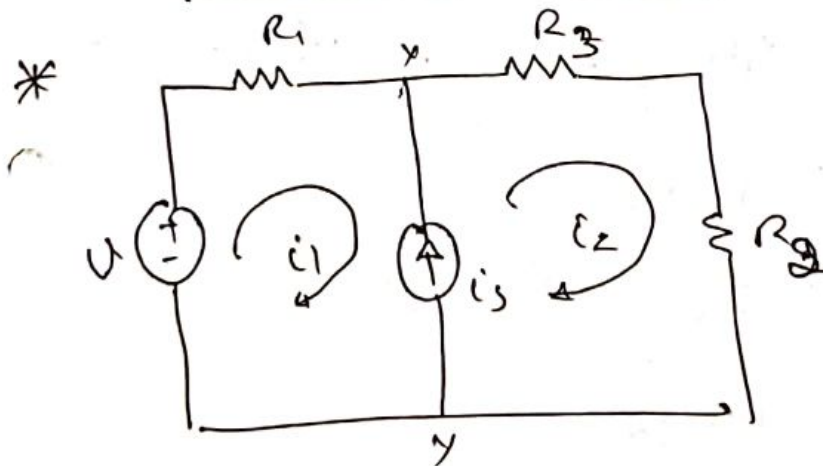

$$i_2 - i_1 = i_s \quad \text{--- (1)}$$

$$\text{M 1: } V - i_1 R_1 - V_{xy} = 0 \quad \text{--- (2)}$$


$$\text{M 2: } -i_2 (R_2 + R_3) + V_{xy} = 0 \quad \text{--- (3)}$$

$$(2) + (3) \quad i_1 R_1 + (R_2 + R_3) i_2 = V$$

Also from eq (1) $i_2 = i_1 + i_s$

$$\therefore i_1 = \frac{V - (R_2 + R_3)i_3}{R_1 + R_2 + R_3}$$

eg:

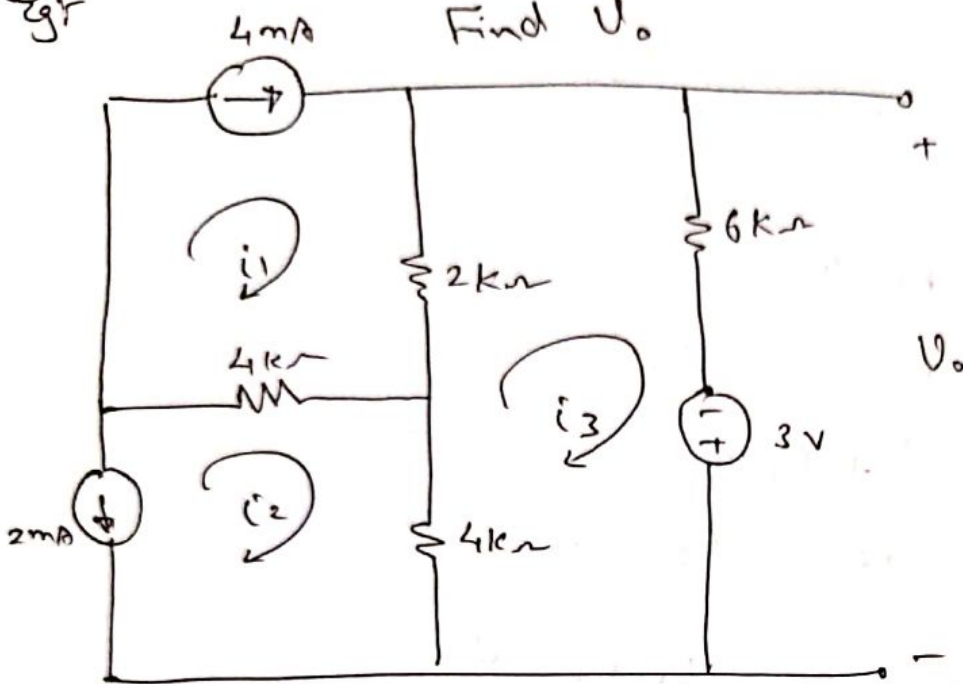

$$i_1 = 4 \text{ mA}$$

$$i_2 = -2 \text{ mA}$$

Mesh 3:-

$$-6k i_3 - 3 - 4k(i_3 - i_2) - 2k(i_3 - i_1) = 0$$

$$\therefore i_3 = 0.25 \text{ mA}$$


$$\{ V_o = 6k i_3 - 3$$

$$V_o = -1.5 \text{ V}$$

Super Mesh:


A more General technique for Mesh analysis method, when a Current Src is Common to two meshes, involves the Concept of Super Mesh.

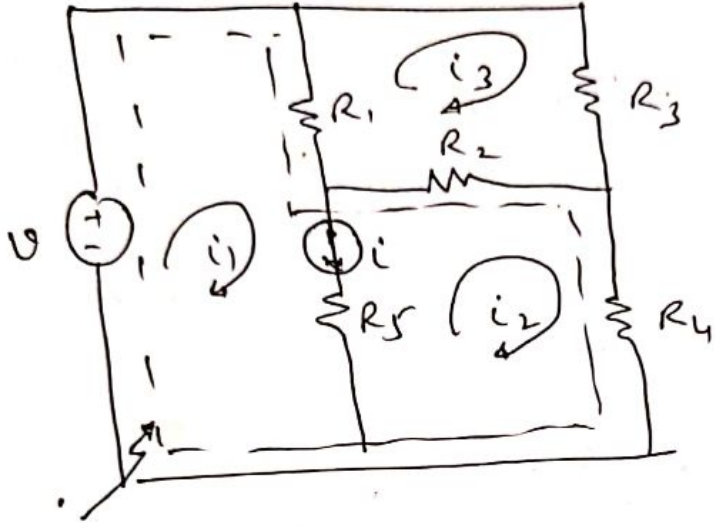A Super Mesh is created from 2 meshes that have a Current Src as a Common element, the Current Src is in the interior of a Super Mesh.




Super Mesh

Ex: Find Current i_0

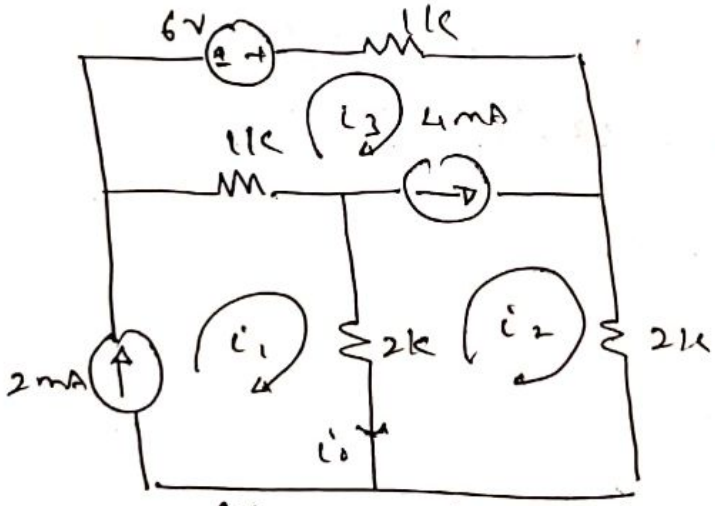

sol:

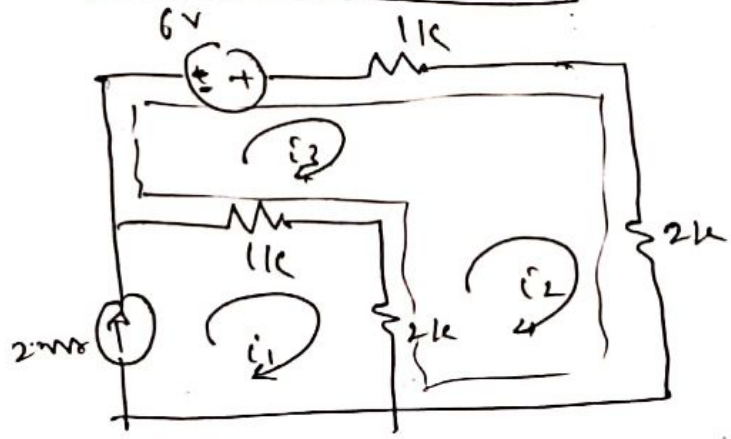

$$M-①, \quad i_1 = 2 \text{ mA}, \text{ Also } i_2 - i_3 = 4 \text{ mA.}$$

$$SM - ② \& ③ \quad + 6 - (11k)i_3 - 2k(i_2) - 2k(i_2 - i_1) - 11k(i_3 - i_1) = 0$$

$$- 6 \leftarrow 11k(i_2 - 4m) - 2ki_2 \leftarrow 2k(i_2 - 2m) \quad \cancel{+ 4}$$

$$+ 6 - 11ki_2 + 4 - \cancel{4} + 4 = 0$$

$$+ 6 - 11k(i_2 - 4m) - 2ki_2 - 2k(i_2 - 2m) - 11k(i_2 - 4m - 2m) = 0$$


$$+ 6 - 11ki_2 + 4 - 2ki_2 - 2ki_2 + 4 - 11ki_2 + 6 = 0$$

$$i_2 = \frac{20}{6} = 3.33 \text{ mA} //$$

$$\text{But } i_0 = i_1 - i_2 = 2 - 3.33$$

$$i_0 = -1.33 \text{ mA} //$$

find i_1, i_2 & i_3 .

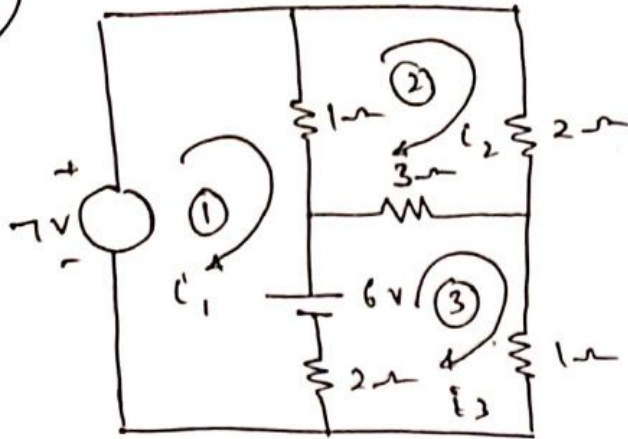

Sol: Applying KVL to Mesh 1:

$$7 - 1(i_1 - i_2) - 6 - 2(i_1 - i_3) = 0$$

$$3i_1 - i_2 - 2i_3 = 1 \quad \text{--- (1)}$$

Mesh 2,

$$-i_1 + 6i_2 - 3i_3 = 0 \quad \text{--- (2)}$$

Mesh 3,

$$-2i_1 - 3i_2 + 6i_3 = 6 \quad \text{--- (3)}$$

$$\Delta = \begin{vmatrix} 3 & -1 & -2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{vmatrix} = 3(36 - 9) + 1(-6 - 6) - 2(3 + 12)$$

$\Delta = 39$

$$\Delta_1 = \begin{vmatrix} 1 & -1 & -2 \\ 0 & 6 & -3 \\ 6 & -3 & 6 \end{vmatrix} = 1(36 - 9) + 1(18) - 2(-36)$$


$\Delta_1 = 117$

$$\Delta_2 = \begin{vmatrix} 3 & 1 & -2 \\ -1 & 0 & -3 \\ -2 & 6 & 6 \end{vmatrix} = 78$$


$$\Delta_3 = \begin{vmatrix} 3 & -1 & 1 \\ -1 & 6 & 0 \\ -2 & -3 & 6 \end{vmatrix} = 117$$

$$\therefore i_1 = \frac{\Delta_1}{\Delta} = \frac{117}{39} = 3A // i_2 = \frac{\Delta_2}{\Delta} = 2A, i_3 = \frac{\Delta_3}{\Delta} = 3A$$

2) Use Mesh Analysis to find i_x ,

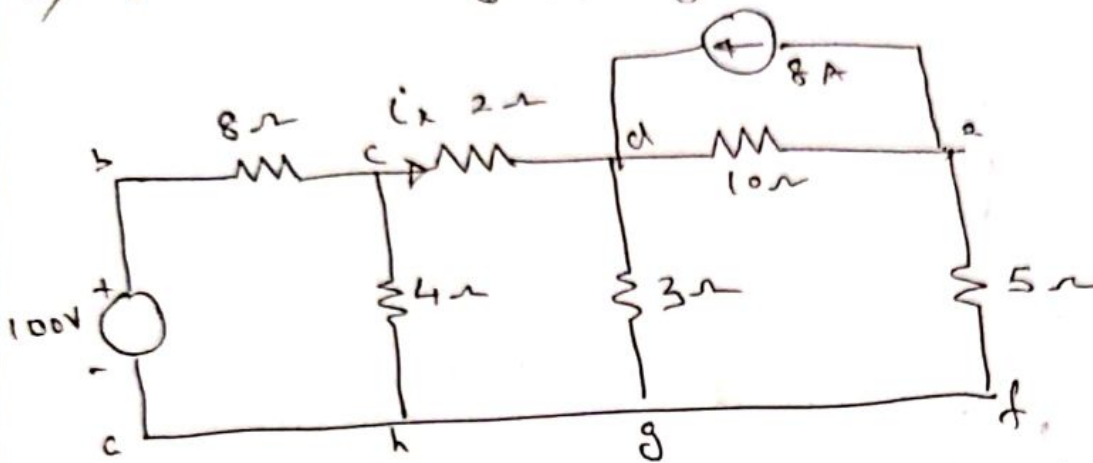

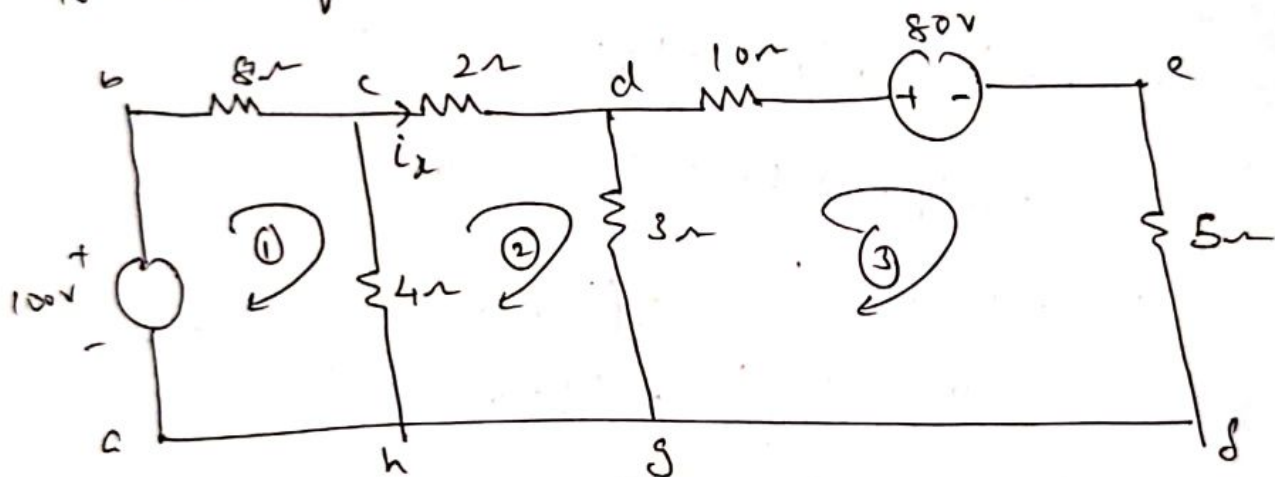Sol/ Convert the current source to its equivalent voltage source




Mesh abch, $12i_1 - 4i_2 = 100$

cdgh, $-4i_1 + 9i_2 - 3i_3 = 0$

dedf, $-3i_2 + 18i_3 = -80$

$$i_2 = i_x = 2.79A //$$

3)

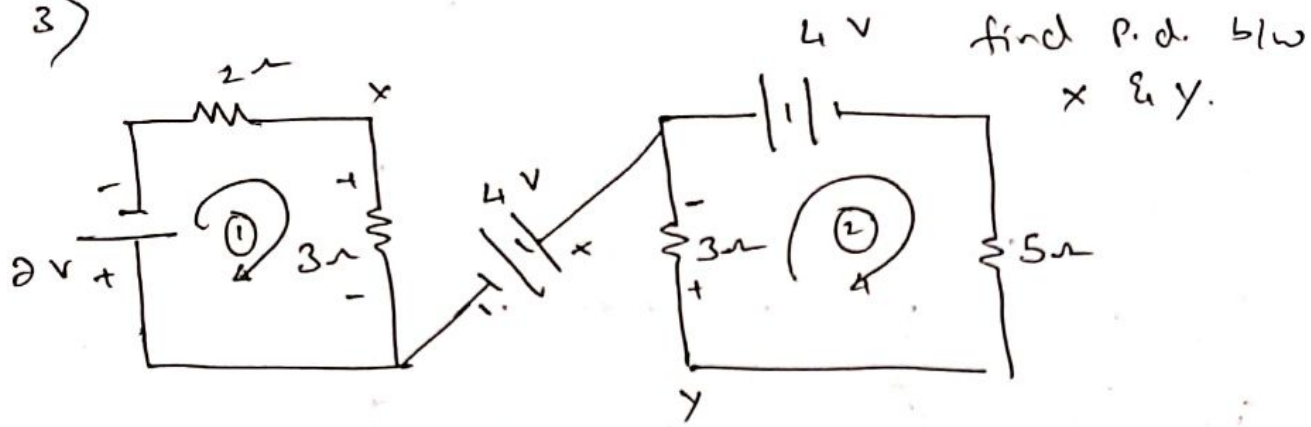

find p.d. b/w x & y.

Apply KVL to loop ①,

$$-2 - 2i_1 - 3i_1 = 0$$

Apply KVL to loop ②

$$-3i_2 - 4 - 5i_2 = 0$$

$$\therefore -5i_1 = 2$$

$$\therefore i_2 = -0.5 \text{ A}$$

$$i_1 = -0.4 \text{ A}$$

$$V_{xy} - 3i_1 + 4 + 3i_2 = 0$$


$$V_{xy} = 3i_1 + 4 + 3i_2 = 0$$

$$V_{xy} = -2i_1 + 4 + 3i_2$$

$$V_{xy} = -3.7 \text{ V}$$



4)

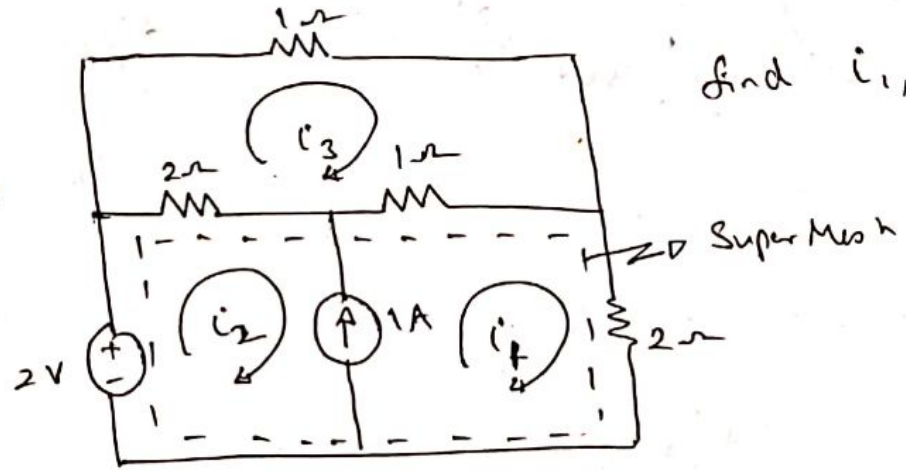

find i_1, i_2 & i_3

Super Mesh: $3i_1 + 3i_2 - 3i_3 = 2$

Mesh 3: $2i_1 + i_2 - 4i_3 = 0$


$$i_1 - i_2 = 1$$

$$i_1 = 1.5 \text{ A} \quad 1/11$$


$$i_2 = 0.5 \text{ A} \quad -1/11$$

$$i_3 = 0.9 \text{ A} \quad 2/11$$

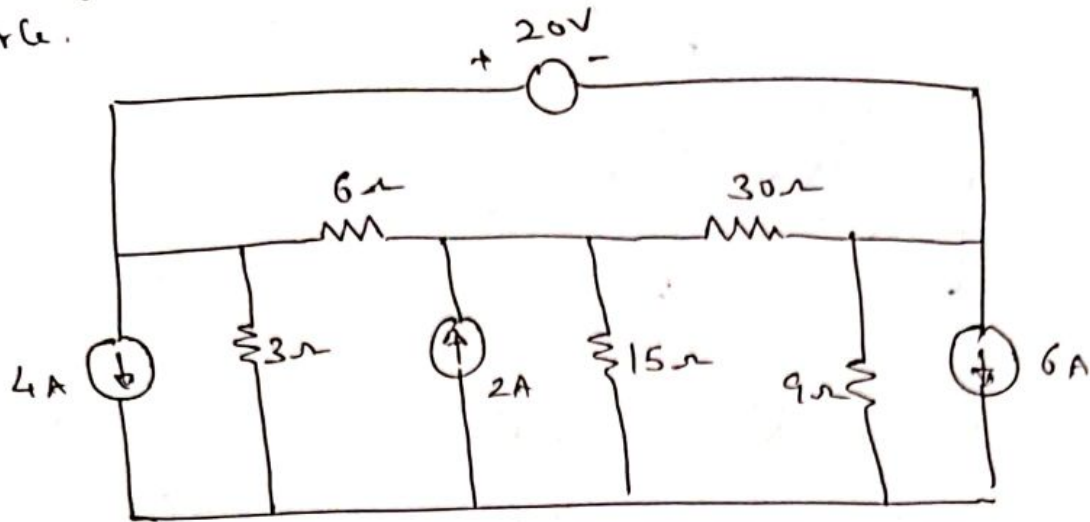5) Using Mesh Current analysis find the voltage across 6A Source.



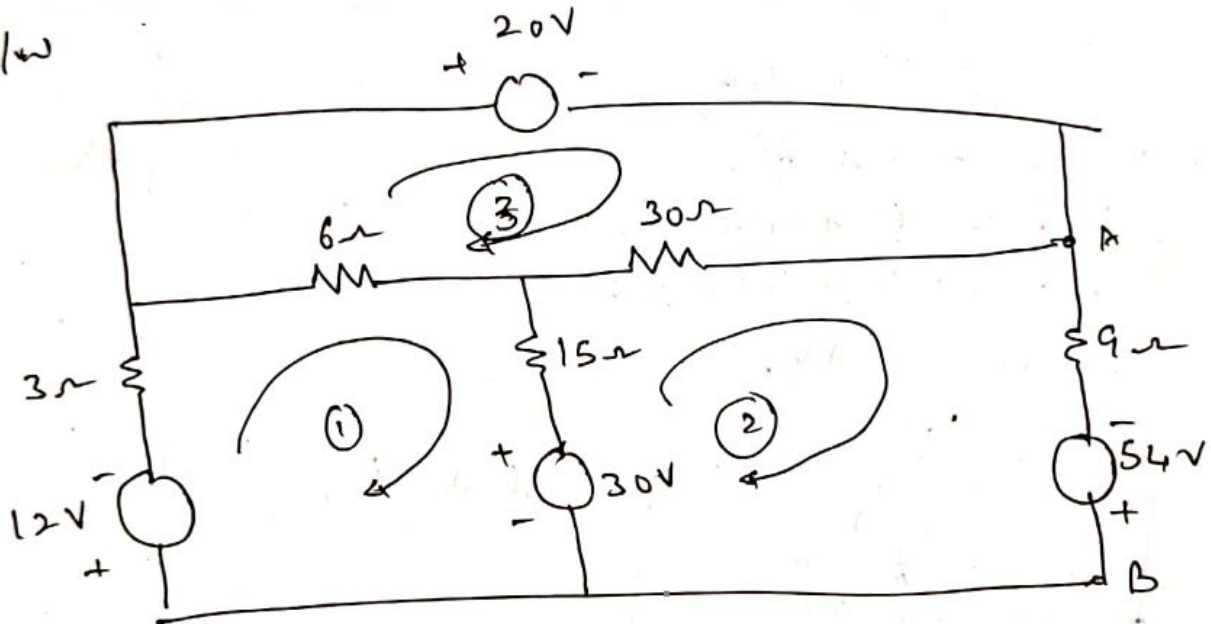Solⁿ Convert all I. Src into voltage Src & draw the n/w



$$24i_1 - 15i_2 - 6i_3 = -42$$

$$-15i_1 + 54i_2 - 30i_3 = 84$$

$$-6i_1 - 30i_2 + 36i_3 = -20$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{23112}{9612} = 2.4 \text{ A}$$


$$V_{AB} = 9 \times i_2 - 54 = -32.4 \text{ V}$$

Which is the drop across current src of 6A

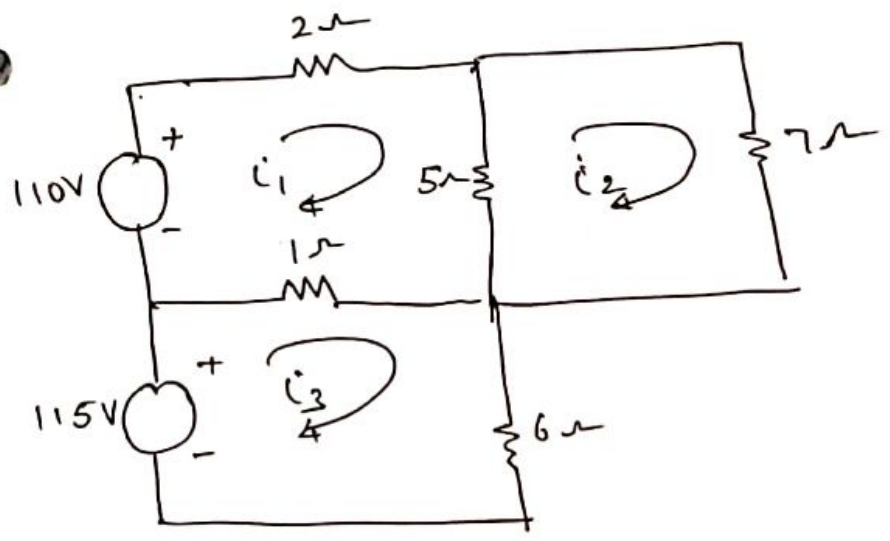6) The loop equations of a n/w are
 $8I_1 - 5I_2 - I_3 = 110$
 $-5I_1 + 12I_2 = 0$
 $-I_1 + 7I_3 = 115$, Draw the n/w

Sol. In Matrix form,

$$\begin{bmatrix} 8 & -5 & -1 \\ -5 & 12 & 0 \\ -1 & 0 & 7 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 110 \\ 0 \\ 115 \end{bmatrix}$$




7) The current equations of a certain ckt are

$$\begin{bmatrix} 3 & -2 & -1 \\ -2 & 5 & -3 \\ -1 & -3 & 8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 6 \\ -1 \\ 0 \end{bmatrix}$$

Draw the n/w.



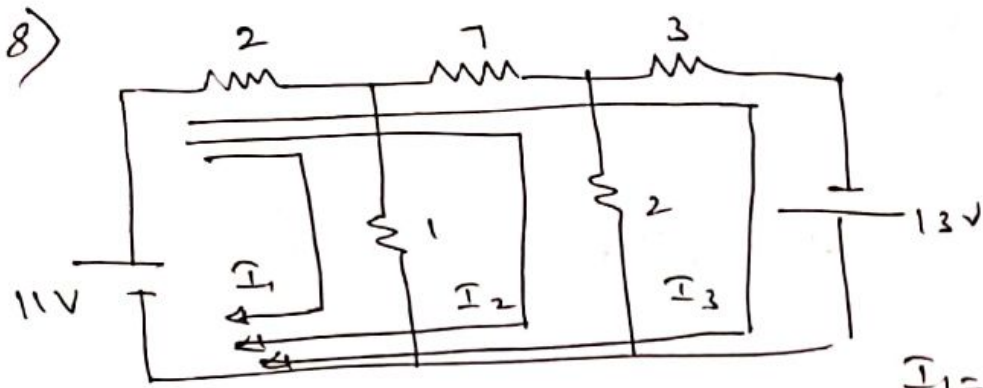


$$I_1 = 3 \text{ A}$$

$$I_2 = -2 \text{ A}$$

$$I_3 = 3 \text{ A}$$

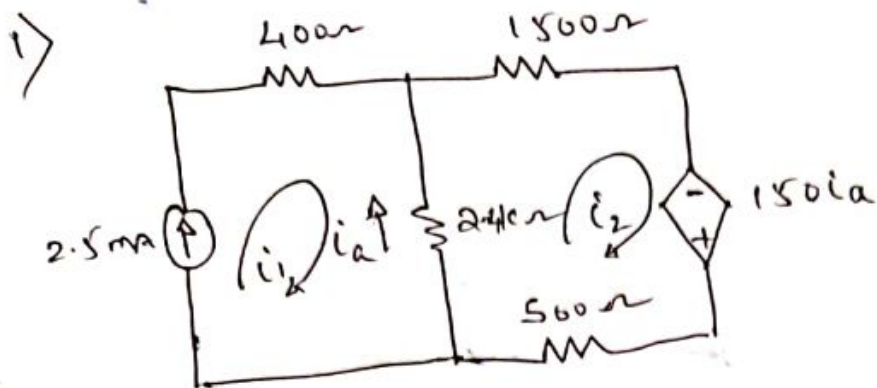Mesh analysis for the ckt's involving dependent srcs.



Sol/ Mesh 1: $i_1 = 2.5 \text{ mA}$, $i_a = i_2 - i_1$

Mesh 2: $-2400 i_1 + 4400 i_2 = 150 i_a$


$$-2400 i_1 + 4400 i_2 = 150 (i_2 - i_1)$$

$$5.625 = 4250 i_2$$

$$i_2 = 1.323 \text{ mA}$$

$$\therefore i_a = i_2 - i_1 = -1.176 \text{ mA}$$

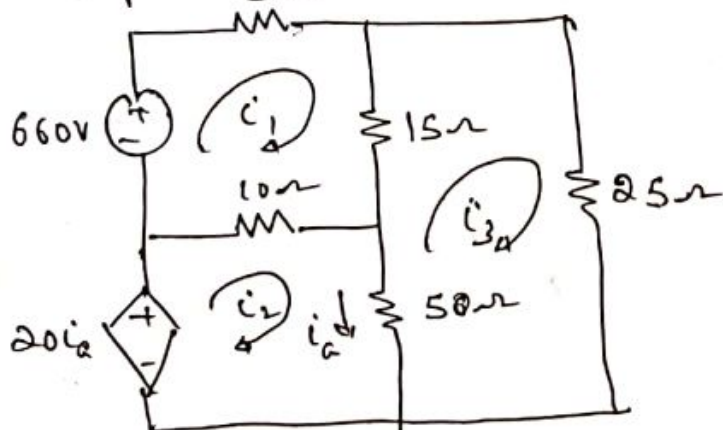2) Find the total power delivered in the ckt by dependent voltage src



Sol/ $30 i_1 - 10 i_2 - 15 i_3 = 660$ — (1)

$$-10 i_1 + 60 i_2 - 50 i_3 = 20 i_a = 20 (i_2 - i_3)$$

$$-10 i_1 + 40 i_2 - 30 i_3 = 0$$
 — (2)


$$-15 i_1 - 50 i_2 + 90 i_3 = 0$$
 — (3)

$$i_2 = 27 \text{ A}, \quad i_3 = 22 \text{ A}$$

$$i_a = i_2 - i_3 = 5 \text{ A}$$

$$P_{20\Omega} = (20 i_a) i_2 = 2700 \text{ W}$$

3)

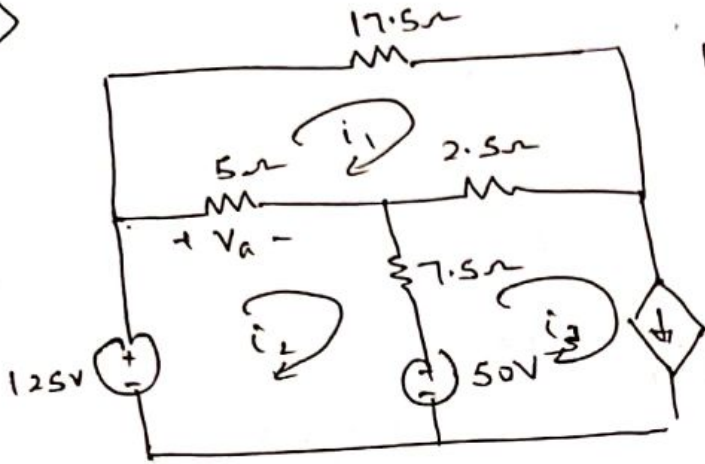

Find the total power delivered in the circuit using Mesh-current Method

$$0.2 V_a \text{ [dependent]}$$

Mesh 1: $25i_1 - 5i_2 - 2.5i_3 = 0$

2: $-5i_1 + 12.5i_2 - 7.5i_3 = 75$

$$i_3 = 0.2 V_a$$

$$V_a = 5(i_2 - i_1)$$

$$\therefore i_3 = 0.2 \times 5(i_2 - i_1) = i_2 - i_1$$


$$i_1 = 3.6 \text{ A}, \quad i_2 = 13.2 \text{ A}$$

$$i_3 = i_2 - i_1 = 9.6 \text{ A}$$

$$P_{5\Omega} = 595.2 \text{ W (absorbed)}$$


$$P_{50V} = 180 \text{ W} \quad i_3 \rightarrow 50(i_2 - i_1)$$
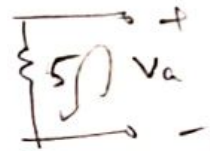
$$P_{125V} = 1650 \text{ W} \quad i_2 \rightarrow 125i_2$$



$$V_a = 5(i_2 - i_1)$$

$$V_a = 5(i_2 - i_1)$$

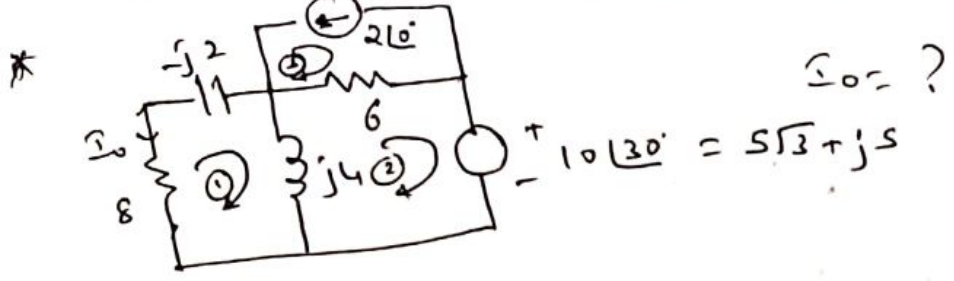

Sol

$$I_3 = -20 \angle 0^\circ = -2$$

$$I_3 = -2 \quad \text{--- (1)}$$

loop 1

$$(8 + j2) I_1 - j4 I_2 = 0 \quad \text{--- (2)}$$


$$-j4 I_1 + (6 + j4) I_2 - 6 I_3 = -(5\sqrt{3} + js) \quad \text{--- (3)}$$

$$\Delta = \begin{vmatrix} 0 & 0 & 1 \\ (8+j2) & -j4 & 0 \\ -j4 & (6+j4) & -6 \end{vmatrix} = 56 + j44$$

$$\Delta_1 = \begin{vmatrix} -2 & 0 & 1 \\ 0 & -j4 & 0 \\ -(5\sqrt{3} + js) & (6+j4) & -6 \end{vmatrix} = \frac{56 - jt}{20 - j(48 + 20\sqrt{3})}$$

$$I_1 = \frac{\Delta_1}{\Delta} = -0.496 - j1.085$$
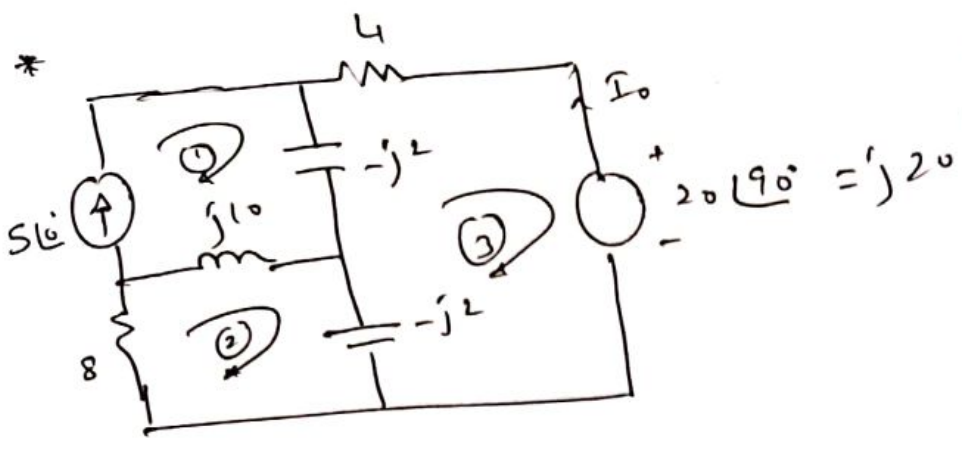
$$I_1 = 1.193 \angle -114.55^\circ \quad \text{[OR]} \quad 1.193 \angle 65.45^\circ$$



Sol

$$I_1 = +5 \text{ --- (1)}$$

$$-j10 I_1 + (8 + j8) I_2 + j2 I_3 = 0 \text{ --- (2)}$$

$$j2 I_1 + j2 I_2 + (4 - j4) I_3 = -j20 \text{ --- (3)}$$

$$\Delta = \begin{vmatrix} 1 & 0 & 0 \\ -j10 & (8+j8) & j2 \\ j2 & j2 & (4-j4) \end{vmatrix} = 68$$


~~$$\Delta_2 = \begin{vmatrix} 1 & -5 & 0 \\ -j10 & 0 & j2 \\ j2 & -j20 & 4-j4 \end{vmatrix} = 180 + j200$$~~

$$\Delta_3 = \begin{vmatrix} 1 & 0 & +5 \\ -j10 & (8+j8) & -j10 \\ j2 & j2 & j2 - j20 \end{vmatrix} = 340 - j240$$

$$I_3 = \frac{\Delta_3}{\Delta} = 5 - j3.529$$

$$I_0 = -I_3 = 6.12 \angle 144^\circ \text{ A}$$

Node voltage Analysis:

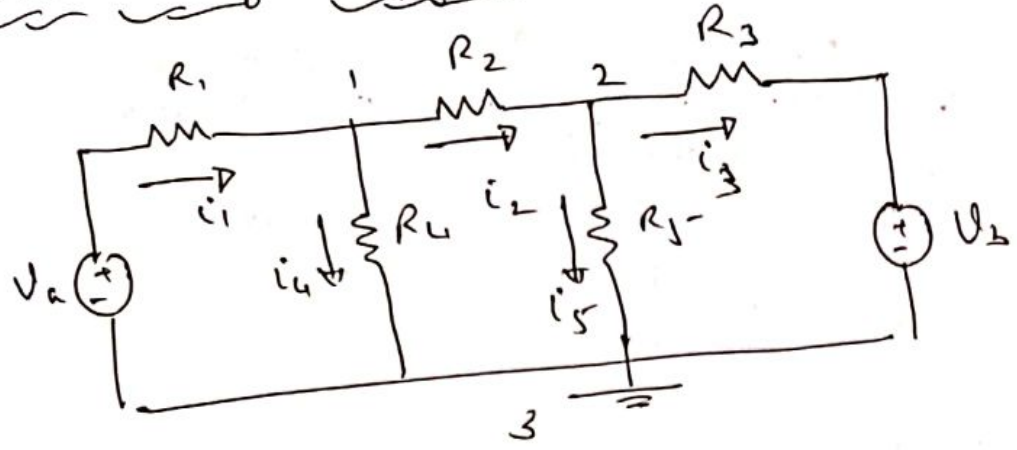

Applying KCL at node 1,

$$i_1 = i_2 + i_4$$

$$\frac{V_a - V_1}{R_1} = \frac{V_1 - V_2}{R_2} + \frac{V_1}{R_4}$$

$$V_1 \left[\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{R_4} \right] - \frac{V_2}{R_2} = \frac{V_a}{R_1} \quad \text{--- (1)}$$

at node 2


$$i_2 = i_3 + i_5$$

$$\frac{V_1 - V_2}{R_2} = \frac{V_2 - V_b}{R_3} + \frac{V_2}{R_5}$$

$$-\frac{V_1}{R_1} + V_2 \left[\frac{1}{R_2} + \frac{1}{R_5} + \frac{1}{R_3} \right] = \frac{V_b}{R_3}$$

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{V_a}{R_1} \\ \frac{V_b}{R_3} \end{bmatrix}$$

Problem 11

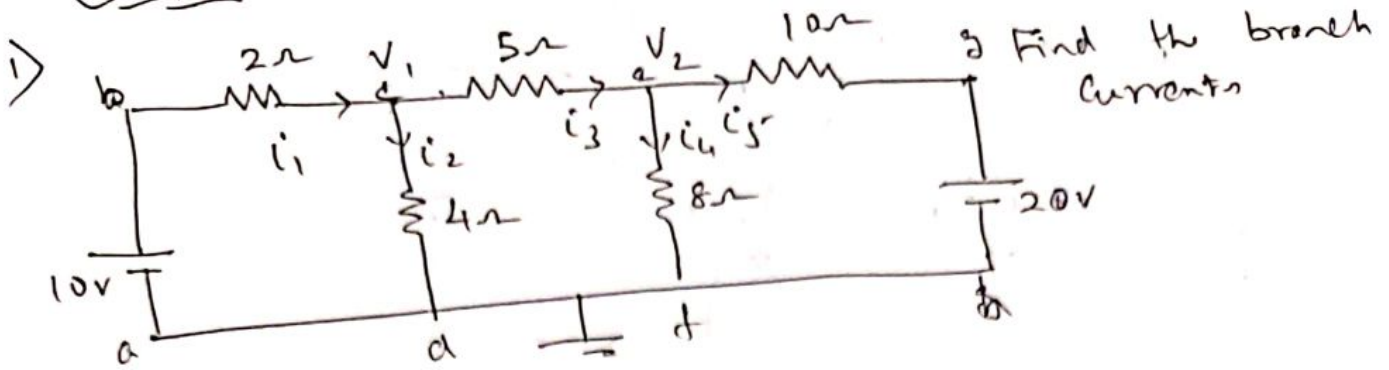

(1) $i_1 = i_2 + i_3$

$$\frac{10 - V_1}{2} = \frac{V_1}{4} + \frac{V_1 - V_2}{5}$$

~~$0.5V_1 - 0.2V_2 = 5$~~

(1) $V_1 \left[\frac{1}{4} + \frac{1}{5} + \frac{1}{2} \right] - \frac{V_2}{5} = 5$

(2) $i_3 = i_4 + i_5$


$$\frac{V_1 - V_2}{5} = \frac{V_2}{8} + \frac{V_2 - 20}{10}$$

$$-0.2V_1 + 0.425V_2 = 2$$

$$V_1 = 6.94V, \quad V_2 = 7.97V$$


$i_{abc} = 1.53A$ $i_{cd} =$ $i_{ce} =$

$i_{ef} =$ ~~i_{fg}~~

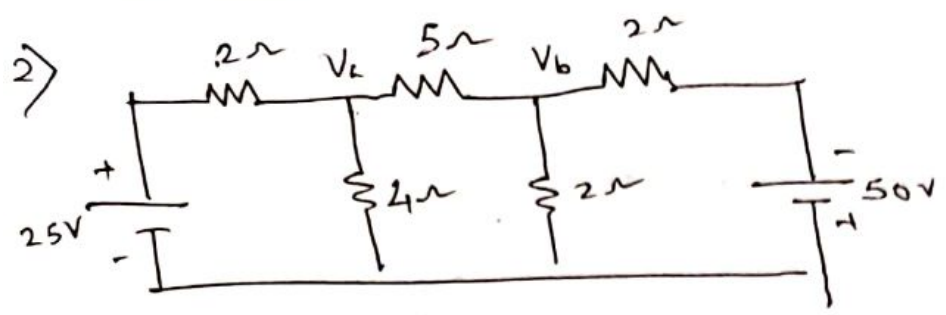

$V_a = 9.09V$
 $V_b = -19.318V$

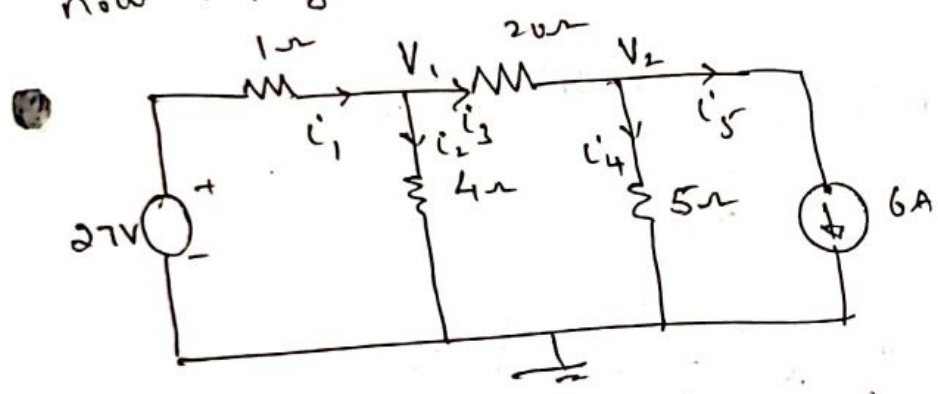3) Find the Power dissipated by the 20Ω resistor by node voltage Method



① $i_1 = i_2 + i_3$ ———

$$\frac{27 - V_1}{1} = \frac{V_1}{4} + \frac{V_1 - V_2}{20}$$

$$V_1 \left[\frac{1}{4} + \frac{1}{20} + 1 \right] - \frac{V_2}{20} = 27 \quad \text{--- (1)}$$

② $i_3 = i_4 + i_5$

$$\frac{V_1 - V_2}{20} = \frac{V_2}{5} + 6$$

$$-V_1 \left[\frac{1}{20} \right] + V_2 \left[\frac{1}{5} + \frac{1}{20} \right] = -6 \quad \text{--- (2)}$$

$$V_1 = 20, \quad V_2 = -20$$


Power dissipated in 20Ω resistor = $\frac{V^2}{R}$

$$= \frac{(V_1 - V_2)^2}{R}$$

$$= \frac{(20 - (-20))^2}{20}$$

$$= 80 \text{ Watts}$$

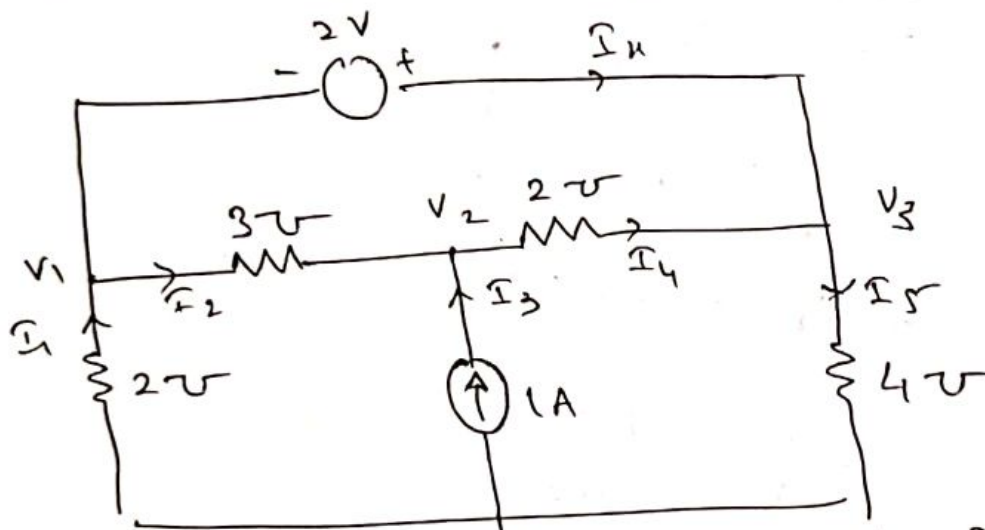4) Determine V_1, V_2 & V_3 by nodal analysis.



sol) let I_x be the current in the 2V voltage source

branch

node (1) $I_1 = I_2 + I_x$

$$-\frac{V_1}{2} = (V_1 - V_2)3 + I_x$$

$$5V_1 - 3V_2 + I_x = 0 \quad \text{--- (1)}$$

node (2) $I_2 + I_3 = I_4$

$$(V_1 - V_2)3 + 1 = (V_2 - V_3)2$$

$$-3V_1 + 5V_2 - 2V_3 = 1 \quad \text{--- (2)}$$

(3) $I_4 + I_x = I_5$

$(V_2 - V_3)2 + I_x = V_3(4)$

$-2V_2 + 6V_3 - I_x = 0$ — (3)


from the n/v, $V_3 - V_1 = 2V$ — (4)

(1) + (2)

$5V_1 - 5V_2 + 6V_3 = 0$ — (5)

• solving (2), (4), & (5)

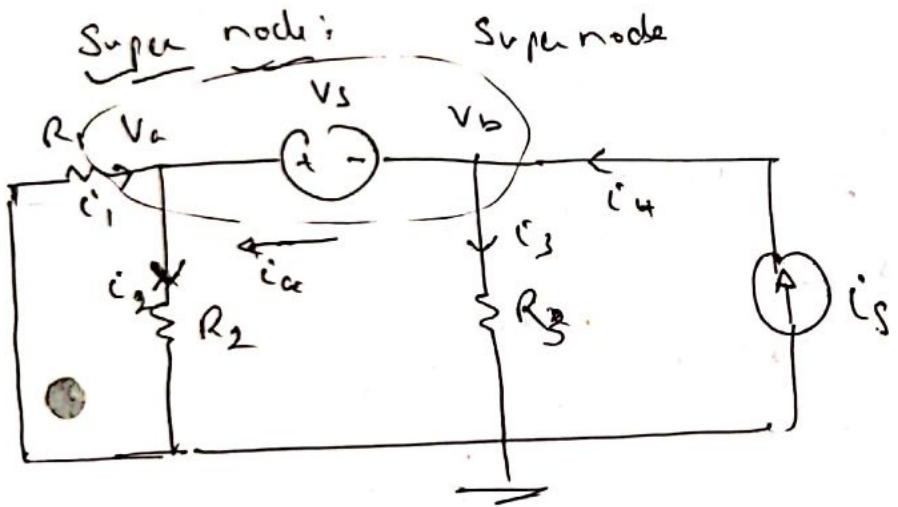$V_1 = -1.161V, V_2 = -0.166V, V_3 = 0.834V$



$V_a - V_b = V_s$ (constraint eq.) — (1)

~~$\frac{V_a}{R_1} + i_a = 0$~~

~~(a) $i_1 + i_a = i_2$
 $\frac{V_a}{R_1} + i_a = \frac{V_a}{R_2}$~~

~~$\frac{V_a}{R_1} - \frac{V_a}{R_2} = -i_a$ — (1)~~

(b) $i_a + i_3 = i_4$
 $i_a + \frac{V_b}{R_3} = i_5$ — (2)

$$\cancel{\frac{V_a}{R_1}} + \cancel{\frac{V_b}{R_3}} \rightarrow \frac{V_a}{R_2}$$

$$(a) \quad i_1 + i_a = i_2$$

$$\frac{V_a}{R_1} + i_a = \frac{V_a}{R_2}$$

$$\frac{V_a}{R_1} - \frac{V_a}{R_2} + i_a = 0 \quad \leftarrow (2)$$

$$(b) \quad i_a + i_3 = i_4$$

$$i_a + \frac{V_b}{R_3} = i_5 \quad \leftarrow (3)$$

$$(2) - (3)$$

$$\frac{V_a}{R_1} - \frac{V_a}{R_2} - \frac{V_b}{R_3} = -i_5 \quad \leftarrow (4)$$

Solving (2) & (4), $V_L =$

[OR]

$$i_1 + i_4 = i_2 + i_3$$

$$\frac{V_a}{R_1} + i_5 = \frac{V_a}{R_2} + \frac{V_b}{R_3}$$


$$\frac{V_a}{R_1} - \frac{V_a}{R_2} - \frac{V_b}{R_3} = -i_5 \quad \leftarrow (5)$$

(4) & (5) also

|||

Solve Prob 4 using Super node Method

(25)

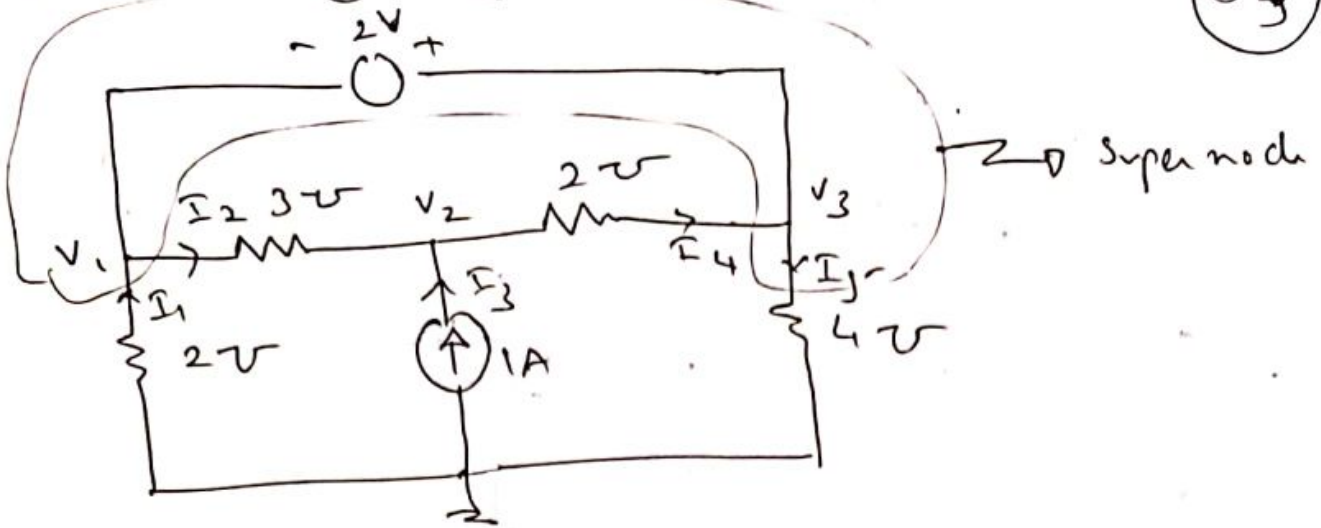

Super node (1) & (3)

$$I_1 + I_4 = I_2 + I_3$$

$$-V_1(2) + (V_2 - V_3)2 = (V_1 - V_2)3 + V_3(4)$$

$$5V_1 - 5V_2 + 6V_3 = 0 \quad \text{--- (1)}$$

Also

$$V_3 - V_1 = 2 \quad \text{--- (2)}$$


$$(2) \quad I_2 + I_3 = I_4$$

$$(V_1 - V_2)(3) + 1 = (V_2 - V_3)2$$

$$-3V_1 + 5V_2 - 2V_3 = 1 \quad \text{--- (3)}$$

$$V_1 = -1.166V, \quad V_2 = -0.166V, \quad V_3 = 0.834V$$

5)

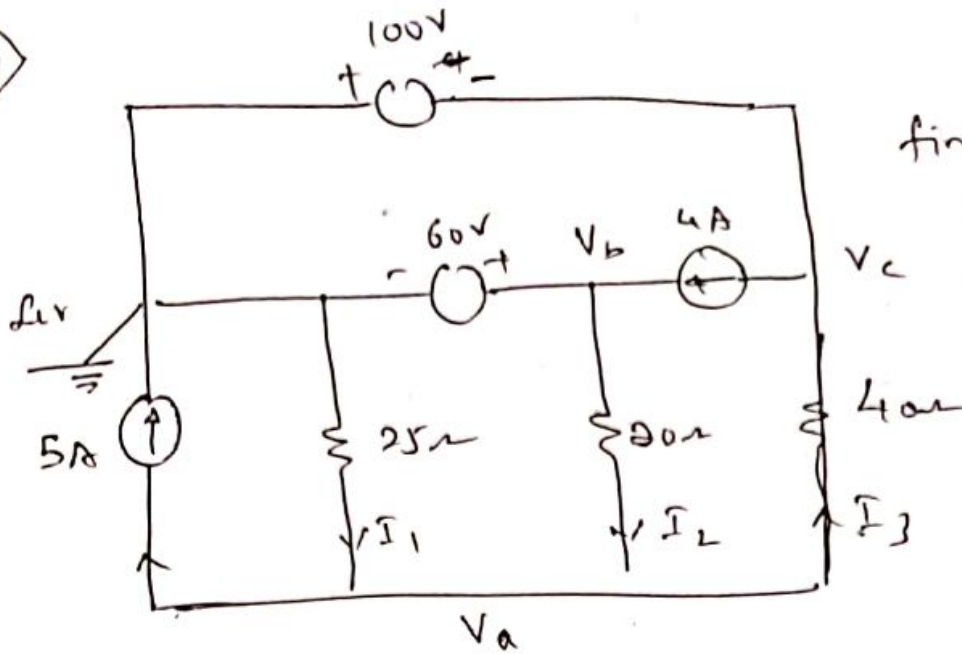

find the voltage across
40Ω & power
supplied by 5A
src.

Sol $V_c = -100V, V_b = 60V.$

Q $5 + I_3 = I_1 + I_2$

$$5 + \frac{V_a - V_c}{40} = -\frac{V_a}{25} + \frac{V_b - V_a}{20}$$


$$5 + \frac{V_a - 100}{40} = -\frac{V_a}{25} + \frac{60 - V_a}{20}$$

$$V_a \left[\frac{1}{25} + \frac{1}{20} + \frac{1}{40} \right] + 5 - \frac{60}{20} + \frac{100}{40} = 0$$

$$V_a = -39.13V$$

$$\begin{aligned} V_{40\Omega} &= V_a - V_c \\ &= -39.13 + 100 \\ &= 60.86V \end{aligned}$$

$$P_{5A \text{ src}} = |V_a| \times 5 = 195.65W$$

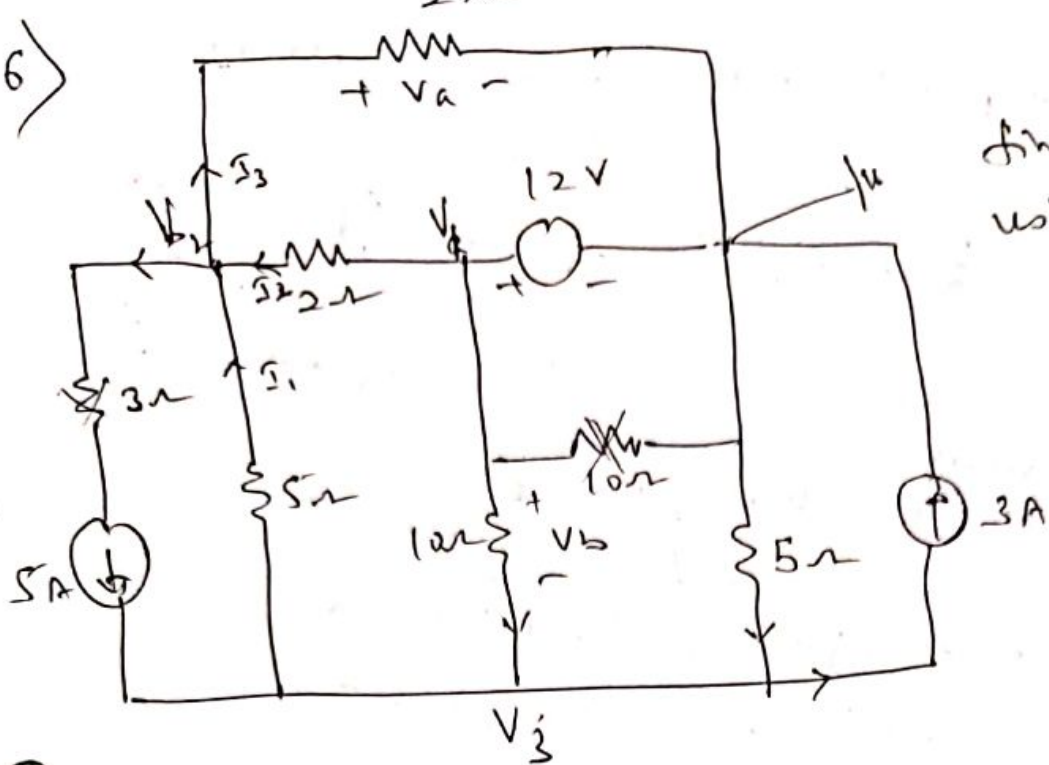

Find V_a & V_b using node voltage method.

so $V_1 = 12V$

Q-2
$$\frac{V_1 - V_2}{2} + \frac{V_2 - V_2}{5} = \frac{V_2}{2} + 5$$

$$V_1 \left[\frac{1}{2} \right] - V_2 \left[\frac{1}{2} + \frac{1}{5} + \frac{1}{2} \right] + V_3 \left[\frac{1}{5} \right] = 5$$

$$0.5V_1 - 1.2V_2 + 0.2V_3 = 5$$

$$0.5V_1 - 1.2V_2 + 0.2V_3 = 5 \quad (1)$$

$$-1.2V_2 + 0.2V_3 = -1 \quad (1')$$

Q-3

$$5 + \frac{V_1 - V_3}{10} - \frac{V_3}{5} = 3 + \frac{V_3 - V_2}{5}$$


$$V_1 \left[\frac{1}{10} \right] + \frac{V_2}{5} - V_3 \left[\frac{1}{10} + \frac{1}{5} + \frac{1}{5} \right] = 3 - 5$$

$$0.1V_1 + 0.2V_2 - 0.5V_3 = -2 \quad (2)$$

$$0.2V_2 - 0.5V_3 = -3.2 \quad (2')$$

$$V_2 = 2.035V, \quad V_3 = 7.21V$$
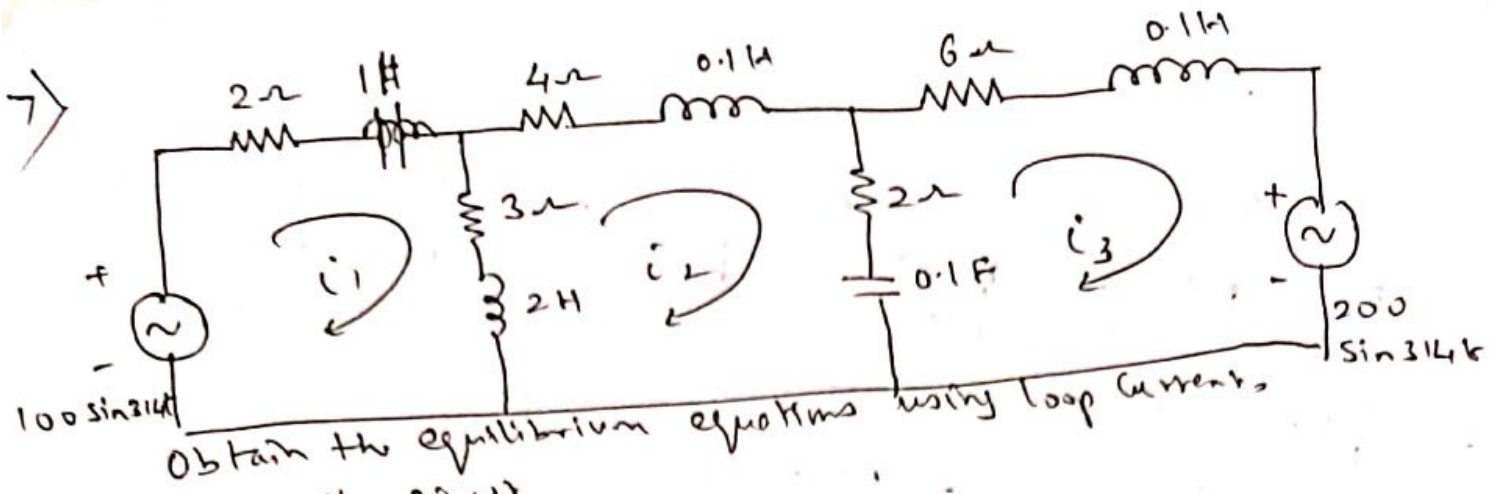
$$V_a = V_2 = 2.035V, \quad V_b = V_1 - V_3 = 4.79V$$



Sol

$$V = V_m \sin \omega t$$

$$V_m = 100, \quad \omega = 314, \quad = 2\pi f$$

$$\therefore f = 50 \text{ Hz}$$

$$Z_1 = R_1 + jX_{L1} = 2 + j\omega L_1 = (2 + j314) \Omega$$

$$Z_2 = R_2 + jX_{L2} = 3 + j\omega L_2 = (3 + j628) \Omega$$

$$Z_3 = R_3 + jX_{L3} = 4 + j\omega L_3 = 4 + j31.4 \Omega$$


$$Z_4 = R_4 - jX_C = 2 - j\frac{1}{\omega C} = 2 - j0.03 \Omega$$

$$Z_5 = 6 + jX_{L4} = 6 + j31.4 \Omega$$

$$\text{R.M.S. value of } V_1 = \frac{100}{\sqrt{2}} = 70.7 \text{ V}$$

$$\therefore V_1 = 70.7 \angle 0^\circ \text{ V}$$
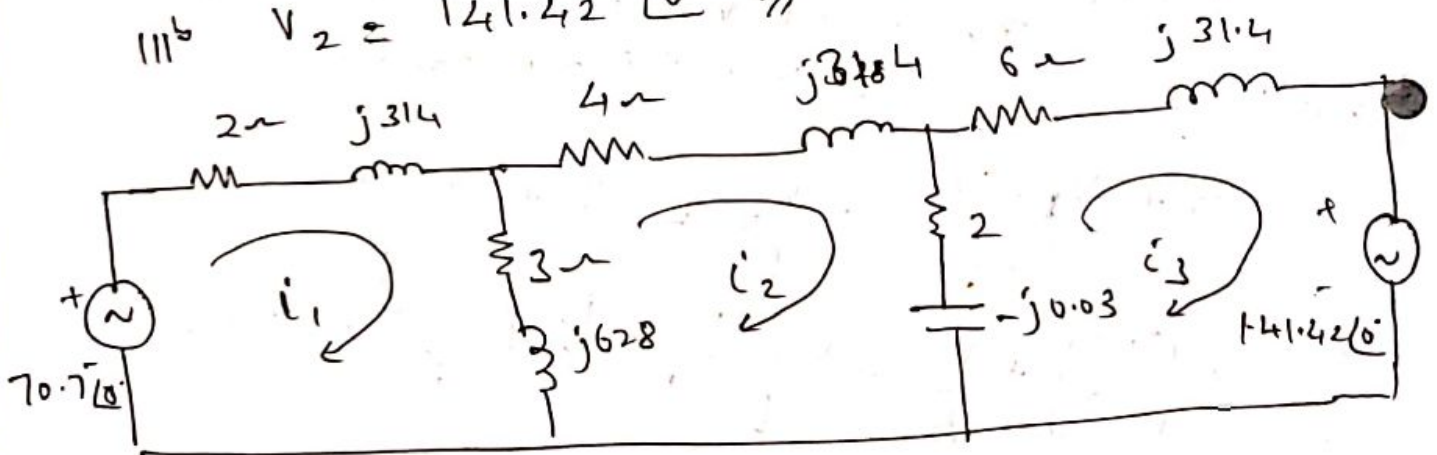
$$\text{III} \quad V_2 = 141.42 \angle 0^\circ \text{ V}$$




loop (1) KVL

$$(5 + j942) i_1 - (3 + j628) i_2 = 70.7 \angle 0^\circ \quad \text{--- (1)}$$

$$\text{loop (2)} \quad -(3 + j628) i_1 + (9 + j659.4) i_2 - (2 - j0.03) i_3 = 0 \quad \text{--- (2)}$$
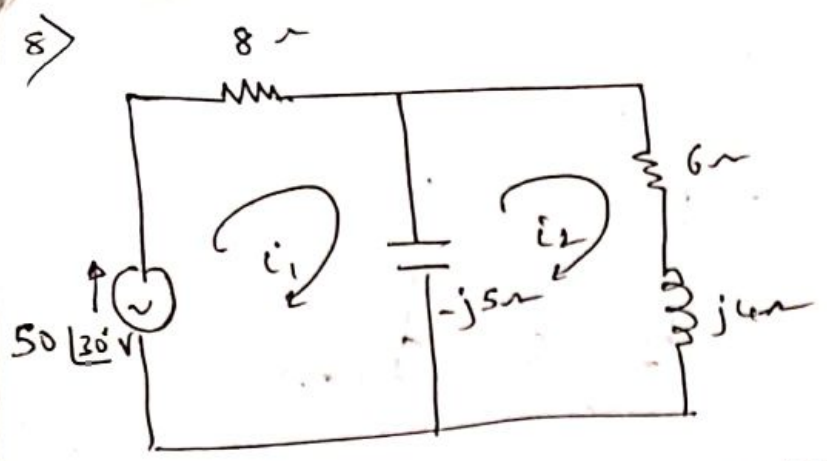
$$\text{loop (3)} \quad -(2 - j0.03) i_2 + (8 + j31.39) i_3 = -141.42 \angle 0^\circ \quad \text{--- (3)}$$



$$50\angle 30^\circ = 43.3 + j25$$

loop 1 $(8 - j5)I_1 + j5I_2 = 50\angle 30^\circ$ — (1)

loop 2 $j5I_1 + (6 - j)I_2 = 0$ — (2)


$\Delta_r = \begin{vmatrix} 8 - j5 & j5 \\ j5 & 6 - j \end{vmatrix} = 68 - j38$

$\Delta_1 = \begin{vmatrix} 43.3 + j25 & j5 \\ 0 & 6 - j \end{vmatrix} = 284.8 + j106.75$

$I_1 = \frac{\Delta_1}{\Delta} = 2.52 + j2.979 = 3.9 \angle 49.7^\circ \text{ A}$

$I_2 = 3.2 \angle -30.8^\circ \text{ A}$

Q) Determine V_1 & V_2 by nodal analysis

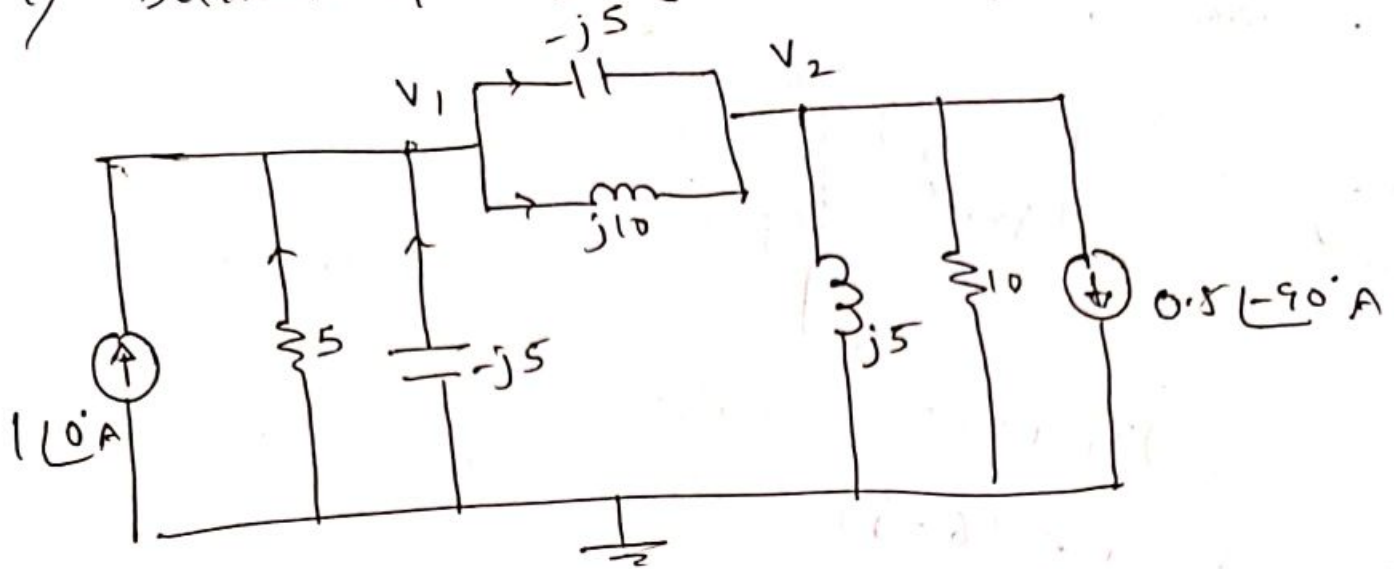

Sol/ @ node ①

$$-\frac{V_1}{5} + \frac{V_1}{j5} + 1 = \frac{V_1 - V_2}{-j5} + \frac{V_1 - V_2}{j10}$$

$$V_1 \left[\frac{1}{j10} + \frac{1}{5} - \frac{1}{j5} - \frac{1}{j5} \right] - V_2 \left[-\frac{1}{j5} + \frac{1}{j10} \right] = 1$$

$$V_1 (0.2 + j0.3) - V_2 (j0.1) = 1 \quad \text{--- (1)}$$

@ node 2,

$$-V_1 (j0.1) + V_2 (0.1 - j0.1) = -0.5 \angle -90^\circ \quad \text{--- (2)}$$

$$V_1 = 1.833 \angle -73^\circ \text{ V}$$


$$V_2 = 4.136 \angle 242.8^\circ \text{ V}$$

Thevenin's Theorem:

"Any 2 terminal linear n/w containing energy sources (generators) & impedances can be replaced with an equivalent circuit (containing) consisting of a voltage source V_{th} in series with an impedance Z_{th} ".

The value of V_{th} is the o.c. voltage b/w the terminals of the n/w & Z_{th} is the impedance measured b/w the terminals of the n/w with all energy sources eliminated (but not their impedances).

i.e. o.c. I_{src} & s.c. V_{src}

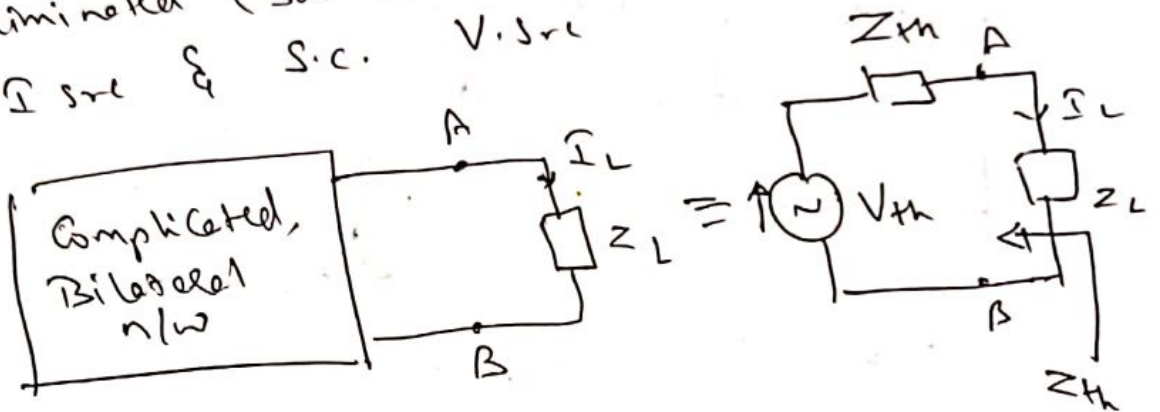

$$I_L = \frac{V_{th}}{Z_{th} + Z_L}$$

Z_{th} → Thevenin's Equivalent impedance.
 V_{oc} or V_{th} → Thevenin's Voltage.

Note * To find Z_{th} , o.c. - I_{src} & s.c. - V_{src}
 Remove the load impedance & find the resistance ~~looking~~ as looked from the terminals of load


* To find V_{th} , o.c. the load,
 & find o.c. voltage across the terminals

Problems:-


1) find $i_{2\Omega}$ using Thevenin's Theorem




Sol/
* S.C. V_{oc} & o.c. I_{sc}

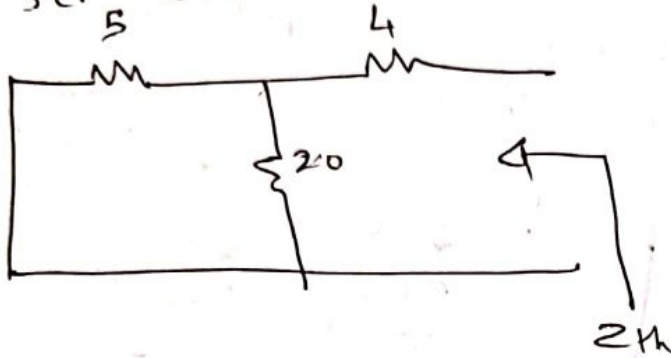

$$Z_{th} = 8\Omega$$

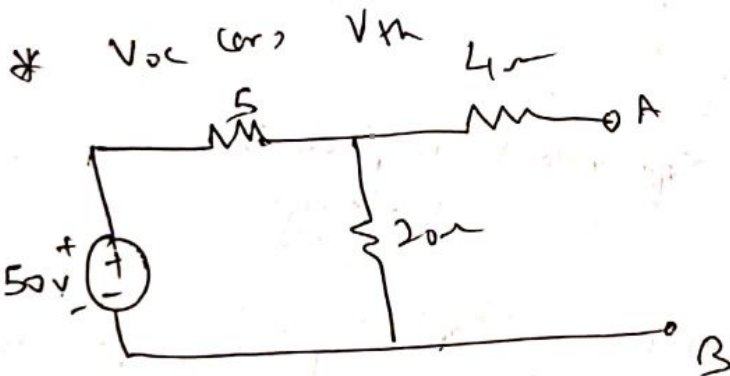
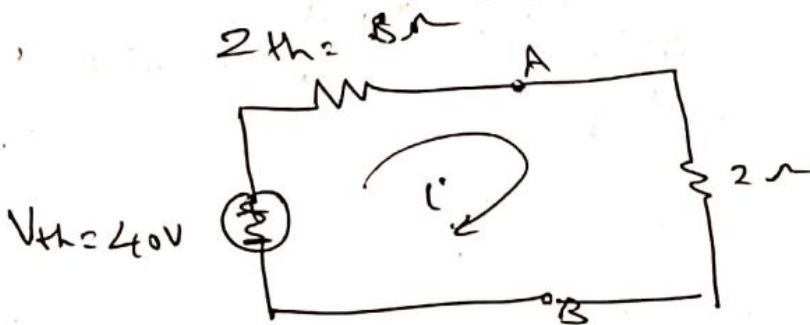
$$V_{20\Omega} = V_{oc} = \frac{20 \times 50}{20 + 5} = 40V$$



$$i_{2\Omega} = \frac{40}{8 + 2} = 4A //$$

To find R_{th} :

(29) a

3 types of ckt are considered

(i) ckt with only independent src & resistors.

deactivate src & find R_{th}
[O.C. I_{src} & S.C. V_{src}]

(ii) ckt - Resistors, dep & Indepen src.

(a) Determine O.C. voltage V_{oc} with the src activated

(b) Find the S.C. current I_{sc} , when src is applied to terminals a-b

(c) $R_t = \frac{V_{oc}}{I_{sc}}$

(iii) If the ckt contains resistors & only dependent src

(a) $V_{oc} = 0$ (since there is no energy src)




(b) Connect 1A current src to terminals a-b & determine V_{ab}

(c) $R_t = \frac{V_{ab}}{1}$

Thevenin's Theorem

(29)₅

Proof:-

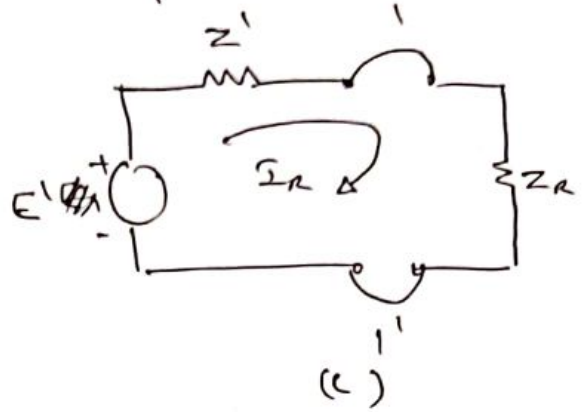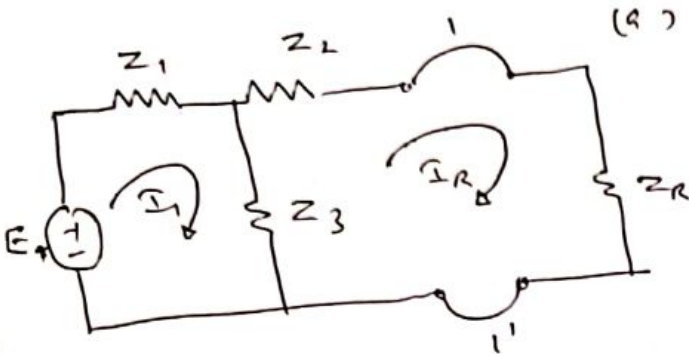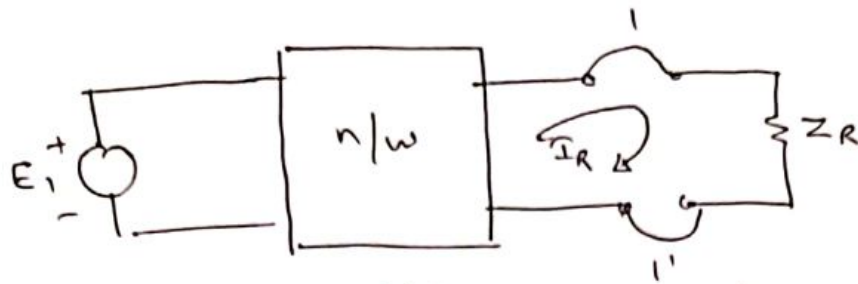

from fig (b)

$$E_1 = I_1 (Z_1 + Z_3) - I_R Z_3 \quad \text{--- (1)}$$

$$0 = -I_1 Z_3 + I_R (Z_2 + Z_3 + Z_R) \quad \text{--- (2)}$$

$$\text{then } I_1 = I_R \left(\frac{Z_2 + Z_3 + Z_R}{Z_3} \right) \quad \text{--- (3)}$$

\therefore from eq (1)

$$I_R = \frac{E_1 \left(\frac{Z_3}{Z_1 + Z_3} \right)}{Z_2 + \frac{Z_1 Z_3}{Z_1 + Z_3} + Z_R} \quad \text{--- (4)}$$

from fig (b) voltage across o.c., 1 & 1'

$$\text{is } E' = \frac{E_1 Z_3}{Z_1 + Z_3} \quad \& \quad Z' = Z_2 + \frac{Z_1 Z_3}{Z_1 + Z_3}$$


from fig (c)

$$I_R = \frac{E'}{Z' + Z_R} \quad \text{--- (5)}$$

eq (4) & (5) are same. Hence proof.


Problems:

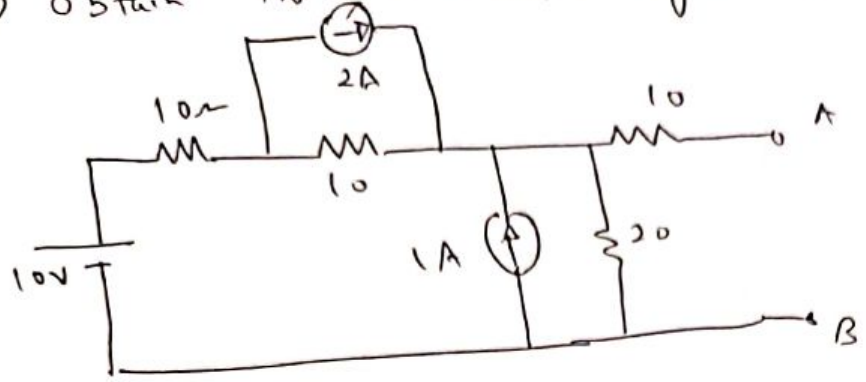1) Obtain the Thevenin's Equivalent circuit




$R_{th} = 20\Omega$
 $V_{th} = 25V$

2)

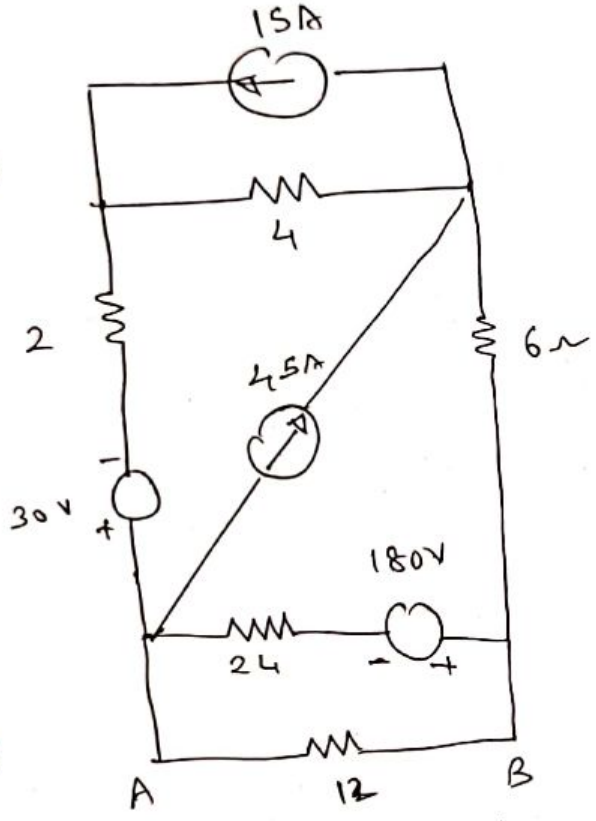


$V_{th} = -180V$
 $R_{th} = 8\Omega$
 $I_{12\Omega} = -9A$

3)

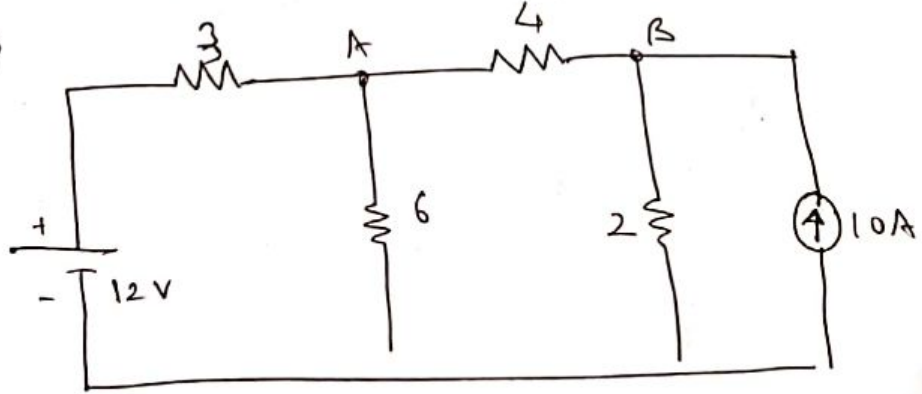

$R_{th} = 4\Omega$
 $V_{th} = -12V$

4) Find the Thevenin equivalent wrt a-b.

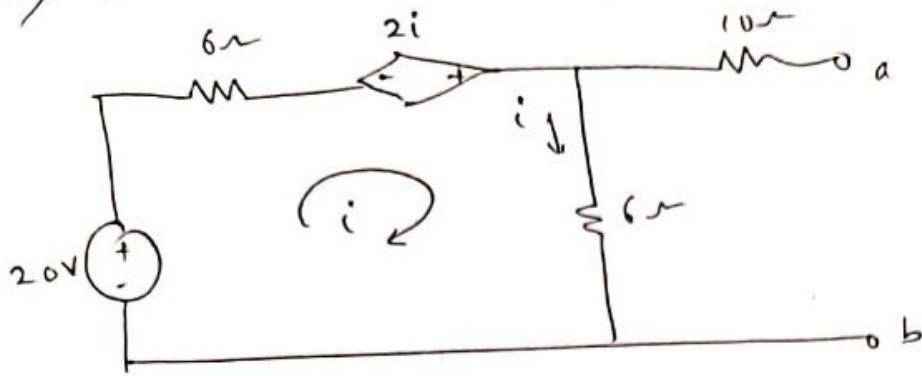


S₁) V_{oc} ,

$$+20 - 6i + 2i - 6i = 0$$

$$i = 2 \text{ A}$$

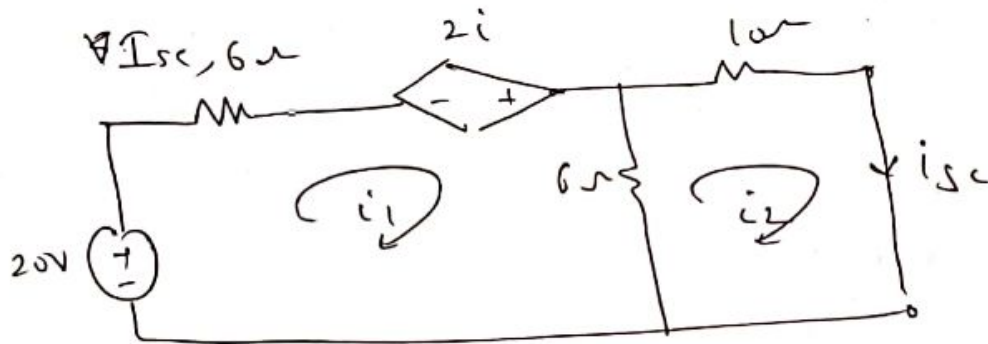
$$\therefore V_{oc} = 6 \times 2 = 12 \text{ V}$$




$$i_2 = 0.88 \text{ A}$$

$$i_{sc} = i_2 = 0.88 \text{ A}$$
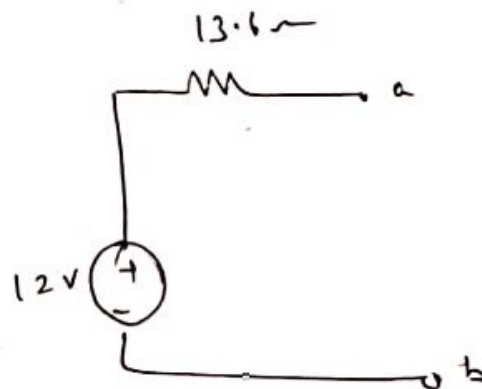
$$\therefore R_t = \frac{V_{oc}}{i_{sc}} = 13.6 \Omega$$




5) Find the V_A using Thevenin's theorem

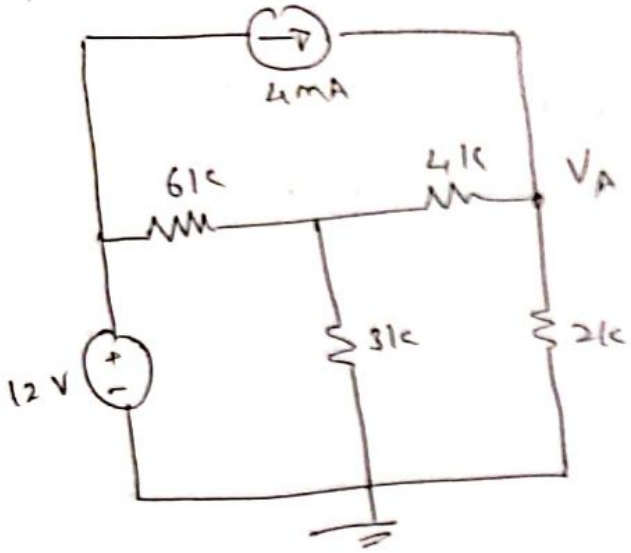


$V_A = 7V$

6) Thevenin's b/w A & B

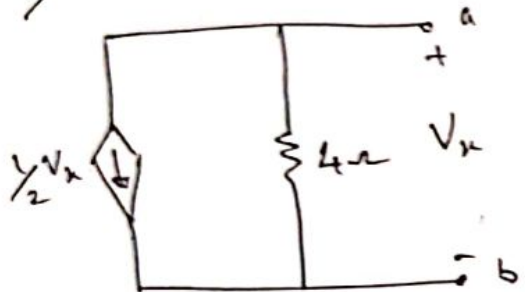


s/


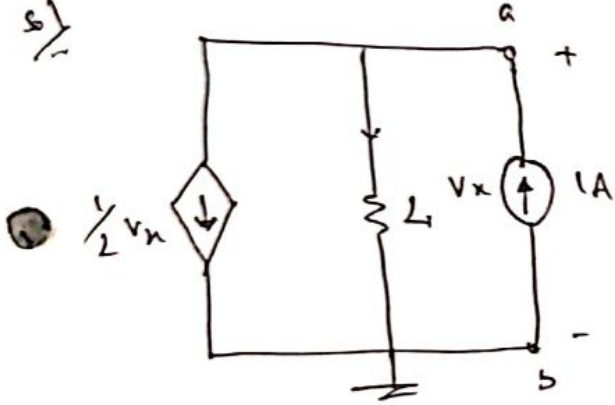


$$\frac{1}{2} V_x + \frac{V_x}{4} = 1$$

$$V_x = 1.33V$$

$$R_t = \frac{V_x}{1} = 1.33\Omega$$

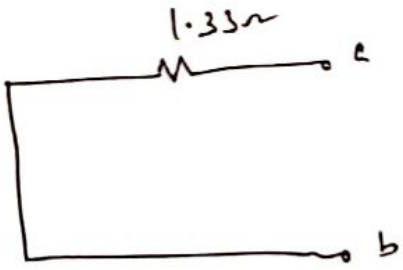

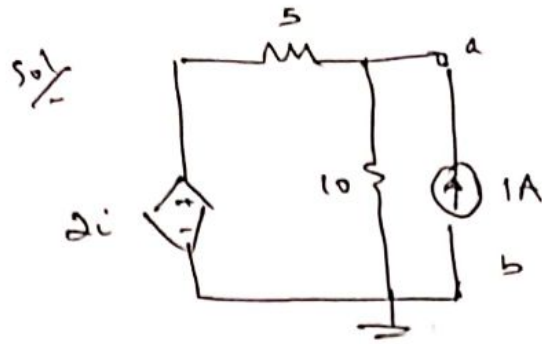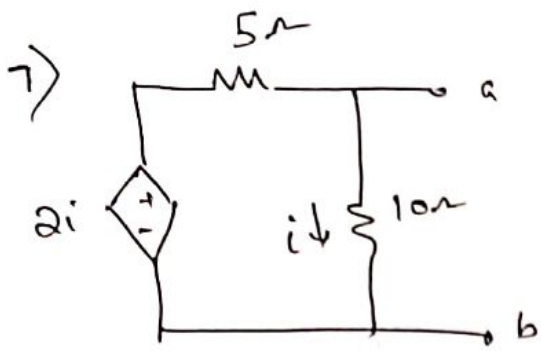


Sol/-

$$\frac{V_a - 2i}{5} + \frac{V_a}{10} = 1$$


$$V_a = \frac{50}{13} \text{ V}$$
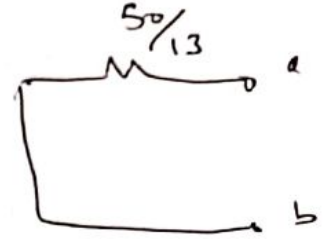
$$R_T = \frac{V_A}{1} = \frac{50}{13} \Omega$$



Norton's Theorem:


" A linear 2-terminal n/w can be replaced by an equivalent ckt consisting of a current src i_n in ||^h with resistor R_n . i_n is the SC current through the terminals & R_n is the equivalent resistance at the terminals when the independent src are deactivated "

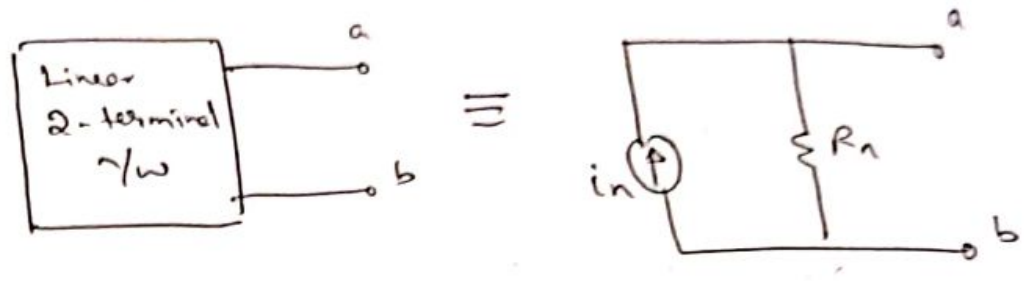


$R_n = R_{th}$, & $i_n = \frac{V_{oc}}{R_{th}}$

Problem:

1) Find the Norton Equivalent


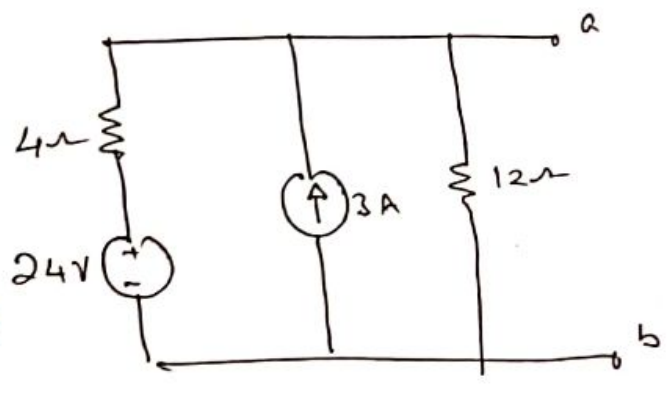


Sol: To find R_n

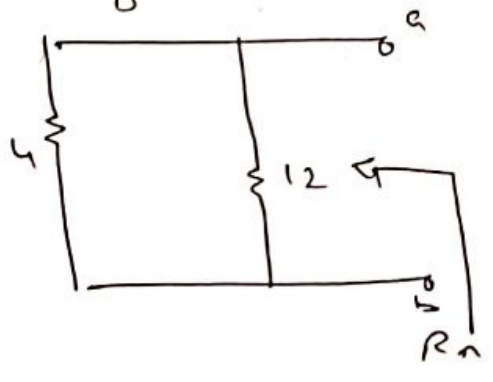


$\therefore R_n = 3 \Omega$


To find in (or) i_{sc}

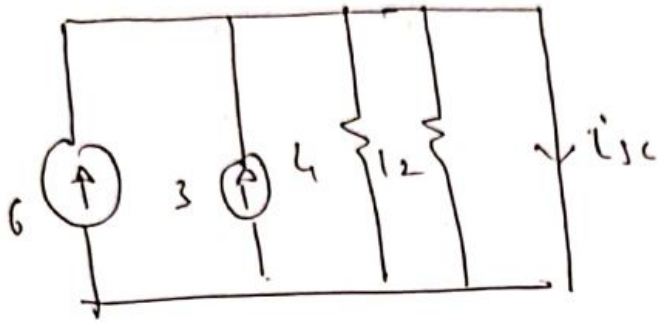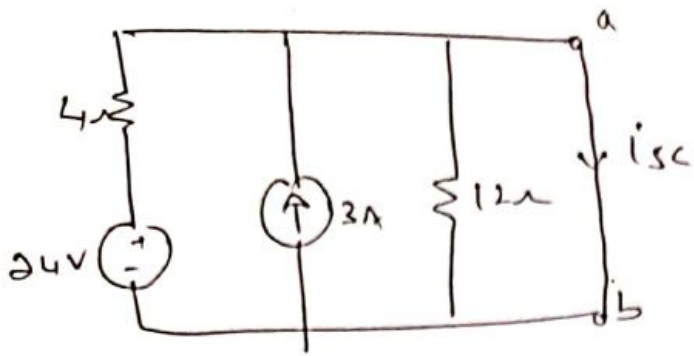


$$\therefore i_{sc} = 9A$$

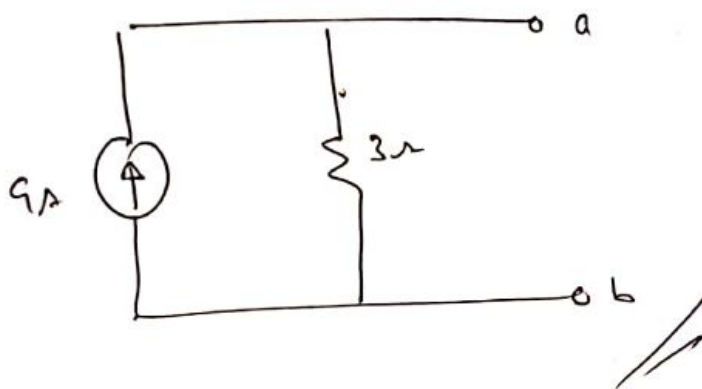

2) find I_0 using Norton's theorem

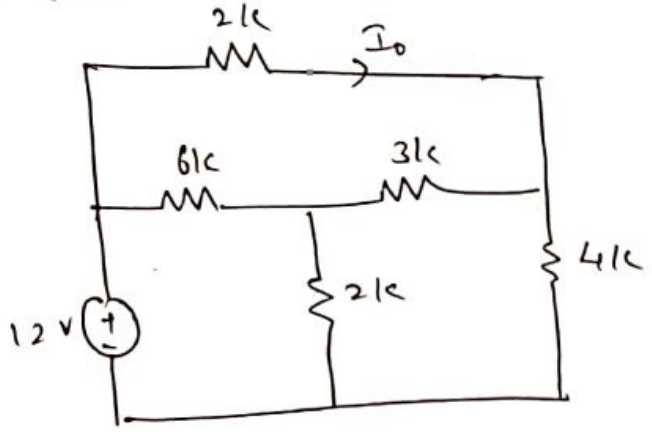


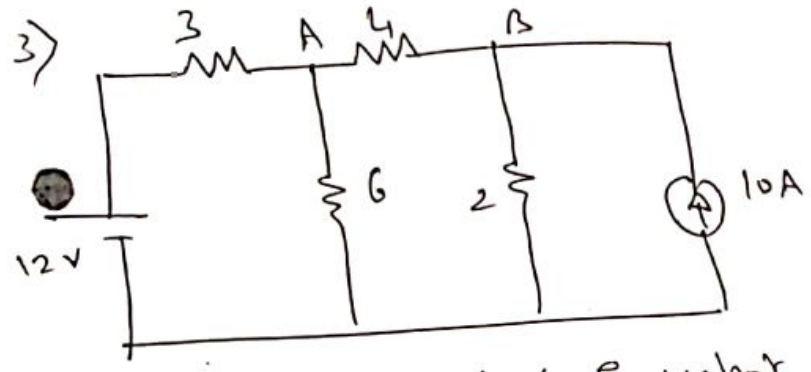$I_0 = 2.57 \text{ mA}$
 $[R_n = 2.12 \text{ k}, I_{sc} = 5 \text{ mA}]$




$I_L = 1.5 \text{ A}$
 $I_{sc} = -3 \text{ A}$
 $R_n = 4 \Omega$

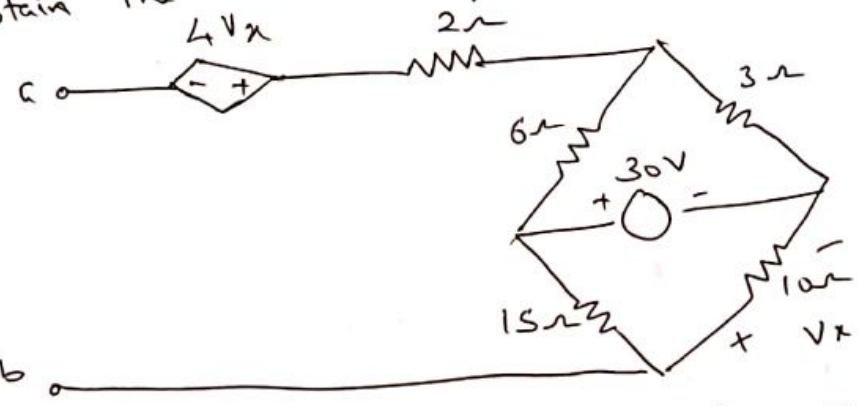4) Obtain the Norton's Equivalent of the n/w shown




$R_{th} = 34 \Omega$
 $I_n = 1.4706 \text{ A}$

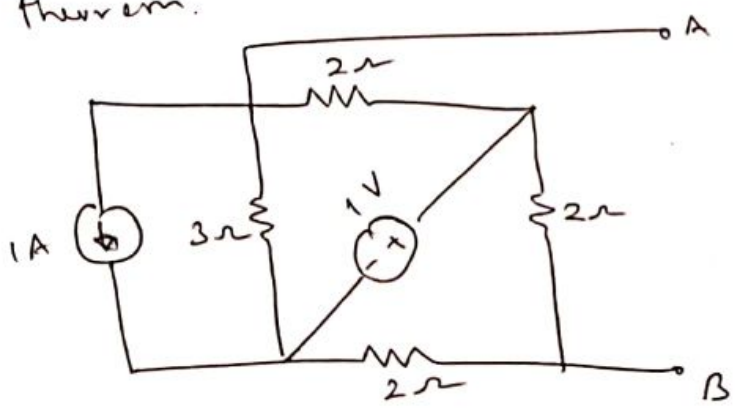5) Determine the current through 1 ohm resistor connected across AB in the n/w shown using Norton's theorem.



$I_{1\Omega} = 0.344 \text{ A}$
 $R_n = 2.2 \Omega, I_n = 0.5 \text{ A}$

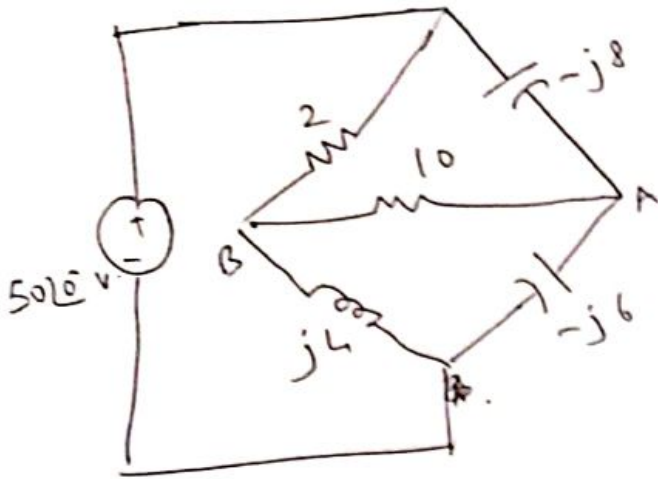6) Find the Thevenin's Equivalent circuit for the portion of the n/w external to the elements b/w A & B.





$$R_{th} = 6.83 \angle -54.17^\circ \Omega$$

$$V_{th} = 30.60 \angle 38.83^\circ \text{ V}$$

$$R_{th} = 3.01 \angle -58.50^\circ \Omega$$
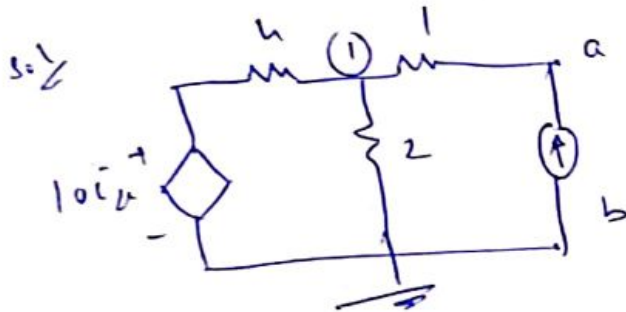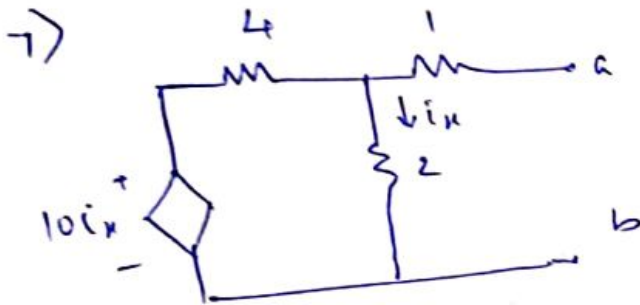
$$V_{th} = 27.2 \angle -47.1^\circ \text{ V}$$



$$i_x = \frac{V_1}{2}$$

$$\frac{V_1 - 10i_x}{4} + \frac{V_1}{2} = 1$$

$$\frac{V_1 - 5V_1}{4} + \frac{V_1}{2} = 1$$

$$V_1 = -2$$

$$\frac{V_{oc} - V_1}{1} = 1$$

$$V_{oc} = 1 + V_1$$


$$V_{oc} = -1$$

$$R_{th} = \frac{V_{oc}}{1} =$$


$$R_{th} = -1 \Omega$$

Norton's Theorem

Proof:

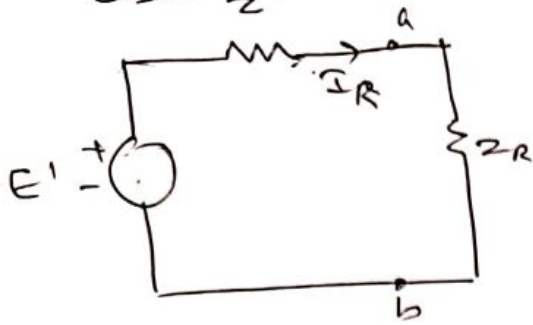

(a)

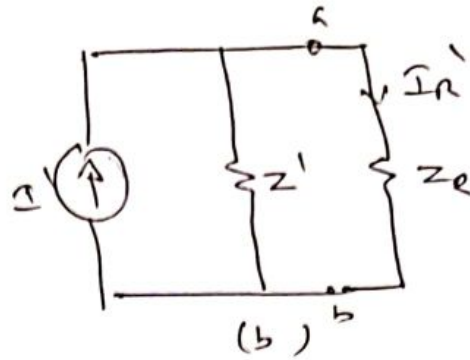

(b)

from fig (a)

$$I_R = \frac{E'}{z' + z_R} = \left(\frac{E'}{z'} \right) \left(\frac{z'}{z' + z_R} \right)$$

~~$$I_R = \frac{E'}{z' + z_R} = \frac{E'}{\frac{1}{y'} + \frac{1}{y_R}}$$~~

~~$$I_R = \frac{E'}{z'} \left(\frac{y_R}{y' + y_R} \right) = \left(\frac{E' y_R}{y' + y_R} \right) \quad \text{--- (1)}$$~~

when $z' = \frac{1}{y'}$ & $z_R = \frac{1}{y_R}$

fig (b)
$$I_{R'} = I' \left(\frac{z'}{z' + z_R} \right)$$

$$I_{R'} = I' \left(\frac{y_R}{y' + y_R} \right) \quad \text{--- (2)}$$

eq (1) & (2) are same if $I' = \frac{E'}{z'} = E' y'$


when $y' = \frac{1}{z'}$

Superposition Theorem:

In any linear circuit containing multiple independent sources, the current (or) voltage at any point in the circuit may be calculated as algebraic sum of the individual contribution of each source acting alone.


Problems:

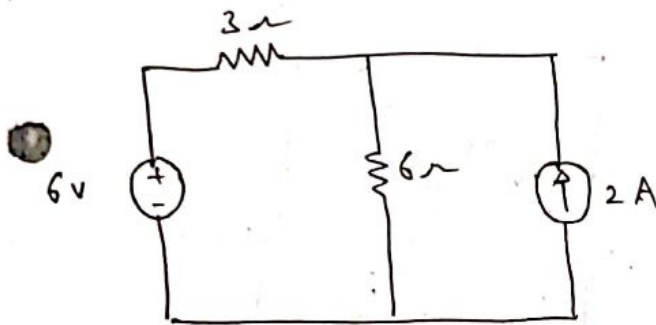1) Find $i_{6\Omega}$ using Principle of Superposition.




So

Set i_{sc} to zero

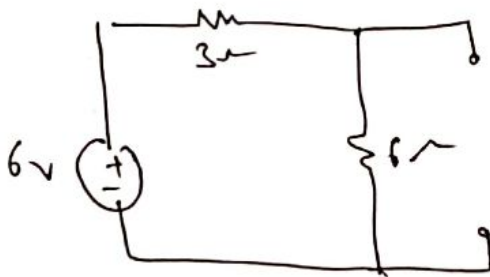

$$i_{6\Omega}^{(1)} = \frac{6}{9} = 0.666A$$


Set V_{sc} to zero

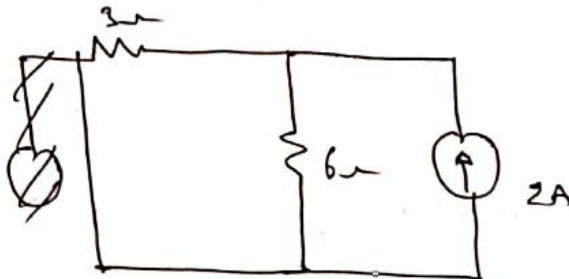

$$i_{6\Omega}^{(2)} = \frac{2 \times 3}{9} = 0.666A$$


$$\therefore i_{6\Omega} = 1.33A$$

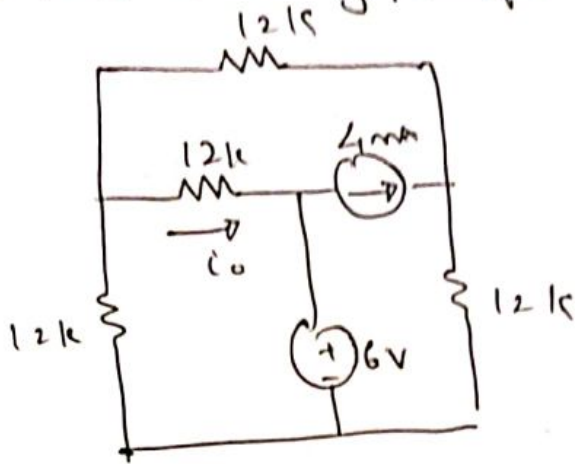2) Find i_0 using principle of Superposition




So a) $I_{src} = 0$
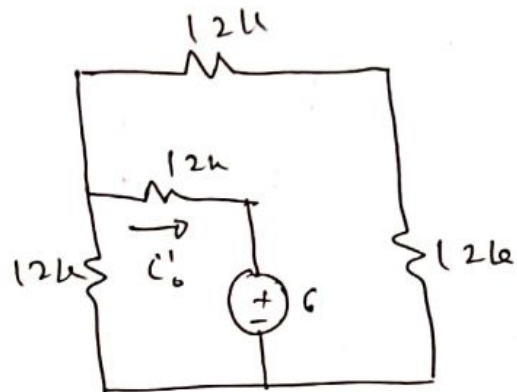
$$i_0'' = \frac{-6}{(8+12)k} = -0.3 \text{ mA}$$



b) $V_{src} = 0$

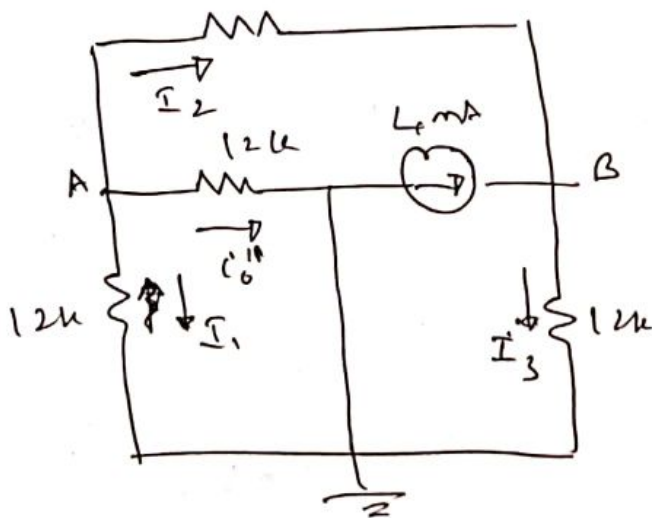

$$i_0''' = 4 \text{ mA}$$

$$i_0 = i_0'' + i_0''' = 4.73 \text{ mA}$$

At A,

$$\frac{V_A}{12k} + \frac{V_A - V_B}{12k} + \frac{V_A}{12k} = 0$$

$$V_A \left[\frac{3}{12k} \right] - \frac{V_B}{12k} = 0 \quad \text{--- (1)}$$

Q B,

$$4 \times 10^{-3} + \frac{V_A - V_B}{12k} = \frac{V_B}{12k}$$


$$-\frac{V_A}{12k} + V_B \left[\frac{2}{12k} \right] = 4 \times 10^{-3} \quad \text{--- (2)}$$

$$V_A = 9.6V, \quad V_B = 28.8V$$


$$\therefore i_0'' = \frac{9.6}{12k} = 0.8mA$$

$$i_0 = i_0' + i_0'' = 0.5mA$$

3) Find i_0 using Superposition

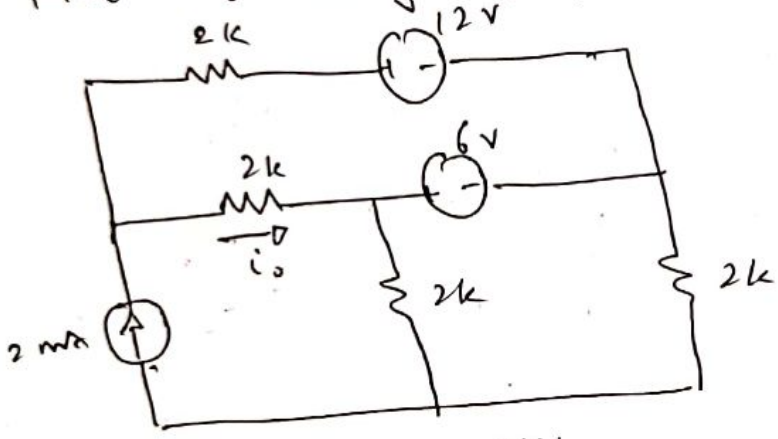


a)

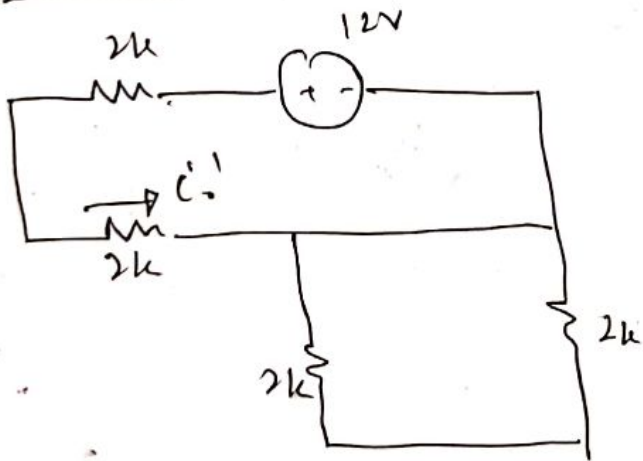


$$i_0' = 3mA$$


b)

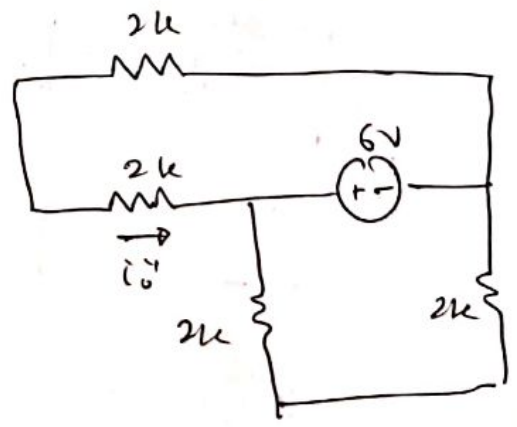


$$i_0'' = -1.5mA$$

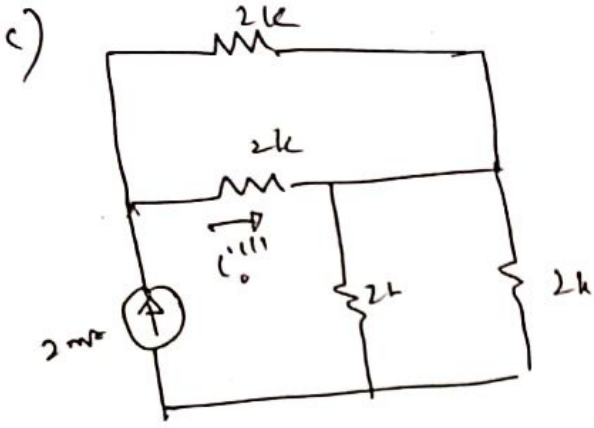

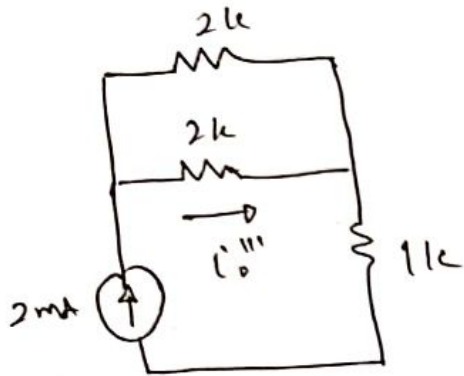
$$i'' = \frac{2\text{mA} \times 2\text{k}}{4\text{k}} = 1\text{mA}$$



$$i_0 = i'' + i''' = 2.5\text{mA}$$

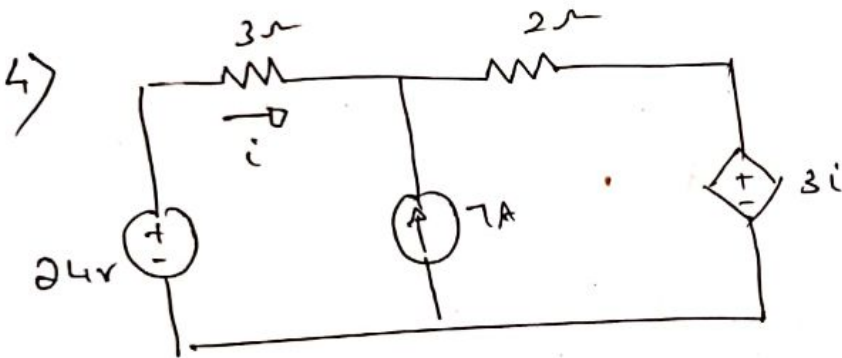


find i

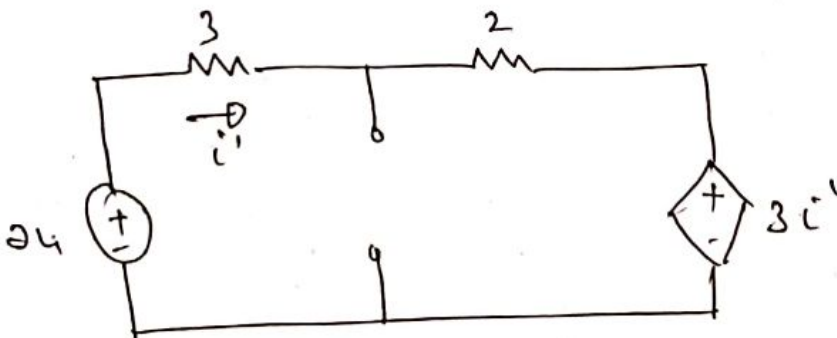

$$i' = \frac{24 - 3i'}{5}$$

$$i' = 3\text{A}$$

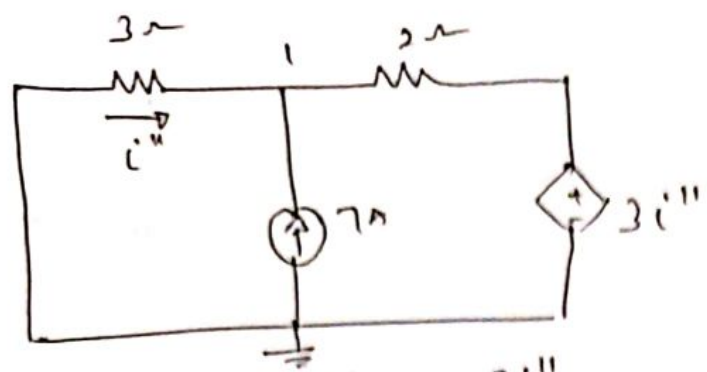

$$i'' + 7 = \frac{V_1 - 3i''}{2}$$

$$i'' = \frac{-V_1}{3}$$


$$i'' + 7 = \frac{-3i'' - 3i''}{2}$$

$$2i'' + 14 = -6i''$$


$$8i'' = -14$$

$$i'' = -7/4$$

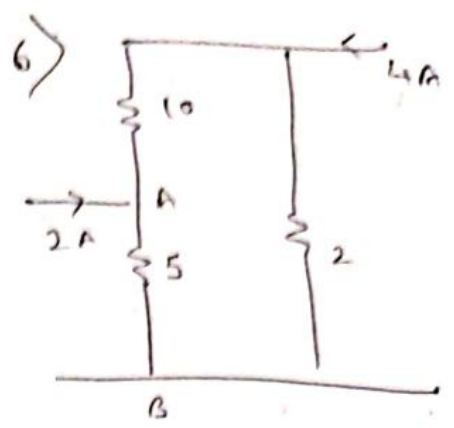
$$\therefore i = i' + i'' = 3 - 7/4 = 5/4 \text{ A}$$



Ans $V_{ab} = 9.6 \text{ V}$

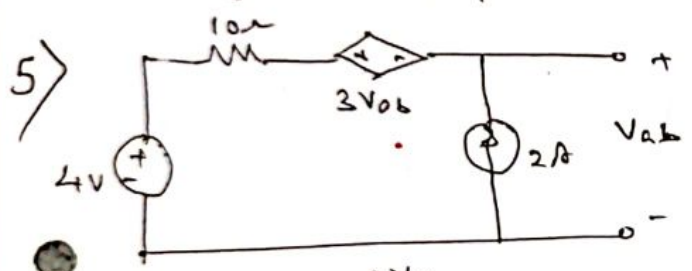


Apply Super position & find V_{ab} .

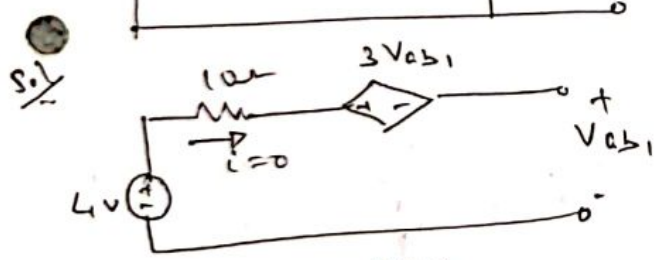

$$4 - 3V_{ab1} - V_{ab1} = 0$$

$$V_{ab1} = 1 \text{ V}$$

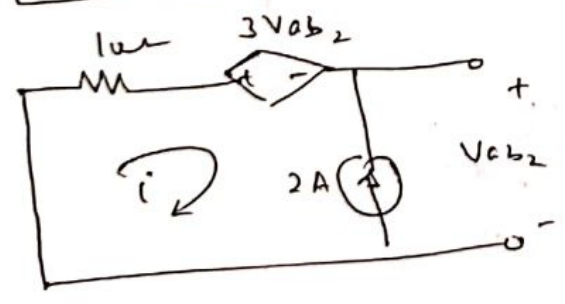

$$+10i - 3V_{ab2} - V_{ab2} = 0$$

$$-20 - 4V_{ab2} = 0$$



$$V_{ab2} = 5 \text{ V}$$

$$\therefore V_{ab} = V_{ab1} + V_{ab2} = 6 \text{ V}$$

Superposition theorem

(37) c

Proof:- Consider linear n/w shown below,

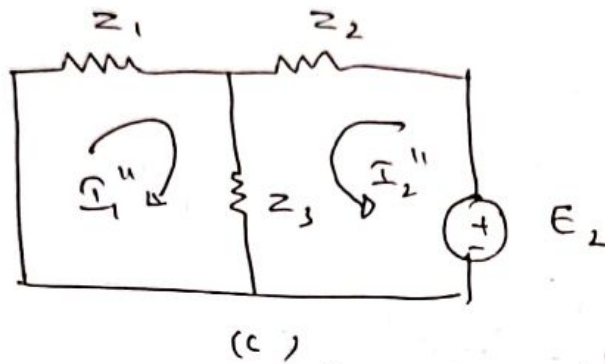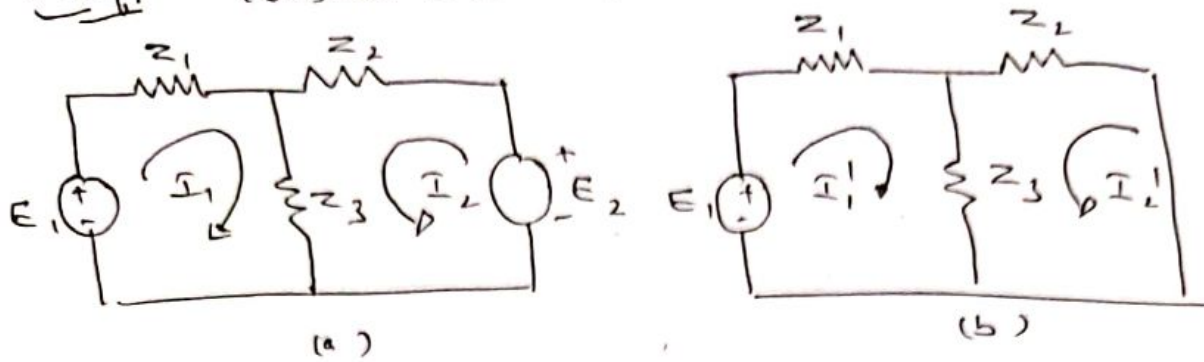

The current flowing in any element is the vector sum of the currents that are separately caused to flow in that element by each energy src.

Consider fig (a)

Apply KVL to loop (1) & (2) we have

$$E_1 = I_1(Z_1 + Z_2) + I_2 Z_3 \quad \text{--- (1)}$$

$$E_2 = I_1(Z_3) + I_2(Z_2 + Z_3) \text{ respectively}$$

Solving above eq's

$$I_1 = \left(\frac{Z_2 + Z_3}{\Sigma Z} \right) E_1 - \left(\frac{Z_3}{\Sigma Z} \right) E_2 \text{ --- (1)}$$

$$I_2 = \left(\frac{-Z_3}{\Sigma Z} \right) E_1 + \left(\frac{Z_1 + Z_3}{\Sigma Z} \right) E_2 \text{ --- (2)}$$

$$\text{Where } \Sigma Z = Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1 //$$

Matching $E_2 = 0$, fig (b)

$$E_1 = \hat{I}_1' (z_1 + z_2) + \hat{I}_2' z_3$$

$$0 = \hat{I}_1' (z_3) + \hat{I}_2' (z_2 + z_3)$$

Solving above (2) equations

$$\hat{I}_1' = \left(\frac{z_2 + z_3}{z_2} \right) E_1 \quad \text{--- (3)}$$

$$\hat{I}_2' = \left(\frac{-z_3}{z_2} \right) E_1 \quad \text{--- (4)}$$

Matching $E_1 = 0$, fig (1)

$$0 = \hat{I}_1'' (z_1 + z_2) + \hat{I}_2'' z_3$$

$$E_2 = \hat{I}_1'' (z_3) + \hat{I}_2'' (z_2 + z_3)$$

Solving above 2 eqs

$$\hat{I}_1'' = \left(\frac{-z_3}{z_2} \right) E_2 \quad \text{--- (5)}$$

$$\hat{I}_2'' = \left(\frac{z_1 + z_2}{z_2} \right) E_2 \quad \text{--- (6)}$$

eq (3) + (5), we have

$$\hat{I}_1' + \hat{I}_1'' = \left(\frac{z_2 + z_3}{z_2} \right) E_1 + \left(\frac{-z_3}{z_2} \right) E_2$$

from eq (1) we have

$$\boxed{\hat{I}_1 = \hat{I}_1' + \hat{I}_1''}$$

Similarly from eq (4), (5) & (6)

$$\boxed{\hat{I}_2 = \hat{I}_2' + \hat{I}_2''}$$


Hence SPT is proved.

Maximum Power Transfer Theorem.

38

General: Max. power will be delivered by a n/w, to an impedance Z_R if the impedance Z_R is the complex conjugate of the impedance of the n/w measured looking back into the terminals of the n/w.

Proof:

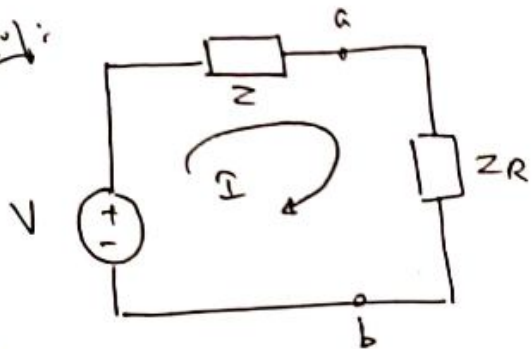

$$I = \frac{V}{Z + Z_R} = \frac{V}{(R_R + R) + j(X_R + X)}$$

But Power delivered to the load is,

$$P = I^2 R_R$$

$$|I| = \frac{V}{\sqrt{(R_R + R)^2 + (X_R + X)^2}} \quad (1)$$

~~$$P = \frac{V^2 R_R}{[(R_R + R)^2 + (X_R + X)^2]}$$~~

$$\therefore P = \frac{V^2 R_R}{(R_R + R)^2 + (X_R + X)^2} \quad (2)$$

For Max. power, $\frac{\partial P}{\partial X_R}$ must be zero

$$\frac{\partial P}{\partial X_R} = 0 - 2(V^2) R_R (X_R + X) \left[[R_R + R]^2 + [X_R + X]^2 \right]^{-2} = 0$$

$$\begin{aligned} X_R + X &= 0 \\ X_R &= -X \end{aligned}$$

i.e. the reactance of the load impedance is of opposite sign to the reactance of the src impedance

Substitute, $X_R = -X$ in eq (1)

$$P = \frac{V^2 R_R}{(R_R + R)^2 + (X_R - X_R)^2}$$

$$P = \frac{V^2 R_R}{(R_R + R)^2}$$

for Max. power.

$$\frac{\partial P}{\partial R_R} = 0$$

$$\frac{\partial P}{\partial R_R} = \frac{V^2 (R_R + R)^2 - 2(E)^2 R_R (R_R + R)}{[R_R + R]^4} = 0$$

$$V^2 [(R_R + R)^2 - 2R_R (R_R + R)] = 0$$

$$V^2 (R_R + R) [R_R + R - 2R_R] = 0$$

$$\therefore R_R = R$$

$\therefore X_R = -X$ & $R_R = R$, the Max. power will be transferred from the Src to load
i.e. for Max. power transfer the load impedance Z_R should be complex conjugate of internal impedance of the Src
i.e. $Z_R = Z^*$



\therefore The Max. power transferred will be

$$P_m = \frac{V^2 R_R}{(R_R + R_R)^2 + (X_R - X_R)^2}$$

$$\therefore P_m = \frac{V^2}{4 R_R}$$

Problems:

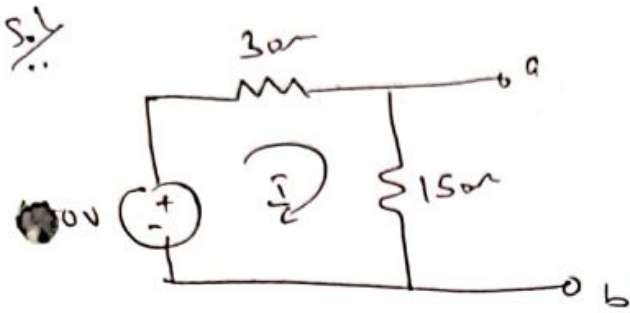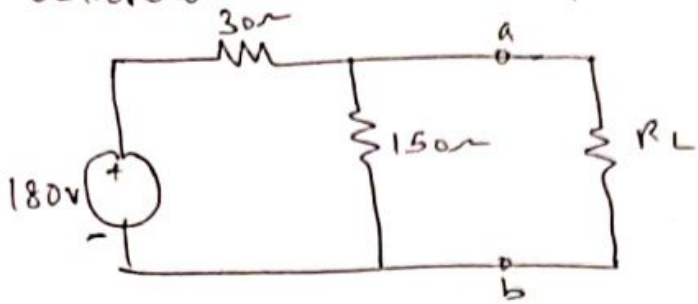1) Find the load R_L that will result in max. power delivered to the load for the ckt. & also find P_{max}




$$R_H = 30\Omega$$

$$V_H = I \times 150 = 150V$$

$$I = 1A$$


Rewriting the ckt,

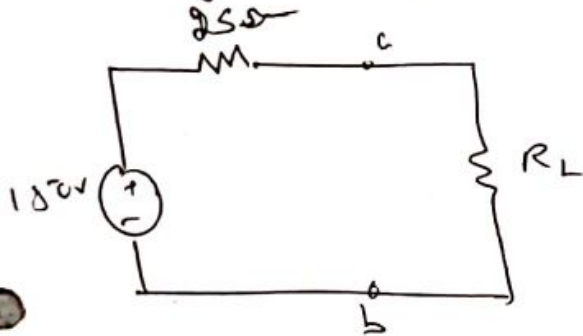

Wkrt


$$\therefore R_L = R_H = 25\Omega$$
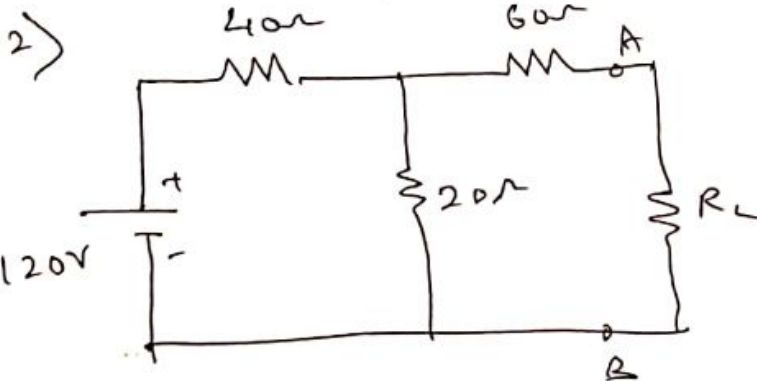
$$\therefore P = \frac{V^2}{4R_L} = 225W$$




$$R_L = 73.33\Omega$$

$$P_{max} = 5.45W$$

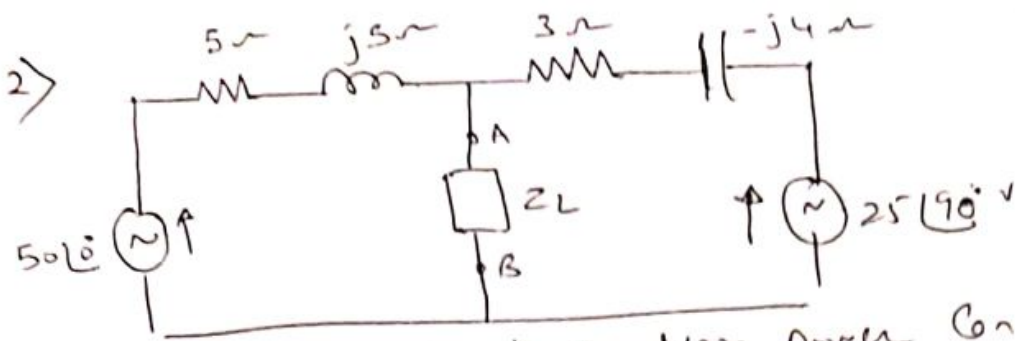

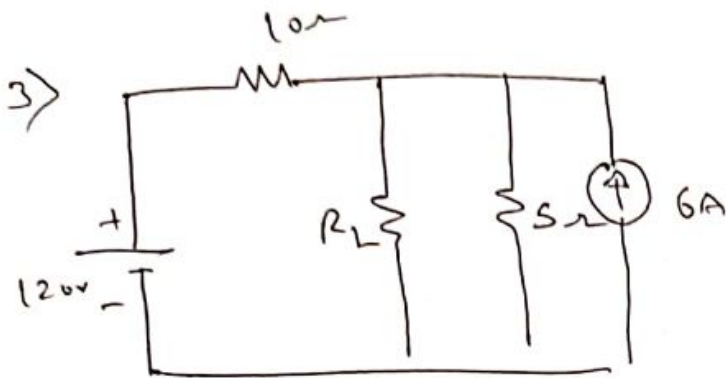Find Z_L such that Max power can be received by it. (Ans: $Z_L = (4.23 + j1.154)\Omega$
 $P = 50.822$)



$R_L = 3.33\Omega$
 $P_{max} = 270W$


MPT:-

In any Linear bilateral n/w, Max. power is transferred from Src to the load when

- Case (1) The Load Resistance is equal to the Src resistance
- Case (2) The Load Resistance is equal to the magnitude of the Src impedance
- Case (3) The load impedance is Complex Conjugate of the Src impedance

Sol

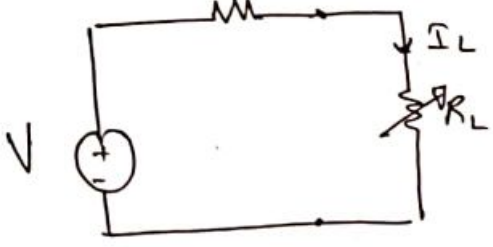Case (1) When Load & Src are purely resistive from the ckt,



$$I_L = \frac{V}{R + R_L} \quad \text{--- (1)}$$

But

$$P = I_L^2 R_L = \frac{V^2 R_L}{(R + R_L)^2}$$


The power transferred is Max, when $\frac{\partial P}{\partial R_L} = 0$

$$\frac{(R + R_L)^2 V^2 - V^2 R_L \cdot 2(R + R_L)}{[R + R_L]^4} = 0$$

$$\therefore P_m = I_L^2 R_L = \frac{V^2}{4R_L}$$

$R_L = R$

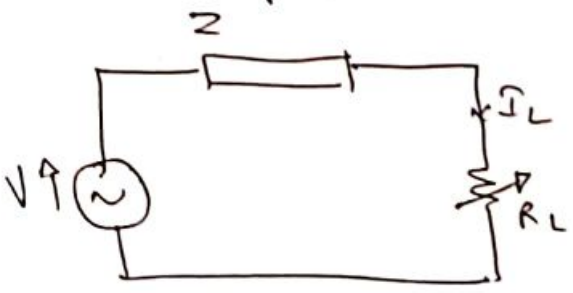Case (2) When load is purely resistive & the Src has impedance



Let Z be the internal impedance of the Src

$$I_L = \frac{V}{(R + R_L) + jX}$$

where $Z = R + jX$

$$|I_L| = \frac{V^2}{\sqrt{(R+R_L)^2 + X^2}}$$

∴ Power is,

$$P = I_L^2 R_L = \left[\frac{V^2}{\sqrt{(R+R_L)^2 + X^2}} \right]^2 R_L$$

$$P = \frac{V^2 R_L}{(R+R_L)^2 + X^2}$$

$$\frac{\partial P}{\partial R_L} = 0$$

$$\therefore R_L^2 = R^2 + X^2$$

$$\text{i.e. } R_L = \sqrt{R^2 + X^2} = |Z|$$


Max. power is transferred when $R_L = |Z|$

$$P_m = I_L^2 R_L \quad \text{when } R_L = |Z|$$

$$P_m =$$

Case (3) when both load & Src have impedance

$$Z = R + jX$$

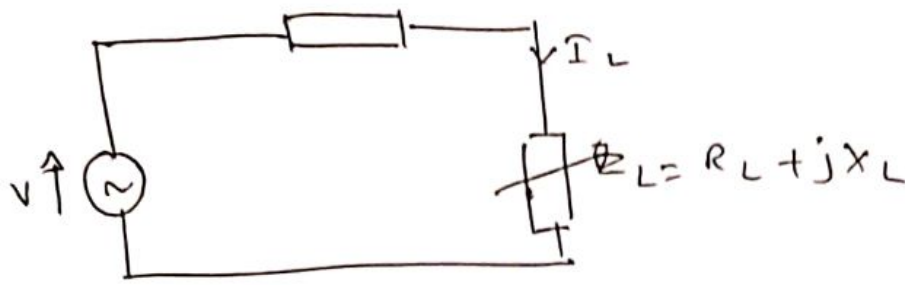

where
$$I_L = \frac{V}{(R + R_L) + j(X + X_L)}$$

$$|I_L| = \frac{V}{\sqrt{(R + R_L)^2 + (X + X_L)^2}}$$

But $P = I_L^2 R_L$

$$P = \frac{V^2 R_L}{(R + R_L)^2 + (X + X_L)^2}$$

∴ power transferred is Max when $X_L = -X_0$ — (1)

$$\therefore P_i = \frac{V^2 R_L}{(R + R_L)^2}$$

Power is Max if $\frac{\partial P_i}{\partial R_L} = 0$

$$R_L = R \quad \text{--- (2)}$$

∴ from (1) & (2) $R_L + jX_L = R + jX$


$$Z_L = Z^*$$

$$P_m = \frac{V^2}{4R_L}$$

Millman's Theorem :-

" If there are a number of voltage sources in the operating conjunction, they may be replaced by a single equivalent voltage source connected in the

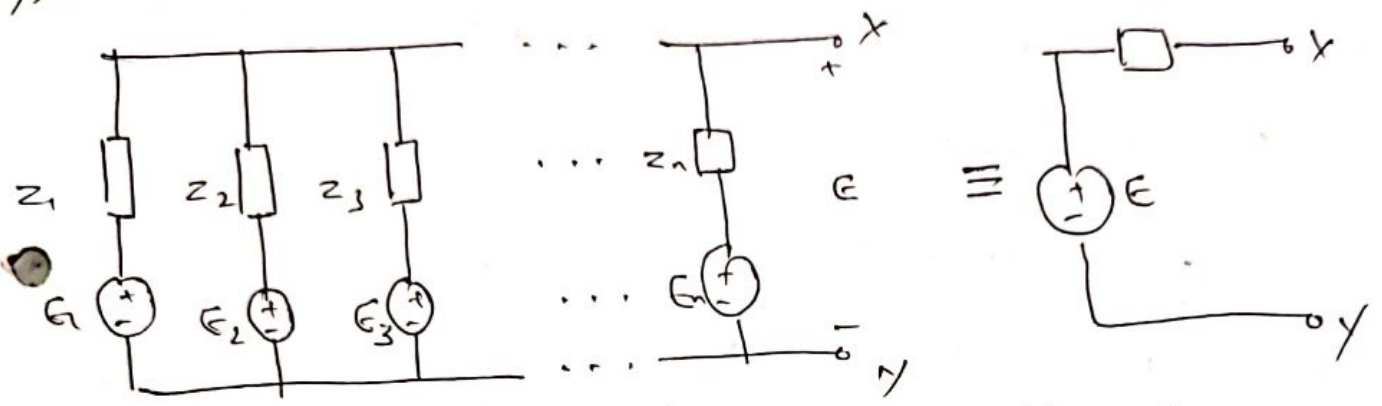~~Proof~~ Let $E_1, E_2, E_3, \dots, E_n$ be the voltage sources with internal impedances $Z_1, Z_2, Z_3, \dots, Z_n$ respectively, b/w x-y connected as shown in the fig:




" It states that if there are n voltage source (b/w x & y) can be replaced by a single equivalent source with voltage E' in series with an equivalent impedance Z' as given by,

$$E' = \frac{E_1 Y_1 + E_2 Y_2 + \dots + E_n Y_n}{Y_1 + Y_2 + \dots + Y_n}$$

$$\& Z' = \frac{1}{Y} = \frac{1}{Y_1 + Y_2 + \dots + Y_n}$$

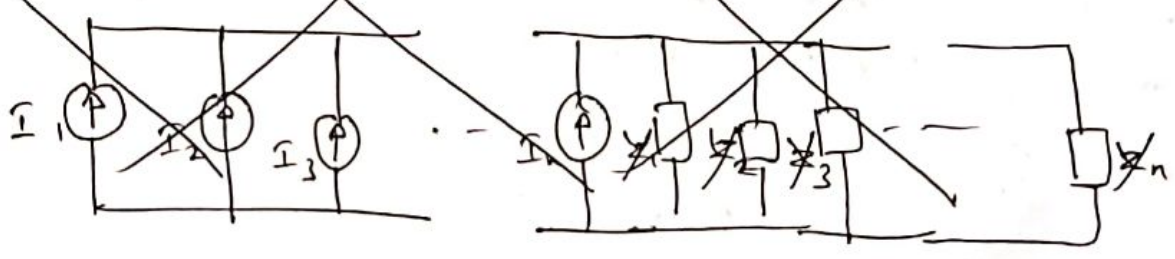~~Proof~~ V. Sources can be replaced by their equivalent I. Sources



Proof: Apply nodal analysis at x

$$\frac{E_1 - E}{z_1} + \frac{E_2 - E}{z_2} + \dots + \frac{E_n - E}{z_n} = 0$$

$$\left[\frac{E_1}{z_1} + \frac{E_2}{z_2} + \dots + \frac{E_n}{z_n} \right] = E \left[\frac{1}{z_1} + \frac{1}{z_2} + \dots + \frac{1}{z_n} \right]$$

$$E_1 Y_1 + E_2 Y_2 + \dots + E_n Y_n = E \left[\frac{1}{z} \right]$$

where $z =$ Equivalent internal impedance

$$\therefore E_1 Y_1 + E_2 Y_2 + \dots + E_n Y_n = E Y$$

$$E = \frac{E_1 Y_1 + E_2 Y_2 + \dots + E_n Y_n}{Y}$$

$$\text{where } Y = Y_1 + Y_2 + \dots + Y_n$$

$$\therefore z = \frac{1}{Y} = \frac{1}{Y_1 + Y_2 + \dots + Y_n}$$


[OR]

Millman's theorem states that if n number of generators having emfs E_1, E_2, \dots, E_n & internal impedances z_1, z_2, \dots, z_n respectively are connected in parallel, then the emf & impedances can be combined to give a single equivalent emf of E with an internal impedance of equivalent value z .

$$\text{where } E = \frac{E_1 Y_1 + E_2 Y_2 + \dots + E_n Y_n}{Y_1 + Y_2 + \dots + Y_n}$$

$$\therefore z = \frac{1}{Y_1 + Y_2 + \dots + Y_n}$$

Problems:

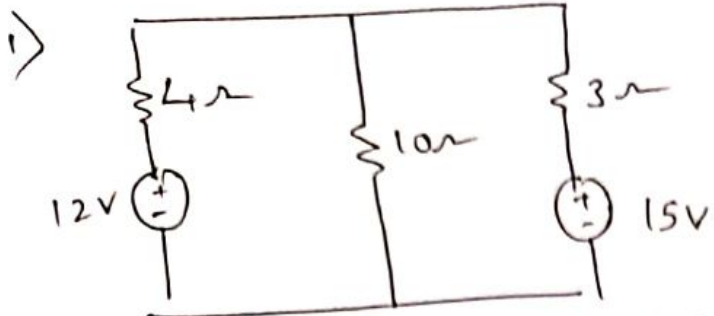


find $I_{10\Omega}$ using Millman's theorem.

$Z_1 = 4\Omega, Z_2 = 3\Omega$ $E_1 = 12V$, & $E_2 = 15V$

$$E = \frac{E_1 Y_1 + E_2 Y_2}{Y_1 + Y_2} = \frac{12 \left(\frac{1}{4}\right) + 15 \left(\frac{1}{3}\right)}{\frac{1}{4} + \frac{1}{3}} = \frac{96}{7} V$$

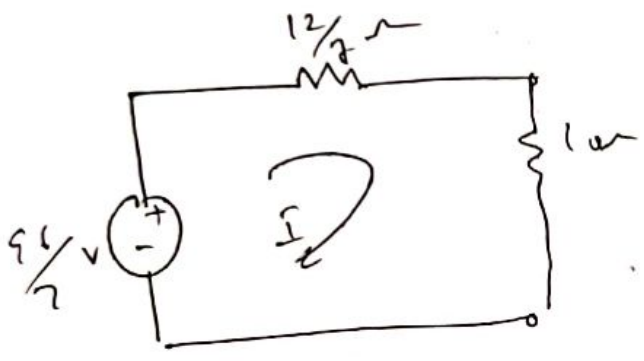
$$Z = \frac{1}{Y_1 + Y_2} = \frac{1}{\frac{1}{4} + \frac{1}{3}} = \frac{12}{7} \Omega$$



$$\therefore I_{10\Omega} = \frac{96/7}{12/7 + 10} = 1.17 A$$


Find $I_{10\Omega}$

$E_1 = 22V, E_2 = 48V$
 $E_3 = -12V$

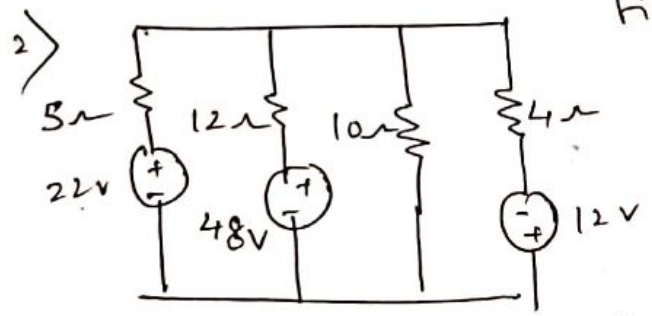


$$E = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3}{Y_1 + Y_2 + Y_3} = \frac{22 \left(\frac{1}{5}\right) + 48 \left(\frac{1}{12}\right) + (-12) \left(\frac{1}{4}\right)}{\frac{1}{5} + \frac{1}{12} + \frac{1}{4}} = 10.13 V$$
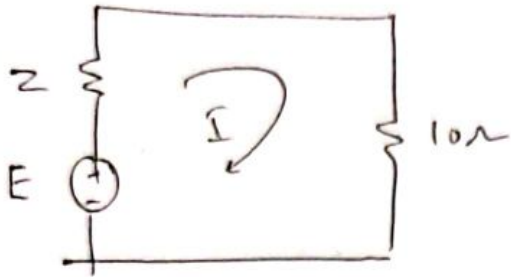
$$Z = \frac{1}{Y_1 + Y_2 + Y_3} = 1.88 \Omega$$




$$I = \frac{E}{Z + 10} = 0.853 \text{ A}$$

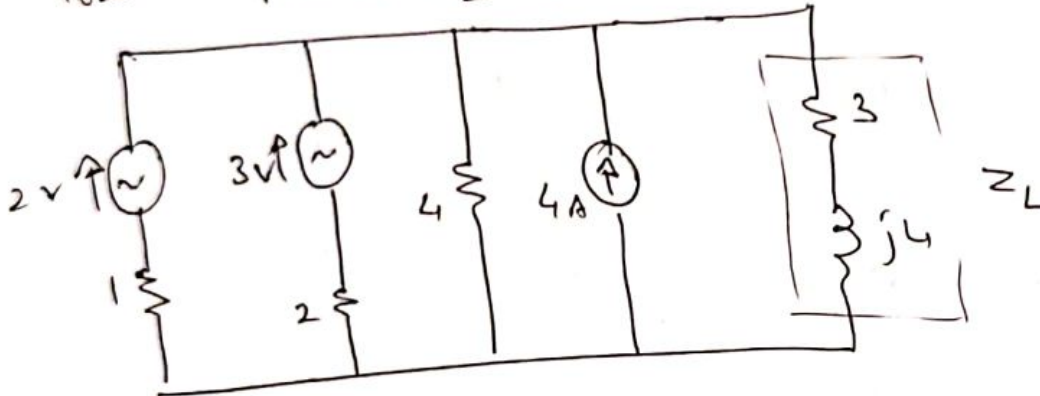3) Using Millman's Theorem, find the current in the load impedance Z_L in the circuit




Sol

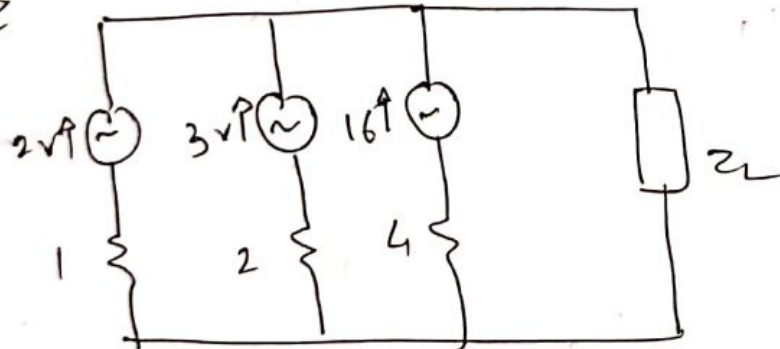

$$E = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3}{Y_1 + Y_2 + Y_3} = \frac{30}{7} \text{ V}$$

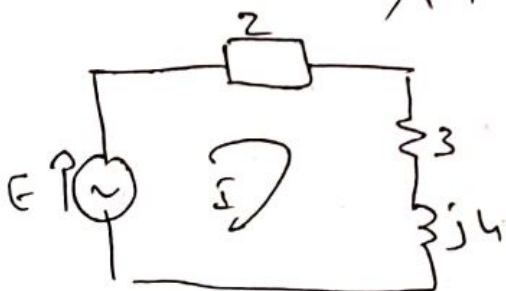
$$Z = \frac{1}{Y_1 + Y_2 + Y_3} = \frac{4}{7} \Omega$$



$$I = \frac{30/7}{\frac{4}{7} + (3 + j4)} = 0.8 \angle -48.25^\circ \text{ A}$$

4) Find I_{2r} using Millman's theorem


(44)

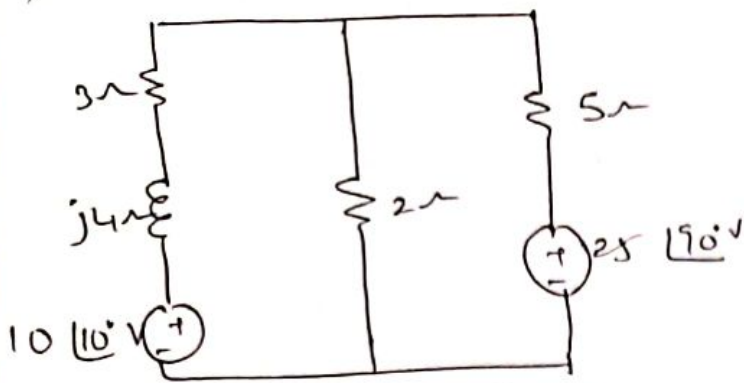

$$E = \frac{E_1 Y_1 + E_2 Y_2}{Y_1 + Y_2} = \frac{10 \angle 0^\circ \left(\frac{1}{3 + j4} \right) + 25 \angle 90^\circ \left(\frac{1}{5} \right)}{\frac{1}{3 + j4} + \frac{1}{5}}$$


$$E = 10.06 \angle 97.12^\circ \text{ V}$$
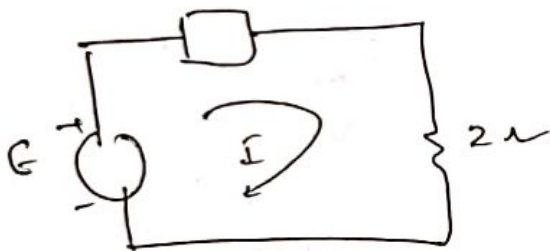
$$I = \frac{E}{Z} = \frac{10.06 \angle 97.12^\circ}{\frac{1}{3 + j4} + \frac{1}{5}} = 2.8 \angle 26.56^\circ \text{ A}$$



$$I = 2.15 \angle 81.63^\circ \text{ A}$$


5)

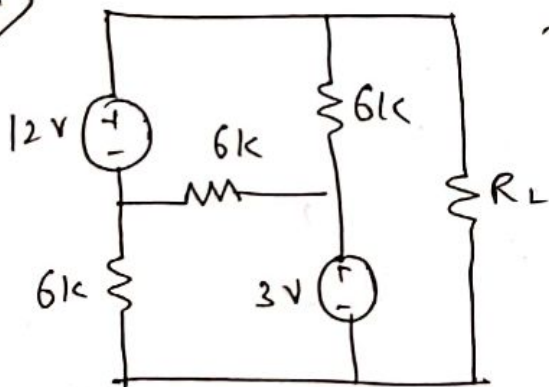


find R_L for Max. power transfer & also find P_{max} .

Ans. $R_L = 2k\Omega$


$P_m = 12.5 \text{ mW}$

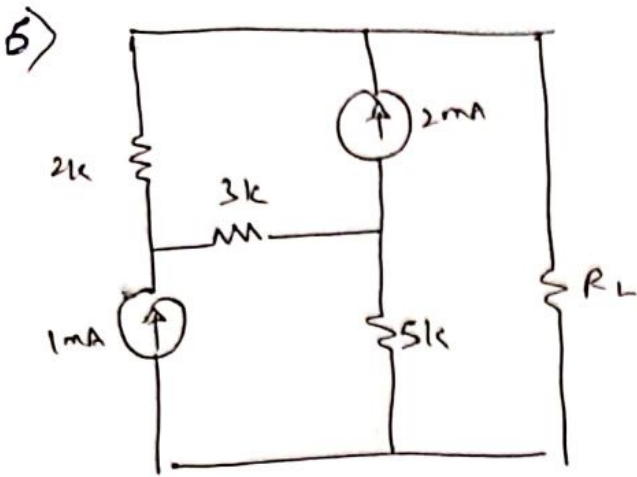

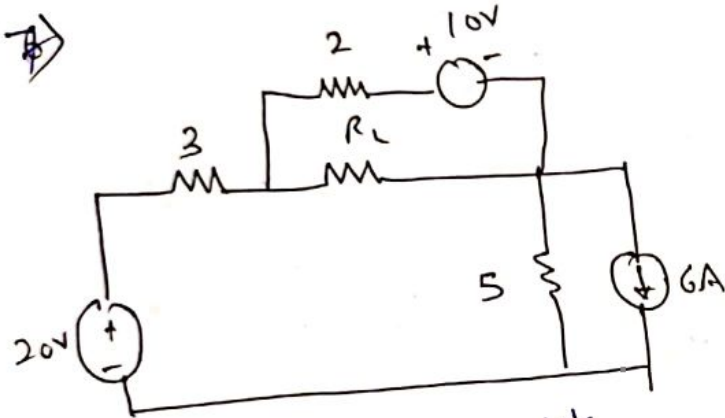
Max. Transfer Theorem
 $R_L = ?$ & $P_{max} = ?$
 $R_L = 10k\Omega$
 $P_{max} = 8.1mW$



$R_L = 1.6\Omega$
 $P_{max} = 625mW$

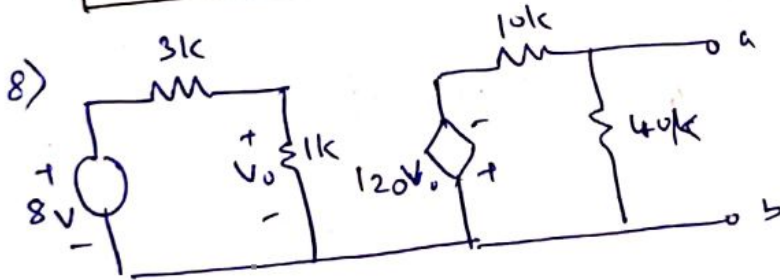

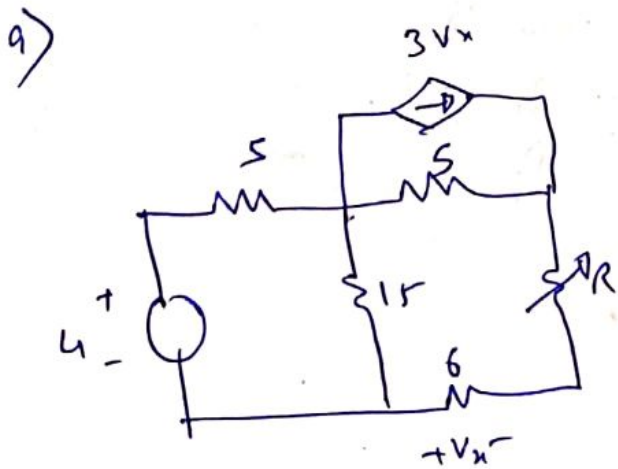
$P_{max} = 1.15W$
 $V_{th} = -19.2V$
 $I_{sc} = -24mA$
 $R_{th} = 8k\Omega$



$R = ?$
 $P_{max} = ?$

20-9-19

MODULE - 3

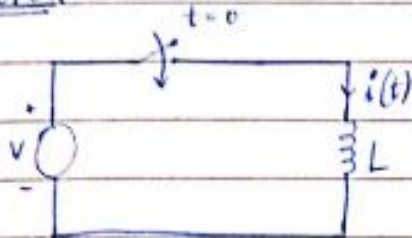INITIAL CONDITIONS:• INDUCTOR:

- The switch is closed at $t=0$.
- At $t=0^-$, corresponds to the instant when the switch is just open. [In the circuit shown above].
- At $t=0^+$ is an instant when the switch is just closed.

The expression for current through inductor is:

$$i = \frac{1}{L} \int_{-\infty}^t v dz$$

$$i = \frac{1}{L} \int_{-\infty}^0 v dz + \frac{1}{L} \int_0^t v dz$$

$$i(t) = i(0^-) + \frac{1}{L} \int_0^t v dz$$


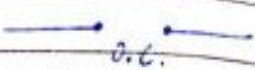
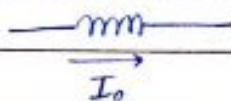

At $t=0^+$,

$$\Rightarrow i(0^+) = i(0^-) + \frac{1}{L} \int_0^{0^+} v dz \quad [\text{Here } t=0^+]$$

$$\Rightarrow \boxed{i(0^+) = i(0^-)}$$

- This equation means that the current in an inductor does not change instantaneously.
- But voltage may vary.

• INITIAL CONDITION EQUIVALENT OF AN INDUCTOR:

	$i(0^-)$	NOTATION	EQUIVALENT @ $t=0^+$
1)	0 [$i(0^+) = 0$]		 s.c.
2)	I_0 $i(0^+) = I_0$		 I_0





• FINAL OR STEADY STATE: [At $t = \infty$]

The final condition equation of an inductor is derived from

$$V = L \frac{di}{dt}$$

* $V = 0$; $i = \text{constant} \Rightarrow$ no resistance, thus, Short circuit.

• FINAL CONDITION EQUIVALENT:

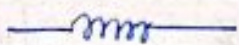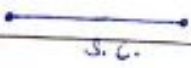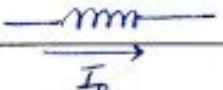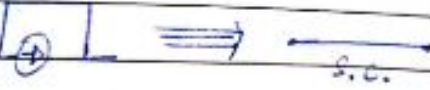	NOTATION	EQUIVALENT @ $t = \infty$
1)	 $d_i \neq 0$	 s.c.
2)	 I_0	 I_0


• CAPACITOR:

Expression for voltage across capacitor is:

$$V = \frac{1}{C} \int_{-\infty}^t i dz$$

$$V(t) = \frac{1}{C} \int_{-\infty}^0 i dz + \frac{1}{C} \int_0^t i dz$$
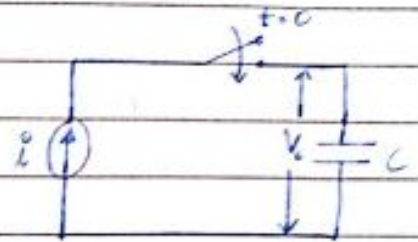
$$V(0^+) = V(0^-) + \frac{1}{C} \int_0^{0^+} i dz$$



[Here $t=0^+$]

$$\therefore \boxed{V(0^+) = V(0^-)}$$

- Thus, the voltage across the capacitor does not change instantaneously.
- But, current may vary.

• INITIAL CONDITION EQUIVALENT:

	$V(0^-)$	NOTATION	EQUIVALENT (a) $t=0^+$
1)	0 [$V(0^+) = 0$]		
2)	V [$V(0^+) = V$]		

→ The final condition equivalent of the capacitor is derived from $i = C \frac{dV}{dt}$

→ At steady state ($t=\infty$), $\frac{dV}{dt} = 0 \Rightarrow i=0$.

4

• FINAL CONDITION EQUIVALENT:

	NOTATION	EQUIVALENT @ $t = \infty$
1)		
2)		

• RESISTOR:

For a resistor, voltage is given by, $V = iR$.
From this, we can observe that the current will change instantaneously if the voltage changes and vice versa.

*** TABLE:

Element:	NOTATION	INITIAL CONDITION $t = 0^+$	FINAL CONDITION (Steady State), $t = \infty$
INDUCTOR			
	\hookrightarrow already in steady state		
CAPACITOR			
	\hookrightarrow already in steady state		


5

• PROCEDURE FOR EVALUATING INITIAL CONDITIONS:

- First, solve for initial values of currents and voltages, then, solve for derivatives.
- For finding initial values of currents and voltages, an equivalent network of the original network at $t = 0^+$ is constructed according to the following rules:
 - ① Replace all inductors with o.c. @ current sources having value of current, flowing at $t = 0^+$.
 - ② Replace all capacitors with s.c. @ Voltage source of value $V_0 = \frac{Q_0}{C}$, if there is an initial charge.
 - ③ All resistors are left in the network without any changes.

PROBLEMS:

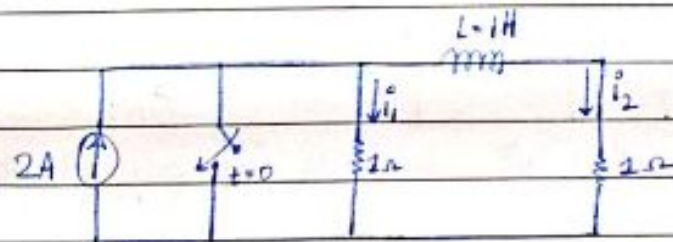1) For the given circuit diagram, find $i_1(0^+)$ and $i_2(0^+)$.




S: The given circuit for $t \leq 0$ is already in steady state. Therefore, the circuit is in steady state with the switch open at $t = 0^-$. Thus, inductor is represented by short circuit.

2-10-19

6

→ Equivalent circuit at $t=0^-$ is:

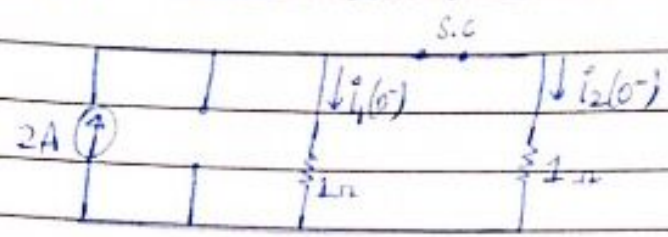


→ $i_2(0^-) = \frac{2 \times 1}{1+1} \Rightarrow i_2(0^-) = 1A$

→ $i_1(0^-) = \frac{2 \times 1}{1+1} \Rightarrow i_1(0^-) = 1A$

→ At $t=0^+$, the current through an inductor doesn't change instantaneously. Thus, $i_2(0^+) = i_2(0^-) = 1A$.

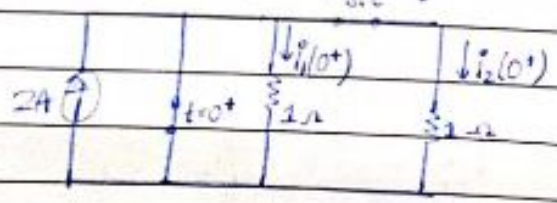
→ At $t=0^+$, the switch is just closed, thus, there is no current flowing through the resistor [\because it chooses least resistant path \rightarrow S.C.]. Thus, $i_1(0^+) = 0$, i.e., current in the resistor changes rapidly from 1A \rightarrow 0A.



Here, $i_2(t)$ changes as it is current through resistor only.

$i_1(t)$ doesn't change as it is current through inductor.

** NOTE:

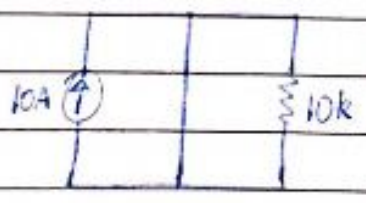


- Current through 10k $= 0$
- Current through S.C. is maximum, as current chooses the least resistant path.


- 1) → At $t=0^-$, switch is closed
- 2) → At $t=0^-$, switch is open.

7

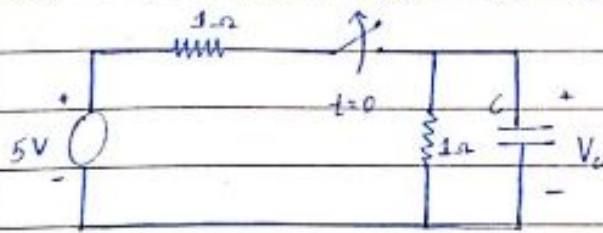2) Find $V_c(0^+)$ such that the switch is closed for a long time.




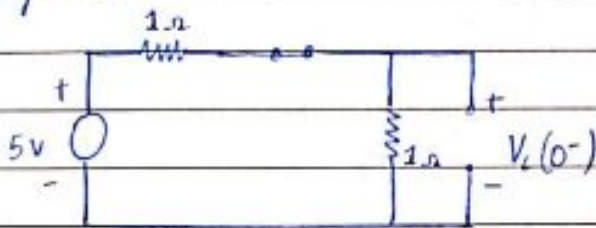S: At $t=0^-$, switch is closed. Thus, the capacitor can be represented by O.C.




$$V_c(0^-) = \frac{5 \times 1}{1+1} \Rightarrow V_c(0^-) = 2.5 \text{ V}$$

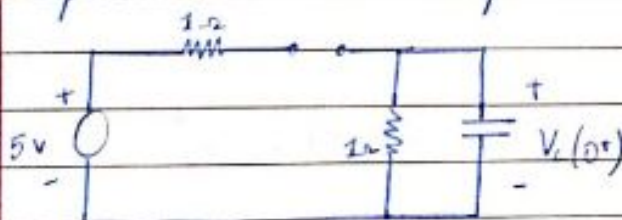→ At $t=0^+$, the switch is open but voltage through the capacitor does not change instantaneously. $\Rightarrow V_c(0^+) = V_c(0^-) = 2.5 \text{ V}$




Here, the switch is just open. The voltage $V_c(0^+) = 2.5 \text{ V}$

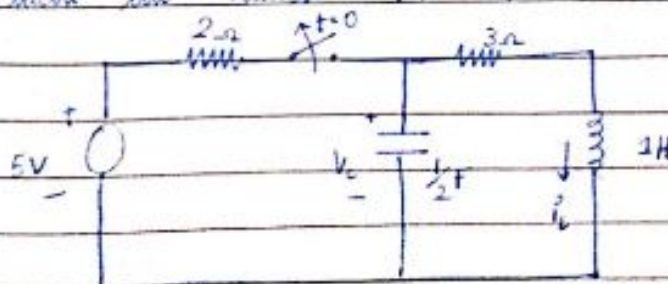3) Find $i_c(0^+)$ and $V_c(0^+)$. Given, the circuit is in steady state with the switch in closed condition.



8

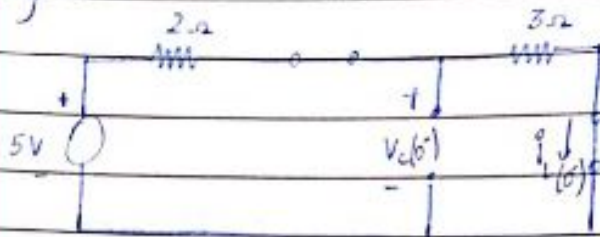S: At $t=0^-$, the switch is closed [Steady State]. Thus, the capacitor is represented by o.c and Inductor is represented by s.c.



Applying KVL, $5 - 2i_1 - 3i_1 = 0$
 $5 = 5i_1$

$i_L = [i_1 = 1A] \Rightarrow i_{\text{inductor}}$

The current does not change instantaneously, i.e., $i_L(0^-) = i_L(0^+)$
 $\therefore [i_L(0^+) = 1A]$

\rightarrow At $t=0^+$, the switch is open.

$i_L(3\Omega) = \frac{1 \times 2}{2+3} = \frac{2}{5}$


$[i_L(0^+) = \frac{2A}{5}]$

$[i_L(0^+) = 1A]$

$V_c(0^+) = \frac{5 \times 3}{2+3} = \frac{5 \times 3}{5} \Rightarrow [V_c(0^+) = 3V]$


\rightarrow At $t=0^+$, the switch is open; the voltage does not change instantaneously. Thus, $V_c(0^+) = V_c(0^-)$.

$\therefore [V_c(0^+) = 3V]$

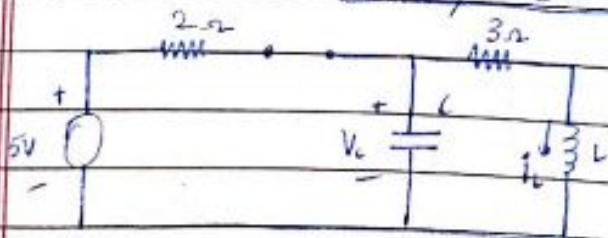


9

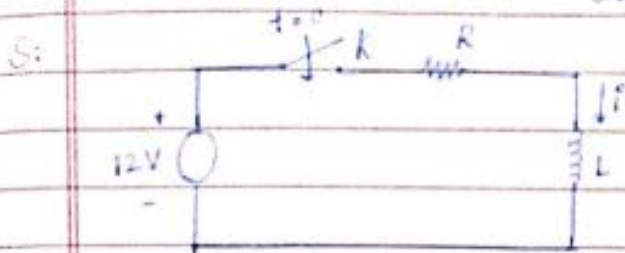4) Switch, K is closed at $t=0$, with zero current in the inductor. Find i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t=0^+$. Given, $R=8\Omega$ & $L=0.2H$.



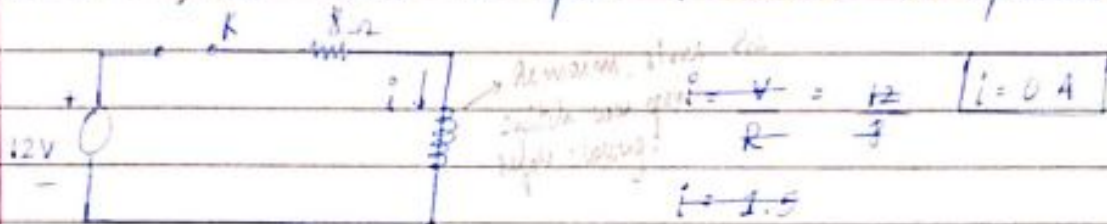At $t=0^-$, the switch is open. Inductor is represented by a short circuit.



The current does not change instantaneously. Thus, $i(0^+) = i(0^-)$
 $\therefore [i(0^+) = 0]$

→ At $t=0^+$, switch is closed. The current through inductance will not change instantaneously. Thus, $i(0^+) = i(0^-) = 0$.


NOTE: $\rightarrow V_L = \frac{1}{C} \int i(z) dz$

$$\rightarrow V_L = L \frac{di}{dt}$$

≈ We can't take $-L \frac{di}{dt}$ coz it is pure inductance.

$t > 0$

→ At $t=0^+$, switch is closed.

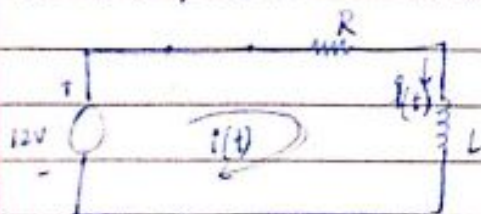

Applying KVL,

$$12 - 8i(t) - L \frac{di(t)}{dt} = 0$$

$$8i(t) + 0.2 \frac{di(t)}{dt} = 12 \quad \text{--- (1)}$$

(10)

$$\text{At } t=0^+, \quad 8i(0^+) + 0.2 \frac{di(0^+)}{dt} = 12$$

$$\frac{di(0^+)}{dt} = \frac{12}{0.2}$$

$$\boxed{\frac{di(0^+)}{dt} = 60 \text{ A/s}} \quad \text{Amperes/second}$$

Differentiating eq (2) w.r.t t .

$$+ 8 \frac{di(t)}{dt} + 0.2 \frac{d^2i(t)}{dt^2} = 12$$

$$\boxed{8 \frac{di(t)}{dt} + 0.2 \frac{d^2i(t)}{dt^2} = 0}$$

$$\text{At } t=0^+, \quad 8 \frac{di(0^+)}{dt} + 0.2 \frac{d^2i(0^+)}{dt^2} = 0$$


$$8(60) + 0.2 \frac{d^2i(0^+)}{dt^2} = 0$$

$$\therefore \frac{d^2i(0^+)}{dt^2} = \frac{-480}{0.2}$$

$$\boxed{\frac{d^2i(0^+)}{dt^2} = -2400 \text{ A/s}^2}$$


5) Switch is closed at $t=0$. Find i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t=0^+$.

S:

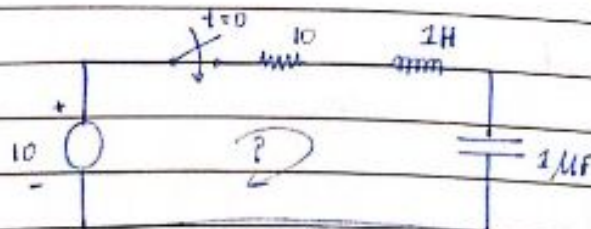

(11)

→ At $t=0^-$, the switch is open.

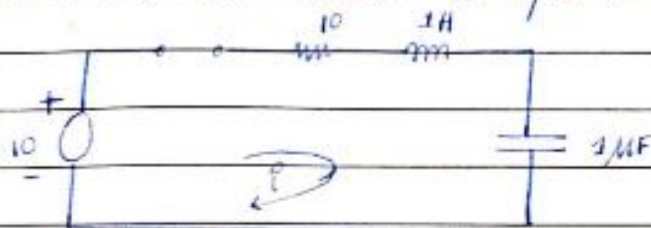


$$V_c(0^-) = 0 = V_c(0^+)$$

$$i(0^-) = 0$$

At $t=0$, The current doesn't change instantaneously. Thus, $i(0^-) = i(0^+) = 0$.

→ At $t=0^+$, the switch is closed.

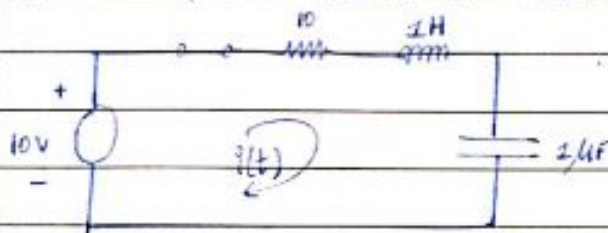

Applying KVL,

$$10 - 10i(t) - 1 \frac{di(t)}{dt} - \frac{1}{2\mu F} \int i(t) dt = 0 \quad \text{--- (1)}$$

$$\Rightarrow 10i(t) + \frac{di(t)}{dt} + V_c(t) = 10 \quad \text{--- (2)}$$

→ At $t=0^+$, $10i(0^+) + \frac{di(0^+)}{dt} + V_c(0^+) = 10$

$$\therefore \frac{di(0^+)}{dt} = 10 \text{ A/s}$$

Differentiate eq. (2) w.r.t 't'.

$$10 \frac{di(t)}{dt} + \frac{d^2i(t)}{dt^2} + \frac{1}{2\mu F} i(t) = 0$$


$$10 \frac{di}{dt} + \frac{d^2i}{dt^2} + \frac{1}{2\mu F} i = 0$$

→ At $t=0^+$, $10(10) + \frac{d^2i(0^+)}{dt^2} + \frac{1}{2\mu F} (0) = 0$


$$\frac{d^2i(0^+)}{dt^2} = -100 \text{ A/s}^2$$

(12)

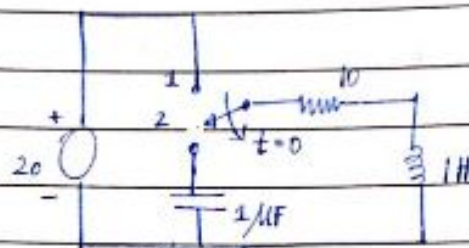- 6) 'K' is changed from position 1 to position 2 at $t=0$, steady state condition has been reached at position 1. Calculate i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t=0^+$.




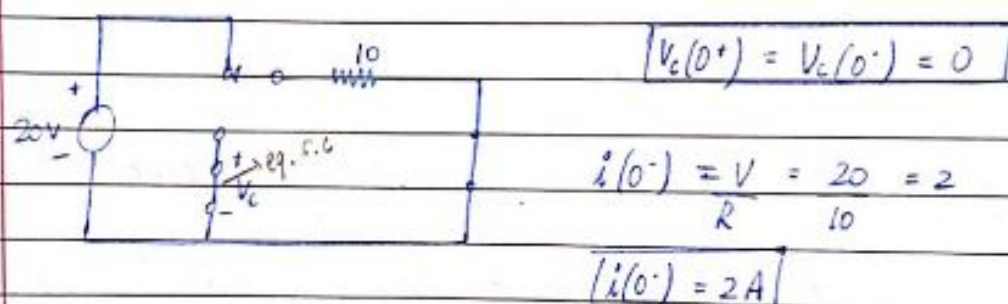- S: At $t=0^-$, the switch is at position (1). Capacitor is S.C. Inductor is S.C.



At $t=0^+$, the voltage and current do not change instantaneously. Thus, $i(0^+) = i(0^-) = 2A$; $V_c(0^+) = V_c(0^-) = 0$.

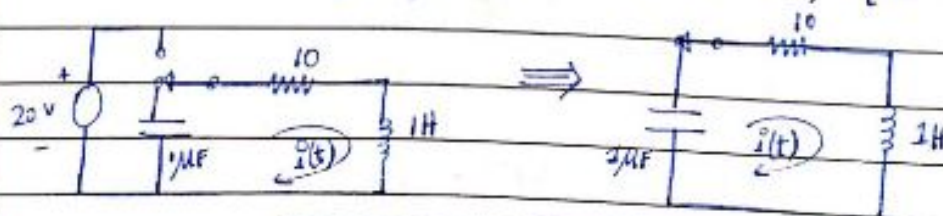→ When switch changes from position (1) to (2); [At $t=0$]



Apply KVL,

$$\frac{-1}{3\mu F} \int i(t) dt - 10i(t) - 1 \frac{di(t)}{dt} = 0 \quad \text{--- (1)}$$

$$\frac{1}{\mu F} \int i(t) dt + 10i(t) + \frac{di(t)}{dt} = 0$$

(13)

classmate

Date _____

Page _____

At $t=0^+$,

$$V_L(0^+) + V_i(0^+) + \frac{di(0^+)}{dt} = 0$$

$$-10(2) = \frac{di(0^+)}{dt}$$

$$\therefore \boxed{\frac{di(0^+)}{dt} = -20 \text{ A/s}}$$

Differentiate eq. (1) w.r.t 't'.

$$\frac{1}{\mu F} \frac{d^2i(t)}{dt^2} + 10 \frac{di(t)}{dt} + \frac{d^2i(t)}{dt^2} = 0$$

$$\frac{1}{\mu F} \frac{d^2i(t)}{dt^2} + 10 \frac{di(t)}{dt} + \frac{d^2i(t)}{dt^2} = 0$$

$$\text{At } t=0^+, \quad V_L(0^+) + 10 \frac{di(0^+)}{dt} + \frac{d^2i(0^+)}{dt^2} = 0 + \frac{1}{\mu F} i(0^+) = 0$$

$$10(-20) + \frac{d^2i(0^+)}{dt^2} + 2 \times 10^6 = 0$$


$$\frac{d^2i(0^+)}{dt^2} = 200 - 2 \times 10^6$$

$$\frac{d^2i(0^+)}{dt^2} = -1.9998 \times 10^6 \approx -2 \times 10^6$$


$$\boxed{\frac{d^2i(0^+)}{dt^2} \approx -2 \text{ MA/s}^2}$$

14

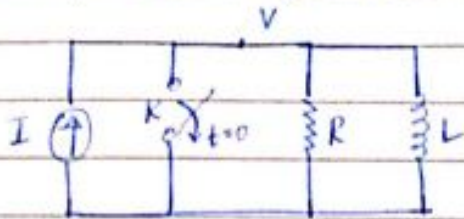10) 'K' is opened at $t=0$. At $t=0^+$, solve for V , $\frac{dV}{dt}$, $\frac{d^2V}{dt^2}$ if $I=2A$, $R=200\Omega$, $L=1H$. Further, switch is open at $t=0^+$ & closed at $t=0^-$.



S: At $t=0^-$,

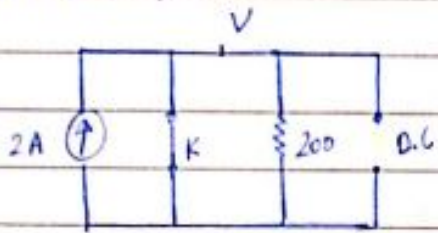

∴ no current flows through S.C. Hence i through L is 0 ⇒ D.C.


→ Voltage through 'K' and current through 'L' do not change instantaneously.

Thus $V(0^-) = 0 \neq V(0^+)$
 $i_L(0^-) = i_L(0^+) = 0$ [∵ D.C.]

At $t=0^+$ switch is open but 'L' is D.C. only.

∴ $V = I \times R = 2 \times 200$

At $t=0^+$

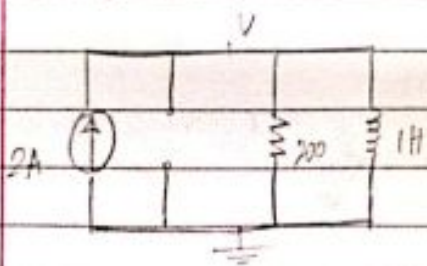

KVL at (V): $0 = -2 + V + \frac{1}{200} \frac{dV}{dt}$

$V(0^+) = 400V$

$\frac{V(t)}{200} - 2 + \frac{dV(t)}{dt} = 0$

At $t=0^+$ $\frac{V(0^+)}{200} - 2 + \frac{dV(0^+)}{dt} = 0$

$V(0^+) = 2 \times 200$

$V(0^+) = 400V$

(15)

Diff. eq. ② w.r.t t

$$-2^{20} + \frac{1}{200} \frac{dV(t)}{dt} + \frac{1}{1} V(t) = 0 \quad \rightarrow \text{②}$$

At $t=0^+$,

$$\frac{1}{200} \frac{dV(0^+)}{dt} + V(0^+) = 0$$

$$\frac{dV(0^+)}{dt} = -400 \times 200$$

$$\frac{dV(0^+)}{dt} = -80000 \text{ V/s}$$

Diff. eq. ② w.r.t t'

$$\frac{1}{200} \frac{d^2V(t)}{dt^2} + \frac{dV(t)}{dt} = 0$$


$$\text{At } t=0^+ \quad \frac{1}{200} \frac{d^2V(0^+)}{dt^2} + \frac{dV(0^+)}{dt} = 0$$

$$\frac{d^2V(0^+)}{dt^2} = -(-80000) \times 200$$


$$\frac{d^2V(0^+)}{dt^2} = 16 \text{ MV/s}^2$$

(17)

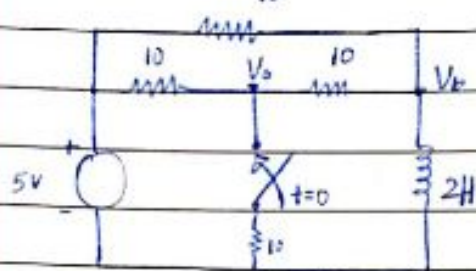12) A steady state is reached with switch 'K' open. At $t=0$, switch is closed. Find $V_a(0^+)$ & $V_b(0^+)$.



S: At $t=0^-$

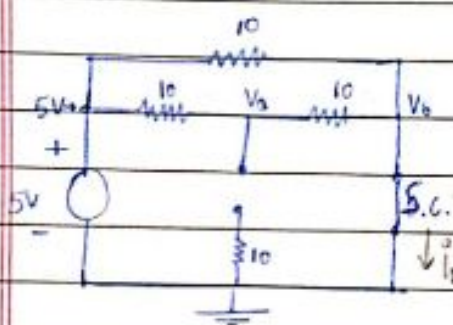


The other loop current can flow through the inductor. So, it's been in a steady state.
 $\downarrow i_L(t) \Rightarrow$ S.C

Apply KCL at V_a :

$$\frac{V_a - 5}{10} + \frac{V_a - V_b}{10} = 0$$
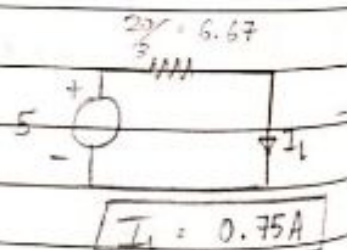
$$\boxed{\frac{V_a [1+1]}{10} - \frac{V_b [1]}{10} = \frac{5}{10}} \rightarrow (1)$$



KCL @ V_b :

$$\frac{V_b - V_a}{10} + \frac{V_b - 5}{10} = 0 + 0.75 = 0$$

$$\boxed{-\frac{V_a [1]}{10} + \frac{V_b [1+1]}{10} = \frac{2}{1.25}} \rightarrow (2)$$


$$\boxed{V_a(0^-) = 7.5 \text{ V}}$$

$$\boxed{V_b(0^-) = 10 \text{ V}}$$

(18)

At $t=0$,

At $t=0^+$

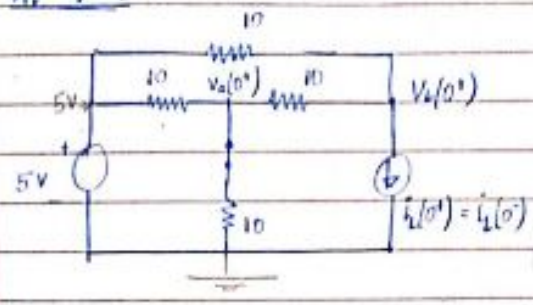

before inductor



flow through the
a steady state.

KCL @ V_a

$$\frac{V_a - 5}{10} + \frac{V_a - V_b}{10} + \frac{V_a}{10} = 0$$


$$\boxed{\frac{V_a}{10} \left[1 + 1 + 1 \right] - \frac{V_b}{10} \left[1 \right] = \frac{1}{2}} \rightarrow (1)$$

KCL @ V_b

$$\frac{V_b - 5}{10} + \frac{V_b - V_a}{10} + i_L(0^-) = 0$$

$$\boxed{-\frac{V_a}{10} \left[1 \right] + \frac{V_b}{10} \left[1 + 1 \right] = -0.25} \rightarrow (2)$$


$\frac{20}{2} = 10$

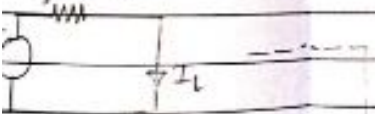

$I_L = 0.75 \text{ A}$

$V_a(0^+) = 1.5 \text{ V}$

$V_b(0^+) = -0.5 \text{ V}$

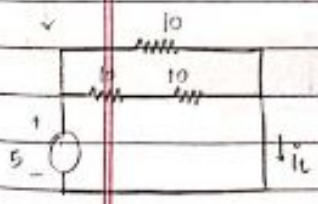

(20)

$$\frac{di(0^+)}{dt} = -4 \text{ A/s} \quad \text{Check}$$

$$\Rightarrow \left[+2i(t) - V_c(t) = 2 \frac{di(t)}{dt} \right] \rightarrow (2)$$

$$\Rightarrow +2i(t) - \frac{V_c(t)}{2} = \frac{di(t)}{dt}$$

$$\text{At } t=0^+ \quad \frac{di(0^+)}{dt} = + (2) - \frac{12}{2} = 2 - 6$$

$$\therefore \frac{di(0^+)}{dt} = -4 \text{ A/s}$$

→ Diff eq (2) w.r.t 't'

$$2 \frac{di(t)}{dt} - 2 \frac{d^2i(t)}{dt^2} - 1 \cdot i(t) = 0$$

$$\text{At } t=0^+ \quad 2 \frac{di(0^+)}{dt} - 2 \frac{d^2i(0^+)}{dt^2} - 1 \cdot i(0^+) = 0$$

$$2(2) - \frac{1}{0.4}(2) = 2 \frac{d^2i(0^+)}{dt^2} \Rightarrow \frac{-8-5}{2} = -6.5$$

$$\Rightarrow \frac{d^2i(0^+)}{dt^2} = -6.5 \text{ A/s}^2$$

→ Differentiate eq (2) w.r.t 't'

$$i_c = C \frac{dv}{dt}$$

$$+2 \frac{di(t)}{dt} - \frac{dV_c(t)}{dt} = 2 \frac{d^2i(t)}{dt^2} \Rightarrow \frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = \frac{-2}{0.4} = 5$$

At $t=0^+$,


$$\frac{dV_c(0^+)}{dt} = 2(2.5) + 10(-4) = 5 - 40$$

$$= 2 \frac{di(0^+)}{dt} - 2 \frac{d^2i(0^+)}{dt^2} = -8 + 13$$

$$\therefore \frac{dV(0^+)}{dt} = 5 \text{ V/s}$$

(21)

For $t = \infty$, switch is open.

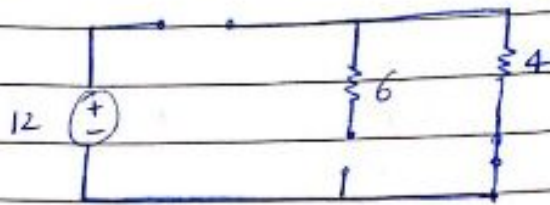


$$i(\infty) = 0 \quad ; \quad V(\infty) = 0$$

10-10-19

• 3 TYPES OF FUNCTION


1) UNIT STEP INPUT:

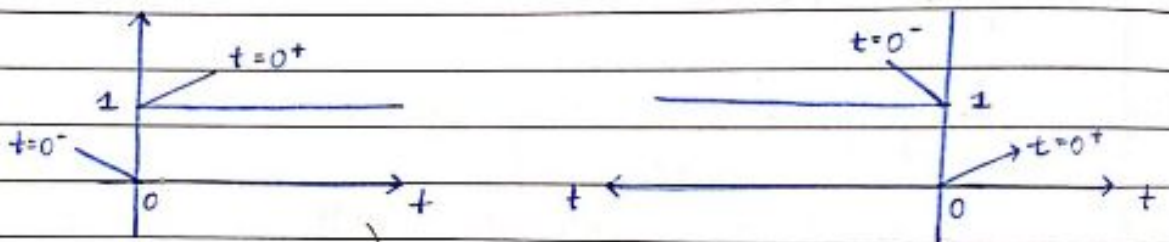

$$u(t) = \begin{cases} 1, & t \geq 0 \\ 0, & t \leq 0 \end{cases}$$



$$u(-t) = \begin{cases} 0, & t \geq 0 \\ 1, & t \leq 0 \end{cases}$$

2) RAMP INPUT:

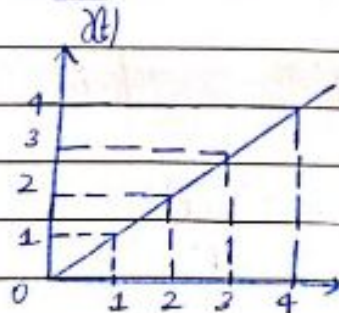


$$r(t) = \begin{cases} t, & t \geq 0 \\ 0, & t \leq 0 \end{cases}$$

3) IMPULSE INPUT:

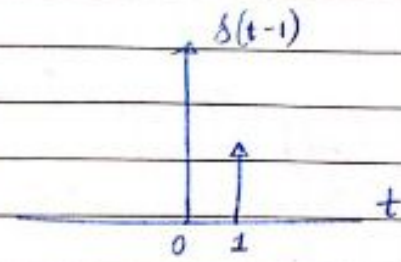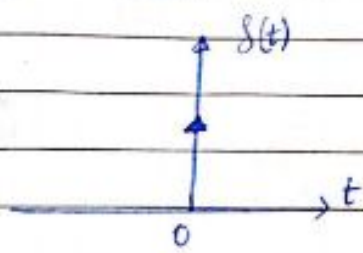


1) For the given circuit, find $i(0^+)$, $v(0^+)$, $\frac{di(0^+)}{dt}$, $\frac{dv(0^+)}{dt}$, $i(\infty)$, $v(\infty)$.

★
Check

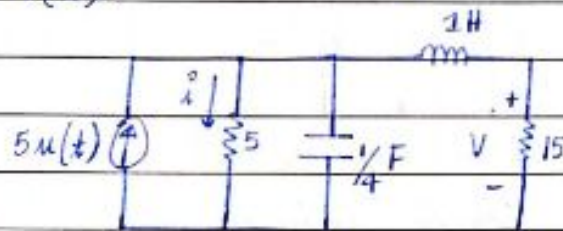


S: At $t=0^-$

Switch is open:

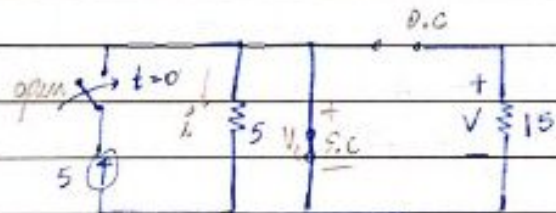

$i(0^-) = 0$


$v(0^-) = 0$

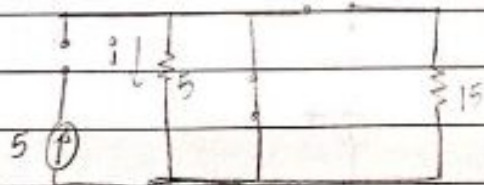

$i(0^-) = i(0^+) = 0$

$v_c(0^-) = v_c(0^+) = 0$

At $t=0$, switch is closed

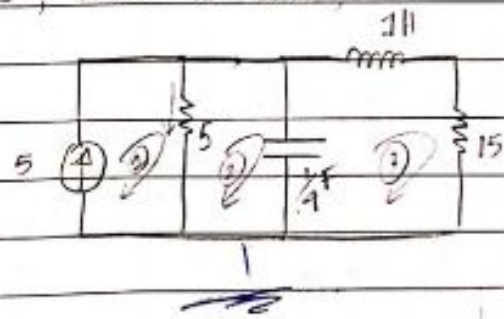

25×10^{-3}
 25μ



$i = \frac{V_c}{5}$

For $u(t)$, $t=0^-$, switch open, $t=0$, s-closed

For $u(-t)$, $t=0^-$, SW-closed, $t=0$ s-open

(23)

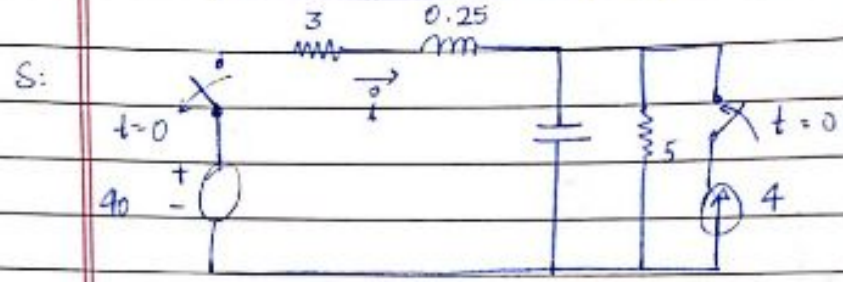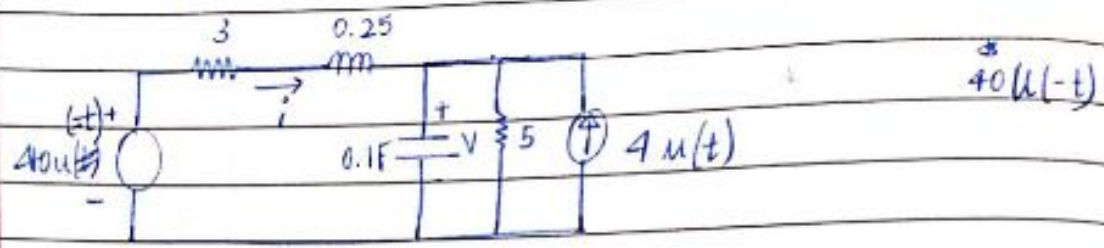
2) For the given circuit $v(0^-)$, $i(0^-)$, $\frac{di(0^+)}{dt}$, $\frac{dv(0^+)}{dt}$, $i(\infty)$, $v(\infty)$



* \rightarrow 'i' is the current through inductor and 'v' is the voltage across the capacitor. These values do not change instantaneously

$\rightarrow i(0^-) = i(0^+) = 5A$ } substitutions shown below.
 $\rightarrow v(0^+) = v(0^-) = 25V$ }


• At $t = 0^-$,

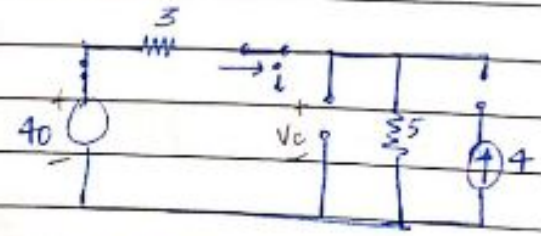

$\rightarrow i(0^-) = \frac{40}{5+3} \Rightarrow i(0^-) = 5A$

$\rightarrow V(0^-) = \frac{40 \times 5}{8} \Rightarrow V(0^-) = 25V$

• At $t > 0$,

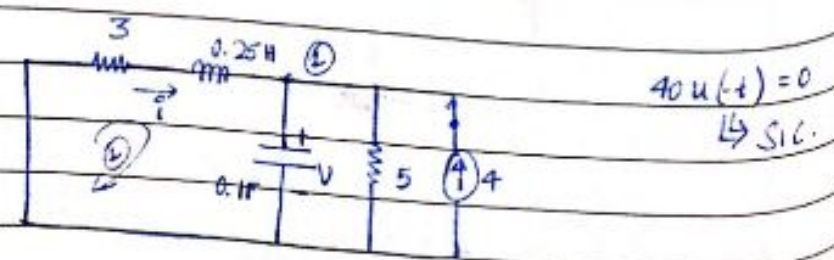

(24)

Applying KVL, loop ①

$$-3i(t) - L \frac{di(t)}{dt} - V_c = 0$$

$$-3i(0^+) - L \frac{di(0^+)}{dt} - V_c(0^+) = 0 \quad [\text{At } t=0^+]$$

$$-3(5) - 0.25 \frac{di(0^+)}{dt} - 25 = 0$$

$$\therefore \boxed{\frac{di(0^+)}{dt} = -160 \text{ A/s}}$$


→ $\left\{ i_c = C \frac{dV}{dt} \right\} \rightarrow$ This cannot be used coz some current does not flow.

Applying KCL at node ①:

$$-i - 4 + C \frac{dV}{dt} + \frac{V}{5} = 0$$

$$\text{At } t=0^+; \quad -5 - 4 + 0.1 \frac{dV(0^+)}{dt} + \frac{25}{5} = 0$$

$$\therefore \boxed{\frac{dV(0^+)}{dt} = 40 \text{ V/s}}$$

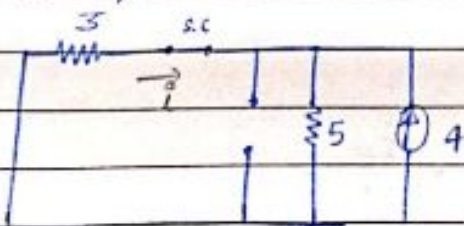→ for $t = \infty$,

$$\rightarrow i(\infty) = -\frac{4 \times 5}{8} \quad \text{-ve bcoz of current direction}$$

$$\therefore \boxed{i(\infty) = -2.5 \text{ A}}$$


$$V(\infty) = +\frac{3 \times 5}{8} = iR$$

$$V(\infty) = \frac{15}{2}$$

$$\therefore \boxed{V(\infty) = 7.5 \text{ V}}$$

①

10-10-19

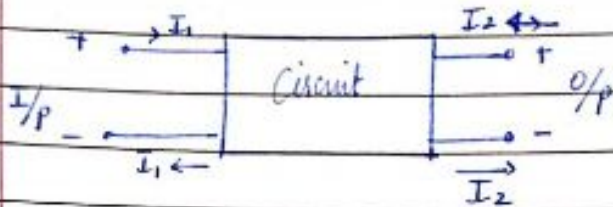
MODULE - 5TWO PORT PARAMETERS

- A pair of terminals through which current may enter or leave a network is known as a port.
- A port is an access to the network and consists of a pair of terminals.
- A two port network has two ports, one of which is the input and the other is the output.

- TYPES OF 2 PARAMETERS [2-PORT]

- ① Admittance @ Y/S.C. parameters
- ② Impedance / Z / O.C. parameters
- ③ Hybrid / H parameters
- ④ Transmission / ABCD parameters.

- ADMITTANCE PARAMETER:

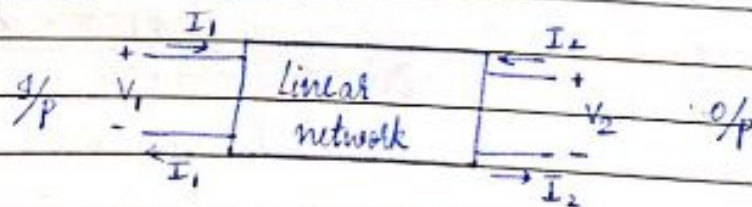

- Consider the network shown. It is assumed that the network
- is linear and contains no dependent sources.
- Considering the principle of superposition, current I_1 can be written as sum of 2 components, one due to V_1 & the other due to V_2 .

(2)


* $Y_{12} = Y_{21}$ (when no dependent sources are there)We have, $I_1 = Y_{11}V_1 + Y_{12}V_2$ and $I_2 = Y_{21}V_1 + Y_{22}V_2$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

where, $Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0 \text{ (s.c.)}}$ \rightarrow i/p admittance / driving port admittance at the i/p port. $Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0 \text{ (s.c.)}}$ \rightarrow Reverse transfer admittance. $Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$ \rightarrow Forward transfer admittance. $Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$ \rightarrow o/p admittance / driving point admittance at the o/p port.

PROBLEMS:

1) Determine admittance parameters.

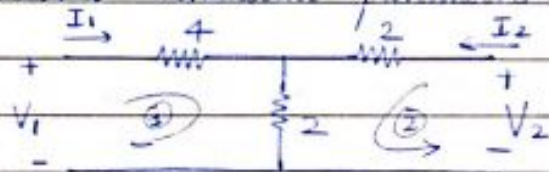* $I_1 \rightarrow$ clockwise } Fixed. $I_2 \rightarrow$ anti-clockwise } \rightarrow If there is a loop to be formed, any direction can be considered.

Standard admittance equations are:

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \rightarrow \textcircled{1}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \rightarrow \textcircled{2}$$

Applying KVL to loop $\textcircled{1}$:

$$V_1 - 4I_1 - 2(I_1 + I_2) = 0$$

$$V_1 = 6I_1 + 2I_2 \rightarrow \textcircled{3}$$

KVL to loop $\textcircled{2}$:

$$-2I_2 - 2(I_1 + I_2) + V_2 = 0$$

$$V_2 = 2I_1 + 4I_2 \rightarrow \textcircled{4}$$


(3)

Thus,
$$\begin{bmatrix} 6 & 2 \\ 2 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


$$\Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 6 & 2 \\ 2 & 4 \end{bmatrix}^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0.2 & -0.1 \\ -0.1 & 0.3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Thus;
$$\begin{matrix} Y_{11} = 0.2 \text{ } \Omega & ; & Y_{12} = -0.1 \text{ } \Omega \\ Y_{21} = -0.1 \text{ } \Omega & ; & Y_{22} = 0.3 \text{ } \Omega \end{matrix}$$

(a)

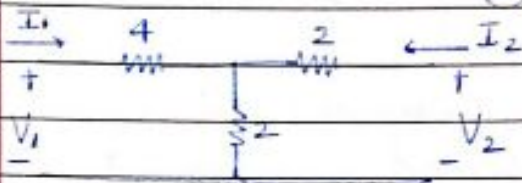

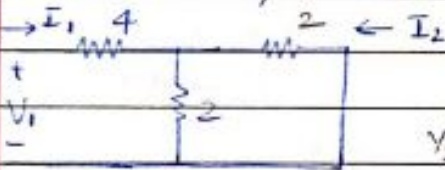\rightarrow When $V_2 = 0$, $Y_{11} = \frac{I_1}{V_1}$; $R = \left[4 + \frac{2 \times 2}{2+2} \right] = 4+1 = 5$



$\therefore Y_{11} = \frac{1}{5} \Rightarrow Y_{11} = 0.2 \text{ } \Omega$


$Y_{21} = \frac{I_2}{V_1}$; $I_2 = \frac{-I_1 \times 2}{2+2} \Rightarrow \boxed{I_2 = \frac{-I_1}{2}}$

$\Rightarrow Y_{21} = \frac{-I_1}{2V_1} = \frac{-I_1}{2(5I_1)} = \frac{-1}{10}$

$Y_{21} = -0.1 \text{ } \Omega$

$Y_{21} = Y_{12} = -0.1 \text{ } \Omega \rightarrow$ When no dependent source on there.

\rightarrow When $V_1 = 0$

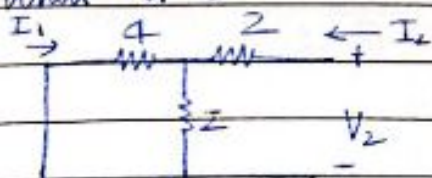

$Y_{22} = \frac{I_2}{V_2}$; $R = \left[2 + \frac{4 \times 2}{4+2} \right] = 3.33$


$\Rightarrow Y_{22} = \frac{1}{R} \Rightarrow Y_{22} = 0.3 \text{ } \Omega$

$Y_{12} = \frac{I_1}{V_2}$; $I_1 = \frac{-I_2 \times 2}{4+2} \Rightarrow \boxed{I_1 = \frac{-I_2}{3}}$ $V_2 = 3.3 I_2$

$Y_{12} = \frac{-I_2}{3V_2} = \frac{-I_2}{3 \times (3.3) I_2} \approx -0.1 \text{ } \Omega$

(5)

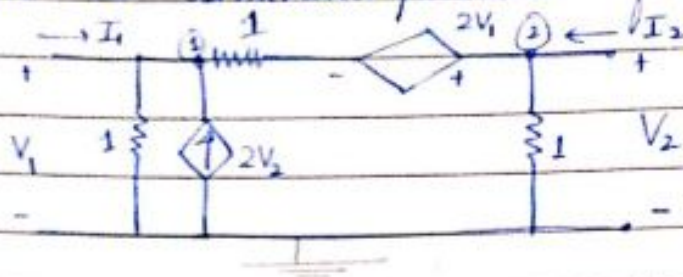2) Find the admittance parameters for the network shown.



S: Standard equations are:

$$Y_{11} V_1 + Y_{12} V_2 = \bar{I}_1 \longrightarrow \textcircled{1}$$

$$Y_{21} V_1 + Y_{22} V_2 = I_2 \longrightarrow \textcircled{2}$$

KCL at $\textcircled{1}$:

$$-I_1 + \frac{V_1}{1} - 2V_2 + \frac{V_1 - (-2V_1)}{1} - V_2 = 0$$

$$\boxed{V_1 [1+1+2] - V_2 [2+1] = I_1} \longrightarrow \textcircled{3}$$

KCL at $\textcircled{2}$:

$$-I_2 + \frac{V_2}{1} + \frac{V_2 - V_1 - 2V_1}{1} = 0$$

$$\boxed{-V_1 [1+2] + V_2 [1+1] = I_2} \longrightarrow \textcircled{4}$$

Comparing $\textcircled{1}$ & $\textcircled{3}$:

$$\boxed{Y_{11} = 4 \Omega^{-1}} ; \boxed{Y_{12} = -3 \Omega^{-1}}$$


Comparing $\textcircled{2}$ & $\textcircled{4}$:

$$\boxed{Y_{21} = -3 \Omega^{-1}} ; \boxed{Y_{22} = 2 \Omega^{-1}}$$

⑥

3) Find the admittance parameters.

① & ② are fixed.

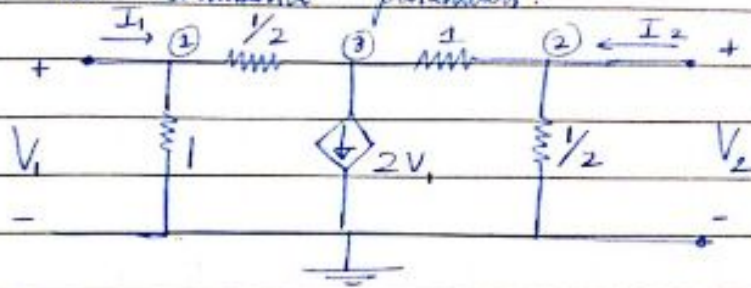

S: Standard equations are:

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \longrightarrow \textcircled{1}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \longrightarrow \textcircled{2}$$

KCL @ node ①:

$$-I_1 + V_1 + 2(V_1 - V_3) = 0$$

$$V_1 [1+2] - 2V_3 = I_1 \longrightarrow \textcircled{3}$$

Subs. ④

$$3V_1 - 2V_2 = I_1$$

⑥

KCL @ ③:

$$2(V_3 - V_1) + 2V_1 + V_3 - V_2 = 0$$

$$-2V_1 + 2V_1 - V_2 + 3V_3 = 0$$

$$-4V_1 - V_2 + 3V_3 = 0 \longrightarrow \textcircled{4}$$

$$\hookrightarrow V_3 = \frac{V_2}{3}$$

KCL @ ②:

$$-I_2 + 2V_2 + V_2 - V_3 = 0$$

$$V_2(2+1) - V_3 = I_2 \longrightarrow \textcircled{5}$$

$$3V_2 - V_2 = I_2$$

$$\Rightarrow V_2 \left[\frac{3-1}{3} \right] = I_2$$

$$\frac{8}{3} V_2 = I_2 \longrightarrow \textcircled{7}$$

(7)

Comparing ③ & ①:

$$Y_{11} = 3 \Omega^{-1}$$


$$Y_{12} = -\frac{2}{3} \Omega^{-1}$$

Comparing ② & ②:

$$Y_{21} = 0$$

$$Y_{22} = \frac{8}{3} \Omega^{-1}$$

• IMPEDENCE PARAMETERS:

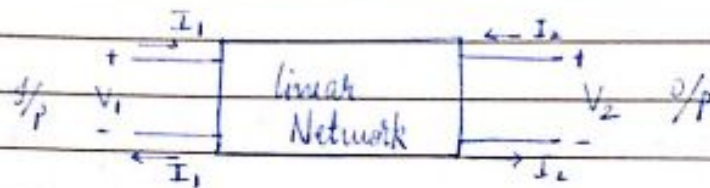

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

where, $Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$ \rightarrow Input impedance when the output is open circuit ($\because I_2 = 0$)

$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$ \rightarrow Reverse transfer impedance when input is O.C ($\because I_1 = 0$)

$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$ \rightarrow Forward transfer impedance when output is O.C ($\because I_2 = 0$)

$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$ \rightarrow Output impedance when input is O.C ($\because I_1 = 0$)

NOTE:

$$Z_{12} = Z_{21}$$


if there are no dependent sources

⑧

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

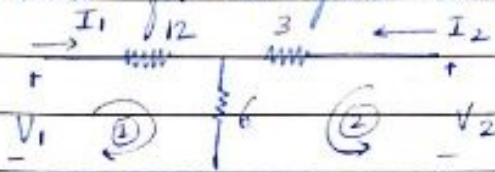1) Find Z-parameters for the given circuit.



S: Standard equations [Impedance parameter eqs] are:

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \longrightarrow \textcircled{1}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \longrightarrow \textcircled{2}$$

Applying KVL to loop ①:

$$V_1 - 12I_1 - 6(I_1 + I_2) = 0$$

$$\boxed{V_1 = 18I_1 + 6I_2} \longrightarrow \textcircled{3}$$

Applying KVL to loop ②:

$$-3I_2 + 6(I_2 + I_1) + V_2 = 0$$

$$\boxed{V_2 = 6I_1 + 9I_2} \longrightarrow \textcircled{4}$$

Comparing ② & ③:

$$\boxed{Z_{11} = 18 \Omega} ; \boxed{Z_{12} = 6 \Omega}$$

Comparing ② & ④:

$$\boxed{Z_{21} = 6 \Omega} ; \boxed{Z_{22} = 9 \Omega}$$

NOTE: 3 types of network:


- 1) T \rightarrow preferred for Z
- 2) Π \rightarrow preferred for Y
- 3) Bridge

* 2) Given: $Z = \begin{bmatrix} 12 & 4 \\ 4 & 8 \end{bmatrix}$ Find the elements of the network.

S: Standard Z parameters equations are:

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \longrightarrow \textcircled{1}$$
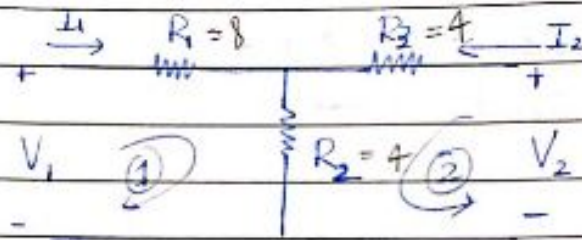
$$V_2 = Z_{21}I_1 + Z_{22}I_2 \longrightarrow \textcircled{2}$$



$$Z_{11} = 12 \Omega, \quad Z_{12} = 4 \Omega$$

$$Z_{21} = 4 \Omega, \quad Z_{22} = 8 \Omega$$

KVL to loop $\textcircled{1}$:

$$V_1 = I_1(R_1 + R_2) + I_2 R_2 \longrightarrow \textcircled{3}$$

$$\text{loop } \textcircled{2}: \quad V_2 = I_1 R_2 + I_2(R_2 + R_3) \longrightarrow \textcircled{4}$$

Comparing $\textcircled{1}$ & $\textcircled{3}$

$$R_2 = Z_{12} \Rightarrow R_2 = 4 \Omega$$

$$R_1 + R_2 = 12 \Rightarrow R_1 = 8 \Omega$$

$$R_2 + R_3 = 8 \Rightarrow R_3 = 4 \Omega$$

(11)

$$I_1 \left[\frac{-R_1 + \beta R_1 R_2 + \beta R_1^2}{1 + \beta R_1} \right] + I_2 \left[\frac{R_1 + R_2 + R_3 + \beta R_1 R_2 + \beta R_1^2}{1 + \beta R_1} \right] = -V_2$$

$$\frac{I_1 R_1}{1 + \beta R_1} \left[-1 - \beta R_1 + \beta R_1 + \beta R_2 \right] + I_2 \left[\frac{-R_1 - R_2 - R_3 + \beta R_1 (R_2 + R_1)}{1 + \beta R_1} \right] = -V_2$$

$$-V_2 = \frac{I_1 R_1}{1 + \beta R_1} (\beta R_2 - 1) + I_2 \left[\frac{-R_1 - R_2 - R_3 - \beta R_1 R_2 - R_3 / (1 + \beta R_1) + \beta R_1^2 / (1 + \beta R_1)}{(1 + \beta R_1)} \right]$$


$$I_1 R_1 \frac{(\beta R_2 - 1)}{1 + \beta R_1} + I_2 \left[\frac{-R_3 - (R_1 + R_2)}{(1 + \beta R_1)} \right] = -V_2$$

Cancelling (-)

$$\Rightarrow \left[\frac{I_1 R_1 (1 - \beta R_2)}{1 + \beta R_1} + I_2 \left[\frac{R_3 + (R_1 + R_2)}{1 + \beta R_1} \right] \right] = V_2$$

$\Rightarrow \Rightarrow Z_{11} = \frac{R_1}{1 + \beta R_1} \Omega$	$Z_{12} = \frac{R_1}{1 + \beta R_1} \Omega$
$Z_{21} = \frac{R_1 (1 - \beta R_2)}{1 + \beta R_1} \Omega$	$Z_{22} = \frac{R_3 + (R_1 + R_2)}{1 + \beta R_1} \Omega$

2. HYBRID PARAMETERS:

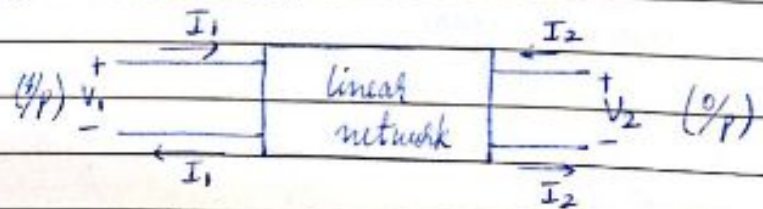

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} \rightarrow \text{Input impedance when } \text{o/p} \text{ is short circuit.}$$


$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} \rightarrow \text{Reverse voltage gain when } \text{i/p} \text{ open circuit.}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0} \rightarrow \text{Forward current gain when } \text{o/p} \text{ is short circuit}$$

(12)

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} \quad \rightarrow \text{Output admittance when input is open circuit.}$$

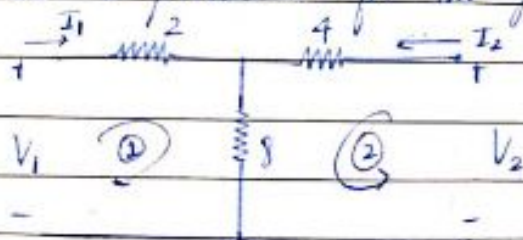1) Find the h-parameters for the given circuit.



S: The standard h-parameter equations are:

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \rightarrow (1)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \rightarrow (2)$$

Applying KVL to loop (1):

$$-2I_1 - 8(I_1 + I_2) + V_1 = 0$$

$$-10I_1 - 8I_2 = -V_1$$

$$\boxed{10I_1 + 8I_2 = V_1} \quad \rightarrow (3)$$

Loop (2):

$$-4I_2 - 8(I_2 + I_1) + V_2 = 0$$

$$\boxed{8I_1 + 12I_2 = V_2} \quad \rightarrow (4)$$

Rearranging eq. (4) \Rightarrow
$$I_2 = \frac{-8I_1 + 1V_2}{12} \quad \rightarrow (5)$$

Comparing (2) & (5)

$$\boxed{h_{21} = -\frac{2}{3}}$$

$$\boxed{h_{22} = \frac{1}{12} \Omega}$$

Substitute (5) in (3)

$$10I_1 + 8 \left(\frac{-8I_1 + 1V_2}{12} \right) = V_1$$


$$I_1 \left(\frac{-64 + 10}{12} \right) + \frac{8}{12} V_2 = V_1$$

$$\boxed{I_1 \left(\frac{-56}{12} \right) + \frac{2}{3} V_2 = V_1} \quad \rightarrow (6)$$

** \Rightarrow Comparing (1) and (6),
$$\boxed{h_{11} = -\frac{14}{3} \Omega} \quad \text{and} \quad \boxed{h_{12} = \frac{2}{3}}$$

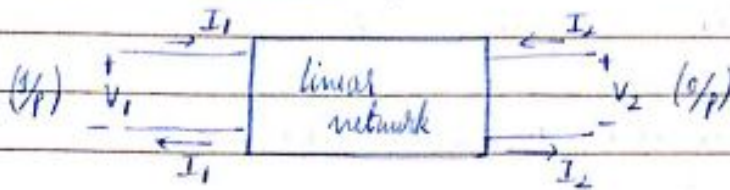(13)

- TRANSMISSION PARAMETERS [Also called A, B, C, D parameters], T parameters, Transmission parameters



$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} \quad \text{(ii)}$$

where $A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \rightarrow$ Reverse voltage gain when o/p is O.C.

$B = - \left. \frac{V_1}{I_2} \right|_{V_2=0} \rightarrow$ Reverse transfer impedance when o/p is S.C.


$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \rightarrow$ Reverse transfer admittance when o/p is O.C.

$D = - \left. \frac{I_1}{I_2} \right|_{V_2=0} \rightarrow$ Reverse current gain when o/p is S.C.

NOTE:

- * 1) When a two port network doesn't contain any dependent source, then $[AD - BC = 1]$.

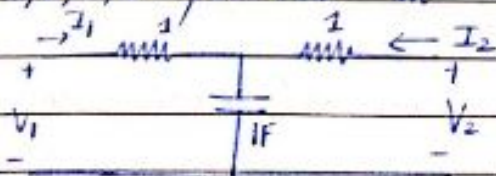- 1) Determine A, B, C, D parameters in S -domain.



S:

\rightarrow The circuit in S -domain is

\rightarrow Standard equations:

$$V_1 = AV_2 - BI_2 \rightarrow \textcircled{1}$$

$$V_1/I_1 = CV_2 - DI_2 \rightarrow \textcircled{2}$$

(14)

Applying KVL to loop (1):

$$-I_1 - \frac{1}{s} [I_1 + I_2] + V_2 = 0$$

$$\boxed{I_1 \left[\frac{1+1}{s} \right] + \frac{1}{s} I_2 = V_2} \rightarrow (3)$$

loop (2):

$$-I_2 - \frac{1}{s} [I_2 + I_1] + V_2 = 0$$

$$\frac{1}{s} I_1 + \left[\frac{1+1}{s} \right] I_2 = V_2$$

Rearranging,

$$I_1 = s \left[V_2 - \left(\frac{1+1}{s} \right) I_2 \right]$$

$$\boxed{I_1 = sV_2 - (s+1)I_2} \rightarrow (4)$$

→ Comparing (2) & (4)

$$\boxed{E = sV} ; \boxed{D = (s+1)}$$

Substitute (4) in (3):

$$\left[sV_2 - (s+1)I_2 \right] \left(\frac{1+1}{s} \right) + \frac{1}{s} I_2 = V_2$$

$$sV_2 + V_2 - (s+1)I_2 - (s+1)I_2 + \frac{1}{s} I_2 = V_2$$

$$I_2 \left(\frac{-(s+1)}{s} - \frac{(s+1)}{s} + \frac{1}{s} \right) + (s+1)V_2 = V_2 \Rightarrow -I_2(s+2) + (s+1)V_2 = V_2$$

$$\boxed{(s+1)V_2 - I_2 \left(\frac{2s^2 + 2s + 1}{s} \right) = V_2} \rightarrow (5)$$

Comparing (1) and (5),

$$\boxed{A = s+1} ; \boxed{B = \frac{2s^2 + 2s + 1}{s}} \text{ *check}$$

$$\therefore \boxed{B = (s+2)r}$$

(15)

RELATIONSHIPS:

1) Relationship between 'z' & 'y' parameters:

(A) 'y' in terms 'z' parameters.

W.k.t

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \longrightarrow (1)$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \longrightarrow (2)$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \longrightarrow (3)$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \longrightarrow (4)$$

$$(3) \rightarrow I_1 = \frac{V_1 - Z_{12}I_2}{Z_{11}} \Rightarrow I_1 = \frac{V_1}{Z_{11}} - \frac{Z_{12}I_2}{Z_{11}} \longrightarrow (5)$$

Subs (5) in eq. (4)

$$V_2 = Z_{21} \left(\frac{V_1 - Z_{12}I_2}{Z_{11}} \right) + Z_{22}I_2$$

$$\Rightarrow V_2 = \frac{Z_{21}V_1}{Z_{11}} + I_2 \left(\frac{Z_{22} - Z_{21}Z_{12}}{Z_{11}} \right)$$

$$I_2 = \frac{(V_2 - \frac{Z_{21}V_1}{Z_{11}}) Z_{11}}{(Z_{11}Z_{22} - Z_{21}Z_{12})} = \frac{Z_{11}V_2 - Z_{21}V_1}{(Z_{11}Z_{22} - Z_{21}Z_{12})}$$

$$I_2 = \frac{V_1 Z_{21}}{(Z_{12}Z_{21} - Z_{11}Z_{22})} + (-) \frac{V_2 Z_{11}}{(Z_{12}Z_{21} - Z_{11}Z_{22})}$$

$$\text{Let } \Delta Z = Z_{11}Z_{22} - Z_{21}Z_{12}$$

$$\Rightarrow I_2 = \frac{Z_{21}V_1}{-\Delta Z} + \frac{Z_{11}V_2}{\Delta Z} \longrightarrow (6)$$

Plug eq. (6) in (5)

$$I_1 = \frac{V_1}{Z_{11}} - \frac{Z_{12}}{Z_{11}} \left(\frac{-Z_{21}V_1 + Z_{11}V_2}{\Delta Z} \right)$$

(16)

$$I_1 = \frac{V_1}{Z_{11}} + \frac{Z_{21} Z_{12} V_1}{Z_{11} \Delta Z} - \frac{Z_{12} V_2}{\Delta Z}$$

$$I_1 = \left(\frac{1 + \frac{Z_{21} Z_{12}}{Z_{11} \Delta Z}}{\frac{Z_{11}}{Z_{11} \Delta Z}} \right) V_1 - \frac{Z_{12} V_2}{\Delta Z}$$

$$I_1 = \left(\frac{\cancel{Z_{11} Z_{12}} + Z_{11} Z_{22} + \cancel{Z_{21} Z_{12}}}{Z_{11} \Delta Z} \right) V_1 - \frac{Z_{12} V_2}{\Delta Z}$$

$$\therefore I_1 = \frac{Z_{22} V_1 - Z_{12} V_2}{\Delta Z} \rightarrow \textcircled{7}$$

31-10-19

- Relationship between 'Z' and 'T' parameters.
- (a) 'Z' in terms of 'T'.

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \rightarrow \textcircled{1}$$

$$V_1 = A V_2 - B I_2 \rightarrow \textcircled{3}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \rightarrow \textcircled{2}$$

$$I_1 = C V_2 - D I_2 \rightarrow \textcircled{4}$$

Rearranging eq. ④.

$$V_2 = \frac{I_1 + D I_2}{C}$$

$$V_2 = \frac{I_1}{C} + \frac{D I_2}{C} \rightarrow \textcircled{5}$$

$$\rightarrow \boxed{Z_{21} = \frac{1}{C}} ; \boxed{Z_{22} = \frac{D}{C}}$$

Substitute ⑤ in ③:

$$V_1 = A \left(\frac{I_1 + D I_2}{C} \right) - B I_2$$

$$V_1 = \left(\frac{A}{C} - \frac{B}{C} \right) I_1 + \left(\frac{AD}{C} - \frac{B}{C} \right) I_2 \rightarrow \textcircled{6}$$

$$\rightarrow \boxed{Z_{11} = \frac{A}{C}} ; \boxed{Z_{12} = \frac{AD - B}{C}}$$

(17)

$$(a) Z_{12} = \frac{AD - BC}{C}$$

$$Z_{12} = \frac{\Delta T}{C} \quad \text{where } \Delta T = AD - BC$$

(b) 'T' in terms of Z

1-parameter

$$V_1 = A I_1 + B I_2 \rightarrow (1)$$

$$I_1 = C I_2 + D I_1 \rightarrow (2)$$

2-parameter

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \rightarrow (3)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \rightarrow (4)$$

Compare (2) & (4)

$$I_1 = \frac{V_2}{Z_{21}} - \frac{Z_{22} I_2}{Z_{21}} \rightarrow (5)$$

Compare (1) & (5)

$$A = \frac{Z_{11}}{Z_{21}} \quad ; \quad D = \frac{Z_{22}}{Z_{21}}$$

Substitute (5) in (3)

$$V_1 = Z_{11} \left(\frac{V_2}{Z_{21}} - \frac{Z_{22} I_2}{Z_{21}} \right) + Z_{12} I_2$$

$$V_1 = \frac{Z_{11}}{Z_{21}} V_2 - \frac{(Z_{22} Z_{11} - Z_{12} Z_{21}) I_2}{Z_{21}} \rightarrow (6)$$

Compare (2) & (6)


$$\therefore A = \frac{Z_{11}}{Z_{21}} \quad ; \quad B = \frac{(Z_{21} Z_{22} - Z_{12} Z_{21})}{Z_{21}}$$

(18)

TANDAKP Problems

Q 1) Complete the given table and also find the values of Y-parameters.

	V_1	V_2	I_1	I_2
1	50	100	-1	27
2	100	50	7	24
3	200	0	(20)	(28)
4	(140.845)	(-98.592)	20	0
5	(135.80)	(56.34)	10	30

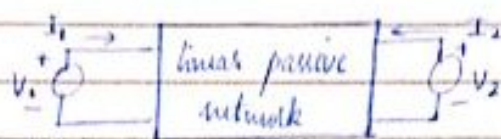

S: Y-parameter equations (in matrix form)

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\text{2 trials } \left\{ \begin{array}{l} I_1 \rightarrow \begin{bmatrix} -1 & 7 \end{bmatrix} \\ I_2 \rightarrow \begin{bmatrix} 27 & 24 \end{bmatrix} \end{array} \right. = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} 50 & 100 \\ 100 & 50 \end{bmatrix}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} -1 & 7 \\ 27 & 24 \end{bmatrix} \begin{bmatrix} 50 & 100 \\ 100 & 50 \end{bmatrix}^{-1}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} -1 & 7 \\ 27 & 24 \end{bmatrix} \begin{bmatrix} -0.0067 & 0.0133 \\ 0.0133 & -0.0067 \end{bmatrix}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 0.1 & -0.06 \\ 0.14 & 0.2 \end{bmatrix} \text{ } \checkmark$$

Calc: Steps \rightarrow Mat A, Shift 4, Inv, Mat B, 2x2, Values AC,
 (Shift 4, Mat A) x (Shift 4, Mat B, Inv) = Ans

(19)

$$A = BC$$

$$B^{-1}A = \underbrace{B^{-1}B} I C$$

classmate
Date
Page

3) →

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 = 200 \\ V_2 = 0 \end{bmatrix}$$

$$= \begin{bmatrix} 0.1 & -0.06 \\ 0.14 & 0.2 \end{bmatrix} \begin{bmatrix} 200 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 28 \end{bmatrix}$$

4) →

$$\begin{bmatrix} 20 \\ 0 \end{bmatrix} = \begin{bmatrix} 0.1 & -0.06 \\ 0.14 & 0.2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} 0.1 & -0.06 \\ 0.14 & 0.2 \end{bmatrix}^{-1} \begin{bmatrix} 20 \\ 0 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} 140.845 \\ -98.592 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


5) →

$$\begin{bmatrix} 10 \\ 80 \end{bmatrix} = \begin{bmatrix} 0.1 & -0.06 \\ 0.14 & 0.2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} 0.1 & -0.06 \\ 0.14 & 0.2 \end{bmatrix}^{-1} \begin{bmatrix} 10 \\ 80 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} 133.80 \\ 56.34 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

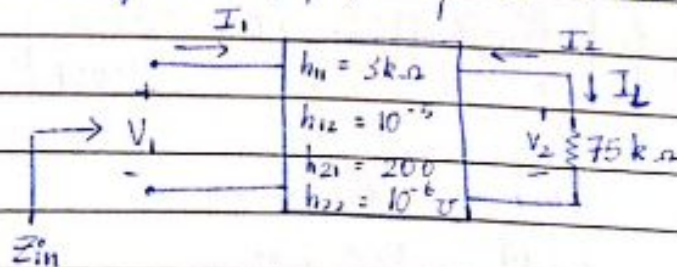2) Find the impedance (input) of the network.



S: Standard equations of h-parameters,

$$\begin{bmatrix} V_1 = h_{11} I_1 + h_{12} V_2 \\ I_2 = h_{21} I_1 + h_{22} V_2 \end{bmatrix} \begin{matrix} \rightarrow \textcircled{1} \\ \rightarrow \textcircled{2} \end{matrix}$$

(20)

$$V_2 = I_2 \times Z_L \rightarrow V_2 = -I_2 Z_L \rightarrow (3)$$

→ Using this in eq. (2):

$$I_2 = h_{21} I_1 + h_{22} (I_2 Z_L)$$

$$I_2 = h_{21} I_1 - h_{22} Z_L I_2$$

$$I_2 (1 + h_{22} Z_L) = h_{21} I_1$$

$$I_2 = \frac{h_{21} I_1}{1 + h_{22} Z_L} = \frac{200 I_1}{1 + (10^{-6} \times 75 \times 10^3)}$$

$$I_2 = \frac{200}{1 + 75 \times 10^{-3}} I_1$$

$$I_2 = 186.046 I_1 \rightarrow (4)$$

→ Subs. (4) in (3)

$$V_2 = -186.046 I_1 \times 75 \times 10^3$$

$$V_2 = -13.95 \times 10^6 I_1 \rightarrow (5)$$


→ Substitute (5) in (1)

$$V_1 = (3 \times 10^3) I_1 + (10^{-5} \times (-13.95 \times 10^6)) I_1$$

$$V_1 = I_1 (3 \times 10^3 - 13.95 \times 10^1)$$

$$\frac{V_1}{I_1} = Z_{in} = 2.86 \text{ k}\Omega$$

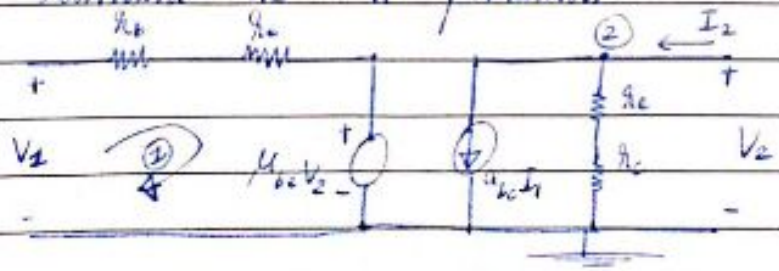* 3) The model of a transistor in CE mode is as shown in figure. Determine its 'h' parameters.



(2)

Standard equations of 'h' parameters,

$$V_1 = h_{11} I_1 + h_{12} I_2 \quad \rightarrow (1)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \rightarrow (2)$$

→ Applying KVL to loop (1):

$$-R_{10} I_1 - R_{1c} I_2 - \mu_{1cc} V_2 + V_1 = 0$$

$$(R_{10} + R_{1c}) I_1 + \mu_{1cc} V_2 = V_1 \quad \rightarrow (3)$$

Compare (1) & (3):

$$\begin{cases} h_{11} = R_{10} + R_{1c} \\ h_{12} = \mu_{1cc} \end{cases}$$

→ Applying KCL @ node (2):


$$R_{1c} I_1 + V_2 - I_2 = 0$$

$$I_2 = \frac{R_{1c} I_1 + V_2}{(R_{1c} + R_{1c})} \quad \rightarrow (4)$$

Compare (2) & (4):

$$\begin{cases} h_{21} = \alpha_{1cc} \\ h_{22} = \frac{1}{R_{1c} + R_{1c}} \end{cases}$$

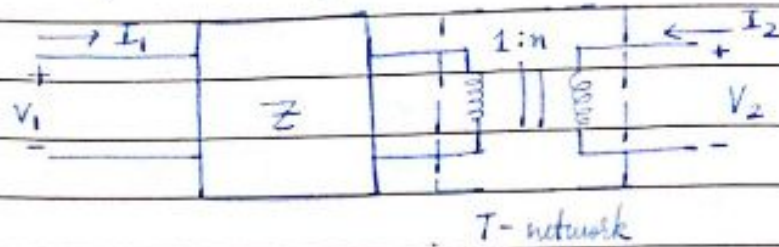
5) Find the Z-parameters of the overall network



S: Overall,

$$[T] = [T]_1 \times [T]_2$$

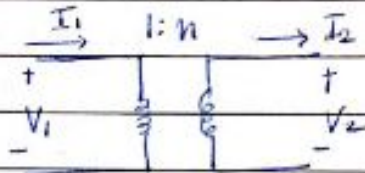First, we should find out the transmission parameters to the network shown:



$$\frac{V_1}{V_2} = \frac{1}{n} = \frac{I_2}{I_1}$$

We know that,

$$V_1 = AV_2 - BI_2 \quad \rightarrow (1)$$

$$I_1 = CV_2 - DI_2 \quad \rightarrow (2)$$

For the given transformer in the circuit, we have,

$$\frac{V_1}{V_2} = \frac{1}{n} = \frac{-I_2}{I_1} \quad \rightarrow (3)$$

Let $I_2 = 0$ in (3):

$$\frac{-V_1}{V_2} = \frac{1}{n}$$

$$V_1 = \frac{1}{n} V_2 \quad \rightarrow (4)$$

Comparing (3) and (4)

$$A = \frac{1}{n} ; B = 0$$

Similarly,

$$\frac{-I_2}{I_1} = \frac{1}{n}$$

$$I_1 = -n I_2 \rightarrow (5)$$

Comparing (2) & (5):

$$C=0; D=n$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1/n & 0 \\ 0 & n \end{bmatrix} \rightarrow (6)$$

→ The Z parameters of the first part of the circuit are:

$$[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

→ 'Y' in terms of 'Z', we have:

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} Z_{11}/Z_{21} & \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{21}} \\ 1/Z_{21} & Z_{22}/Z_{21} \end{bmatrix} \rightarrow (7)$$

The overall A, B, C, D parameters of the network can be obtained by multiplying the equations (6) & (7).

$$\begin{aligned} \begin{bmatrix} A & B \\ C & D \end{bmatrix} &= \begin{bmatrix} Z_{11}/Z_{21} & \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{21}} \\ 1/Z_{21} & Z_{22}/Z_{21} \end{bmatrix} \begin{bmatrix} 1/n & 0 \\ 0 & n \end{bmatrix} \\ &= \begin{bmatrix} Z_{11} + 0 & n(Z_{11}Z_{22} - Z_{12}Z_{21}) \\ Z_{21} \times n & Z_{22} \end{bmatrix} \\ \begin{bmatrix} A & B \\ C & D \end{bmatrix}_T &= \begin{bmatrix} Z_{11} & n(Z_{11}Z_{22} - Z_{12}Z_{21}) \\ Z_{21} \times n & Z_{22} \end{bmatrix} \\ \text{(overall A, B, C, D)} &= \begin{bmatrix} Z_{11} & n(Z_{11}Z_{22} - Z_{12}Z_{21}) \\ Z_{21} \times n & Z_{22} \end{bmatrix} \end{aligned}$$


Overall \bar{z} ,

$$[Z]_T = \begin{bmatrix} A/C & \Delta T/C \\ 1/C & D/C \end{bmatrix}$$

$$[\bar{z}]_T = \begin{bmatrix} Z_{11} & \frac{Z_{11} n Z_{22} - Z_{12} Z_{21} + Z_{21} Z_{12}}{n Z_{21}} \\ n Z_{21} & \frac{Z_{11} Z_{22} + Z_{12} Z_{21}}{n Z_{21}} \end{bmatrix}$$



$$[\bar{z}]_T = \begin{bmatrix} Z_{11} & n Z_{12} \\ n Z_{21} & n^2 Z_{22} \end{bmatrix}$$

• RESONANT CIRCUITS:

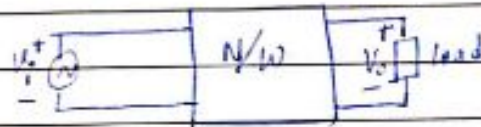

A given network will resonate when the net reactance, i.e., $X=0$. A two port network in general offers a complex impedance, consisting of resistive and reactive components.

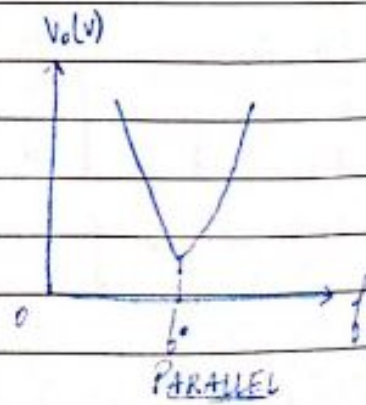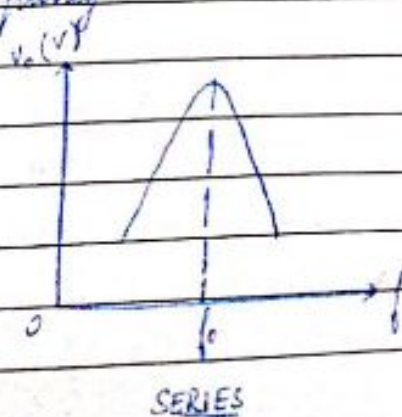At certain conditions, the impedance offered by the network is purely resistive; such a phenomena is called RESONANCE. The frequency at which this happens is called Resonant frequency.




A circuit becomes resonant circuit when the current drawn from the supply is in phase with the applied sinusoidal voltage. Then,

- 1) Resultant reactance = 0
- 2) Circuit behaves as a resistive circuit.
- 3) P.f. = 1 [Power factor]

• TYPES OF RESONANT CIRCUITS:

- 1) Series resonant circuit
- 2) Parallel resonant circuit [Anti-resonant]

✓ • SERIES RESONANCE:

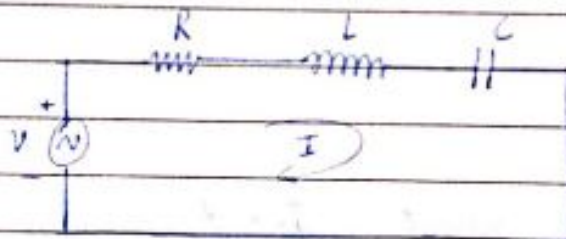

→ Consider the series RLC circuit shown above, where V = sinusoidal voltage, I = current flowing in the loop.

→ The circuit is said to be resonant when the resultant reactance of the circuit is zero.

→ The impedance of the given circuit at any frequency is:

$$\boxed{Z = R + j(X_L - X_C)} \longrightarrow \textcircled{1}$$

$$Z = R + j \left[\omega L - \frac{1}{\omega C} \right] \longrightarrow \textcircled{2}$$

$$\boxed{I = \frac{V}{Z} = \frac{V}{R + j(X_L - X_C)}} \longrightarrow \textcircled{3}$$

(26)

→ At resonance, the circuit must have unity P.F.
i.e.,

$$P.F. = \cos \phi = \frac{R}{Z}$$

i.e., $X_L - X_C = 0$

$$\rightarrow \omega L - \frac{1}{\omega C} = 0$$


$$\rightarrow \omega = \frac{1}{\sqrt{LC}}$$

$$\rightarrow \boxed{f_0 = \frac{1}{2\pi\sqrt{LC}}} \text{ Hz}$$

$$\boxed{\omega_0 = \frac{1}{\sqrt{LC}}} \text{ rad/sec}$$

→ f_0 = Resonant frequency.

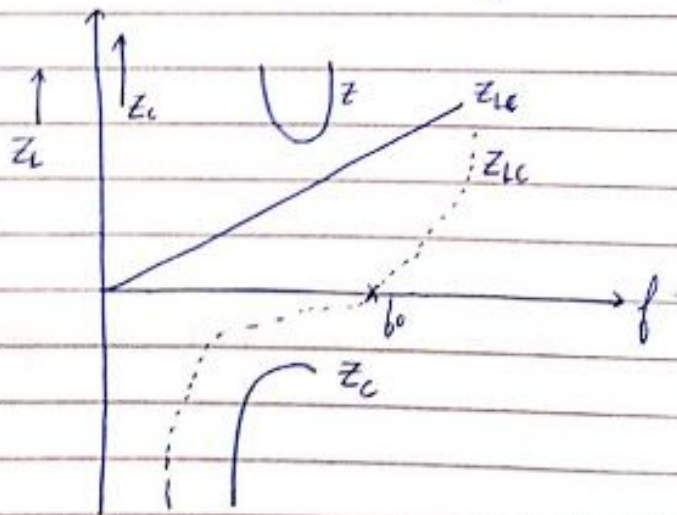7-11-19 → At resonance, the current, $I_0 = \frac{V}{R}$.



② → For $f < f_0$, Z_{ic} becomes capacitive

(2) For $f > f_0$,

Z_{LC} becomes inductive.

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

• VARIATION OF CURRENT, VOLTAGE WITH FREQUENCY:

→ The impedance of series RLC circuit is

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$I = \frac{V}{Z} \Rightarrow I = \frac{V}{R + j\left(\omega L - \frac{1}{\omega C}\right)}$$

***. Expression for frequency at which V_C (Voltage across capacitor) is maximum.

$$V_C = \frac{I}{j\omega C}$$

$$\Rightarrow V_C = \frac{V}{\left[R + j\left(\omega L - \frac{1}{\omega C}\right)\right] \times j\omega C}$$

$$|V_C| = \frac{V}{\omega C \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \quad \longrightarrow \textcircled{1}$$

Squaring on both sides,

$$V_C^2 = \frac{V^2}{(\omega C)^2 \left(R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2\right)}$$

→ The frequency at which V_C is maximum is obtained by

$$\frac{\partial V_C^2}{\partial \omega} = 0$$

(28)

$$\Rightarrow \frac{\partial V_c^2}{\partial \omega} = 0 = \frac{V^2}{C^2} \frac{\partial}{\partial \omega} \left[\frac{1}{\omega^2 \left[R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2 \right]} \right]$$

$$0 = \frac{V^2}{C^2} \left[\frac{0 - \frac{\partial}{\partial \omega} \left[\omega^2 \left[R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2 \right] \right]}{\left[\omega^2 \left[R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2 \right] \right]^2} \right]$$

$$\Rightarrow \frac{\partial}{\partial \omega} \left[\frac{\omega^2 R^2 + \left(\omega^2 L - 1 \right)^2}{C} \right] = 0$$

$$2R^2\omega + \frac{\partial}{\partial \omega} \left(\frac{\omega^2 L - 1}{C} \right) (2\omega L) = 0$$

$$\cancel{2R^2\omega} + \underbrace{\frac{\partial}{\partial \omega} \left[R^2 + \frac{\partial}{\partial \omega} \left(\omega^2 L - 1 \right) \right]}_{\text{can't be zero}} = 0$$

$$\Rightarrow R^2 + 2L(\omega^2 L - 1) = 0$$

$$R^2 + 2\omega^2 L^2 - 2L = 0$$

$$R^2 C + 2\omega^2 L^2 C - 2L = 0$$

$$2\omega^2 L^2 C = 2L - R^2 C$$

$$\omega^2 = \frac{2L - R^2 C}{2L^2 C}$$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{2L^2}$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$


$$\omega = \frac{1}{\sqrt{LC}} \left(\sqrt{\frac{1 - R^2 C}{2L}} \right)$$

$$\text{(for } V_c(\text{max.})) \leftarrow \omega_c = \omega_0 \left(\sqrt{\frac{1 - R^2 C}{2L}} \right) \text{ rad/sec}$$

$$\Rightarrow \boxed{f_c = f_0 \sqrt{\frac{1 - R^2 C}{2L}} \text{ Hz}} \quad (f_0 \text{ is frequency at } V_c(\text{max.}))$$

(29)

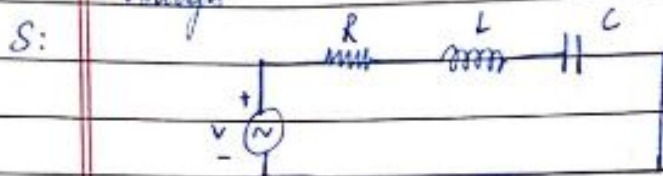- 2) A series RLC circuit has $R = 25 \Omega$, $L = 0.04 \text{ H}$ & $C = 0.01 \mu\text{F}$. Calculate the resonant frequency and also if a 1V source of same frequency as the resonant frequency is applied to the circuit. Calculate the frequencies at which the voltage across 'L' and 'C' are maximum and their respective voltage. [Circuit not given]



$$\rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.04 \times 0.01 \times 10^{-6}}}$$

$$f_0 = 7957.74 \text{ Hz}$$

$$\rightarrow f_c = f_0 \sqrt{\frac{1-R^2C}{2L}} = 7957.74 \sqrt{\frac{1-(25)^2 \times 0.01 \times 10^{-6}}{2 \times 0.04}}$$

$$f_c = 7957.342 \text{ Hz}$$

$$\rightarrow f_L = \frac{f_0}{\sqrt{\frac{1-R^2C}{2L}}} = \frac{f_0}{0.9999} = \frac{7957.74}{0.9999}$$

$$f_L = 7958.05 \text{ Hz}$$

$$\rightarrow V_L = I \cdot X_L \text{ [at Resonance]}$$

$$\Rightarrow V_L = \bar{I}_0 \omega_0 L$$

$$V_L = \frac{V}{R} \omega_0 L = \frac{1}{25} \times 2\pi f_0 \times 0.04$$

$$V_L = \frac{0.04 \times 2\pi \times 7957.74}{25}$$

$$V_L = 79.9999 \text{ V}$$


(30)

$$\rightarrow V_c = I X_c = I_0 \times \frac{1}{\omega_0 C} = \frac{V \times I}{R \omega_0 C}$$

$$V_c = \frac{1 \times 1}{\sqrt{5} \times \pi \times 7957.74 \times 0.01 \times 10^{-6}}$$

$$V_c = 80 \text{ V}$$

• SELECTIVITY AND BANDWIDTH:

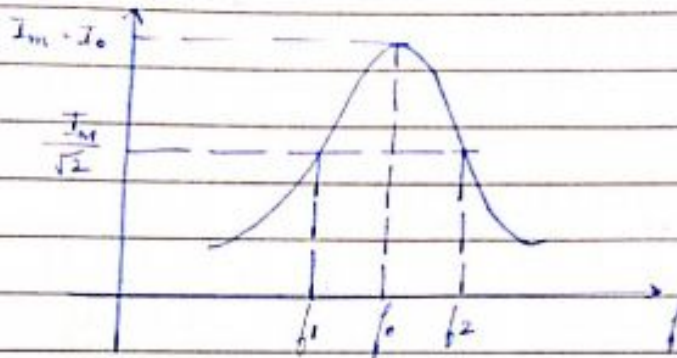

- At resonant frequency, the impedance of RLC circuit is minimum. Hence, the current is maximum.
- As the frequency of the applied voltage deviates on either side of the resonant frequency, the impedance increases and the current decreases. The above figure shows the variation of current with frequency. The frequencies f_1 and f_2 are called half power frequencies or 3Db frequencies.
- The bandwidth, $(f_2 - f_1)$ is called half power bandwidth or 3Db bandwidth.
- SELECTIVITY: Selectivity of a resonant circuit is defined as the ratio of resonant frequency to the bandwidth.

$$\text{Selectivity} = \frac{f_0}{\text{BW}} = \frac{f_0}{f_2 - f_1}$$

(31)

- To prove that the power at frequency f_0 and f_2 is half of the power at resonance.

→ The current in series RLC circuit is:

$$I = \frac{V}{R + j\left(\omega L - \frac{1}{\omega C}\right)} \longrightarrow \textcircled{1}$$

At resonant frequency, $I = I_0 = \frac{V}{R} \longrightarrow \textcircled{2}$

At upper cut-off frequency (f_2)/upper half power frequency:

$$|I_2| = \frac{|I_0|}{\sqrt{2}} = \frac{|V|}{R\sqrt{2}} = \left| \frac{V}{R + jR} \right|$$

↳ Inductive

$$|I_2| = \left| \frac{V}{R + jR} \right| \longrightarrow \textcircled{3}$$

From eq. (1) @ f_2 :

$$I_2 = \frac{V}{R + j\left(\omega_2 L - \frac{1}{\omega_2 C}\right)} \longrightarrow \textcircled{4}$$

Comparing eq. (3) & (4)

$$R = \frac{\omega_2 L - \frac{1}{\omega_2 C}}{\omega_2 C}$$

Similarly, at lower cut-off frequency (f_1),

$$|I_1| = \frac{|I_0|}{\sqrt{2}} = \frac{|V|}{R\sqrt{2}} = \left| \frac{V}{R - jR} \right|$$

$$|I_1| = \left| \frac{V}{R - jR} \right| \longrightarrow \textcircled{5}$$

(32)

From eq. (1) @ f_1 :

$$I_1 = \frac{V}{R + j(\omega_1 L - \frac{1}{\omega_1 C})} \longrightarrow (7)$$

Comparing equations (6) & (7):

$$\boxed{R = \frac{1}{\omega_1 C} - \omega_1 L} \longrightarrow (8)^*$$

→ The current ratio is expressed in decibels as $20 \log_{10} \left(\frac{I_1}{I_0} \right)$

$$\Rightarrow 20 \log_{10} \left(\frac{\frac{I_0}{\sqrt{2}}}{I_0} \right)$$

$$\Rightarrow -3 \text{ dB}$$

→ The power dissipated at the resonant frequency,

$$\boxed{P_0 = I_0^2 R}$$

→ The power dissipated at lower cut-off frequency is

$$P_1 = I_1^2 R$$

$$P_1 = \frac{I_0^2 R}{2}$$

$$\boxed{P_1 = \frac{P_0}{2}}$$

→ Similarly, $\boxed{P_2 = \frac{P_0}{2}}$

Therefore, the power at the frequencies f_1 and f_2 is half of the power at resonance. Hence, they are called as half power frequencies.

• TRANSFER FUNCTION:

A transfer function, $H(j\omega)$ is also known as network function, it is an important tool for finding the frequency response of a circuit.

A transfer function is defined as the ratio of output response $Y(j\omega)$ to the sinusoidal i/p signal $X(j\omega)$.

i.e.,
$$H(j\omega) = \frac{Y(j\omega)}{X(j\omega)}$$


→ The roots of $Y(j\omega) = 0$ are called as zeros of $H(j\omega)$ and are represented as $j\omega = z_1, z_2, \dots$

→ Similarly, the roots of $X(j\omega) = 0$ are called as Poles of $H(j\omega)$ and are represented as $j\omega = p_1, p_2, \dots$

→ To avoid complexity, $(j\omega)$ will be replaced by s while working and then s is replaced back $(j\omega)$ at the end.

i.e.,
$$H(s) = \frac{Y(s)}{X(s)}$$

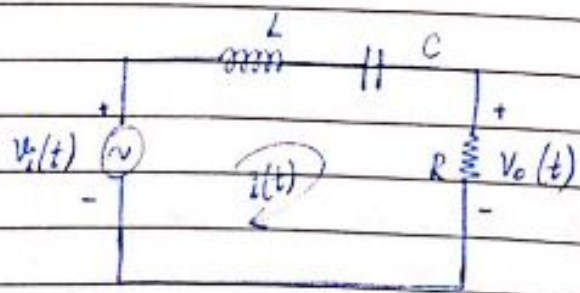• TRANSFER FUNCTION OF SERIES RESONANT CIRCUIT:




$$H(j\omega) = \frac{Y(j\omega)}{X(j\omega)}$$


$$o(j\omega) = 10^{-1} \cos^{-1} \left(\frac{z}{x} \right)$$

24

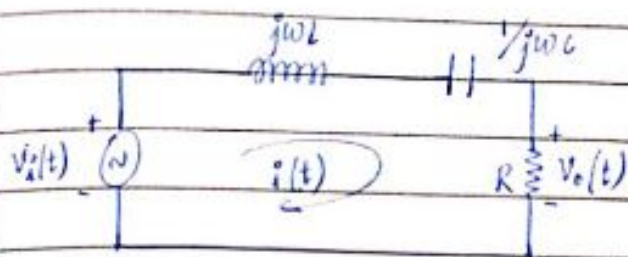Consider the series resonant circuit as shown:



→ In s domain,

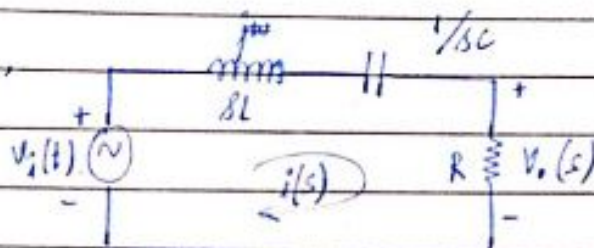

From this circuit,

$$i(s) = \frac{V_i(s)}{R + (sL + \frac{1}{sC})}$$

$$\rightarrow V_o(s) = R i(s)$$

$$V_o(s) = \frac{V_i(s) R}{R + sL + \frac{1}{sC}}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{R}{R + sL + \frac{1}{sC}}$$

$$\begin{aligned} \Rightarrow H(s) &= \frac{V_o(s)}{V_i(s)} = \frac{R}{R + sL + \frac{1}{sC}} \\ &= \frac{R s C}{R s C + L C s^2 + 1} \\ &= \frac{R s C}{L C (s^2 + (\frac{R}{L})s + \frac{1}{L C})} \end{aligned}$$

$$H(s) = \frac{(\frac{R}{L})s}{s^2 + (\frac{R}{L})s + \frac{1}{L C}}$$

Substituting s by $j\omega$


$$\Rightarrow H(j\omega) = \frac{(R/L)j\omega}{(j\omega)^2 + (R/L)j\omega + 1/LC} = \frac{(R/L)j\omega}{\left(\frac{1}{LC} - \omega^2\right) + j\left(\frac{R}{L}\right)\omega}$$

Taking the magnitude,

$$|H(j\omega)| = \frac{(R/L)\omega}{\sqrt{\left(\frac{1}{LC} - \omega^2\right)^2 + \left(\frac{R}{L}\omega\right)^2}} \quad \text{--- } \textcircled{1}$$

$X^2 \qquad Y^2$
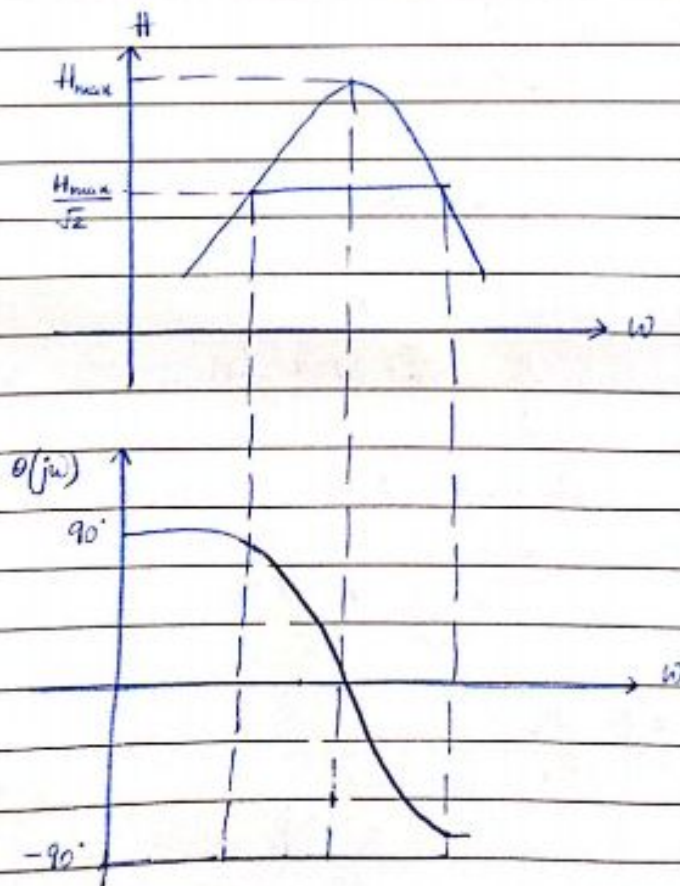
$$\rightarrow \theta(j\omega) = \angle H(j\omega) = 90 - \tan^{-1}\left(\frac{\frac{R}{L}\omega}{\frac{1}{LC} - \omega^2}\right) \rightarrow 90 - \tan^{-1}\left(\frac{Y}{X}\right)$$



(3)

$$H_{max} = 1$$

$$H_{max} = |H(j\omega)|_{\omega=\omega_0}$$

→ Taking $\omega = \omega_0$ in eq. (2) $\left[\omega = \omega_0 = \frac{1}{\sqrt{LC}} \right]$

$$\begin{aligned} |H(j\omega)| &= \frac{R \omega_0 \times 1}{L \sqrt{LC}} \\ &= \frac{R \times 1}{L \sqrt{LC}} \times \frac{1}{\sqrt{\left(\frac{1}{LC} - \frac{1}{LC}\right)^2 + \left(\frac{1}{\sqrt{LC}} \times R\right)^2}} \\ &= \frac{R \times 1}{L \sqrt{LC}} \times \frac{1}{\sqrt{0 + \frac{R^2}{L^2} \left(\frac{1}{LC}\right)^2}} \end{aligned}$$

$$= \frac{R \times 1}{L \sqrt{LC}} \times \frac{1}{\frac{R \times 1}{L \sqrt{LC}}}$$

$$= 1$$

$$\therefore H_{max} = 1$$

- EXPRESSION FOR CUT-OFF FREQUENCY, BANDWIDTH AND QUALITY FACTOR.

Let (ω_c) denote the angular cut-off frequency at \pm half power points in the frequency response.

We know that, at resonance,

$$I_0 = \frac{V}{R}$$

$$\frac{I_0}{\sqrt{2}} = \frac{V_0}{R\sqrt{2}} \quad \text{--- (1)}$$

We know that,

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

(37)

$$\Rightarrow |Z| = \sqrt{R^2 + \left(\omega_c L - \frac{1}{\omega_c C}\right)^2}$$

But,

$$\frac{I_0}{\sqrt{2}} = \frac{V}{|Z|} = \frac{V}{\sqrt{R^2 + \left(\omega_c L - \frac{1}{\omega_c C}\right)^2}} \quad \text{--- (2)}$$

Comparing eq. (1) and (2):

$$\sqrt{2} R = \sqrt{R^2 + \left(\omega_c L - \frac{1}{\omega_c C}\right)^2}$$

Squaring on both sides.

$$2R^2 = R^2 + \left(\omega_c L - \frac{1}{\omega_c C}\right)^2$$

$$R^2 = \left(\omega_c L - \frac{1}{\omega_c C}\right)^2$$

$$\omega_c R = \omega_c^2 LC - 1$$

$$\omega_c^2 LC - \omega_c R - 1 = 0$$

Taking square root,

$$\pm R = \left(\omega_c L - \frac{1}{\omega_c C}\right)$$

$$\omega_c^2 L - 1 = \pm \omega_c R$$

$$L\omega_c^2 \pm \omega_c R - 1 = 0$$

Thus, we have,

$$\omega_c = \frac{\pm R \pm \sqrt{R^2 + \frac{4L}{C}}}{2L}$$

$$\omega_c = \frac{\pm R \pm \sqrt{\frac{(R)^2 + 1}{(2L)^2 LC}}}{2L}$$

(3)

→ From the above equation, we can obtain '4' solutions, out of which only 2 are positive:

$$\omega_{c1} = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \longrightarrow (3)$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \longrightarrow (4)$$

$$\rightarrow f_{c1} = \frac{1}{2\pi} \left[\frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right]$$

$$f_{c2} = \frac{1}{2\pi} \left[\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right]$$

→ Usually, $\left(\frac{R}{2L}\right)$ will be a small value. Therefore, $\left(\frac{R}{2L}\right)^2$ will be further small. Hence, it may be neglected.

Thus,

$$f_{c1} = \frac{1}{2\pi} \left[\frac{-R}{2L} + \sqrt{\frac{1}{LC}} \right]$$

$$f_{c2} = \frac{1}{2\pi} \left[\frac{R}{2L} + \sqrt{\frac{1}{LC}} \right]$$

$$\rightarrow \text{B.W} = f_{c2} - f_{c1} = \frac{1}{2\pi} \left[\frac{+R}{2L} + \sqrt{\frac{1}{LC}} + \frac{R}{2L} - \sqrt{\frac{1}{LC}} \right]$$

$$\boxed{\text{B.W} = \frac{R}{2\pi L}}$$

(39)

→ Quality factor (Q),

$$Q = \frac{f_0}{\text{BW}} = \frac{\omega_0 L}{R}$$

$$Q = \frac{\omega_0 L}{R}$$

• RESONANT FREQUENCY IN TERMS OF HALF POWER FREQUENCIES:

Prove that the resonant frequency is the geometric mean of the two half power frequencies.

$$f_0 = \sqrt{f_1 f_2}$$

PROOF: We know that, @ ω_1 , $R = \frac{1}{\omega_1 C} - \omega_1 L$ → (1)

Similarly, @ ω_2 , $-R = \frac{1}{\omega_2 C} - \omega_2 L$ → (2)

$$R = \omega_2 L - \frac{1}{\omega_2 C} \rightarrow (3)$$

Equating (1) & (3):

$$\frac{1}{\omega_1 C} - \omega_1 L = \omega_2 L - \frac{1}{\omega_2 C}$$

$$\frac{1}{\omega_1 C} + \frac{1}{\omega_2 C} = L(\omega_1 + \omega_2)$$

$$\frac{L(\omega_2 + \omega_1)}{C \omega_1 \omega_2} = L(\omega_1 + \omega_2)$$

$$\frac{1}{\omega_1 \omega_2} = LC$$

$$\Rightarrow \omega_1 \omega_2 = \frac{1}{LC}$$

40

classmate

Date _____

Page _____

Taking square root, we have:

$$\sqrt{\omega_1 \omega_2} = \frac{1}{\sqrt{LC}} = \omega_0$$


$$\sqrt{2\pi f_1 \times 2\pi f_2} = 2\pi f_0$$

$$\Rightarrow 2\pi f_0 = 2\pi \sqrt{f_1 f_2}$$

$$\therefore \boxed{f_0 = \sqrt{f_1 f_2}}$$

1) Determine the equation for transfer function for the given circuit diagram.

H.W

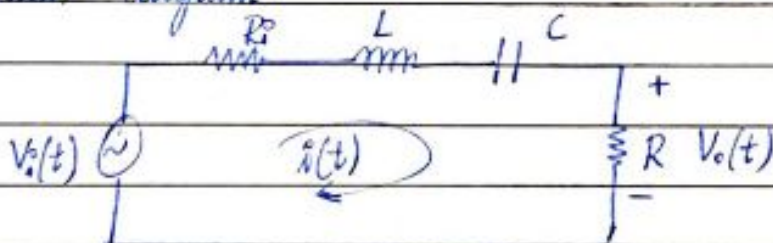

S:


(+1)

DERIVATION

12-11-19

1) For the given circuit, show that $|V_o|_{max} = \frac{Q|V_s|}{\sqrt{1 - \frac{1}{4Q^2}}}$, at resonance.

S:

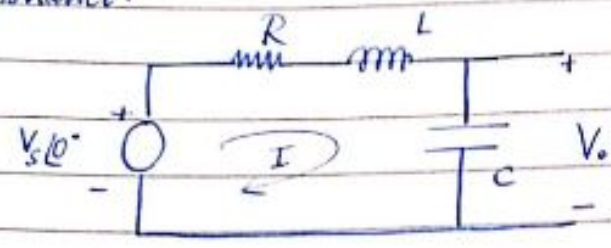

i) $|V_o| = ?$ — (1)

ii) $\frac{\partial |V_o|}{\partial \omega} = 0$

$\left(\frac{\partial}{\partial \omega} \right)_{\omega_{max}}$

iii) Subs. in eq. (1)

$V_o = I(-jX_c)$ $\because V_o = 'V'$ across capacitor

$V_o = \frac{V_s / 0}{R + j(\omega L - \frac{1}{\omega C})} \times \frac{-j}{\omega C}$

$|V_o| = \frac{|V_s|}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \times \frac{1}{\omega C}$ $\left(\frac{1}{\sqrt{(\omega C)^2}} \right)$ — (2)

$|V_o| = \frac{|V_s|}{\sqrt{(\omega^2 LC - 1)^2 + (\omega RC)^2}}$

$|V_o| = \frac{|V_s|}{\sqrt{1 + \omega^4 L^2 C^2 - 2\omega^2 LC + \omega^2 R^2 C^2}}$ — X

$|V_o| = \frac{|V_s|}{\sqrt{X}}$

Differentiate partially w.r.t 'w'.

\rightarrow this is constant \rightarrow can't be zero.

$\frac{\partial |V_o|}{\partial \omega} = |V_s| \left[\frac{-1}{2} X^{-3/2} \frac{\partial X}{\partial \omega} \right] = 0$

$\frac{\partial X}{\partial \omega} = \frac{\partial (1 + \omega^4 L^2 C^2 - 2\omega^2 LC + \omega^2 R^2 C^2)}{\partial \omega}$

$= 4\omega^3 L^2 C^2 - 4\omega LC + 2\omega R^2 C^2$

$\Rightarrow 4\omega^3 L^2 C^2 - 4\omega LC + 2\omega R^2 C^2 = 0$

$2\omega C [2\omega^2 L^2 C - 2L + R^2 C] = 0$

(72)

$$2\omega^2 L^2 C - 2L + R^2 C = 0$$

$$2\omega^2 L^2 C = 2L - R^2 C$$

$$\omega^2 = \frac{2L - R^2 C}{2L^2 C} = \frac{1}{LC} \left[\frac{1 - R^2 C}{2L} \right] \rightarrow (2)$$

$$\omega^2 = \frac{1}{LC} - \frac{1}{2(L)^2} \left. \right\} \times$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{1}{2(L)^2}} \left. \right\} \times$$

We know that,

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\sqrt{LC}} \times \frac{L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q^2 = \frac{L}{R^2 C}$$

$$(2) \Rightarrow \omega^2 = \frac{1}{LC} \left[1 - \frac{1}{2Q^2} \right]$$

$$\omega = \sqrt{\frac{1}{LC} \left(1 - \frac{1}{2Q^2} \right)} = \frac{1}{\sqrt{LC}} \sqrt{\left(1 - \frac{1}{2Q^2} \right)}$$

$$\omega = \omega_0 \sqrt{\left(1 - \frac{1}{2Q^2} \right)}$$

$$\Rightarrow \boxed{\omega_{max} = \omega_0 \sqrt{\left(1 - \frac{1}{2Q^2} \right)}} \rightarrow (3)$$

$\rightarrow \omega_3 \left[\frac{\partial |V_o|}{\partial \omega} = 0 \right]$ is condition for ω_{max}

Substituting for ω_{max} in eq. (1), we have:

$$|V_o|_{max} = \frac{|V_s|}{\sqrt{(\omega_{max}^2 LC - 1)^2 + (\omega_{max} RC)^2}} \rightarrow (4)$$

$$\Rightarrow (\omega_{max} RC)^2 = \left(\omega_0 \sqrt{\frac{1 - 1}{2Q^2}} RC \right)^2 = (\omega_0 RC)^2 \times \left(\frac{1 - 1}{2Q^2} \right)$$

$$= \frac{1 \times R^2 C^2}{LC} \left(\frac{1 - 1}{2Q^2} \right) = \frac{R^2 C}{L} \left(\frac{1 - 1}{2Q^2} \right)$$

$$\rightarrow (W_{max RC})^2 = \frac{1}{Q^2} \left[1 - \frac{1}{\alpha Q^2} \right]$$

$$= \frac{1}{Q^2} - \frac{1}{\alpha Q^4}$$

$$\rightarrow (W_{max LC} - 1)^2 = \left[W_0^2 \left(\frac{1}{\alpha Q^2} \right) LC - 1 \right]^2$$

$$= \left(\frac{-1}{\alpha Q^2} \right)^2$$

$$= \frac{1}{4Q^4}$$

Substitute in eq. (4)


$$|V_o|_{max} = \frac{|V_s|}{\sqrt{\frac{1}{4Q^4} + \frac{1}{Q^2} - \frac{1}{\alpha Q^2}}} = \frac{|V_s|}{\sqrt{\frac{1}{Q^2} - \frac{1}{4Q^4}}}$$

$$|V_o|_{max} = \frac{|V_s|}{Q \sqrt{1 - \frac{1}{4Q^2}}}$$

$$\boxed{|V_o|_{max} = \frac{Q |V_s|}{\sqrt{1 - \frac{1}{4Q^2}}}} \quad \text{at resonance.}$$

Hence, proved.

2) For the given circuit, find ω_0 , Q_0 & $|V_o|_{max}$.

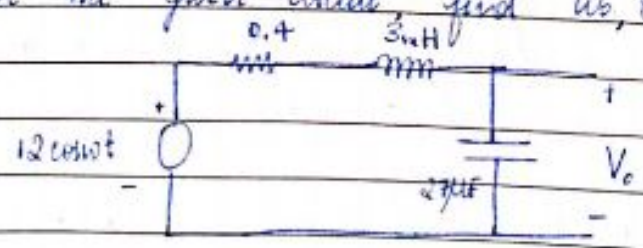

S:

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{3 \times 10^{-3} \times 27 \times 10^{-6}}} = \frac{1}{0.9 \times 10^{-4}} = 3.513 \text{ k rad/s}$$

(4)

$$V_s = \frac{V_m}{\sqrt{2}} = V_{rms}, \quad V_m = 12$$

$$V_s = \frac{12}{\sqrt{2}} = 8.48$$

$$|V_o|_{max} = |V_s| Q$$

$$\sqrt{1 - \frac{1}{4Q^2}}$$

$$Q_o = \frac{L}{R^2 C} = \frac{3 \times 10^{-3}}{(0.4)^2 \times 27 \times 10^{-6}}$$


$$Q_o = \frac{\omega_o L}{R} = \frac{3513 \times 3 \times 10^{-3}}{0.4}$$

$$Q_o = 26.35$$

$$|V_o|_{max} = \frac{8.48 \times 26.35}{\sqrt{1 - \frac{1}{4(26.35)^2}}} = \frac{223.448}{0.9998}$$

$$|V_o|_{max} = 223.5 \text{ V}$$

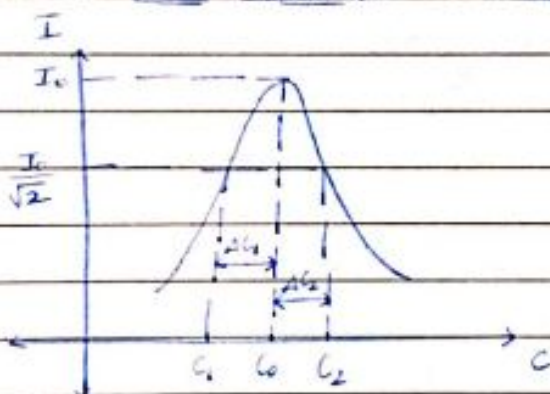• SELECTIVITY ~~A~~ WITH VARIABLE CAPACITANCE:



- let C_o be the capacitance at resonance.
- C_1, C_2 are the values of capacitance at lower and upper cut-off frequencies respectively.
- we know that,

$$\omega_1 L_1 - \frac{1}{\omega_1 C_1} = -R \quad [\text{from geometric mean of } f]$$

$$\omega L_2 - \frac{1}{\omega C_2} = R$$

Here L is constant Thus it's not ωL_2 ,
it's ωL_1

(45)

Here, $L_1 = L_2 = L$.

$$\Rightarrow \boxed{\omega L - \frac{1}{\omega C_1} = -R} \rightarrow (1)$$

$$\boxed{\omega L - \frac{1}{\omega C_2} = R} \rightarrow (2)$$

From equation (1) and (2), we have,

$$(2) - (1) \Rightarrow \frac{1}{\omega C_1} - \frac{1}{\omega C_2} = 2R$$

$$\boxed{\frac{C_2 - C_1}{\omega C_1 C_2} = 2R} \rightarrow (3)$$

$$\text{But } C_2 = C_0 + \Delta C_2 \approx C_0$$

$$C_1 = C_0 - \Delta C_1 \approx C_0$$

$$\Rightarrow C_1 C_2 = C_0^2 \rightarrow \text{only for denominator}$$

$$(3) \Rightarrow \frac{C_2 - C_1}{\omega C_0^2} = 2R$$

At resonance, net reactance = 0

$$\Rightarrow \frac{1}{\omega C_0} = \omega L$$


$$\Rightarrow \frac{C_2 - C_1}{C_0} = \frac{2R}{\omega L}$$

$$\frac{C_0}{C_2 - C_1} = \frac{\omega L}{2R} \quad [\text{reciprocal}]$$

$$\boxed{\frac{C_0}{C_2 - C_1} = Q} \quad \left[\because \frac{\omega L}{R} = Q \right]$$

where $\frac{C_0}{C_2 - C_1}$ gives the selectivity of the series resonant circuit with variable capacitance.

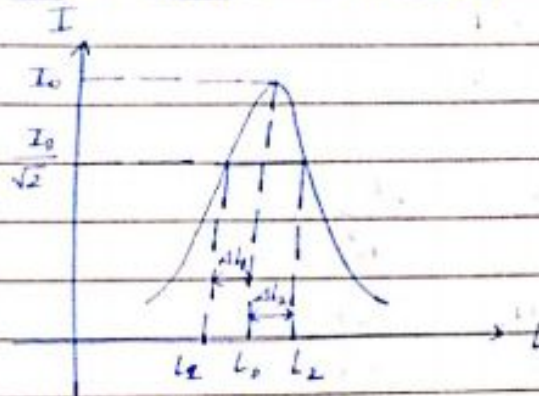• SELECTIVITY WITH VARIABLE INDUCTANCE: (n.w) $\frac{I_0}{I_2 - I_1} = Q$



→ Let L_0 be the impedance at resonance.

We know that,

$$\omega L_1 - \frac{1}{\omega C_1} = -R$$

$$\omega L_2 - \frac{1}{\omega C_2} = R$$

Here, $C_1 = C_2 = C$

$$\Rightarrow \omega L_1 - \frac{1}{\omega C} = -R \quad \text{--- (1)}$$

$$\omega L_2 - \frac{1}{\omega C} = R \quad \text{--- (2)}$$

$$L_2 - L_1 = 2R$$

$$L_0 = \frac{\omega L_0}{\omega}$$

$$L_0 = \frac{\omega L_0}{\omega}$$

$$\frac{L_2 - L_1}{L_0} = \frac{2R}{\omega L_0}$$

$$(2) - (1) \Rightarrow \omega L_2 - \omega L_1 = 2R$$

$$L_2 - L_1 = \frac{2R}{\omega}$$

ω

$$L_1 L_2 (L_2 - L_1) = \frac{2R(L_1 L_2)}{\omega}$$

to

$$L_0 = \frac{\omega L_0}{\omega}$$

$$\frac{L_2 - L_1}{L_0} = \frac{2R}{\omega L_0}$$

$$\left\{ \text{Since } Q = \frac{\omega L_0}{R} \right\}$$

~~$L_1 L_2 (L_2 - L_1)$ on both sides~~

① SERIES $Z = X + jY$
 $Y = 0$
 $\omega_j = ?$
 $f = ?$

② Parallel
 $Y = \alpha + j\beta$ (Admittance)
 $\beta = 0$
 $\omega_j = ?$
 $f = ?$


99

• PARALLEL RESONANT CIRCUIT : [ANTI RESONANT CIRCUIT]

- TYPES:
- 1) Dual of series resonant circuit
 - 2) General case RL-RC parallel circuit
 - 3) Practical C-RL parallel resonant circuit.

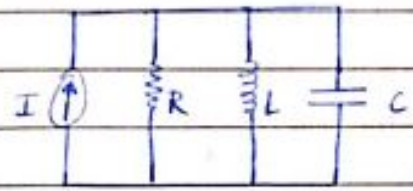1) DUAL OF SERIES RESONANT CIRCUIT:

Duality means opposite \Rightarrow [Current becomes voltage, & vice versa.
 Series becomes parallel & vice versa.]



From the circuit, the net admittance is:

$$Y = Y_R + Y_L + Y_C = \frac{1}{R} + \frac{1}{j\omega L} + \frac{1}{j\omega C}$$

$$Y = \frac{1}{R} - \frac{j}{\omega L} + j\omega C$$

$$Y = \frac{1}{R} + j \left(\omega C - \frac{1}{\omega L} \right)$$

At resonance, imaginary part = 0

$$\Rightarrow \omega C - \frac{1}{\omega L} = 0$$

$$\omega C = \frac{1}{\omega L}$$


$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

(49)

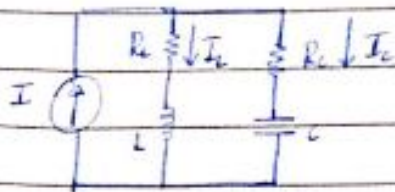x) GENERAL CASE R-L - RC parallel CIRCUIT:

The total admittance is:

$$Y = Y_{RL} + Y_{RC} \longrightarrow \textcircled{1}$$

$$\rightarrow Y_{RL} = \frac{1}{R_L + j\omega L} \times \frac{R_L - j\omega L}{R_L - j\omega L} = \frac{R_L - j\omega L}{R_L^2 - (j\omega L)^2}$$

$$Y_{RL} = \frac{R_L - j\omega L}{R_L^2 + \omega^2 L^2}$$

$$Y_{RL} = \frac{R_L}{R_L^2 + \omega^2 L^2} - j \frac{\omega L}{R_L^2 + \omega^2 L^2} \longrightarrow \textcircled{2}$$

$$\rightarrow Y_{RC} = \frac{1}{R_C + \frac{1}{j\omega C}} = \frac{1}{R_C - \frac{j}{\omega C}} = \frac{\omega C}{R_C \omega C - j}$$

$$Y_{RC} = \frac{\omega C}{R_C \omega C - j} \times \frac{(R_C \omega C + j)}{(R_C \omega C + j)} = \frac{R_C \omega^2 C^2 + j\omega C}{(R_C \omega C)^2 - 1}$$

$$Y_{RC} = \frac{1}{R_C - \frac{j}{\omega C}} \cdot \frac{(R_C + \frac{j}{\omega C})}{(R_C + \frac{j}{\omega C})}$$

$$Y_{RC} = \frac{R_C \omega^2 C^2}{(R_C \omega C)^2 - 1} + j \frac{\omega C}{(R_C \omega C)^2 - 1} \longrightarrow \textcircled{3}$$

Using $\textcircled{2}$ & $\textcircled{3}$ in $\textcircled{1}$; equating imaginary part to zero, we have,

$$\frac{\omega L}{R_L^2 + \omega^2 L^2} - \frac{1/\omega C}{R_C^2 + \frac{1}{\omega^2 C^2}} = 0$$

$$\frac{\omega L}{R_L^2 + \omega^2 L^2} - \frac{\omega C}{R_C^2 \omega^2 C^2 + 1} = 0$$

$$\omega L R_c^2 \omega^2 C^2 + \omega L - [\omega C R_c^2 + \omega^3 C L^2] = 0$$

$$\omega^3 R_c^2 L C^2 + \omega L - \omega C R_c^2 - \omega^3 C L^2 = 0$$

$$\omega [\omega^2 R_c^2 L C^2 + L - C R_c^2 - \omega^2 C L^2] = 0$$

$$\omega^2 [R_c^2 L C^2 - C L^2] = R_c^2 C - L$$

$$\boxed{\omega^2 = \frac{R_c^2 C - L}{R_c^2 L C^2 - C L^2}}$$


$$\omega = \sqrt{\frac{R_c^2 C - L}{R_c^2 L C^2 - C L^2}}$$

$$\omega = \sqrt{\frac{R_c^2 C - L}{L C (R_c^2 C - L)}} = \frac{1}{\sqrt{L C}} \sqrt{\frac{R_c^2 C - L}{R_c^2 C - L}}$$

$$\boxed{\omega = \omega_0 \sqrt{\frac{R_c^2 - 1/C}{R_c^2 - 1/C}}}$$

$$\Rightarrow \underbrace{f = f_0 \sqrt{\frac{R_c^2 - 1/C}{R_c^2 - 1/C}}}_{\text{found in 1st derivation}} \quad \textcircled{a} \quad \underbrace{f_p = f_0 \sqrt{\frac{R_c^2 - 1/C}{R_c^2 - 1/C}}}_{\text{parallel circuit}}$$

3) PRACTICAL C-RL PARALLEL CIRCUIT:

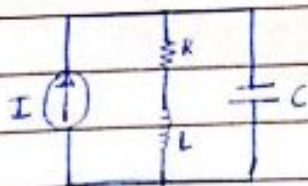

The total admittance is:

$$Y = Y_{Rc} + Y_C$$

$$Y = \frac{1}{R + j\omega L} + \frac{1}{j\omega C}$$

$$Y = \frac{1}{R + j\omega L} - \frac{j\omega L}{R^2 + \omega^2 L^2} + j\omega C$$

from previous derivation.

(51)

Equating imaginary part to zero.

$$\omega C - \frac{\omega L}{R^2 + \omega^2 L^2} = 0$$

$$\omega C = \frac{\omega L}{R^2 + \omega^2 L^2}$$

$$R^2 C + \omega^2 L^2 C = L$$

$$\omega^2 L^2 C = L - R^2 C$$

$$\omega^2 = \frac{L - R^2 C}{L^2 C}$$

$$\omega^2 = \frac{1}{LC} - \left(\frac{R}{L}\right)^2$$

$$\omega = \sqrt{\frac{1}{LC} - \left(\frac{R}{L}\right)^2}$$

$$\omega = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{R^2 C}{L}}$$

$$\omega = \omega_0 \sqrt{1 - \frac{R^2 C}{L}}$$

$$f = f_0 \sqrt{1 - \frac{R^2 C}{L}}$$

(a)

$$f_p = f_c \sqrt{1 - \frac{R^2 C}{L}}$$

• IMPEDENCE OF ANTI-RESONANT CIRCUIT [DYNAMIC RESISTANCE]

For case 3),

$$Y = \frac{R}{R^2 + L^2 \omega^2} + j \left[\frac{\omega C}{R^2 + L^2 \omega^2} - \frac{\omega L}{R^2 + L^2 \omega^2} \right]$$

At resonance, imaginary part is zero.

$$Y_0 = \frac{R}{R^2 + L^2 \omega^2}$$

$$Y_0 = \frac{R}{\frac{R^2 + L^2}{L^2 C^2}} = \frac{R}{R^2 + \frac{L}{C}}$$

∵ $R^2 \ll \frac{L}{C}$, then,

$$Y_0 = \frac{R}{L/C} = \frac{RC}{L}$$

$$\boxed{Z_0 = \frac{L}{RC}}$$

—x—END—x—

(1)

13-11-19

MODULE - 4

LAPLACE TRANSFORMS

DEFINITION:

$$F(s) = L\{f(t)\} = \int_0^{\infty} f(t) e^{-st} dt.$$

• INVERSE LAPLACE:



$$f(t) = L^{-1}\{F(s)\} = \frac{1}{2\pi j} \int_{\sigma-j\infty}^{\sigma+j\infty} F(s) e^{st} ds$$

• SINGULARITY FUNCTIONS:

- 1) Unit-step Function
- 2) Ramp
- 3) Delta

1) UNIT STEP FUNCTION:


$$\rightarrow u(t) = \begin{cases} 1 & \text{for } t \geq 0 \\ 0 & \text{for } t < 0 \end{cases}$$

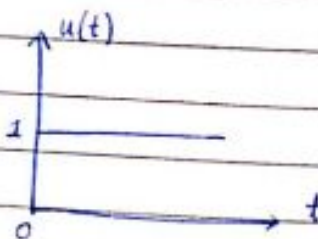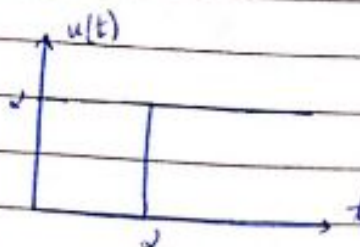→ $2u(t-2)$ 

②

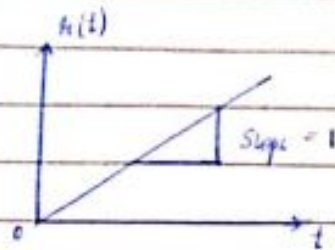2) RAMP FUNCTION:

$$R(t) = \begin{cases} t & , t \geq 0 \\ 0 & , t < 0 \end{cases}$$




$$\text{Slope} = \tan \theta = \frac{y}{x} = \frac{y_2 - y_1}{x_2 - x_1}$$

$$\begin{aligned} \rightarrow \delta(t) &= \text{slope} \times (t) \times u(t) \\ &= \text{slope} \times (t) \times u(t) \quad (\because u(t) = 1 \text{ for } t > 0) \end{aligned}$$

* Slope = +ve

Slope = -ve


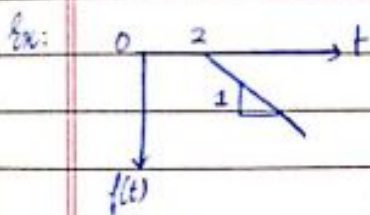
$$\rightarrow \delta(t-2) = \text{slope} \times (t-2) \times u(t-2)$$



$$f(t) = -1 \times (t-2)$$

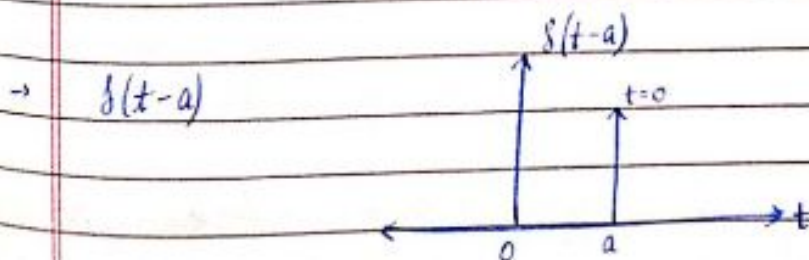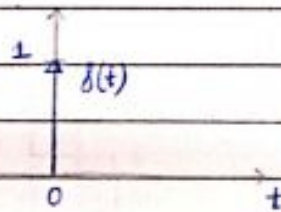3) DELTA FUNCTION:


$$\delta(t) = \begin{cases} 1 & , t = 0 \\ 0 & , t \neq 0 \end{cases}$$



3

• EXPRESS the given waveforms in terms of $u(t)$ and $R(t)$


1)

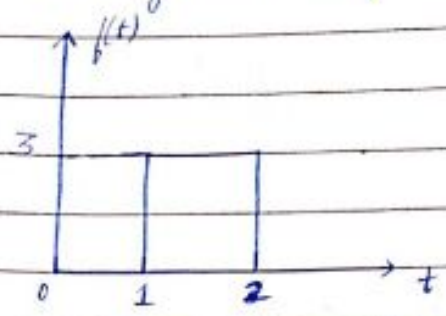

$$f(t) = 3u(t-1) - 3u(t-2)$$

↑ rise ↓ fall

2)

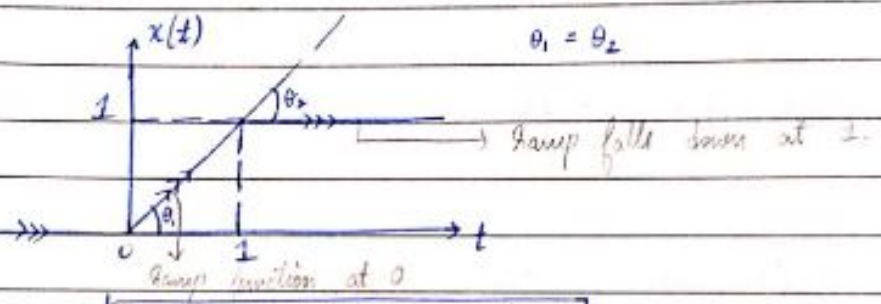


$$x(t) = 1R(t) - 1R(t-1)$$

$$x(t) = 1 \cdot t \cdot u(t) - 1 \cdot (t-1) u(t-1)$$

[∵ $R(t) = \text{Slope} \times t + u(t)$]

3)

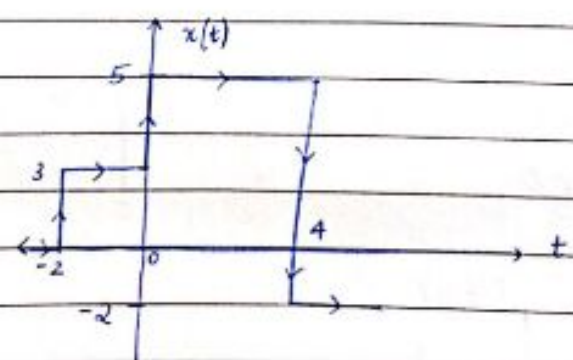


$$x(t) = 3u(t+2) + 2u(t) - 5u(t-4) - 2u(t-4)$$

$$\Rightarrow x(t) = 3u(t+2) + 2u(t) - 7u(t-4)$$

④

1)

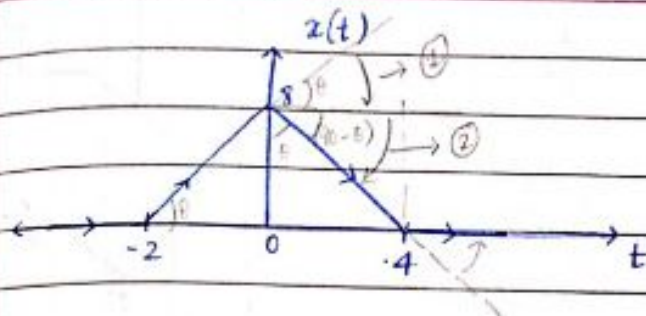

$$(0, 8), (-2, 0) \rightarrow \frac{8-0}{0-(-2)} = 4$$

$$(0, 8), (4, 0) \rightarrow \frac{8-0}{0-4} = -2$$

$$x(t) = 4r(t+2) - 2r(t-4)$$

Starting point of (1)

$$x(t) = 4r(t+2) - 4r(t) - 2r(t) + 2r(t-4)$$

Starting point of (2)

$$\Rightarrow x(t) = 4r(t+2) - 6r(t) + 2r(t-4)$$

⑤





$$x(t) = 4(t+2)u(t+2) - 6tu(t) + 2(t-4)u(t-4)$$

→ Always just consider starting point.


4-11-19

Function $f(t)$	Laplace Transform $F(s)$	WAVEFORM
1) $u(t)$ [Unit Step function]	$\frac{1}{s}$	
2) $Au(t)$	$\frac{A}{s}$	
3) Delayed unit step $u(t-T)$	$\frac{e^{-Ts}}{s}$	
4) Ramp input, $r(t) = tu(t)$	$\frac{1}{s^2}$	

5

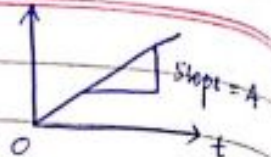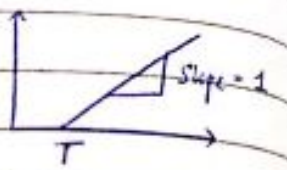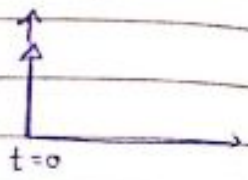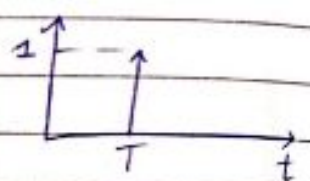5)	$A t u(t)$	$\frac{A}{s^2}$	
6)	Delayed unit ramp, $g(t-T) = (t-T) u(t-T)$	$\frac{e^{-Ts}}{s^2}$	
7)	Delta, $\delta(t)$ [Unit impulse]	1	
8)	Delayed unit impulse $\delta(t-T)$	e^{-Ts}	

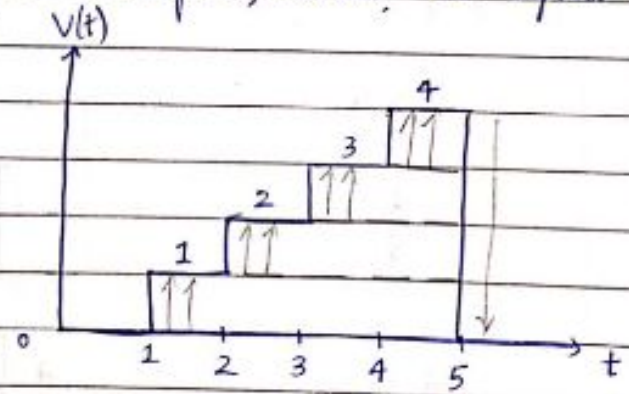
1) For the given waveform, obtain the Laplace transform.



$$v(t) = u(t-1) + u(t-2) + u(t-3) + u(t-4) - 4u(t-5)$$

$$V(s) = \frac{e^{-s}}{s} + \frac{e^{-2s}}{s} + \frac{e^{-3s}}{s} + \frac{e^{-4s}}{s} - \frac{4e^{-5s}}{s}$$

⑥

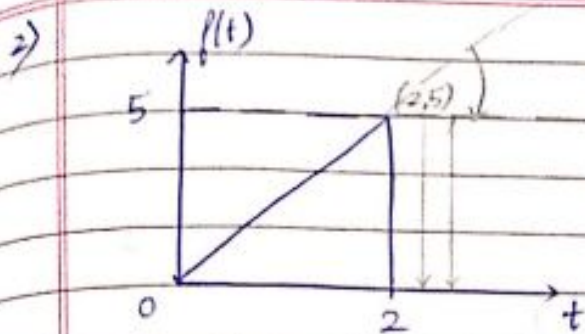

S:

$$f(t) = \frac{5}{2} \mathcal{R}(t) - \frac{5}{2} \mathcal{R}(t-2) - 5u(t-2)$$

$$f(t) = \frac{5}{2s^2} - \frac{5}{2} e^{-2s} - \frac{5e^{-2s}}{s}$$

$$f(t) = \frac{5(1 - e^{-2t})}{2s^2} - \frac{5e^{-2t}}{s}$$

⑦

3) $f(t) = x(t) \times g(t)$ → giving pulse.

$$g(t) = u(t) - u(t-2) \quad \text{[The window from } 0 \rightarrow 2]$$

$$y = x(t) = mx + c = \frac{5}{2}t + 0$$

$$x(t) = \frac{5t}{2}$$


$$\textcircled{1} \Rightarrow f(t) = \frac{5t}{2} \times [u(t) - u(t-2)]$$

$$= \frac{5t}{2} u(t) - \frac{5t}{2} u(t-2)$$

$$= \frac{5t}{2} u(t) - \frac{5}{2} (t-2+2) u(t-2) \quad \text{[All } t \text{ subtract } 2 \text{ to } t]$$

$$f(t) = \frac{5t}{2} u(t) - \frac{5}{2} (t-2) u(t-2) - 5u(t-2)$$

3)

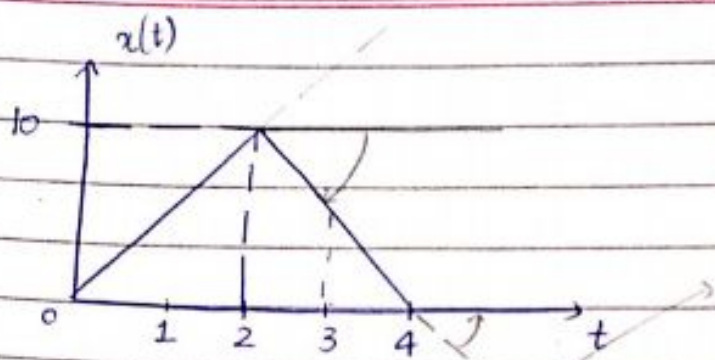

$$\text{Slope} = \frac{10-0}{4-2} = \frac{10}{2}$$


$$x(t) = \frac{10}{2} r(t) - \frac{10}{2} r(t-2) - \frac{10}{2} r(t-2) + \frac{10}{2} r(t-4)$$

$$x(t) = 5r(t) - 10r(t-2) + 5r(t-4)$$

$$x(t) = \frac{5}{s^2} - \frac{10e^{-2s}}{s^2} + \frac{5e^{-4s}}{s^2}$$

$$x(t) = \frac{5 - 10e^{-2s} + 5e^{-4s}}{s^2}$$

* 4)

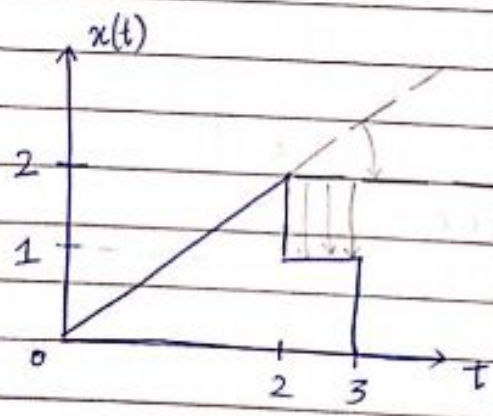

$$x(t) = \frac{2}{2} r(t) - \frac{2}{2} r(t-2) - 1u(t-2) - 1u(t-3)$$

$$x(t) = r(t) - r(t-2) - u(t-2) - u(t-3)$$

$$x(t) = \frac{1}{s^2} - \frac{e^{-2s}}{s^2} - \frac{e^{-2s}}{s} - \frac{e^{-3s}}{s}$$

②

⇒ Laplace transform of PERIODIC FUNCTION

Consider a periodic function of time period, T satisfying the condition,

$$f(t + nT) = f(t)$$



where, n is a positive or negative integer.

→ Laplace transform of such a periodic function is given by

$$F(s) = \frac{F_1(s)}{1 - e^{-sT}}$$

→ $F_1(s)$ is the Laplace transform of first cycle of the periodic function.

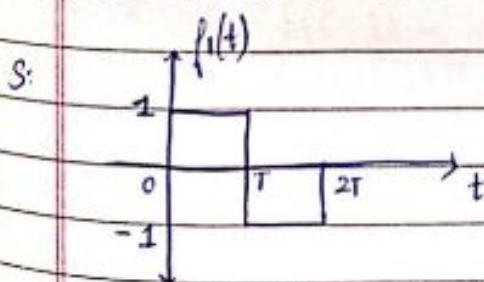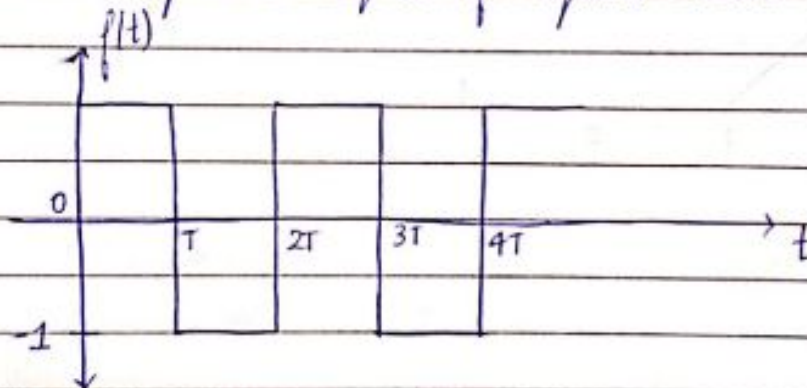1) Obtain the Laplace transform of square wave train



$$f_1(t) = u(t) - 2u(t-T) + u(t-2T)$$

$$f_1(s) = \frac{1}{s} - \frac{2e^{-Ts}}{s} + \frac{e^{-2Ts}}{s}$$

From the formula, $F(s) = \frac{F_1(s)}{1 - e^{-sT}}$


$$\text{Here, } T = 2T$$

9


$$F(s) = \frac{1}{s} - \frac{2e^{-Ts}}{s} + \frac{e^{-2Ts}}{s}$$

$$F(s) = \frac{1 - 2e^{-Ts} + e^{-2Ts}}{s(1 - e^{-2Ts})}$$

2)

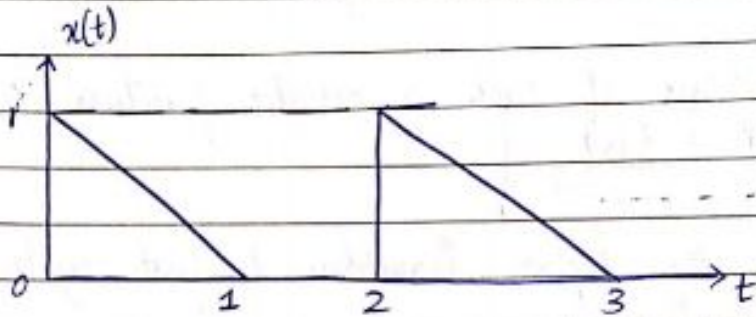

S:

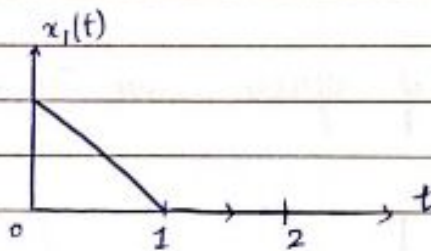

$$x_1(t) = y(t) \cdot g(t) \rightarrow \text{①}$$

$$y(t) = mx + c$$

$$= \frac{-1}{1}x + 1$$

$$g(t) = u(t) - u(t-1)$$

its 'x' axis
dead after 1

$$y(t) = -(t-1)$$

$$x_1(t) = -(t-1)[u(t) - u(t-1)]$$

$$x_1(t) = +u(t) - t u(t) + (t-1)u(t-1)$$

$$x_1(t) = u(t) - t u(t) + (t-1)u(t-1)$$

$$x_1(s) = \frac{1}{s} - \frac{1}{s^2} + \frac{e^{-s}}{s^2}$$

$$F(s) = \frac{x_1(s)}{1 - e^{-sT}}$$

$$F(s) = \frac{\frac{1}{s} - \frac{1}{s^2} + \frac{e^{-s}}{s^2}}{1 - e^{-2s}}$$

$$F(s) = \frac{s(1 + e^{-s}) - 1}{s^2(1 - e^{-2s})}$$

11-11-19

INITIAL VALUE THEOREM:

$$f(0^+) = \lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} [sF(s)]$$

The only restriction is that $f(t)$ must be continuous or at the most a step discontinuity at $t=0$.

PROOF:

We know that, Laplace transform of:

$$L[f'(t)] = sF(s) - f(0^-)$$

Using the standard form of Laplace transform:

$$\int_0^{\infty} f'(t) e^{-st} dt = sF(s) - f(0^-)$$

[Applying $\lim_{s \rightarrow \infty}$ on both sides]

$$\lim_{s \rightarrow \infty} \int_0^{\infty} f'(t) e^{-st} dt = \lim_{s \rightarrow \infty} [sF(s) - f(0^-)]$$

$$0 = \lim_{s \rightarrow \infty} [sF(s) - f(0^-)]$$

(11)

$$\rightarrow \lim_{s \rightarrow 0} [sF(s)] = f(0^-)$$

$$f(0^-) = f(0^+).$$

$$\text{Thus, } \boxed{f(0^+) = \lim_{s \rightarrow 0} [sF(s)] = f(0^-)}$$

(12)

$$\boxed{\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow 0} [sF(s)]}$$

• FINAL VALUE THEOREM: $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$

$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} [sF(s)]$$

PROOF: We know that,

$$L[f'(t)] = sF(s) - f(0^-)$$

$$\int_0^{\infty} f'(t) e^{-st} dt = sF(s) - f(0^-)$$

Applying $\lim_{s \rightarrow 0}$ on both sides.

$$\lim_{s \rightarrow 0} \int_0^{\infty} f'(t) e^{-st} dt = \lim_{s \rightarrow 0} sF(s) - f(0^-)$$

$$\Rightarrow \int_0^{\infty} f'(t) dt = \lim_{s \rightarrow 0} sF(s) - f(0^-)$$

$$f(t) \Big|_0^{\infty} = \lim_{s \rightarrow 0} sF(s) - f(0^-)$$


$$f(\infty) - f(0^+) = \lim_{s \rightarrow 0} sF(s) \cdot f(0^-)$$

$$\boxed{f(\infty) = \lim_{s \rightarrow 0} sF(s)}$$


(2)

$$\boxed{\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)}$$

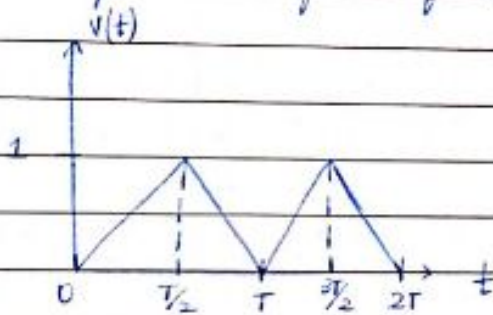1) Find the Laplace Transform of the periodic function



s:

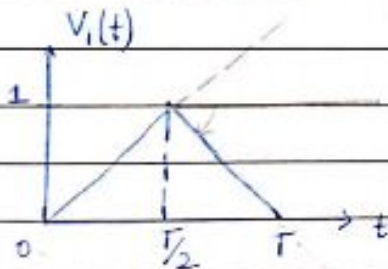

$$v_1(t) = \frac{2}{T} \mathcal{L}(t) - \frac{2}{T} \mathcal{L}(t-T) - \frac{2}{T} \mathcal{L}(t-T) + \frac{2}{T} \mathcal{L}(t-T)$$

$$v_1(t) = \frac{2}{T} \mathcal{L}(t) - \frac{4}{T} \mathcal{L}(t-T) + \frac{2}{T} \mathcal{L}(t-T)$$

$$v_1(s) = \frac{2 \times 1}{T s^2} - \frac{4}{T} \frac{e^{-\frac{T}{2}s}}{s^2} + \frac{2}{T} \frac{e^{-Ts}}{s^2}$$

$$\boxed{v_1(s) = \frac{2}{s^2 T} [1 - 2e^{-\frac{T}{2}s} + e^{-Ts}]}$$

(13)

classmate

Date _____

Page _____

$$F(s) = \frac{V_1/s}{1 - e^{-sT}} \quad [T = T]$$

$$F(s) = \frac{2 [1 - 2e^{-T/2} + e^{-Ts}]}{Ts^2 (1 - e^{-Ts})}$$

2) Find $f(0)$ and $f(\infty)$ for the given Transfer function.

$$F(s) = \frac{s^3 + 7s^2 + 5}{s(s^2 + 3s^2 + 4s + 2)}$$

S:

Using Initial value theorem,

$$f(0) = \lim_{s \rightarrow 0} s F(s)$$

$$f(0) = \lim_{s \rightarrow 0} s \left[\frac{s^3 + 7s^2 + 5}{s(s^2 + 3s^2 + 4s + 2)} \right]$$

$$f(0) = \lim_{s \rightarrow 0} \frac{s^2 [1 + 7/s + 5/s^2]}{s^2 [1 + 3/s + 4/s^2 + 2/s^3]} = \frac{1}{1}$$

$$\Rightarrow \boxed{f(0) = 1}$$

$$f(\infty) = \lim_{s \rightarrow 0} s F(s) \quad [\text{Using Final Value theorem}]$$

$$= \lim_{s \rightarrow 0} s \left[\frac{s^3 + 7s^2 + 5}{s(s^2 + 3s^2 + 4s + 2)} \right]$$

$$= \frac{0 + 0 + 5}{0 + 0 + 0 + 2}$$

$$\boxed{f(\infty) = \frac{5}{2}}$$

3) $F(s) = \frac{s(s+4)(s+8)}{(s+1)(s+6)}$. Find $f(0)$ & $f(\infty)$.

S: Using initial value problem,

$$f(0) = \lim_{s \rightarrow \infty} s F(s)$$

$$= \lim_{s \rightarrow \infty} s \left[\frac{s(s+4)(s+8)}{(s+1)(s+6)} \right]$$

$$= \lim_{s \rightarrow \infty} s^2 \left[\frac{s^2 + 12s + 32}{s^2 + 7s + 6} \right]$$

$$= \lim_{s \rightarrow \infty} \frac{s^2 \left[1 + \frac{12}{s} + \frac{32}{s^2} \right]}{s^2 \left[1 + \frac{7}{s} + \frac{6}{s^2} \right]}$$

$$= \infty \left[\frac{1+0+0}{1+0+0} \right]$$

$$\boxed{f(0) = \infty}$$

$$f(\infty) = \lim_{s \rightarrow 0} s F(s)$$

$$= \lim_{s \rightarrow 0} s \left[\frac{s(s+4)(s+8)}{(s+1)(s+6)} \right]$$

$$\boxed{f(\infty) = 0}$$

4) $F(s) = \frac{(s+2)e^{2s}}{s^2+5}$

$$S: f(0) = \lim_{s \rightarrow \infty} s \left[\frac{(s+2)e^{2s}}{s^2+5} \right]$$

$$= \lim_{s \rightarrow \infty} \frac{s^2 \left[\left(1 + \frac{2}{s}\right) e^{2s} \right]}{s^2 \left[1 + \frac{5}{s^2} \right]}$$

$$= \frac{(1+0)(e^{2(\infty)})}{1+0}$$

$$\boxed{f(0) = \infty}$$


$$f(\infty) = \lim_{s \rightarrow 0} s \left[\frac{(s+2)e^{2s}}{s^2+5} \right]$$

$$= 0 \left[\frac{2e^0}{5} \right]$$

$$\boxed{f(\infty) = 0}$$

15


5) Find the Laplace transform of $f(t)$.

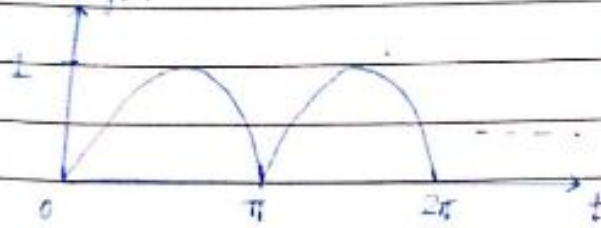

S:

Consider the first cycle.

~~$f(t)$~~ \rightarrow $T = \pi$

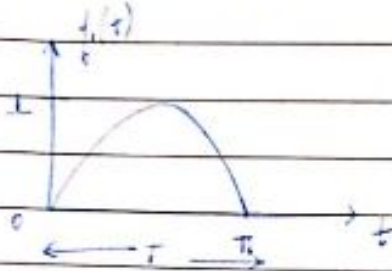

- $\rightarrow f_1(t)$ is made up of two sinusoidal waveforms.
- \rightarrow Consider ~~is~~ a sinusoidal waveform with time period $T = 2\pi$.




$$f_1(t) = \sin(\omega t) u(t)$$

$$\rightarrow \omega = \frac{2\pi}{T} = \frac{2\pi}{2\pi} \Rightarrow \frac{2\pi}{2\pi} \Rightarrow \boxed{\omega = 1} \quad [\because T = 2\pi]$$

$$\rightarrow \boxed{f_1(t) = \sin t \cdot u(t)}$$

Now, it is necessary to cancel the cycles [half cycles] after $T = \pi$

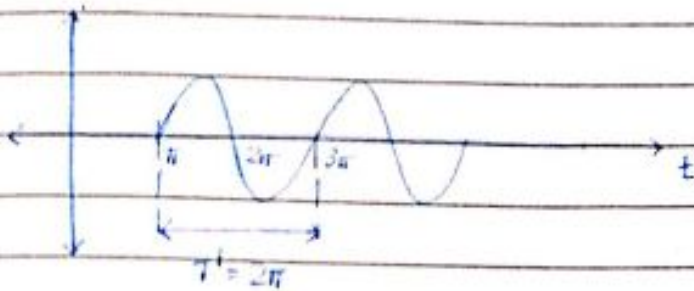So, consider the shifted sine wave with period $T' = 2\pi$.



$$f_2(t) = \sin(t - \pi) u(t - \pi)$$

$$\begin{aligned} \therefore f_1(t) &= f_2(t) + f_3(t) \\ &= \sin t u(t) + \sin(t - \pi) u(t - \pi) \end{aligned}$$

$$\boxed{f_1(s) = \frac{1}{s^2 + 1} + \frac{e^{-\pi s}}{s^2 + 1} \times (1)}$$


$$F(s) = \frac{f_1(s)}{1 - e^{-sT}}$$

$$\boxed{F(s) = \frac{(1 + e^{-\pi s})}{(s^2 + 1)(1 - e^{-\pi s})}}$$


$$\boxed{F(s) = \coth \left(\frac{\pi s}{2} \right) \frac{\pi s}{2}}$$

28-11-19

1)

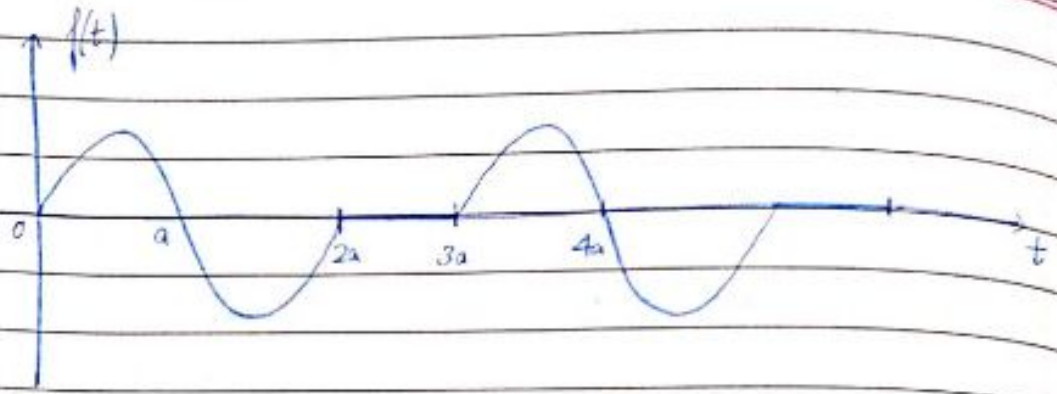

8.

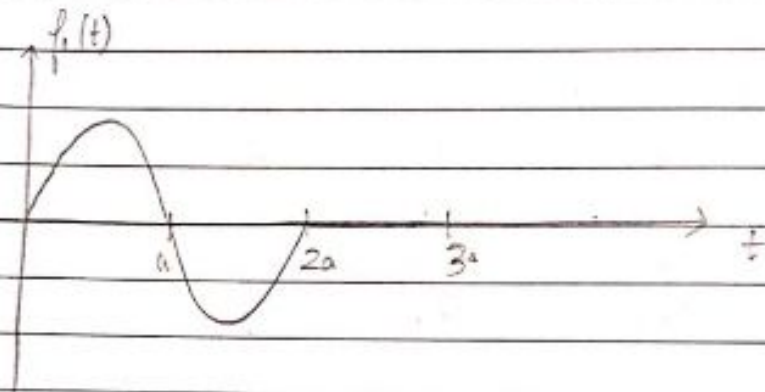

$$f_1(t) = \sin(\omega t) u(t)$$

$$\omega = \frac{2\pi}{T} = \frac{2\pi}{2a}$$

$$f_1(t) = \sin\left(\frac{\pi t}{a}\right) u(t)$$

dead time $\tau = 2a$

$$f_2(t) = -\sin \omega(t-2a) u(t-2a)$$

$$\omega = \frac{2\pi}{T} = \frac{2\pi}{2a}$$

$$f_2(t) = -\sin \frac{\pi(t-2a)}{a} u(t-2a)$$

$$f_3(t) = f_1(t) + f_2(t)$$


$$f_3(t) = \sin\left(\frac{\pi t}{a}\right) u(t) - \sin \frac{\pi(t-2a)}{a} u(t-2a)$$

$$f_3(s) = \frac{\tau/a}{s^2 + (\pi/a)^2} - \frac{e^{-2as}}{s^2 + (\pi/a)^2}$$

$$F_s = \frac{f_3(s)}{1 - e^{-\tau s}} \quad (\tau = 2a)$$

$$V(s) = \frac{f_1(s)}{1 - e^{-3s}}$$

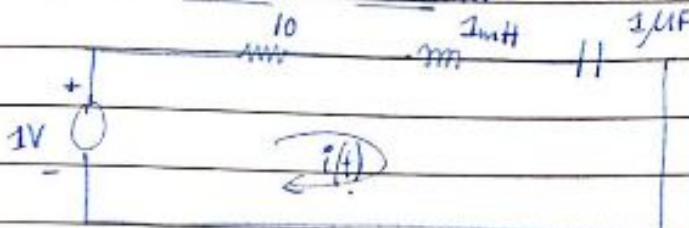2) Using Laplace transform, obtain an expression for current.
Assume zero initial conditions.



8: Applying KVL to the given loop:

$$1 - 10i(t) - L \frac{di(t)}{dt} - \frac{1}{C} \int i(t) dt = 0$$

$$\Rightarrow 1 = 10i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt$$

Applying Laplace:

$$\frac{1}{s} = 10I(s) + L[sI(s) - \cancel{I(0^-)}] + \frac{1}{C} \left[\frac{1}{s} I(s) \right]$$

$$\frac{1}{s} = 10I(s) + LsI(s) + \frac{1}{Cs} I(s)$$

$$\frac{1}{s} = I(s) \left[10 + Ls + \frac{1}{Cs} \right]$$

$$\frac{1}{s} = I(s) \left[\frac{10Cs + Ls^2 + 1}{Cs} \right]$$

$$I(s) = \frac{C}{10Cs + Ls^2 + 1}$$

— x — END — x —